

Sources of Error



EIE 240 Electrical and Electronic Measurement (2/2014)
Class 3, January 30, 2015

Errors in Electrical Measurements

- Systematic error \Rightarrow every times you measure
e.g. loading or insertion of the measurement
instrument
- Meter error \Rightarrow scaling (inaccurate marking),
pointer bending, friction, no calibration
- Random error \Rightarrow temperature effect, noises
(unwanted signals)
- Reading error \Rightarrow parallax, read a wrong scale
- Recording error \Rightarrow for many measured values

2

Background


- Electric charge, $e^- = 1.6 \times 10^{-19}$ Coulombs
- Current, $I = dq/dt$ Coulomb/sec = Amps
- Voltage, the difference in electrical potential between two points (Joules/Coulomb)
- Power, $P = IV$ Watts
- Energy, $E = Pt$ Units (kW·hr)
- Ohm's Law, $V = IR$

3

Background (Cont'd)


- Kirchhoff's Current Law (KCL)

$$I_1 - I_2 - I_3 = 0$$

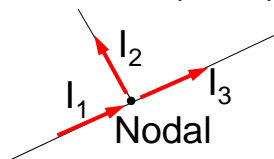

- Kirchhoff's Voltage Law (KVL)


$$-V_1 + I_1 R_1 + V_2 + I_2 R_2 = 0$$

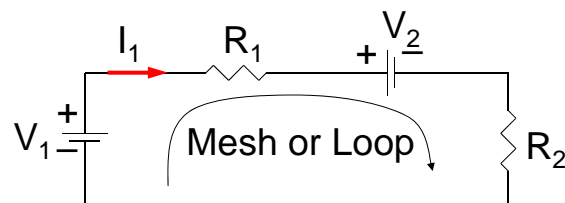


4

Background (Cont'd)

- Thévenin's Theorem

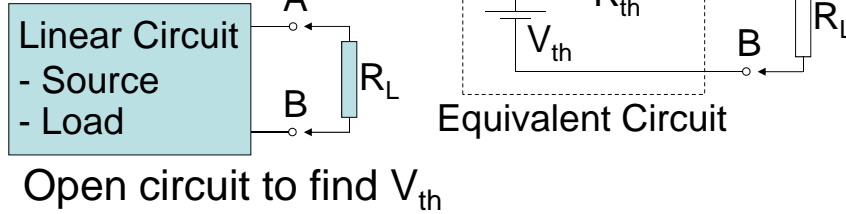

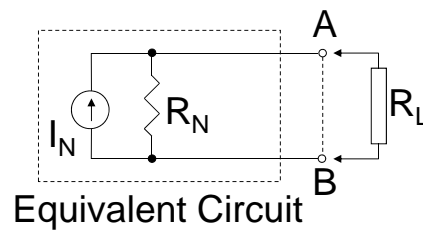- Norton's Theorem
- Short circuit to find I_N




5


Background (Cont'd)

Example

No Load \Rightarrow Equivalent Source

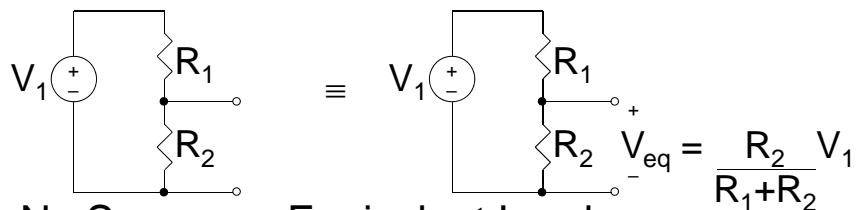



No Source \Rightarrow Equivalent Load

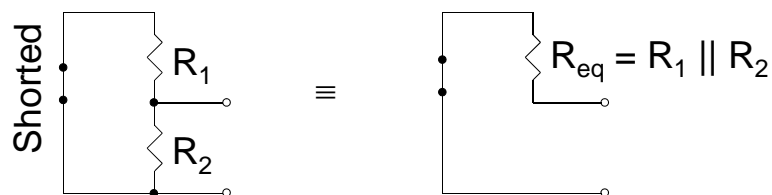

6

Background (Cont'd)

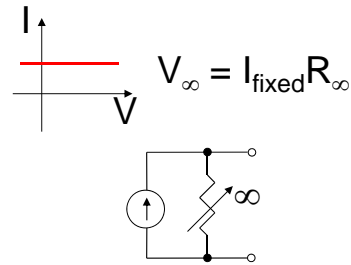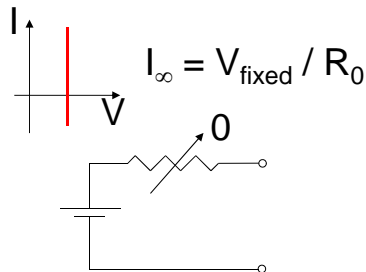- Ideal Voltage Source Vs. Ideal Current Source



- Superposition Theorem (for linear resistive network containing several sources)


Voltage source $\text{---} \oplus \text{---} \Rightarrow$ Short Circuit $\text{---} 0 \text{ V} \text{---}$

Current source $\text{---} \rightarrow \text{---} \Rightarrow$ Open Circuit $\text{---} 0 \text{ A} \text{---}$

Vector summation of the individual voltage or current caused by each separate source 7

Background (Cont'd)


Example

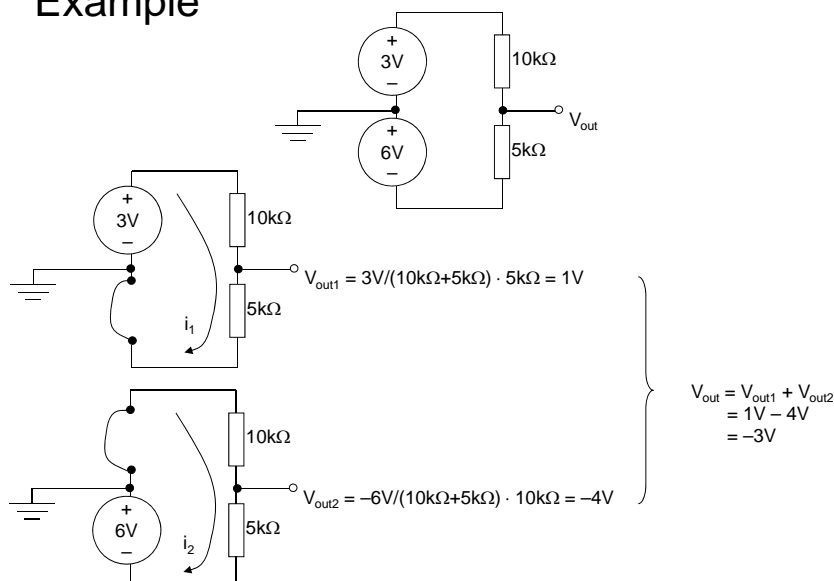

8

Background (Cont'd)

- The Maximum Power Transfer Theorem

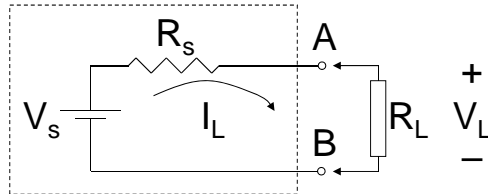


If V_s and R_s are fixed, when $I_L \uparrow$ then $V_L \downarrow$

$$\begin{aligned} P_L &= (I_L)^2 R_L \\ &= (V_s / (R_s + R_L))^2 R_L \\ &= V_s^2 R_L / (R_s + R_L)^2 \\ &= [V_s^2 R_s / (R_s + R_L)^2] (R_L / R_s) \end{aligned}$$

9

Background (Cont'd)

- The Maximum Power Transfer Theorem

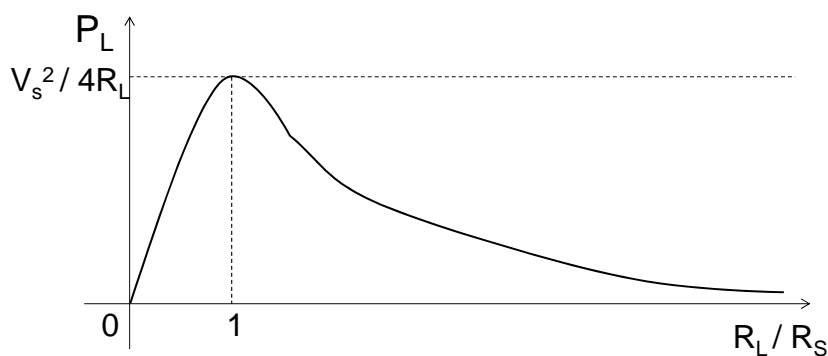


Maximum power is at $R_L = R_s$

Therefore $V_L = V_s / 2$ and $I_L = V_s / 2R_L$

$$P_L = (I_L)^2 R_L = (V_s / 2R_L)^2 R_L = V_s^2 / 4R_L \quad 10$$

Ammeter Loading

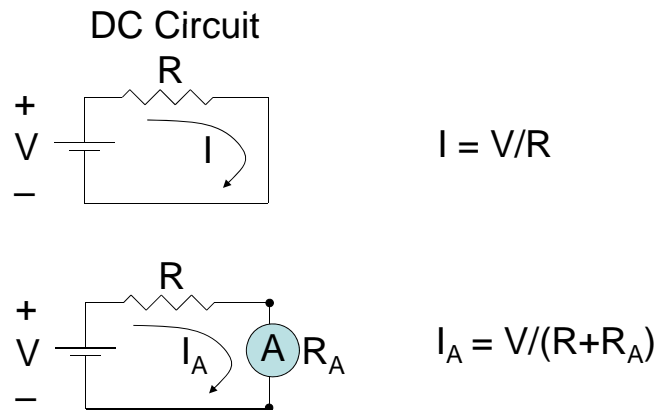For current measurement, open circuit to put an ammeter.



11

Ammeter Loading (Cont'd)

$$\begin{aligned}
 \text{Loading error, } I_A - I &= V/(R+R_A) - V/R \\
 &= \frac{VR - V(R+R_A)}{R(R+R_A)} \\
 &= \frac{-VR_A}{R(R+R_A)}
 \end{aligned}$$

$$\begin{aligned}
 \% \text{ Loading Error} &= (I_A - I)/I \times 100\% \\
 &= \frac{-R_A}{R+R_A} \times 100\%
 \end{aligned}$$

It means if $R_A \uparrow$ then error \uparrow

12

Ammeter Loading (Cont'd)

- Using ammeters connected in series with the circuit being measured, it might not be practical or possible to redesign the meter for a lower input (lead-to-lead) resistance!
- However, we could select a value of shunt resistor to place in the circuit based on voltage drop, and it would be best to choose the lowest practical resistance.

13


Ammeter Loading (Cont'd)

- One ingenious way to reduce the impact that a current-measuring device has on a circuit is to use the circuit wire as part of the ammeter movement itself.
- All current-carrying wires produce a magnetic field, the strength of which is in direct proportion to the strength of the current.
- By building an instrument that measures the strength of that magnetic field, a non-contact ammeter can be produced.

14

Ammeter Loading (Cont'd)

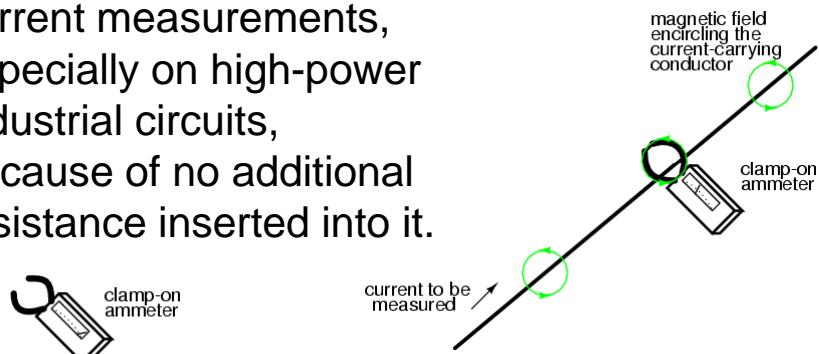
- Ammeters of this design are called "clamp-on" meters because they have "jaws" which can be opened and secured around a circuit wire.
- Clamp-on ammeters make for quick and safe current measurements, especially on high-power industrial circuits, because of no additional resistance inserted into it.



15

Voltmeter Loading

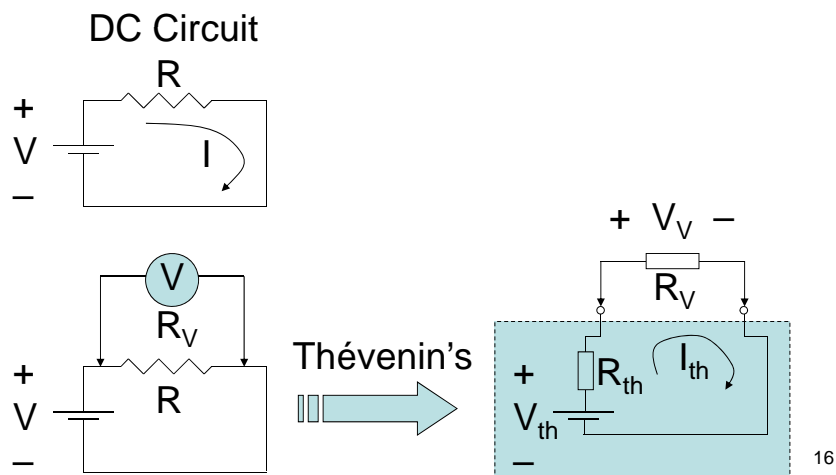For voltage measurement, voltmeter is placed in parallel with the circuit element.



16


Voltmeter Loading (Cont'd)

$$I_{th} = V_{th} / (R_{th} + R_V)$$

$$V_V = I_{th} R_V = V_{th} R_V / (R_{th} + R_V) \quad , \text{ Voltage Divider}$$

$$(V_V / V_{th}) = R_V / (R_{th} + R_V)$$
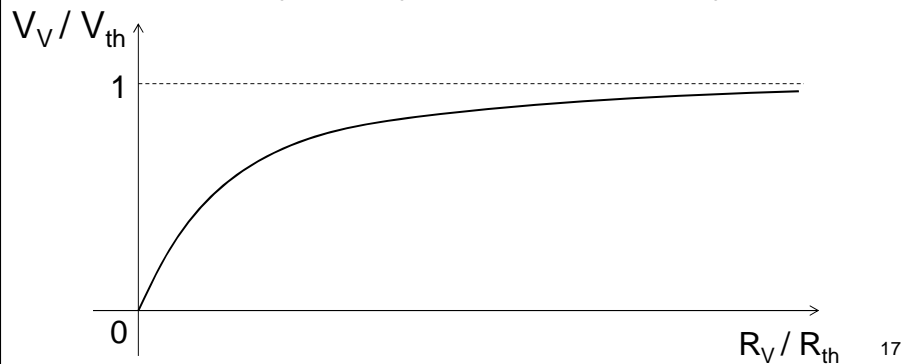
$$= [R_{th} / (R_{th} + R_V)] (R_V / R_{th})$$



Voltmeter Loading (Cont'd)

$$\text{Error} = V_V - V_{th}$$

$$= \left(\frac{R_V}{R_{th} + R_V} - 1 \right) V_{th}$$

$$\% \text{ Error} = (V_V - V_{th}) / V_{th} \times 100\%$$


$$= \frac{-R_{th}}{R_{th} + R_V} \times 100\%$$

It means if $R_V \uparrow$ then error \downarrow

18

Ohmmeter Loading

Using a circuit within the instrument

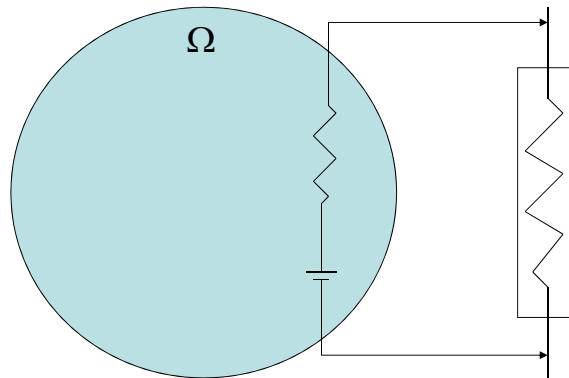

19

Analog Ammeters & Voltmeters

- The users have to read the meter manual to find the basic accuracy specifications.
- Moving-coil-based analog meters are characterized by their full-scale deflection (f.s.d.) and effective resistance of the meters (few Ω - $k\Omega$)
- Typical meters produce a f.s.d. current of $50\ \mu\text{A}$ - $1\ \text{mA}$ (this is not the ranges of the meters)



20

Percentage of FSD


- The accuracy of analog ammeters and voltmeters are quoted as a percentage of the full-scale deflection of pointer on the linear scale for all reading on the selected range.
- e.g. an ammeter having accuracy $\pm 2\%$ f.s.d. within the range 0-10 A,
Relative error $\Rightarrow \pm 2\%$ of 10 A
Absolute error $\Rightarrow \pm 0.2$ A
- When a measured value is close to full scale, or at least above $2/3$ of full scale, the published accuracy is meaningful.



21

Percentage of Midscale

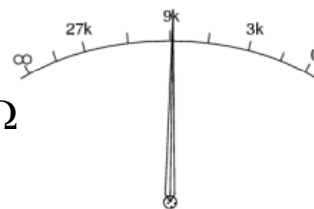- Moving-coil-based ohmmeters is characterized by their midscale deflection of the pointer on nonlinear scale.
- What figure lies exactly between infinity and zero?
- e.g. $\pm 3\%$ of midscale
Relative error $\Rightarrow \pm 3\%$ of 9 k Ω
Absolute error $\Rightarrow \pm 0.27$ k Ω



22

Percentage of DMM Reading

- In the case of digital instruments, the accuracy is generally quoted as \pm the percentage of the reading ± 1 digit.
- e.g. $\pm 0.5\%$ Reading ± 1 Digit
when you read a voltage 1.2 V with a digit of 0.03 V (depending on the range selected)
error = $\pm 0.5\%$ of 1.2 V ± 0.03 V
= ± 0.036 V \Rightarrow absolute error
= $\pm 3\%$ of reading \Rightarrow relative error

23


Potential Meter

- Before the moving coil meter, potentiometer was used in measuring the voltage in a circuit
- Calculated from a fraction of a known voltage (on resistive slide wire)
- Based on voltage divider (linearly)
- By means of a galvanometer (no deflection or null-balance)



24

Calibration of Potentiometer

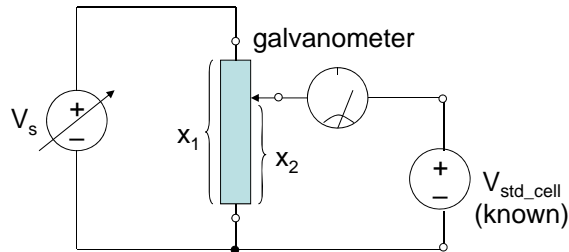

- The end of a uniform resistance wire is at x_1
- The sliding contact or wiper is then adjusted to x_2
- The standard electrochemical cell whose E.M.F. is known (e.g. 1.0183 volts for Weston cell)


25

Calibration of Potentiometer (Cont'd)

- Adjust supply voltage V_s until the galvanometer shows zero (voltage on R_2 equals to the standard cell voltage or no current flows through the galvanometer)
- $$\frac{x_2}{x_1} V_s = V_{std_cell}$$
$$V_s = \frac{x_1}{x_2} V_{std_cell}$$

26

Measuring of Potentiometer

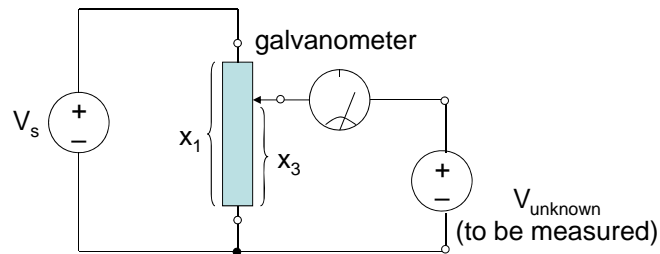

- Slide the wiper (change x_3) until the galvanometer shows zero again
- $$V_{\text{unknown}} = \frac{x_3}{x_1} V_s$$
$$= \frac{x_3}{x_2} V_{\text{std_cell}}$$

27

Rheostat

- Variable resistor with two terminals






28

Loading for a Potentiometer



Resistor

- Fixed
- Adjustable Potentiometer

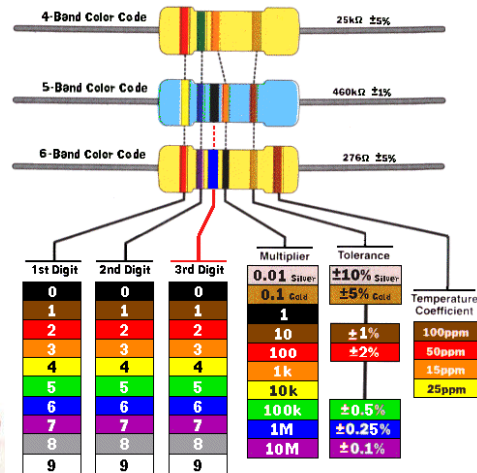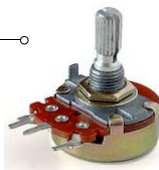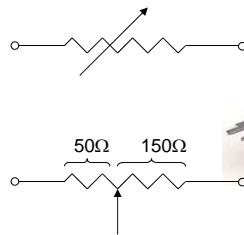


29

Loading of a Potentiometer (Cont'd)

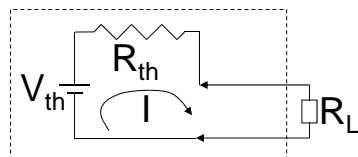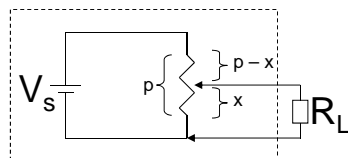

Thévenin's

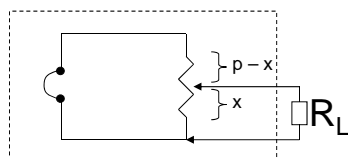

Superposition

Voltage Divider

$$V_{th} = (x/p) V_s$$

$$\frac{1}{R_{th}} = \frac{1}{(x/p)R_p} + \frac{1}{((p-x)/p)R_p}$$

$$R_{th} = (x/p)R_p(1 - x/p)$$

30

Loading of a Potentiometer (Cont'd)

$$\begin{aligned}
 V_{th} &= I (R_{th} + R_L) \\
 (x/p)V_s &= I [(x/p)(1 - x/p)R_p + R_L] \\
 I &= \frac{(x/p)V_s}{(x/p)(1 - x/p)R_p + R_L} \\
 V_L = IR_L &= \frac{(x/p)V_s R_L}{(x/p)(1 - x/p)R_p + R_L} \\
 &= \frac{(x/p)V_s}{(R_p/R_L)(x/p)(1 - x/p) + 1}
 \end{aligned}$$

It means the relationship between V_L and x is nonlinear!

31

Loading of a Potentiometer (Cont'd)

Error,

$$\begin{aligned}
 V_{th} - V_L &= (x/p)V_s \left[1 - \frac{1}{(R_p/R_L)(x/p)(1 - x/p) + 1} \right] \\
 &= (x/p)V_s \left[\frac{(R_p/R_L)(x/p)(1 - x/p)}{(R_p/R_L)(x/p)(1 - x/p) + 1} \right]
 \end{aligned}$$

If $R_L \gg R_p$ then $R_p/R_L \approx 0$

Error $\approx (x/p)V_s(R_p/R_L)(x/p)(1 - x/p)$

$\approx V_s(R_p/R_L)[(x/p)^2 - (x/p)^3]$, $R_L \uparrow$ error \downarrow

% Error $\approx (R_p/R_L)[(x/p) - (x/p)^2] \times 100\%$

32

Loading of a Potentiometer (Cont'd)

$$\text{Let } d(\text{Error})/dx = V_s(R_p/R_L)[2x/p^2 - 3x^2/p^3] = 0$$

$$\text{We get } 2x/p^2 = 3x^2/p^3$$

$$x/p = 2/3 \quad \text{for the maximum}$$

Therefore,

$$\begin{aligned} \text{the max error} &= V_s(R_p/R_L)[(2/3)^2 - (2/3)^3] \\ &\approx 0.148 V_s(R_p/R_L) \end{aligned}$$

and the max % error $\approx 22.2 (R_p/R_L) \%$

33


Potentiometric Voltage Measurement

- One ingenious solution to the problem of voltmeter loading is that of the *potentiometric* or *null-balance* instrument.
- In a potentiometric instrument, a precision adjustable voltage source is compared against the measured voltage, and a sensitive device called a *null detector* is used to indicate when the two voltages are equal.

34


Potentiometric Voltage Measurement (Cont'd)

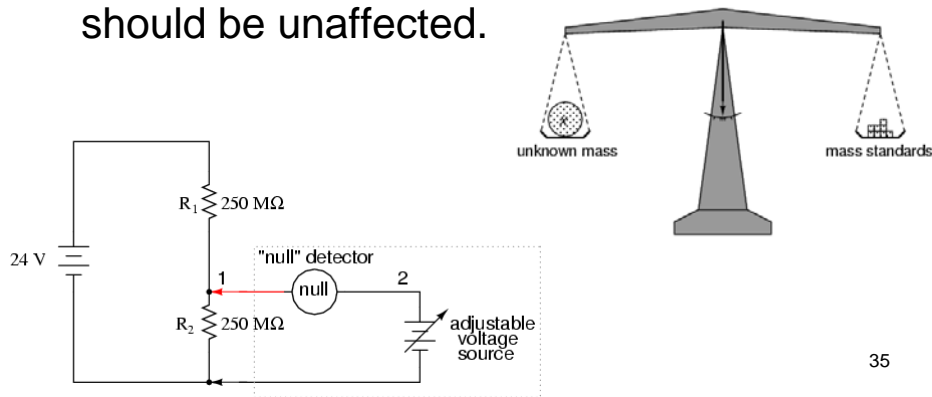- When the voltages are equal, there will be zero current drawn from the circuit under test, and thus the measured voltage should be unaffected.



Null Detector

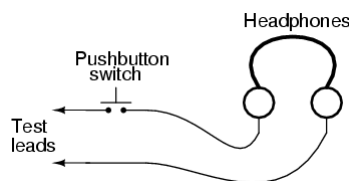- An extremely simple type of sensitive null detector is a set of audio headphones.
- When a DC voltage is initially applied to a speaker, the resulting current through it will move the speaker cone and produce an audible "click."
- Another "click" sound will be heard when the DC source is disconnected.



Reference

- <http://en.wikipedia.org/wiki/Potentiometer>
- http://www.allaboutcircuits.com/vol_1/chpt_8/5.html
- http://www.allaboutcircuits.com/vol_1/chpt_8/3.html