

ชื่อ.....รหัสนักศึกษา.....เลขที่นั่งสอบ.....



Seat No.

**King Mongkut's University of Technology Thonburi**

**Midterm Examination for Semester 1/2559**

**Friday 23nd September 2016**

**TIME 09:00-12:00**

**CPE221 Circuits and Electronics for Computer Engineers**

**Computer Engineer Student 2<sup>nd</sup> Year**

**Directions**

1. There are 6 Questions in 5 pages (include this page) for 100 points
2. Do all questions
3. Fill Student name, student ID in every Page
4. Calculator is allowed
5. Do not permit any note, book into exam room
6. Do not bring exam sheet out of exam room


**Kraikron Settakraikron**

**This exam has already verified by Computer Engineering Department**

**(Assoc.Prof.Dr.Natasha Dejdumrong)**


**President of Curriculum**

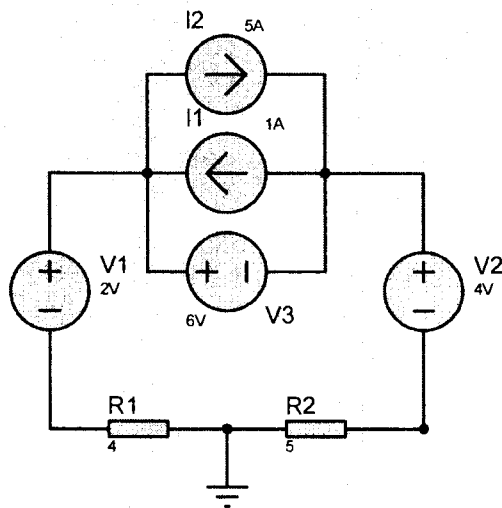1. Find  $I_1$  that supplied by  $V_1$  (15)




2. From Q1 find  $I_2$  that supplied by  $V_2$  using SuperPosition (15)

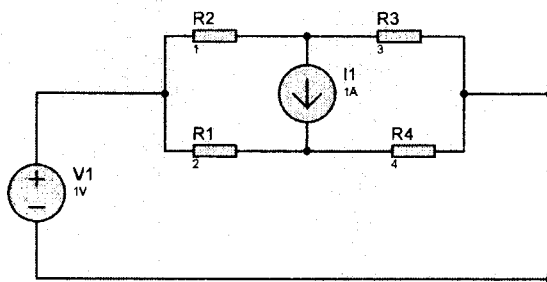
3. Find  $V_{th}$  and  $R_{th}$  for Thevenin Equivalent Circuit (15)




4. Find  $V_{out}$  (20)


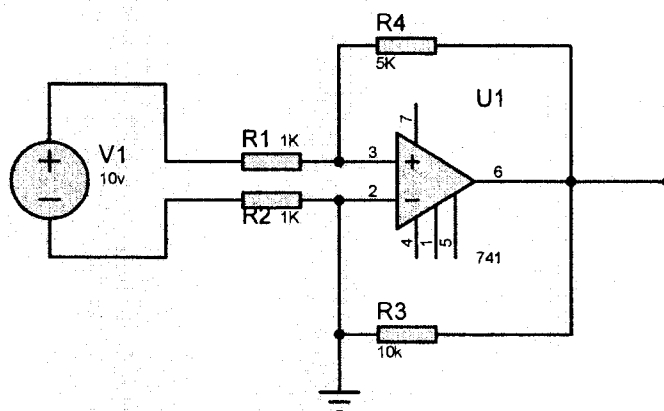


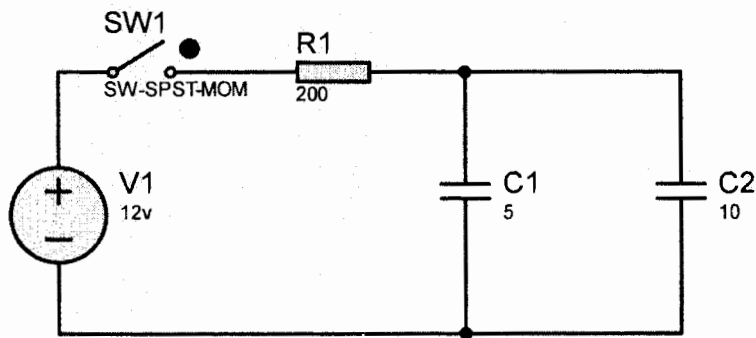5. Power on at  $t=0$ , Find Completed current  $I_{C1}$  that pass-through  $C1$  (20)



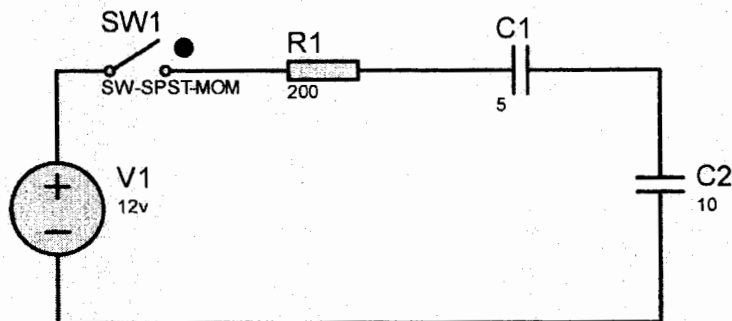- 6) Power on at  $t=0$ , Find Completed Voltage across  $C2$  (20)



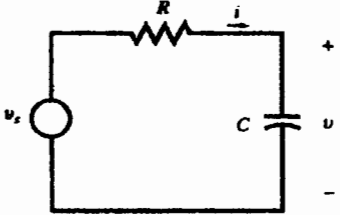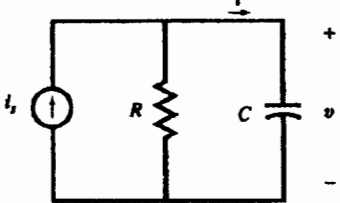RC circuit	Unit Step Response	Unit Impulse Response
	$v_s = u(t)$ $\begin{cases} v = (1 - e^{-t/RC})u(t) \\ i = (1/R)e^{-t/RC}u(t) \end{cases}$	$v_s = \delta(t)$ $\begin{cases} h_v = (1/RC)e^{-t/RC}u(t) \\ h_i = -(1/R^2C)e^{-t/RC}u(t) + (1/R)\delta(t) \end{cases}$
	$i_s = u(t)$ $\begin{cases} v = R(1 - e^{-t/RC})u(t) \\ i = e^{-t/RC}u(t) \end{cases}$	$i_s = \delta(t)$ $\begin{cases} h_v = (1/C)e^{-t/RC}u(t) \\ h_i = -(1/RC)e^{-t/RC}u(t) + \delta(t) \end{cases}$