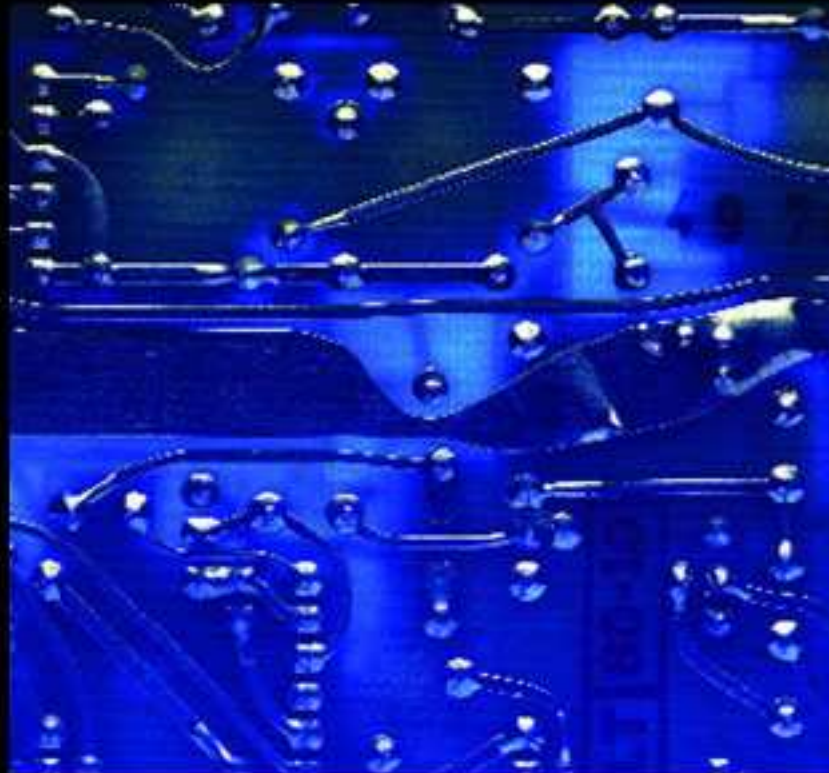


# ELECTRONIC DEVICES AND CIRCUIT THEORY

TENTH EDITION

BOYLESTAD



PEARSON

## Chapter 14 Feedback and Oscillator Circuits

# Feedback Concepts


The effects of negative feedback on an amplifier:

## Disadvantage

- **Lower gain**
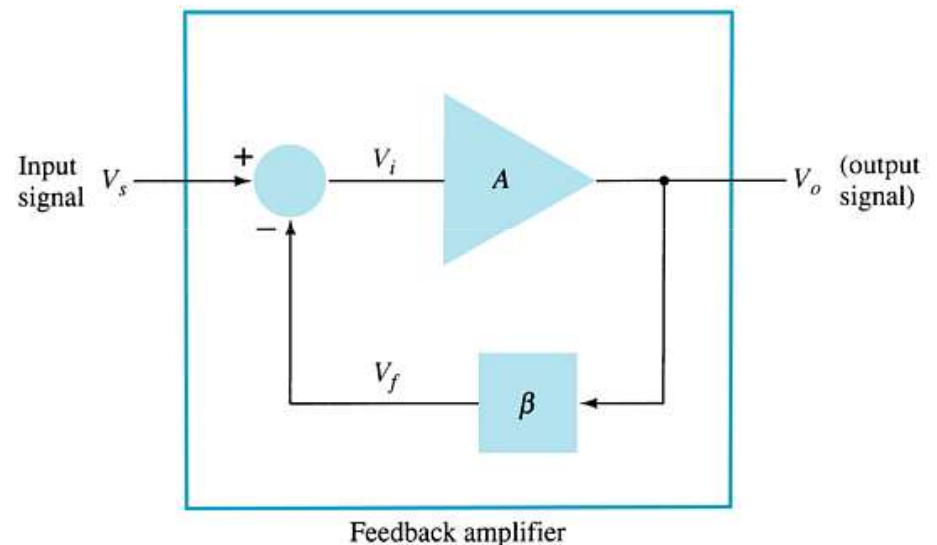
## Advantages

- **Higher input impedance**
- **More stable gain**
- **Improved frequency response**
- **Lower output impedance**
- **Reduced noise**
- **More linear operation**



# Feedback Connection Types


- **Voltage-series feedback**
- **Voltage-shunt feedback**
- **Current-series feedback**
- **Current-shunt feedback**

# Voltage-Series Feedback

For voltage-series feedback, the output voltage is fed back in series to the input.


The feedback gain is given by:
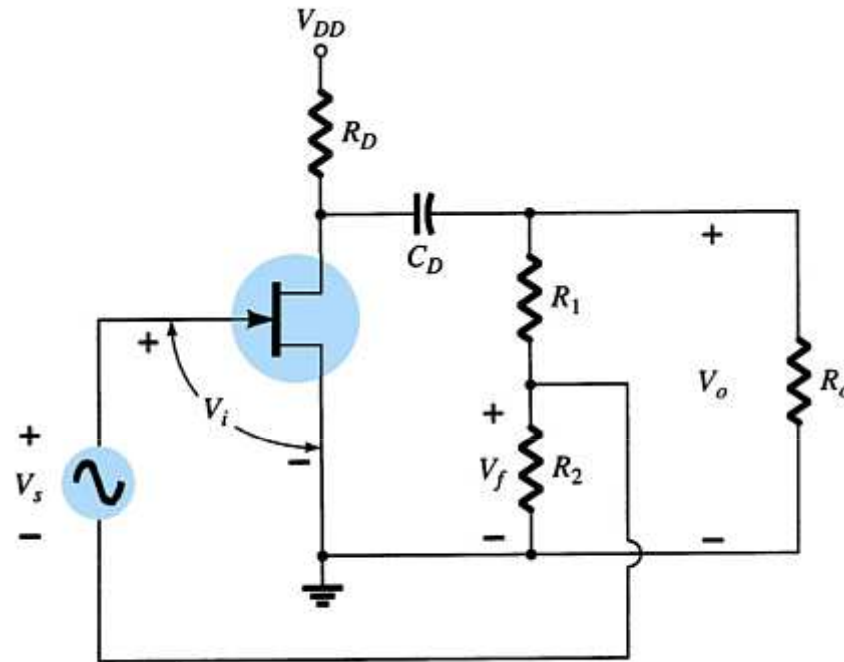
$$A_f \cong \frac{1}{\beta} = \frac{R_1 + R_2}{R_2}$$



# Voltage-Shunt Feedback

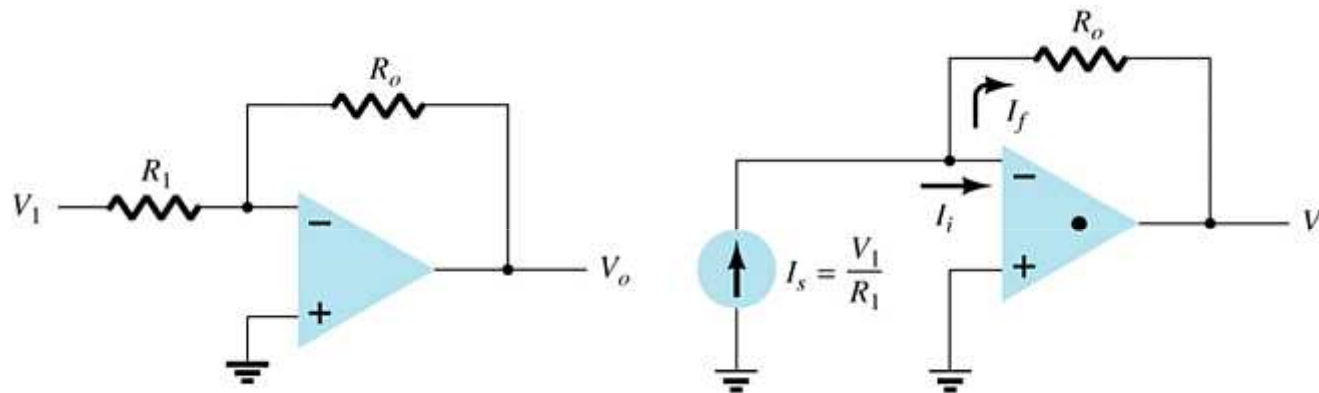**For a voltage-shunt feedback amplifier, the output voltage is fed back in parallel with the input.**




**The feedback gain is given by**

$$A_f = -\frac{R_o}{R_i}$$
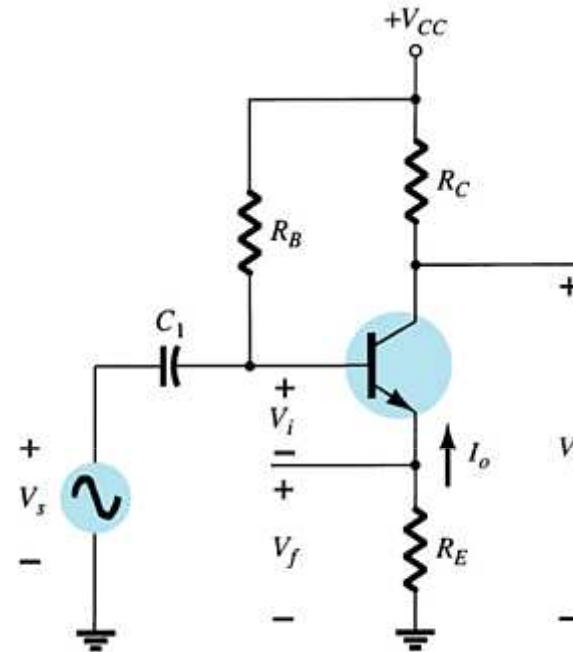
# Current-Series Feedback

For a current-series feedback amplifier, a portion of the output current is fed back in series with the input.



To determine the feedback gain:


$$A_f = \frac{I_o}{V_s} = \frac{A}{1 + \beta A} = \frac{-h_{fe}/h_{ie}}{1 + (-R_E)\left(\frac{-h_{fe}}{h_{ie} + R_E}\right)} \cong \frac{-h_{fe}}{h_{ie} + h_{fe}R_E}$$

# Current-Shunt Feedback

For a current-shunt feedback amplifier, a portion of the output current is directed back in parallel with the input.

The feedback gain is given by:

$$A_f = \frac{I_o}{I_s}$$

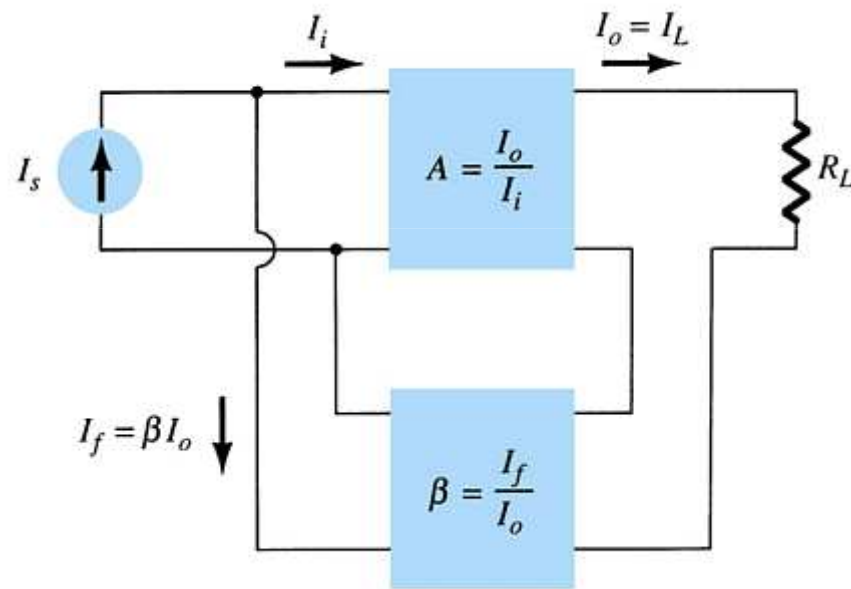

# Summary of Feedback Effects

Summary of Gain, Feedback, and Gain with Feedback					
		Voltage-Series	Voltage-Shunt	Current-Series	Current
<i>Shunt</i>					
Gain without feedback	$A$	$\frac{V_o}{V_i}$	$\frac{V_o}{I_i}$	$\frac{I_o}{V_i}$	$\frac{I_o}{I_i}$
Feedback	$b$	$\frac{V_f}{V_o}$	$\frac{I_f}{V_o}$	$\frac{V_f}{I_o}$	$\frac{I_f}{I_o}$
	$A_f$	$\frac{V_o}{V_s}$	$\frac{V_o}{I_s}$	$\frac{I_o}{V_s}$	$\frac{I_o}{I_s}$

Effect of Feedback Connection on Input and Output Impedance			
Voltage-Series	Current-Series	Voltage-Shunt	Current-Shunt
$Z_{if} = Z_i (1 + \beta A)$ (increased)	$Z_i (1 + \beta A)$ (increased)	$\frac{Z_i}{1 + \beta A}$ (decreased)	$\frac{Z_i}{1 + \beta A}$ (decreased)
$Z_{of} = \frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)



# Frequency Distortion with Feedback


- **If the feedback network is purely resistive, then the gain with feedback will be less dependent on frequency variations. In some cases the resistive feedback removes all dependence on frequency variations.**
- **If the feedback includes frequency dependent components (capacitors and inductors), then the frequency response of the amplifier will be affected.**

# Noise and Nonlinear Distortion

- **The feedback network reduces noise by cancellation. The phase of the feedback signal is often opposite the phase of the input signal.**
- **Nonlinear distortion is also reduced simply because the gain is reduced. The amplifier is operating in midrange and not at the extremes.**

# Bandwidth with Feedback

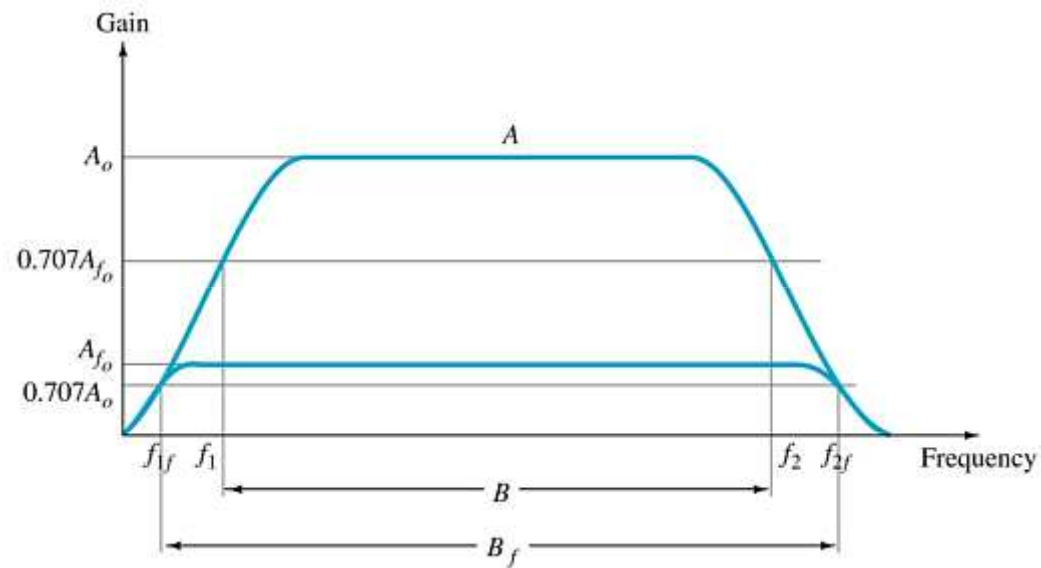**Feedback increases the bandwidth of an amplifier.**




# Gain Stability with Feedback

**Gain calculations with feedback are often based on external resistive elements in the circuit. By removing gain calculations from internal variations of  $\beta$  and  $g_m$ , the gain becomes more stable.**

# Phase and Frequency Considerations

**At higher frequencies the feedback signal may no longer be out of phase with the input. The feedback is thus positive and the amplifier, itself, becomes unstable and begins to**

# Oscillator Operation

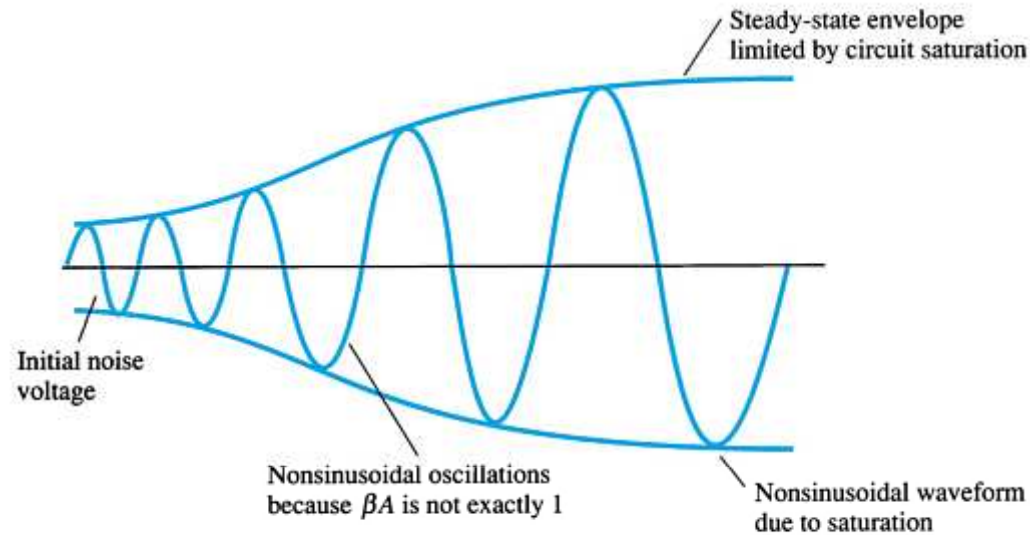

**The feedback signal must be positive.**

**If the feedback signal is not positive or the gain is less than one, the oscillations dampens out.**

**The overall gain must equal one (unity gain).**

**If the overall gain is greater than one, the oscillator eventually saturates.**

# Types of Oscillator Circuits

**Phase-shift oscillator**  
**Wien bridge oscillator**  
**Tuned oscillator circuits**  
**Crystal oscillators**  
**Unijunction oscillator**


# Phase-Shift Oscillator

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity.

The RC networks provide the necessary phase shift for a positive feedback.

The values of the RC components also determine the frequency of oscillation:

$$f = \frac{1}{2\pi RC\sqrt{6}}$$

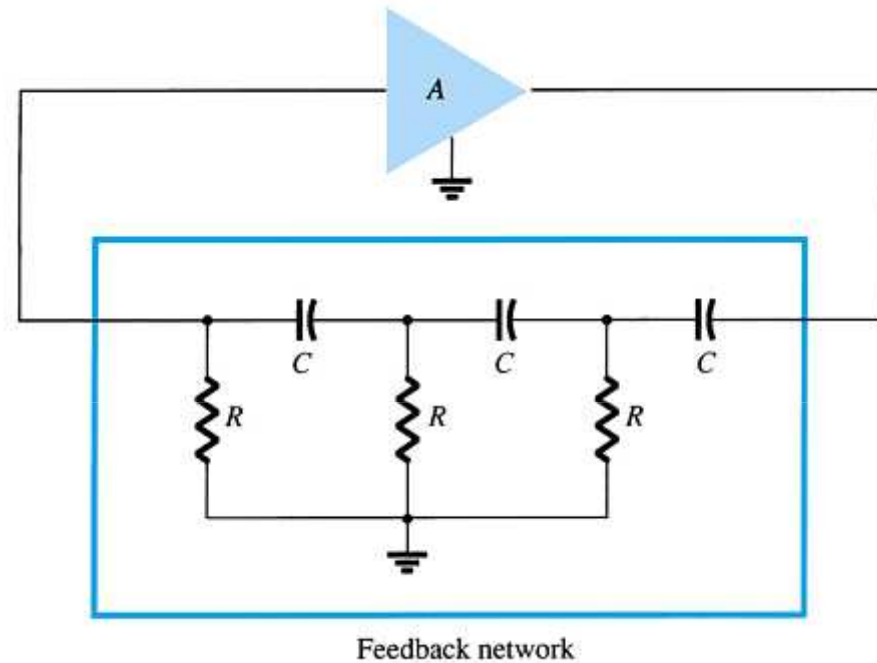

[more...](#)




# Phase-Shift Oscillator

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity.

The RC networks provide the necessary phase shift for a positive feedback.

The values of the RC components also determine the frequency of oscillation:


$$f = \frac{1}{2\pi\sqrt{6}RC}$$

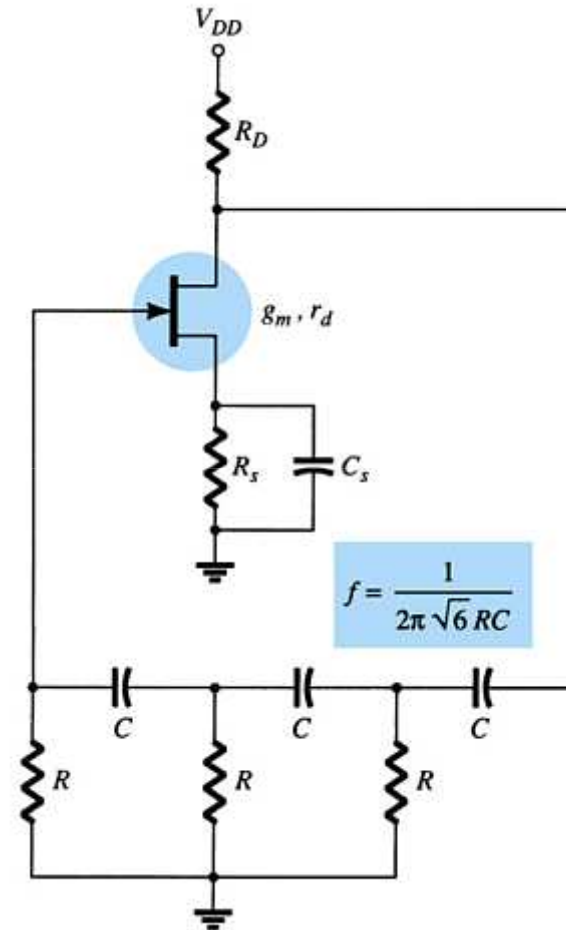
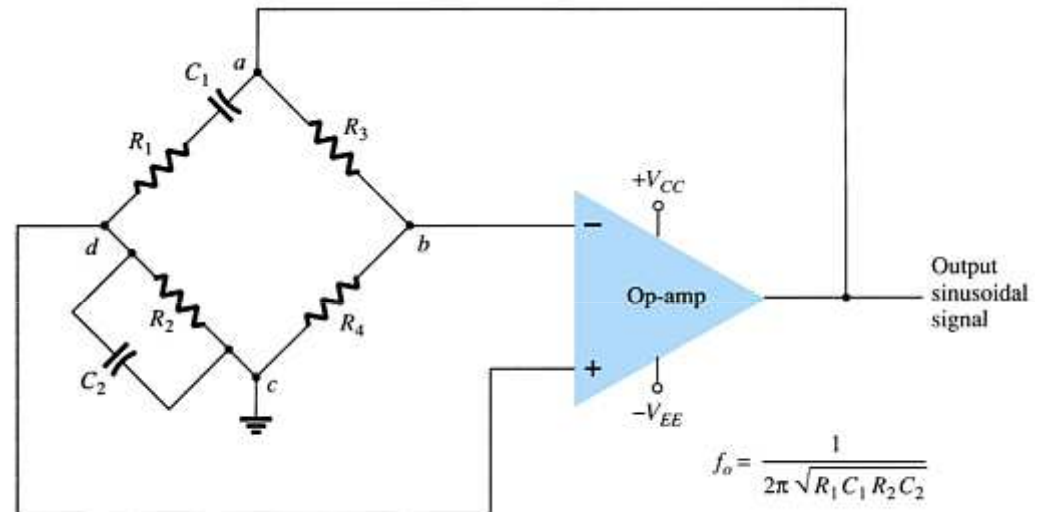
# Wien Bridge Oscillator

The amplifier must supply enough gain to compensate for losses. The overall gain must be unity.

- The feedback resistors are  $R_3$  and  $R_4$ .
- The phase-shift components are  $R_1$ ,  $C_1$  and  $R_2$ ,  $C_2$ .



# Tuned Oscillator Circuits

**Tuned oscillators use a parallel LC resonant circuit (LC tank) to provide the oscillations.**

**There are two common types:**

**Colpitts**—The resonant circuit is an inductor and two capacitors.

**Hartley**—The resonant circuit is a tapped inductor or two inductors and one capacitor.


# Colpitts Oscillator Circuit

The frequency of oscillation is determined by:

$$f_o = \frac{1}{2\pi\sqrt{LC_{eq}}}$$

where:

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

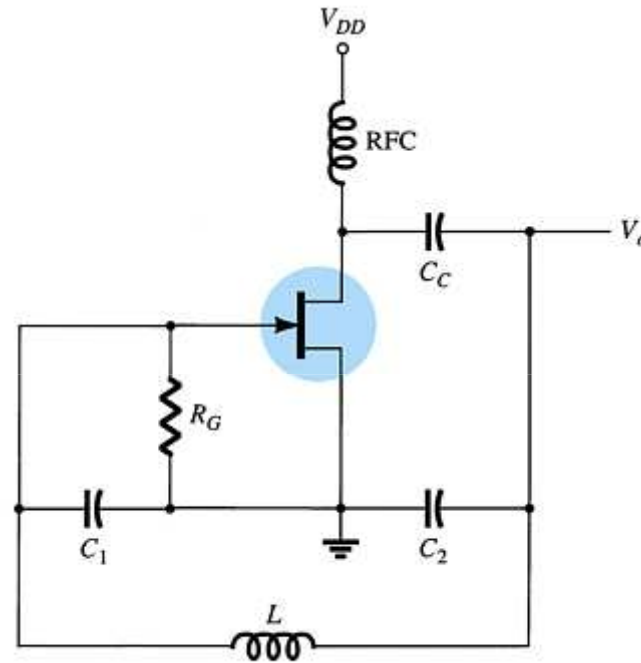


# Hartley Oscillator Circuit

The frequency of oscillation is determined by:

$$f_o = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

where:

$$L_{eq} = L_1 + L_2 + 2M$$

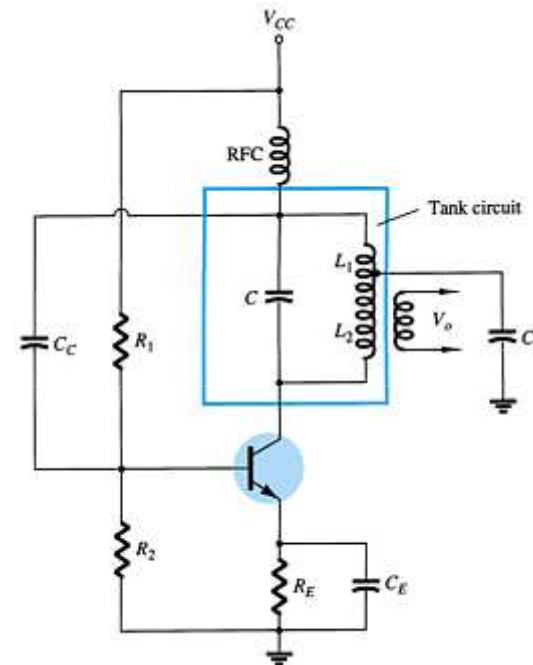

# Crystal Oscillators

The crystal appears as a resonant circuit.

The crystal has two resonant frequencies:


## Series resonant condition

- RLC determine the resonant frequency
- The crystal has a low impedance
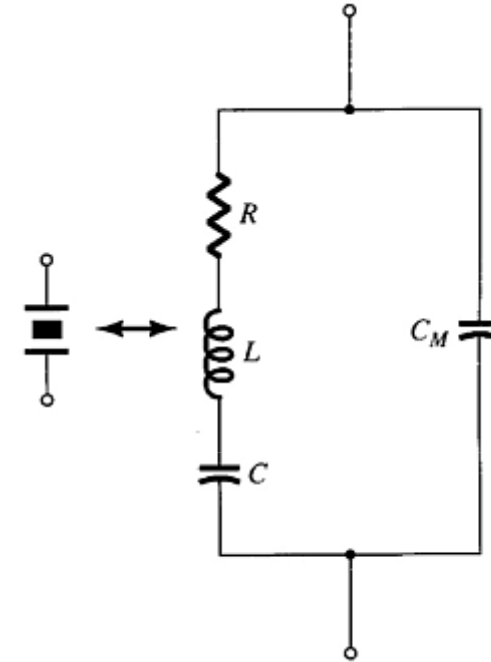
## Parallel resonant condition



- RL and  $C_M$  determine the resonant frequency
- The crystal has a high impedance

The series and parallel resonant frequencies are very close, within 1% of each other.



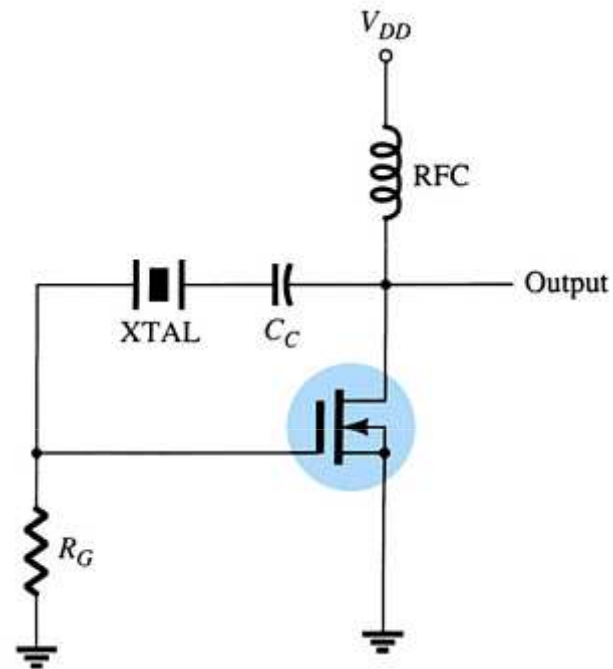
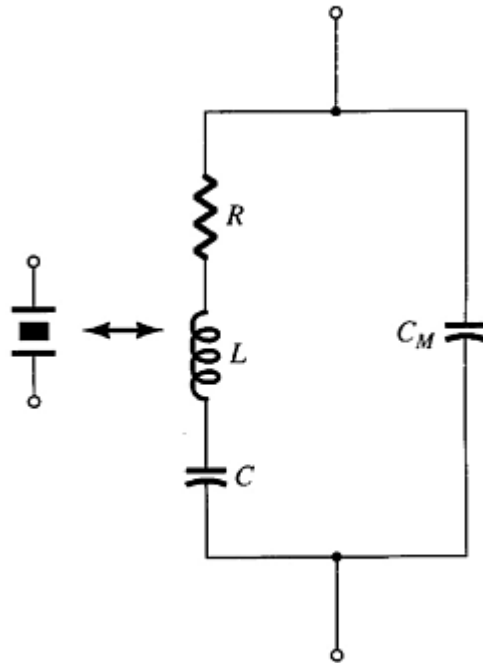
# Series Resonant Crystal Oscillator

- RLC determine the resonant frequency
- The crystal has a low impedance


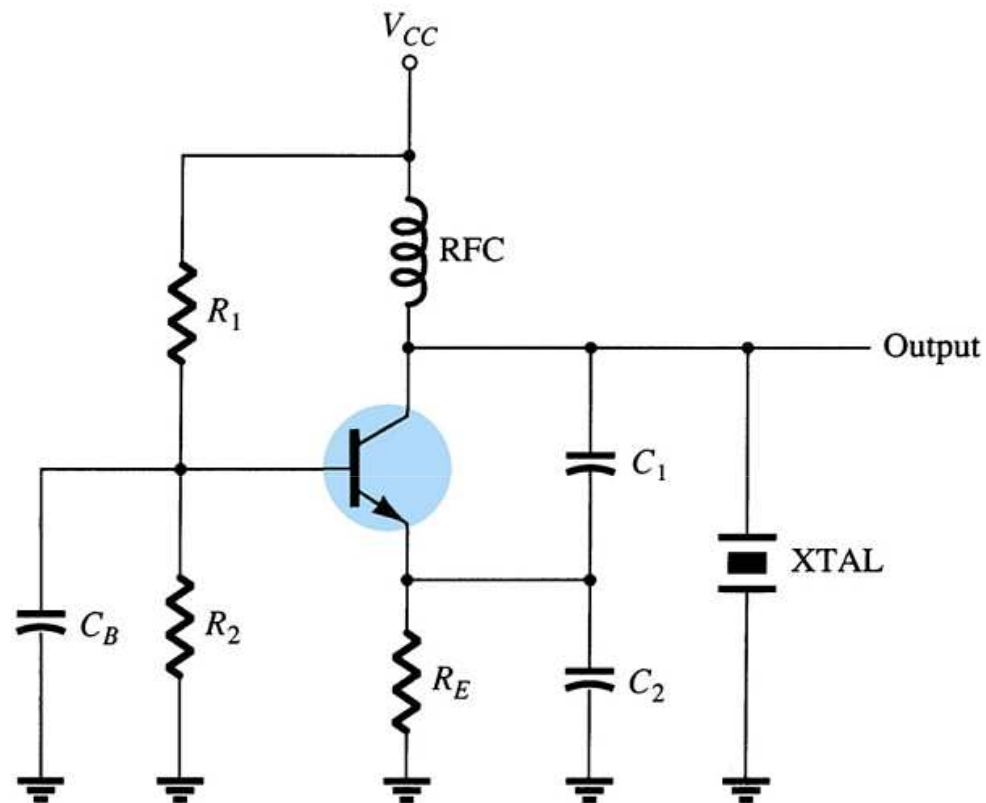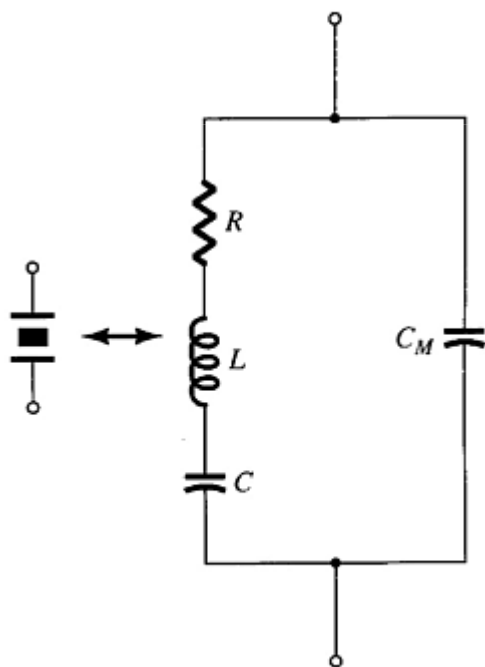
# Parallel Resonant Crystal Oscillator

- $R_L$  and  $C_M$  determine the resonant frequency
- The crystal has a high impedance






# Unijunction Oscillator

The output frequency is determined by:

$$f_o = \frac{1}{R_T C_T \ln[1/(1 - \eta)]}$$

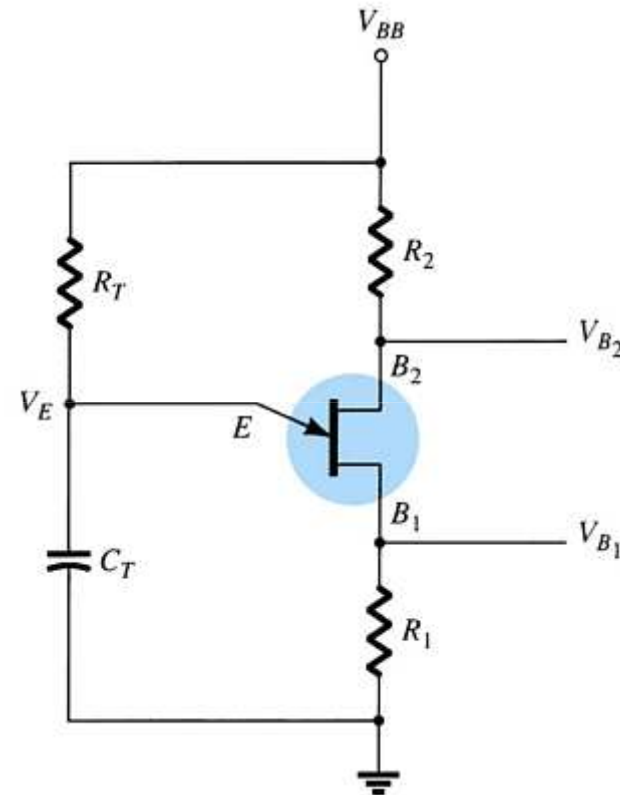Where  $\eta$  is a rating of the unijunction transistor with values between 0.4 and 0.6.



# Unijunction Oscillator Waveforms

The unijunction oscillator (or relaxation oscillator) produces a sawtooth waveform.

