

---

ENE 104

# Electric Circuit Theory

---



## Lecture 06: Basic RL and RC Circuits

---

**Week #6 : Dejwoot KHAWPARISUTH**

office: CB40906 Tel: 02-470-9065


Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

- **time constants** for RL and RC circuits
- the **natural** and **forced response**
- the **total response**
- the effect of **initial conditions** on circuit response
- **RL** and **RC** circuit response

- A **natural** response
- A **transient** response
- A **forced** response

# The Source-Free RL Circuit:

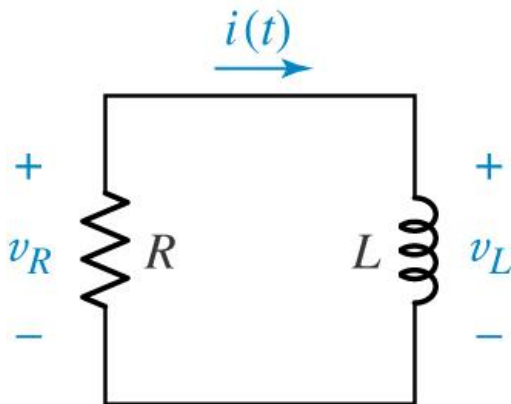

A series RL circuit for which  $i(t)$  is to be determined, subject to the initial condition that  $i(0) = I_0$ .

$$Ri + v_L = Ri + L \frac{di}{dt}$$

$$\frac{di}{dt} + \frac{R}{L}i = 0$$


$$\frac{di}{i} = -\frac{R}{L}dt$$

$$\int_{t_0}^{i(t)} \frac{di'}{i'} = \int_0^t -\frac{R}{L}dt'$$

$$\ln i - \ln I_0 = -\frac{R}{L}(t - 0)$$

$$\text{so } \boxed{i(t) = I_0 e^{-Rt/L}}$$

# The Source-Free RL Circuit:

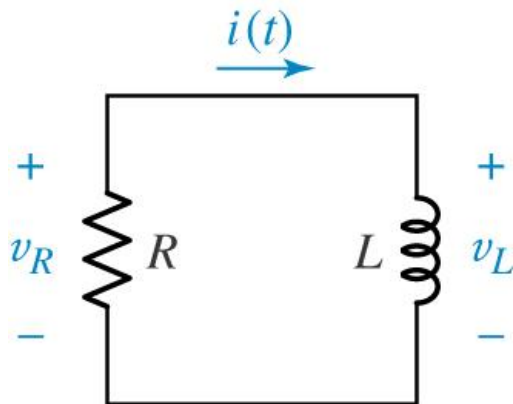

A series RL circuit for which  $i(t)$  is to be determined, subject to the initial condition that  $i(0) = I_0$ .

$$i(t) = I_0 e^{-Rt/L}$$


The power:  $p_R = i^2 R = I_0^2 R \cdot e^{\frac{-2Rt}{L}}$

The total energy: 
$$w_R = \int_0^{\infty} p_R dt = I_0^2 R \int_0^{\infty} e^{\frac{-2Rt}{L}} dt$$



$$= I_0^2 R \left( \frac{-L}{2R} \right) e^{\frac{-2Rt}{L}} \bigg|_0^{\infty} = \frac{1}{2} L I_0^2$$
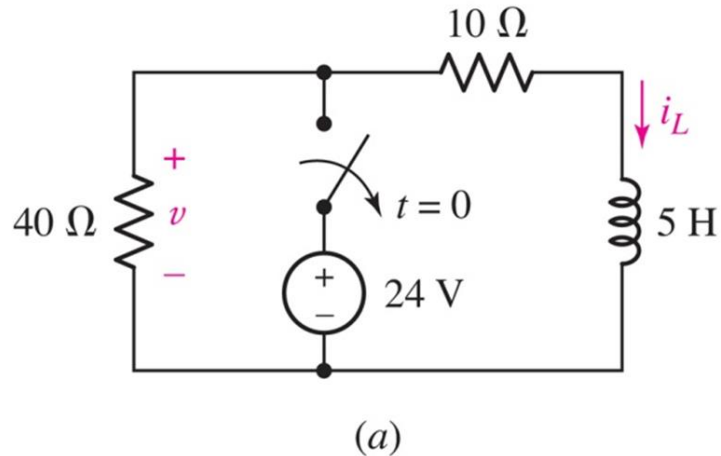
# Example 8.1:

find the current through the 5-H inductor at  $t = 200\text{ms}$




$$i_L(t) = I_0 e^{\frac{-Rt}{L}}$$

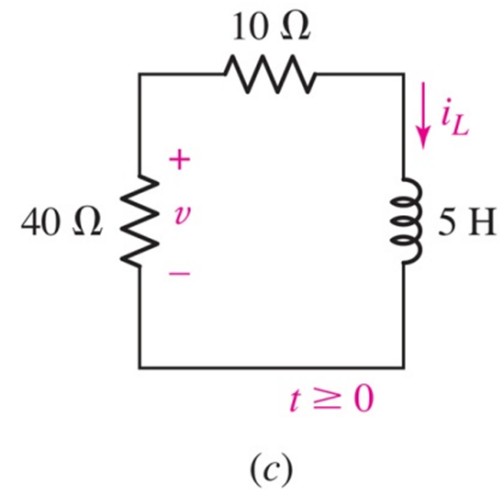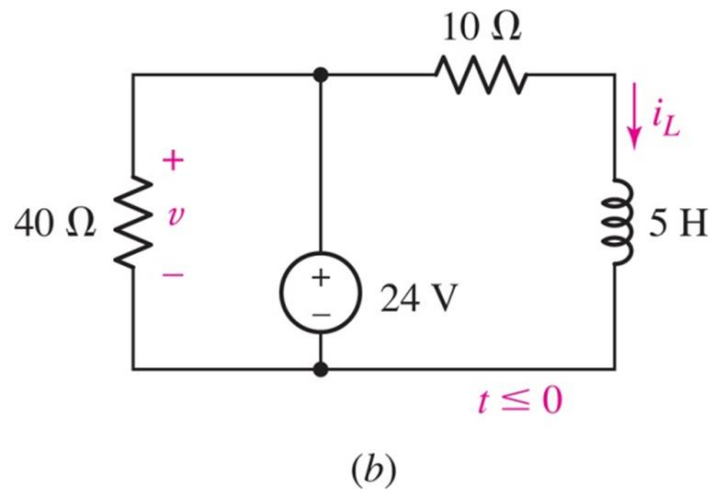
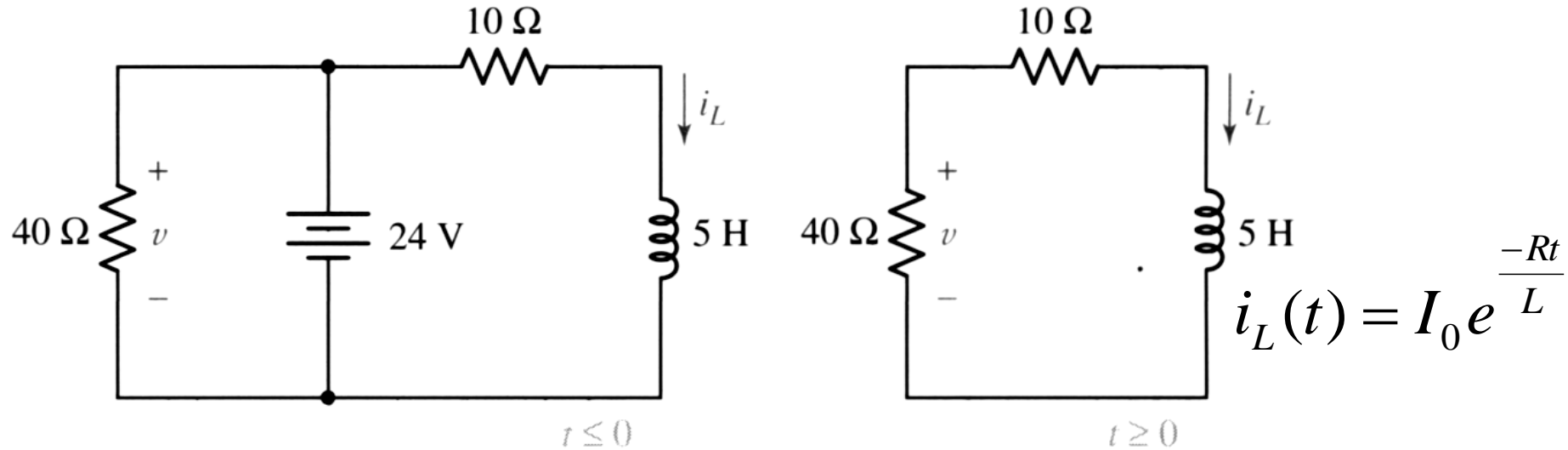
# Example :

find the current through the 5-H inductor at  $t = 200\text{ms}$




$$I_0 = \frac{24}{10} = 2.4$$

$$i_L(t = 200\text{ms.}) = 2.4e^{-10t} = 324.8\text{mA.}$$
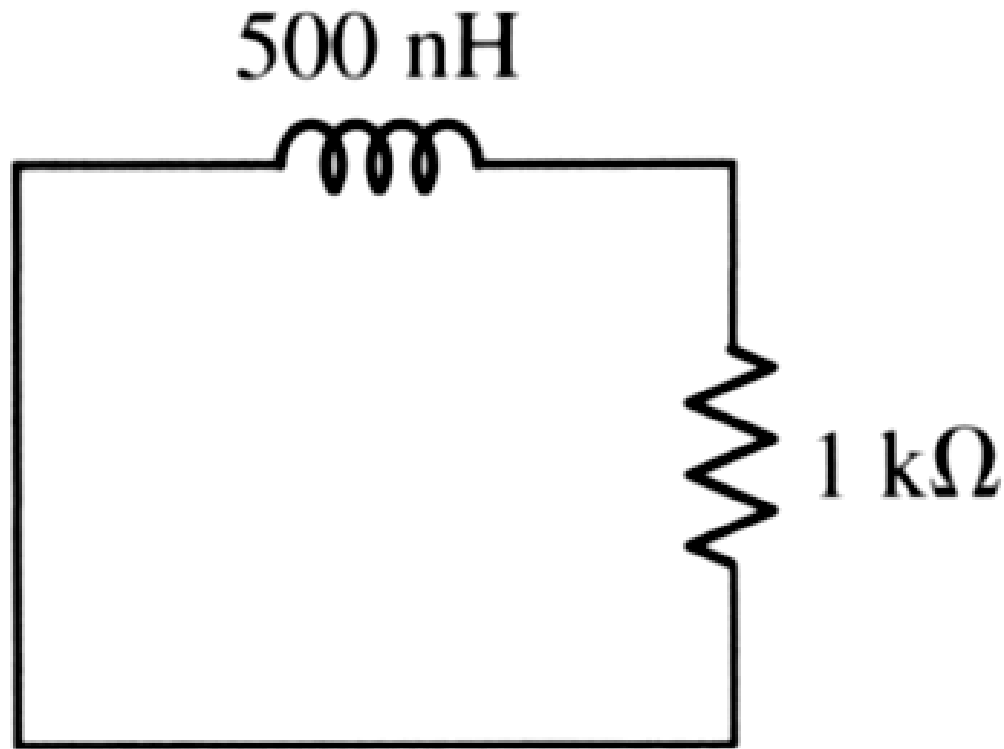
# Practice: 8.1

---


Determine the energy remaining in the inductor at  $t = 2 \text{ ns}$  if it is initially storing  $7 \text{ } \mu\text{J}$




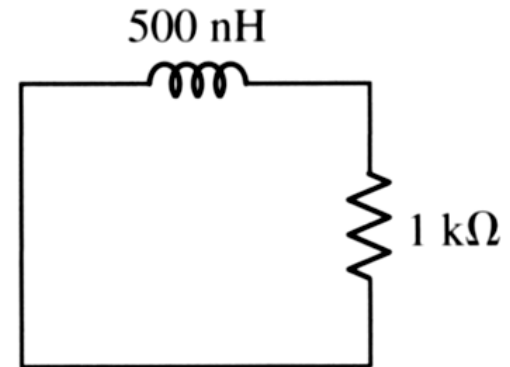
# Practice: 8.1

7  $\mu\text{J}$  stored in a 500 nH inductor



a current magnitude =  $\sqrt{\frac{2 \times 7 \times 10^{-6}}{500 \times 10^{-9}}} = 5.292 \text{ A}$


$$i(t) = I_o e^{-t/\tau} \text{ where } \tau = \frac{L}{R} = \frac{500 \times 10^{-9}}{1000} = 500 \text{ ps}$$

$$i(2 \text{ ns}) = 5.292 \exp\left(\frac{-2 \times 10^{-9}}{500 \times 10^{-12}}\right) = 96.93 \text{ mA}$$

$$w(2 \text{ ns}) = \frac{1}{2} L i^2 = 0.5(500 \times 10^{-9})(96.93 \times 10^{-3})^2$$

# Properties of the Exponential resp: Page 10

$$i_L(t) = I_0 e^{\frac{-Rt}{L}}$$

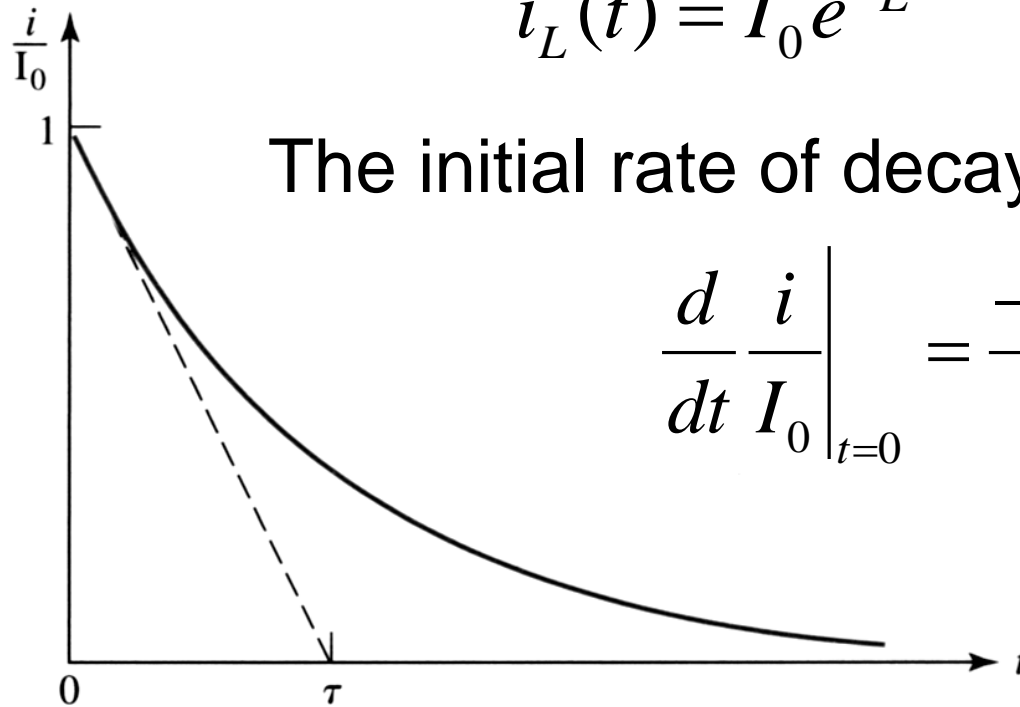

The initial rate of decay:


$$\left. \frac{d}{dt} \frac{i}{I_0} \right|_{t=0} = \frac{-R}{L} e^{\frac{-Rt}{L}} \bigg|_{t=0} = \frac{-R}{L}$$

$$\tau = \frac{L}{R}$$

$$\frac{i(\tau)}{I_0} = e^{-1} = 0.3679 \quad \text{or} \quad i(\tau) = 0.3679 I_0$$

# Properties of the Exponential resp: Page 11

---

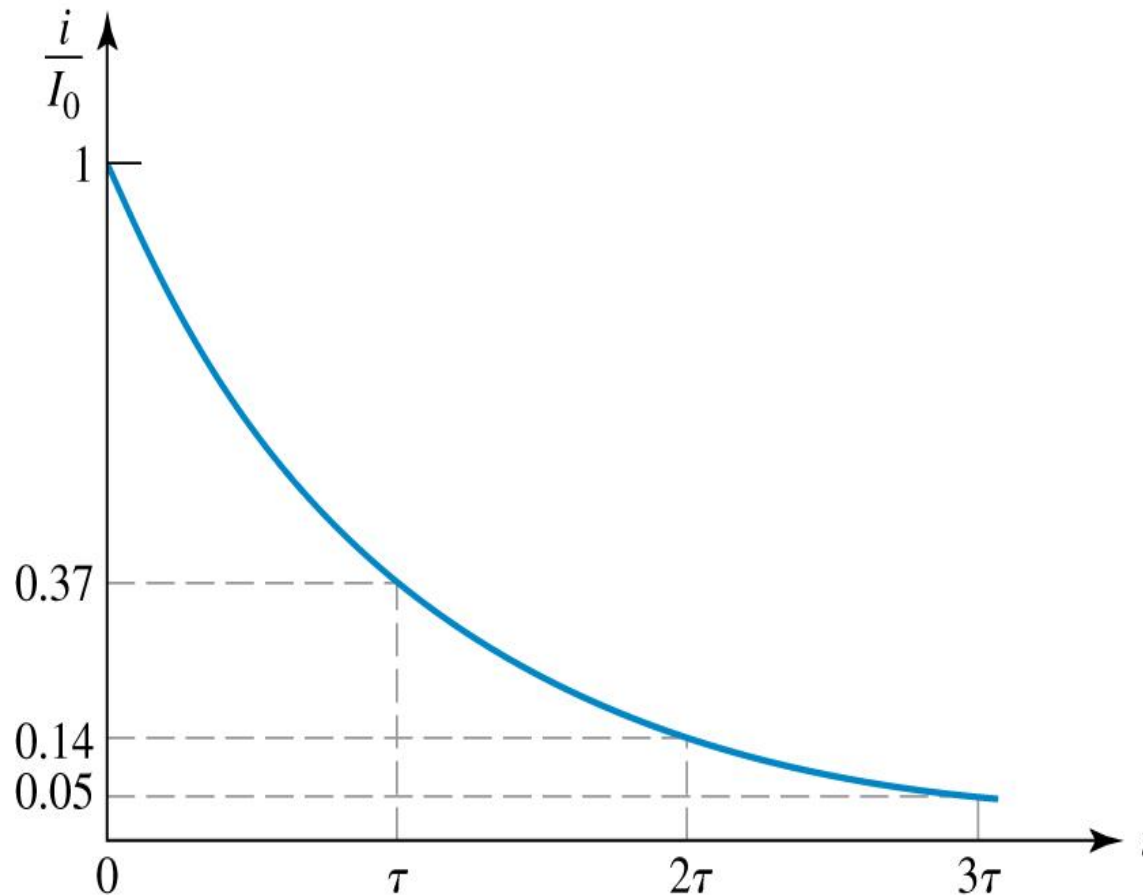

**A plot of the exponential response versus time.**

# Practice: 8.2

---

In a source-free series RL circuit, find the numerical value of the ratio: (a)  $i(2\tau)/i(\tau)$ , (b)  $i(0.5\tau)/i(0)$ , and (c)  $t/\tau$  if

$\frac{i(t)}{i(0)} = 0.2$ ; (d)  $t/\tau$  if  $i(0) - i(t) = i(0)\ln 2$ .

$$i(t) = I_o e^{-t/\tau}$$


$$i(0) = I_o$$

$$\frac{i(2\tau)}{i(\tau)} = \frac{e^{-2}}{e^{-1}} =$$

$$\frac{i(0.5\tau)}{i(0)} = e^{-0.5} =$$

$$\frac{i(t)}{i(0)} = e^{-t/\tau} = 0.2, \text{ so } \frac{t}{\tau} = -\ln 0.2 =$$

# The Source-Free RC Circuit:

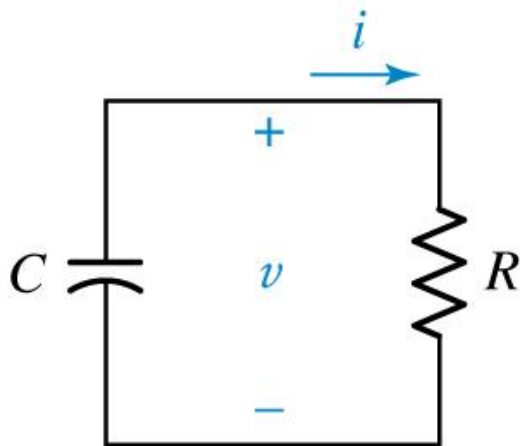

A parallel RC circuit for which  $v(t)$  is to be determined, subject to the initial condition that  $v(0) = V_0$ .


$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

$$\frac{dv}{dt} + \frac{v}{RC} = 0$$

$$\rightarrow v(t) = v(0)e^{\frac{-t}{RC}} = V_0 e^{\frac{-t}{RC}}$$


# The Source-Free RC Circuit:

---

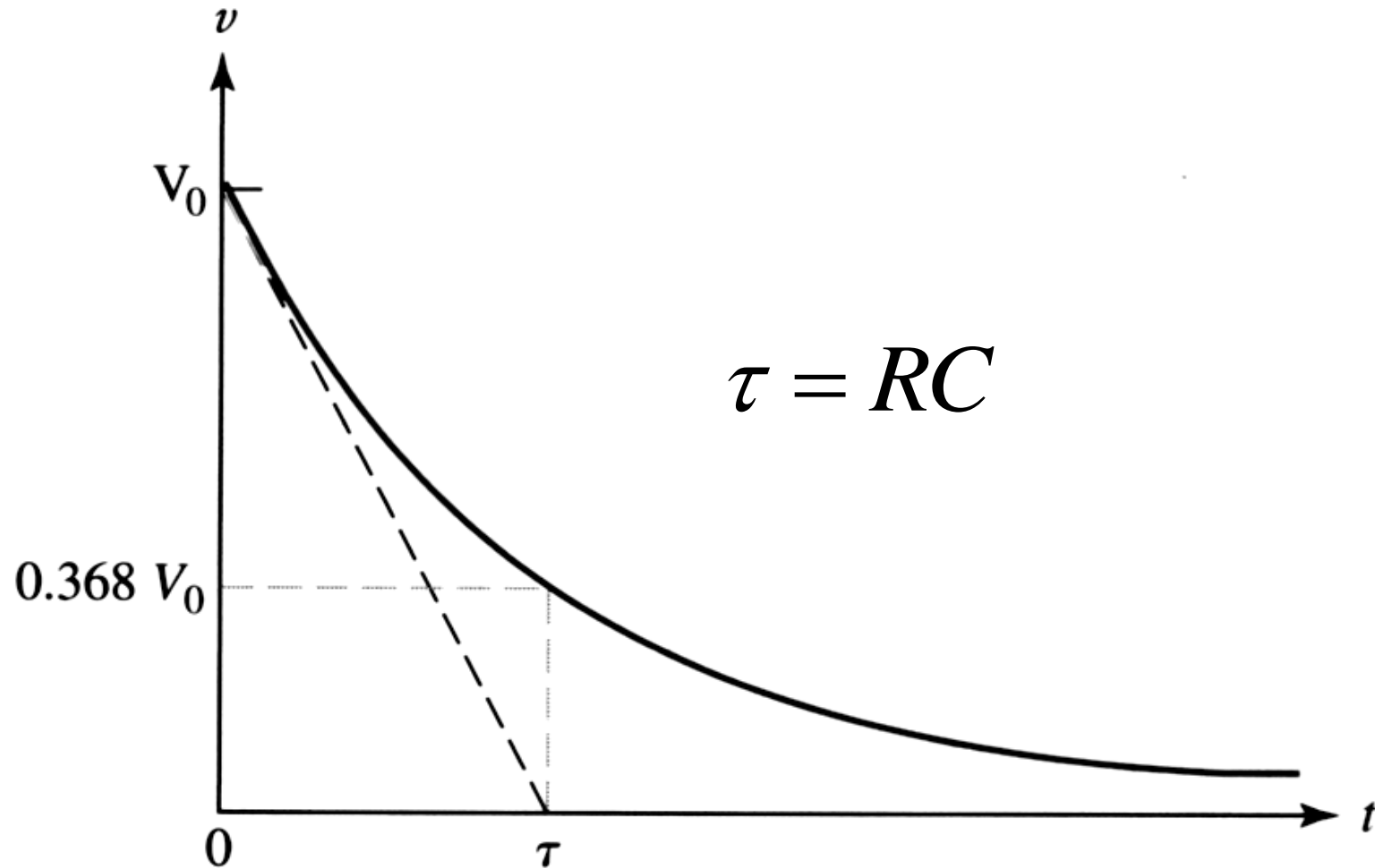


# Practice: 8.3

Find  $v(0)$  and  $v(2ms)$

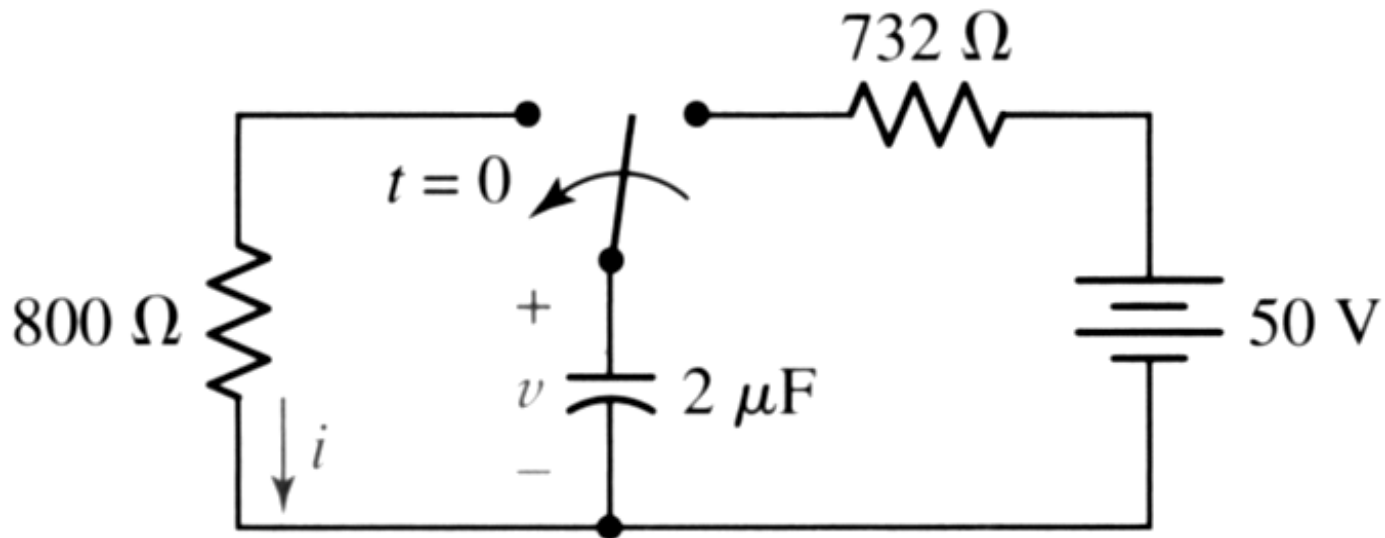

## Practice: 8.3

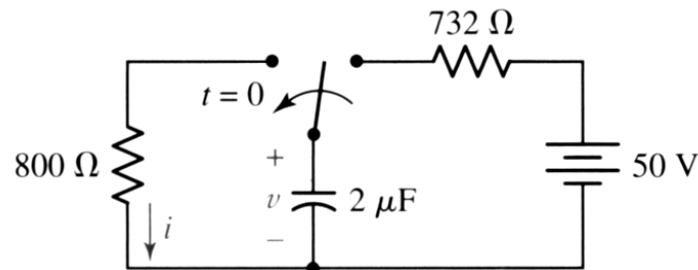

With no current flow permitted through the capacitor (it is assumed any transients have long since died out),  $v = 50$  V.

After the switch is thrown, the only remaining circuit is a simple source-free RC circuit.


$$\tau = RC = 1.6 \text{ ms}$$

$$v(t) = v(0) e^{-t/\tau} \quad \text{so} \quad v(2\text{ms}) = 50 \exp\left(\frac{-2 \times 10^{-3}}{1.6 \times 10^{-3}}\right)$$


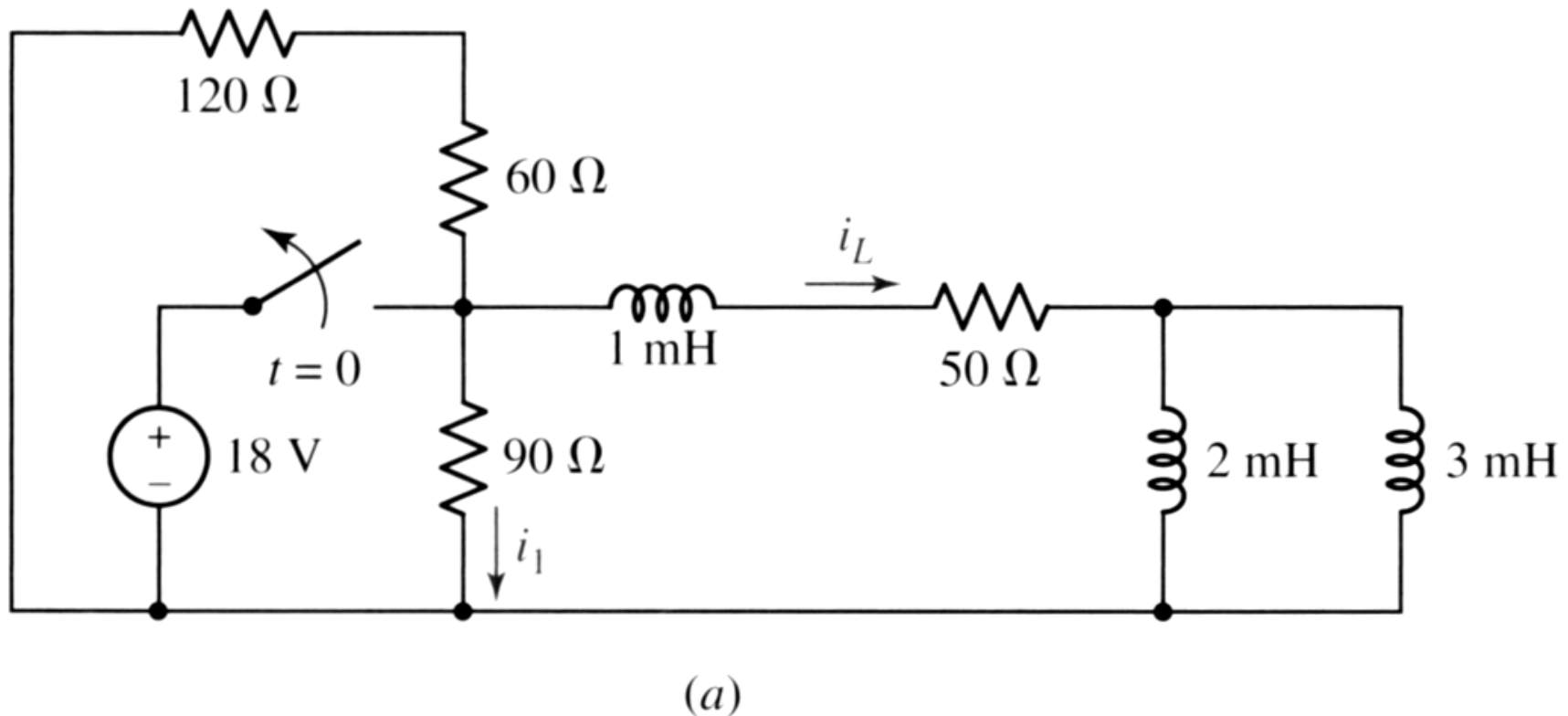
## Example 8.2:

determine both  $i_1$  and  $i_L$  in the circuit




# Example :

determine both  $i_1$  and  $i_L$  in the circuit

$$t < 0, i_L = \frac{18}{50} = 360 \text{ mA.}$$
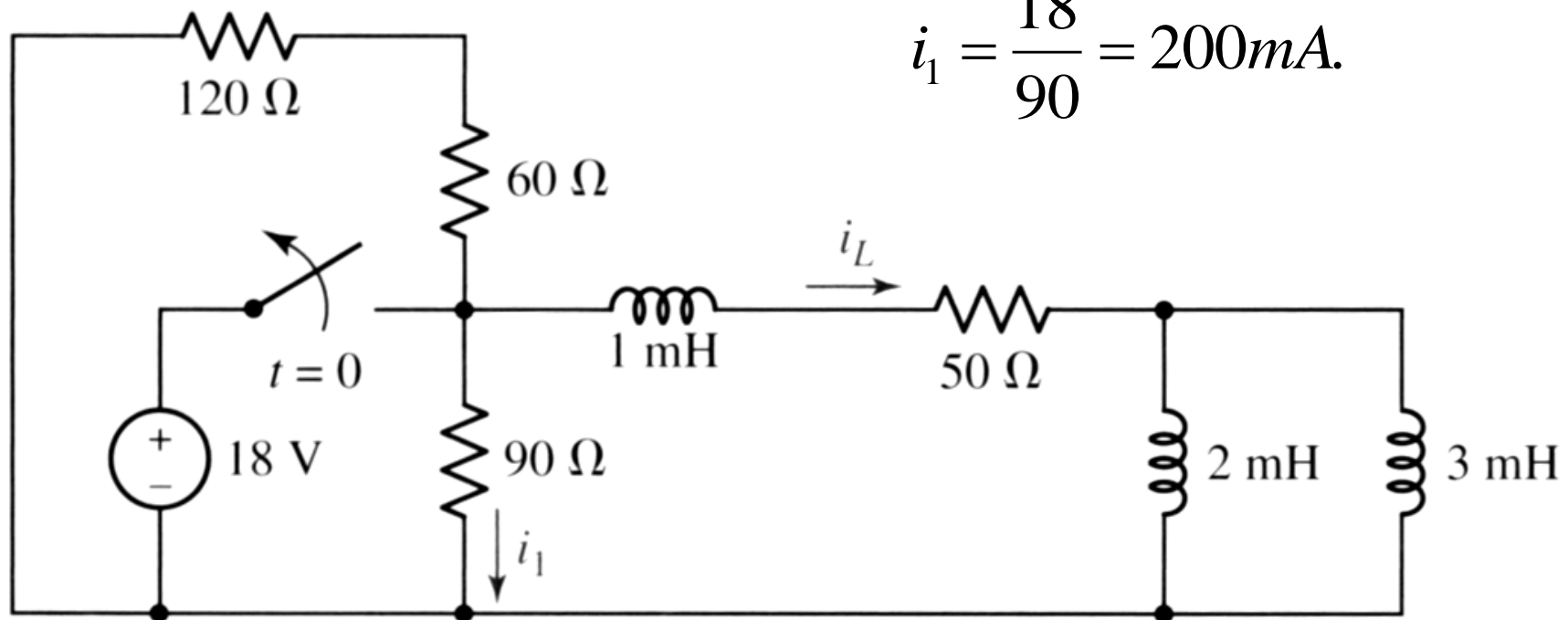
$$i_1 = \frac{18}{90} = 200 \text{ mA.}$$



# Example :

determine both  $i_1$  and  $i_L$  in the circuit


For  $t > 0$ ,

$$L_{eq} = \frac{2 \times 3}{2 + 3} + 1 = 2.2 \text{ mH}.$$

$$R_{eq} = \frac{90 \times (60 + 120)}{90 + 180} + 50 = 110 \Omega$$

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{2.2 \times 10^{-3}}{110} = 20 \mu\text{s}.$$

$$i(t) = I_0 e^{-Rt/L}$$

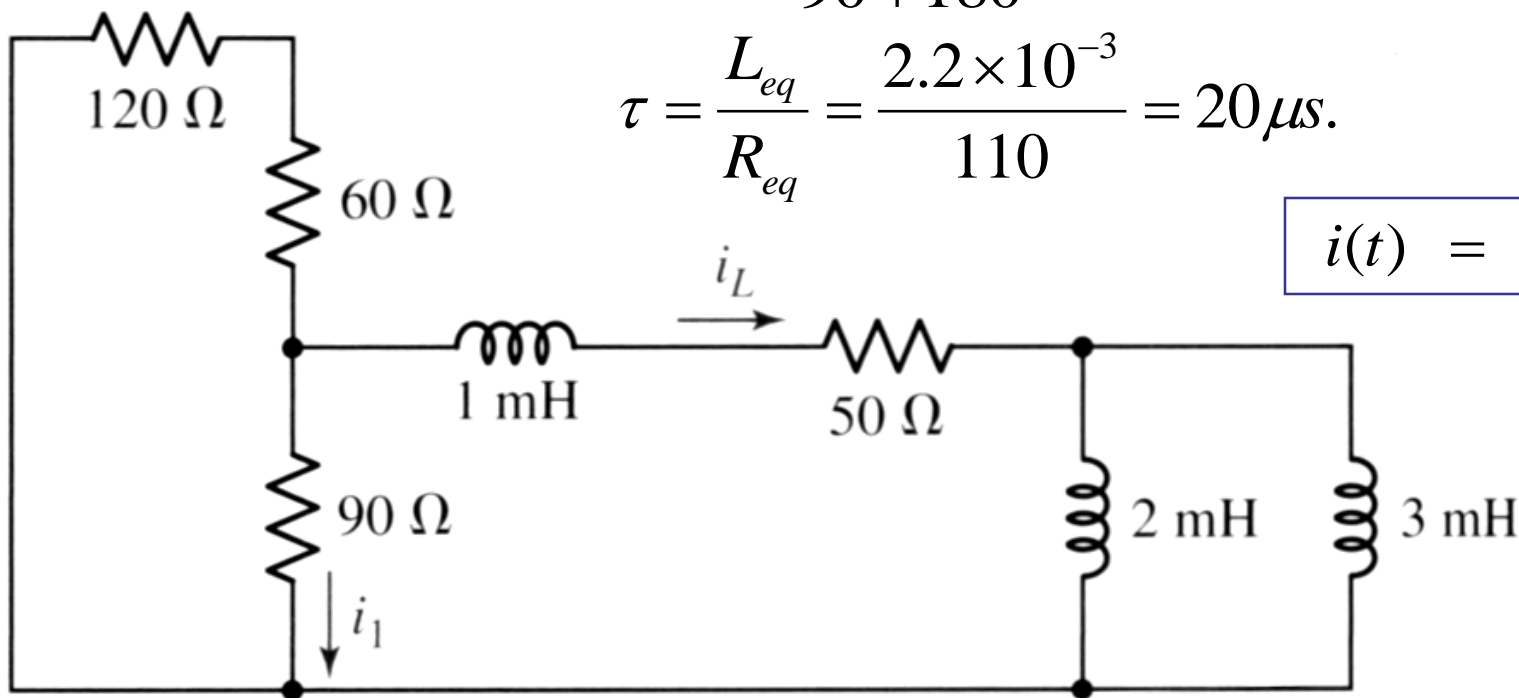


# Example :


determine both  $i_1$  and  $i_L$  in the circuit

For  $t > 0$ ,  $i_L(0^+) = i_L(0^-) = 360 \text{ mA}$ .
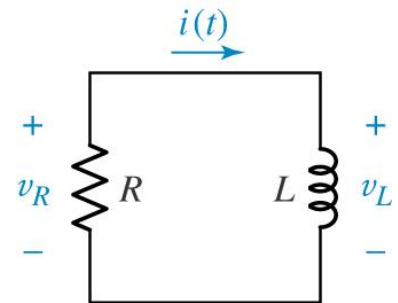
$$i_L(t) = 360e^{\frac{-Rt}{L}} = 360e^{\frac{-t}{\tau}} = 360e^{-50000t} \text{ mA}.$$



$$i(t) = I_0 e^{-Rt/L}$$

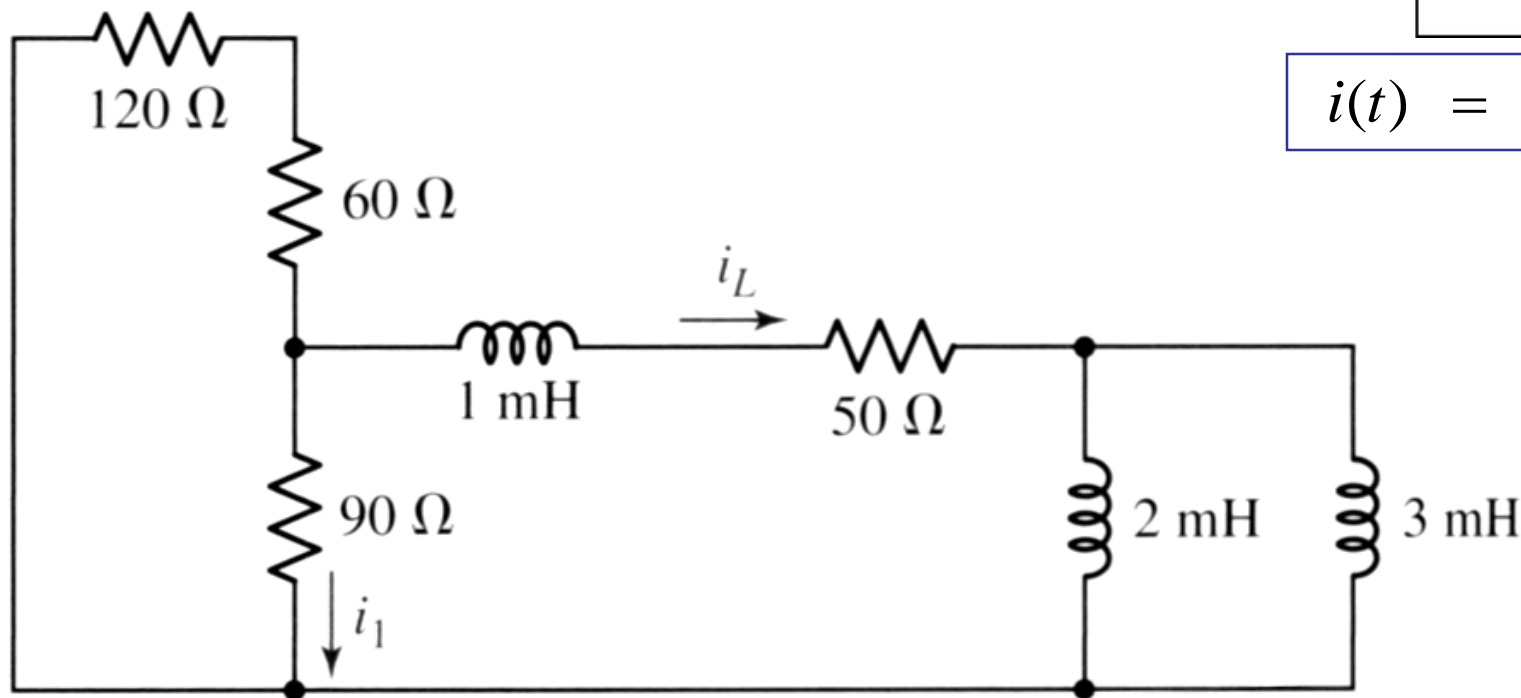


# Example :


determine both  $i_1$  and  $i_L$  in the circuit

For  $t > 0$ ,  $i_1(0^+) = -i_L(0^+) \frac{120 + 60}{120 + 60 + 90} = -240 \text{ mA}.$

$$i_1(t) = -240e^{-50000t} \text{ mA}.$$

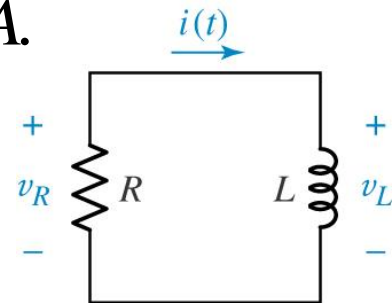


$$i(t) = I_0 e^{-Rt/L}$$

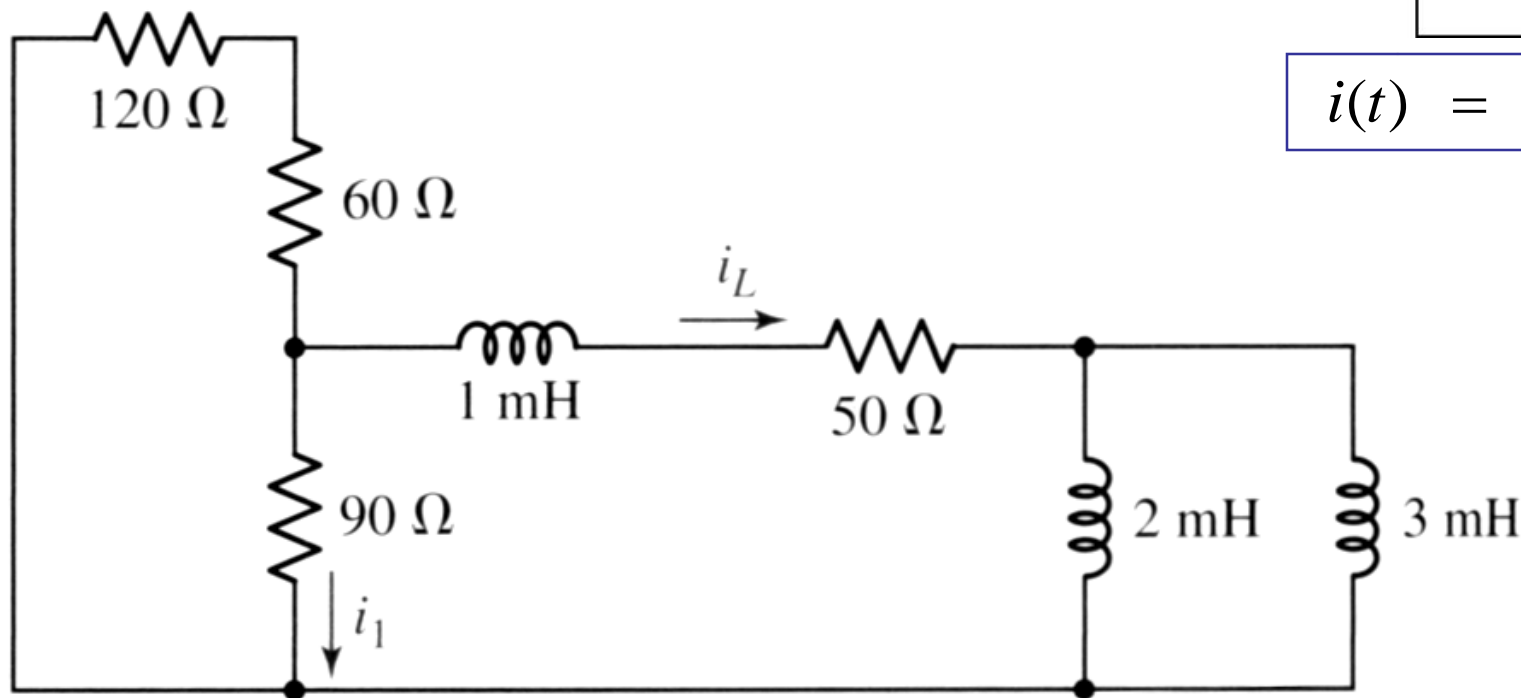
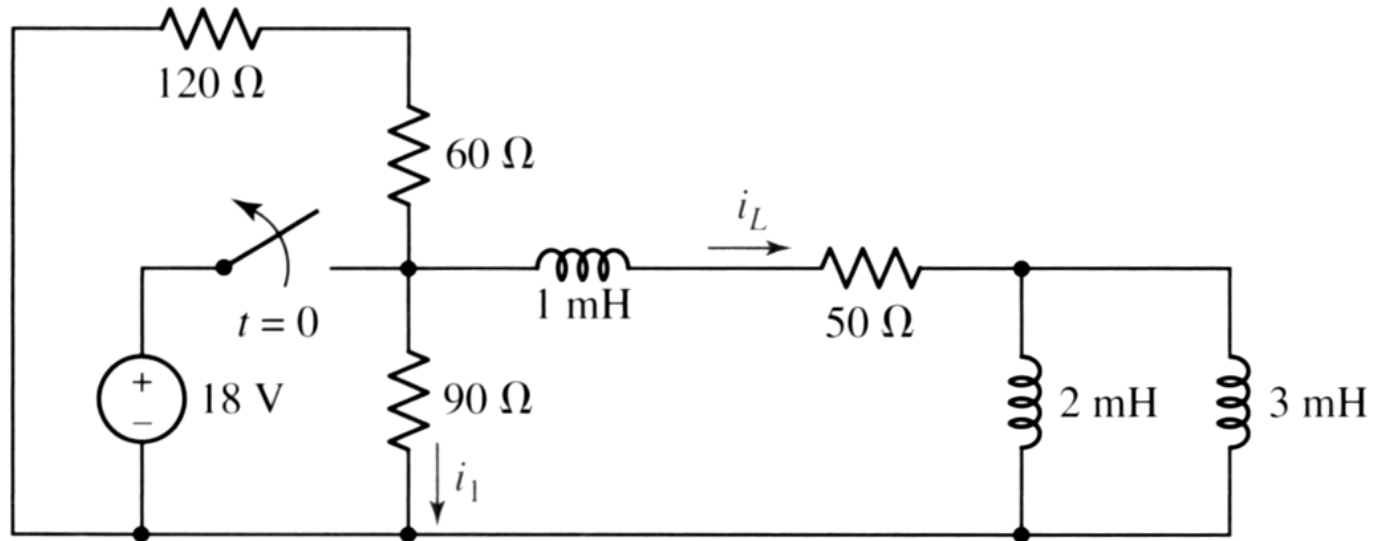
# Example :

determine both  $i_1$  and  $i_L$  in the circuit




$$i_L(t) = \begin{cases} 360 \text{ mA} & (t < 0) \\ 360e^{-50000t} \text{ mA} & (t > 0) \end{cases}$$

$$i_1(t) = \begin{cases} 200 \text{ mA} & (t < 0) \\ -240e^{-50000t} \text{ mA} & (t > 0) \end{cases}$$
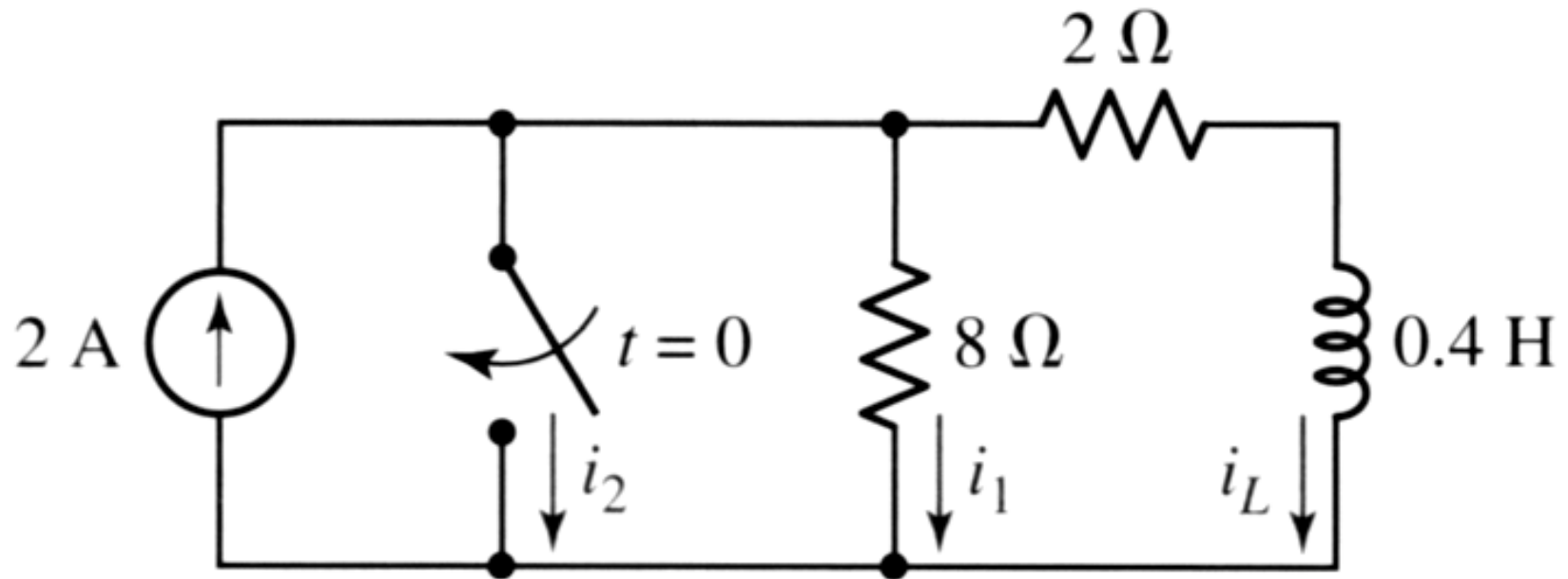
# Practice: 8.4


at  $t = 0.15\text{s}$ . find the value of  $i_L$ ,  $i_1$ ,  $i_2$



# Example :

at  $t = 0.15$  s. find the value of  $i_L$ ,  $i_1$ ,  $i_2$

For  $t < 0$ ,

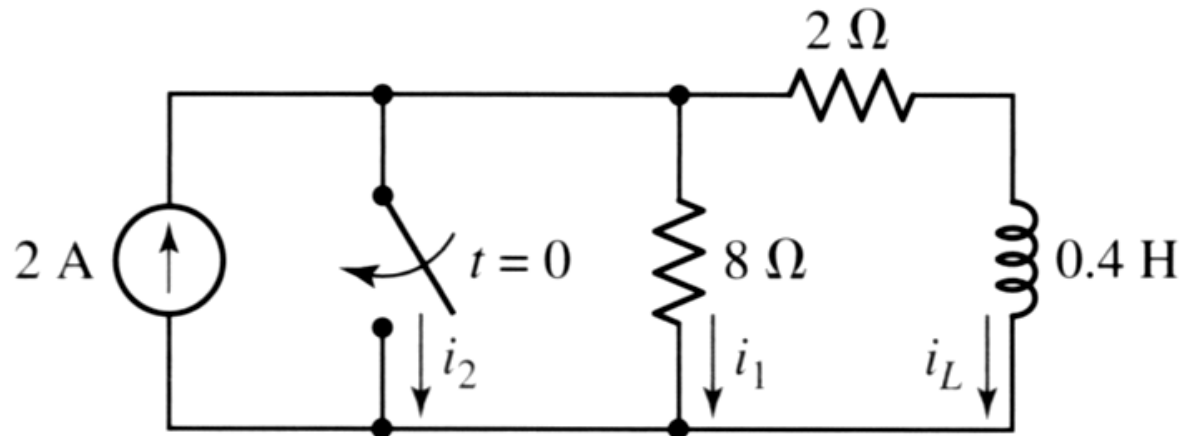

$$i_L = \frac{8}{8+2} \cdot 2\text{ A} = 1.6\text{ A} = i_L(0^-) = i_L(0^+) = I_0$$


$$i_1 = \frac{2}{8+2} \cdot 2\text{ A} = 0.4\text{ A}.$$




# Example :

at  $t = 0.15\text{s}$ . find the value of  $i_L$ ,  $i_1$ ,  $i_2$

For  $t > 0$ ,

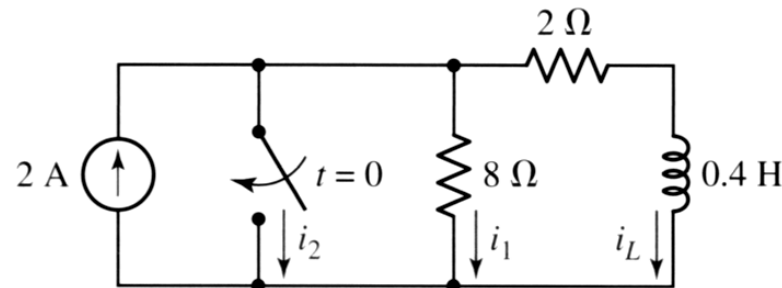

$$R_{eq} = 2\Omega$$

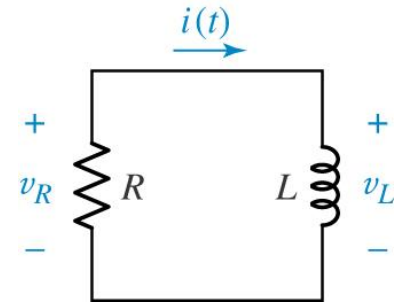


$$i(t) = I_0 e^{-Rt/L}$$

$$i_L(t = 0.15\text{s.}) = 1.6e^{\frac{-Rt}{L}} = 1.6e^{\frac{-2t}{0.4}} = 0.756\text{A.}$$

$$i_2 = 2 - i_L = 1.244\text{A.}$$

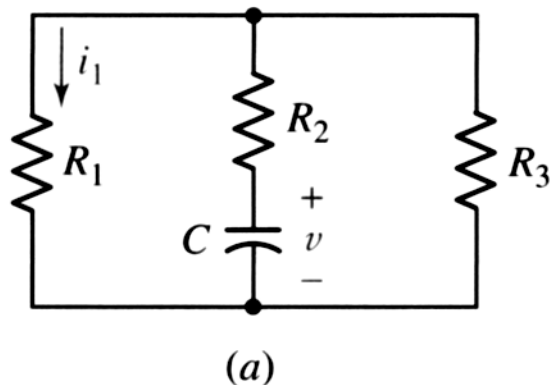
# Example 8.3:

find  $v(0^+)$  and  $i_1(0^+)$  if  $v(0^-) = V_0$



$$v_C(0^+) = v_C(0^-) = V_0$$

$$i_1(t) = i_1(0^+)e^{\frac{-t}{\tau}}$$

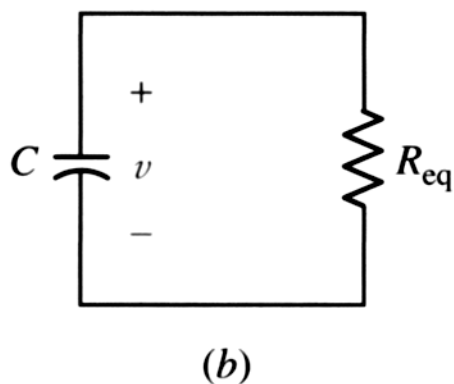


$$\tau = R_{eq}C$$

$$i_1(0^+) = \frac{V_0}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} \cdot \frac{R_3}{R_1 + R_3}$$

$$R_{eq} = R_2 + R_1 // R_3$$
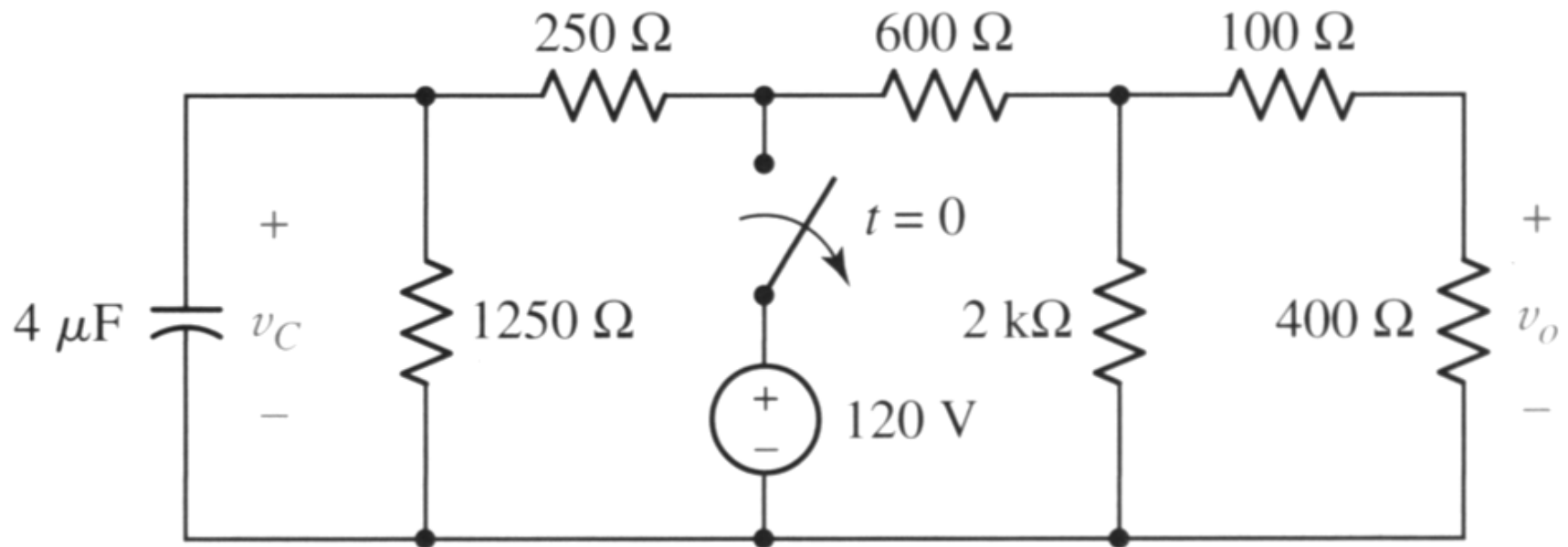
# Practice: 8.5


find  $v_C$  and  $v_O$  at  $t = 0^-$ ,  $0^+$ ,  $1.3\text{ms}$ .



# Example :

find  $v_C$  and  $v_o$  at  $t = 0^-$ ,  $0^+$ ,  $1.3\text{ms}$ .

For  $t < 0$ ,

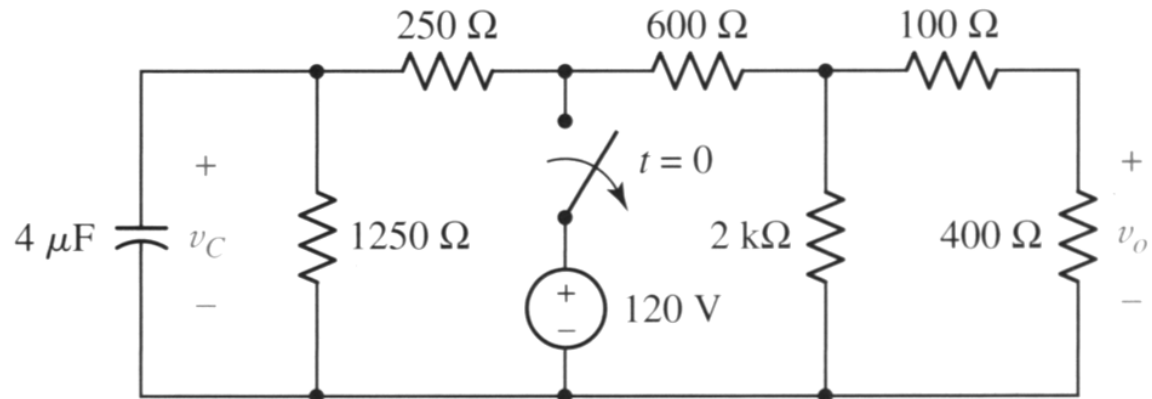


$$v_C = \frac{1250}{1250 + 250} \cdot 120\text{V} = 100\text{V} = v_C(0^-) = v_C(0^+)$$

$$v_o(0^-) = \left[ \frac{(400 + 100) \cdot 2k}{400 + 100 + 2k} + 600 \right]^{-1} \cdot 120 \cdot \frac{2k}{400 + 100 + 2k} \cdot 400 = 38.4\text{V}.$$

# Example :

find  $v_C$  and  $v_o$  at  $t = 0^-$ ,  $0^+$ ,  $1.3\text{ms}$ .

For  $t=0^+$ ,

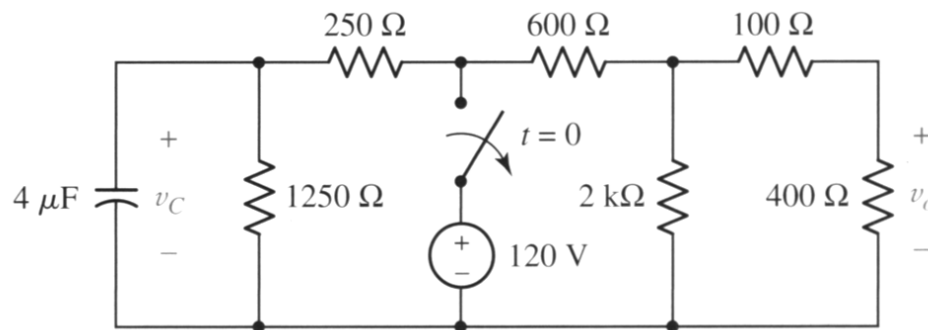



$$v_C(0^+) = v_C(0^-) = 100V.$$

$$v_o(0^+) = \frac{100V.}{250 + 600 + 500 // 2k} \cdot \frac{2k}{400 + 100 + 2k} \cdot 400 = 25.6V.$$

# Example :

find  $v_C$  and  $v_o$  at  $t = 0^-$ ,  $0^+$ ,  $1.3\text{ms}$ .

For  $t=1.3\text{ms}$ .,

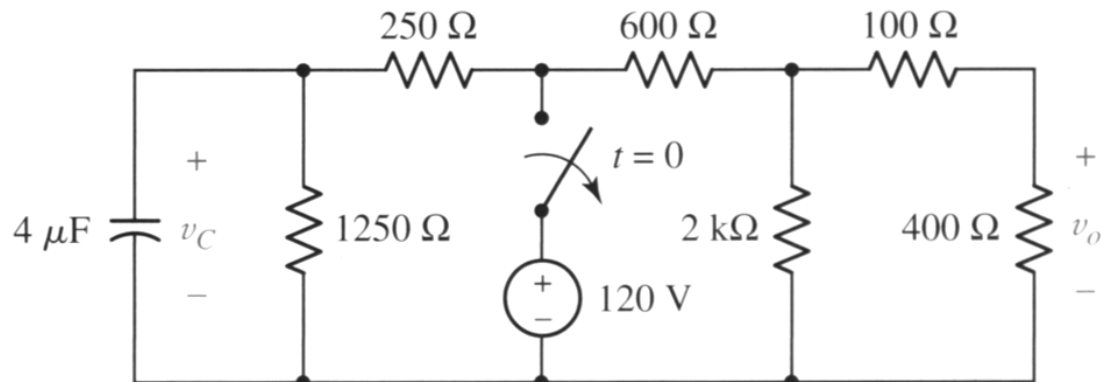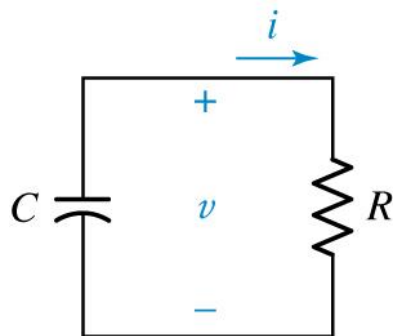

$$\begin{aligned}
 R_{eq} &= 1250 // \{250 + 600 + [2k // (100 + 400)]\} \\
 &= 1250 // \{850 + 400\} \\
 &= 625\Omega
 \end{aligned}$$

$$\tau = R_{eq}C = (625) \cdot (4\mu F) = 0.0025$$

$$v_C(t) = v_C(0^+)e^{\frac{-t}{\tau}} = 100e^{-400t} \text{ V.}$$


$$v_C(t = 1.3\text{ms.}) = 59.45\text{V.}$$

$$\frac{1}{\tau} = 400$$


$$v_o(t = 1.3\text{ms.}) = v_o(0^+)e^{-400t} = 25.6e^{-400t} = 15.22\text{V.}$$

# The Unit-Step Function:

---

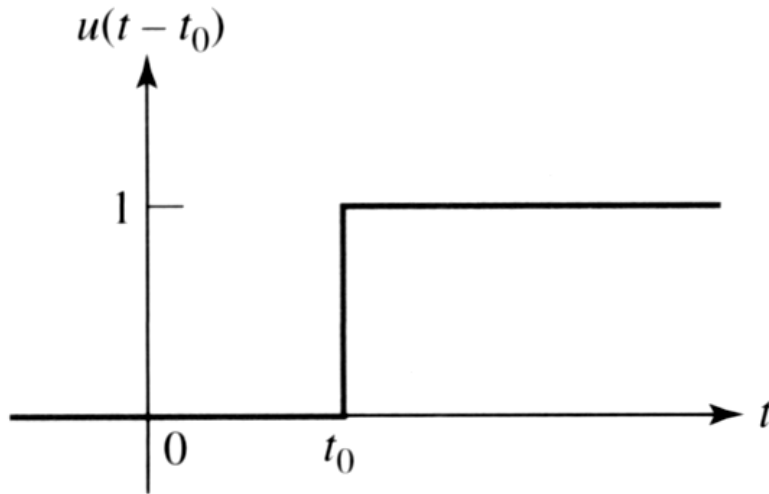

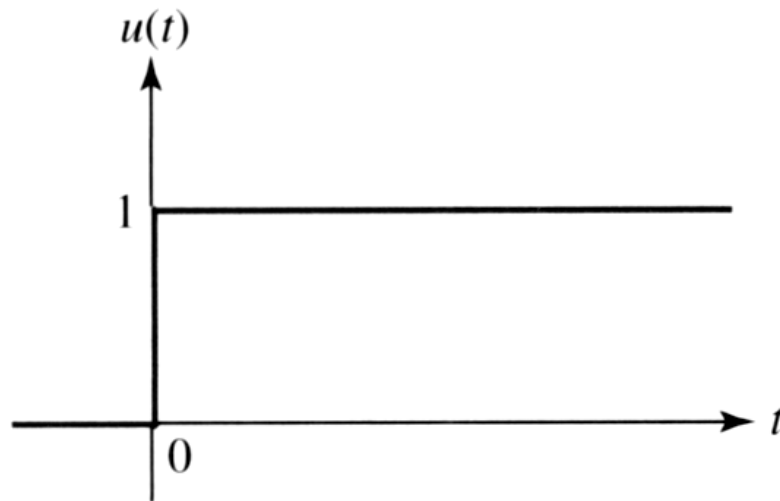
$$u(t - t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$



$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$


# The Unit-Step Function:

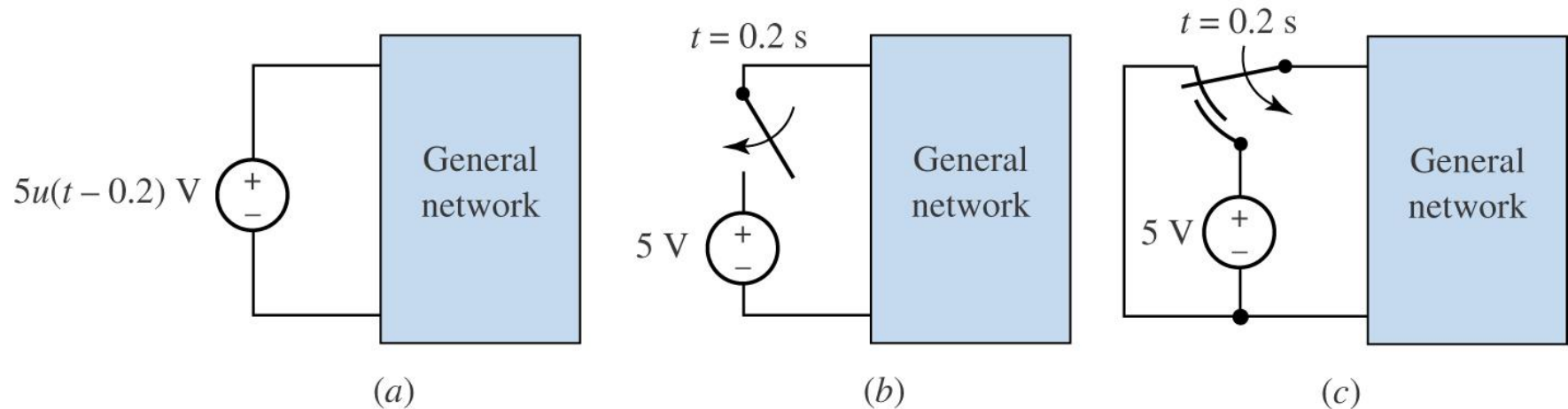


(a) A voltage-step forcing function is shown as the source driving a general network. (b) A simple circuit which, although not the exact equivalent of part (a), may be used as its equivalent in many cases. (c) An exact equivalent of part (a).



# The Unit-Step Function:

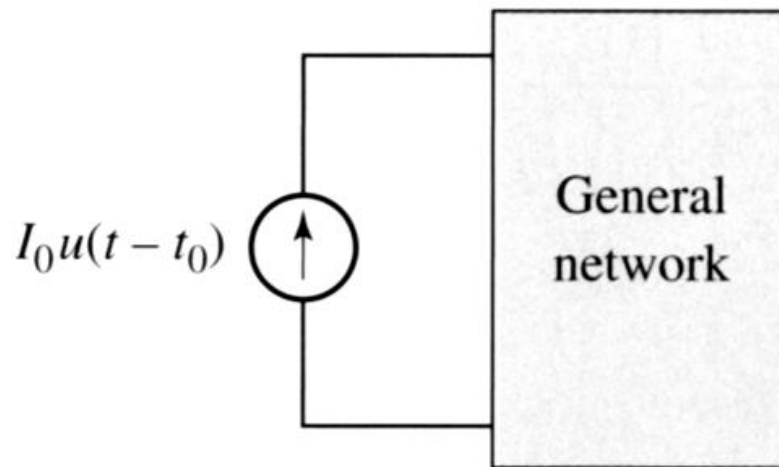


(a)

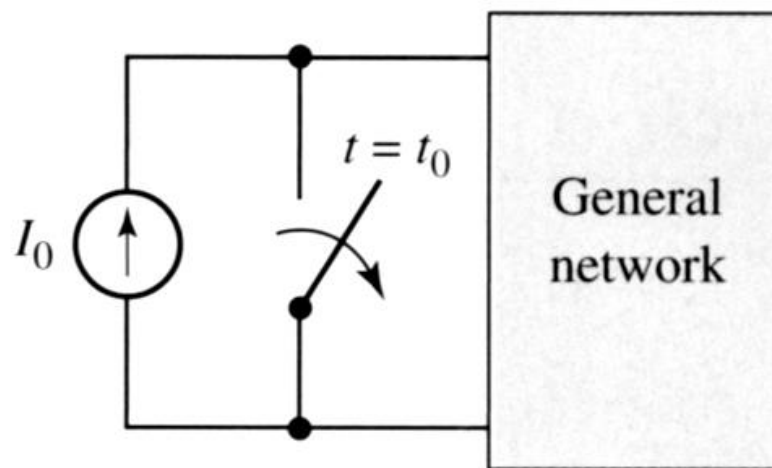



(b)

# The Rectangular Pulse Function:

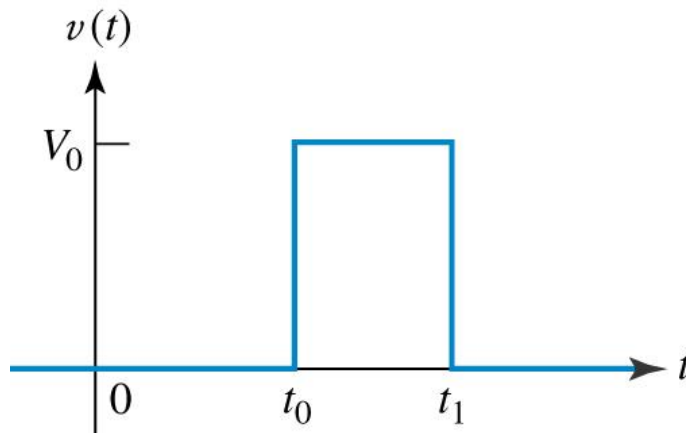

The rectangular pulse function
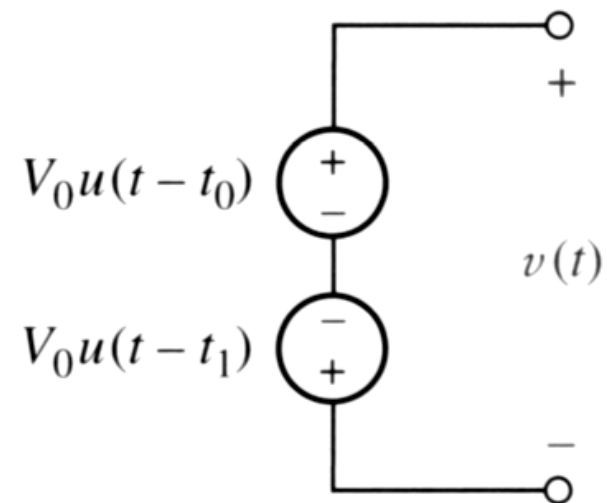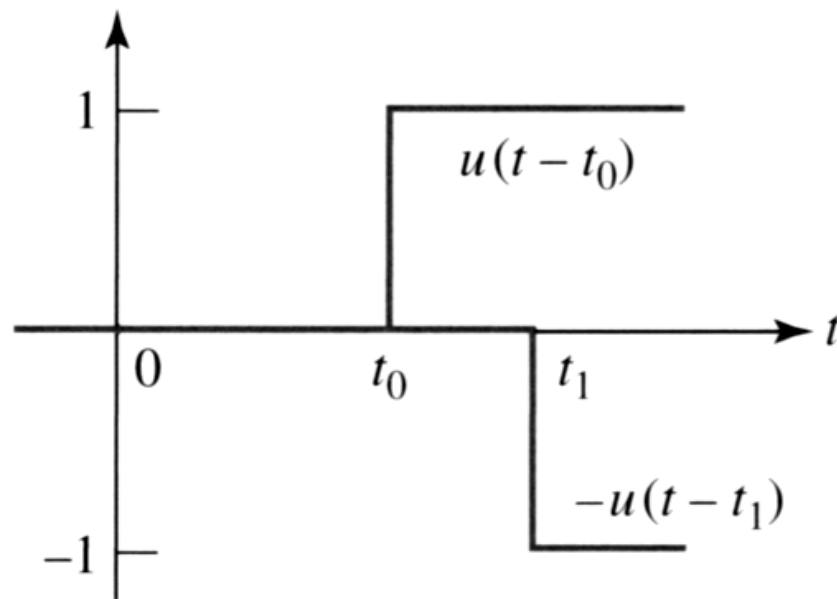
$$v(t - t_0) = \begin{cases} 0 & t < t_0 \\ V_0 & t_0 < t < t_1 \\ 0 & t > t_1 \end{cases}$$



# Practice: 8.6

---

Evaluate each of the following at  $t = 0.8$ :


- (a)  $3u(t) - 2u(-t) + 0.8u(1 - t)$ ; (b)  $[4u(t)]u(-t)$ ;  
(c)  $2u(t)\sin\pi t$ .

$$(a) \quad 3 - 0 + 0.8 = \underline{3.8}$$

$$(b) \quad [4] (0) = \underline{0}$$

$$(c) \quad 2 \sin 0.8 \pi = \underline{1.176}$$

# Driven RL Circuits:

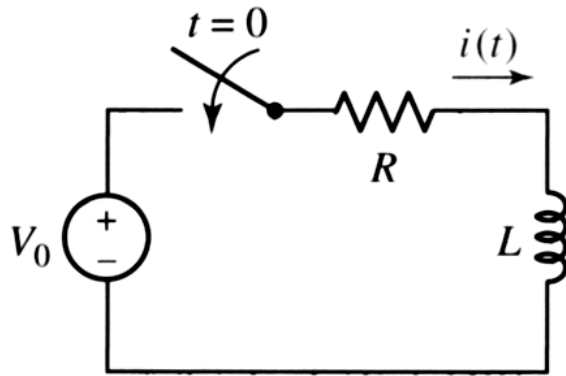


(a)

$$Ri(t) + L \frac{di(t)}{dt} = V_0 u(t)$$

$$i(t) = 0, t < 0$$

for positive time;  $t > 0$

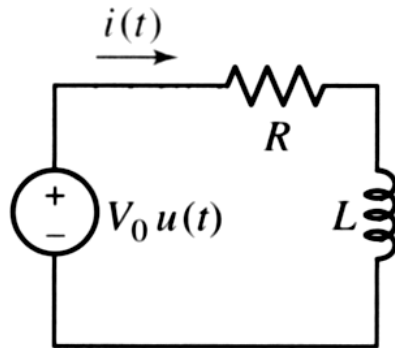

(b)

$$Ri(t) + L \frac{di(t)}{dt} = V_0$$


yielding;

$$\frac{L di(t)}{V_0 - Ri(t)} = dt$$

integrated;

$$-\frac{L}{R} \ln(V_0 - Ri) = t + k$$

# Driven RL Circuits:

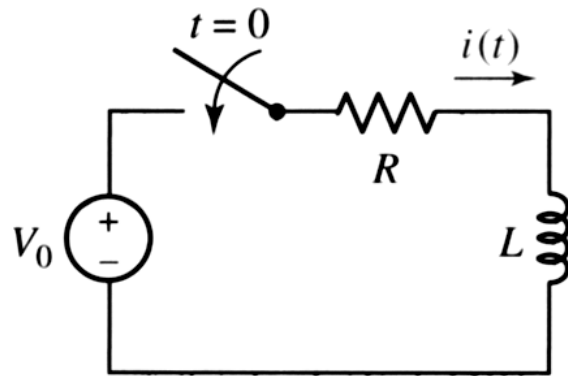

(a)


$$-\frac{L}{R} \ln(V_0 - Ri) = t + k$$

setting  $i = 0$  for  $t = 0$ , we obtain;

$$-\frac{L}{R} \ln(V_0) = k$$

And, hence,
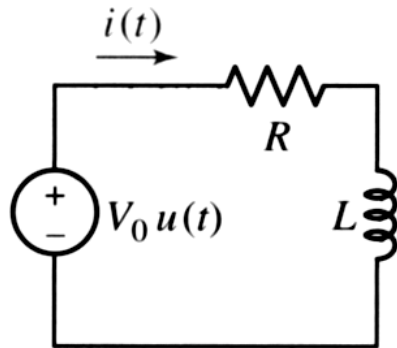
$$-\frac{L}{R} \{\ln(V_0 - Ri) - \ln(V_0)\} = t$$



(b)

$$\frac{V_0 - Ri}{V_0} = e^{-\frac{Rt}{L}}$$

or

$$i(t) = \left( \frac{V_0}{R} - \frac{V_0}{R} e^{-\frac{Rt}{L}} \right) u(t)$$

# Practice: 8.7

---

The voltage source  $60 - 40u(t)$  V is in series with a  $10\text{-}\Omega$  resistor and a  $50\text{-mH}$  inductor. Find the magnitudes of the inductor current and voltage at  $t$  equal to (a)  $0^-$ ; (b)  $0^+$ ; (c)  $\infty$ ; (d)  $3\text{ms}$ .

- (a)  $t = 0^-$ , so only 60 V is across the RL circuit. Thus  $|v_L(0^-)| = \underline{0}$  and  $|i_L(0^-)| = \frac{60}{10} = \underline{6 \text{ A}}$
- (b) At  $t = 0^+$ , the source voltage changes to  $60 - 40 = 20 \text{ V}$ . The inductor current cannot change, so  $|i_L(0^+)| = \underline{6 \text{ A}}$ . The current through the resistor is 6 A, so the voltage dropped across the inductor is  $20 - 10(6) = -40 \text{ V}$ . Thus,  $|v_L(0^+)| = \underline{40 \text{ V}}$
- (c) At  $t = \infty$ , the source voltage is 20 V but all transients have died out. Thus,  $|i_L(\infty)| = \frac{20}{10} = \underline{2 \text{ A}}$  and  $|v_L(\infty)| = \underline{0}$ . The direction of  $i_L$  has not changed.
- (d) For  $t > 0$ ,  $|i_L(t)| = \left| i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau} \right|$

$$\text{where } |i_L(t)| = 2 \text{ A} \quad \text{and} \quad \tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{10} = 5 \text{ ms}.$$

$$\text{Thus, } i_L(3 \text{ ms}) = 2 + (6 - 2)e^{-3/5} = \underline{4.195 \text{ A}}$$

$$\text{We then find that } |v_L(3 \text{ ms})| = |20 - 4.195(10)| = \underline{21.95 \text{ V}}$$

# Natural and Forced Response:

---

The solution of any linear differential equation may be expressed as the sum of two parts:

- the complementary solution (natural response)
- the particular solution (forced response)

let consider;  $\frac{di}{dt} + Pi = Q$  ;Q = a forcing function  
 $di + Pi \cdot dt = Q \cdot dt$

$$i = e^{-Pt} \int Q e^{-Pt} dt + A e^{-Pt}$$



# Natural and Forced Response:

---

$$i = e^{-Pt} \int Q e^{-Pt} dt + A e^{-Pt}$$

For a source free circuit,  $Q$  must be zero, and the solution is the natural response:

$$i_n = A e^{-Pt}$$

The first term is also called the steady state response, the particular solution, or the particular integral.

When  $Q$  is a constant,

$$i_f = \frac{Q}{P}$$

# Natural and Forced Response:


---

$$i = e^{-Pt} \int Q e^{-Pt} dt + A e^{-Pt}$$

or the complete response;

$$i(t) = i_f + i_n = \frac{Q}{P} + A e^{-Pt}$$

# Determination of the complete res.:

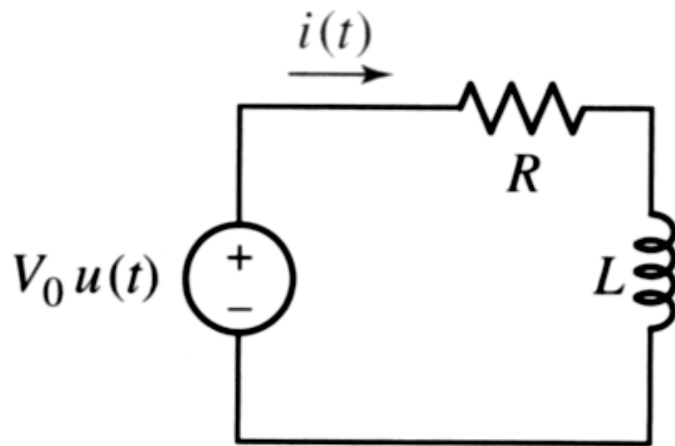

$$i(t) = i_f + i_n$$

$$i_n(t) = A e^{\frac{-Rt}{L}}$$



$$i_f = \frac{V_0}{R}$$

$$\therefore i(t) = i_n(t) + i_f = A e^{\frac{-Rt}{L}} + \frac{V_0}{R}$$


apply initial condition to evaluate A,  $i = 0$  when  $t = 0$ ;

$$0 = A + \frac{V_0}{R} \quad \text{so} \quad i(t) = -\frac{V_0}{R} e^{\frac{-Rt}{L}} + \frac{V_0}{R}$$


# Determination of the complete res.:

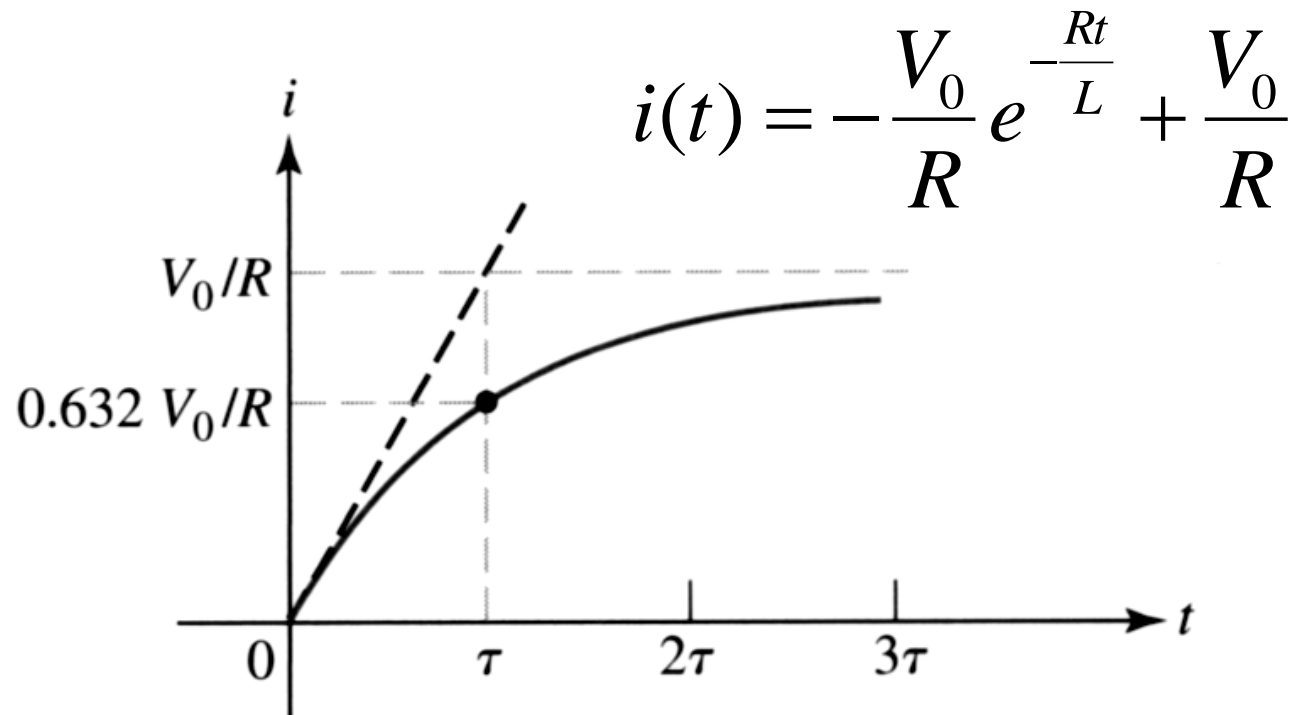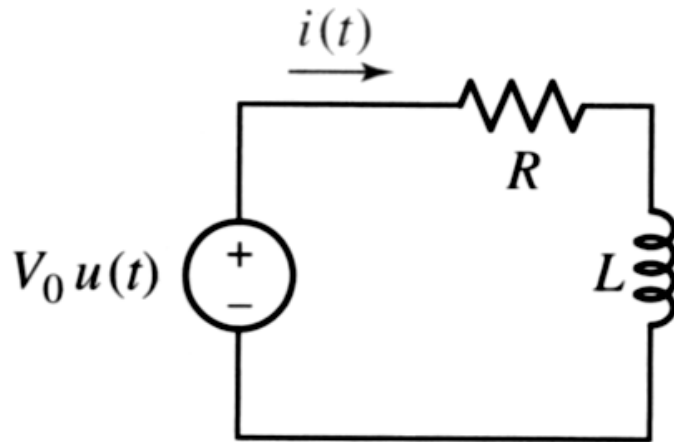

# Example 8.4:

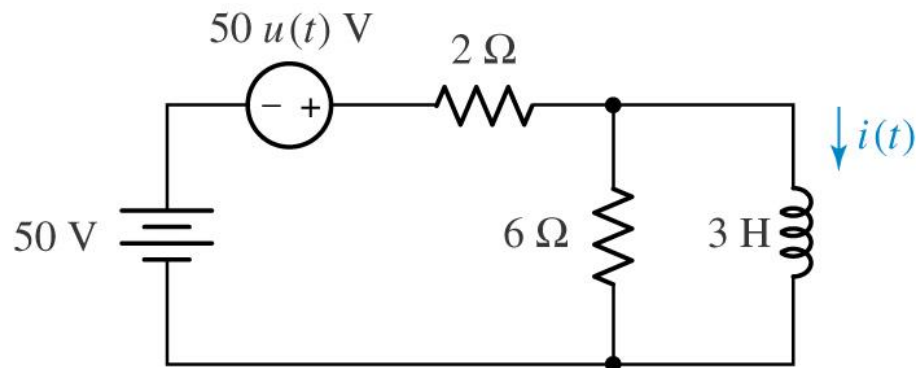


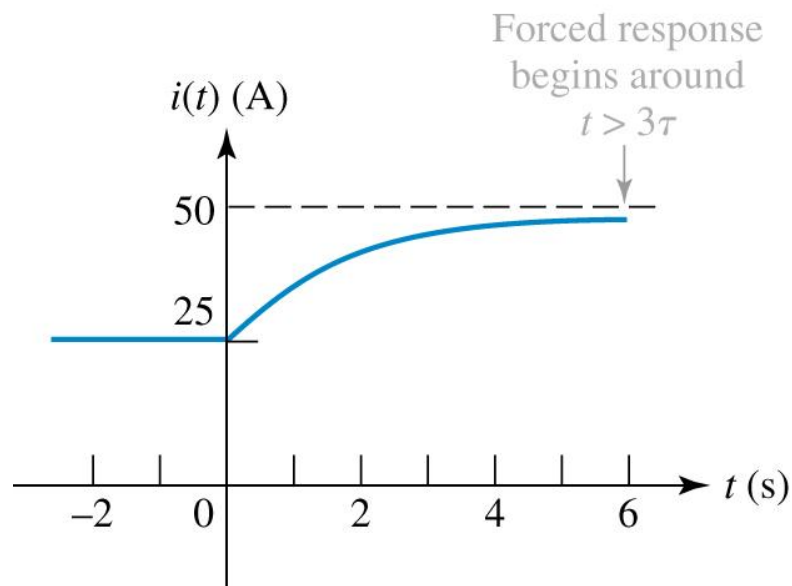**Circuit for which a complete response  $i(t)$  is desired.**



**The desired current response as a function of time.**

# Example :

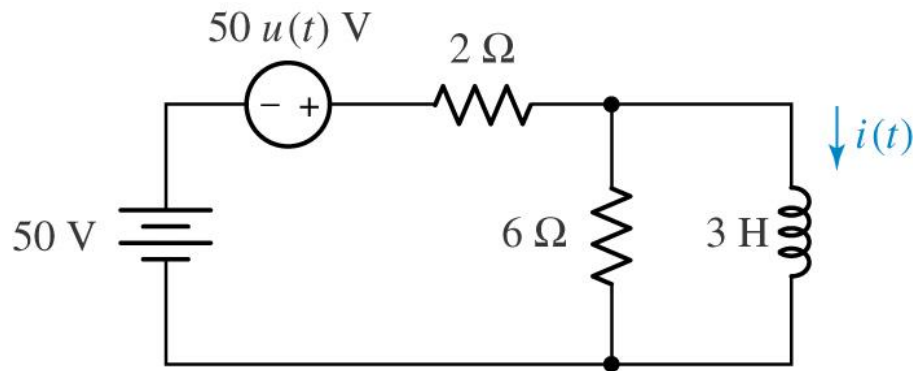

$$R_{eq} = 2 // 6 = \frac{2 \times 6}{2 + 6} = 1.5 \Omega$$

$$i(t) = i_f + i_n$$

$$i_n(t) = A e^{\frac{-R_{eq}t}{L}} = A e^{\frac{-t}{\tau}}, t > 0$$

$$i_f = \frac{100}{2} = 50 A.$$


$$\therefore i(t) = 50 + A e^{\frac{-1.5t}{3}}, t > 0$$

To find A, @t=0<sup>-</sup>;  $i(0^-) = \frac{50}{2} = 25 A.$


$$25 = 50 + A \quad ; A = -25$$

$$\therefore i(t) = 50 - 25e^{-0.5t}, t > 0 \quad \text{or} \quad i(t) = 25 + 25(1 - e^{-0.5t})u(t) A.$$

# Example :

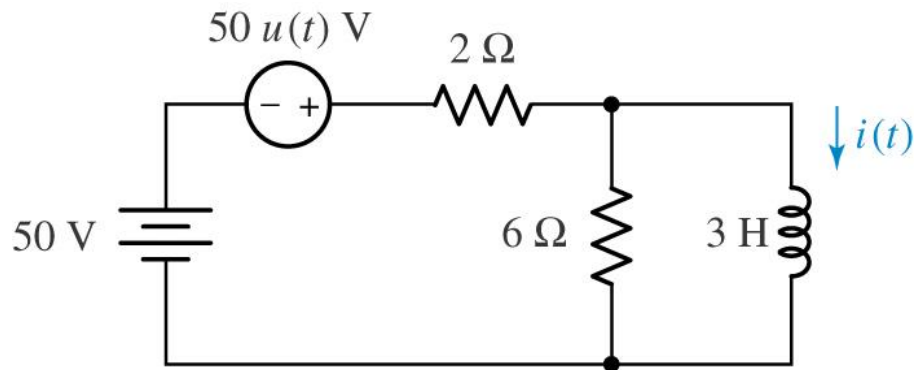
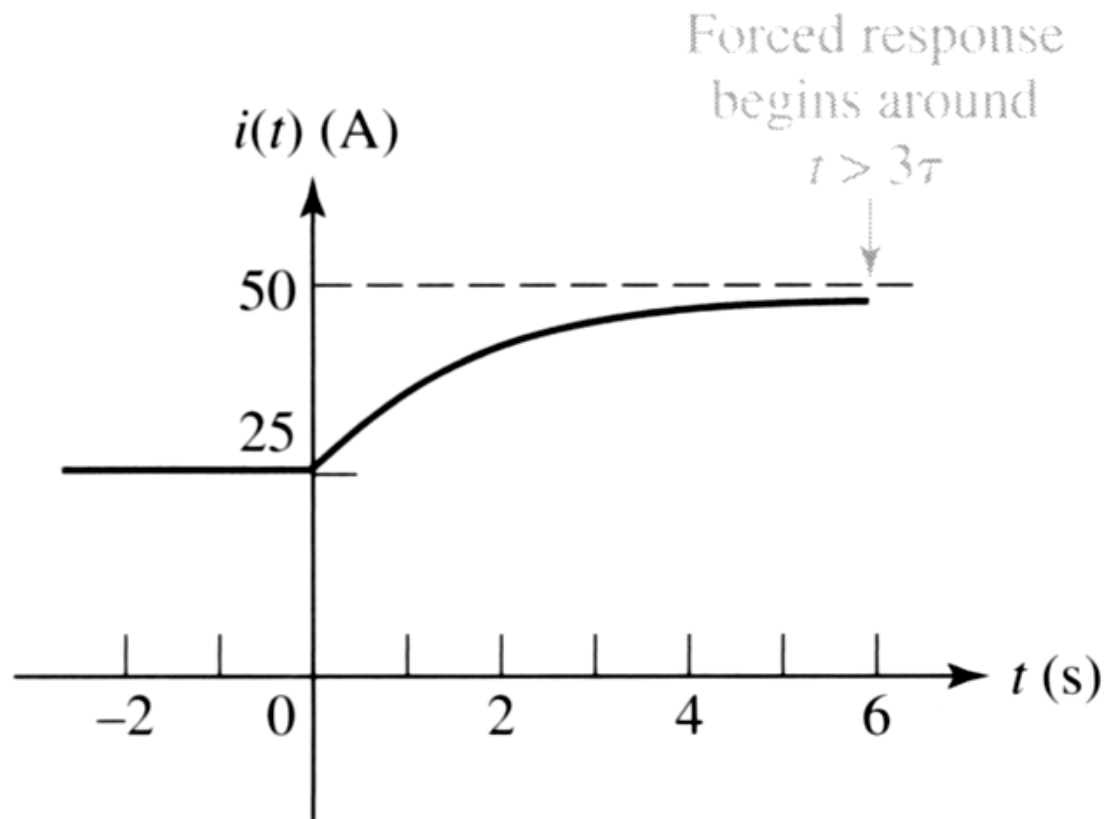
$$i(t) = 25 + 25(1 - e^{-0.5t})u(t) \text{ A.}$$



# Practice: 8.8

---

A voltage source,  $v_s = 20e^{-100t}u(t)$  V, is in series with a  $200\text{-}\Omega$  resistor and a  $4\text{-H}$  inductor. Find the magnitude of the inductor current at  $t$  equal to (a)  $0^-$ ; (b)  $0^+$ ; (c)  $8\text{ ms}$ ; (d)  $15\text{ ms}$ .

$$v_s(0^-) = 0 \quad \text{so} \quad i_L(0^-) =$$

$$i_L(0^+) = i_L(0^-) \quad \text{so} \quad i_L(0^+) =$$



# Practice: 8.8

---

$$v_s(t) = 200i_L(t) + v_L(t)$$

or

$$20e^{-100t} = 200i_L + 4 \frac{di_L}{dt} \quad [1]$$

$$i_L(t) = i_f + i_n$$

$$i_n(t) = Ae^{-t/\tau} \text{ where } \tau = \frac{L}{R} = \frac{4}{200} = 20 \text{ ms}$$

If we assume  $i_f(t) = Be^{-100t}$  then  $i_L(t) = Ae^{-50t} + Be^{-100t}$

$$\text{so } \frac{di_L}{dt} = -50Ae^{-50t} - 100Be^{-100t}$$

Substituting back in Eq. [1],

$$200i_L + 4 \frac{di_L}{dt} = 200Ae^{-50t} + 200Be^{-100t} - 200Ae^{-50t} - 400Be^{-100t} = -200Be^{-100t}$$

Thus, referring to Eq. [1],  $20 = -200 \underline{B}$  so  $B = \frac{-20}{200} = -0.1$

Thus,  $i_L(t) = A e^{-50t} - 0.1 e^{-100t}$



since  $i_L(0^+) = A - 0.1 = 0$ ,  $A = 0.1$  and  $i_L(t) = 0.1(e^{-50t} - e^{-100t})$  amperes

(c)  $i_L(8 \text{ ms}) = \underline{22.10 \text{ mA}}$

(d)  $i_L(15 \text{ ms}) = \underline{24.92 \text{ mA}}$

## Example 8.5:

find the current response

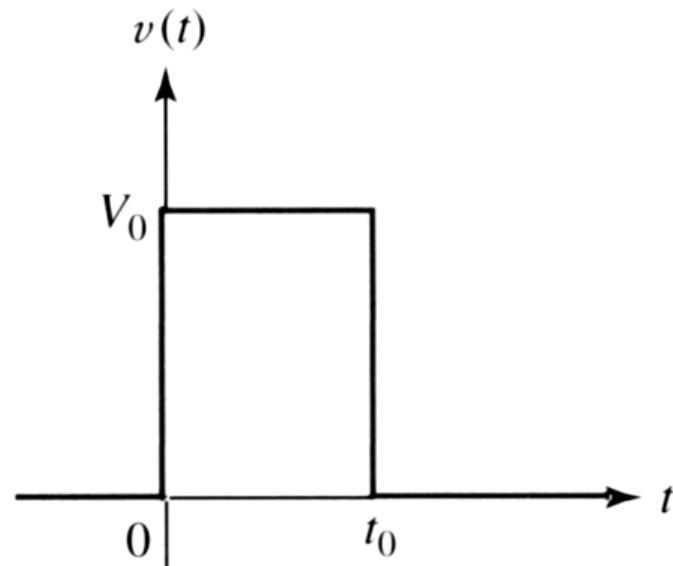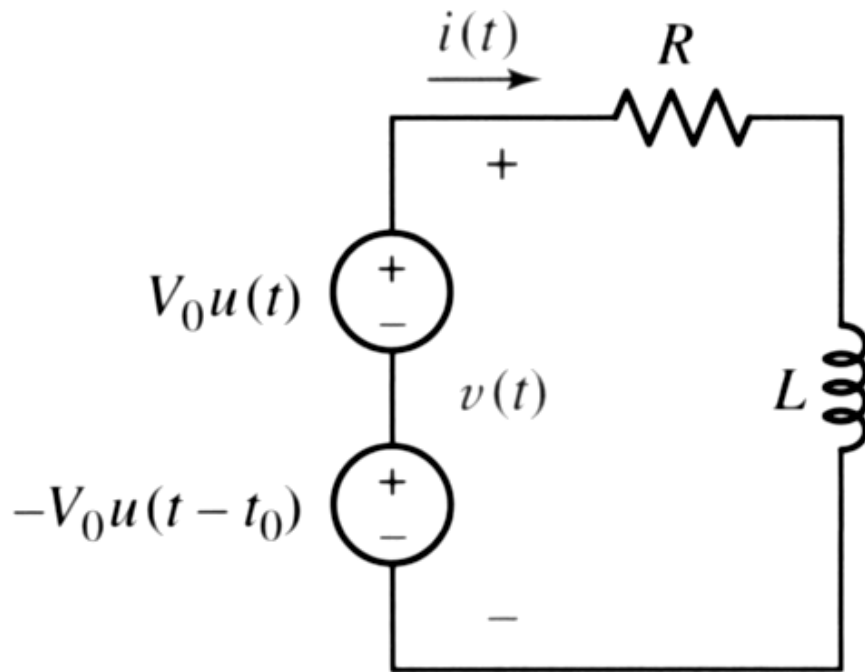


# Example :

find the current response

$$i(t) = i_1(t) + i_2(t)$$

$$i_1(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right), t > 0$$
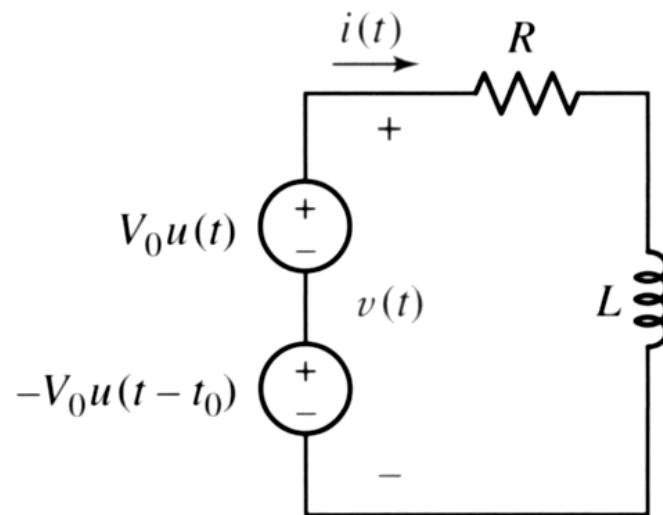
$$i_2(t) = -\frac{V_0}{R} \left( 1 - e^{-\frac{R(t-t_0)}{L}} \right), t > t_0$$



$$\therefore i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right), 0 < t < t_0$$

and



$$\therefore i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right) - \frac{V_0}{R} \left( 1 - e^{-\frac{R(t-t_0)}{L}} \right), t > t_0$$

# Example :


find the current response

$$\therefore i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right), 0 < t < t_0$$
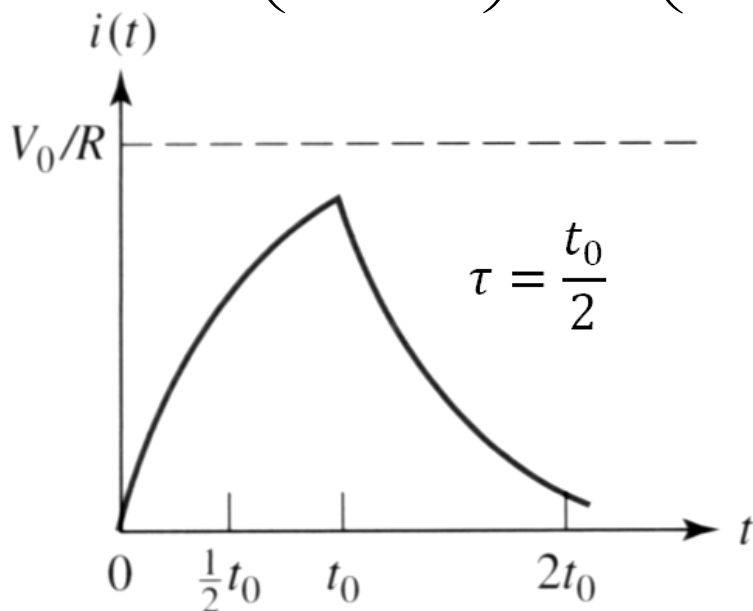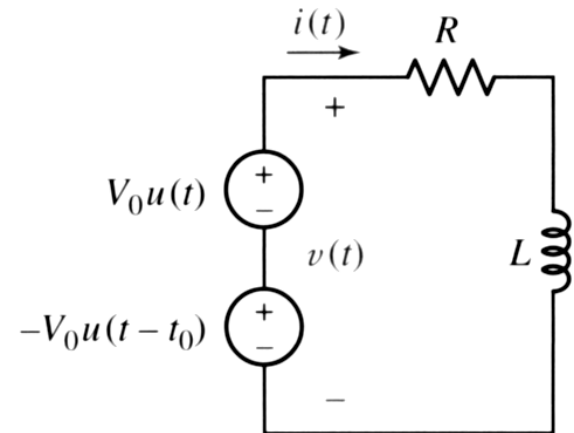
$$\therefore i(t) = \frac{V_0}{R} \left( 1 - e^{-\frac{Rt}{L}} \right) - \frac{V_0}{R} \left( 1 - e^{-\frac{R(t-t_0)}{L}} \right), t > t_0$$



(a)

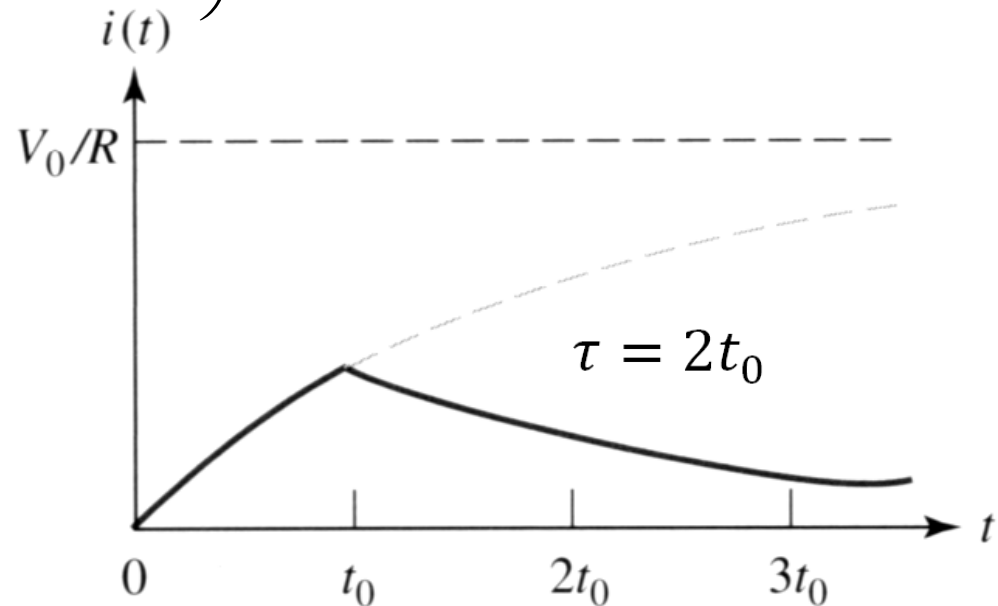

(b)


# Summary:

---

1. With all independent sources killed, simplify the circuit to determine  $R_{eq}$ ,  $L_{eq}$  and the time constant  $\tau = L_{eq} / R_{eq}$ .
2. Viewing  $L_{eq}$  as a short circuit, use dc analysis methods to find  $i_L(0^-)$  the inductor current just prior to the discontinuity.
3. Again viewing  $L_{eq}$  as a short circuit, use dc analysis methods to find the forced response. This is the value approached by  $f(t)$  as  $t \rightarrow \infty$ ; we represent it by  $f(\infty)$ .
4. Write the total response as the sum of the forced and natural responses:  $f(t) = f(\infty) + Ae^{-t/\tau}$ .
5. Find  $f(0^+)$  by using the condition that  $i_L(0^+) = i_L(0^-)$ . If desired,  $L_{eq}$  may be replaced by a current source  $i_L(0^+)$  [an open circuit if  $i_L(0^+) = 0$ ] for this calculation. With the exception of inductor currents (and capacitor voltages), other currents and voltages in the circuit may change abruptly.
6.  $f(0^+) = f(\infty) + A$  and  $f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$ , or total response = final value + (initial value — final value)  $e^{-t/\tau}$ .
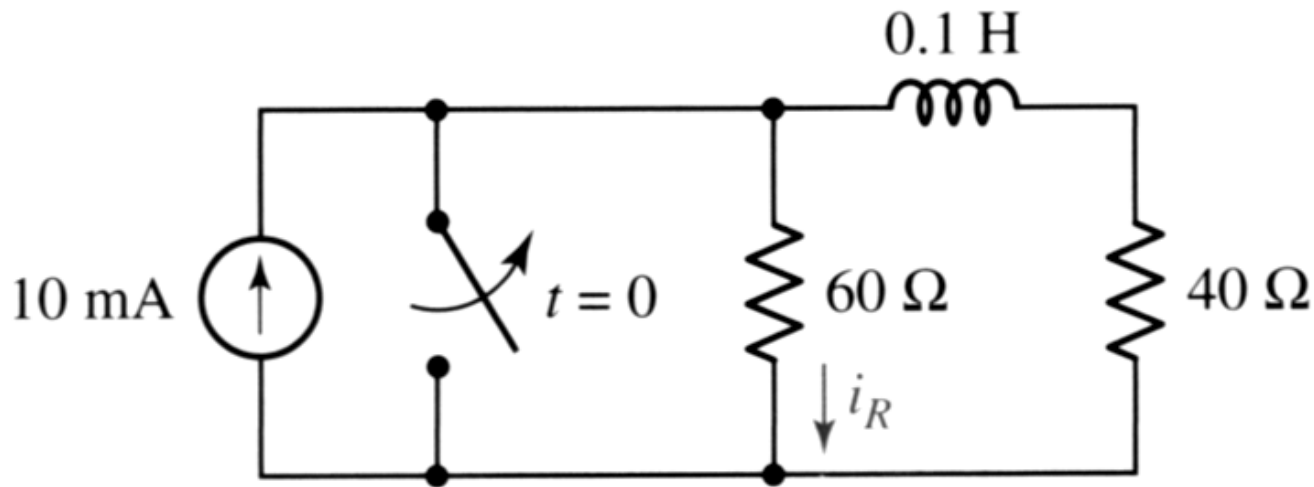
# Practice: 8.9


The circuit shown has been in the form shown for a very long time. The switch opens at  $t = 0$ . find  $i_R$  at  $t$  equal to (a)  $0^-$ ; (b)  $0^+$ ; (c)  $\infty$ ; (d) 1.5 ms.



# Practice: 8.9

(a)  $i_R(0^-) = \underline{0}$

(b)  $i_L(0^-) = 0$  so  $i_L(0^+) = 0$

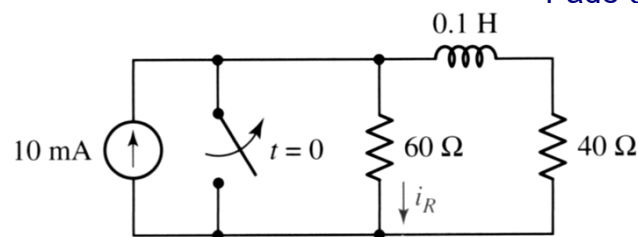

Thus, all of the source current is shunted through the  $60\text{-}\Omega$  resistor; hence,  
 $i_R(0^+) = \underline{10\text{ mA}}$

(c)  $i_R(\infty) = 10 \times \frac{40}{40 + 60} = \underline{4\text{ mA}}$

(d)  $\tau = \frac{L}{R_{\text{eq}}} = \frac{0.1}{40 + 60} = 1\text{ ms}$




$$\begin{aligned} i_R(t) &= i_R(\infty) + [i_R(0^+) - i(\infty)]e^{-t/\tau} \\ &= 4 + [10 - 4]e^{-10^3 t} \text{ mA} \end{aligned}$$

so  $i_R(1.5\text{ ms}) = \underline{5.339\text{ mA}}$


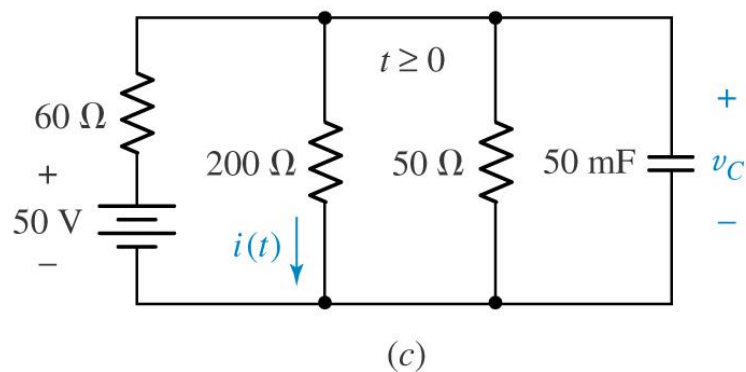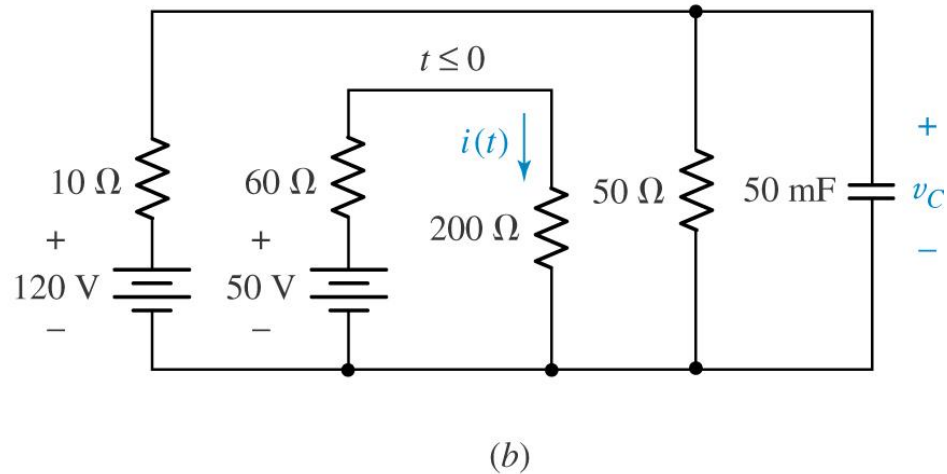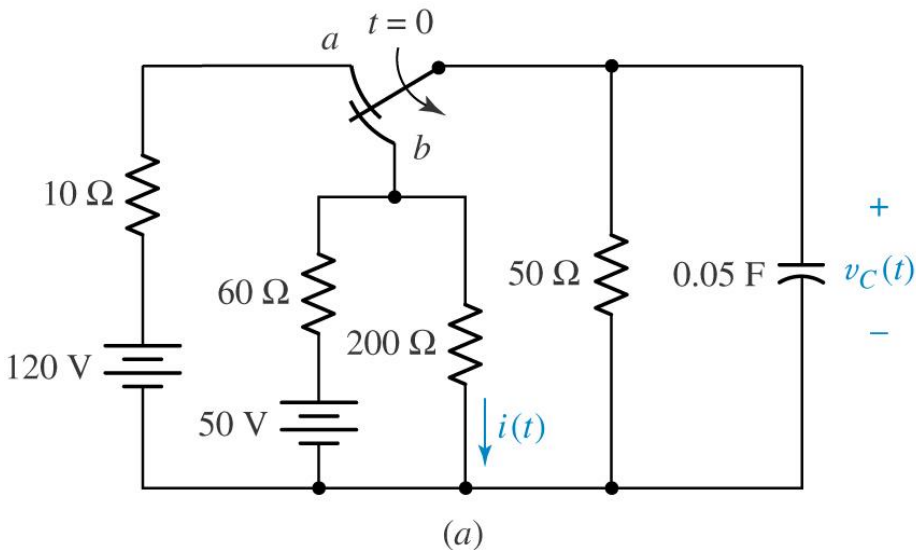
# Driven RC Circuits: Example


Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the  $200\text{-}\Omega$  resistor of the circuit shown in (a).




**(a) Original circuit; (b) circuit valid for  $t \leq 0$ ; (c) circuit for  $t \geq 0$ .**
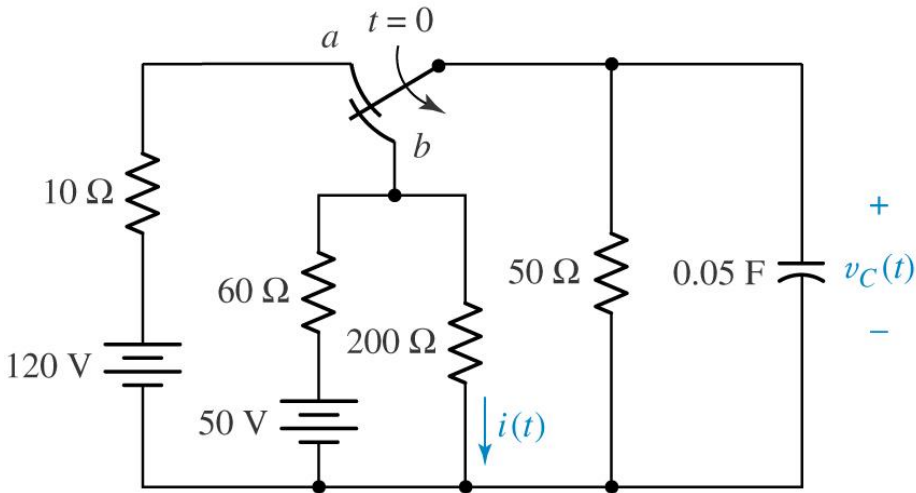
# Driven RC Circuits: Example

Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the  $200\text{-}\Omega$  resistor of the circuit shown in (a).



$$v_C(t) = v_{Cf} + v_{Cn}$$

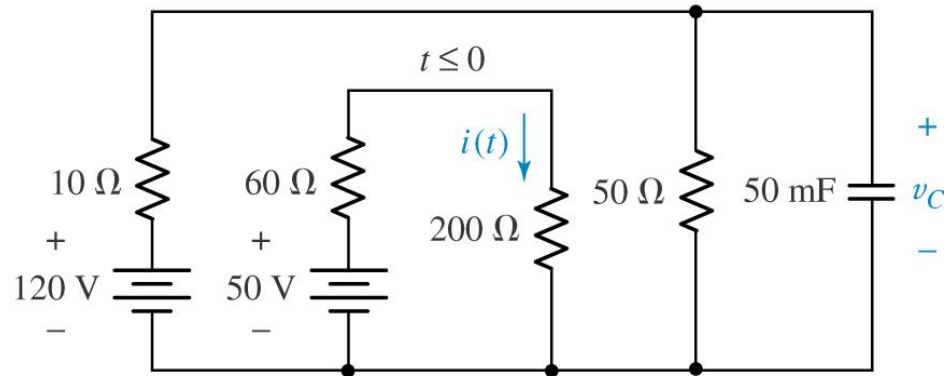


$$v_C(0^-) = \frac{50}{50 + 10} \cdot 120 = 100 = v_C(0^+)$$

$$i(0^-) = \frac{50}{260} = 192.3 \text{ mA}$$
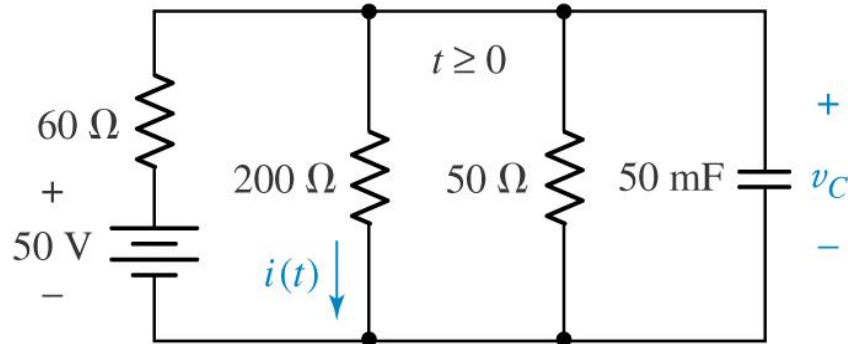
# Driven RC Circuits: Example


Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the 200- $\Omega$  resistor of the circuit shown in (a).



$$R_{eq} = 60 // 200 // 50$$

$$= \frac{1}{\frac{1}{60} + \frac{1}{200} + \frac{1}{50}} = 24\Omega$$
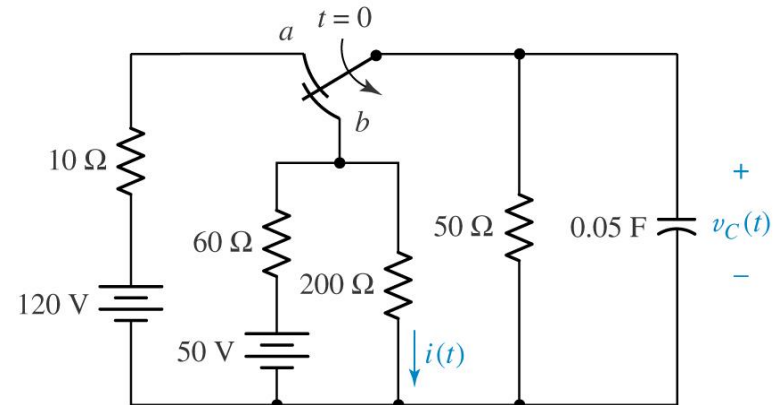
$$v_{Cf} = \frac{50 \times 200 / (50 + 200)}{60 + 50 \times 200 / (50 + 200)} \cdot 50 = 20V.$$



$$v_C(t) = v_{Cf} + v_{Cn}$$

$$v_{Cn}(t) = Ae^{\frac{-t}{R_{eq}C}} = Ae^{\frac{-t}{1.2}}$$

# Driven RC Circuits: Example

Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the 200- $\Omega$  resistor of the circuit shown in (a).


$$\therefore v_C(t) = 20 + Ae^{\frac{-t}{1.2}}$$

To find A, @t=0;

$$v_C(0^+) = v_C(0^-) = 100 = 20 + A$$


$$\therefore A = 80$$

$$; v_C(t) = 20 + 80e^{\frac{-t}{1.2}}$$

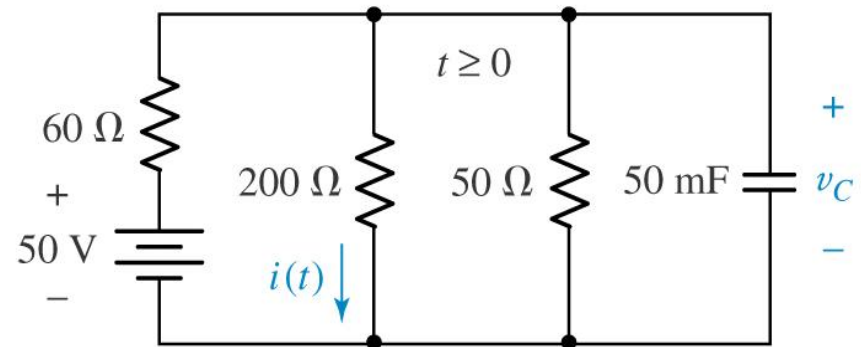
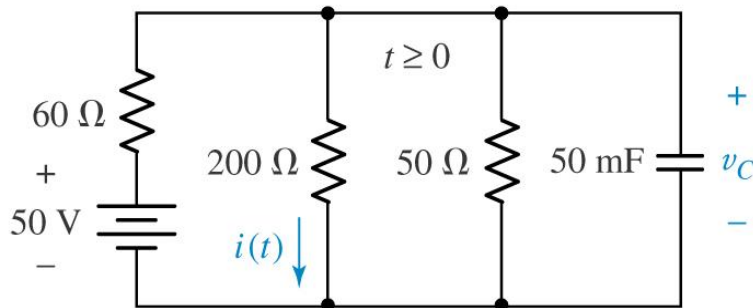
# Driven RC Circuits: Example

Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the 200- $\Omega$  resistor of the circuit shown in (a).



$$i(0^+) = \frac{v_C(0^+)}{200} = \frac{100}{200} = 0.5A.$$

$$i_f = i(t = \infty) = \frac{50}{60 + \frac{50 \times 200}{50 + 200}} \cdot \frac{50}{50 + 200} = 0.1A.$$

$$\therefore i(t) = i_f + i_n(t) = 0.1 + Ae^{\frac{-t}{1.2}}$$

To find A, @t=0;


$$i(0^+) = 0.5 = 0.1 + A$$

$$\therefore A = 0.4$$


$$\therefore i(t) = 0.1 + 0.4e^{\frac{-t}{1.2}}, t > 0$$
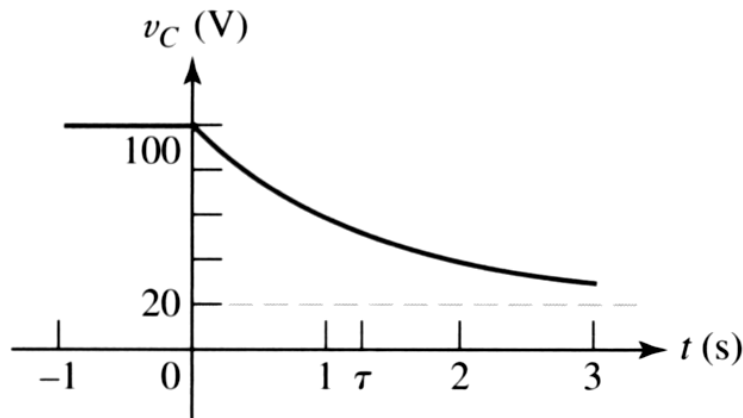
# Driven RC Circuits: Example


Find the capacitor voltage  $v_C(t)$  and the current  $i(t)$  in the  $200\text{-}\Omega$  resistor of the circuit shown in (a).



(a)

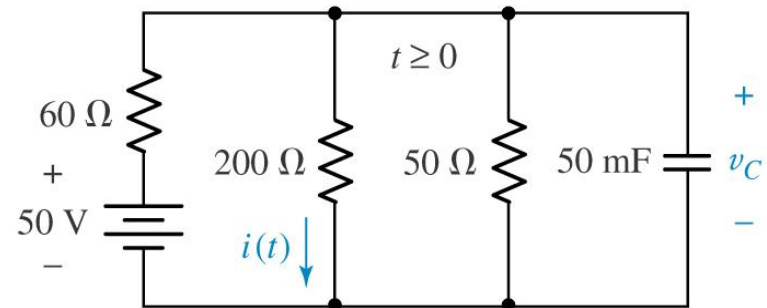

$$v_C(t) = 20 + 80e^{\frac{-t}{1.2}}$$

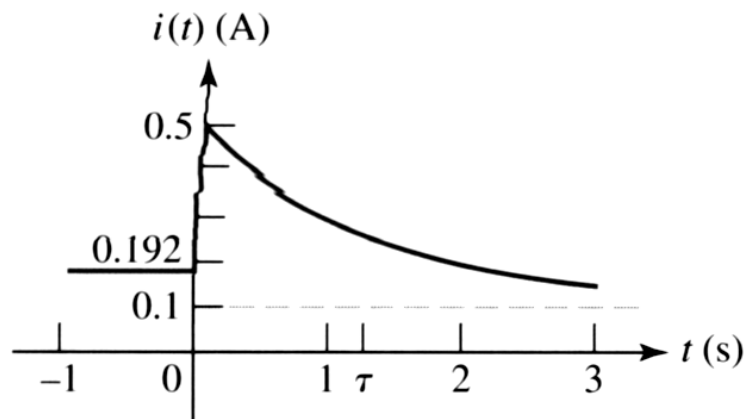


(b)


$$i(t) = 0.1 + 0.4e^{\frac{-t}{1.2}}$$
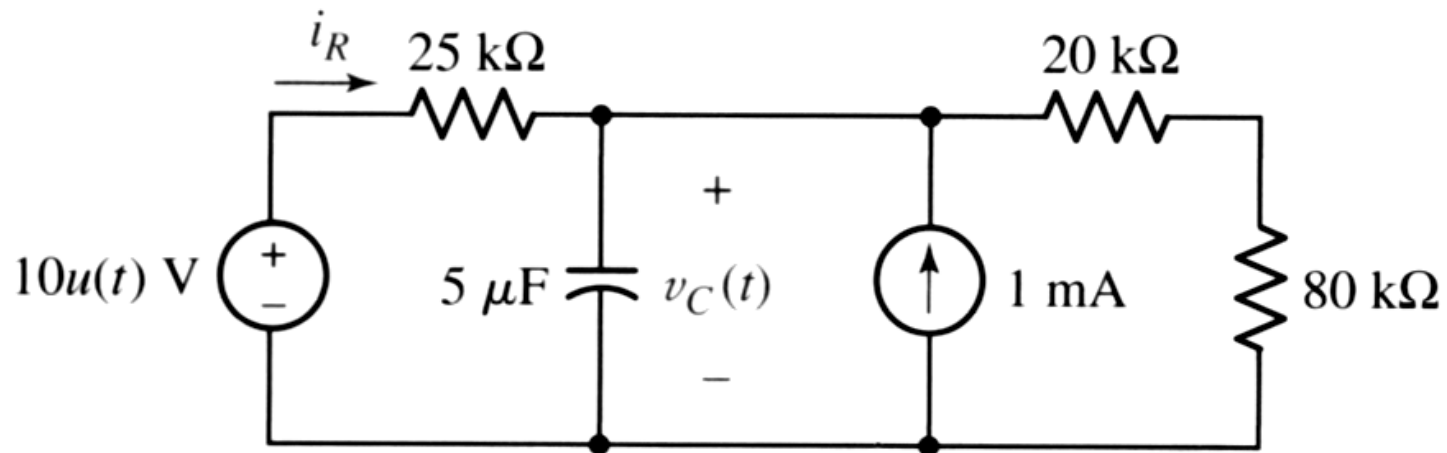
# Practice: 8.10

For the circuit, find  $v_C(t)$  at  $t$  equal to (a)  $0^-$ ; (b)  $0^+$ ; (c)  $\infty$ ; (d) 0.08 s.



# Practice: 8.10

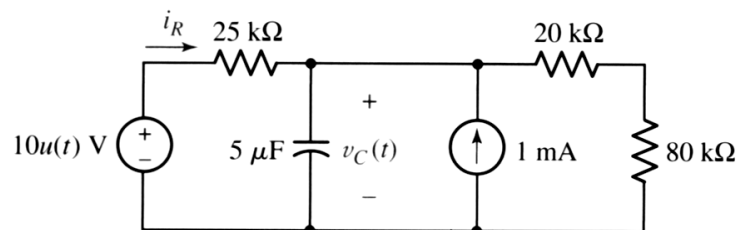

(a) At  $t = 0^-$ , only the current source is on, so

$$v_C(0^-) = 1 \times [25 // (20 + 80)] = \underline{20\text{ V}}$$

(b)  $v_C(0^+) = v_C(0^-)$ , so  $v_C(0^+) = \underline{20\text{ V}}$

(c) At  $t = \infty$ , both sources are on, so

$$\begin{aligned} v_C(\infty) &= 1 \times [25 // (20 + 80)] + 10 \times \frac{(100)}{125} \\ &= 20 + 8 = \underline{28\text{ V}} \end{aligned}$$

$$(d) \quad v_C(t) = v_C(\infty) + [v_C(0^+) - v_C(\infty)]e^{-t/\tau}$$

where  $\tau = R_{eq} C$

$$R_{eq} = 25 // 100 = 20\text{ k}\Omega, \text{ so } \tau = 100\text{ ms}$$

$$\begin{aligned} \text{Thus, } v_C(80\text{ ms}) &= 28 + [20 - 28]e^{-80/100} \\ &= \underline{24.41\text{ V}} \end{aligned}$$



# Summary :

---

1. With all independent sources killed, simplify the circuit to determine  $R_{eq}$ ,  $C_{eq}$  and the time constant  $\tau = R_{eq}C_{eq}$ .
2. Viewing  $C_{eq}$  as an open circuit, use dc analysis methods to find  $v_C(0^-)$  the capacitor voltage just prior to the discontinuity.
3. Again viewing  $C_{eq}$  as an open circuit, use dc analysis methods to find the forced response. This is the value approached by  $f(t)$  as  $t \rightarrow \infty$ ; we represent it by  $f(\infty)$ .
4. Write the total response as the sum of the forced and natural responses:  $f(t) = f(\infty) + Ae^{-t/\tau}$ .
5. Find  $f(0^+)$  by using the condition that  $v_C(0^+) = v_C(0^-)$ . If desired,  $C_{eq}$  may be replaced by a voltage source  $v_C(0^+)$  [a short circuit if  $v_C(0^+) = 0$ ] for this calculation. With the exception of capacitor voltages (and inductor currents), other currents and voltages in the circuit may change abruptly.
6.  $f(0^+) = f(\infty) + A$  and  $f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-t/\tau}$ , or total response = final value + (initial value — final value)  $e^{-t/\tau}$ .

**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**