



Seat No. : \_\_\_\_\_

**King Mongkut's University of Technology Thonburi**  
**Final Exam of Second Semester, Academic Year 2016**

CPE 223 Digital System Design  
Monday 8 May 2017

CPE(Inter.) Students  
13.00-16.00

**Instructions**

1. This examination contains 7 problems, 8 pages (including this cover page),  
The total score is 40 points.
2. The answers must be written in the space provided.
3. **No calculator, book, note, and dictionary** allowed in the exam room.

**Students must raise their hand to inform to the proctor upon their completion of the examination, to ask for permission to leave the examination room.**

**Students must not take the examination and the answers out of the examination room.**

**Students will be punished if they violate any examination rules. The highest punishment is dismissal.**

This examination is prepared by

Asst. Prof. Sanan Srakaew  
Tel. 0-2470-9083


This examination paper is approved by Computer Engineering Department.

Assoc. Prof. Dr. Natasha Dejdumrong  
Head of Curriculum

Problem	1	2	3	4	5	6	7	Total
Points	4	5	3	6	6	6	10	40
Earned Points								

Student Name: \_\_\_\_\_ I.D.: \_\_\_\_\_

1. In Figure 1, a 4-to-1-line multiplexer circuit.

 

**Figure 1:** A 4-to-1-line multiplexer circuit.

(a) Write a Verilog module using gate-level design(structural Verilog) (2 points)

(b) Rewrite a Verilog module in (a) using behavioral model. (2 points)

2.

(a) Sketch a full adder circuit using AND, OR, and XOR gates. (1 point)

(b) Write a full adder gate-level Verilog module, namely **full\_adder**. (2 points)

(c) Write a 4-bit full adder Verilog module, namely **adder\_4bit**, using **full\_adder**. (2 points)

3. Given a dataflow Verilog module below:

```
module fun(A,B,D, En);  
  
    input A, B;  
    output [3:0] D;  
    input En;  
  
    assign D[0] = !((!A) && (!B) && (!En)),  
           D[1] = !(!A) && B && (!En),  
           D[2] = !(A && (!B) && (!En))  
           D[3] = !(A && B && (!En));  
endmodule
```

Draw a NAND-gate-only circuit to represent the Verilog module above. (3 points)

4. Write a Verilog code to implement an 8-bit 4-to-1 multiplexer.

(6 points)

**module** mux\_4\_to\_1 (a, b, c, d, out, out\_bar, sel);


input [7:0] \_\_\_\_\_

output \_\_\_\_\_

input [1:0] sel;

**endmodule**

5. Given a 4-bit binary ripple counter circuit using D flip-flops shown in Figure 2 below:

 

**Figure 2:** A 4-bit binary ripple counter using D flip-flops.

- (a) Write a Verilog module of D flip-flop. (2 points)

```

module DFF (D, Clock, clear, q, qbar);
    input  D, Clock, clear;
    output reg q;
    output qbar;


```

**endmodule**

- (b) Using DFF module above, write a Verilog module to implement the 4-bit binary ripple counter. (2 points)

- (c) Rewrite the 4-bit binary ripple counter Verilog module using behavioral model. (2 points)

6. From a simple BCD counter given in Figure 3 below:

 

**Figure 3.** A simple BCD counter.

Write BCD counter and BCD to 7-segment Verilog behavioral modules. Assume the common anode 7-segment display is used. (6 points)

7. What is your Final project name? Draw a block diagram of the top module of your Final project. Pick one module in the top module and write a Verilog code for that module. (10 points)