
ENE 104

Electric Circuit Theory



Lecture 07: The RLC Circuit

Week #8 : Dejwoot KHAWPARISUTH

office: CB40906 Tel: 02-470-9065

Email: dejwoot.kha@mail.kmutt.ac.th

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

- the characteristic damping factor and resonant frequency for both series and parallel RLC circuits
- overdamped, critically damped, and underdamped response
- the complete response
- op amps


The Source-Free parallel Circuit:

The natural response:

$$i(0^+) = I_0$$

$$v(0^+) = V_0$$

The nodal equation:

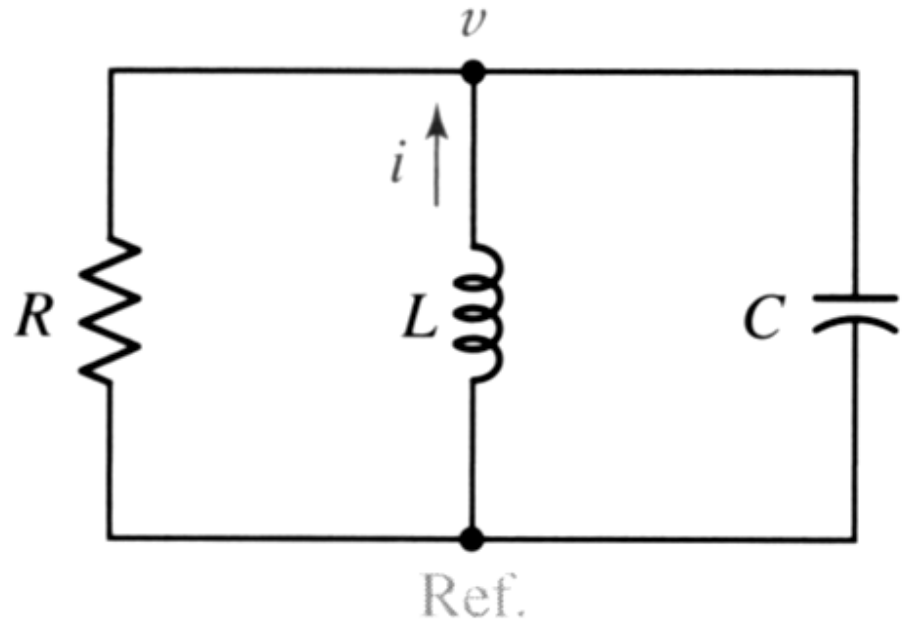

$$\frac{v}{R} + \frac{1}{L} \int_{t_0}^t v dt' - i(t_0) + C \frac{dv}{dt} = 0$$

$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$


The Solution:

Assume: $v = Ae^{st}$

Then, $CA s^2 e^{st} + \frac{1}{R} A s e^{st} + \frac{1}{L} A e^{st} = 0$

Or, $A e^{st} \left(C s^2 + \frac{1}{R} s + \frac{1}{L} \right) = 0$

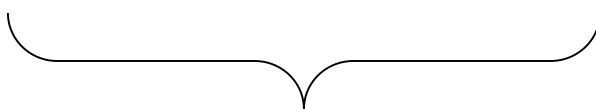So, $\left(C s^2 + \frac{1}{R} s + \frac{1}{L} \right) = 0$



the characteristic equation

The Solution:

Two solutions: $\left(Cs^2 + \frac{1}{R}s + \frac{1}{L} \right) = 0$

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \longrightarrow \quad v_1 = A_1 e^{s_1 t}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \quad \longrightarrow \quad v_2 = A_2 e^{s_2 t}$$

Satisfies,

$$C \frac{d^2 v_1}{dt^2} + \frac{1}{R} \frac{dv_1}{dt} + \frac{1}{L} v_1 = 0$$

$$C \frac{d^2 v_2}{dt^2} + \frac{1}{R} \frac{dv_2}{dt} + \frac{1}{L} v_2 = 0$$

The Solution:

$$\left. \begin{aligned} C \frac{d^2 v_1}{dt^2} + \frac{1}{R} \frac{dv_1}{dt} + \frac{1}{L} v_1 &= 0 \\ C \frac{d^2 v_2}{dt^2} + \frac{1}{R} \frac{dv_2}{dt} + \frac{1}{L} v_2 &= 0 \end{aligned} \right\} \quad C \frac{d^2 (v_1 + v_2)}{dt^2} + \frac{1}{R} \frac{d(v_1 + v_2)}{dt} + \frac{1}{L} (v_1 + v_2) = 0$$

the general form of the natural response:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Definition of Frequency Terms:

$$v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} \left\{ \begin{array}{l} s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \\ s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} \end{array} \right.$$

the resonant frequency: $\omega_0 = \frac{1}{\sqrt{LC}}$

the neper frequency, or
the exponential damping coefficient: $\alpha = \frac{1}{2RC}$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Practice: 9.1

A parallel RLC circuit contains a $100\text{-}\Omega$ resistor and has the parameter values $\alpha = 1000\text{ s}^{-1}$ and $\omega_0 = 800\text{ rad/s}$. Find: (a) C ; (b) L ; (c) s_1 ; (d) s_2

$$\alpha = 1000\text{ s}^{-1} \text{ and } \omega_0 = 800\text{ rad/s, with } R = 100\text{ }\Omega.$$

$$(a) \quad \alpha = \frac{1}{2RC} \quad \text{so} \quad C = \frac{1}{2R\alpha} = \underline{5\mu\text{F}}$$

$$(b) \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{so} \quad L = \frac{1}{C\omega_0^2} = \underline{312.5\text{ mH}}$$

$$(c) \quad s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = \underline{-400\text{ s}^{-1}}$$

$$(d) \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = \underline{-1600\text{ s}^{-1}}$$

The Overdamped Parallel RLC:

$$\alpha > \omega_0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$


if $LC > 4R^2C^2$

then $\sqrt{\alpha^2 - \omega_0^2} < \alpha$

$$\left(-\alpha - \sqrt{\alpha^2 - \omega_0^2}\right) < \left(-\alpha + \sqrt{\alpha^2 - \omega_0^2}\right) < 0$$

Both s_1 and s_2 are negative real number

Example:

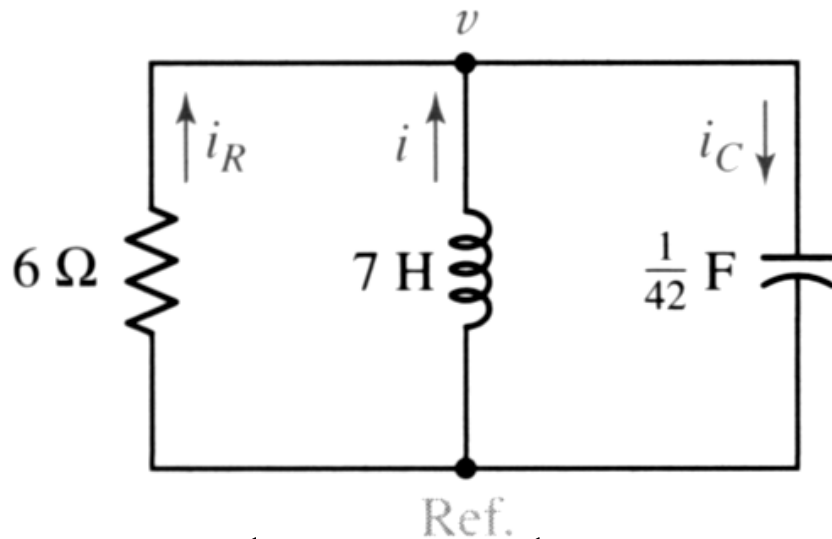

The initial conditions:

$$i(0) = 10A.$$

$$v(0) = 0$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 6 \cdot \frac{1}{42}} = 3.5, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{7 \cdot \frac{1}{42}}} = \sqrt{6}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -3.5 \pm \sqrt{3.5^2 - 6} = -1, -6$$

$$v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

Example: Finding A_1 and A_2

$$v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

At $t = 0$,

The initial conditions:

$$i(0) = 10 \text{ A.}$$

$$v(0) = 0 \text{ V.}$$

$$v(0) = 0 = A_1 + A_2 \dots (*) \quad \Rightarrow \quad x(0) = A_1 + A_2 \dots (*)$$

And evaluating the derivative at $t = 0^+$,

$$\frac{dv}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = -A_1 - 6A_2 \dots (**)$$

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0^+} = A_1 s_1 + A_2 s_2 \dots (**)$$

Example: Finding A_1 and A_2

$$v(t) = A_1 e^{-t} + A_2 e^{-6t}$$

$$v(0) = 0 = A_1 + A_2 \dots (*)$$

$$\left. \frac{dv}{dt} \right|_{t=0} = -A_1 - 6A_2 \dots (**)$$

From $i_C(t) = C \frac{dv_C(t)}{dt}$


$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(t=0^+)}{C} = \frac{i(0^+) + i_R(0^+)}{C} = \frac{10 + 0}{\frac{1}{42}} = 420 \text{ V/s.}$$

$$420 = -A_1 - 6A_2 \dots (**)$$

$$\Rightarrow A_1 = 84, A_2 = -84$$

$$\therefore v(t) = 84e^{-t} - 84e^{-6t} = 84(e^{-t} - e^{-6t})$$

Graphical Representation:

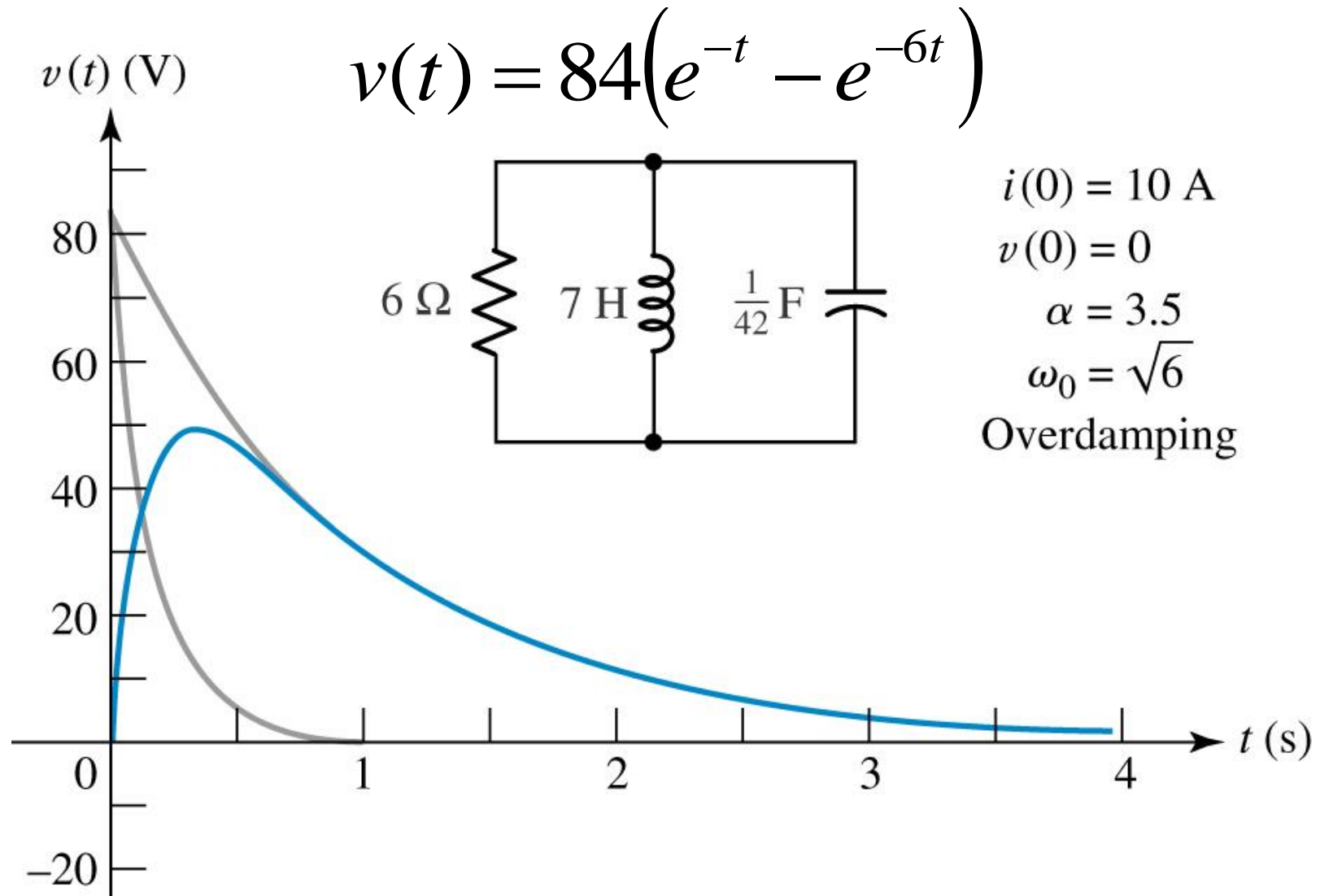

The response of the parallel network shown.

The settling time:

$$v(t) = 84(e^{-t} - e^{-6t})$$


To determine maximum:

$$\frac{dv}{dt} = 84(-e^{-t} + 6e^{-6t}) = 0$$

$$-e^{-t_m} + 6e^{-6t_m} = 0$$



$$\Rightarrow t_m = 0.358 \text{ s.}$$

$$\Rightarrow v(t_m) = 48.9 \text{ V.}$$

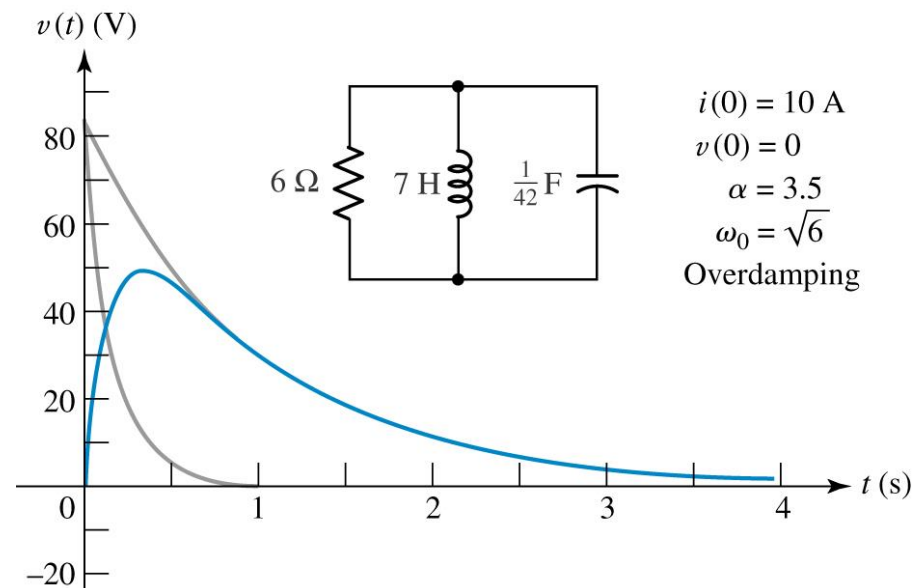

The settling time, t_s , is the time required for the response to drop to 1% ($t_s = 5.15 \text{ s.}$)

Example: find $v_C(t)$

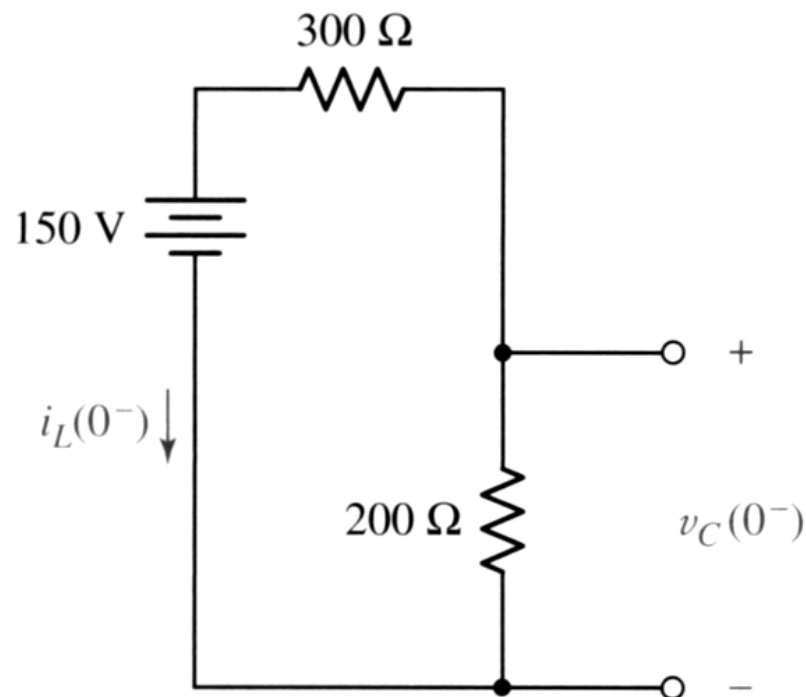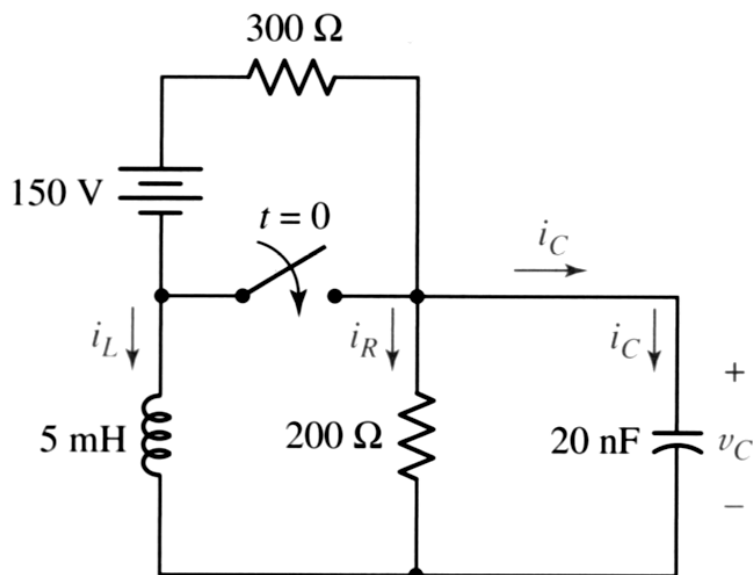


For $t < 0$, find the initial conditions;

$$i_L(0^-) = \frac{-150}{300\Omega + 200\Omega} = -0.3 \text{ A.} = i_L(0^+)$$

$$v_C(0^-) = -i_L(0^-) \cdot 200\Omega = 60 \text{ V.} = v_C(0^+)$$


Example:

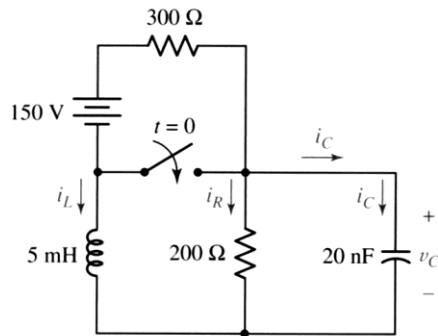


The initial conditions:

$$i_L(0^-) = i_L(0^+) = -0.3 \text{ A.}$$

$$v_C(0^-) = v_C(0^+) = 60 \text{ V.}$$

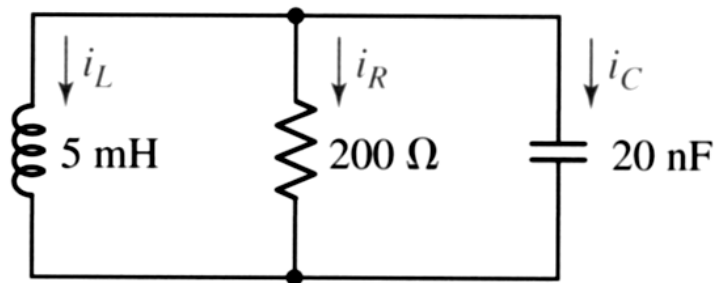

$$i_L(0^-) = i_L(0^+) = -0.3 \text{ A}$$

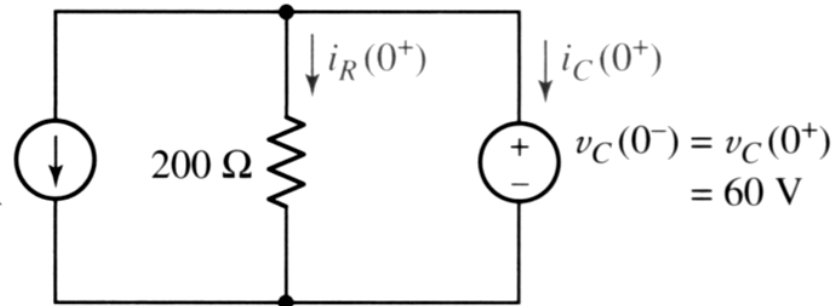

$$v_C(0^-) = v_C(0^+) = 60 \text{ V}$$

For $t > 0$;

$$\alpha = \frac{1}{2RC} = 125000 \text{ s}^{-1}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = 100000 \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -50000, \quad -200000 \text{ s}^{-1}$$

$$v_C(t) = A_1 e^{-50000t} + A_2 e^{-200000t}$$

Example: Finding A_1 and A_2

$$v_C(t) = A_1 e^{-50000t} + A_2 e^{-200000t}$$

The initial conditions:

$$\begin{aligned} i_L(0^-) &= i_L(0^+) = -0.3 \text{ A.} \\ v_C(0^-) &= v_C(0^+) = 60 \text{ V.} \end{aligned}$$

At $t = 0$,

$$\Rightarrow x(0) = A_1 + A_2 \dots (*) \quad v_C(0^+) = 60 = A_1 + A_2 \dots (*)$$

And evaluating the derivative at $t = 0$,

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0^+} = A_1 s_1 + A_2 s_2 \dots (**)$$

$$\left. \frac{dv_C}{dt} \right|_{t=0^+} = -50000A_1 - 200000A_2 \dots (**)$$

Example: Finding A_1 and A_2

$$v(t) = A_1 e^{-50000t} + A_2 e^{-200000t}$$

The initial conditions:

$$\begin{aligned} i_L(0^-) &= i_L(0^+) = -0.3 \text{ A.} \\ v_C(0^-) &= v_C(0^+) = 60 \text{ V.} \end{aligned}$$

From $i_C(t) = C \frac{dv_C(t)}{dt}$


$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{-i_L(0^+) - i_R(0^+)}{C} = \frac{0.3 - 60/200\Omega}{20 \times 10^{-9}} = 0$$

$$0 = -50000A_1 - 200000A_2 \dots (**)$$

$$\Rightarrow A_1 = 80, A_2 = -20$$

$$\therefore v_C(t) = 80e^{-50000t} - 20e^{-200000t} \text{ V.}, t > 0$$

Practice: 9.2 find ...

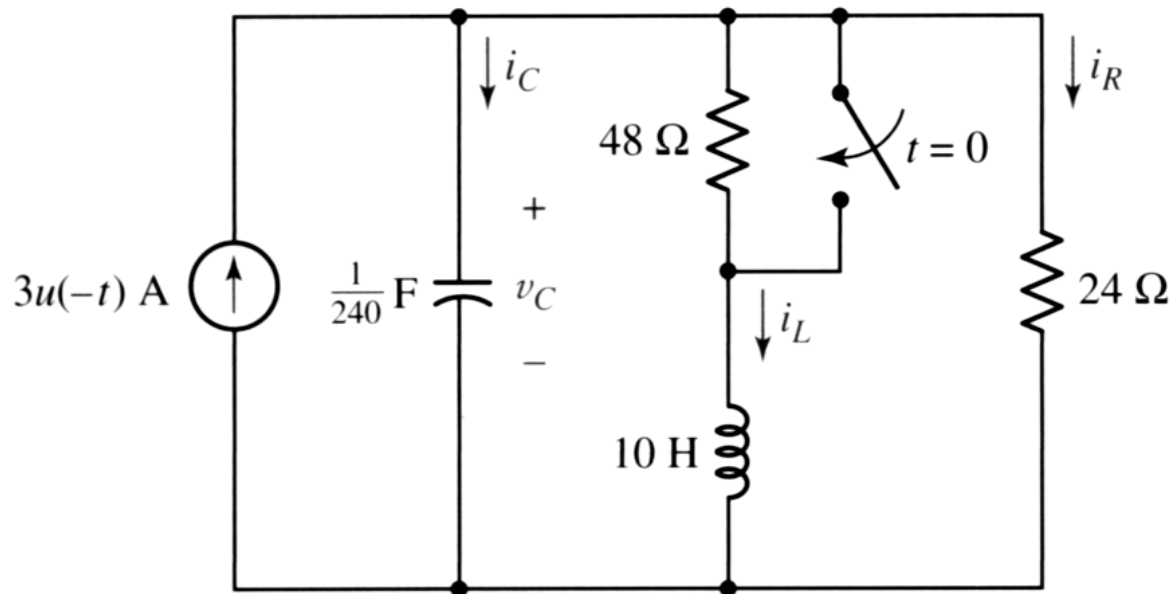

$$i_L(0^-) = \dots \text{ A.}$$


$$i_R(0^+) = \dots \text{ A.}$$

$$v_C(0.2) = \dots \text{ V.}$$

$$v_C(0^-) = \dots \text{ V.}$$

$$i_C(0^+) = \dots \text{ A.}$$



Practice : find ...

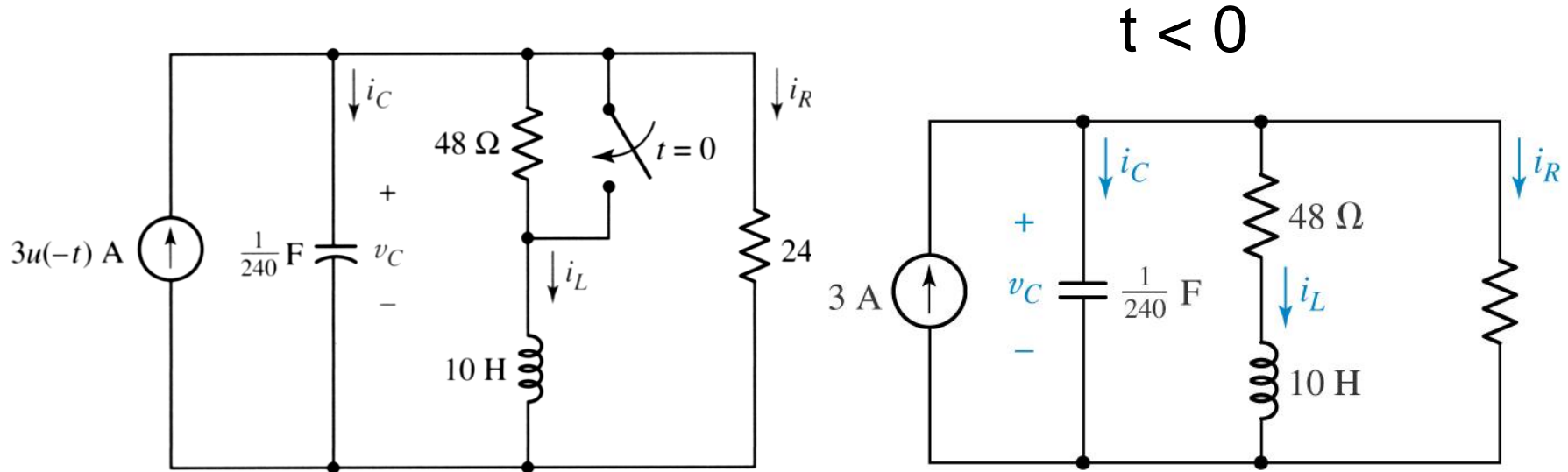

$$i_L(0^-) = 3 \cdot \frac{24\Omega}{24\Omega + 48\Omega} = 1 \quad \text{A.}$$

$$v_C(0^-) = i_L(0^-) \cdot 48\Omega = 48 \quad \text{V.}$$

Practice : find ...

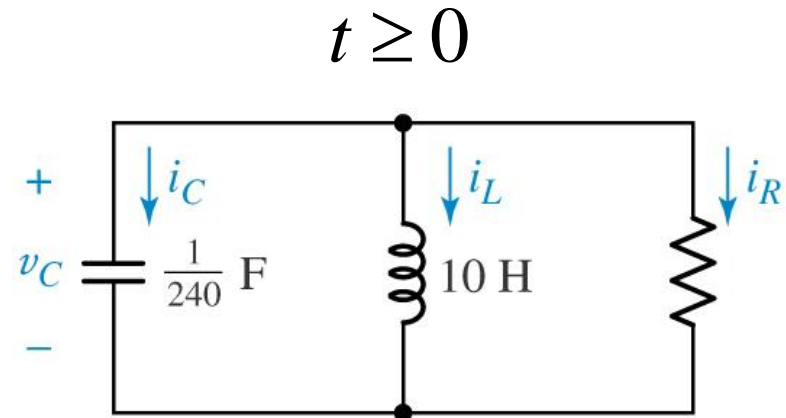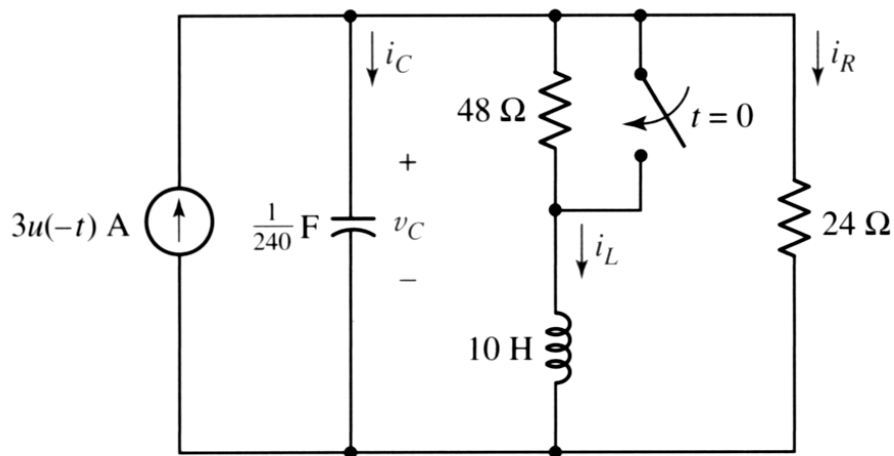


$$i_R(0^+) = \frac{v_C(0^+)}{24\Omega} = 2 \quad \text{A.}$$

$$i_C(0^+) = -i_R(0^+) - i_L(0^+) = -2 - 1 = -3 \quad \text{A.}$$

$$v_C(0.2) = \dots \quad \text{V.}$$

Practice : find $v_C(t=0.2)$

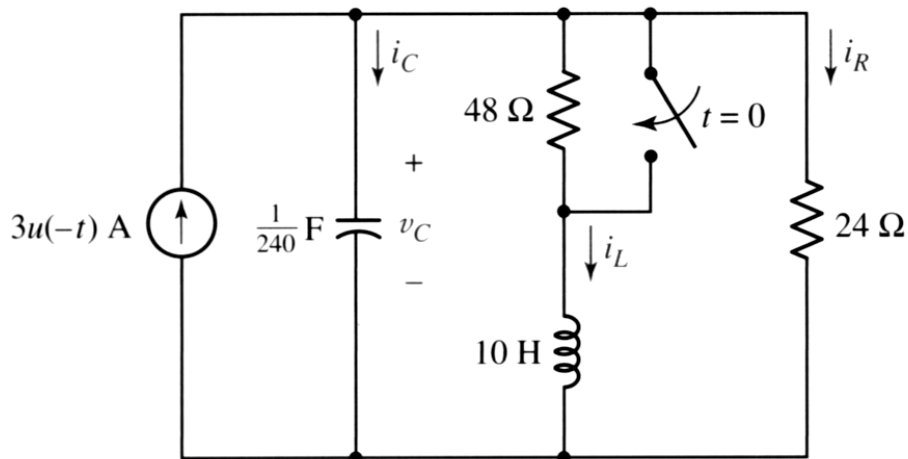

The initial conditions:

$$i_L(0^-) = i_L(0^+) = 1 \text{ A.}$$

$$v_C(0^-) = v_C(0^+) = 48 \text{ V.}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 24\Omega \cdot \frac{1}{240}F} \text{ s}^{-1}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10H \cdot \frac{1}{240}F}} \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} \text{ s}^{-1}$$

Critical Damping:

$$\alpha = \omega_0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

or $LC = 4R^2C^2$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

thus $s_1 = s_2$

$$\alpha = \frac{1}{2RC}$$

$$C \frac{d^2v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

Becomes: $\frac{d^2v}{dt^2} + 2\alpha \frac{dv}{dt} + \alpha^2 v = 0$

The solution: \Rightarrow

$$v(t) = e^{-\alpha t} (A_1 t + A_2)$$

Critical Damping :

$$\alpha = \frac{1}{2RC} = \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{7H \cdot \frac{1}{42}F}} = \sqrt{6} \text{ rad/s}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha = -\sqrt{6}$$


$$v(t) = e^{-\sqrt{6}t} (A_1 t + A_2)$$

The initial conditions:

$$i(0) = 10 \text{ A.}$$

$$v(0) = 0 \text{ V.}$$
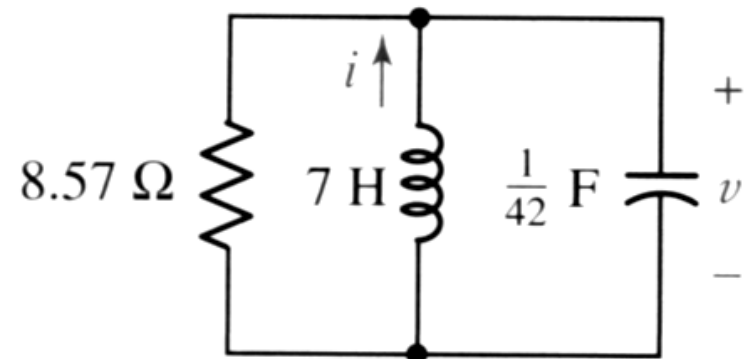
$$6\Omega \rightarrow \frac{7\sqrt{6}}{2} \cong 8.57\Omega$$



Critical Damping :

$$v(t) = e^{-\sqrt{6}t} (A_1 t + A_2)$$

At $t = 0$,


$$v(0) = 0 = A_2 \dots (*)$$

$$\Rightarrow x(0) = A_2 \dots (*)$$

The initial conditions:

$$i(0) = 10 \text{ A.}$$

$$v(0) = 0 \text{ V.}$$

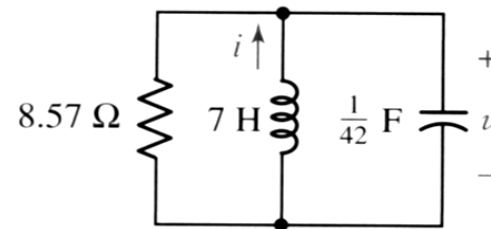

And evaluating the derivative at $t = 0$,

$$\frac{dv}{dt} = -A_1 t (-\sqrt{6}) e^{-\sqrt{6}t} + A_1 e^{-\sqrt{6}t}$$


$$\left. \frac{dv}{dt} \right|_{t=0} = A_1 \dots (**)$$

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = A_1 - \alpha A_2 \dots (**)$$

Critical Damping: Finding A_1 and A_2

$$v(t) = e^{-\sqrt{6}t} (A_1 t + A_2) \quad v(0) = 0 = A_2 \dots (*)$$

From $i_C(t) = C \frac{dv_C(t)}{dt}$

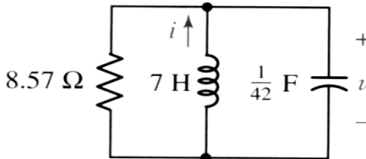


$$\left. \frac{dv}{dt} \right|_{t=0} = A_1 \dots (**)$$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(t=0^+)}{C} = \frac{i(0^+) + i_R(0^+)}{C} = \frac{10 + 0}{1/42} = 420 \text{ V/s.}$$

$$420 = A_1 \dots (**)$$


$$\therefore v(t) = 420te^{-\sqrt{6}t} \text{ V.}$$

Critical Damping :

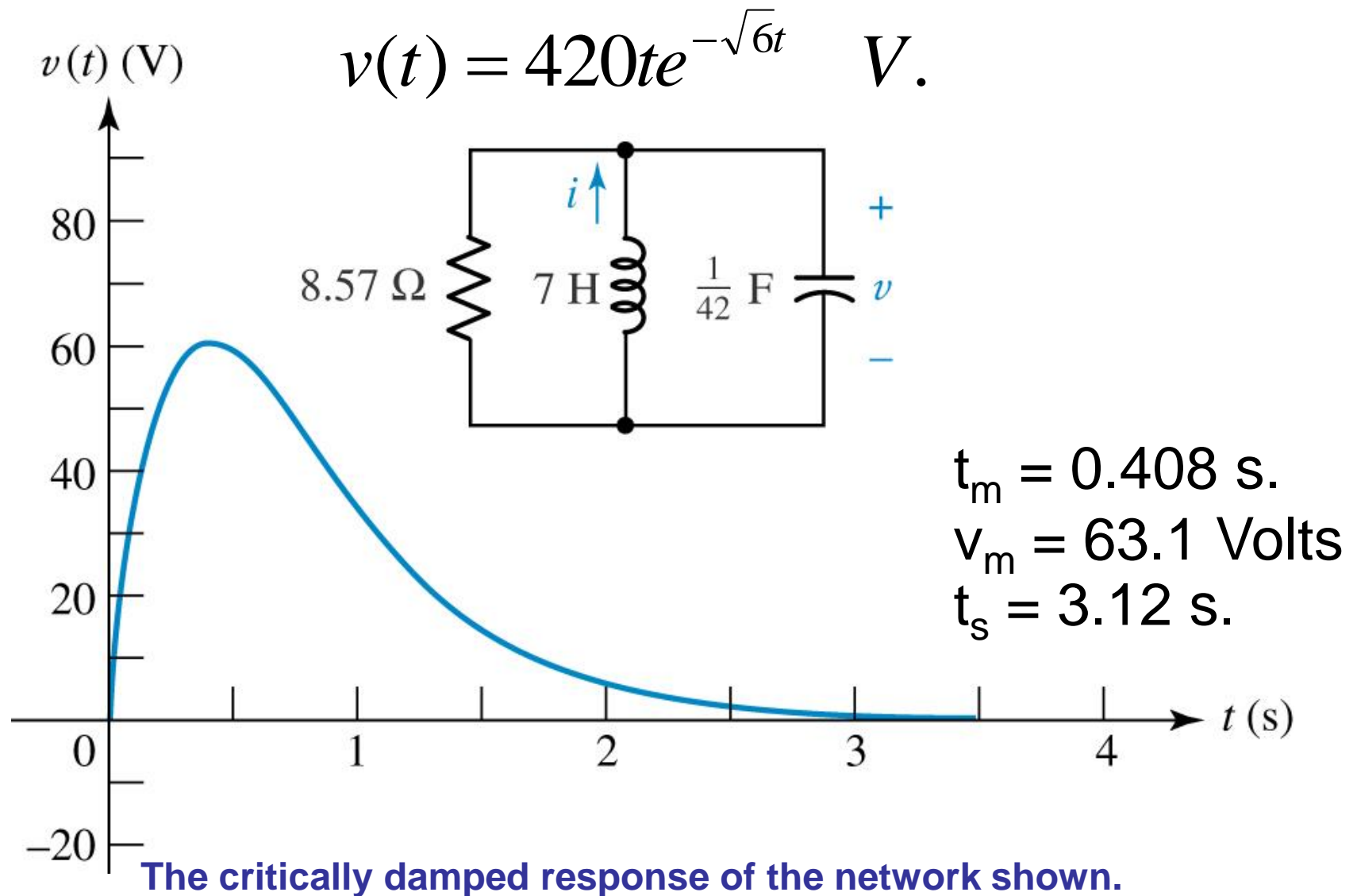


Practice: 9.3

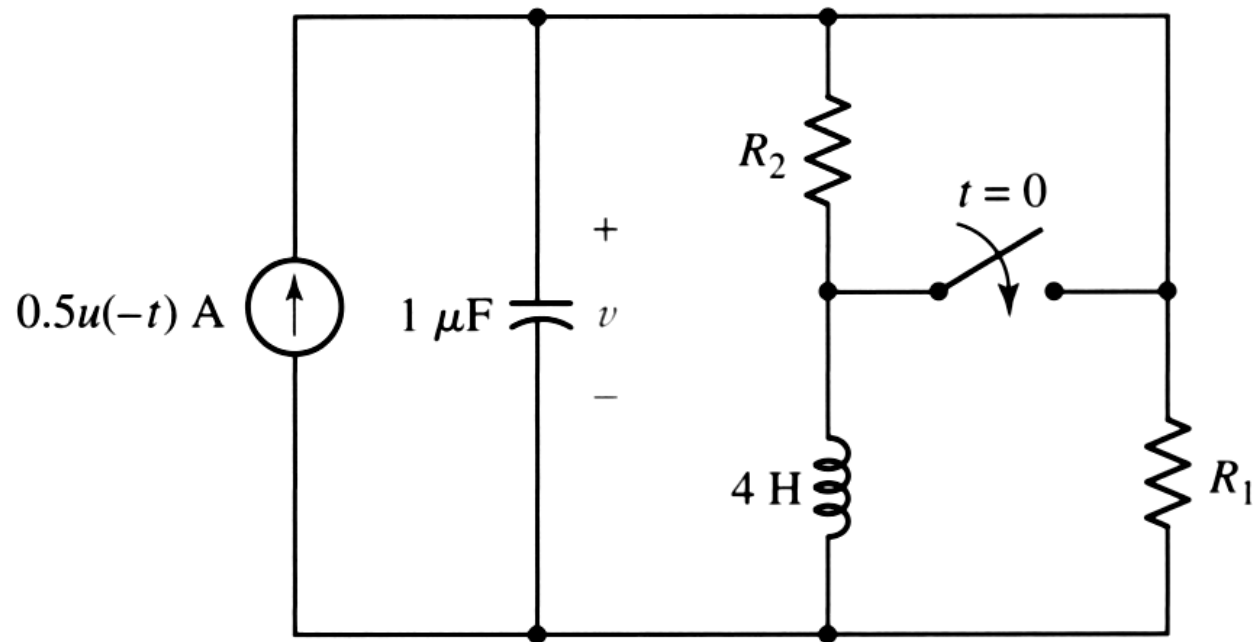- Choose R_1 so that the response after $t = 0$ will be critically damped
- Select R_2 to obtain $v(0) = 100$ V.
- Find $v(t)$ at $t = 1$ ms.



Practice :

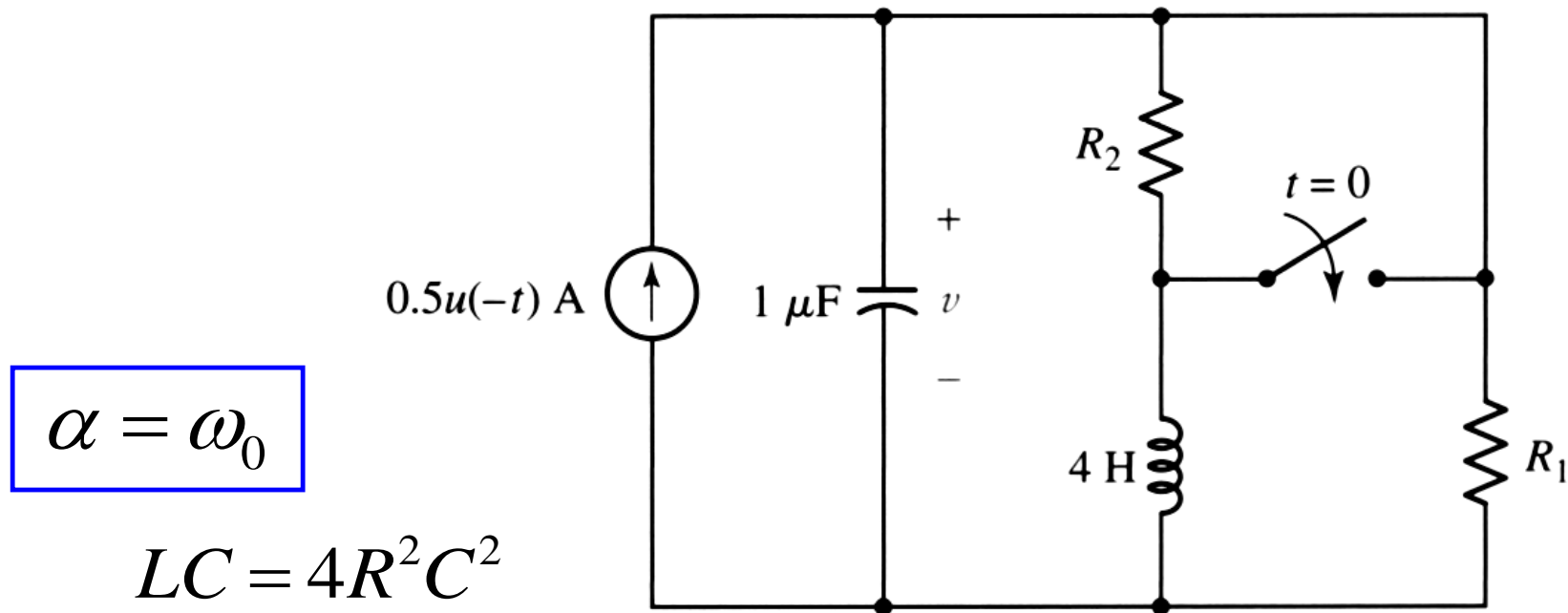
- Choose R_1 so that the response after $t = 0$ will be critically damped



$$\therefore R_1 = \sqrt{\frac{L}{4C}} = \sqrt{\frac{4H}{4 \cdot 1 \times 10^{-6} F}} = 1 \text{ k}\Omega$$

Practice :

- Select R_2 to obtain $v(0) = 100$ V.

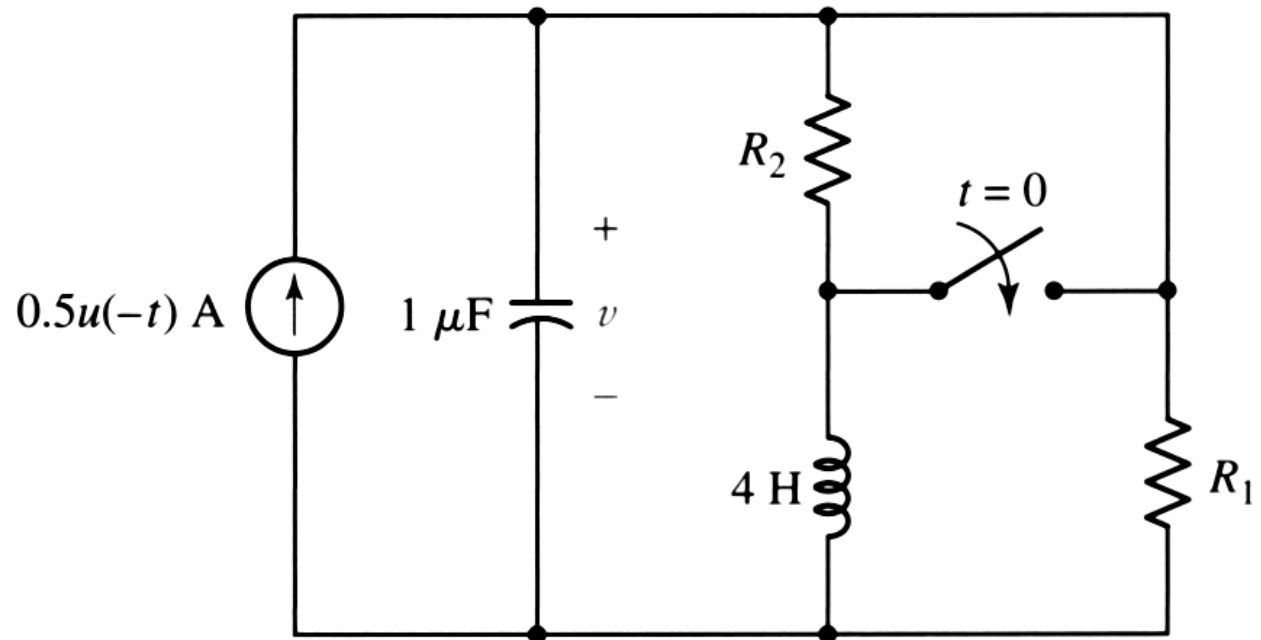

$$(0.5 \text{ A}) \cdot \left(\frac{R_1}{R_1 + R_2} \right) R_2 = 100 \text{ V.} \quad ; R_1 = 1 \text{ k}\Omega$$

$$\Rightarrow R_2 = 250 \text{ } \Omega$$

The Underdamped Parallel RLC:

$$\alpha < \omega_0$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Then let $\sqrt{\alpha^2 - \omega_0^2} = \sqrt{-1} \cdot \sqrt{\omega_0^2 - \alpha^2} = j\sqrt{\omega_0^2 - \alpha^2}$

the natural resonant frequency: $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$

$$\begin{aligned} v(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) \\ &= e^{-\alpha t} [(A_1 + A_2) \cos \omega_d t + j(A_1 - A_2) \sin \omega_d t] \end{aligned}$$

$$\therefore v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

Example: Underdamped

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \cdot 10.5\Omega \cdot \frac{1}{42}F} = 2 \quad s^{-1}, \quad \omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{6} \quad rad/s$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{6 - 2^2} = \sqrt{2} \quad rad/s$$

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$


$$\therefore v(t) = e^{-2t} (B_1 \cos \sqrt{2}t + B_2 \sin \sqrt{2}t)$$

The initial conditions:

$$i(0) = 10 \quad A.$$

$$v(0) = 0 \quad V.$$

$$8.57\Omega \rightarrow 10.5\Omega$$

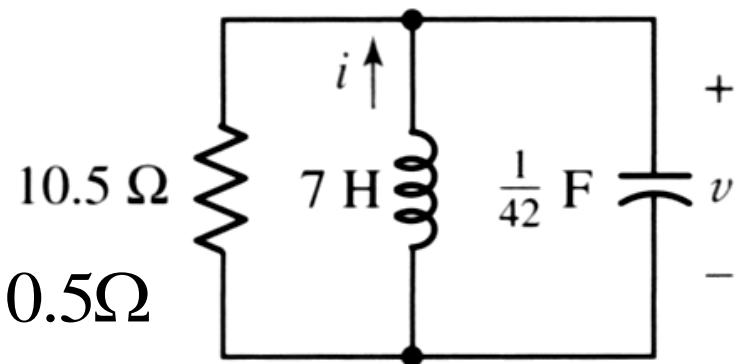

Example: Underdamped

$$v(t) = e^{-2t} (B_1 \cos \sqrt{2}t + B_2 \sin \sqrt{2}t)$$

At $t = 0$,


$$v(0) = 0 = B_1 \dots (*)$$

$$\Rightarrow x(0) = B_1 \dots (*)$$

The initial conditions:

$$i(0) = 10 \text{ A.}$$

$$v(0) = 0 \text{ V.}$$

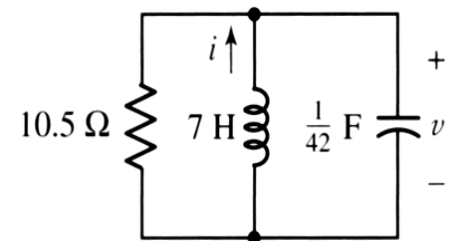

And evaluating the derivative at $t = 0$,

$$\frac{dv}{dt} = \sqrt{2}B_2 e^{-2t} \cos \sqrt{2}t - 2B_2 e^{-2t} \sin \sqrt{2}t$$

$$\left. \frac{dv}{dt} \right|_{t=0} = \sqrt{2}B_2 \dots (**)$$


$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2 \dots (**)$$

Example: Underdamped

$$v(t) = e^{-2t} (B_1 \cos \sqrt{2}t + B_2 \sin \sqrt{2}t)$$

$$v(0) = 0 = B_1 \dots (*)$$

From
$$i_C(t) = C \frac{dv_C(t)}{dt}$$
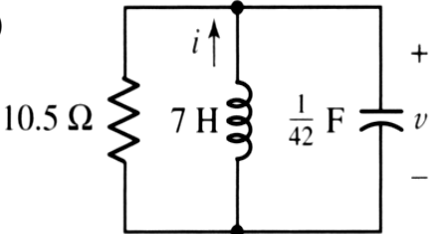
$$\left. \frac{dv}{dt} \right|_{t=0} = \sqrt{2} B_2 \dots (**)$$


$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(t=0^+)}{C} = \frac{i(0^+) + i_R(0^+)}{C} = \frac{10 + 0}{1/42} = 420 \text{ V/s.}$$


$$420 = \sqrt{2} B_2 \dots (**)$$

$$\Rightarrow B_1 = 0, B_2 = 210\sqrt{2}$$

$$\therefore v(t) = 210\sqrt{2}e^{-2t} \sin \sqrt{2}t \quad \text{V.}$$

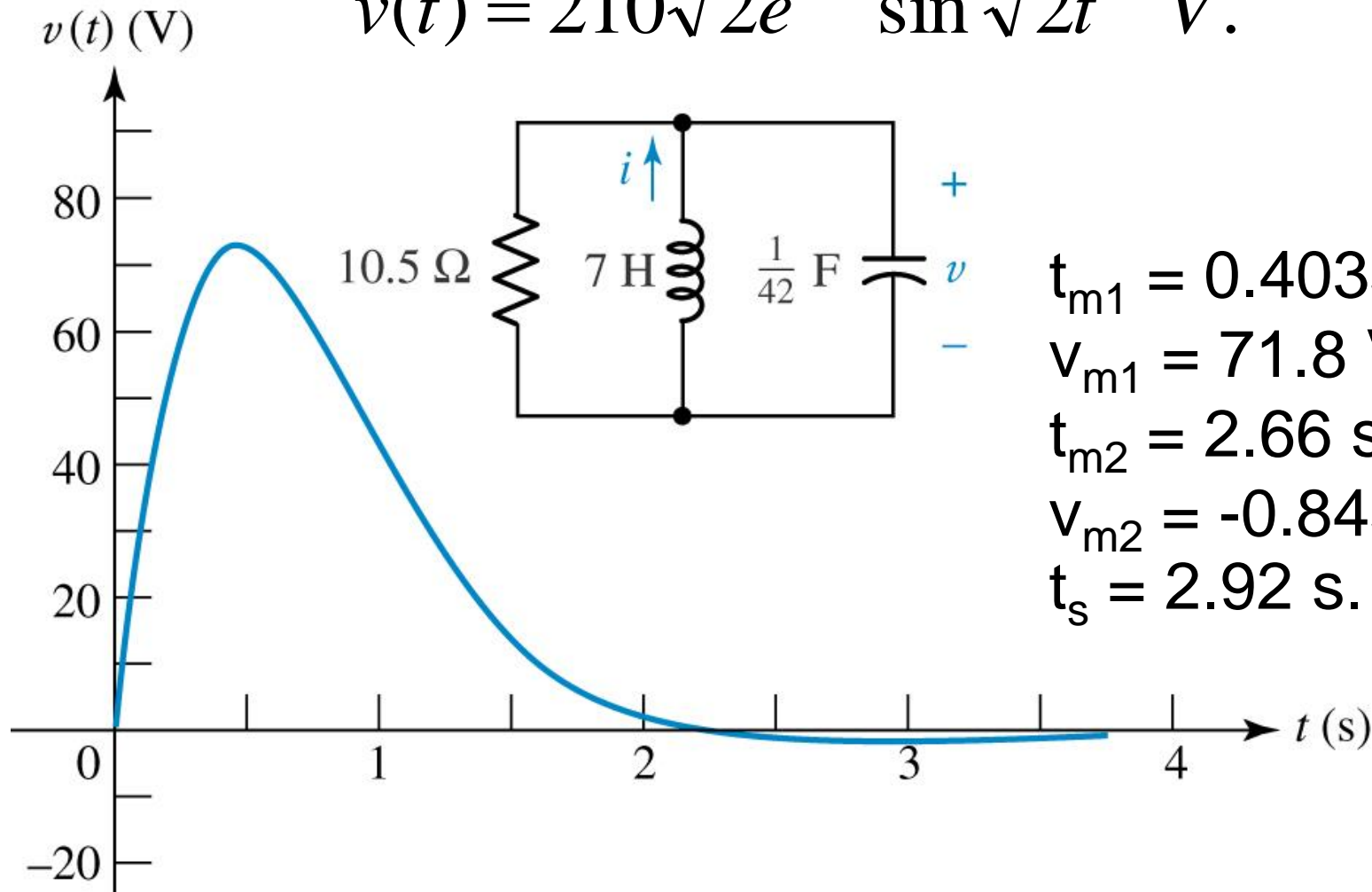Example: Underdamped


$$v(t) = 210\sqrt{2}e^{-2t} \sin \sqrt{2}t \quad \text{V.}$$



$$\begin{aligned} t_{m1} &= 0.4035 \text{ s.} \\ v_{m1} &= 71.8 \text{ Volts} \\ t_{m2} &= 2.66 \text{ s.} \\ v_{m2} &= -0.845 \text{ Volts} \\ t_s &= 2.92 \text{ s.} \end{aligned}$$


The underdamped response of the network shown.

Example:

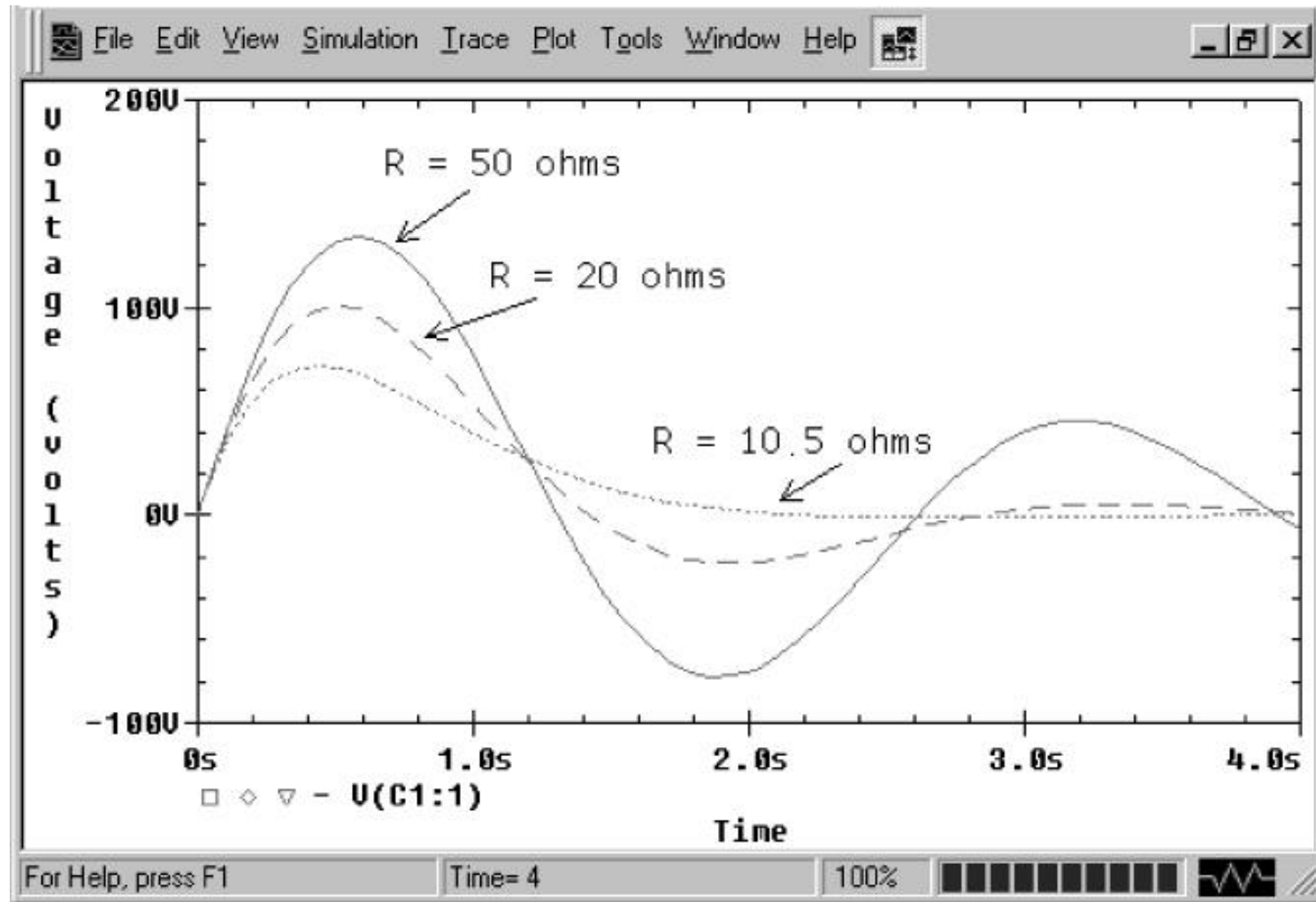




The response of the network for three different resistance values, showing an increase in the magnitude of oscillation.

Example:

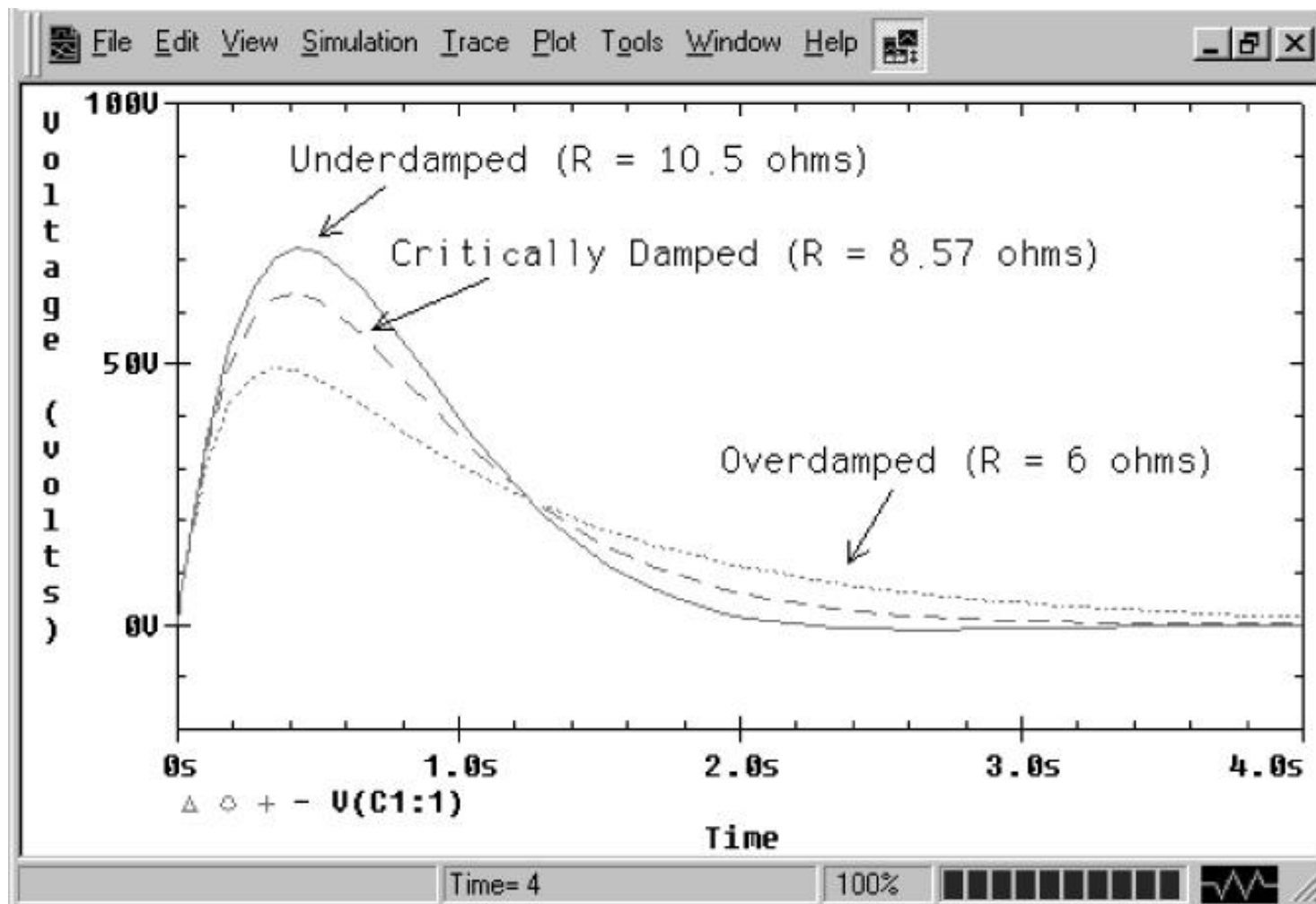


Simulated overdamped, critically damped, and underdamped voltage response for a parallel RLC network with $L = 7 \text{ H}$ and $C = 1/42 \text{ F}$.

Example: find $i_L(t)$

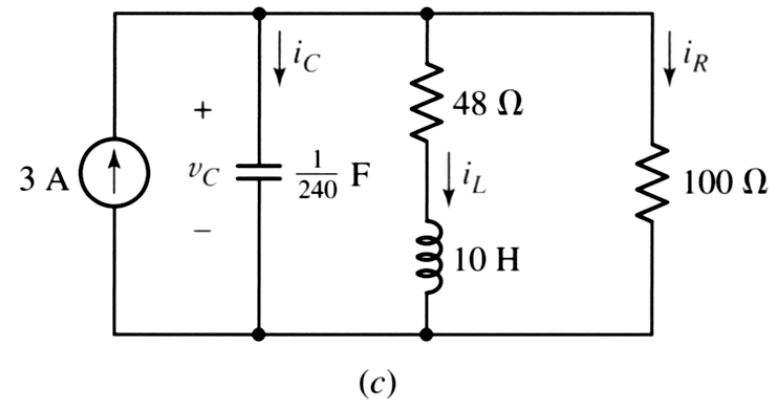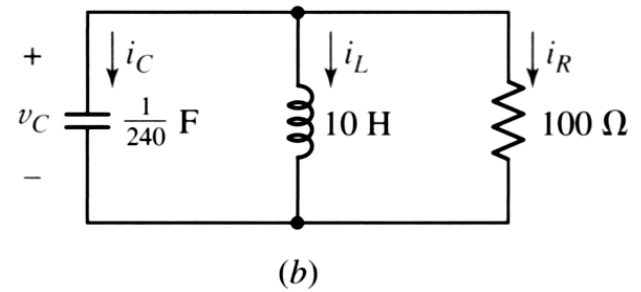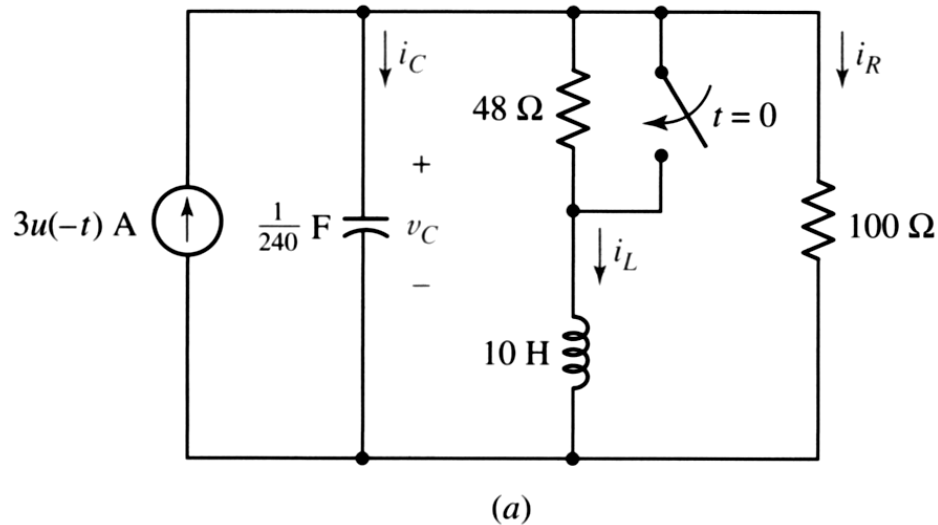

Example: find $i_L(t)$


Determine the initial conditions:

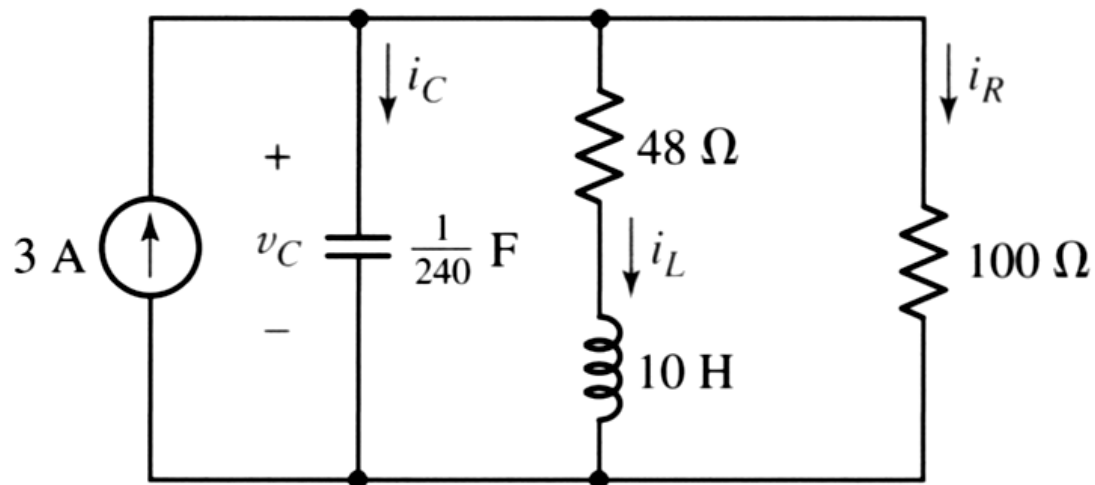

$$i_L(0^-) = 3 \cdot \frac{100\Omega}{48\Omega + 100\Omega} = 2.027 \text{ A.}$$

$$v_C(0^-) = i_L(0^-) \cdot 48\Omega = 97.30 \text{ V.}$$

Example: find $i_L(t)$

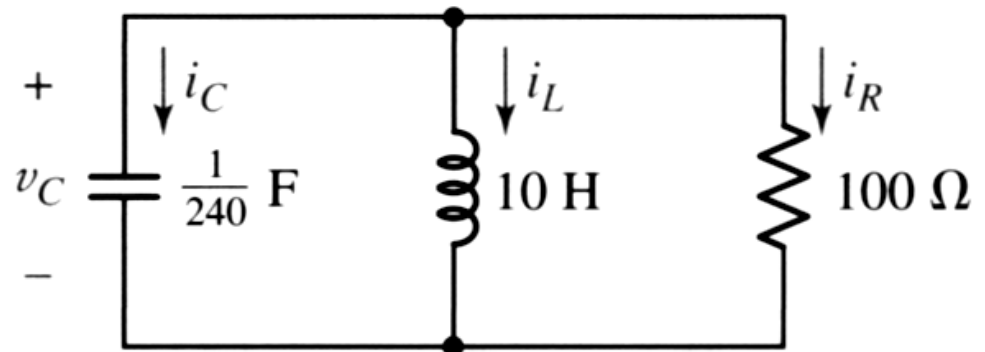

$$\begin{aligned}\alpha &= \frac{1}{2RC} \\ &= \frac{1}{2 \cdot 100 \Omega \cdot \frac{1}{240} \text{ F}} = 1.2 \text{ s}^{-1}\end{aligned}$$

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{10 \text{ H} \cdot \frac{1}{240} \text{ F}}} = 4.899 \text{ rad/s}\end{aligned}$$


$\alpha < \omega_0$

→
 $i_L(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$

Example: find $i_L(t)$

$$\alpha < \omega_0$$

An underdamped C/T

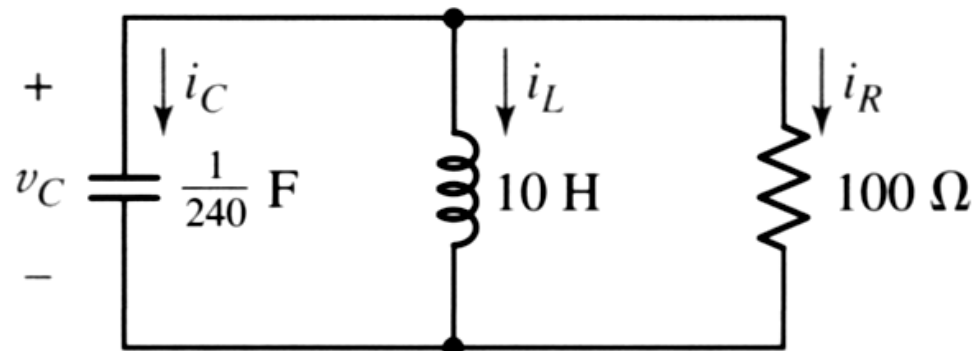

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 4.75 \text{ rad/s}$$

$$\longrightarrow i_L(t) = e^{-1.2t} (B_1 \cos 4.75t + B_2 \sin 4.75t)$$

At $t = 0$, $\Rightarrow x(0) = B_1 \dots (*)$; $B_1 = i_L(0^+) = 2.027$

And evaluating the derivative at $t = 0$,

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2 \dots (**)$$


Example: find $i_L(t)$

from $v_L(t) = L \frac{di_L}{dt}$


$$\left. \frac{di_L}{dt} \right|_{t=0^+} = -1.2B_1 + 4.75B_2 = \frac{v_L(0^+)}{L} = \frac{v_C(0^+)}{L} = \frac{97.3}{10H}$$

$$\therefore B_2 = 2.561$$

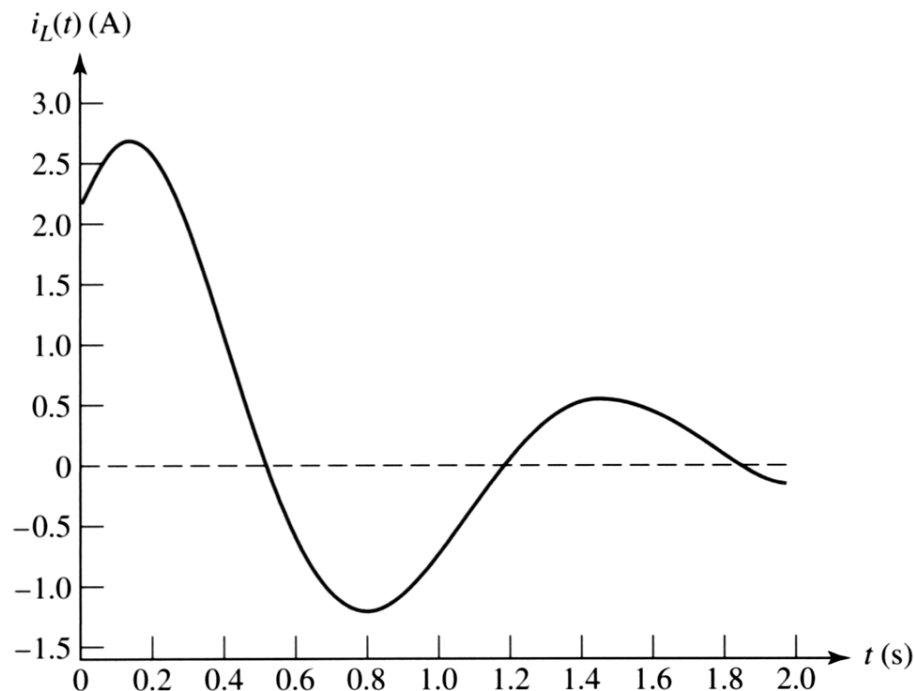→ $i_L(t) = e^{-1.2t} (2.027 \cos 4.75t + 2.561 \sin 4.75t) \quad \text{A.}$



Practice: 9.4

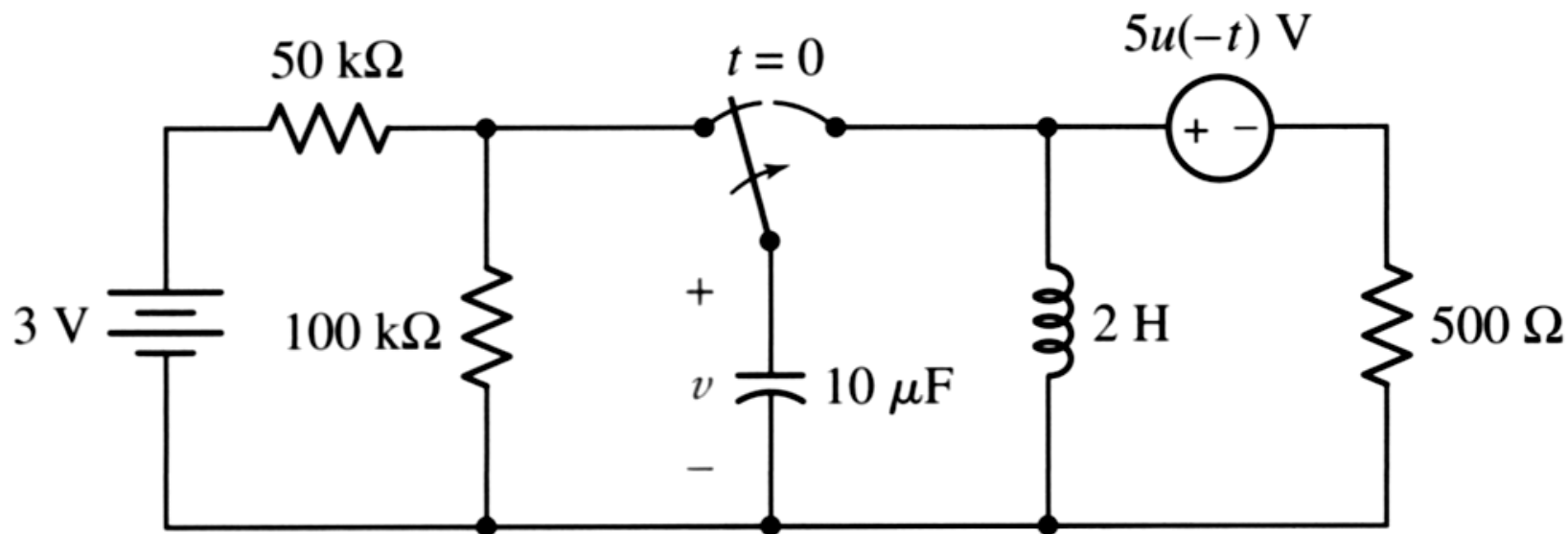


- Find
- $\frac{dv}{dt}$ at $t = 0^+$
 - $v(t)$ at $t = 1$ ms.
 - t_0 , the first value of t greater than zero at which $v = 0$

Practice :

From

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

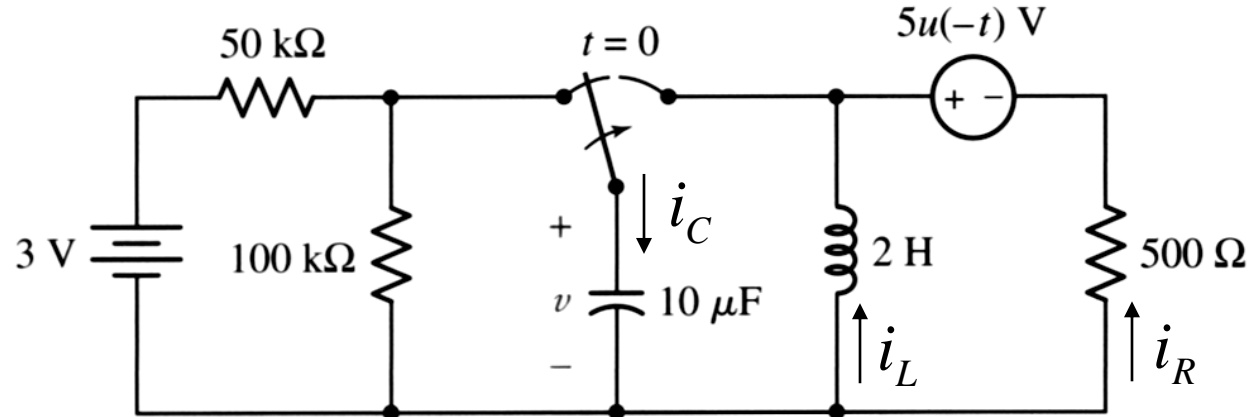

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(t=0^+)}{C} = \frac{i_L(0^+) + i_R(0^+)}{C} = \frac{i_L(0^-) + i_R(0^+)}{C} \text{ V/s.}$$

$$i_L(0^-) = \frac{-5 \text{ V}}{500 \Omega} = -0.01 \text{ A.}$$

$$i_R(0^+) = \frac{-v_C(0^+)}{500 \Omega} = \frac{-v_C(0^-)}{500 \Omega} = \frac{-2 \text{ V}}{500 \Omega} = -0.004 \text{ A.}$$

$$\longrightarrow \left. \frac{dv}{dt} \right|_{t=0^+} = -1400 \text{ V/s.}$$


Practice : $v(t=1\text{ms.})$

$$\alpha = \frac{1}{2RC}$$

$$= \frac{1}{2 \cdot 500\Omega \cdot 10\mu F} = 100 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
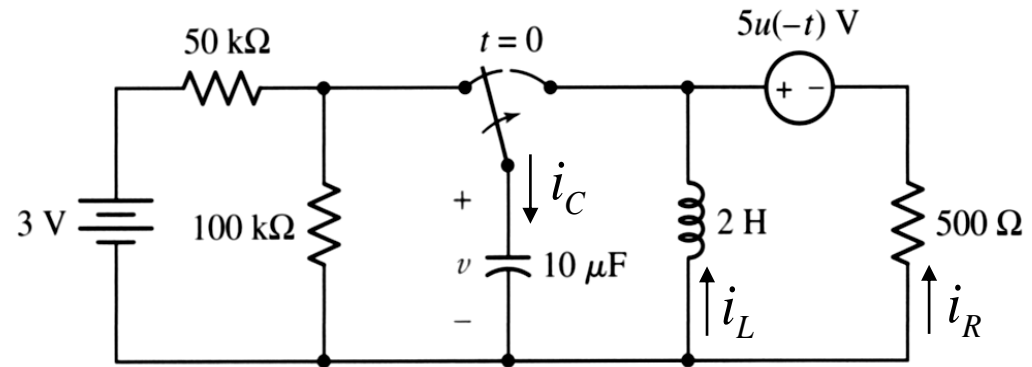
$$= \frac{1}{\sqrt{2H \cdot 10\mu F}} = 223.6 \text{ rad/s}$$




$\alpha < \omega_0$

→

$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

Practice : $v(t=1\text{ms.})$

$$\alpha < \omega_0$$

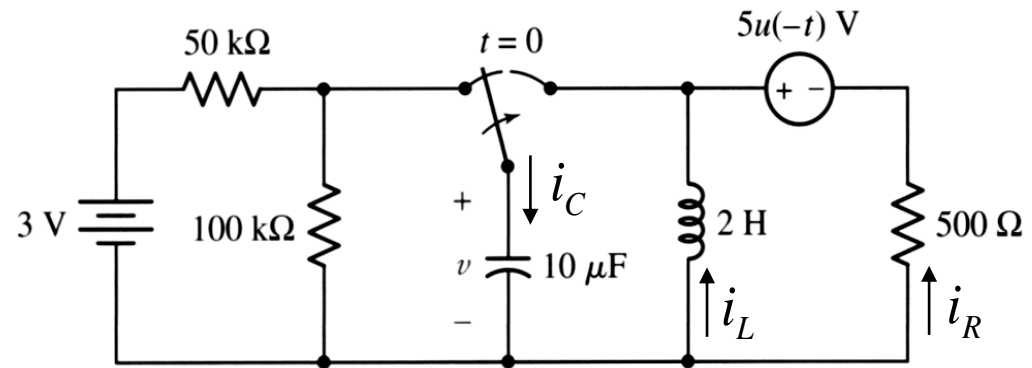

An underdamped C/T

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 200 \text{ rad/s}$$

$$\longrightarrow v(t) = e^{-100t} (B_1 \cos 200t + B_2 \sin 200t)$$

$$\text{At } t = 0, \Rightarrow x(0) = B_1 \dots (*) \quad ; B_1 = v(0^+) = 2$$

And evaluating the derivative at $t = 0$,

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2 \dots (**)$$

Practice : $v(t=1\text{ms.})$

$$v(t) = e^{-100t} (B_1 \cos 200t + B_2 \sin 200t) \quad ; B_1 = 2$$

From $i_C(t) = C \frac{dv_C(t)}{dt}$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = -1400 = -100B_1 + 200B_2 \quad \Rightarrow B_2 = -6$$

$$\Rightarrow v(t) = e^{-100t} (2 \cos 200t - 6 \sin 200t)$$

$$\therefore v(t = 1\text{ms.}) = 0.695 \quad V.$$

Homework:

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.

Copyright ©2002 McGraw-Hill. All rights reserved.