

---

ENE 104

# Electric Circuit Theory

---



## Lecture 02: Voltage and Current Laws

---

**Week #2 : Dejwoot KHAWPARISUTH**

office: CB40906 Tel: 02-470-9065

Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>


# Objectives :

---

- Definition of nodes, paths, loops, and branches
- Kirchhoff's current law (KCL)
- Kirchhoff's voltage law (KVL)
- Analyzing simple series and parallel circuits
- Simplify series and parallel connected sources
- Reducing series and parallel resistor combinations
- Voltage and current division


# Nodes, Paths, Loops, and Branches: <sup>Page 3</sup>

---

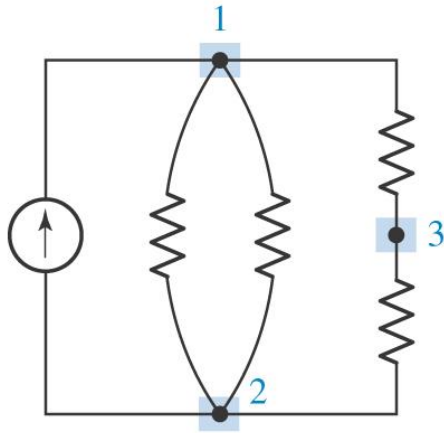

(a)

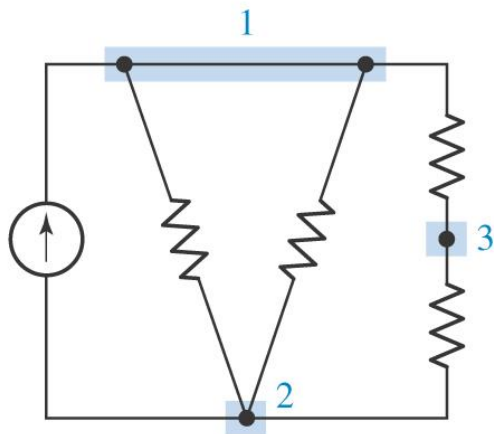(a) A circuit containing three **nodes** and five **branches**.




(b)

(b) Node 1 is redrawn to look like two nodes; it is still one node.
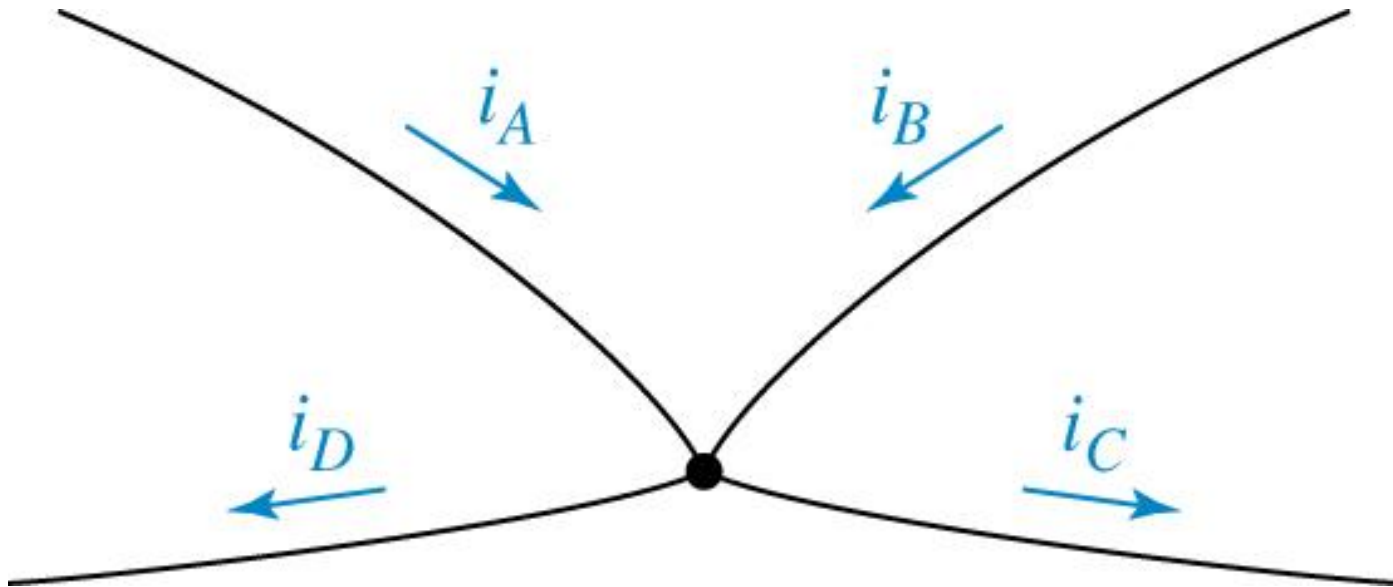
# Kirchoff's Current Law (KCL):


---

The algebraic sum of the currents entering any node is zero



# Kirchoff's Current Law (KCL):

---

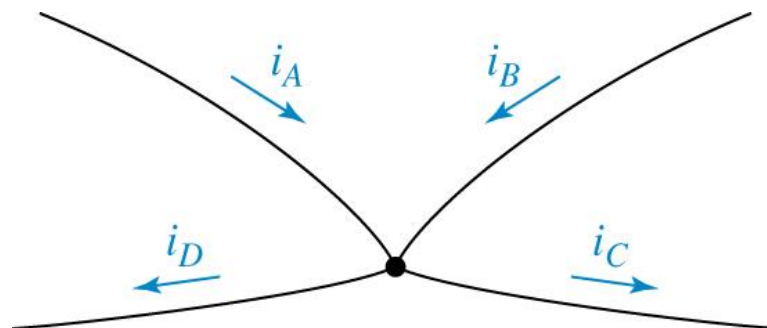


Entering the node:  $i_A + i_B + (-i_C) + (-i_D) = 0$

Leaving the node:  $(-i_A) + (-i_B) + i_C + i_D = 0$

Or:  $i_A + i_B = i_C + i_D$

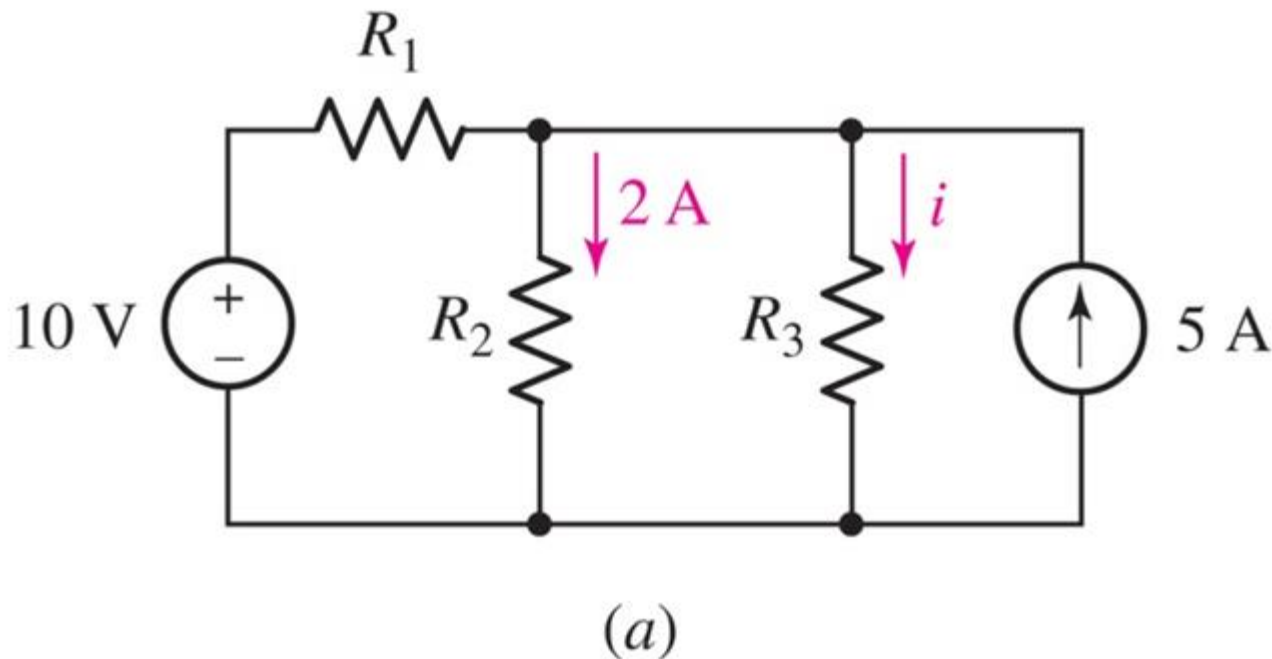
# Example: 3.1

Compute the **current through resistor  $R_3$**  if it is known that the voltage source supplies a current of 3 A.


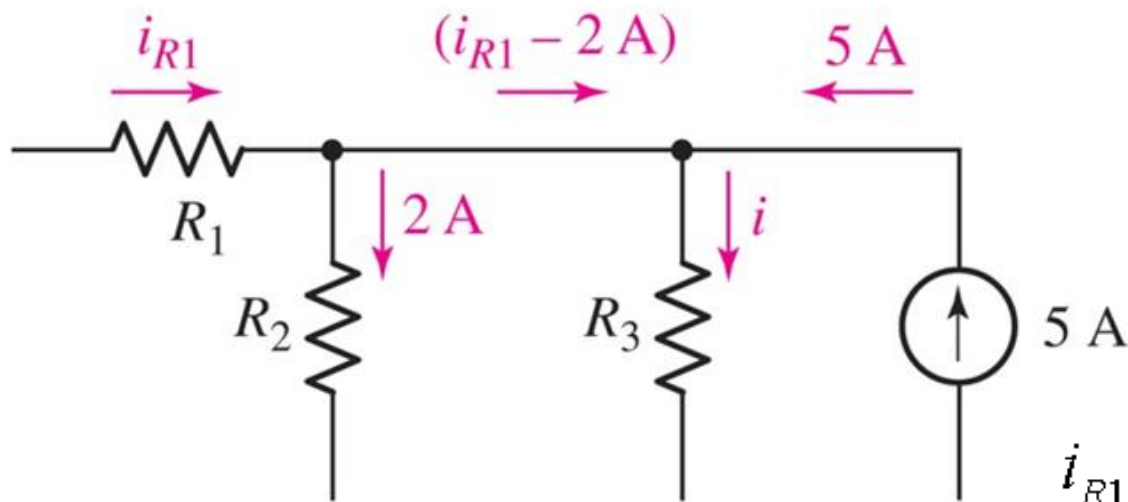
# Example:


Compute the current through resistor  $R_3$  if it is known that the voltage source supplies a current of 3 A.



$$i_{R1} + 5A. = i + 2A.$$

$$\begin{aligned}\therefore i &= i_{R1} + 5A. - 2A. \\ &= 3A. + 5A. - 2A.\end{aligned}$$

# Practice: 3.1

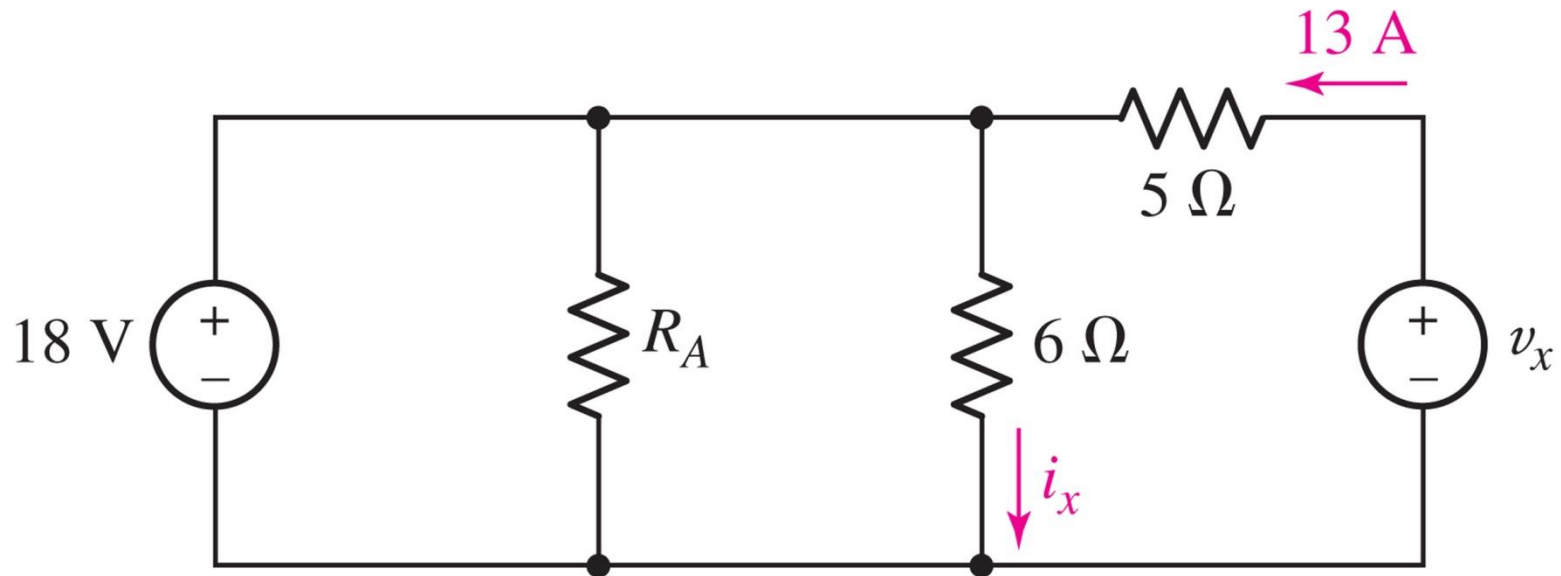


Count the number of branches and nodes in the circuit. If  $i_x = 3\text{ A}$ . and the 18-V source delivers 8 A. of current, what is the value of  $R_A$ ?


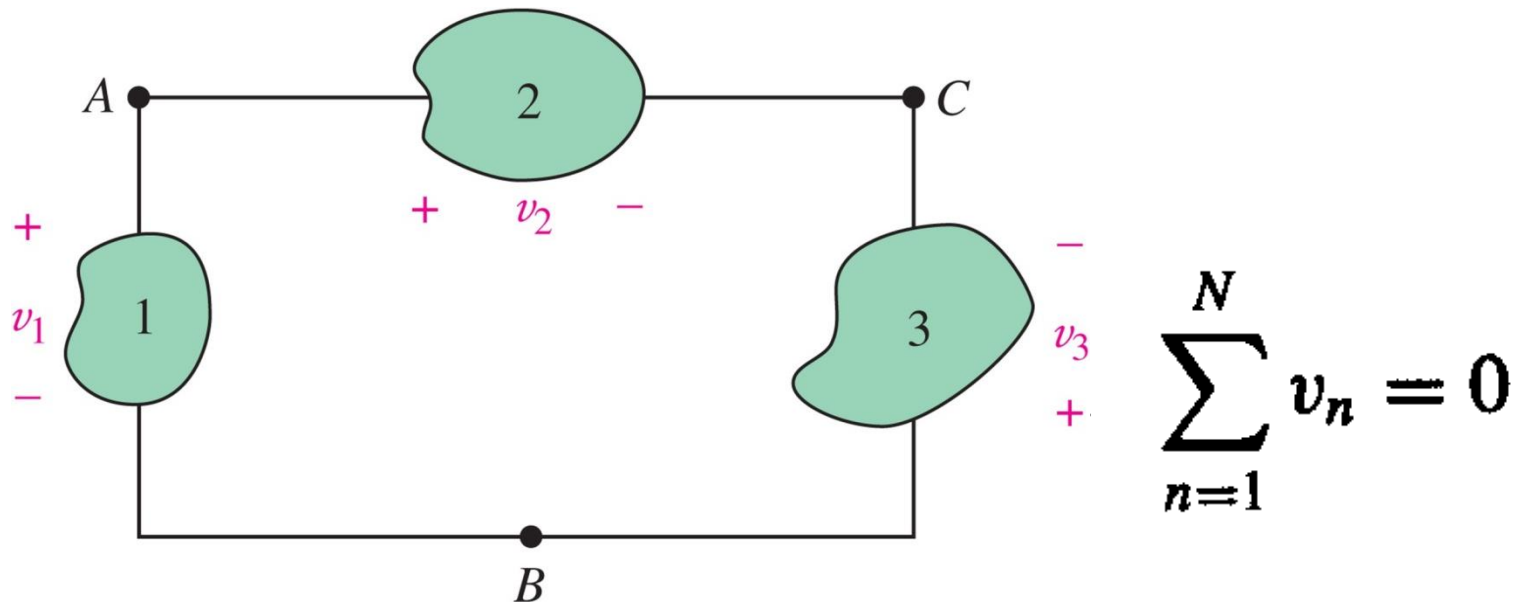
# Kirchoff's Voltage Law (KVL):

---


The algebraic sum of the voltages around any closed path is zero



The potential difference between points A and B is independent of the path selected


# Example: 3.2

Find  $v_x$  and  $i_x$

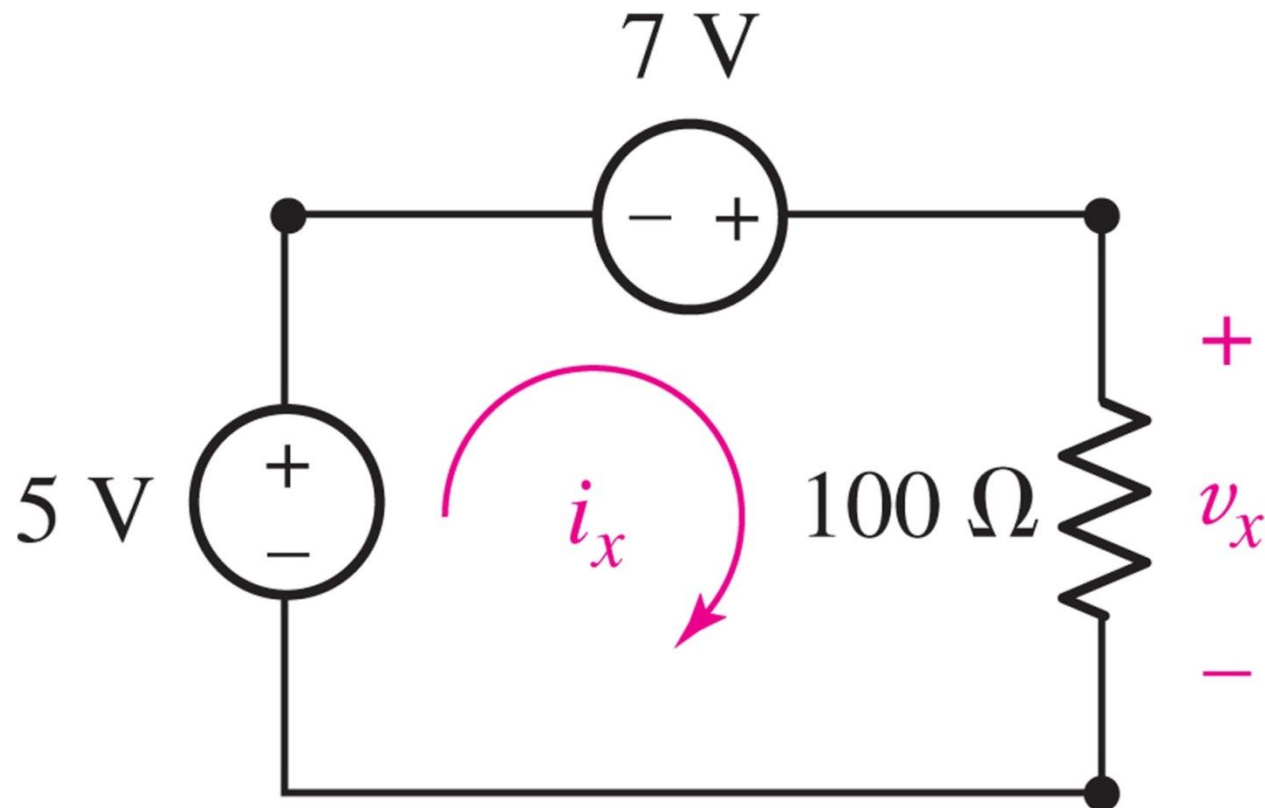

# Example:

Find  $v_x$  and  $i_x$

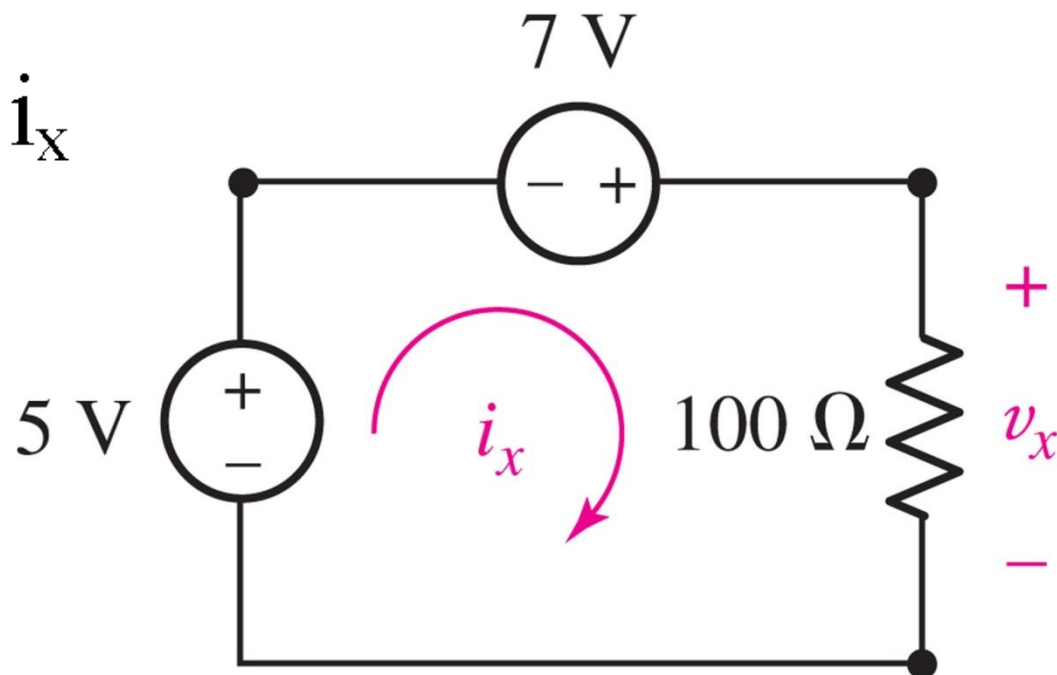


$$-5 - 7 + v_x = 0$$

$$\therefore v_x = 12V.$$

# Practice: 3.2


---

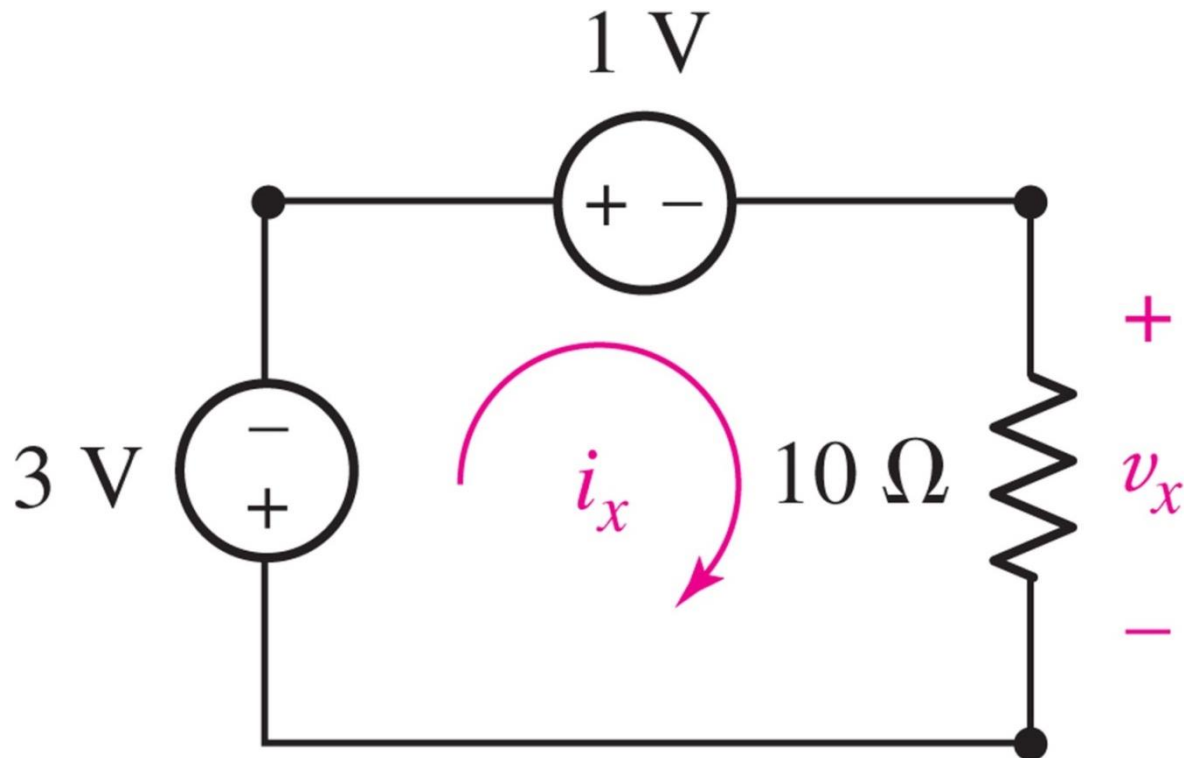


Determine  $i_x$  and  $v_x$

# Example: 3.4

Determine  $v_x$

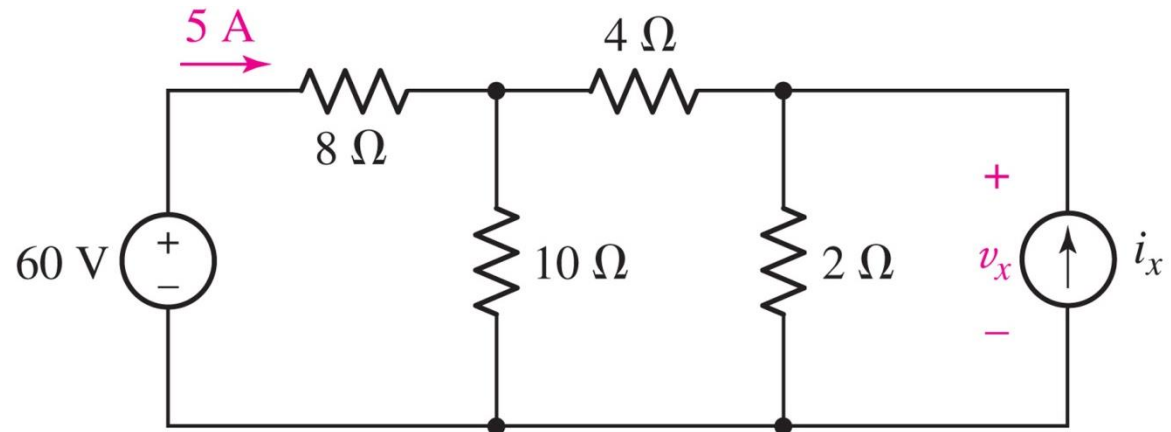


(a)

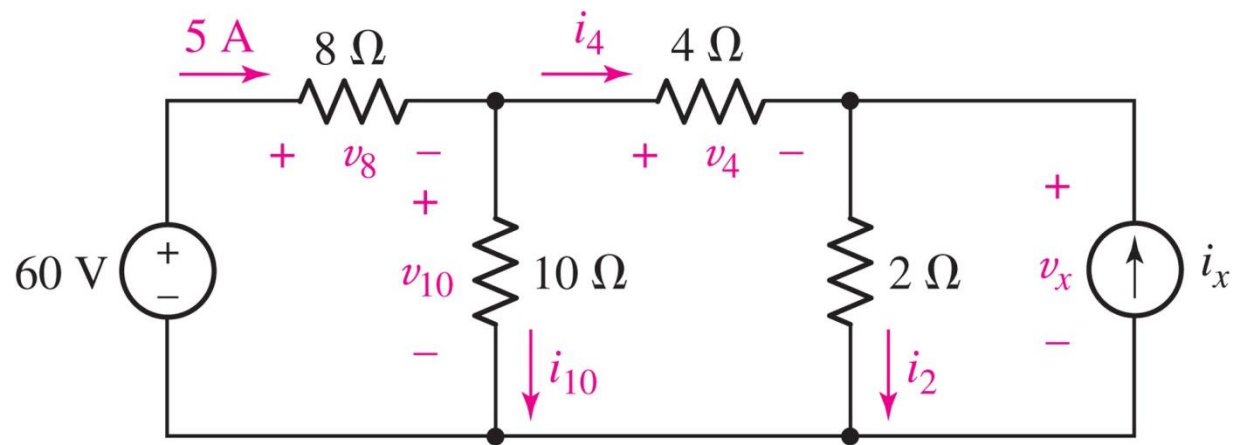

(b)

# Example:

Determine  $v_x$

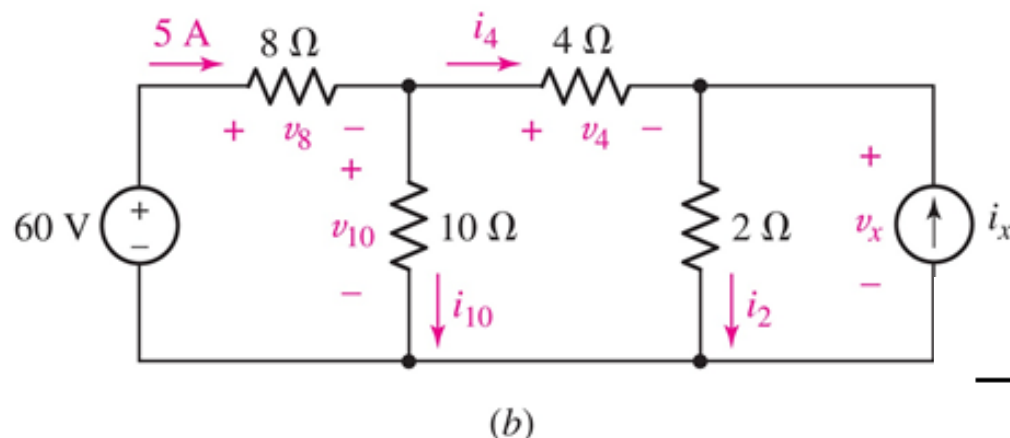


$$-60 + v_8 + v_{10} = 0$$

$$v_8 = 40 \text{ Volts}$$




$$i_{10} = \frac{20V.}{10\Omega} = 2 \text{ Amp.}$$

# Practice: 3.3

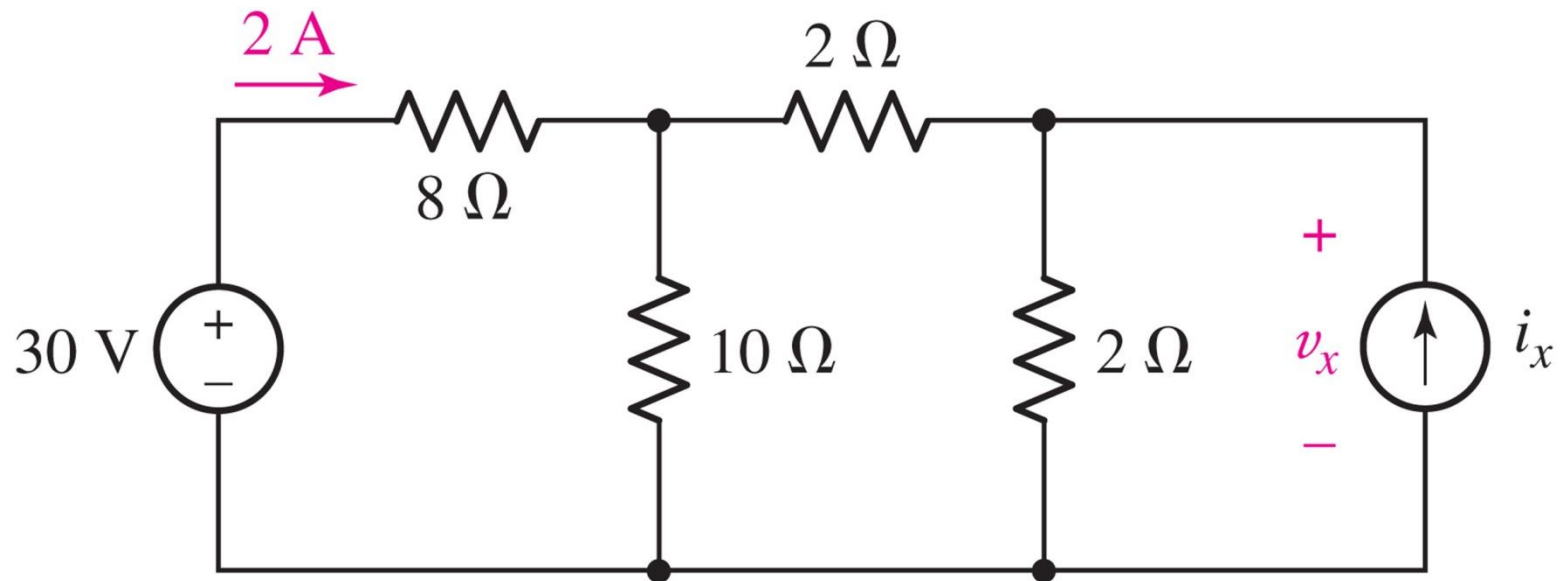

Determine  $v_x$

# The Single Loop Circuit:

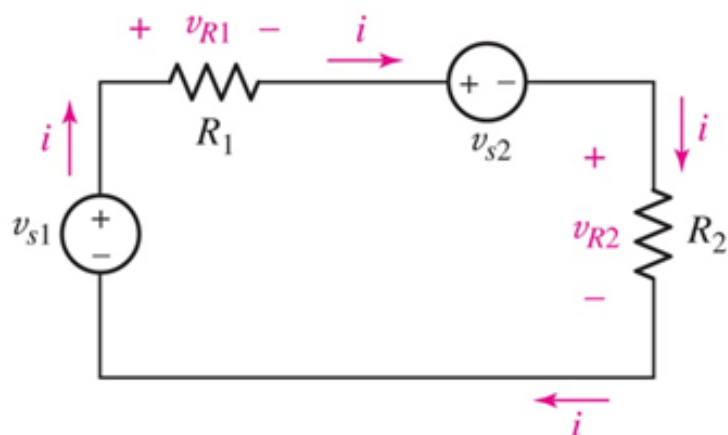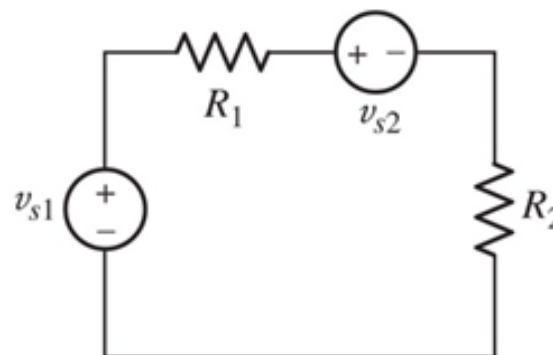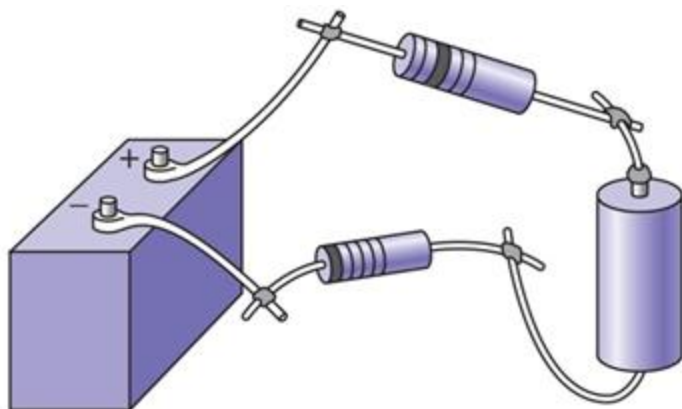


$$-v_{s1} + v_{R1} + v_{s2} + v_{R2} = 0$$

$$-v_{s1} + R_1 i + v_{s2} + R_2 i = 0$$

$$\therefore i = \frac{v_{s1} - v_{s2}}{R_1 + R_2}$$




# Practice: 3.5

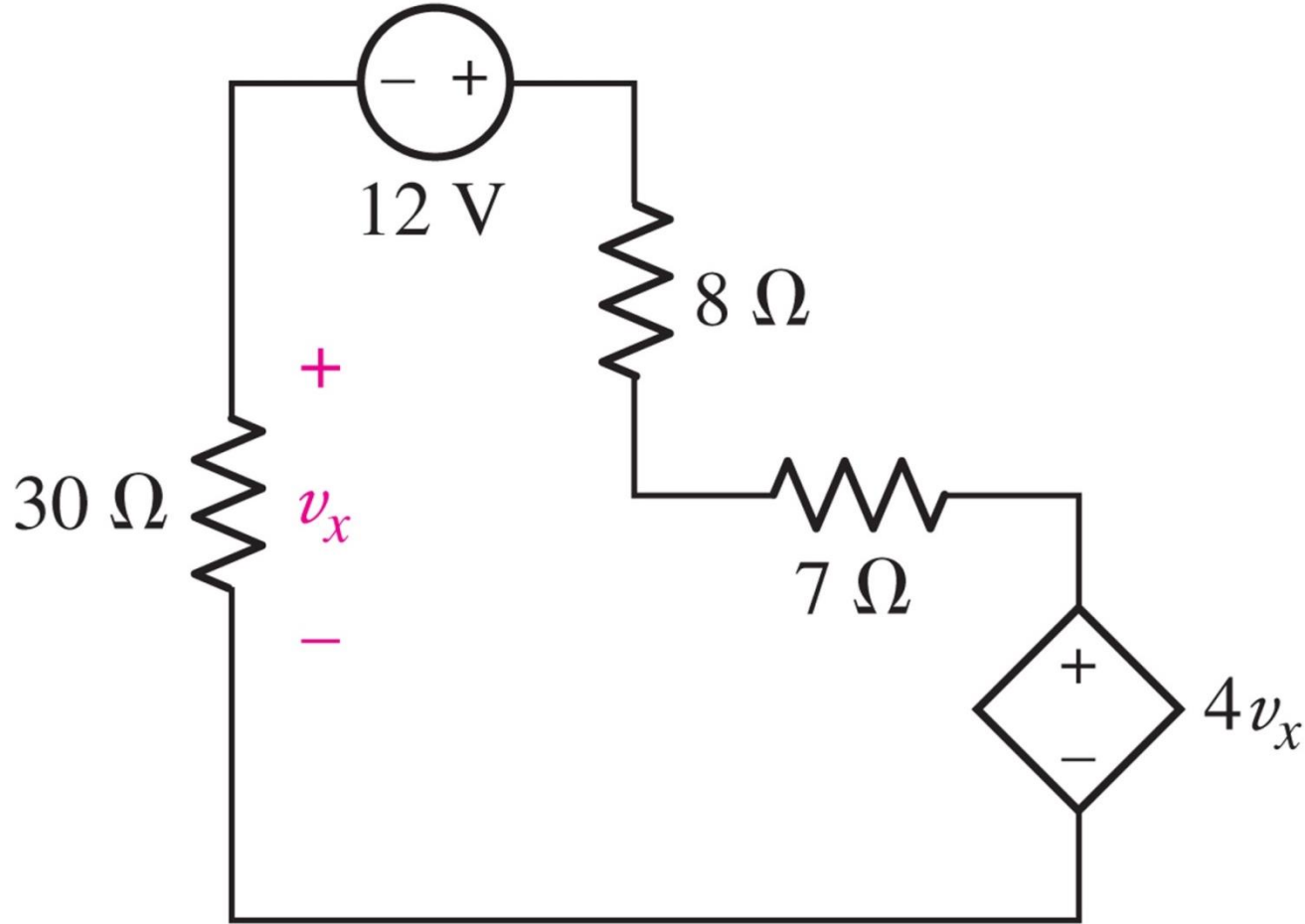


Find the power absorbed by each of the five elements in the circuit.

# The Single Node-Pair Circuit:

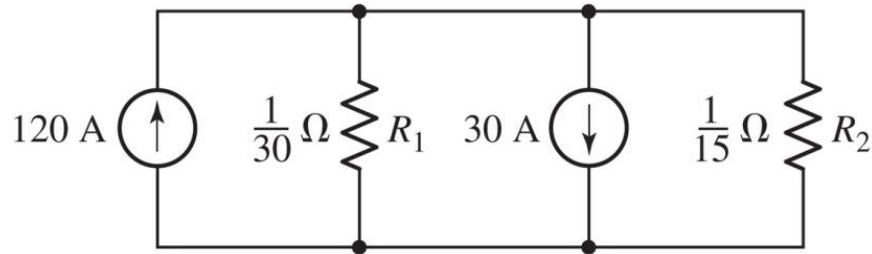

(a)

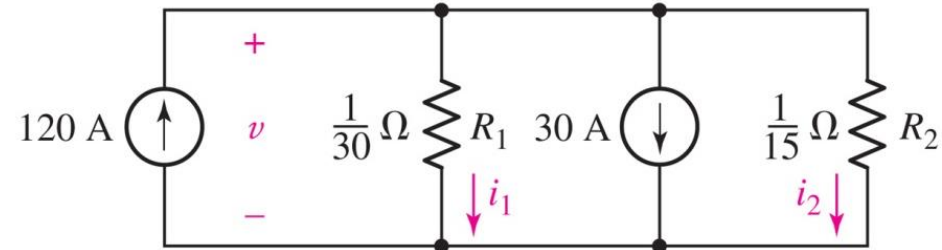

(b)


$$-120 + i_1 + 30 + i_2 = 0$$

$$-120 + 30v + 30 + 15v = 0$$

$$\therefore v = 2 \text{ Volts}$$


# Practice: 3.6

---

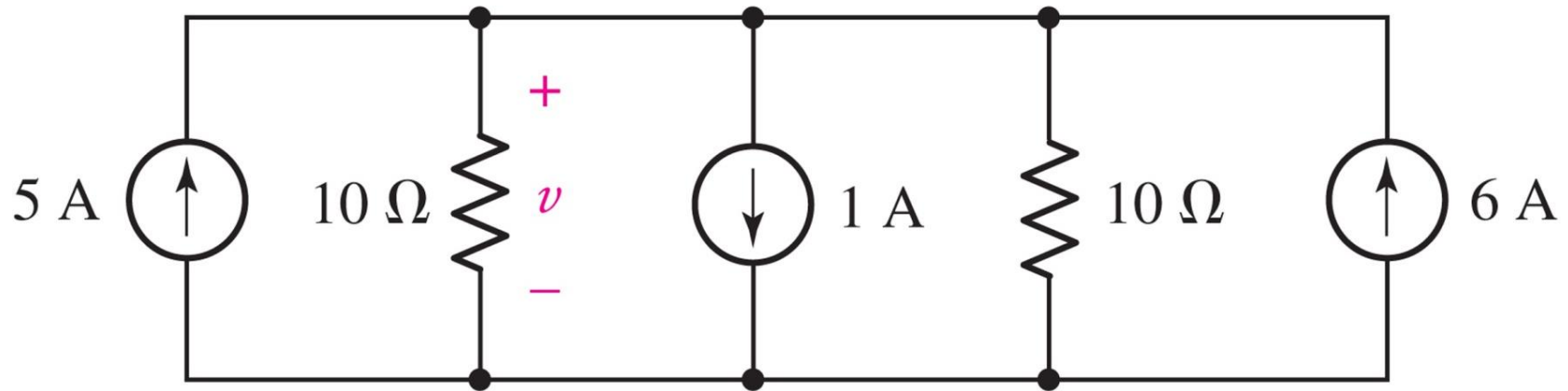

Determine  $v$




# Practice: 3.7

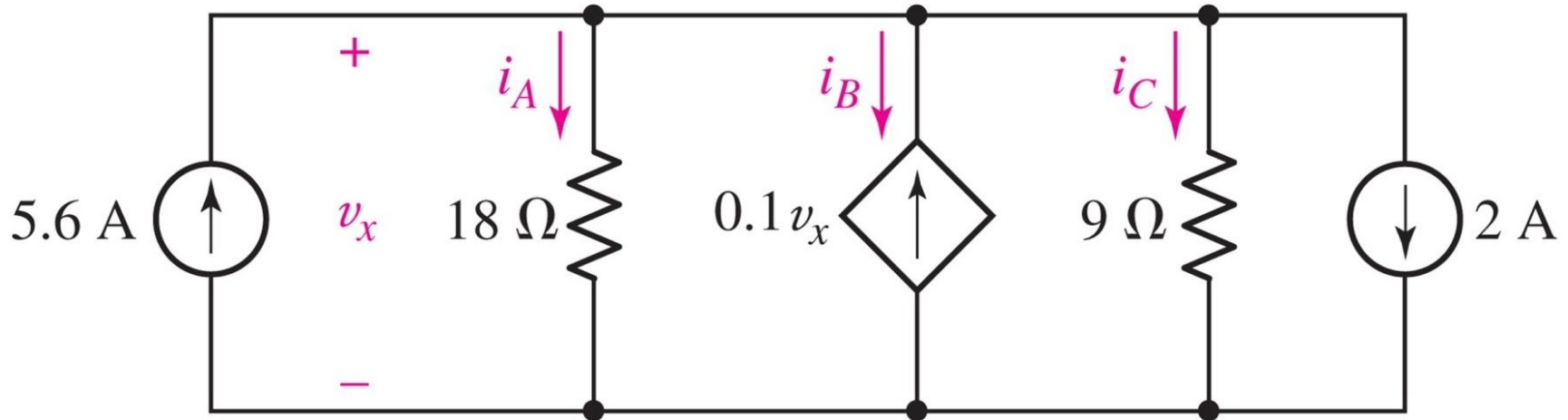

For the single-node-pair circuit of the figure, find  $i_A$ ,  $i_B$  and  $i_C$

# Example: 3.8


Find  $i_1, i_2, i_3$ , and  $i_4$

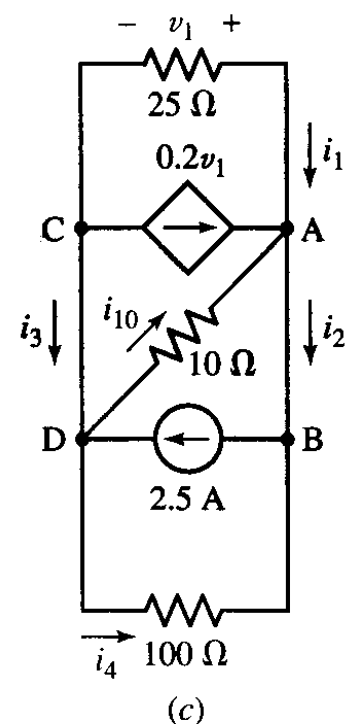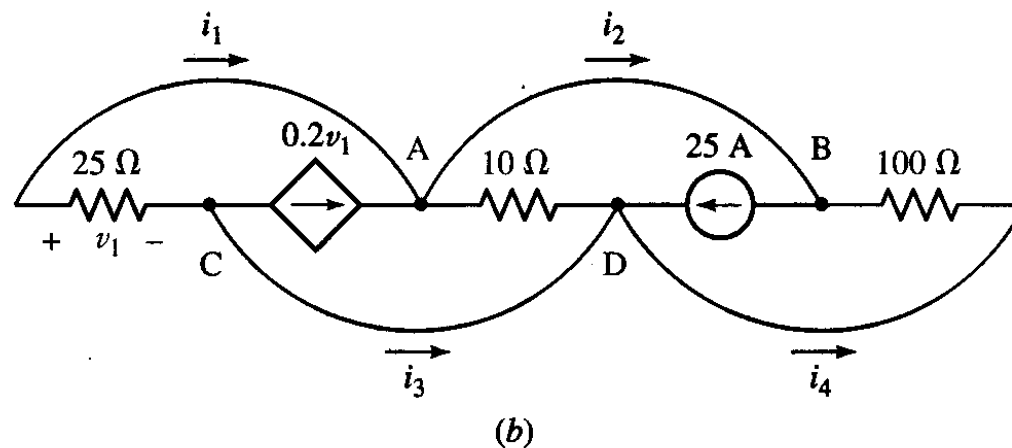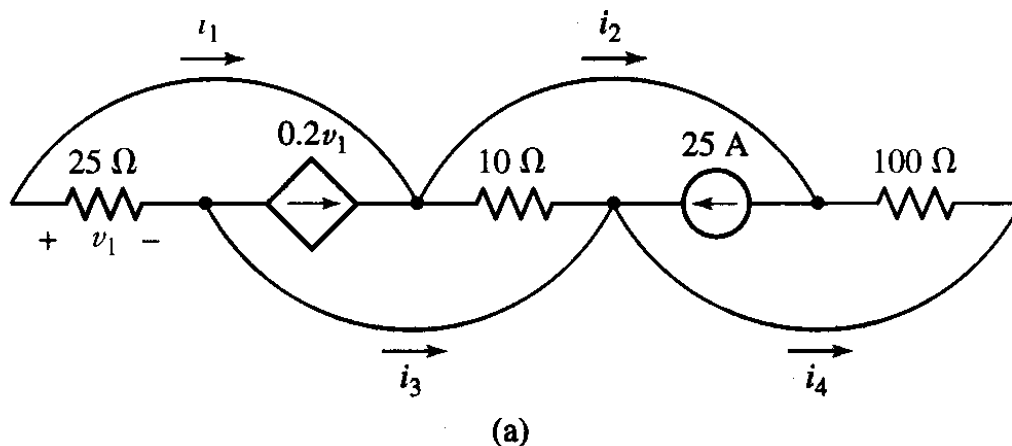

(a) A single-node-pair circuit. (b) Circuit with points labeled to assist in redrawing. (c) Redrawn circuit.

# Example:

Find  $i_1, i_2, i_3$ , and  $i_4$

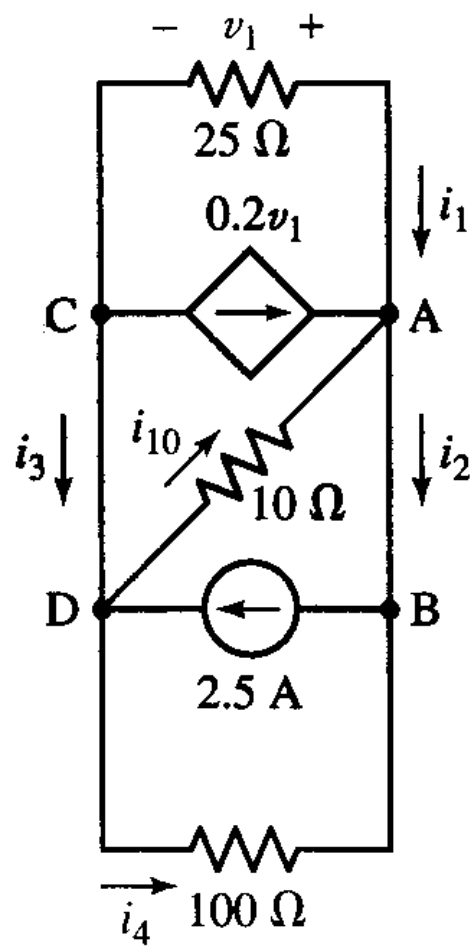

(c)

$$\frac{v_1}{25} - 0.2v_1 + \frac{v_1}{10} + 2.5 + \frac{v_1}{100} = 0$$


$$\text{Solving, we find } v_1 = \frac{250}{5} = 50 \text{ V.}$$

$$i_1 = \frac{-v_1}{25} = -2 \text{ Amp.}$$

, ...

# Series and Parallel Connected: Page 23


## Independent Sources:

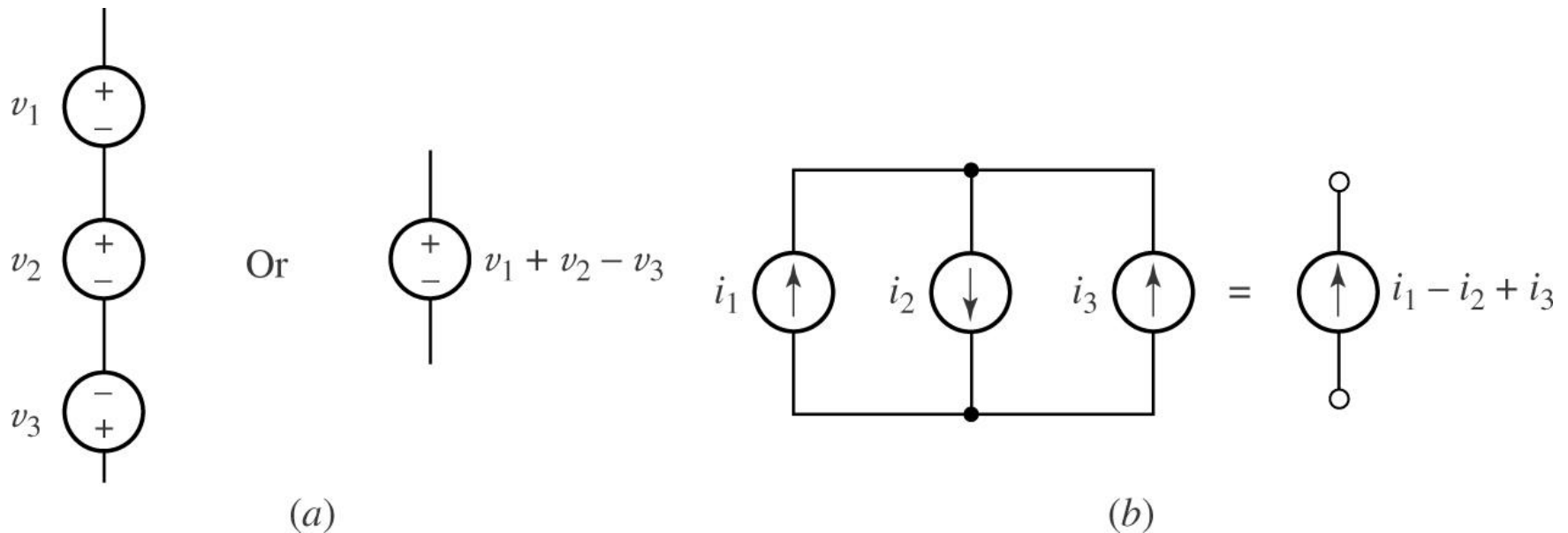


(a) Series connected voltage sources can be replaced by a single source. (b) Parallel current sources can be replaced by a single source.

# Series and Parallel Connected: Page 24

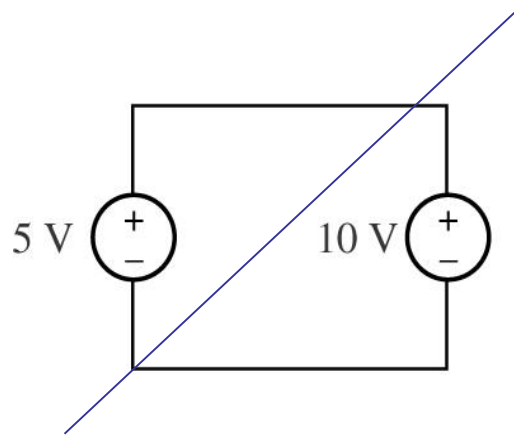
**Examples of circuits with multiple sources, some of which are “illegal” as they violate Kirchhoff’s laws.**




(a)

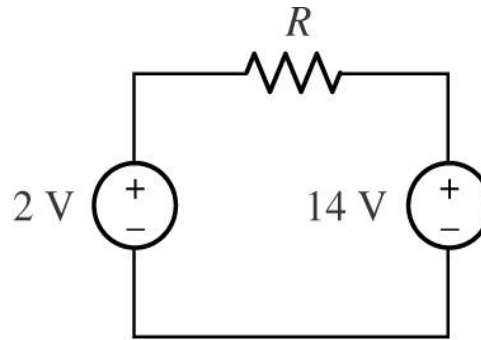

(b)

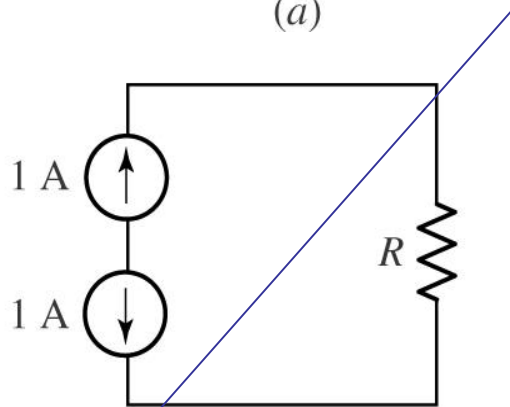

(c)

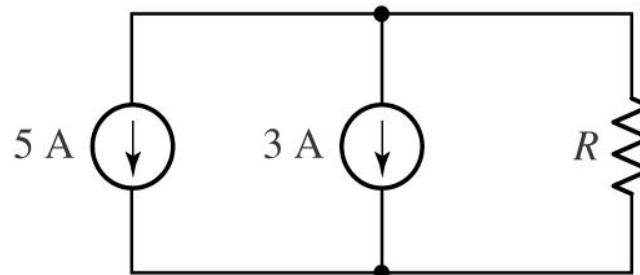


(d)




# Practice: 3.8

---

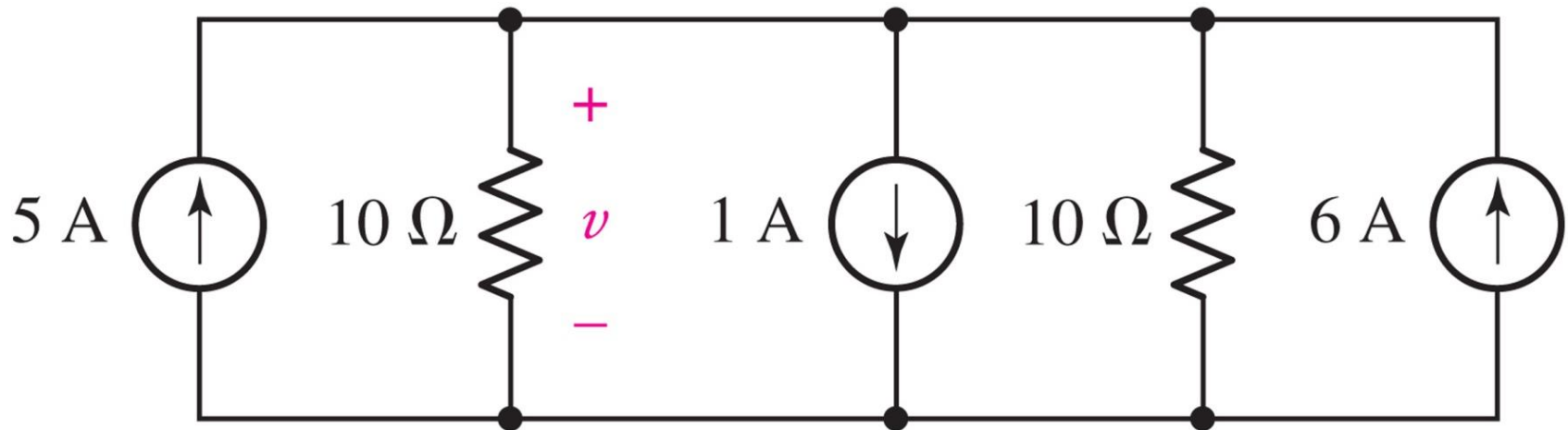

Determine  $v$  in the circuit of the figure by first combining the three current sources.
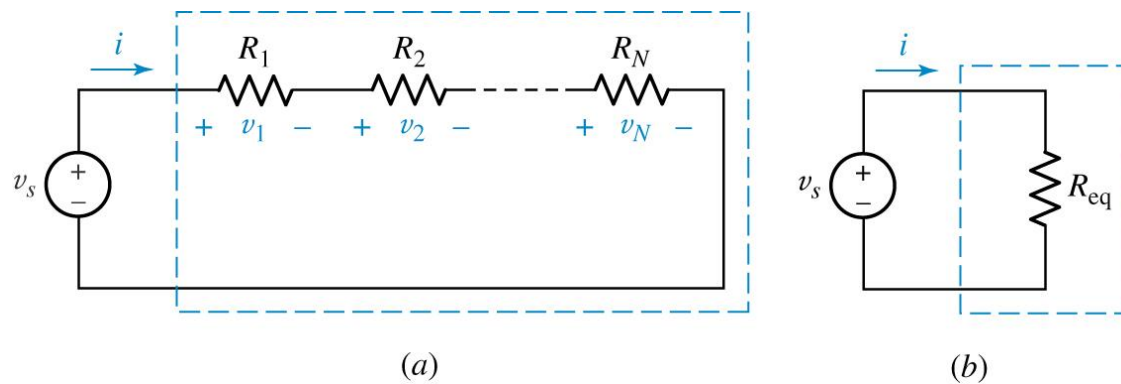
# Resistors in Series and Parallel: <sup>Page 26</sup>



**(a) Series combination of  $N$  resistors. (b) Electrically equivalent circuit.**

First, apply KVL:

$$v_s = v_1 + v_2 + \cdots + v_N$$

and then Ohm's law:

$$v_s = R_1 i + R_2 i + \cdots + R_N i = (R_1 + R_2 + \cdots + R_N) i$$


circuit shown

$$v_s = R_{eq} i$$


Thus, the value of the equivalent resistance for  $N$  series resistors is

$$R_{eq} = R_1 + R_2 + \cdots + R_N$$

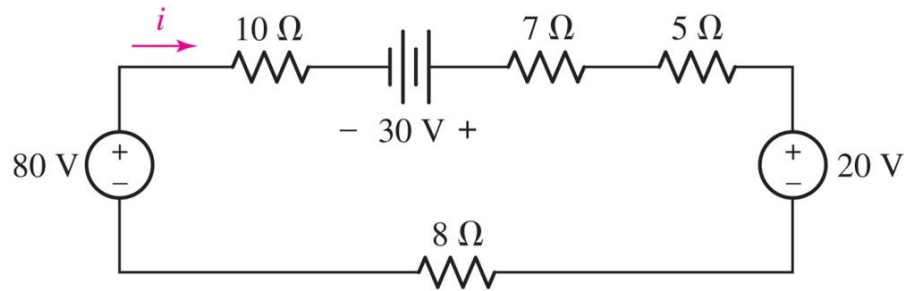
# Resistors in Series and Parallel: <sup>Page 27</sup>



(a)

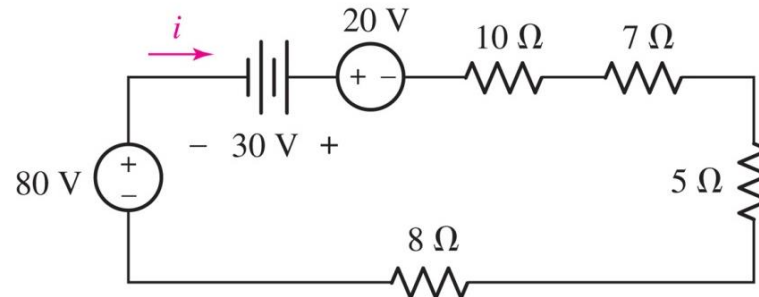


(b)

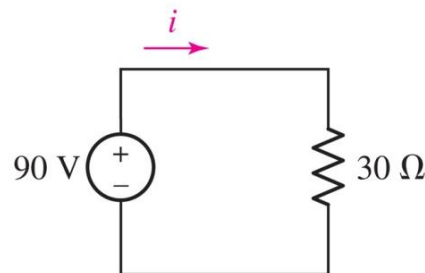


(c)

# Practice: 3.9

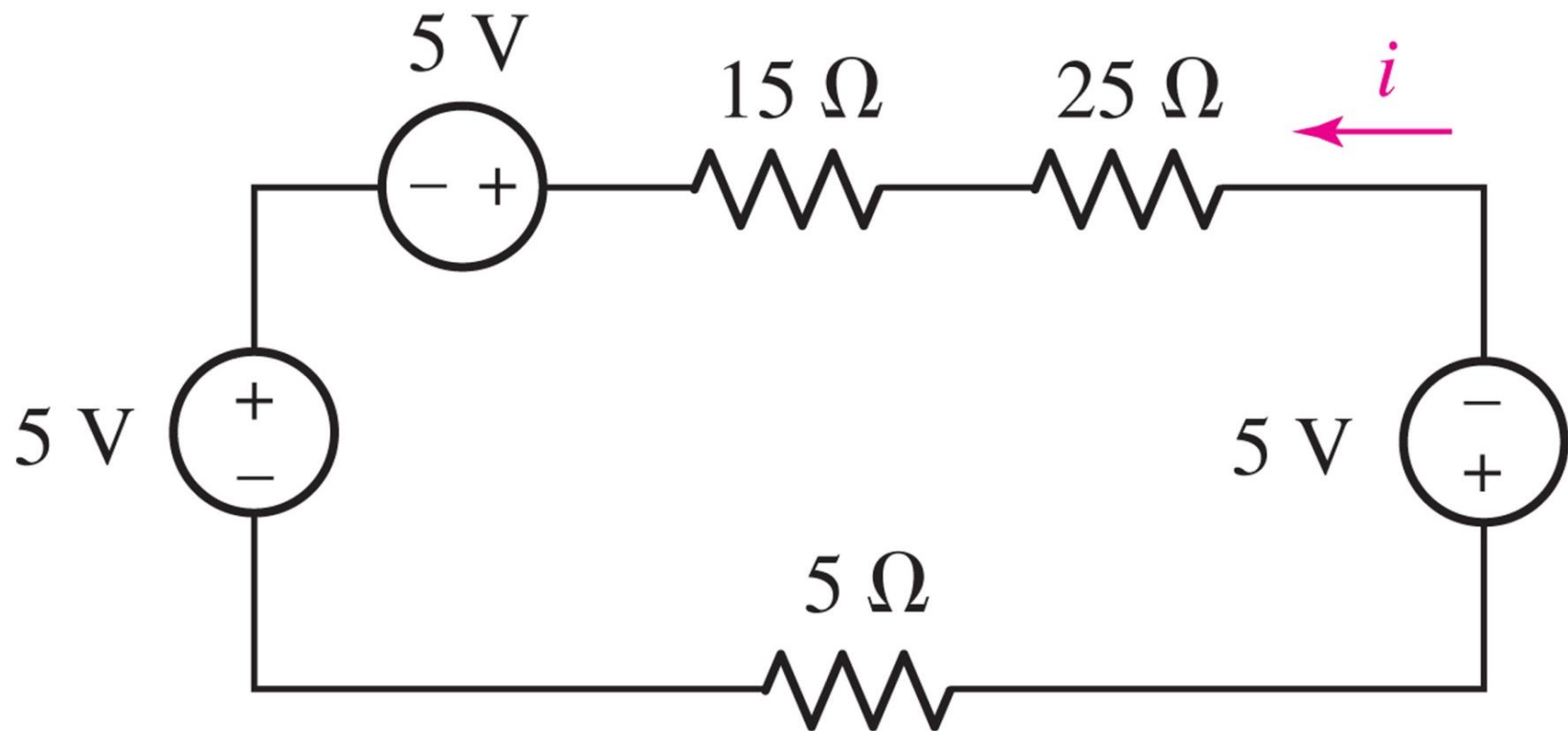


Determine  $i$  in the circuit
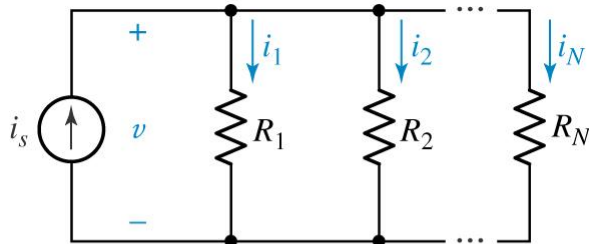
# Resistors in Series and Parallel: Page 29



(a)

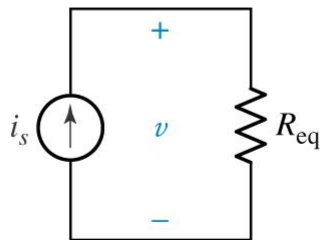

(b)

**(a) A circuit with  $N$  resistors in parallel. (b) Equivalent circuit.**

**Beginning with a simple KCL equation,**

$$i_s = i_1 + i_2 + \dots + i_N$$

**or** 
$$i_s = \frac{v}{R_1} + \frac{v}{R_2} + \dots + \frac{v}{R_N} = \frac{v}{R_{eq}}$$

**Thus,** 
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


**A special case worth remembering is**

$$R_{eq} = R_1 \parallel R_2 = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

# Practice: 3.10


---

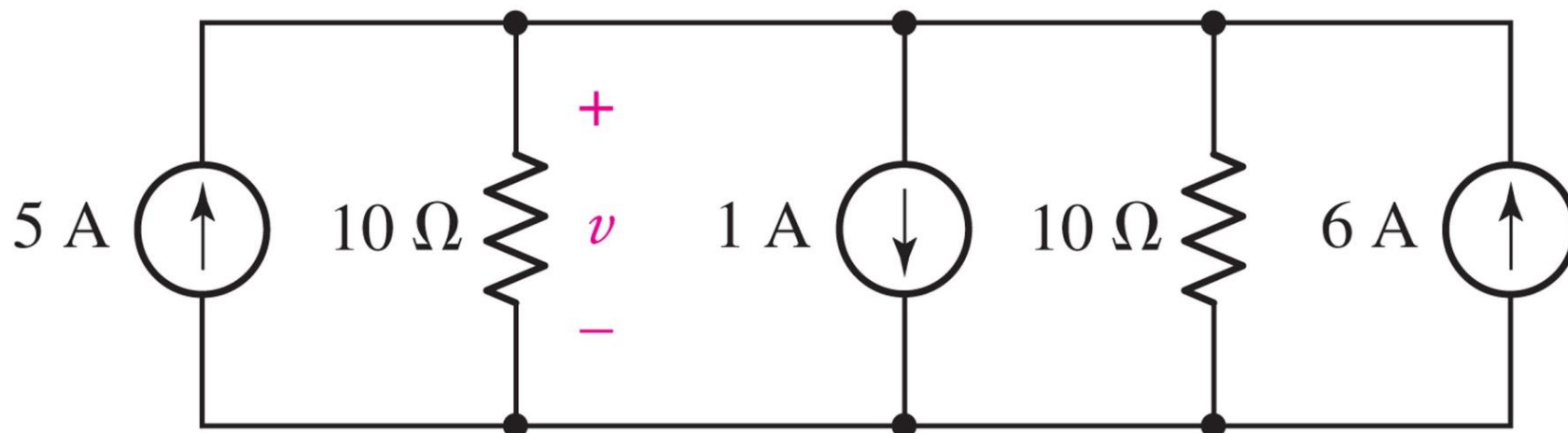

Determine  $v$  in the circuit by first combining the three current sources, and then the two  $10\ \Omega$  resistors.



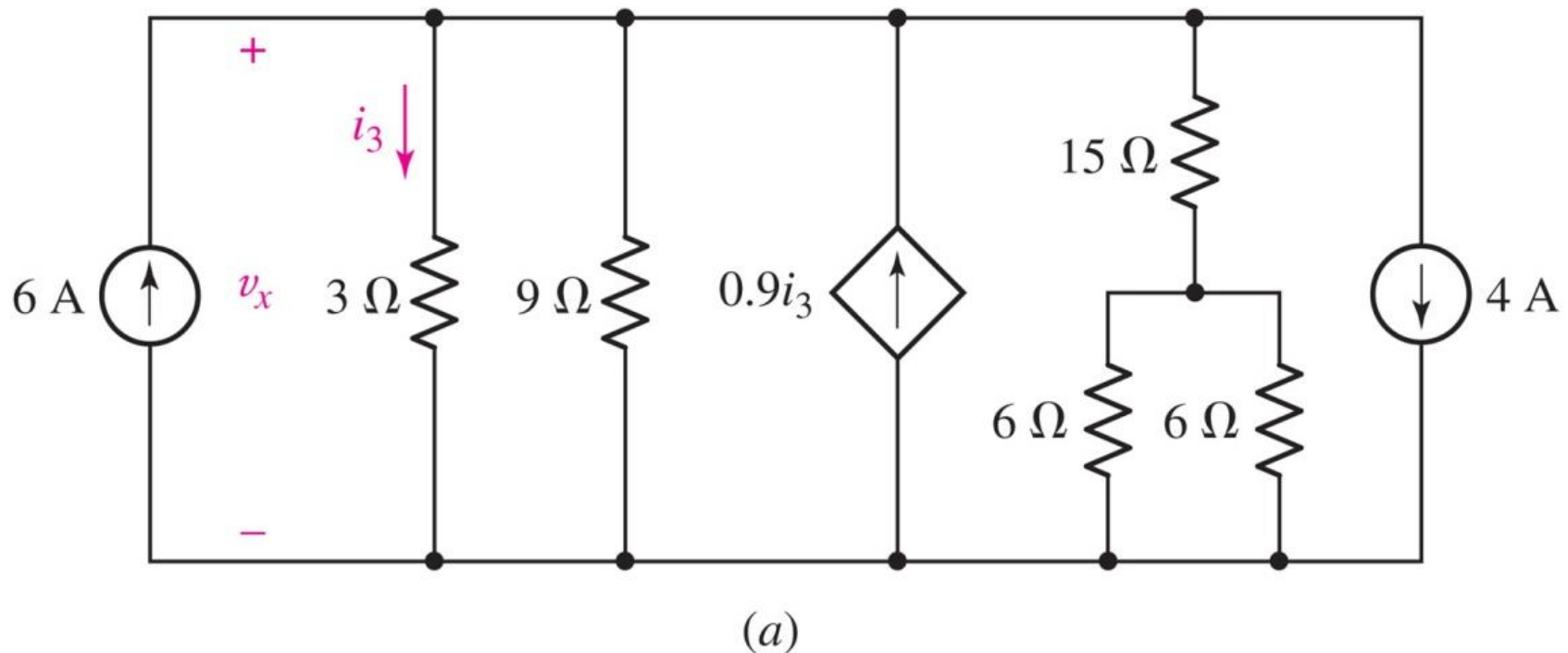
# Example: 3.11

Calculate the power and voltage of the dependent source


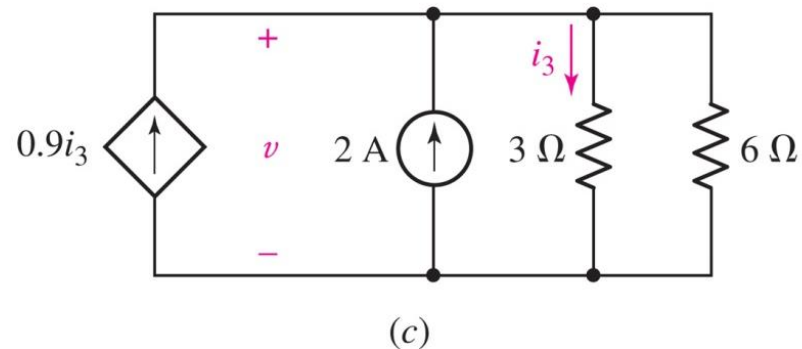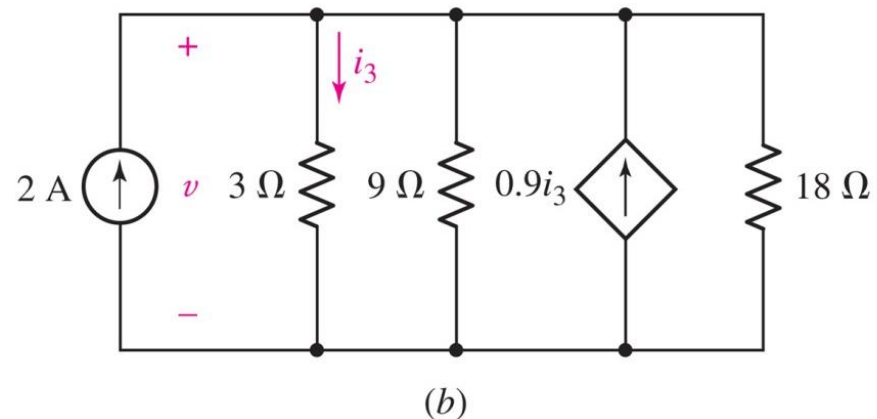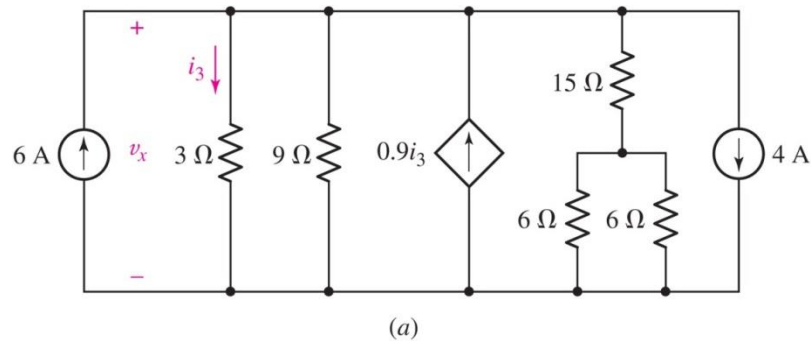
# Example:


Calculate the power and voltage of the dependent source




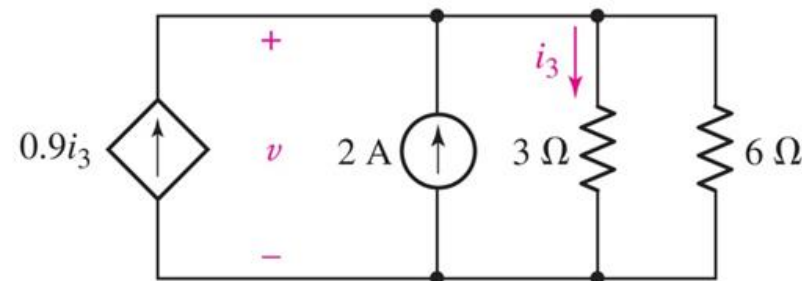
# Example:

Calculate the power and voltage of the dependent source



$$\text{From the top node: } -0.9i_3 - 2 + i_3 + \frac{v}{6} = 0$$

$$\text{The other equation: } v = 3i_3$$

$$\therefore i_3 = \frac{10}{3} \text{ Amp.}$$


$$\therefore v = 3i_3 = 10 \text{ Volts}$$

The dependent source furnishes:

$$v \times 0.9i_3 = 10(0.9)\left(\frac{10}{3}\right) = 30 \text{ Watts.}$$


# Practice: 3.11

---

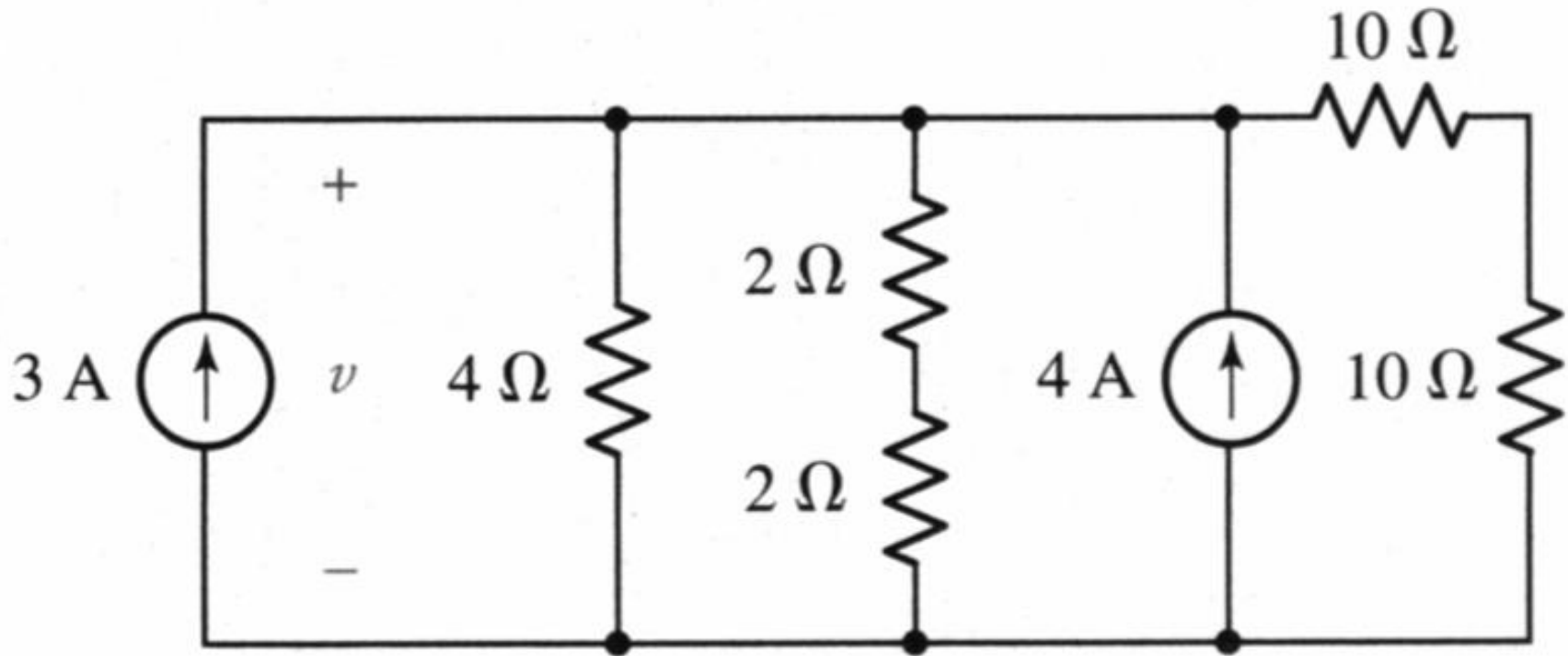

Find the voltage  $v$

# Voltage and Current division:

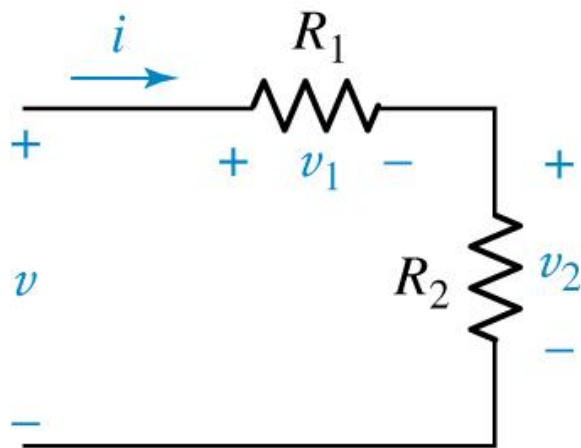

An illustration of voltage division.

We may find  $v_2$  by applying KVL and Ohm's law:

$$v = v_1 + v_2 = iR_1 + iR_2 = i(R_1 + R_2)$$

so 
$$i = \frac{v}{R_1 + R_2}$$

Thus, 
$$v_2 = iR_2 = \left( \frac{v}{R_1 + R_2} \right) R_2$$


or 
$$v_2 = \frac{R_2}{R_1 + R_2} v$$

For a string of  $N$  series resistors, we may write:

$$v_k = \frac{R_k}{R_1 + R_2 + \cdots + R_N} v$$


# Practice: 3.12

---

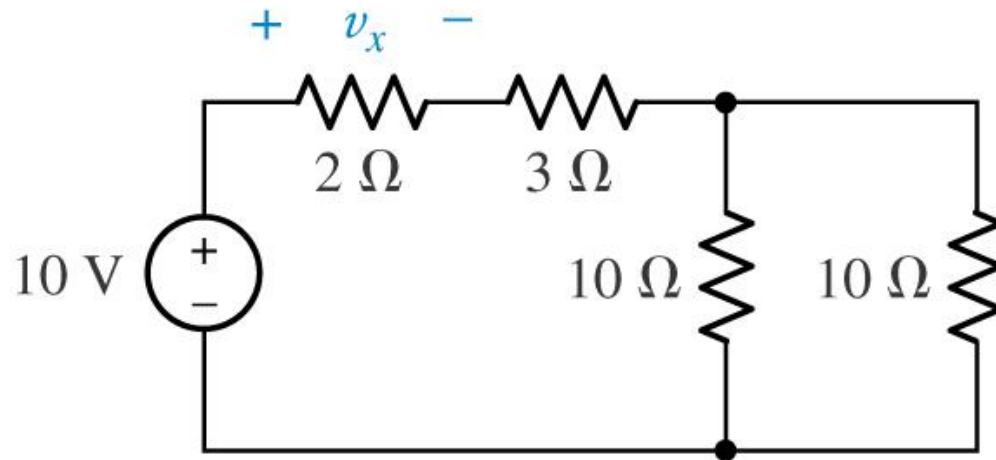

**Use voltage division to determine  $v_x$  in the adjacent circuit.**

# Voltage and Current division:

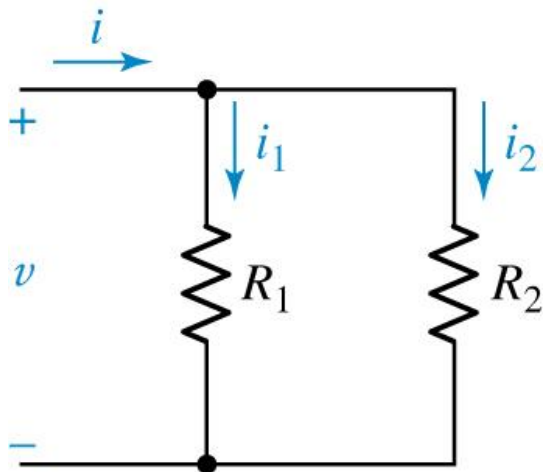

An illustration of current division.

The current flowing through  $R_2$  is

$$i_2 = \frac{v}{R_2} = \frac{i(R_1 \parallel R_2)}{R_2} = \frac{i}{R_2} \frac{R_1 R_2}{R_1 + R_2}$$


or

$$i_2 = i \frac{R_1}{R_1 + R_2}$$

For a parallel combination of  $N$  resistors, the current through  $R_k$  is

$$i_k = i \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \cdots + \frac{1}{R_N}}$$


# Example:

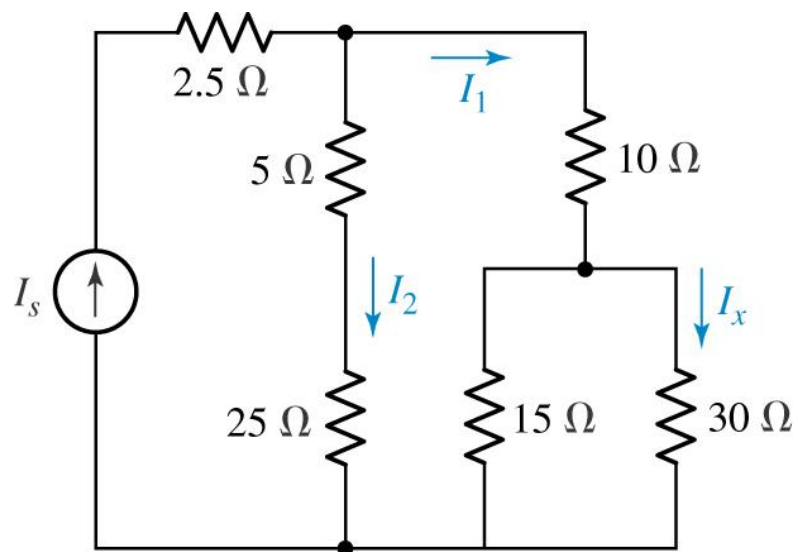

**Determine the current  $I_x$  if  $I_1 = 100\text{ mA}$ .**


# Practice: 3.13

Find  $i_1$ ,  $i_2$ , and  $v_3$

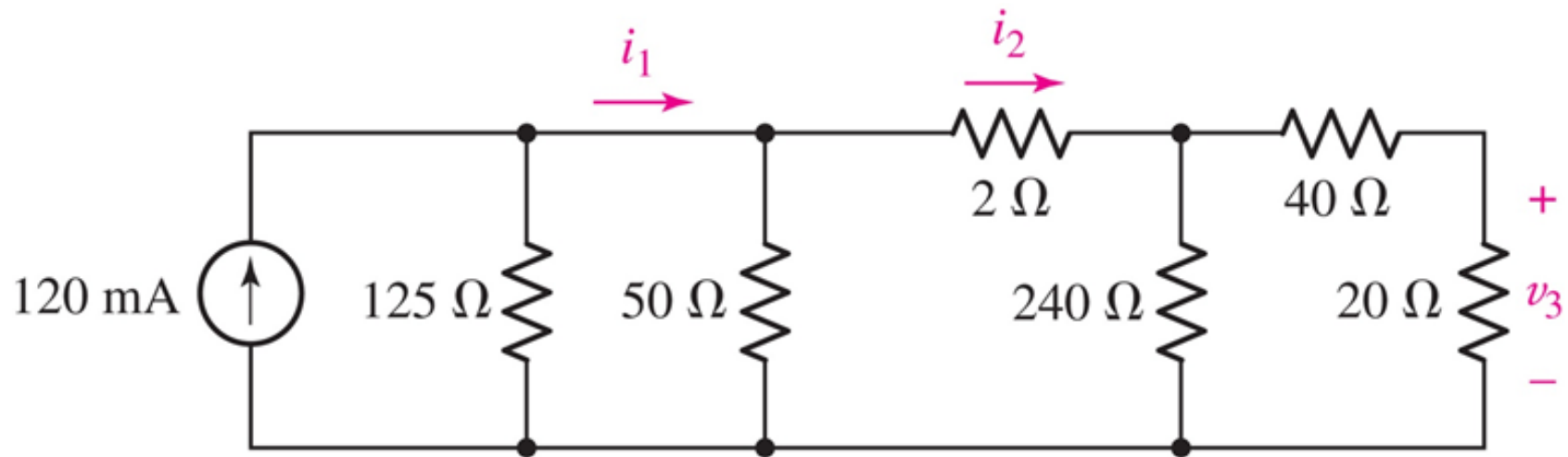

# Example:

Find  $i_1$ ,  $i_2$ , and  $v_3$

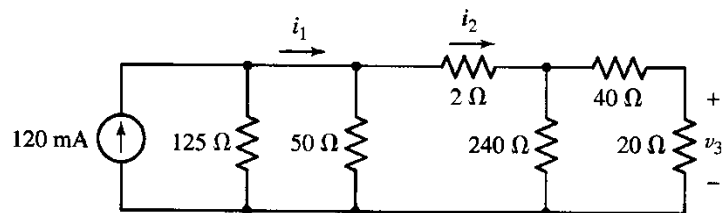

$$\begin{aligned}
 & (((40\Omega + 20\Omega) // 240\Omega) + 2\Omega) // 50\Omega \\
 &= ((60\Omega // 240\Omega) + 2\Omega) // 50\Omega \\
 &= \left( \frac{60 \times 240}{60 + 240} + 2\Omega \right) // 50\Omega \\
 &= (48\Omega + 2\Omega) // 50\Omega \\
 &= 25\Omega
 \end{aligned}$$

Current division:

$$i_1 = \left( \frac{125}{125 + 25} \right) \times 120 \text{ mA} = 100 \text{ mA}.$$

$$i_2 = \left( \frac{50}{50 + 50} \right) \times i_1 = 50 \text{ mA}.$$

$$i_{20\Omega} = \left( \frac{240}{240 + 60} \right) \times i_2 = 40 \text{ mA}.$$

$$v_3 = i_{20\Omega} \times 20\Omega = 0.8 \text{ Volts}.$$




# Homework:

---

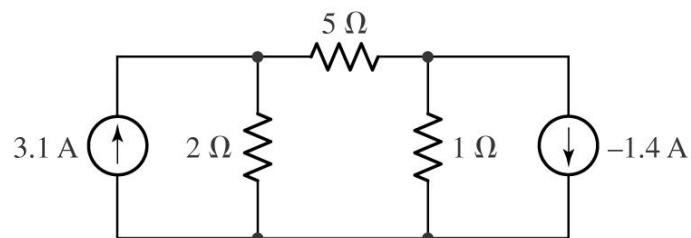
# Ch4-Nodal and Mesh Analysis: Page 42

Nodal Analysis: is based on KCL


Obtain values for the unknown voltages across the elements in the circuit below.



(a)

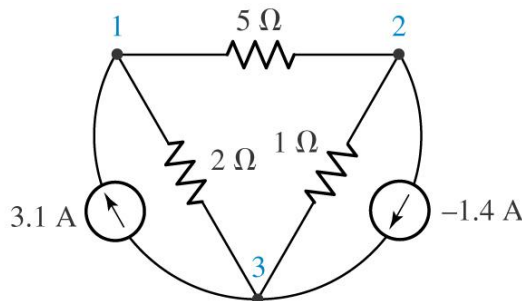


(b)

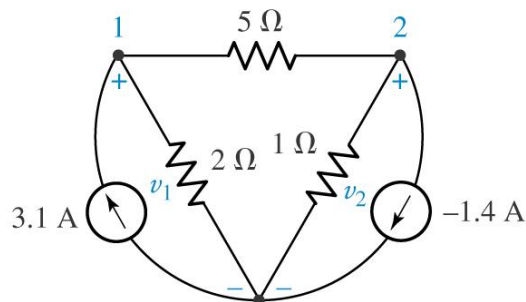

Reference node

(c)

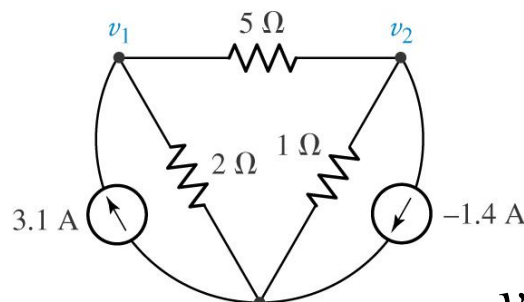

Ref.

(d)



*At node 1*

$$\frac{v_1}{2} + \frac{v_1 - v_2}{5} = 3.1$$

*At node 2*

$$\frac{v_2}{1} + \frac{v_2 - v_1}{5} = -(-1.4)$$


# Practice: 4.1

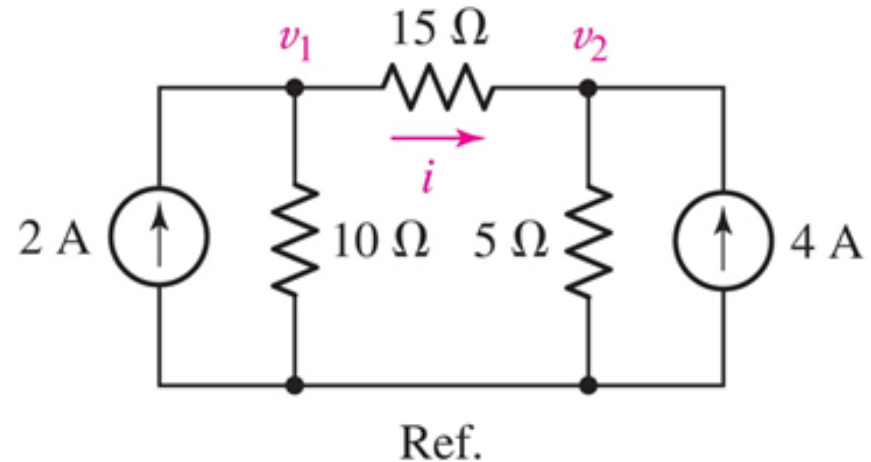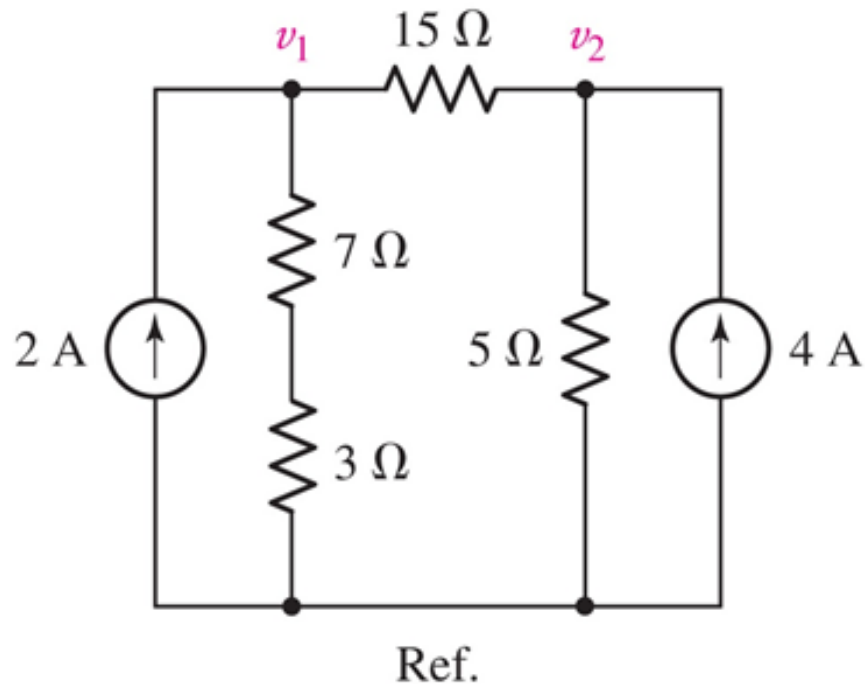

Compute the voltage across each current source.



# Example: 4.2

find the nodes voltages:

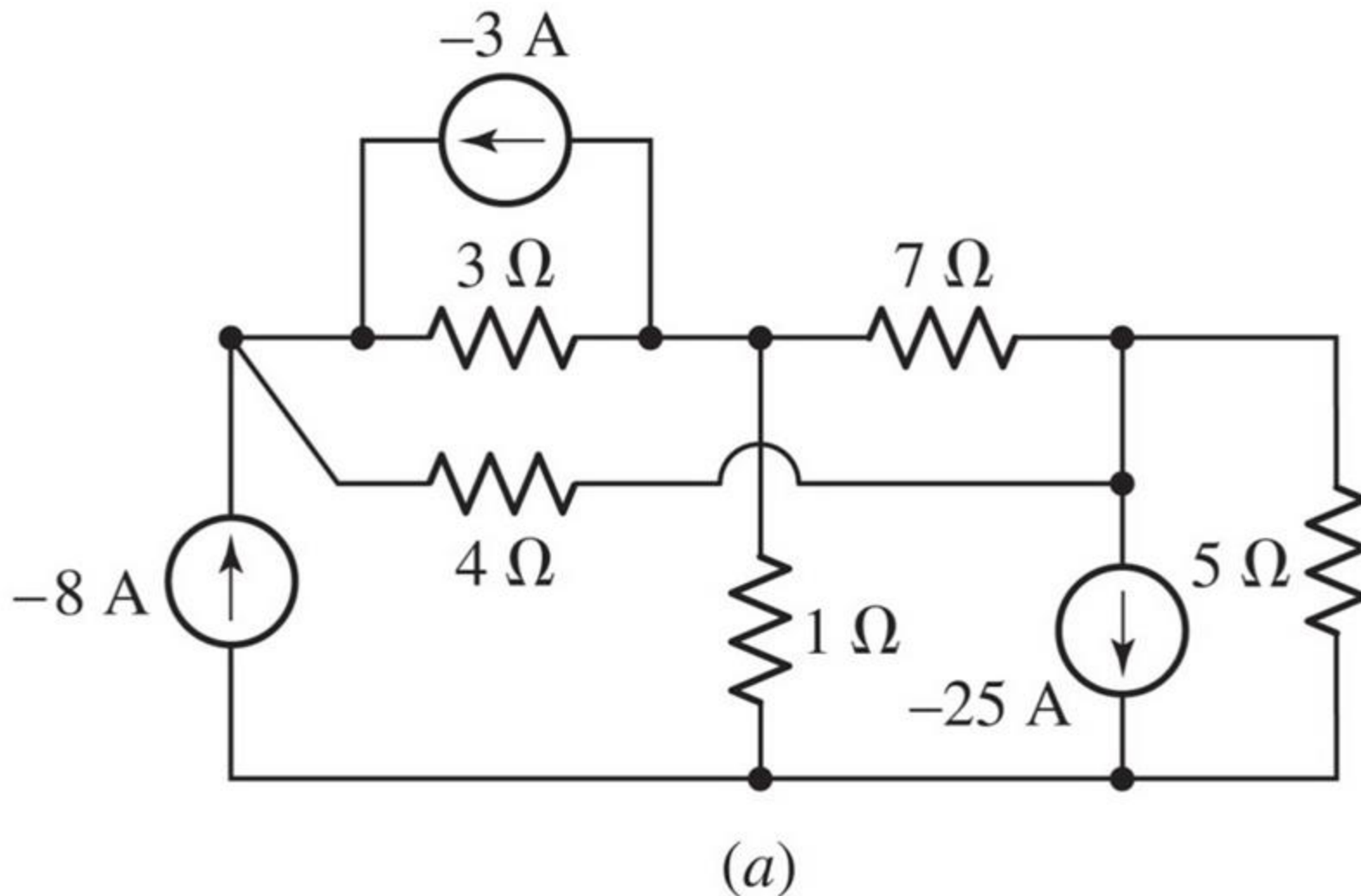


# Example:

find the nodes voltages:

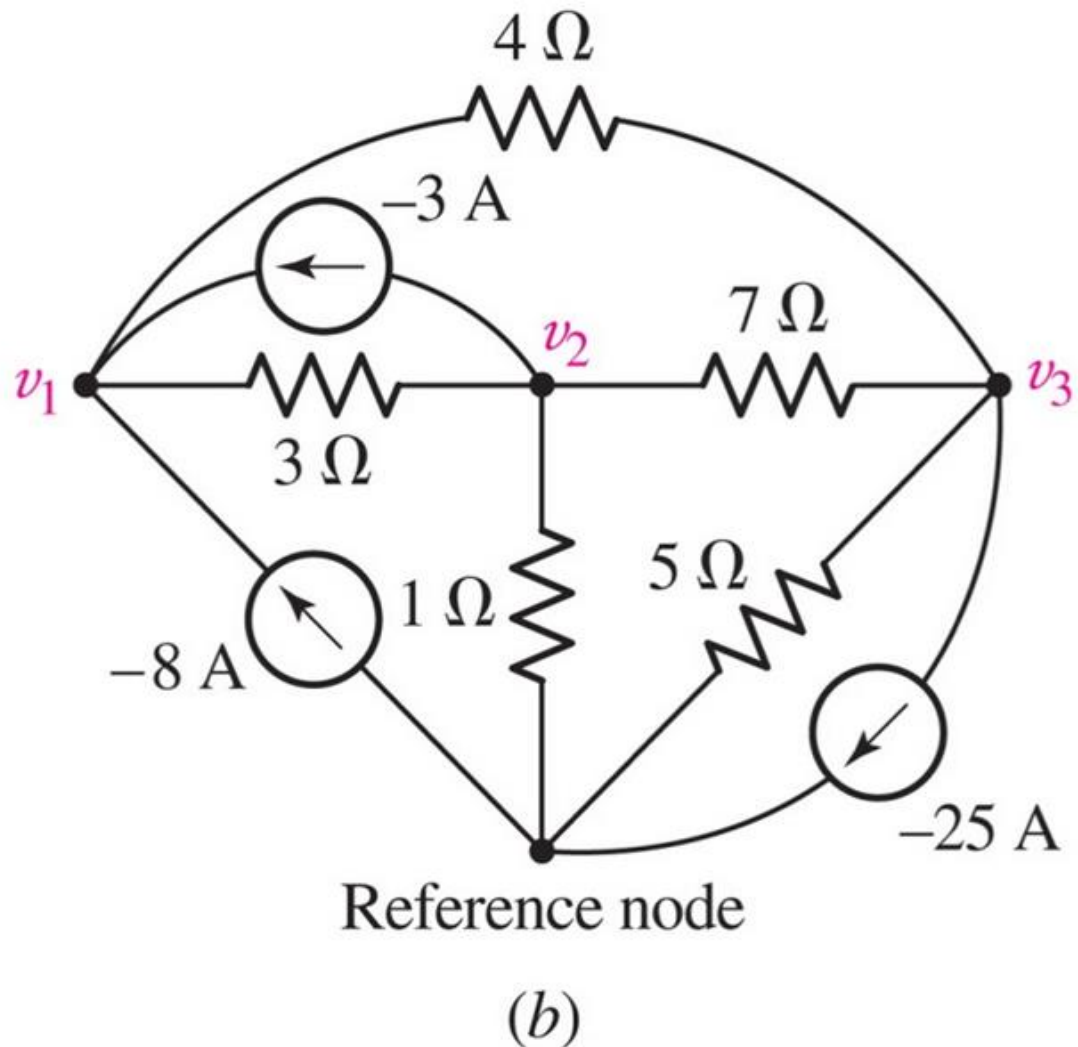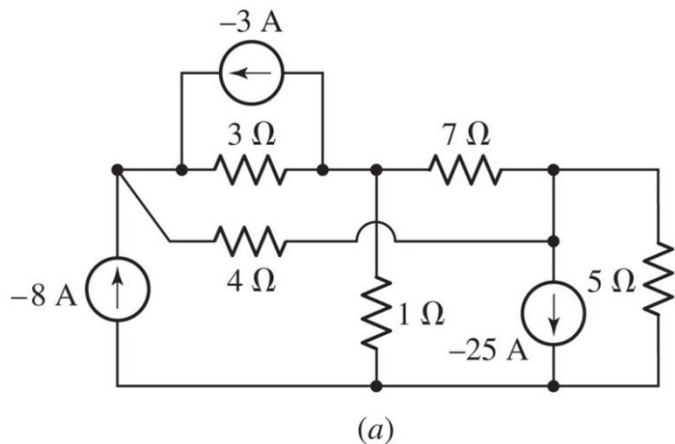

# Example:

find the nodes voltages:

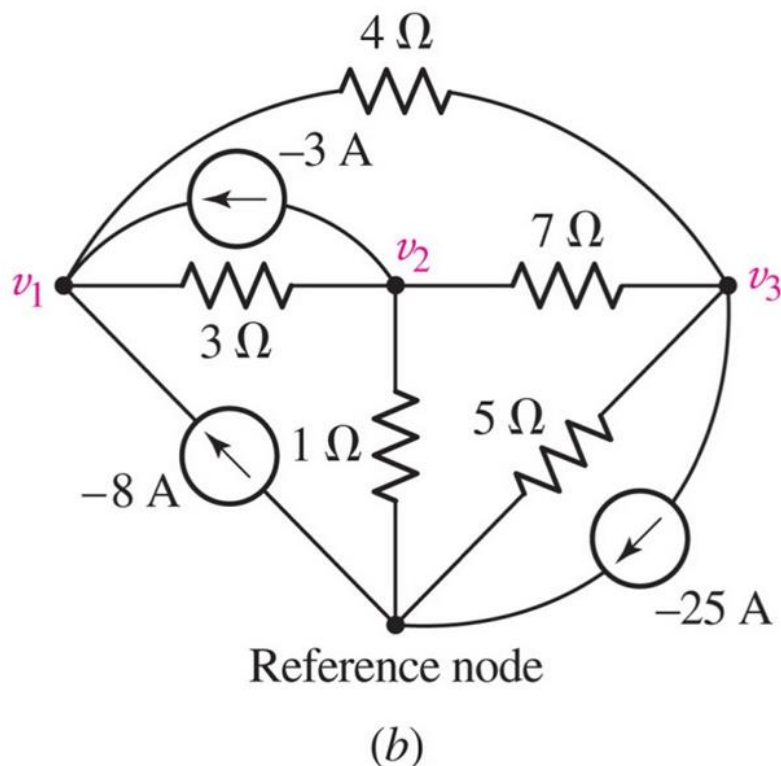

A KCL equation for node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

Node 2:

$$\frac{v_2 - v_3}{7} + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) = 0$$

Node 3:

$$\frac{v_3 - v_2}{7} + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$

# Example:

---

find the nodes voltages:

A KCL equation for node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

Node 2:

$$\frac{v_2 - v_3}{7} + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) = 0$$

Node 3:

$$\frac{v_3 - v_2}{7} + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$



Node 1:

$$0.5833v_1 - 0.3333v_2 - 0.25v_3 = -11$$

Node 2:

$$-0.3333v_1 + 1.4762v_2 - 0.1429v_3 = 3$$

Node 3:

$$-0.25v_1 - 0.1429v_2 + 0.5929v_3 = 25$$

# Example:

find the nodes voltages: (matrix methods)

Node 1:

$$0.5833v_1 - 0.3333v_2 - 0.25v_3 = -11$$

Node 2:

$$-0.3333v_1 + 1.4762v_2 - 0.1429v_3 = 3$$

Node 3:

$$-0.25v_1 - 0.1429v_2 + 0.5929v_3 = 25$$



$v_1$

$$= \frac{\begin{vmatrix} -11 & -0.3333 & -0.2500 \\ 3 & 1.4762 & -0.1429 \\ 25 & -0.1429 & 0.5929 \end{vmatrix}}{\begin{vmatrix} 0.5833 & -0.3333 & -0.2500 \\ -0.3333 & 1.4762 & -0.1429 \\ -0.2500 & -0.1429 & 0.5929 \end{vmatrix}} = \frac{1.714}{0.3167} = 5.412 \text{ Volts.}$$



# Example:

find the nodes voltages: (matrix methods)

Node 1:

$$0.5833v_1 - 0.3333v_2 - 0.25v_3 = -11$$

Node 2:

$$-0.3333v_1 + 1.4762v_2 - 0.1429v_3 = 3$$

Node 3:

$$-0.25v_1 - 0.1429v_2 + 0.5929v_3 = 25$$




$$v_2 = \frac{\begin{vmatrix} 0.5833 & -11 & -0.2500 \\ -0.3333 & 3 & -0.1429 \\ -0.2500 & 25 & 0.5929 \end{vmatrix}}{0.3167}$$

$$= \frac{2.45}{0.3167} = 7.736 \text{ Volts.}$$

$$v_3 = \frac{\begin{vmatrix} 0.5833 & -0.3333 & -11 \\ -0.3333 & 1.4762 & 3 \\ -0.2500 & -0.1429 & 25 \end{vmatrix}}{0.3167}$$

$$= \frac{14.67}{0.3167} = 46.32 \text{ Volts.}$$


# Practice: 4.2

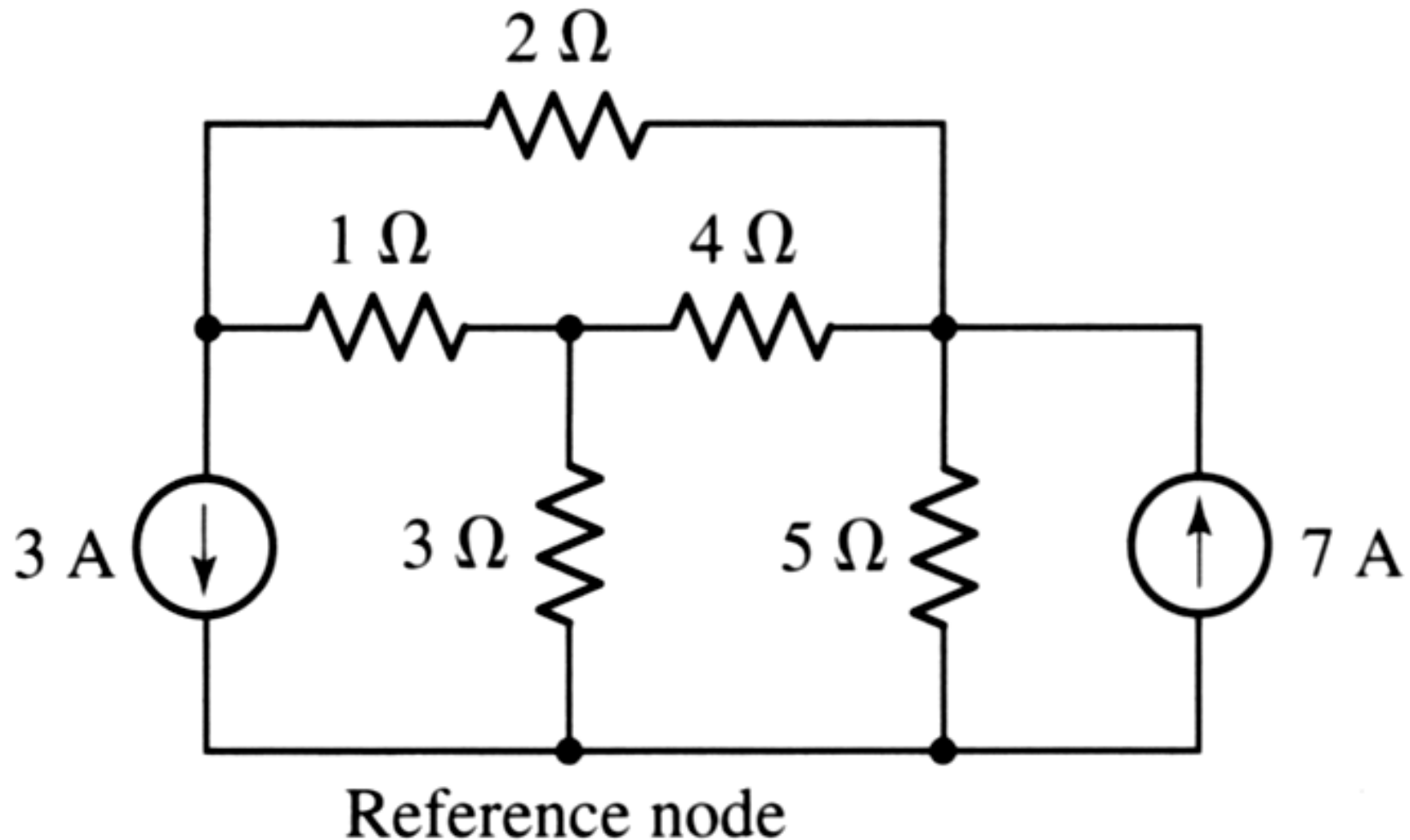

Compute the voltage across each current source.


# The Supernode:

find the nodes voltages:

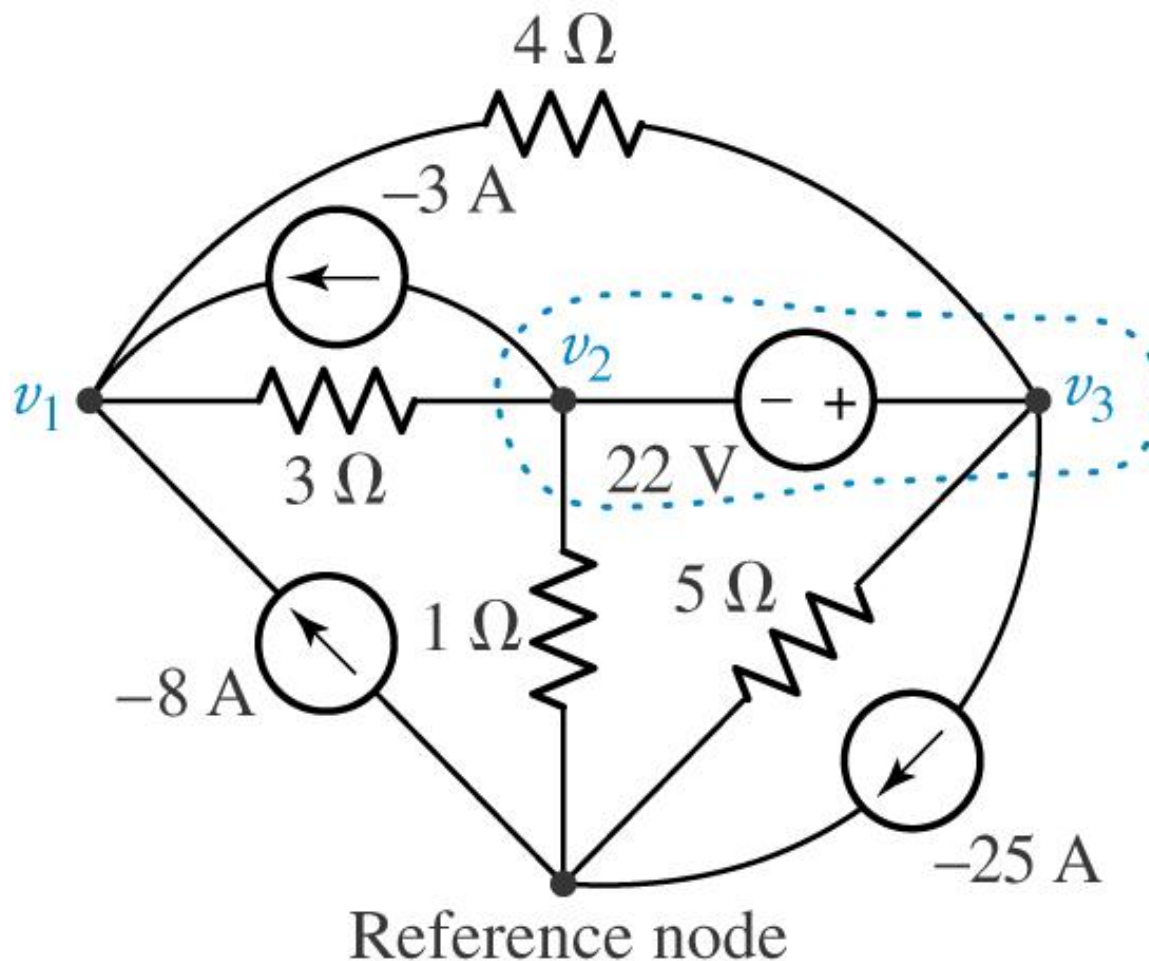

# The Supernode:

find the nodes voltages:

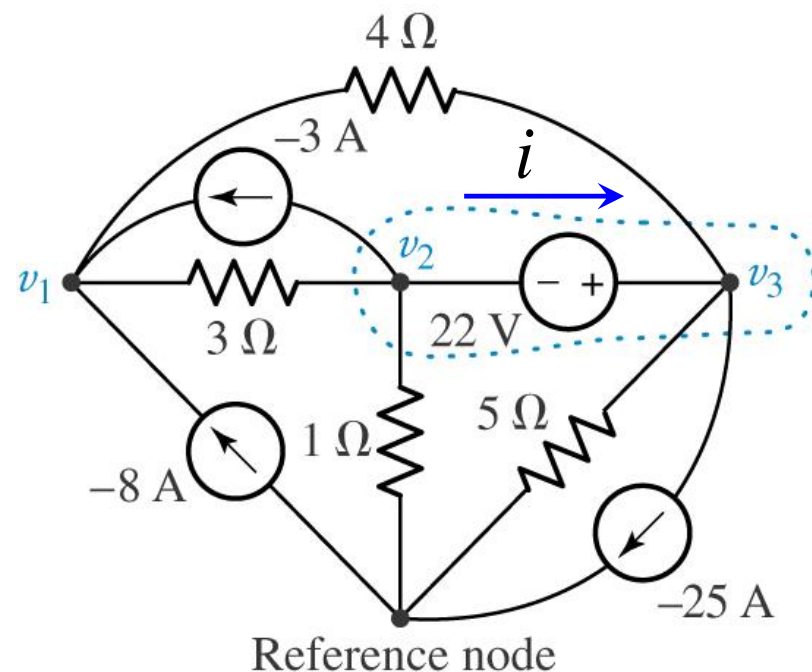

A KCL equation for  
Node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

Node 2:

$$i + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) = 0$$

Node 3:

$$-i + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$

**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**

