

---

ENE 104

Electric Circuit Theory

---



**Lecture 10:**  
**AC Power Circuit Analysis**

---

**Week #12 : Dejwoot KHAWPARISUTH**  
**office: CB40906 Tel: 02-470-9065**  
**Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)**

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

- the instantaneous power
- the average power
- the rms value of a time-varying waveform
- complex power: average and reactive power
- the power factor, how to improve.

# Instantaneous Power:

---

$$p(t) = v(t)i(t)$$

the device is a **resistor**:

$$p(t) = i^2(t)R = \frac{v^2(t)}{R}$$

the device is entirely **inductive**:

$$p(t) = Li(t) \frac{di(t)}{dt} = \frac{1}{L} v(t) \int_{-\infty}^t v(t') dt'$$

the device is entirely **capacitive**:


$$p(t) = Cv(t) \frac{dv(t)}{dt} = \frac{1}{C} i(t) \int_{-\infty}^t i(t') dt'$$

# Instantaneous Power:

---

Consider the series RL circuit,
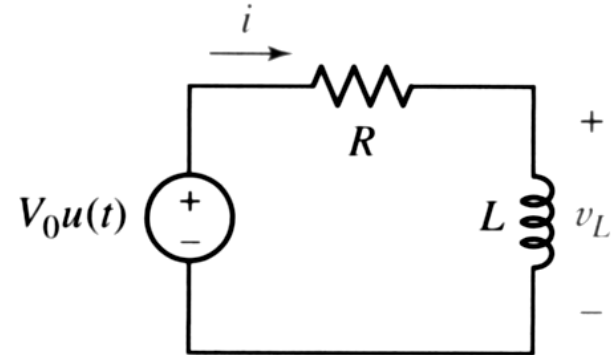
$$i(t) = \frac{V_0}{R} (1 - e^{-Rt/L}) u(t)$$




The total power delivered by the source

$$p(t) = v(t)i(t) = \frac{V_0^2}{R} (1 - e^{-Rt/L}) u(t)$$
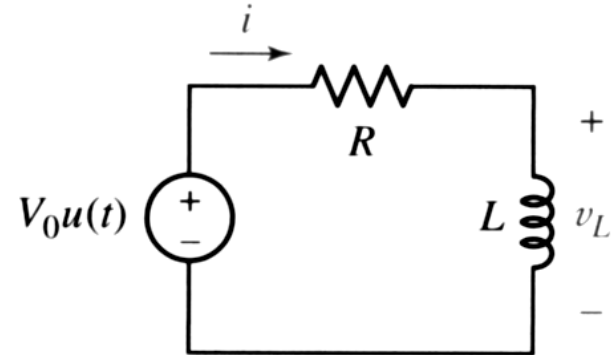
# Instantaneous Power:

Consider the series RL circuit,

$$i(t) = \frac{V_0}{R} (1 - e^{-Rt/L}) u(t)$$




The power delivered to the resistor is

$$p_R(t) = i^2(t)R = \frac{V_0^2}{R} (1 - e^{-Rt/L})^2 u(t)$$
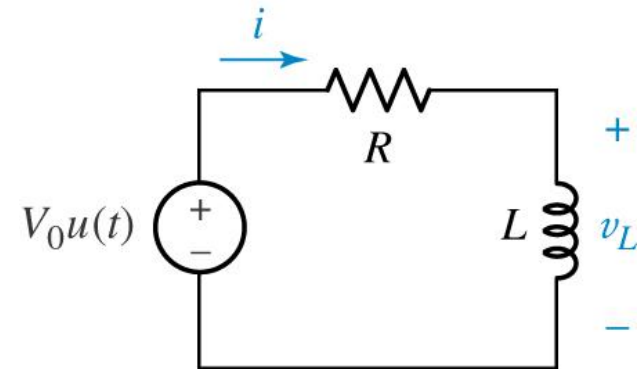
# Instantaneous Power:

Consider the series RL circuit,

$$i(t) = \frac{V_0}{R} (1 - e^{-Rt/L}) u(t)$$



to determine the power absorbed by the inductor, first

$$\begin{aligned} v_L(t) &= L \frac{di(t)}{dt} \\ &= V_0 e^{-Rt/L} u(t) + \frac{LV_0}{R} (1 - e^{-Rt/L}) \frac{du(t)}{dt} \\ &= V_0 e^{-Rt/L} u(t) \end{aligned}$$



Then,

$$p_L(t) = v_L(t)i(t) = \frac{V_0^2}{R} e^{-Rt/L} (1 - e^{-Rt/L})^2 u(t)$$

# Instantaneous Power:


Consider the series RL circuit,

$$p(t) = p_R(t) + p_L(t)$$

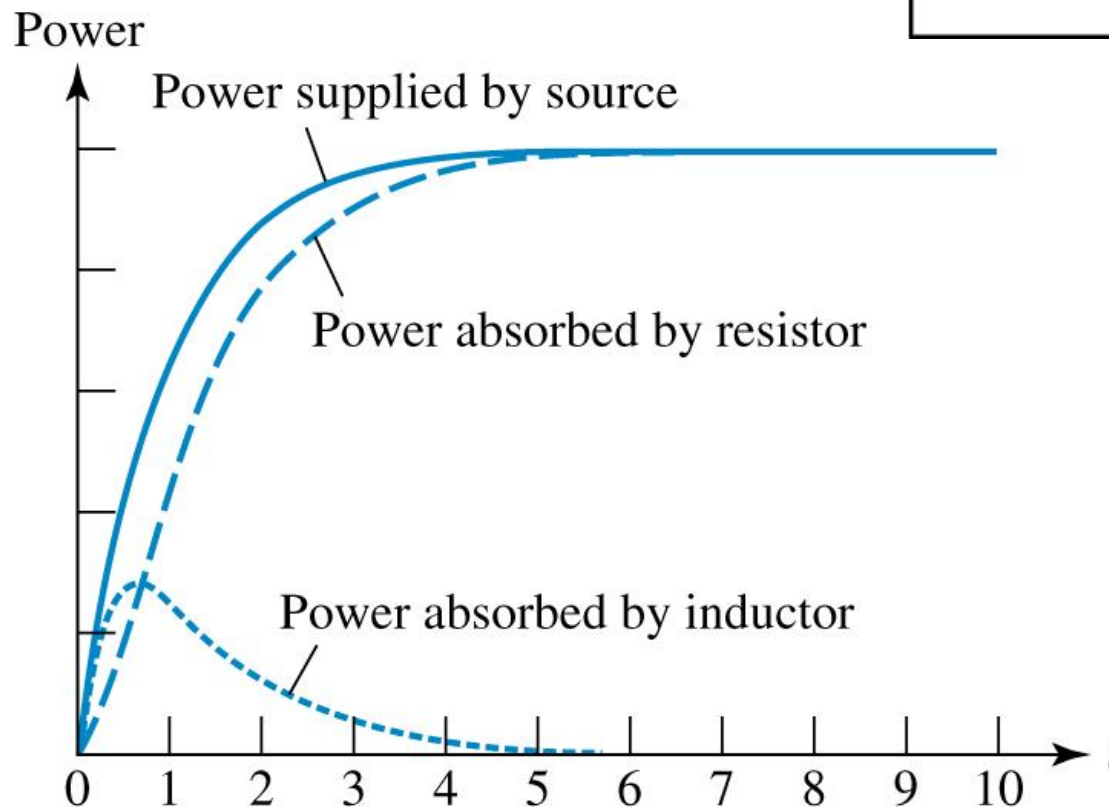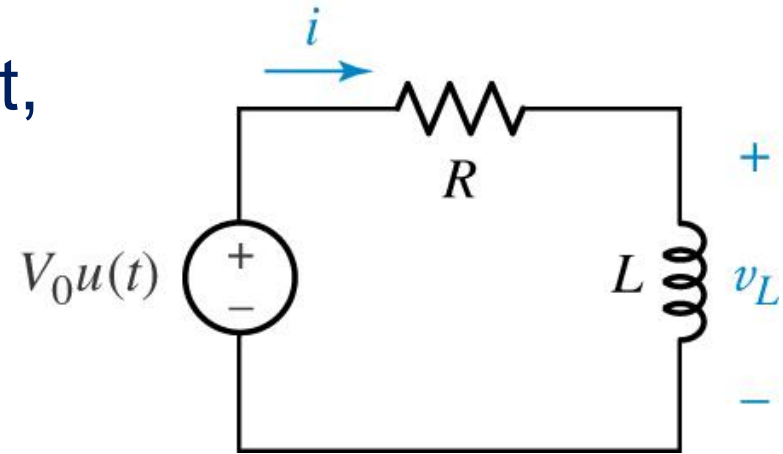

# Instantaneous Power:

Power Due to Sinusoidal Excitation:

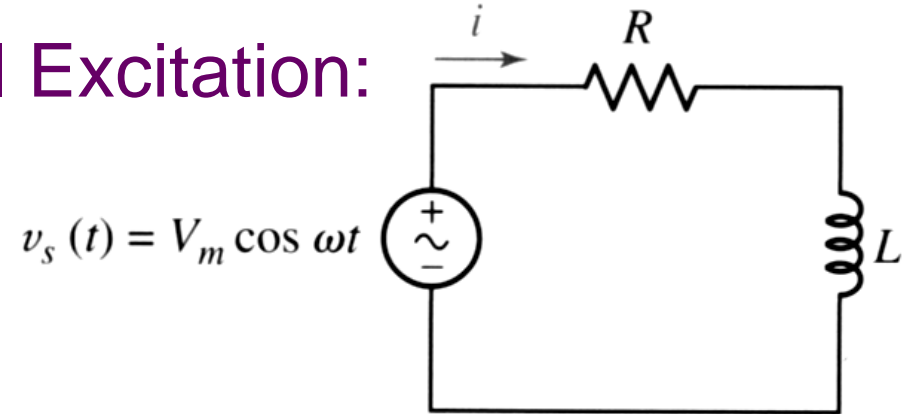

the response is

$$i(t) = I_m \cos(\omega t + \phi)$$

Where

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$

$$\phi = -\tan^{-1} \frac{\omega L}{R}$$



# Practice: 11.1

---

A current source of  $12\cos(2000t)$  A., a 200-ohm resistor, and a 0.2-H inductor are in parallel. Assume steady-state conditions exist. At  $t = 1\text{ ms.}$ , find the power being absorbed by the

- (a) resistor
- (b) inductor
- (c) sinusoidal source

# Practice: 11.1

---

- define voltage  $v(t)$  across the parallel combination

$$12\angle 0^\circ = \frac{\mathbf{V}}{200} + \frac{\mathbf{V}}{j0.2(2000)}$$

where  $\mathbf{V} = 2147\angle 26.57^\circ \text{ V}$  so  $v(t) = 2147 \cos(2000t + 26.57^\circ) \text{ V}$

$$(a) \quad P_R(t) = \frac{v^2(t)}{200} \text{ so } P(0.001) = \underline{13.98 \text{ kW}}$$

$$(b) \quad i_L(t) = 12 \cos 2000t - \frac{v(t)}{200}$$

$$v(0.001) = -1672 \text{ V} \text{ so } i_L(0.001) = 3.366 \text{ A}$$


$$\text{Thus, } P_L(0.001) = -1672 \times 3.366 = \underline{-5.628 \text{ kW}}$$

$$(c) \quad P_S(0.001) = -(13.98 - 5.628) = \underline{-8.352 \text{ kW (absorbed)}}$$
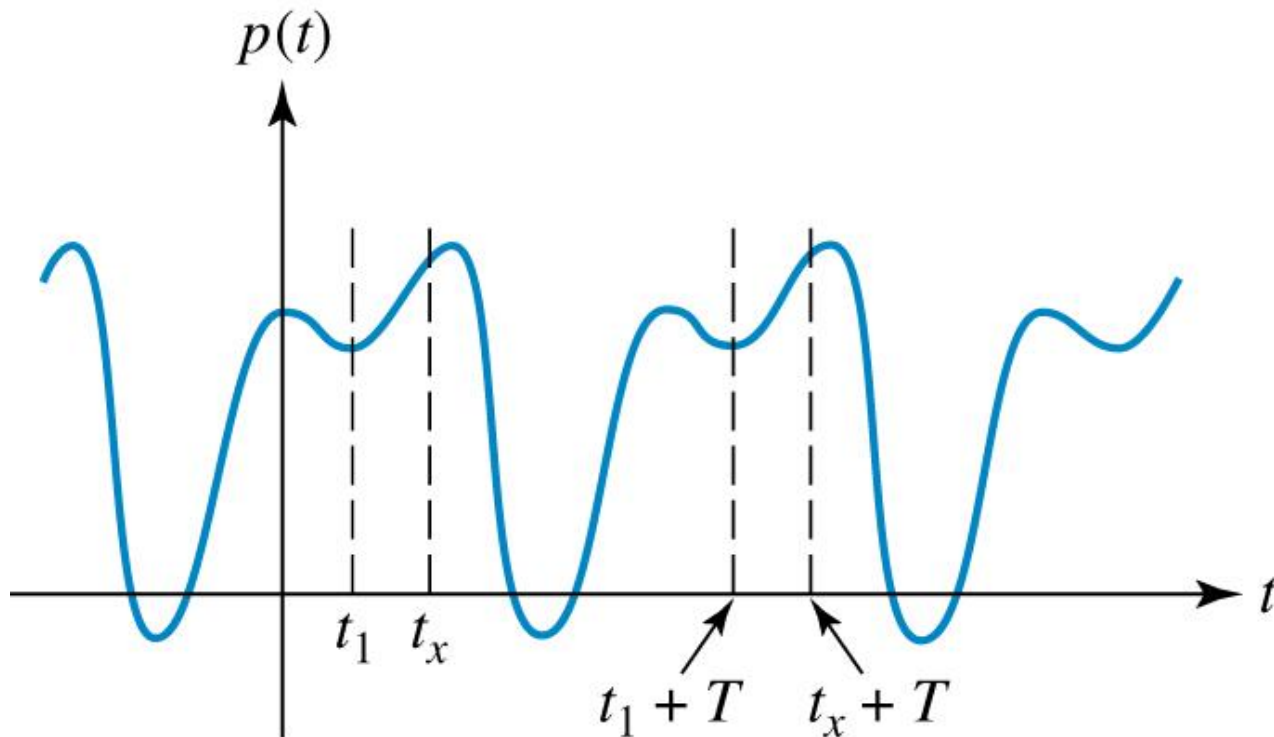
# Average Power:

$$P = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} p(t) dt$$

For Periodic Waveforms:  $f(t) = f(t + T)$




$$P_1 = \frac{1}{T} \int_{t_1}^{t_1+T} p(t) dt$$

$$P_x = \frac{1}{T} \int_{t_x}^{t_x+T} p(t) dt$$

# Average Power:

For Periodic Waveforms:

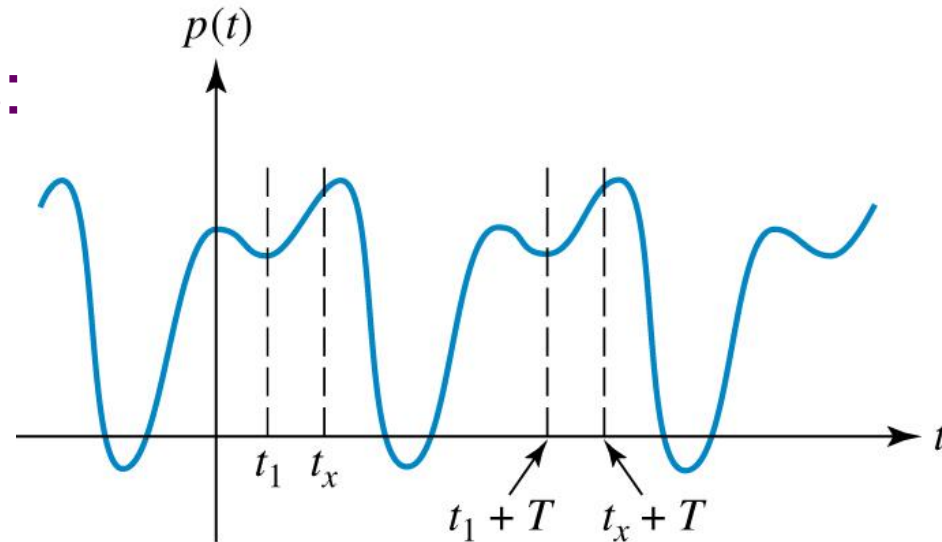


$$P = \frac{1}{nT} \int_{t_x}^{t_x + nT} p(t) dt \quad n = 1, 2, 3, \dots$$

$$P = \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt$$

$$P = \lim_{n \rightarrow \infty} \frac{1}{nT} \int_{-nT/2}^{nT/2} p(t) dt$$
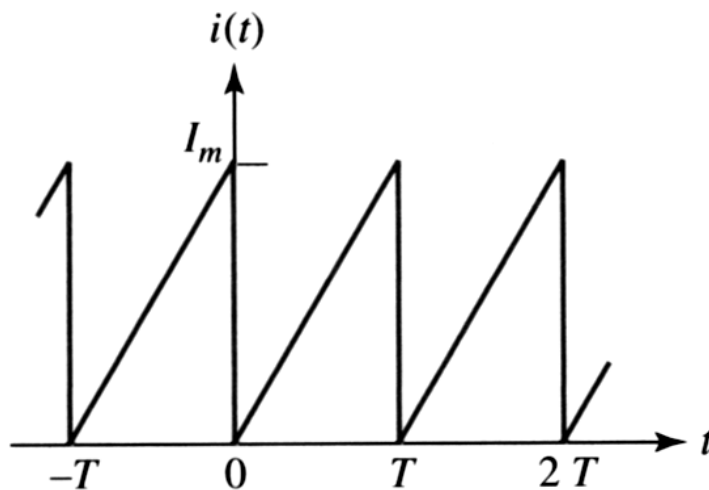
# Example:

find the average power delivered to a resistor  $R$  by the periodic sawtooth current waveform




$$i(t) = \frac{I_m}{T} t, \quad 0 < t \leq T$$

$$i(t) = \frac{I_m}{T} (t - T), \quad T < t \leq 2T$$

$$p(t) = v(t)i(t) = i^2(t)R = \frac{v^2(t)}{R}$$

# Example:

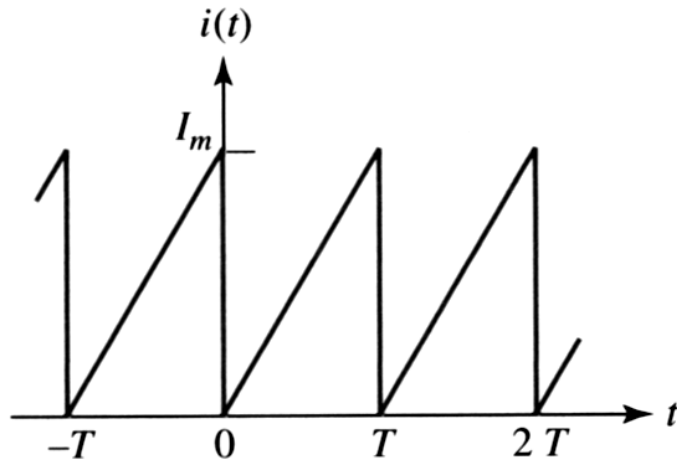


(a)

$$i(t) = \frac{I_m}{T} t, \quad 0 < t \leq T$$

$$i(t) = \frac{I_m}{T} (t - T), \quad T < t \leq 2T$$
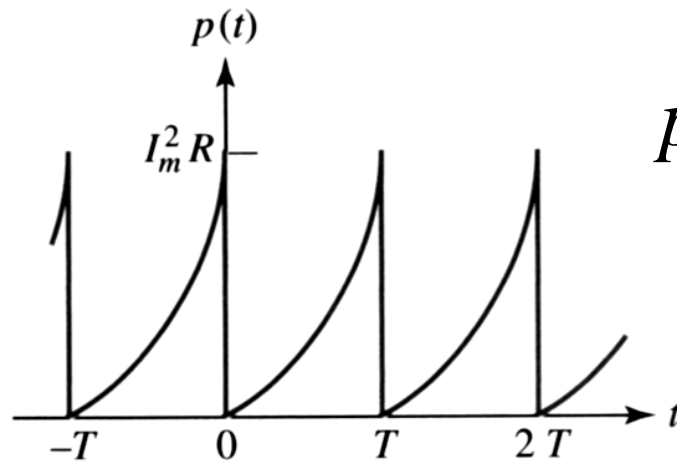
$$p(t) = \frac{1}{T^2} I_m^2 R t^2, \quad 0 < t \leq T$$



(b)

$$p(t) = \frac{1}{T^2} I_m^2 R (t - T)^2, \quad T < t \leq 2T$$

$$P = \frac{1}{T} \int_0^T \frac{I_m^2 R}{T^2} t^2 dt = \frac{1}{3} I_m^2 R$$

# Average Power:

---

In the Sinusoidal Steady State

$$v(t) = V_m \cos(\omega t + \theta)$$

$$i(t) = I_m \cos(\omega t + \phi)$$

the instantaneous power is

$$p(t) = V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi)$$

Or 
$$p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi)$$

By inspection:

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

# Example:

---

Given the time-domain voltage  $v = 4\cos(\pi t / 6)$  V., find both the **average power** and an expression for the **instantaneous power** that result when the corresponding phasor voltage  $\mathbf{V} = 4 \angle 0^\circ$  V. is applied across an impedance  $\mathbf{Z} = 2 \angle 60^\circ$  ohm.

Sol:



# Example:

---

$$v = 4 \cos(\pi t / 6) \text{ V.} \rightarrow \mathbf{V} = 4 \angle 0^\circ \text{ V.}$$

$$\mathbf{Z} = 2 \angle 60^\circ \text{ ohm.}$$

Sol:

The **phasor current** is  $\mathbf{V}/\mathbf{Z} = 2 \angle -60^\circ \rightarrow i = 2 \cos(\pi t / 6 - 60^\circ)$

So the **average power** is:

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$$

$$= \frac{1}{2} (4)(2) \cos(60^\circ) = 2W$$

# Example:


---

$$v = 4 \cos(\pi t / 6) \qquad i = 2 \cos(\pi t / 6 - 60^\circ)$$

the instantaneous power is:

$$\begin{aligned} p(t) &= V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi) \\ &= \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi) \\ &= 8 \cos\left(\frac{\pi t}{6}\right) \cos\left(\frac{\pi t}{6} - 60^\circ\right) = 2 + 4 \cos\left(\frac{\pi t}{3} - 60^\circ\right) \end{aligned}$$

# Example:

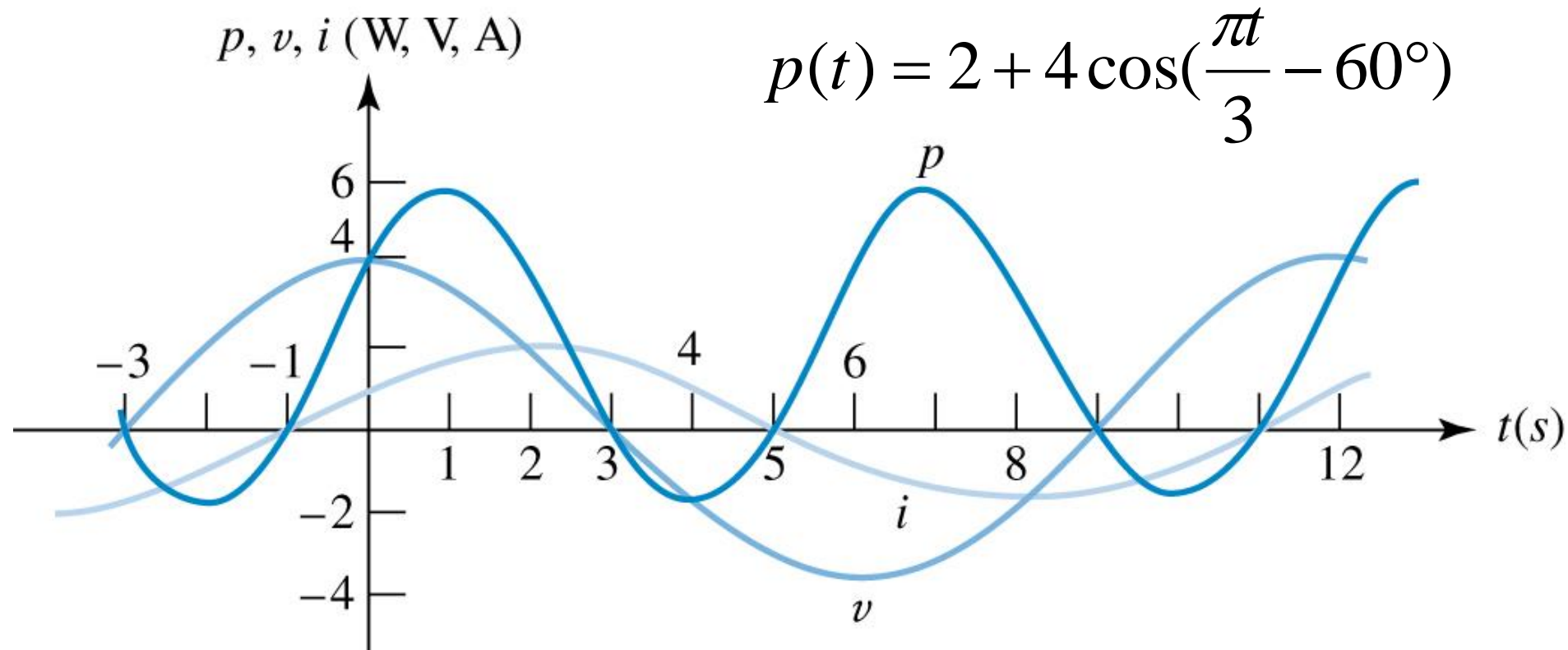

$$v = 4 \cos(\pi t / 6)$$

$$i = 2 \cos(\pi t / 6 - 60^\circ)$$

## Practice: 11.2

---

Given the phasor voltage  $\mathbf{V} = 115\sqrt{2} \angle 45^\circ$  V. across an impedance  $\mathbf{Z} = 16.26 \angle 19.3^\circ$  ohm., obtain an expression for the instantaneous power, and compute the average power if  $\omega = 50$  rad/s.

**Sol:**

$$p(t) = V_m I_m \cos(\omega t + \theta) \cos(\omega t + \phi)$$

$$p(t) = \frac{1}{2} V_m I_m \cos(\theta - \phi) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta + \phi)$$

# Practice: 11.2

---

$$\mathbf{I} = \frac{\mathbf{V}}{\mathbf{Z}} = \frac{115\sqrt{2}\angle 45^\circ}{16.26\angle 19.3^\circ} = 10\angle 25.7^\circ \text{ A}$$

$$\begin{aligned} P(t) &= 115\sqrt{2} \cos(\omega t + 45^\circ) \cdot 10 \cos(\omega t + 25.7^\circ) \\ &= \frac{1150\sqrt{2}}{2} [\cos(2\omega t + 45^\circ + 25.7^\circ) + \cos(45^\circ - 25.7^\circ)] \\ &= \underline{767.5 + 813.2 \cos(2\omega t + 70.7^\circ) \text{ W}} \quad \text{and} \quad \underline{P = 767.5 \text{ W}} \end{aligned}$$

# Average Power:

---

Absorbed by an Ideal Resistor:

$$P_R = \frac{1}{2} V_m I_m \cos(0) = \frac{1}{2} V_m I_m$$

Or

$$P_R = \frac{1}{2} I_m^2 R = \frac{V_m^2}{2R}$$

Absorbed by Purely Reactive Elements:

$$P_x = 0$$

# Example:

---

Find the average power being delivered to an impedance  $\mathbf{Z_L} = 8 - j11$  ohm. by a current  $\mathbf{I} = 5 \angle 20^\circ$  A.

Sol:

$$P_R = \frac{1}{2} I_m^2 R = \frac{1}{2} (5)^2 8 = 100 \text{ W.}$$

# Practice: 11.3

---

Calculate the average power delivered to the impedance  $6\angle 25^\circ \Omega$  by the current  $\mathbf{I} = 2 + j5 \text{ A}$ .

$$\mathbf{I} = 2 + j5 = 5.385 \angle 68.20^\circ \text{ A}$$

$$6\angle 25^\circ \Omega = 5.438 + j2.536 \Omega$$


$$\therefore P = \frac{1}{2} (5.385)^2 \square 5.438 = \underline{78.85 \text{ W}}$$



# Practice: 11.4


Compute the average power delivered to each of the passive elements.

Sol:

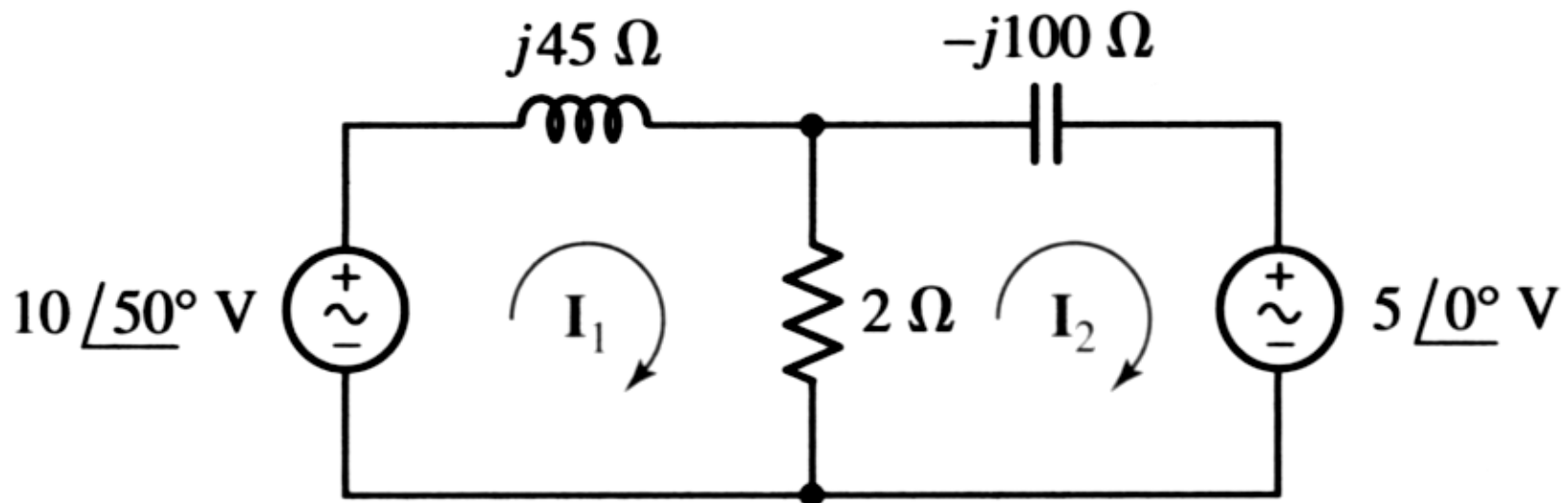

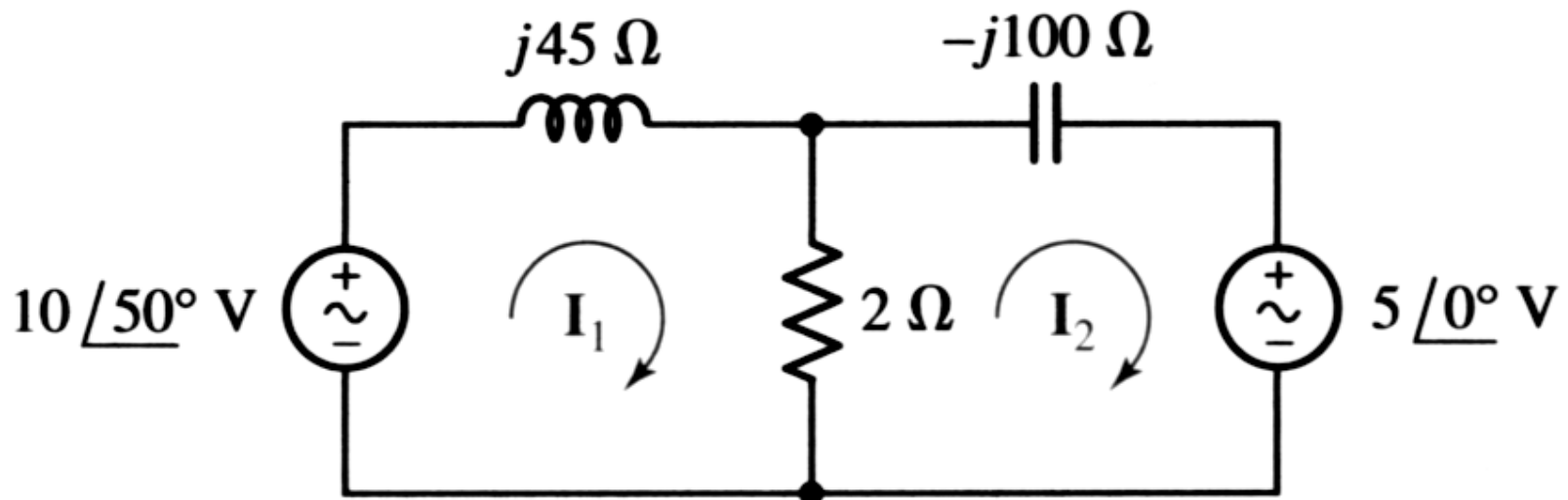
# Practice: 11.4

For the circuit in the figure below, compute the average power delivered to each of the passive elements. Verify your answer by computing the power delivered by the two sources.



# Practice: 11.4

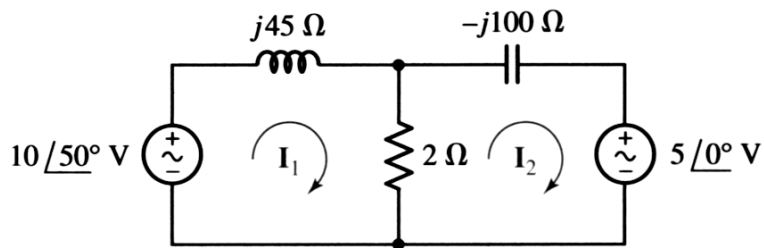

mesh 1:  $10\angle 50^\circ = (2 + j45)\mathbf{I}_1 - 2\mathbf{I}_2$


mesh 2:  $-5 = -2\mathbf{I}_1 + (2 - j100)\mathbf{I}_2$

Solving,  $\mathbf{I}_1 = 0.1742 - j0.1352 \text{ A} = 0.2205\angle -37.82^\circ \text{ A}$

$\mathbf{I}_2 = 0.0018 - j0.0466 \text{ A} = 0.04664\angle -87.79^\circ \text{ A}$

# Practice: 11.4

So

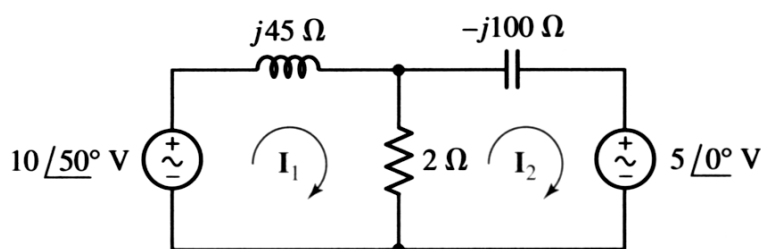

$$P_{2\Omega} = \frac{1}{2} (I_1 - I_2)^2 \times 2 = (0.1938)^2 = \underline{37.56 \text{ mW}}$$

The left source supplies

$$P = \frac{1}{2} (10)(0.2205) \cos(50^\circ + 37.82^\circ) = 41.94 \text{ mW}$$


and the right source supplies

$$P = -\frac{1}{2} (5)(0.04664) \cos(87.79^\circ) = -4.496 \text{ mW}$$

$$41.94 - 4.496 = 37.44 \text{ mW} - \text{agrees within rounding error}$$

# Maximum Power Transfer:


---

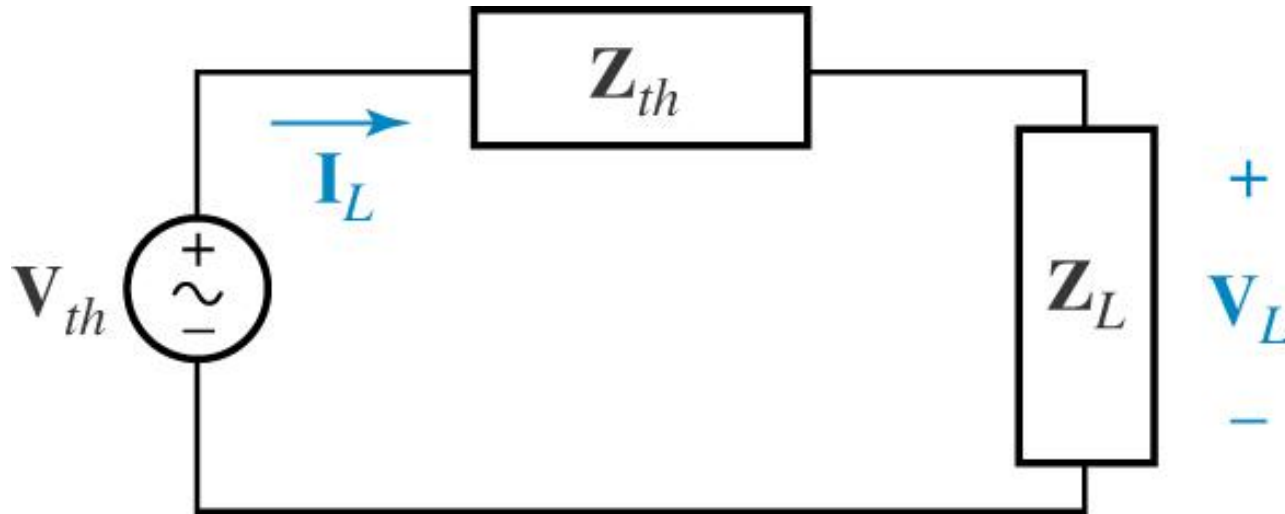

An independent voltage source in *series* with an impedance  $\mathbf{Z}_{th}$  delivers a **maximum average power** to that load impedance  $\mathbf{Z}_L$  which is the conjugate of  $\mathbf{Z}_{th}$ , or  $\mathbf{Z}_L = \mathbf{Z}_{th}^*$
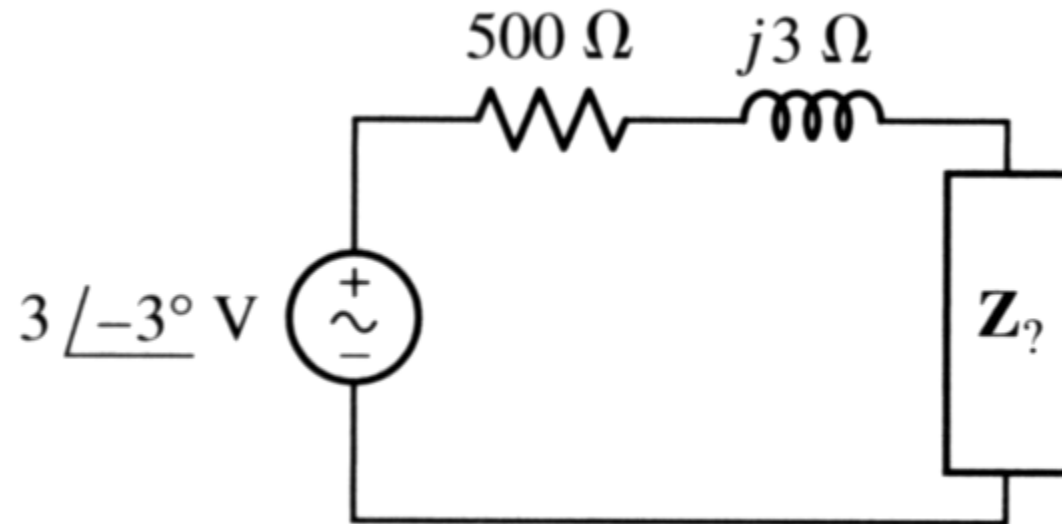
## Example 11.5:

If we are assured that the voltage source is delivering maximum average power to the unknown impedance, what is its value?




Sol:

$$Z_? = Z_{th}^* = 500 - j3 \quad \Omega$$
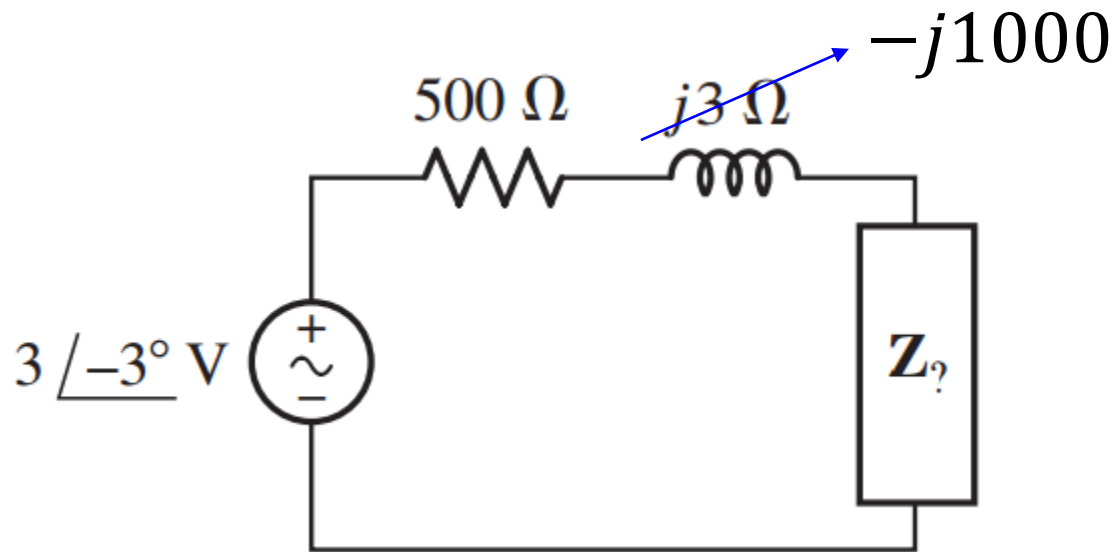
# Practice: 11.5

If the 30-mH inductor of Example 11.5 is replaced with a  $10\text{-}\mu\text{F}$  capacitor, what is the value of the inductive component of the unknown impedance  $\mathbf{Z}_?$  if it is known that  $\mathbf{Z}_?$  is absorbing maximum power?



# Practice: 11.5

---

$$\mathbf{Z}_{TH} = 500 - \frac{j}{(100)(10 \times 10^{-6})} = 500 - j1000 \, \Omega$$

$\mathbf{Z}_L$  must be  $\mathbf{Z}_{TH}^* = 500 + j1000 \, \Omega$  if it is absorbing maximum power.

Thus, the inductive component of the load is  $\frac{1000}{100} = \underline{10 \, \text{H}}$



# Average Power:

---

For Nonperiodic Function: for example

$$i(t) = \sin t + \sin \pi t$$

the average power delivered to a 1 ohm resistor:

$$\begin{aligned}
 P &= \lim_{\tau \rightarrow \infty} \frac{1}{\tau} \int_{-\tau/2}^{\tau/2} (\sin^2 t + \sin^2 \pi t + 2 \sin t \sin \pi t) dt \\
 &= \frac{1}{2} + \frac{1}{2} = 1 \quad \text{Watt}
 \end{aligned}$$

# Average Power:

---

For

$$i(t) = I_{m1} \cos \omega_1 t + I_{m2} \cos \omega_2 t + \dots + I_{mN} \cos \omega_N t$$

the average power delivered to a resistor R:

$$P = \frac{1}{2} (I_{m1}^2 + I_{m2}^2 + \dots + I_{mN}^2) R$$

A voltage source  $v_s$  is connected across a  $4\text{-}\Omega$  resistor. Find the average power absorbed by the resistor if  $v_s$  equals (a)  $8\sin 200t$  (b)  $8\sin 200t - 6\cos(200t - 45^\circ)$  V. (c)  $8\sin 200t - 4\sin 100t$  V. (d)  $8\sin 200t - 6\cos(200t - 45^\circ) - 5\sin 100t + 4$  V.

# Practice: 11.6

---

$$(a) \quad P = \frac{1}{2} \frac{(8)^2}{4} = \underline{8 \text{ W}}$$

$$(b) \quad \mathbf{V}_s = 8\angle -90^\circ - 6\angle -45^\circ = 5.667\angle -138.5^\circ \text{ V}$$

$$\therefore P = \frac{1}{2} \frac{(5.667)^2}{4} = \underline{4.014 \text{ W}}$$

$$(c) \quad P = \frac{1}{2} \frac{8^2}{4} + \frac{1}{2} \frac{4^2}{4} = \underline{10 \text{ W}}$$

(the sinusoids have different frequencies, so superposition applies to this power calculation).

$$(d) \quad \text{Combining the two sinusoids with } \omega = 200 \text{ rad/s,}$$


$$8\angle -90^\circ - 6\angle -45^\circ = 5.667\angle -138.5^\circ \text{ V}$$

$$\therefore P = \frac{1}{2} \frac{(5.667)^2}{4} + \frac{1}{2} \left( \frac{5^2}{4} \right) + \frac{4^2}{4} = \underline{11.14 \text{ W}}$$


(the average power provided by the dc source is simply 4 W; it operates at a “frequency” different from the other sources).
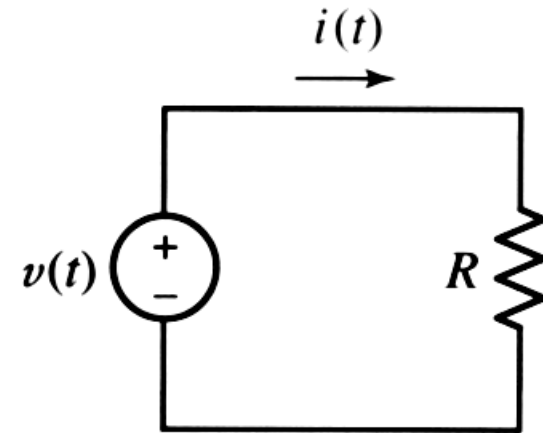
# Effective Values:

If the resistor received the same average power in part (a) and (b), then the effective value of  $i(t)$  is equal to  $I_{\text{eff}}$ , and the effective value of  $v(t)$  is equal to  $V_{\text{eff}}$



(a)

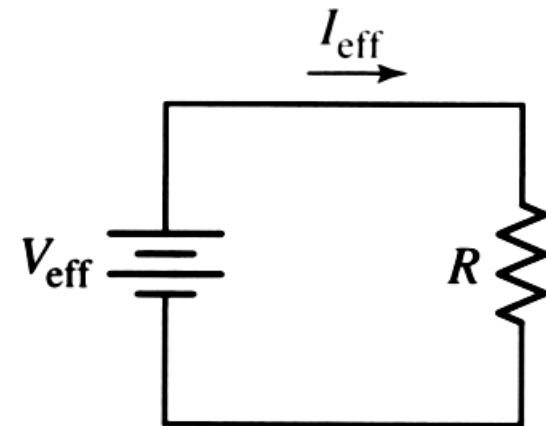

(b)


# Effective Values:

of a Periodic Waveform:  
the **average power** delivered  
to the resistor,


$$P = \frac{1}{T} \int_0^T i^2 dt = \frac{R}{T} \int_0^T i^2 dt$$

the power delivered by the  
direct current is:

$$P = I_{eff}^2 R$$

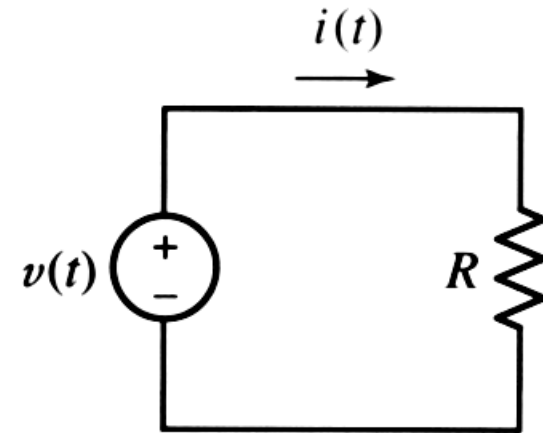

(a)

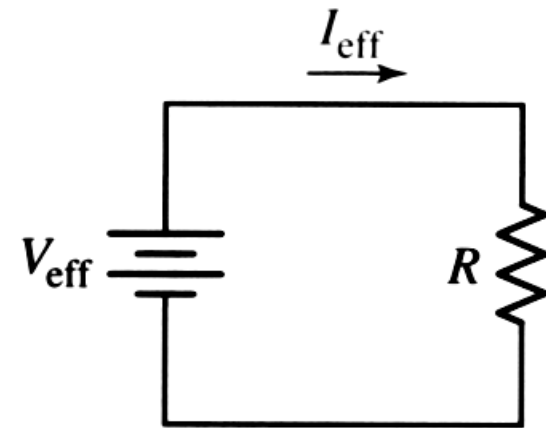

(b)

# Effective Values:


of a Periodic Waveform:

$$\frac{R}{T} \int_0^T i^2 dt = I_{eff}^2 R$$


we get

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

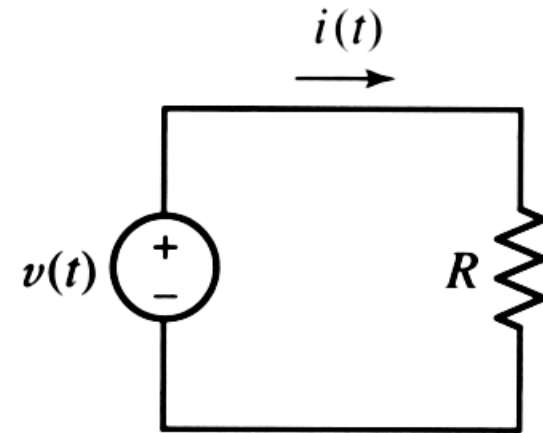**note:** the effective value is often called the **root-mean-square** value, or simply the **rms** value.



(a)

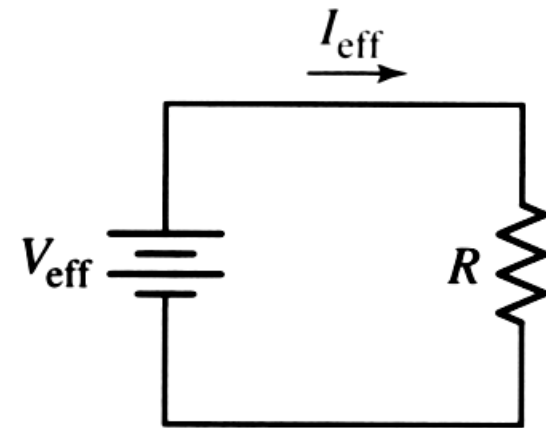

(b)

# Effective Values:

of a sinusoidal Waveform:

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

which has a period  $T = \frac{2\pi}{\omega}$

to obtain the effective value

$$\begin{aligned} I_{eff} &= \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt} \\ &= I_m \sqrt{\frac{\omega}{2\pi} \int_0^{2\pi/\omega} \left[ \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) \right] dt} \end{aligned}$$



# Effective Values:

of a sinusoidal Waveform

$$i(t) = I_m \cos(\omega t + \phi)$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \cos^2(\omega t + \phi) dt}$$

$$= I_m \sqrt{\frac{\omega}{2\pi} \int_0^{2\pi/\omega} \left[ \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) \right] dt}$$

$$= I_m \sqrt{\frac{\omega}{4\pi} [t]_0^{2\pi/\omega}}$$

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

# Effective Values:

---

Use of RMS Values to  
Compute Average Power

$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

$$P = \frac{1}{2} I_m^2 R = I_{eff}^2 R = \frac{V_{eff}^2}{R}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

# Effective Values:

---

with Multiple-Frequency  
Circuits


$$I_{eff} = \frac{I_m}{\sqrt{2}}$$

$$P = (I_{1eff}^2 + I_{2eff}^2 + \dots + I_{Neff}^2)R$$

$$I_{eff} = \sqrt{I_{1eff}^2 + I_{2eff}^2 + \dots + I_{Neff}^2}$$
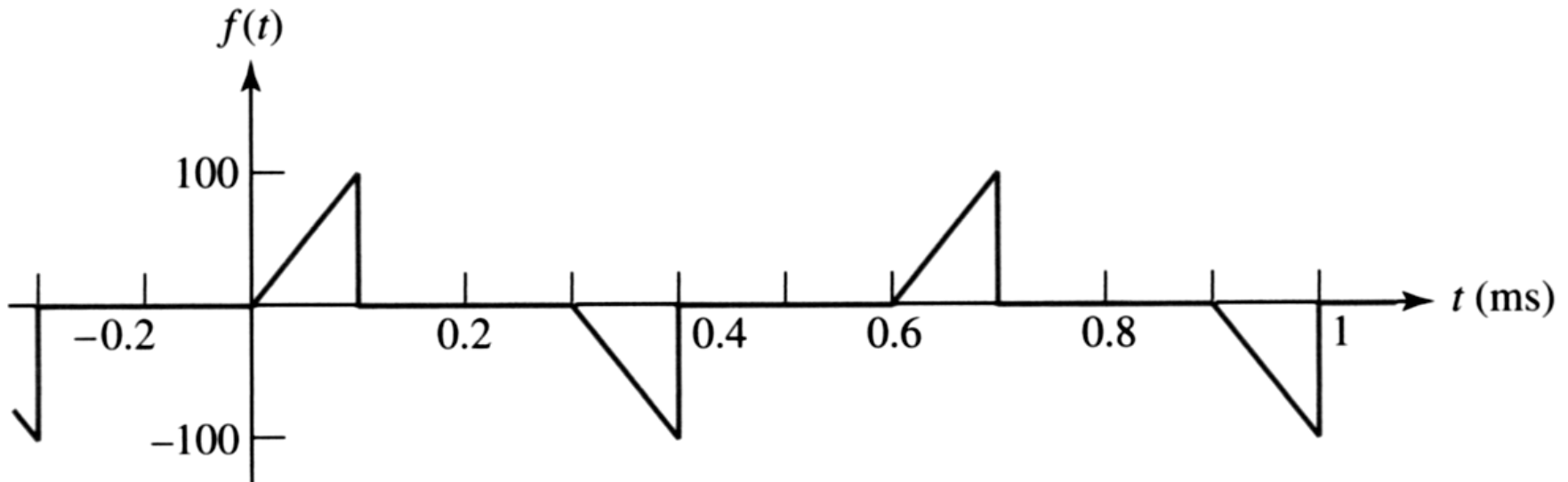
# Effective Values: Example

Ex22 Page 384: find the effective value of:



$$I_{eff} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$$

Calculate the effective value of each of the periodic voltages: (a)  $6\cos 25t$ ; (b)  $6\cos 25t + 4\sin(25t + 30^\circ)$  V. (c)  $6\cos 25t + 5\cos^2(25t)$  V. (d)  $6\cos 25t + 5\sin 30t + 4$  V.

$$(a) \quad \frac{6}{\sqrt{2}} = \underline{4.243}$$

$$(b) \quad 6 \cos 25t + 4 \sin (25t + 30^\circ)$$

may be combined:  $6 \angle 0^\circ + 4 \angle (30^\circ - 90^\circ) = 8.718 \angle -23.41^\circ$

$$\therefore \text{effective value is } \frac{8.718}{\sqrt{2}} = \underline{6.165}$$

$$(c) \quad \cos^2 25t = \frac{1}{2}(1 + \cos 50t)$$

The effective value is

$$\begin{aligned} & \left[ \frac{1}{T} \int_0^T (6 \cos 25t + 5 \cos^2 25t)^2 dt \right]^{1/2} \\ &= \left[ \frac{1}{T} \int_0^T (36 \cos^2 25t + 60 \cos^3 25t + 25 \cos^4 25t) dt \right]^{1/2} \\ &= \left[ \frac{1}{T} \int_0^T 36 \cos^2 25t dt + \frac{1}{T} \int_0^T 60 \cos^3 25t dt + \frac{1}{T} \int_0^T 25 \cos^4 25t dt \right]^{1/2} \end{aligned}$$

where  $T = \frac{1}{25}$  seconds

Solving each integral, we obtain

# Practice: 11.7

---

$$\left[ \frac{36}{T} \int_0^T \left( \frac{1}{2} + \frac{1}{2} \cos 50t \right) dt + \frac{60}{T} \int_0^T \left( \frac{1}{2} \cos 25t + \frac{1}{4} \cos 75t + \frac{1}{4} \cos 25t \right) dt + \frac{25}{T} \int_0^T \left( \frac{1}{4} + \frac{1}{2} \cos 50t + \frac{1}{8} + \frac{1}{8} \cos 100t \right) dt \right]^{1/2}$$

$$= \left[ \frac{36 \times 25}{2} \left( \frac{1}{25} \right) + (60)(25)(0) + (25)(25) \left( \frac{1}{4} + \frac{1}{8} \right) \left( \frac{1}{25} \right) \right]^{1/2}$$

$$= \sqrt{18 + \frac{75}{8}} = \underline{5.232}$$

$$(d) \quad [36 + 25 + 16]^{1/2} = \underline{8.775}$$



# Apparent power and Power factor: <sup>Page 49</sup>

---

The sinusoidal voltage  $v = V_m \cos(\omega t + \theta)$

is applied to the network and the resultant sinusoidal current is

$$i = I_m \cos(\omega t + \phi)$$

the average power delivered to the network


$$P = \frac{1}{2} V_m I_m \cos(\theta - \phi) = V_{eff} I_{eff} \cos(\theta - \phi)$$

the apparent power:  $V_{eff} I_{eff}$

the power factor:  $PF = \frac{P}{V_{eff} I_{eff}}$

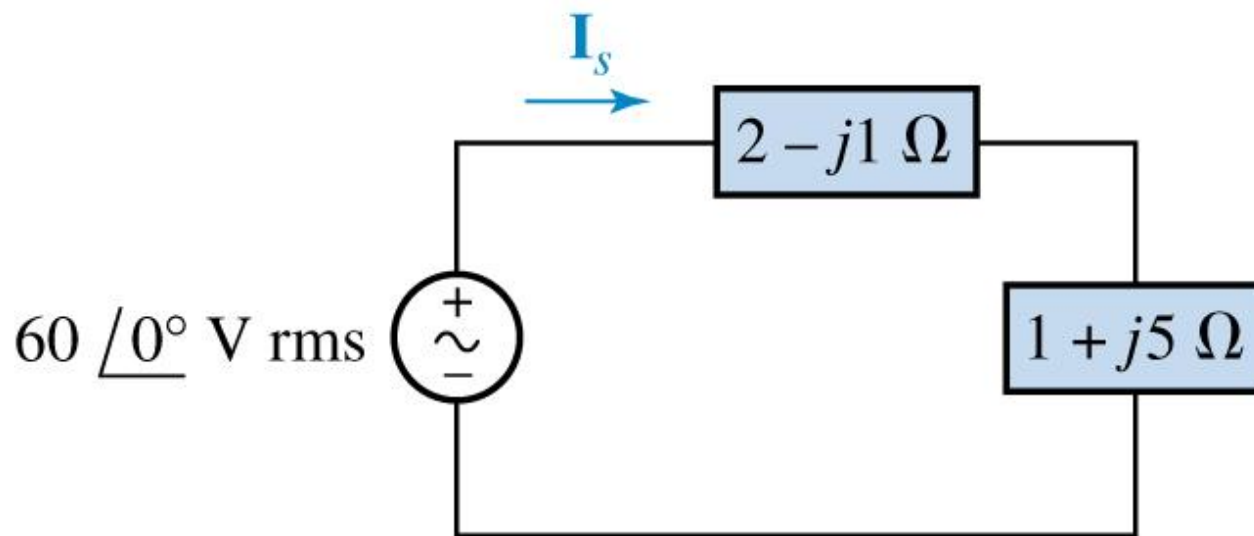
# Example:

Calculate values for the average power delivered to each of the two loads, the apparent power supplied by the source, and the power factor of the combined load.


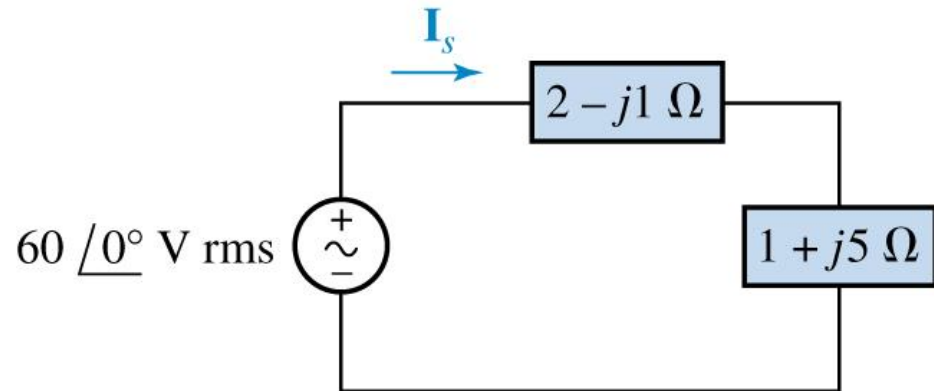
# Example:

Calculate values for the average power delivered to each of the two loads, the apparent power supplied by the source, and the power factor of the combined load.




$$P = V_{eff} I_{eff} \cos(\text{ang} V - \text{ang} I)$$

$$V_{eff} I_{eff}$$

$$PF = \frac{P}{V_{eff} I_{eff}}$$

# Example:

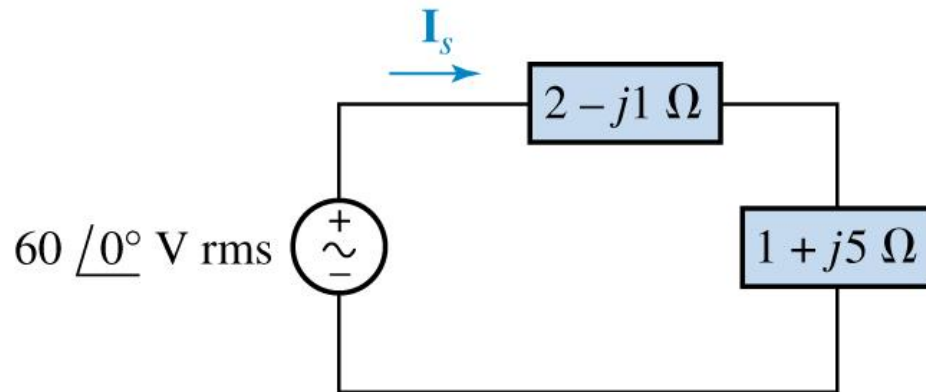

$$3 + j4 = 5 \angle -53.13^\circ$$

$$I_s = \frac{60 \angle 0^\circ}{(2 - j1) + (1 + j5)} = 12 \angle -53.13^\circ \text{ A.rms}$$


$$\begin{aligned} P_s &= V_{eff} I_{eff} \cos(\text{ang} V - \text{ang} I) \\ &= (60) \cdot (12) \cos[0^\circ - (-53.1^\circ)] \\ &= 432 \text{ W.} \end{aligned}$$

# Example:

the apparent power  
supplied by the source:

$$= V_{eff} I_{eff} = (60) \cdot (12) = 720 \text{ VA.}$$

the power factor of the  
combined load.

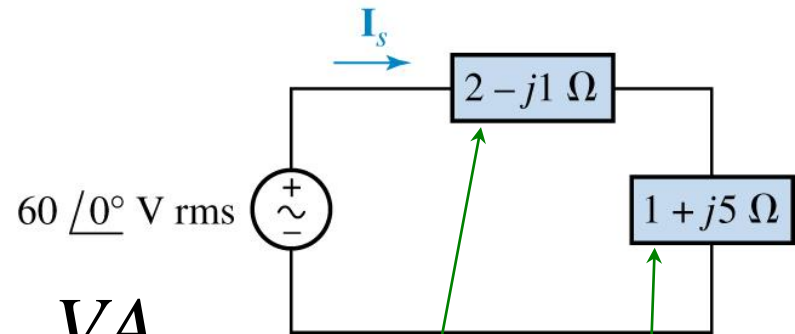


$$P = (12)^2 \cdot 2$$

$$P = (12)^2 \cdot 1$$


$$PF = \frac{P}{V_{eff} I_{eff}} = \frac{432}{(60) \cdot (12)} = 0.6$$
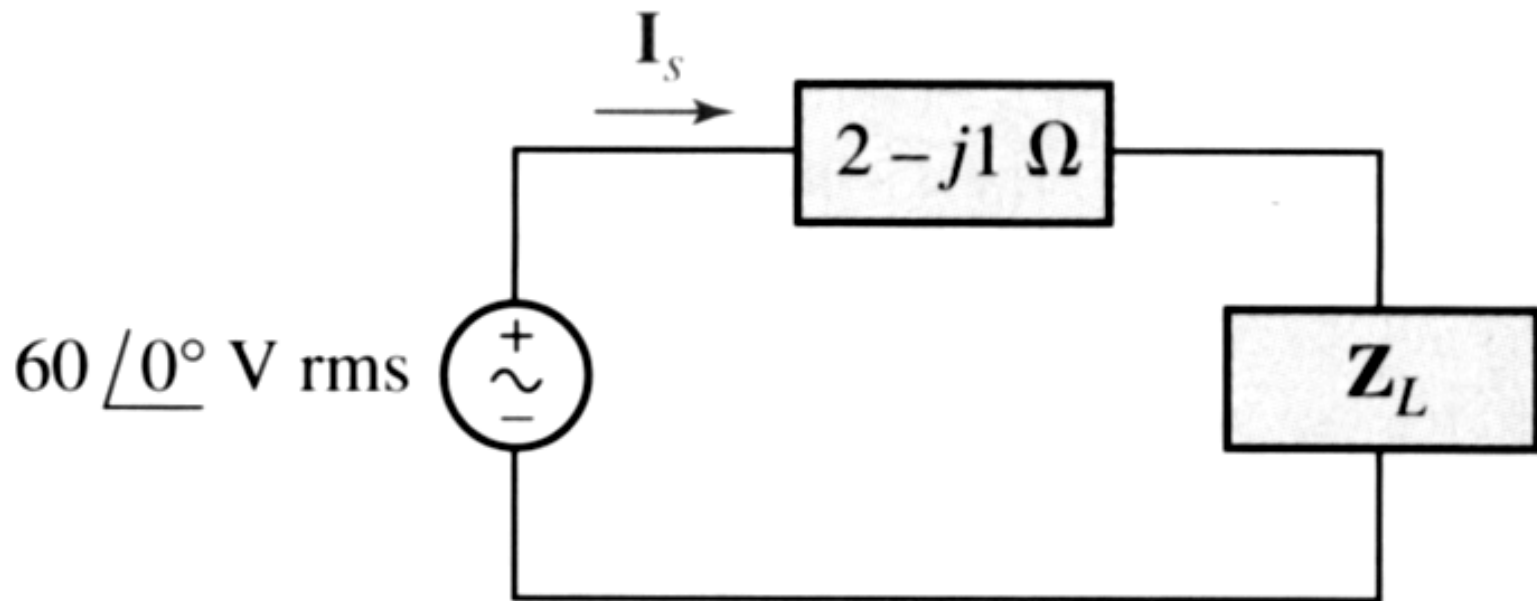
# Practice: 11.8

For the circuit of the figure below, determine the power factor of the combined loads if  $Z_L = 10\Omega$ .



# Practice: 11.8

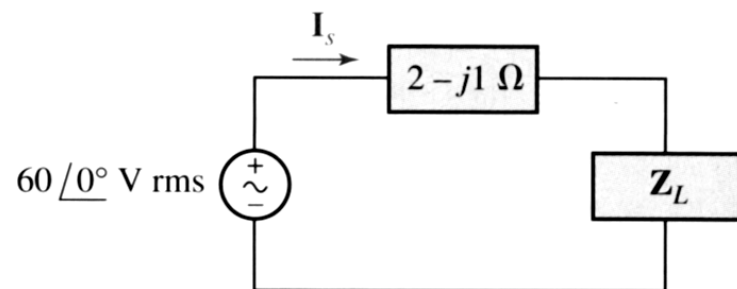

$$\mathbf{I}_s = \frac{60}{2 - j + 10} = 4.983 \angle 4.764^\circ \text{ A rms}$$

$$PF = \cos(0^\circ - 4.764^\circ) = \underline{0.9965 \text{ leading}} \quad (\text{since the current is leading the voltage})$$

# Complex Power:

the average power,

$$P = V_{eff} I_{eff} \cos(\theta - \phi)$$


express as,

$$P = V_{eff} I_{eff} \operatorname{Re}\{e^{j(\theta-\phi)}\} = \operatorname{Re}\{V_{eff} e^{j\theta} I_{eff} e^{-j\phi}\} = \operatorname{Re}\{V_{eff} \mathbf{I}_{eff}^*\}$$

the complex power,

$$S = V_{eff} \mathbf{I}_{eff}^* = V_{eff} I_{eff} e^{j(\theta-\phi)} = P + jQ$$

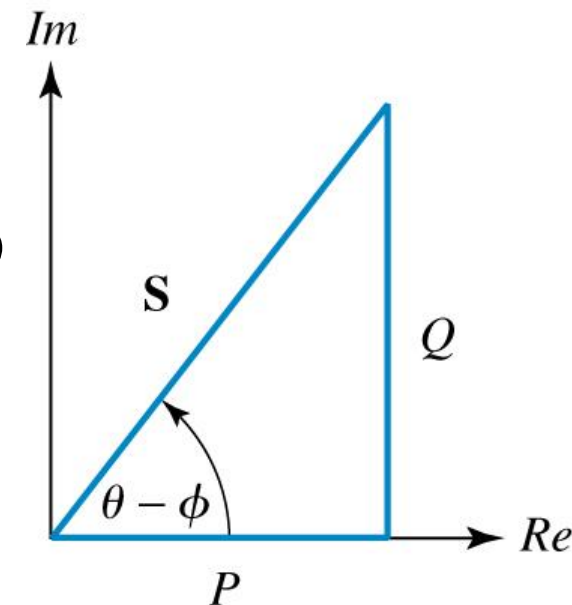
$$Q = V_{eff} I_{eff} \sin(\theta - \phi)$$




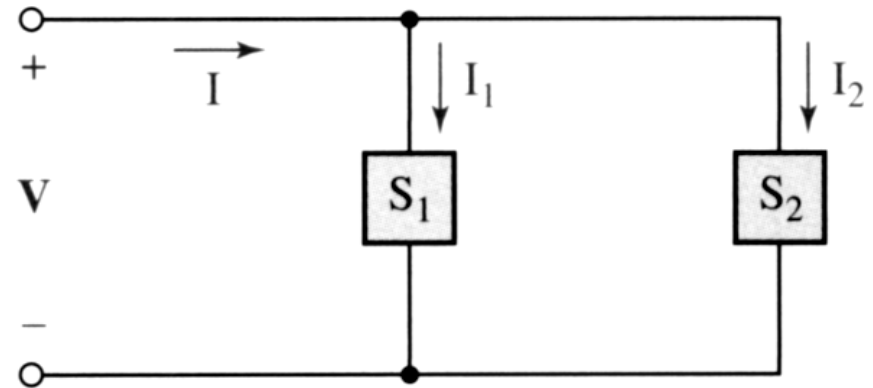
# Power Measurement:



The complex power delivered to several interconnected loads is the sum of the complex power delivered to each of the individual loads.



$$\mathbf{S} = \mathbf{V}\mathbf{I}^* = \mathbf{V}(\mathbf{I}_1 + \mathbf{I}_2)^* = \mathbf{V}(\mathbf{I}_1^* + \mathbf{I}_2^*) = \mathbf{V}\mathbf{I}_1^* + \mathbf{V}\mathbf{I}_2^*$$
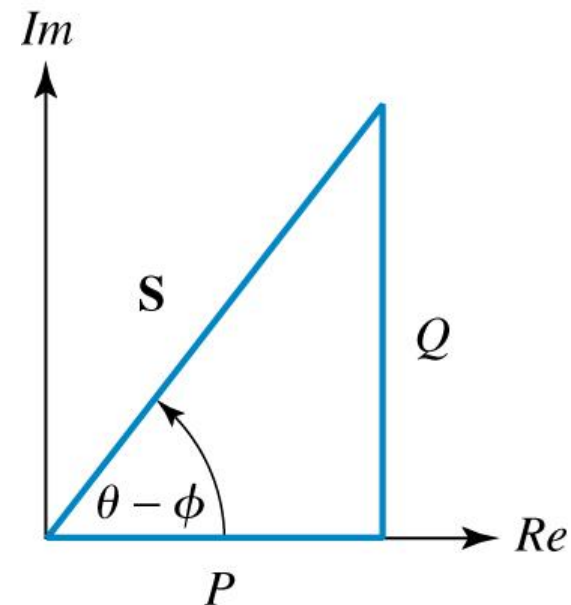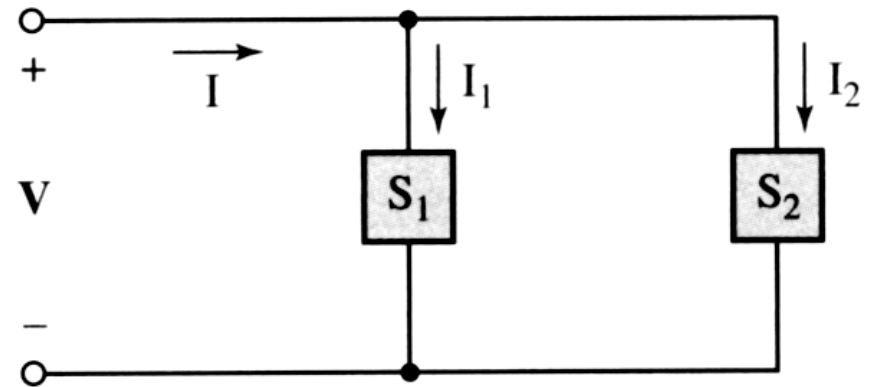
# Example:

An industrial consumer is operating a 50-kW induction motor at a lagging PF of 0.8. The source voltage is 230 Vrms. In order to obtain lower electrical rates, the customer wishes to raise the PF to 0.95 lagging. Specify a suitable solution.



# Example:

---

A purely reactive load must be added to the system, in parallel, since the supply voltage must not change.

The complex power supplied to the motor must have a real part of 50-kW and an angle of

$$\cos^{-1}(0.8)=36.9^{\circ}$$

Hence,

$$\begin{aligned} \mathbf{S}_1 &= \frac{50 \angle 36.9^{\circ}}{0.8} \\ &= 50 + j37.5 \quad kVA \end{aligned}$$

# Example:


$$\mathbf{S}_1 = \frac{50 \angle 36.9^\circ}{0.8} = 50 + j37.5 \quad kVA$$

To achieve a PF of 0.95, the total complex power must become:

$$\begin{aligned} \mathbf{S} &= \frac{50}{0.95} \angle \cos^{-1}(0.95) \\ &= 50 + j16.43 \quad kVA \end{aligned}$$


Thus the corrective load is

$$\mathbf{S}_2 = -j21.07 \quad kVA$$

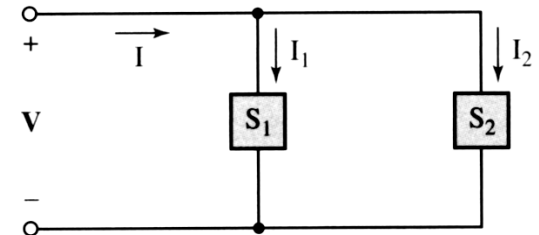

# Example:

$$\mathbf{S}_2 = -j21.07 \text{ kVA}$$

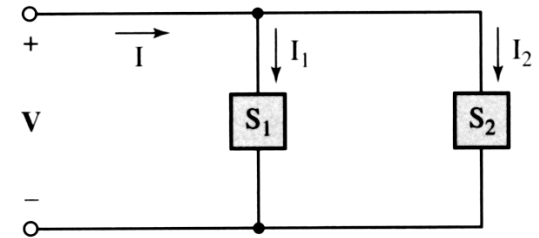

We select a phase angle of  $0^\circ$  for the voltage source, and the current drawn by  $Z_2$  is

$$I_2^* = \frac{S_2}{V} = \frac{-j21070}{230} = -j91.6 \text{ A.}$$


Or 
$$I_2 = j91.6 \text{ A.}$$

Therefore, 
$$Z_2 = \frac{V}{I_2} = \frac{230}{j91.6} = -j2.51 \text{ } \Omega$$


# Practice: 11.9

Find the complex power absorbed by the

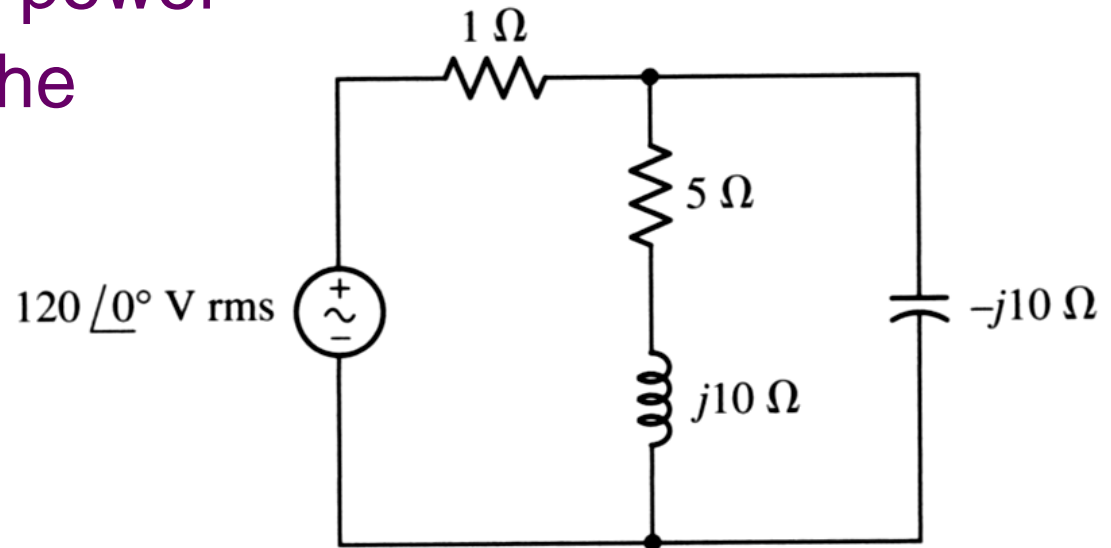- (a) 1-ohm R
- (b)  $-j10\ \Omega$
- (c)  $5+j10\ \Omega$
- (d) source



# Practice: 11.9

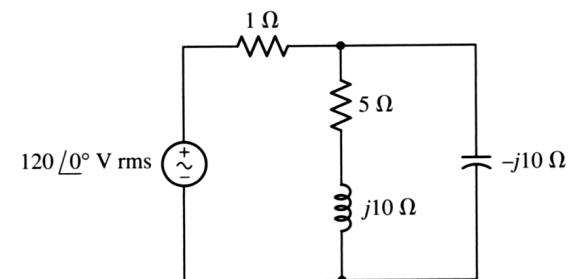

$$\mathbf{Z} = 1 + (5 + j10) // -j10 = 23.26 \angle -25.46^\circ \Omega$$


(a) The current through the  $1\text{-}\Omega$  resistor is

$$\frac{120}{23.26 \angle -25.46^\circ} = 5.159 \angle 25.46^\circ \text{ A rms}$$

so it absorbs a complex power

$$(5.159^2)(1) = \underline{26.62 + j0 \text{ VA}}$$

# Practice: 11.9

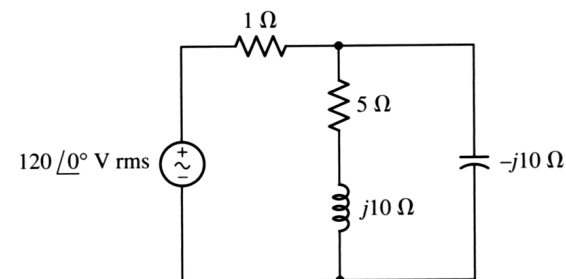

$$(b) \quad (5 + j10) // -j10 = 22.36 \angle -26.57^\circ \Omega$$

so the voltage across the capacitor is

$$120 \angle 0^\circ \left[ \frac{22.36 \angle -26.57^\circ}{1 + 22.36 \angle -26.57^\circ} \right] = 115.4 \angle -1.11^\circ \text{ V rms}$$

and the current through it is


$$\frac{115.4 \angle -1.11^\circ}{-j10} = 11.54 \angle 88.89^\circ \text{ A rms}$$

so the complex power it absorbs is

$$S = (115.4 \angle -1.11^\circ)(11.54 \angle -88.89^\circ) = \underline{1332 \angle -90^\circ \text{ VA}}$$



# Practice: 11.9

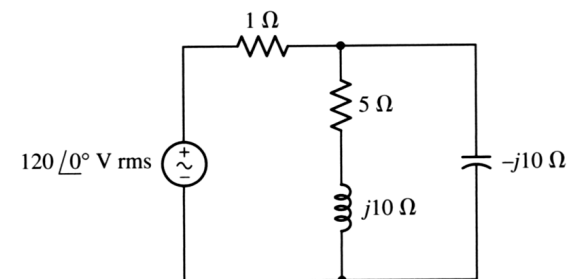

- (c) The current through the  $5 + j10 - \Omega$  impedance is

$$\frac{115.4 \angle -1.11^\circ}{5 + j10} = 10.32 \angle -64.54^\circ \text{ A rms}$$

and so it absorbs complex power

$$\begin{aligned} (115.4 \angle -1.11^\circ)(10.32 \angle +64.54^\circ) &= 1191 \angle 63.43^\circ \text{ VA} \\ &= \underline{532.7 + j1065 \text{ VA}} \text{ (either form is acceptable)} \end{aligned}$$

- (d) The complex power *absorbed* by the source is

$$\begin{aligned} \mathbf{S} &= (120 \angle 0^\circ) (-5.159 \angle +25.46^\circ)^* \\ &= (120 \angle 0^\circ) (5.159 \angle +154.54^\circ) \\ &= 619.1 \angle 154.5^\circ \text{ VA} \\ &= \underline{-559.0 + j266.1 \text{ VA}} \text{ (either form is acceptable)} \end{aligned}$$

# Practice: 11.10

---

A 440-V<sub>rms</sub> source supplies power to a load  $Z_L = 10 + j2 \Omega$  through a transmission line having a total resistance of  $1.5\Omega$ . Find (a) the average and apparent power supplied to the load; (b) the average and apparent power lost in the transmission line; (c) the average and apparent power supplied by the source; (d) the power factor at which the source operates.

# Practice: 11.10

The current through the line and load is

$$\frac{440}{10 + j2 + 1.5} = 37.70 \angle -9.866^\circ \text{ A rms}$$

- (a) The average power supplied to the load is simply  $(37.70^2)(10) = \underline{14.21 \text{ kW}}$ .

The apparent power requires the voltage across the load, which is

$$(37.70 \angle -9.866^\circ)(10 + j2) = 384.5 \angle 1.444^\circ \text{ V rms}.$$

so the apparent power is

$$(384.5)(37.70) = \underline{14.50 \text{ kVA}}.$$

- (b) The average power lost in the line is simply

$$(37.70^2)(1.5) = \underline{2.132 \text{ kW}}$$

The line impedance is purely resistive, so the apparent power is equal to the average power: 2.132 kVA

- (c) The source supplies a complex power

$$\begin{aligned} (440 \angle 0^\circ)(37.70 \angle +9.866^\circ) &= 16.59 \angle 9.866^\circ \text{ kVA} \\ &= 16.34 + j2.842 \text{ kVA} \end{aligned}$$


Thus, it supplies an average power of 16.34 kVA and an apparent power of 16.59 kVA

- (d) The power factor of the source is


$$\cos(9.866^\circ) = \underline{0.9852 \text{ lagging}}$$

จากวงจรตามรูป ให้หา

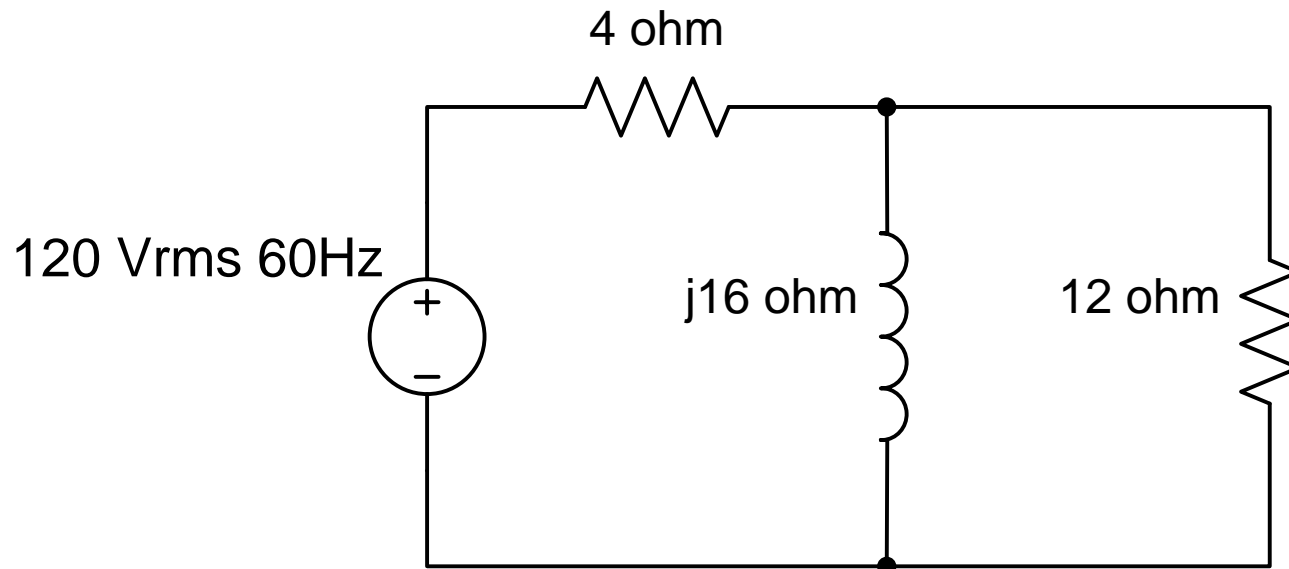- 1) the average power ที่จ่ายโดย แหล่งจ่าย (source)
- 2) ค่า power factor ที่แหล่งจ่าย (source)
- 3) ขนาดของ ตัวเก็บประจุ (capacitor) ที่เมื่อนำไปต่อขนานกับ แหล่งจ่าย ทำให้ค่า power factor = 1




# Example: Final 2/47

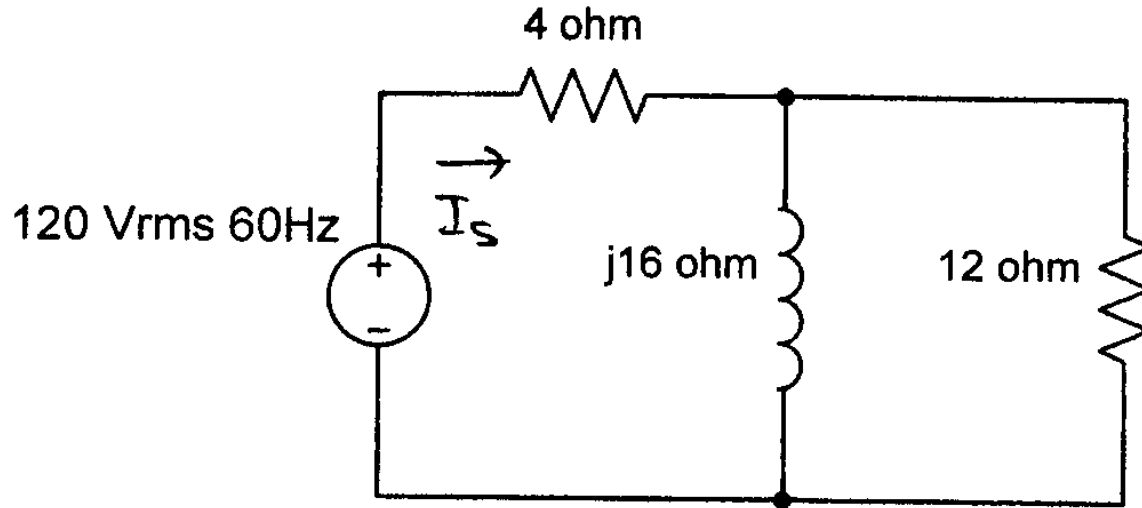

A hand-drawn equivalent circuit diagram showing a 120Vrms 60Hz AC source in series with a box labeled  $Z$ .

$$\begin{aligned} Z &= 4 + (j16 \parallel 12) = 4 + \frac{j192}{12 + j16} \\ &= 11.68 + j5.76 = 13.02 \angle 26.25^\circ \end{aligned}$$

# Example: Final 2/47

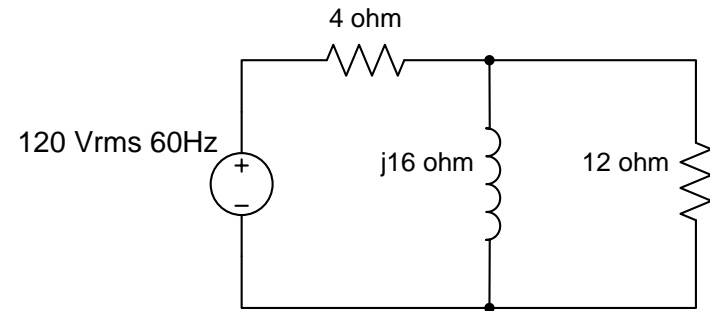

$$[3.2] \quad I_s = \frac{120}{13.02 \angle 26.25^\circ} = 9.214 \angle -26.25^\circ = 8.26 - j4.08$$

$$\therefore PF = \cos 26.25^\circ = 0.8969 \text{ lag } \underline{\underline{Ans}}$$

$$[3.1] \quad P_s = (120) (9.214) (0.8969) \\ = 991.7 \text{ Watts. } \underline{\underline{Ans}}$$


[3.3]

$$Z_L = 11.68 + j5.76$$

$$\frac{1}{Z_L} = Y_L = 0.068 - j0.034$$

$$\therefore j120\pi C = j0.034$$
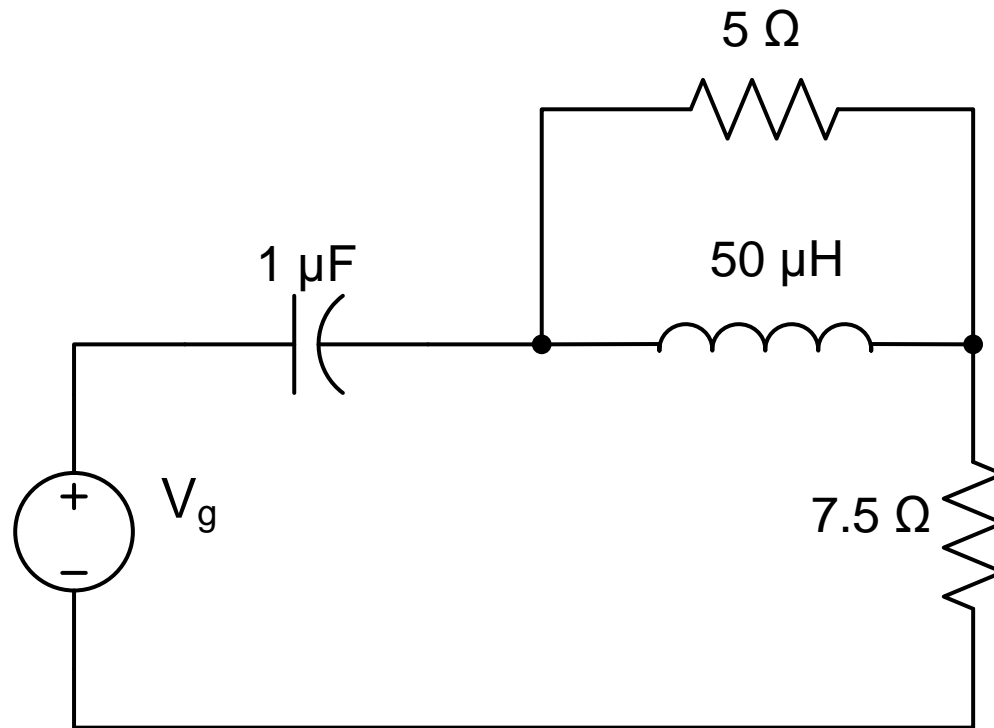
$$C = 90.1 \mu\text{F.} \quad \underline{\text{Ans}}$$





Find the average power, the reactive power, and the apparent power supplied by the voltage source in the circuit if  $v_g = 50 \cos 10^5 t$  V.


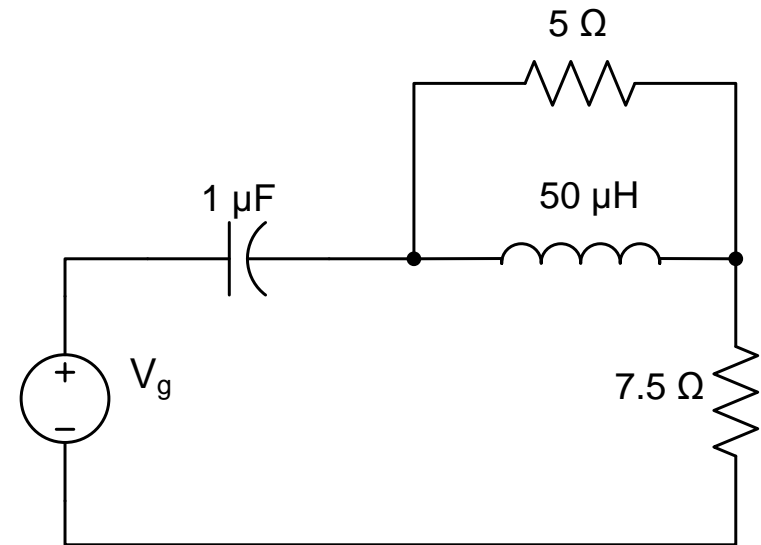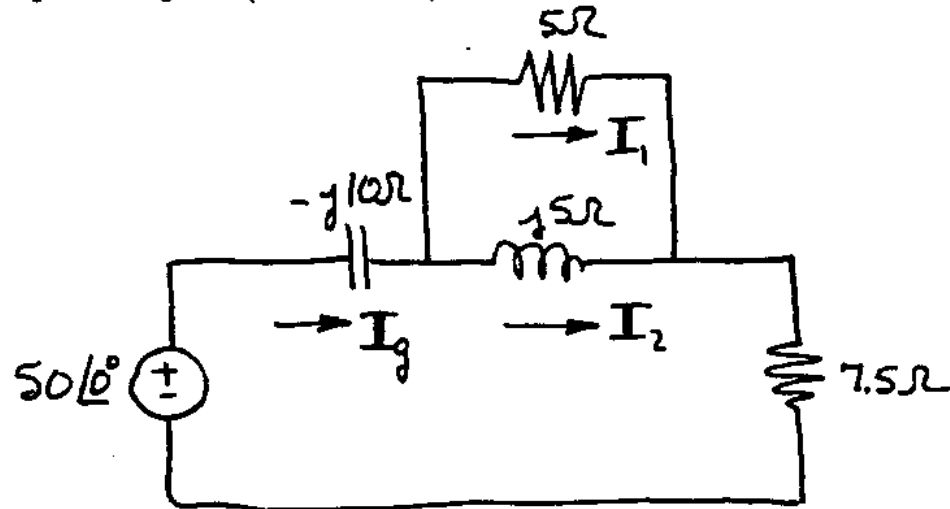
# Ex:

$$\frac{1}{j\omega C} = \frac{10^6}{j10^5} = -j10\Omega$$

$$j\omega L = j10^5(50 \times 10^{-6}) = j5\Omega$$



$$Z = -j10 + \frac{(5)(j5)}{5 + j5} + 7.5 = 10 - j7.5\Omega \quad I_g = \frac{50\angle 0^\circ}{10 - j7.5} = 3.2 + j2.4 A$$

$$S_g = \frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = 25(3.2 - j2.4) = 80 - j60 \text{ VA}$$

$$P = 80 \text{ W (del)}; \quad Q = 60 \text{ VAR (abs)}$$

$$|S| = |S_g| = 100 \text{ VA}$$

# Summary:

Term	Symbol	Unit	Description
Instantaneous power	$p(t)$	W	$p(t) = v(t)i(t)$ . It is the value of the power at a specific instant in time. It is <i>not</i> the product of the voltage and current phasors!
Average power	$P$	W	In the sinusoidal steady state, $P = \frac{1}{2} V_m I_m \cos(\theta - \phi)$ , where $\theta$ is the angle of the voltage and $\phi$ is the angle of the current. Reactances do not contribute to $P$
Effective or rms value	$V_{\text{rms}}$ or $I_{\text{rms}}$	V or A	Defined, e.g., as $I_{\text{eff}} = \sqrt{\frac{1}{T} \int_0^T i^2 dt}$ ; if $i(t)$ is sinusoidal, then $I_{\text{eff}} = I_m / \sqrt{2}$
Apparent power	$ \mathbf{S} $	VA	$ \mathbf{S}  = V_{\text{eff}} I_{\text{eff}}$ , and is the maximum value the average power can be; $P =  \mathbf{S} $ only for purely resistive loads
Power factor	PF	None	Ratio of the average power to the apparent power. The PF is unity for a purely resistive load, and zero for a purely reactive load
Reactive power	$Q$	VAR	A means of measuring the energy flow rate to and from reactive loads
Complex power	$\mathbf{S}$	VA	A convenient complex quantity that contains both the average power $P$ and the reactive power $Q$ : $\mathbf{S} = P + jQ$



**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**