
ENE 104

Electric Circuit Theory



Lecture 04:
Useful Circuit Analysis Techniques

Week #4 : Dejwoot KHAWPARISUTH
office: CB40906 Tel: 02-470-9065
Email: dejwoot.kha@mail.kmutt.ac.th

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

Objectives :

- Superposition
- Source transformation
- the Thevenin equivalent of any network
- the Norton equivalent of any network
- the load resistance that will result in maximum power transfer
- a Δ -connected network, a Y-connected network
- a dc sweep in PSpice


Ch5-Useful Techniques:

Learning methods of simplifying the analysis of more complicated circuits.

The principle of superposition:


The response in a linear circuit having more than one independent source can be obtained by adding the responses caused by the separate independent sources acting alone.

The Superposition Principle:

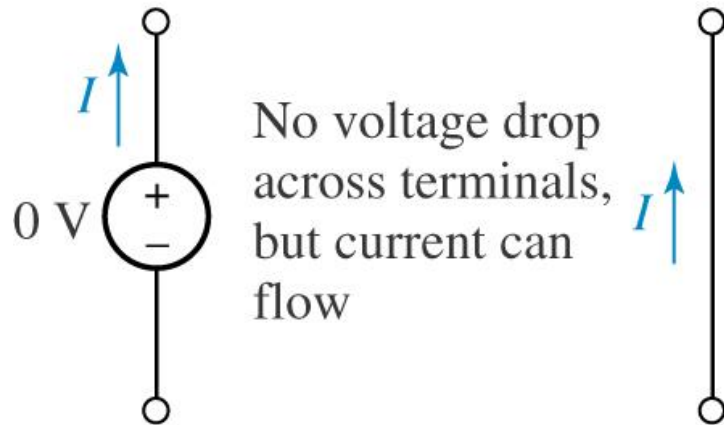

(a)

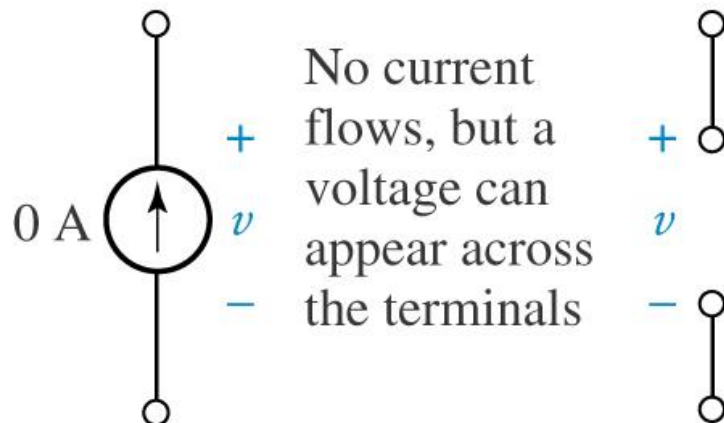(a) A voltage source set to zero acts like a short circuit.




(b)

(b) A current source set to zero acts like an open circuit.

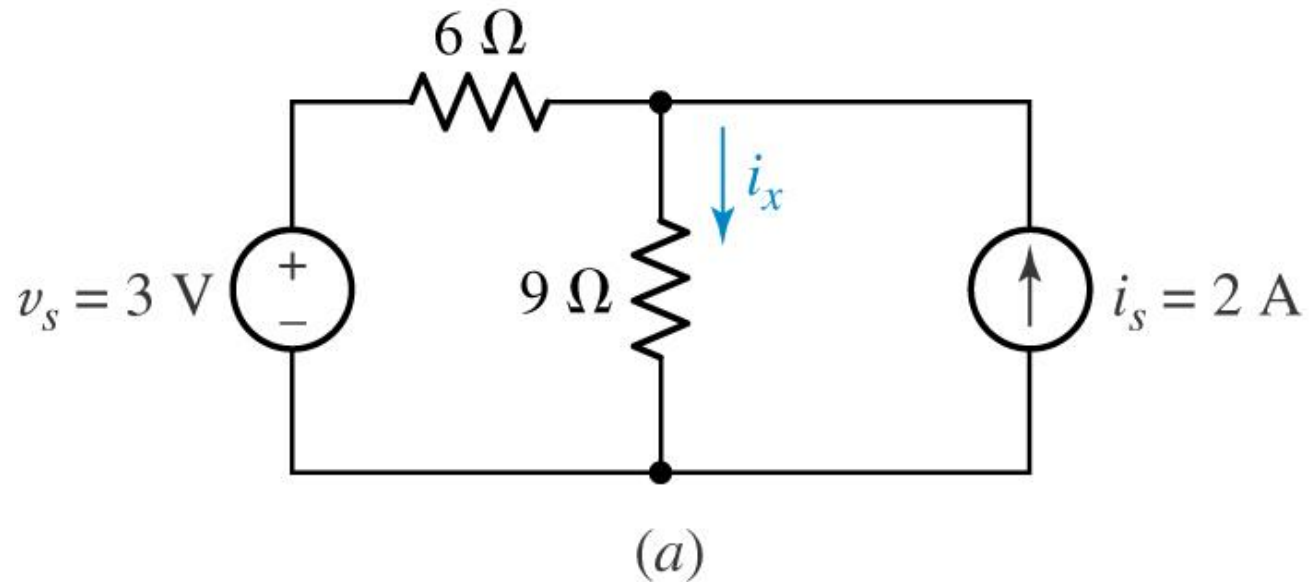
Example 5.1:

Use superposition to find the current i_x .



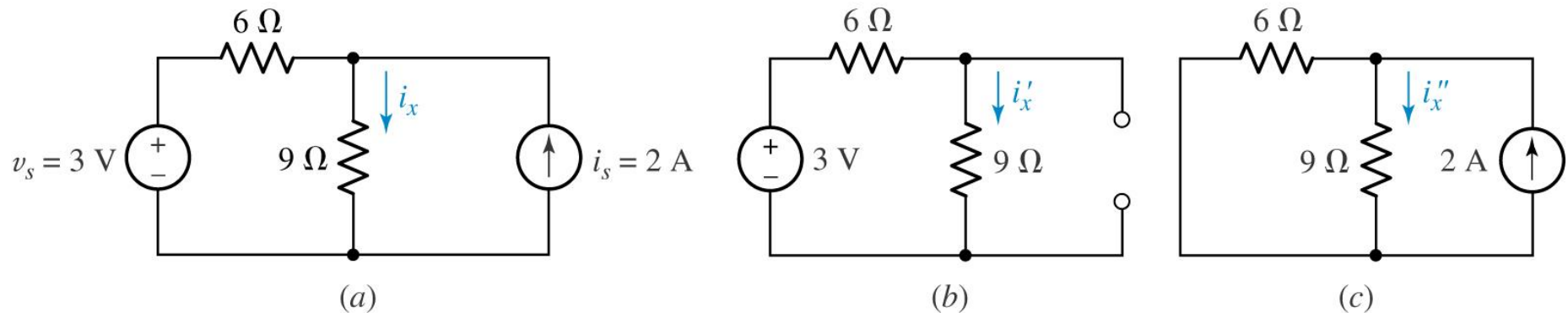
Example:

Use superposition to find the current i_x .



$$i_x = i'_x + i''_x = \frac{3}{6+9} + 2 \left(\frac{6}{6+9} \right) = 0.2 + 0.8 = 1.0 \text{ A.}$$


The Superposition Principle:

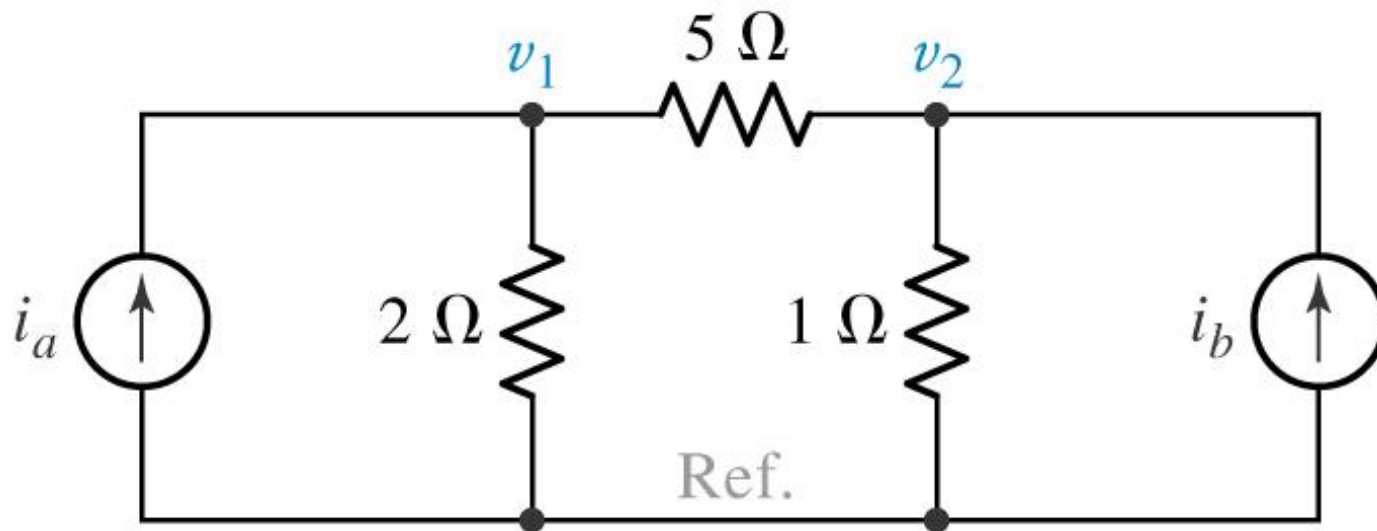

Sources are often called forcing functions.

→ responses

The Superposition Principle:

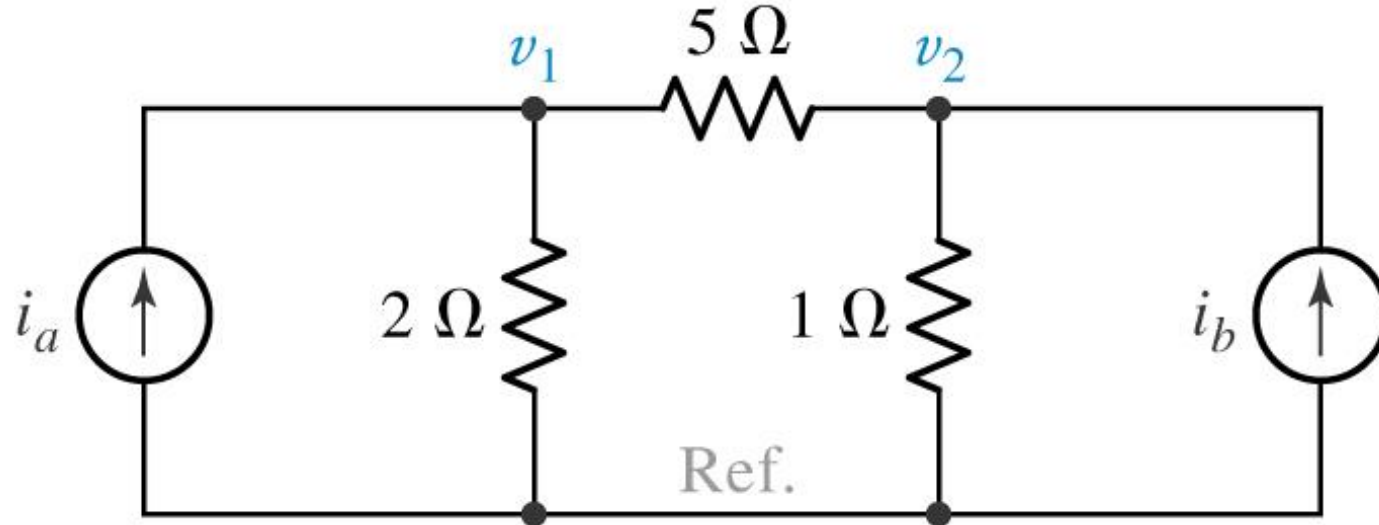

Nodal equations:

$$0.7v_1 - 0.2v_2 = i_a \quad \dots [1]$$

$$-0.2v_1 + 1.2v_2 = i_b \quad \dots [2]$$

The Superposition Principle:


Change the two forcing functions:

$$0.7v_{1x} - 0.2v_{2x} = i_{ax} \quad \dots [3]$$

$$-0.2v_{1x} + 1.2v_{2x} = i_{bx} \quad \dots [4]$$

$$0.7v_{1y} - 0.2v_{2y} = i_{ay} \quad \dots [5]$$
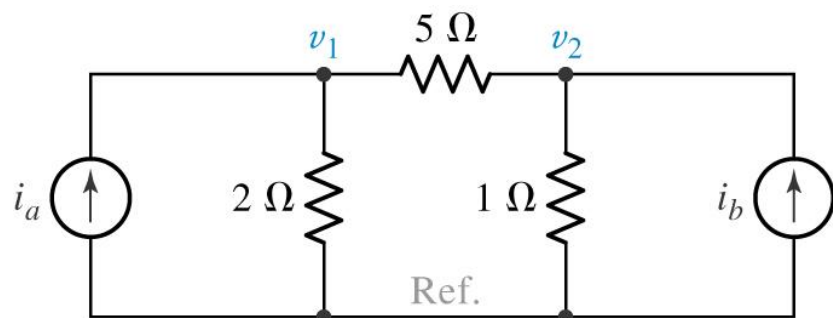
$$-0.2v_{1y} + 1.2v_{2y} = i_{by} \quad \dots [6]$$



$$(0.7v_{1x} + 0.7v_{1y}) - (0.2v_{2x} + 0.2v_{2y}) = (i_{ax} + i_{ay}) \quad \dots [7]$$


$$0.7v_1 - 0.2v_2 = i_a \quad \dots [1]$$

$$-(0.2v_{1x} + 0.2v_{1y}) + (1.2v_{2x} + 1.2v_{2y}) = (i_{bx} + i_{by}) \quad \dots [8]$$


$$-0.2v_1 + 1.2v_2 = i_b \quad \dots [2]$$

Practice: 5.1

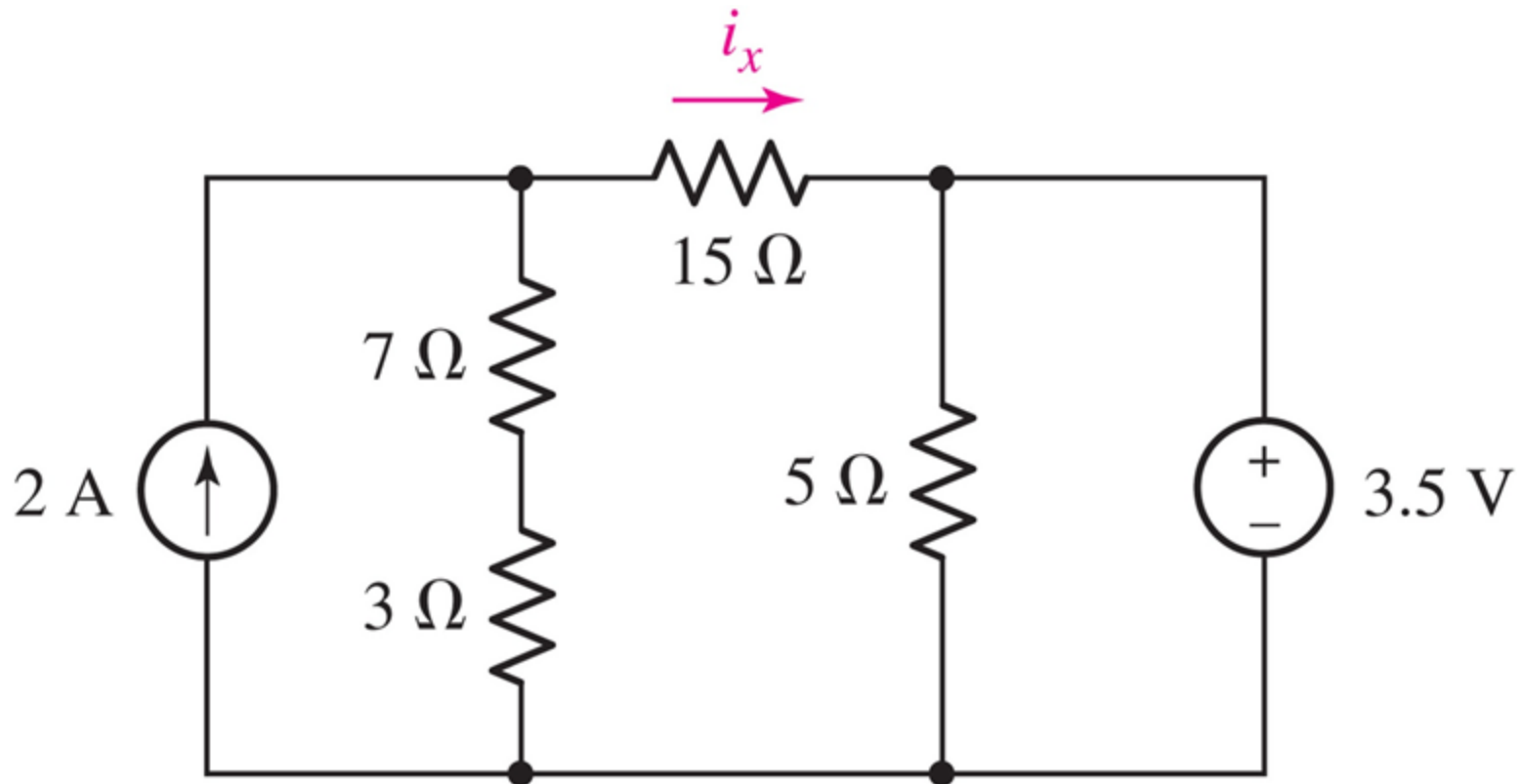Use superposition to find the current i_x .




Practice: 5.1

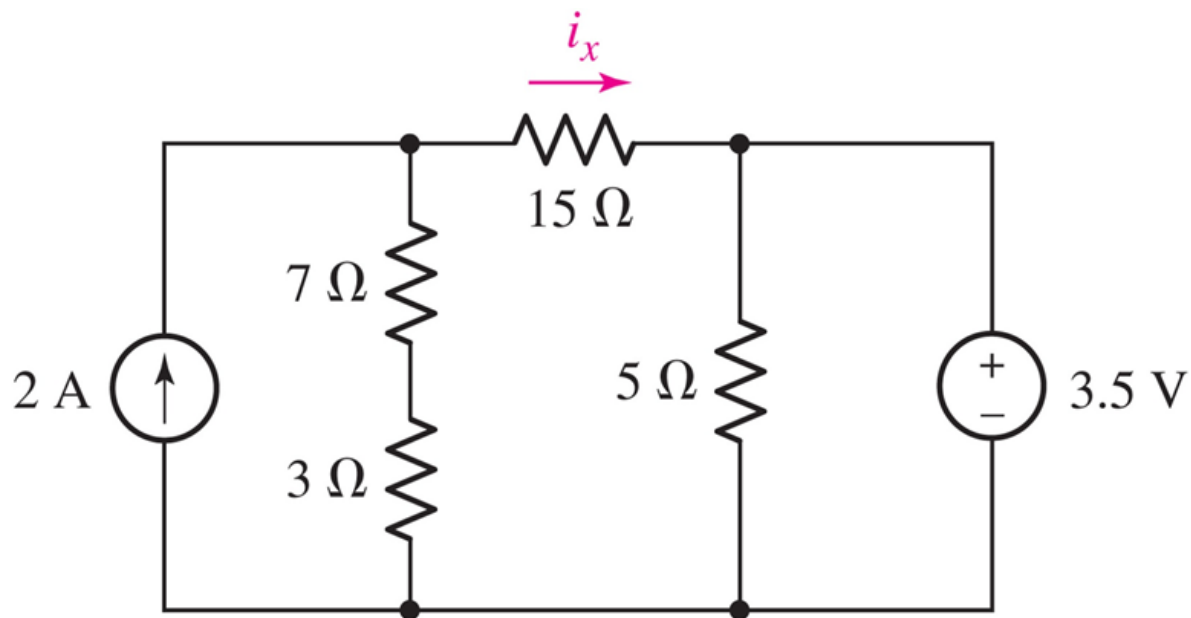

$$i_x = i_x|_{2A} + i_x|_{3.5V} = \frac{10}{(10 + 15)}(2A) + \frac{-3.5V}{25\Omega}$$

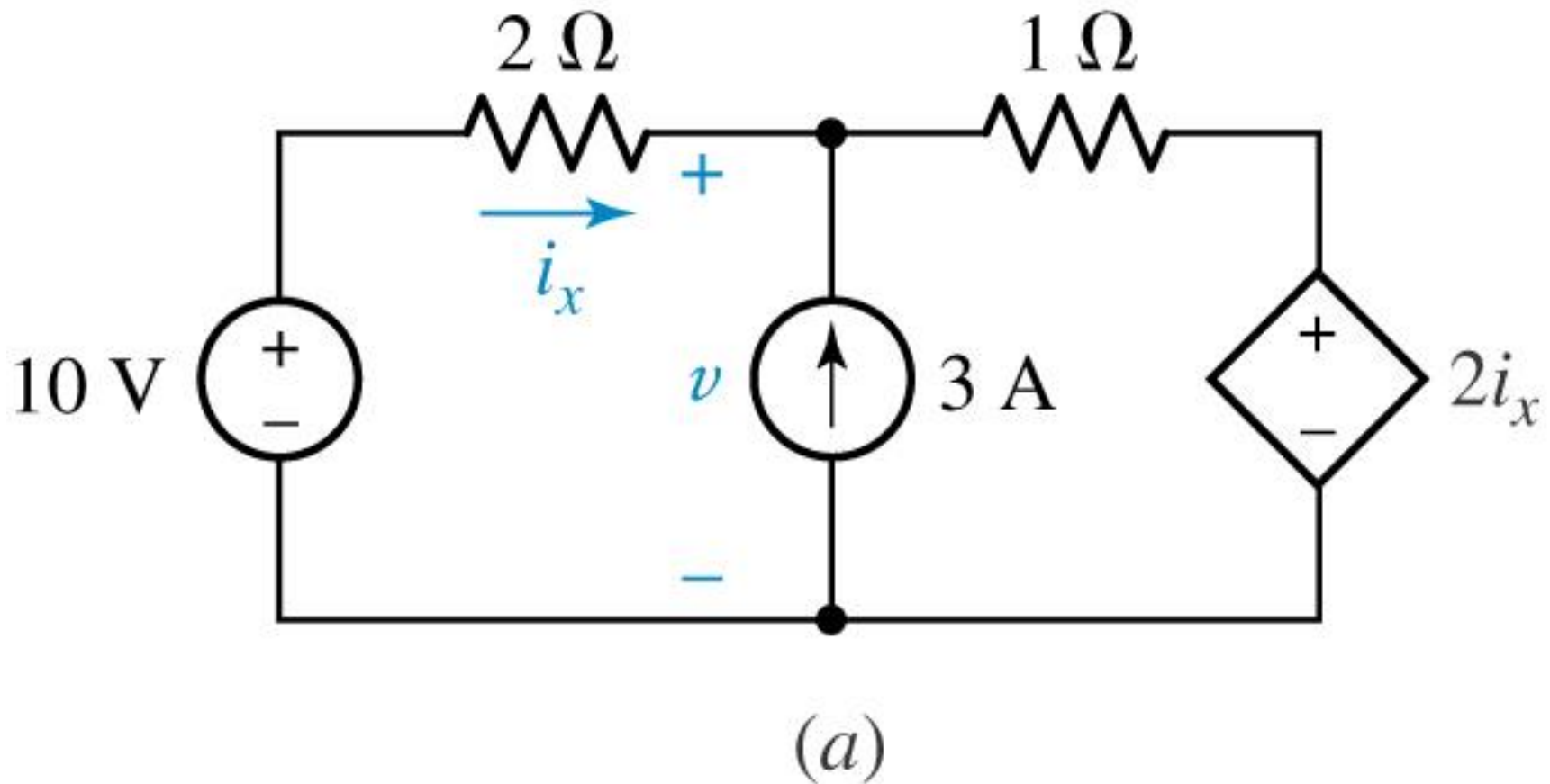
Example 5.3:

Use superposition to find the current i_x .



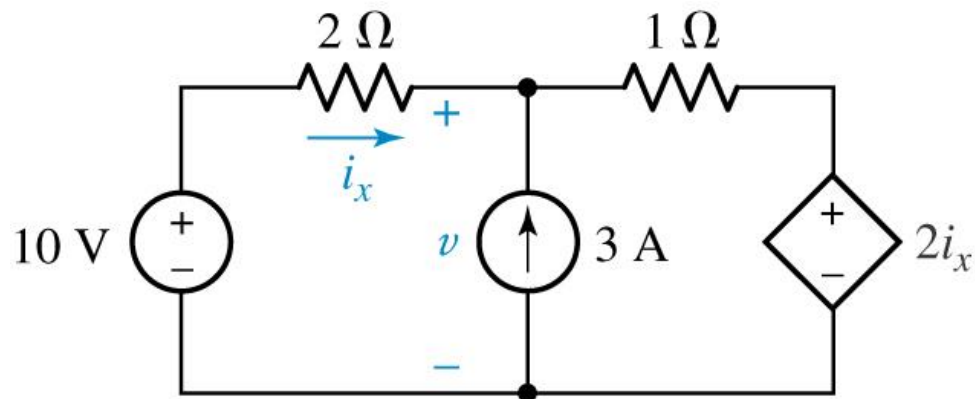
Example:

Use superposition to find the current i_x .




(a)

$$i_x = i'_x + i''_x$$

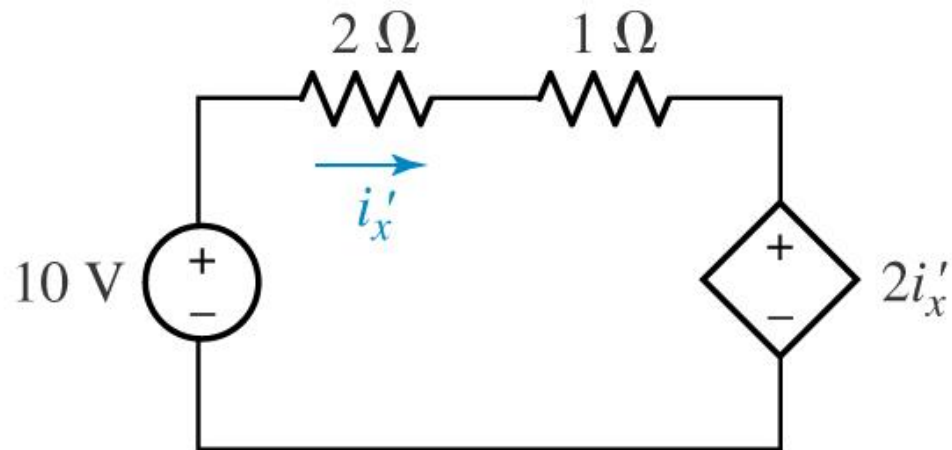


(b)

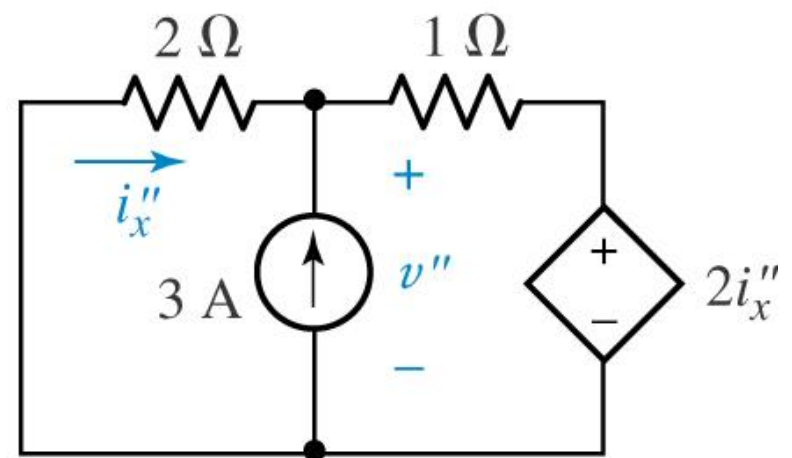

(c)

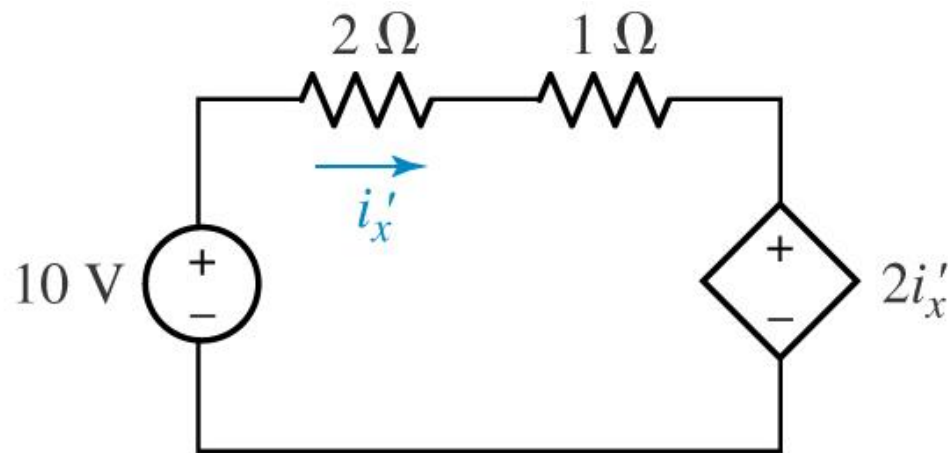Example:


Use superposition to find the current i_x .



(b)

Figure b:
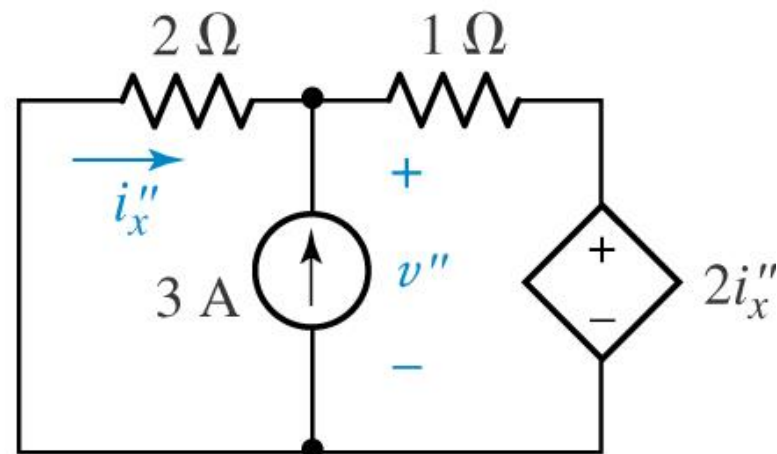
$$\begin{aligned} -10 + 2i'_x + 1i'_x + 2i'_x &= 0 \\ \therefore i'_x &= 2 \text{ A.} \end{aligned}$$



(c)

Figure c:


$$\frac{v''}{2} + \frac{v'' - 2i''_x}{1} = 3 \quad \dots [1]$$

And

$$v'' = -2i''_x \quad \dots [2]$$

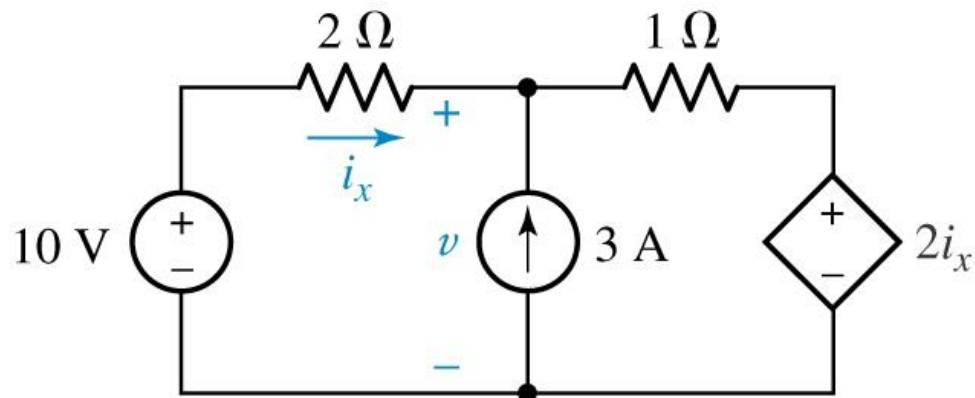
Example:

Use superposition to find the current i_x .




(a)
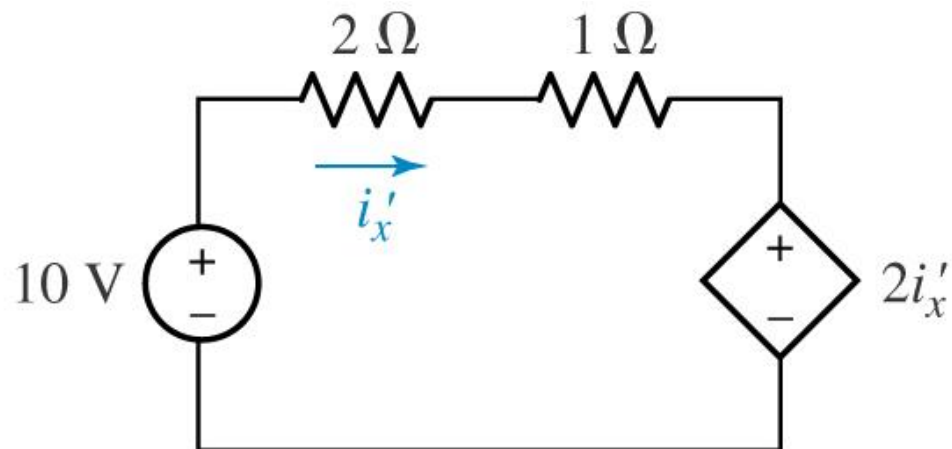
$$\begin{aligned} i_x &= i'_x + i''_x \text{ A.} \\ &= 2 + (-0.6) \text{ A.} \\ &= 1.4 \text{ A.} \end{aligned}$$




(b)

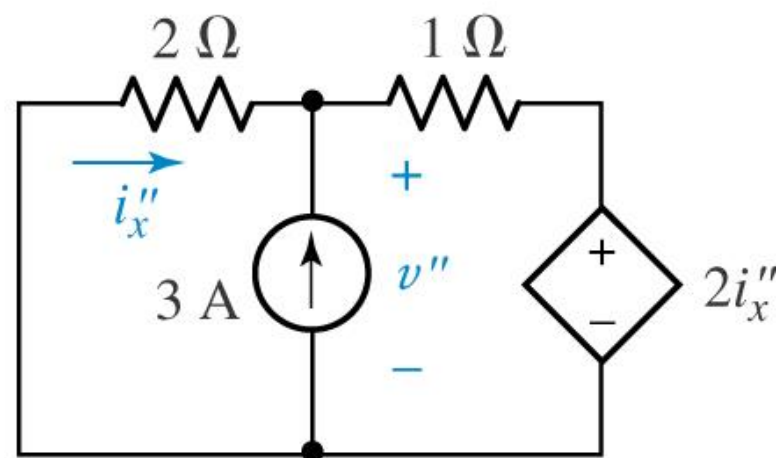


(c)

Practice: 5.2

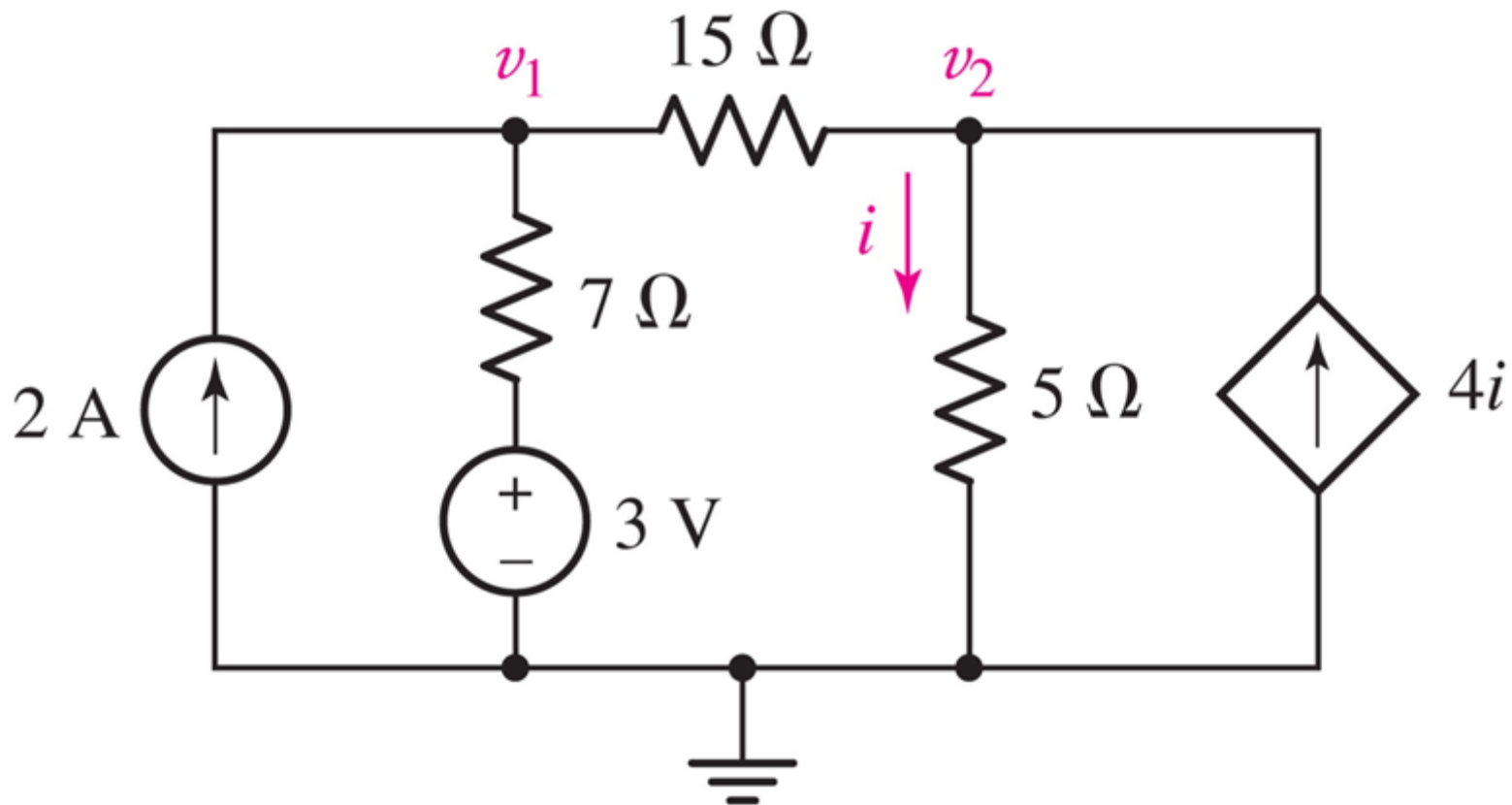Use superposition to obtain the voltage across each current source.





Practice: 5.2

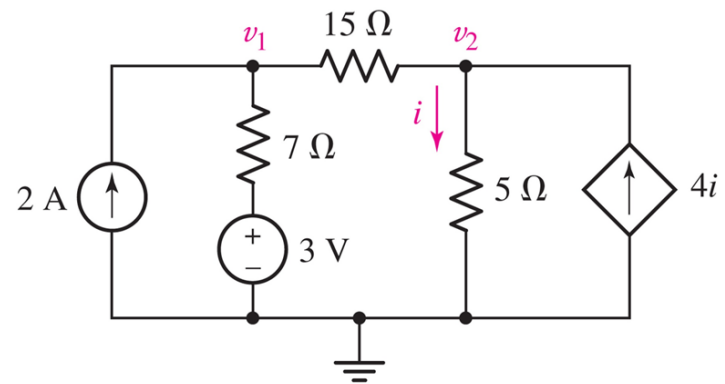


$$v_1|_{2A} = \frac{5}{(22+5)} (4i)(7\Omega) = \frac{5}{(22+5)} \left(4 \frac{v_2}{5\Omega} \right) (7\Omega)$$

$$v_2|_{2A} = \frac{5}{(22+5)} (4i)(5\Omega) = \frac{5}{(22+5)} \left(4 \frac{v_2}{5\Omega} \right) (5\Omega)$$


Pspice: dc sweep

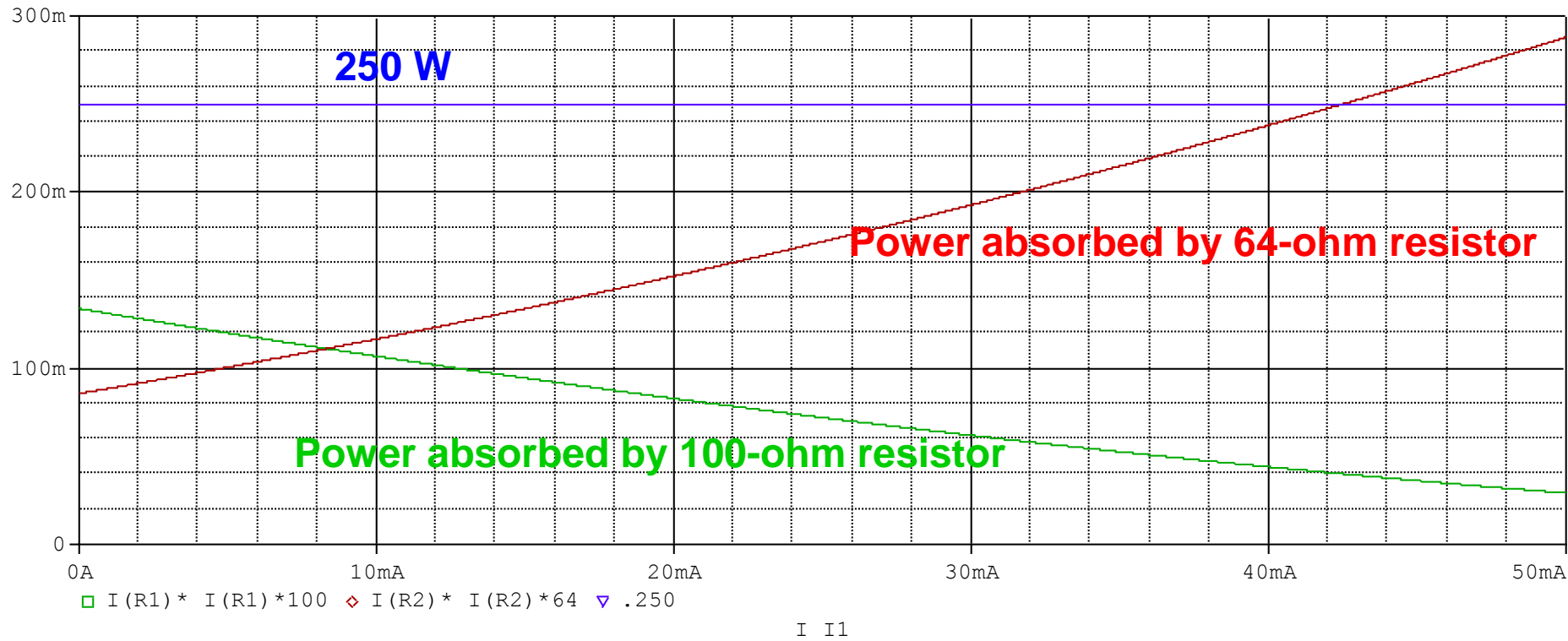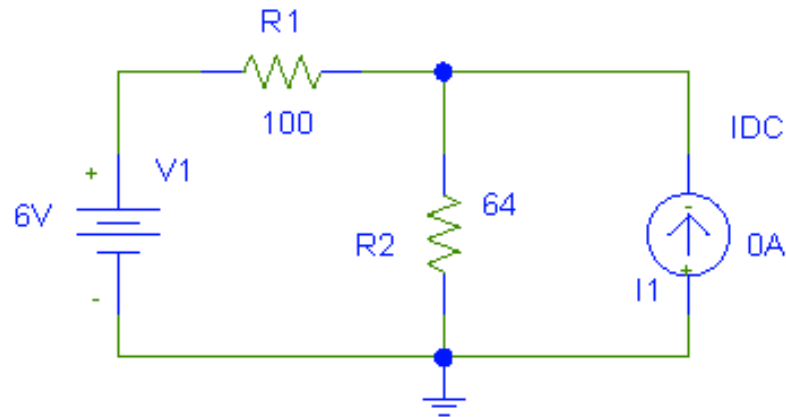

Source Transformation:

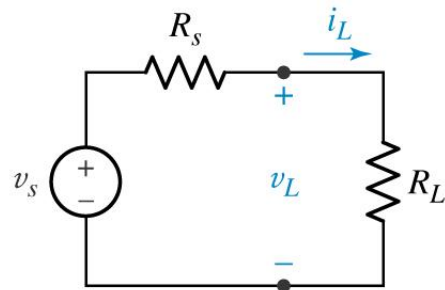


(a)

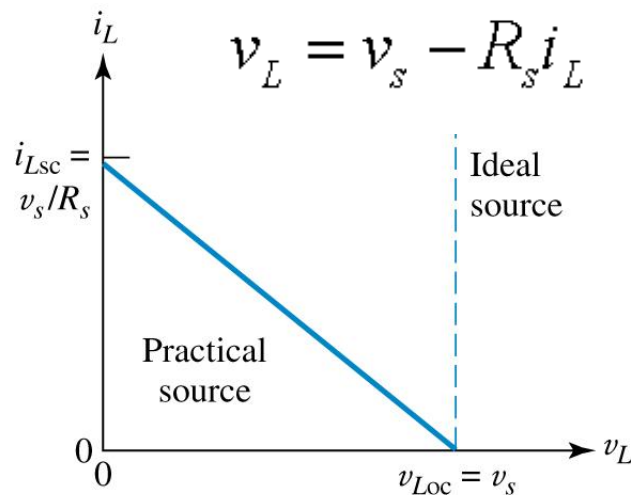


(b)

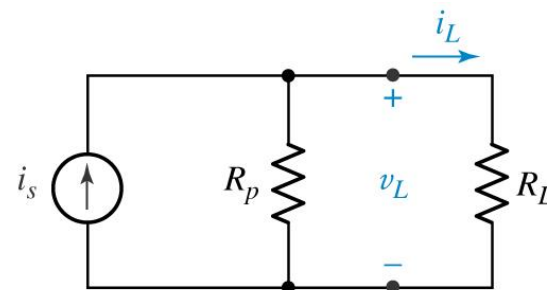(a) A general practical voltage source connected to a load resistor R_L . (b) The terminal characteristics compared to an ideal source.




(a)

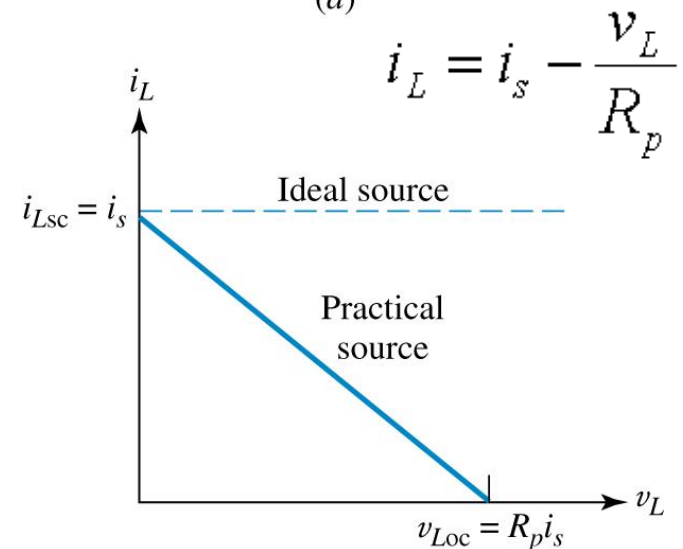

(b)


(a) A general practical current source connected to a load resistor R_L . (b) The terminal characteristics compared to an ideal source.

Equivalent Sources:

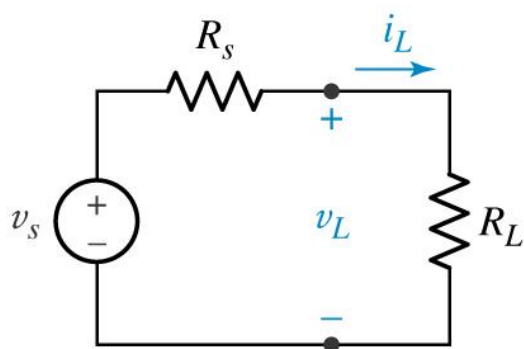

$$v_L = v_s \frac{R_L}{R_s + R_L}$$


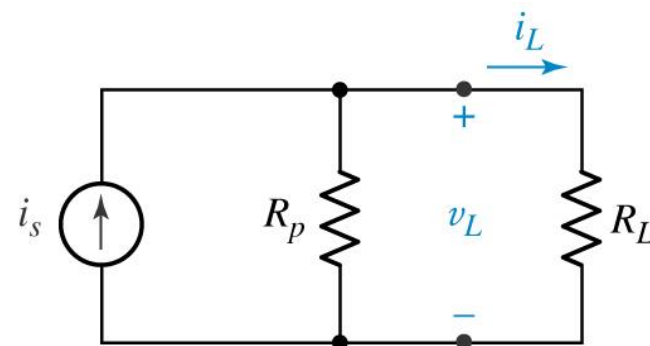
$$= \left(\frac{v_s}{R_s + R_L} \right) \cdot R_L$$



$$v_L = \left(i_s \frac{R_p}{R_p + R_L} \right) \cdot R_L$$

$$= \left(\frac{i_s R_p}{R_p + R_L} \right) \cdot R_L$$

Equivalent Sources:

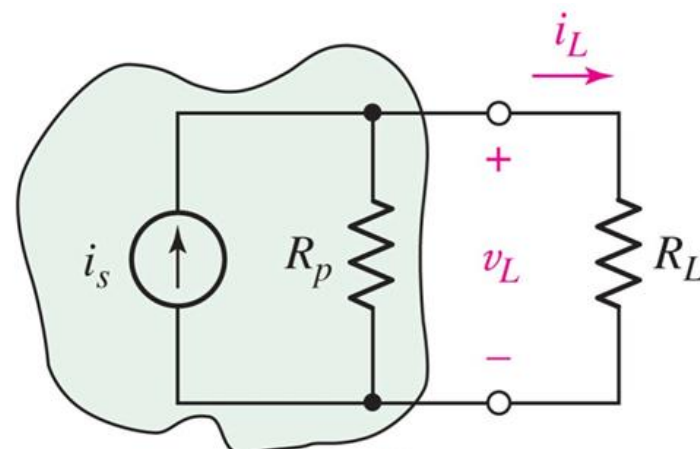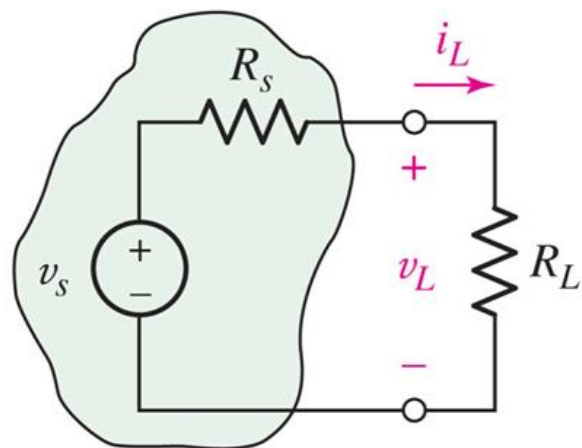


The two practical sources are electrically equivalent,
If

$$R_s = R_p$$


And

$$v_s = R_p i_s = R_s i_s$$

Example 5.4:

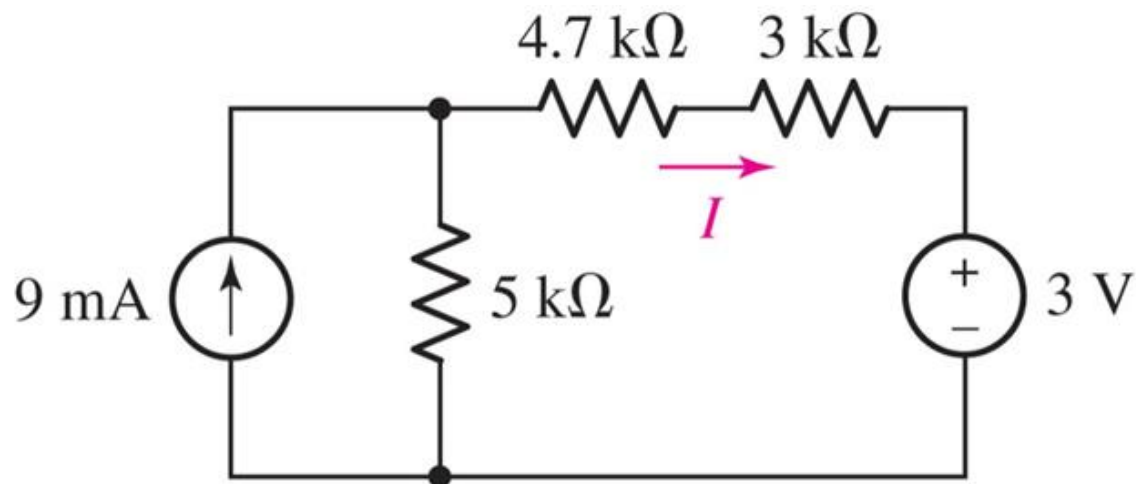


(a)

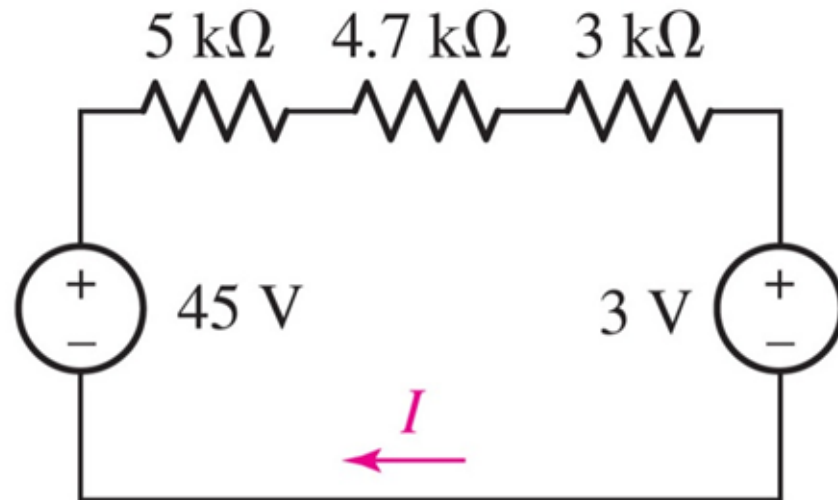


(b)

Practice: 5.3



compute the current i_x after performing a source transformation on the voltage source

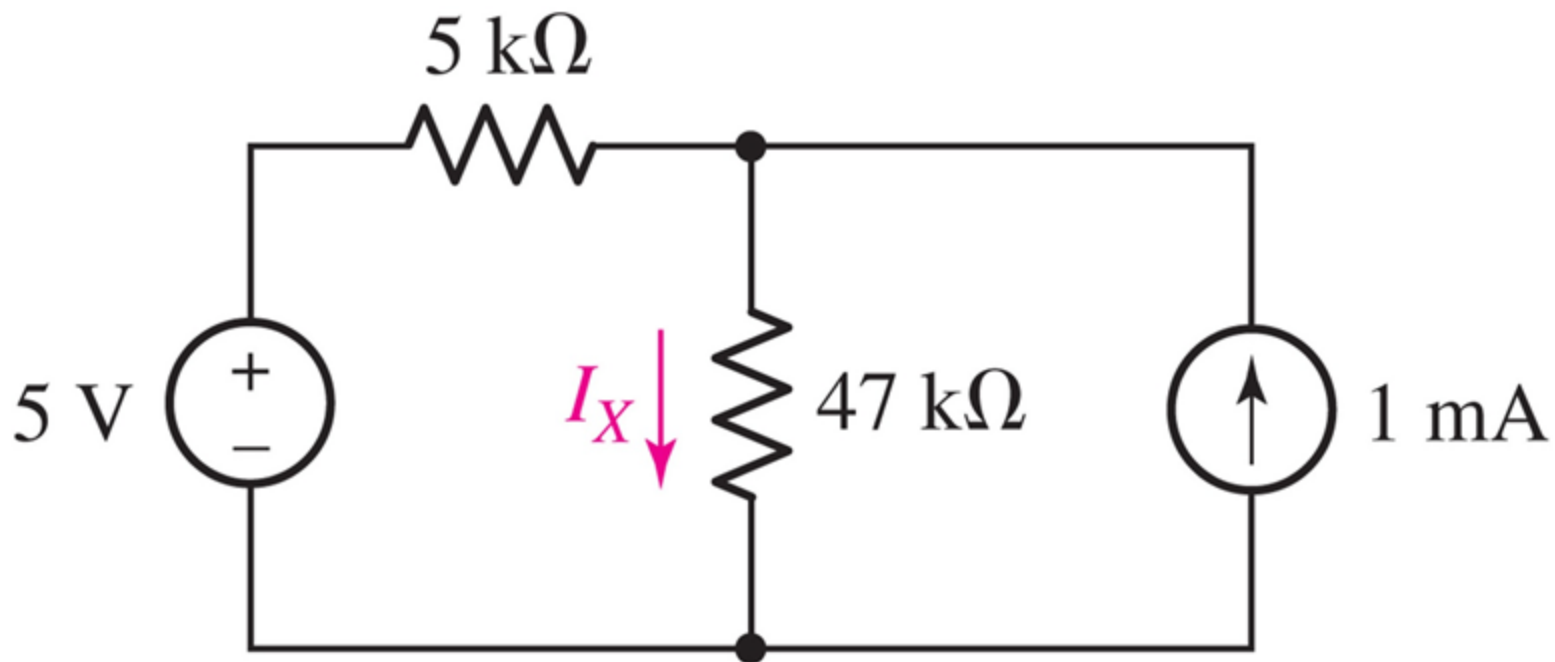



Example 5.5:

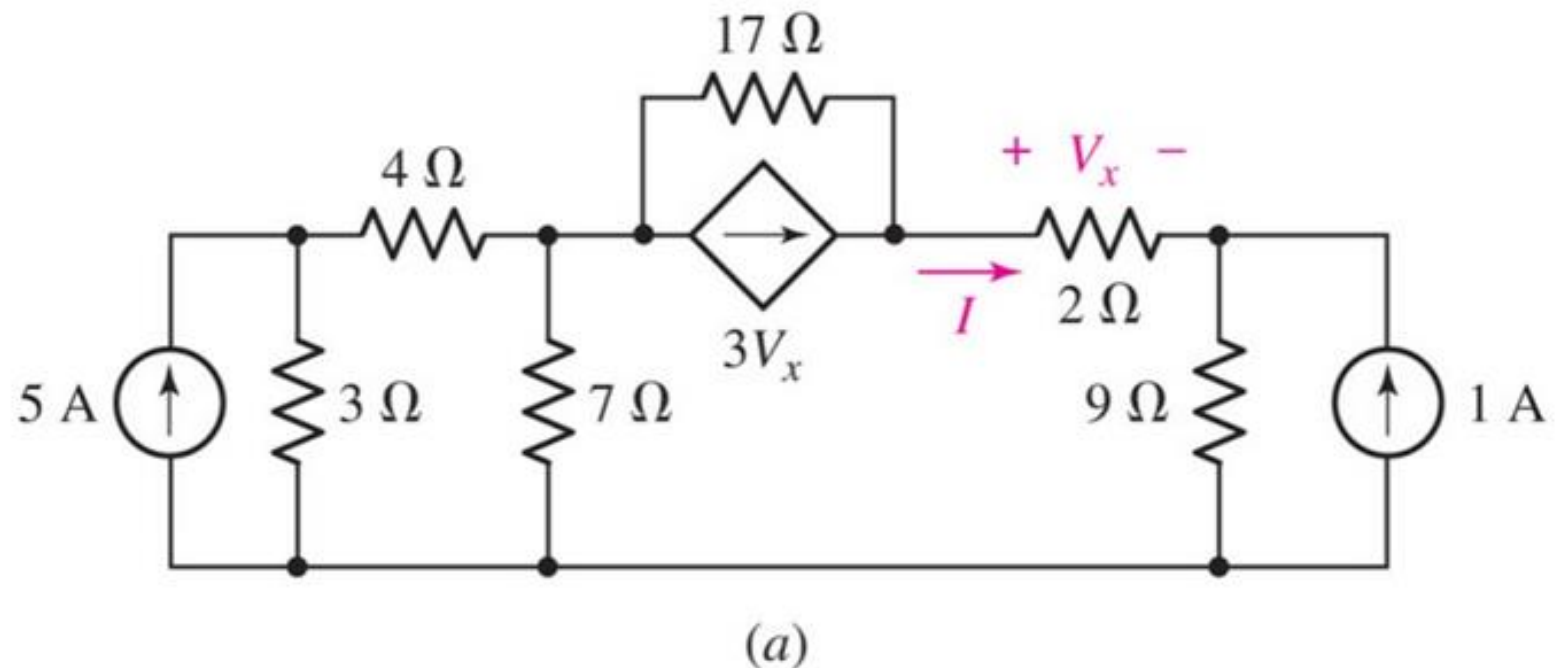



Example:

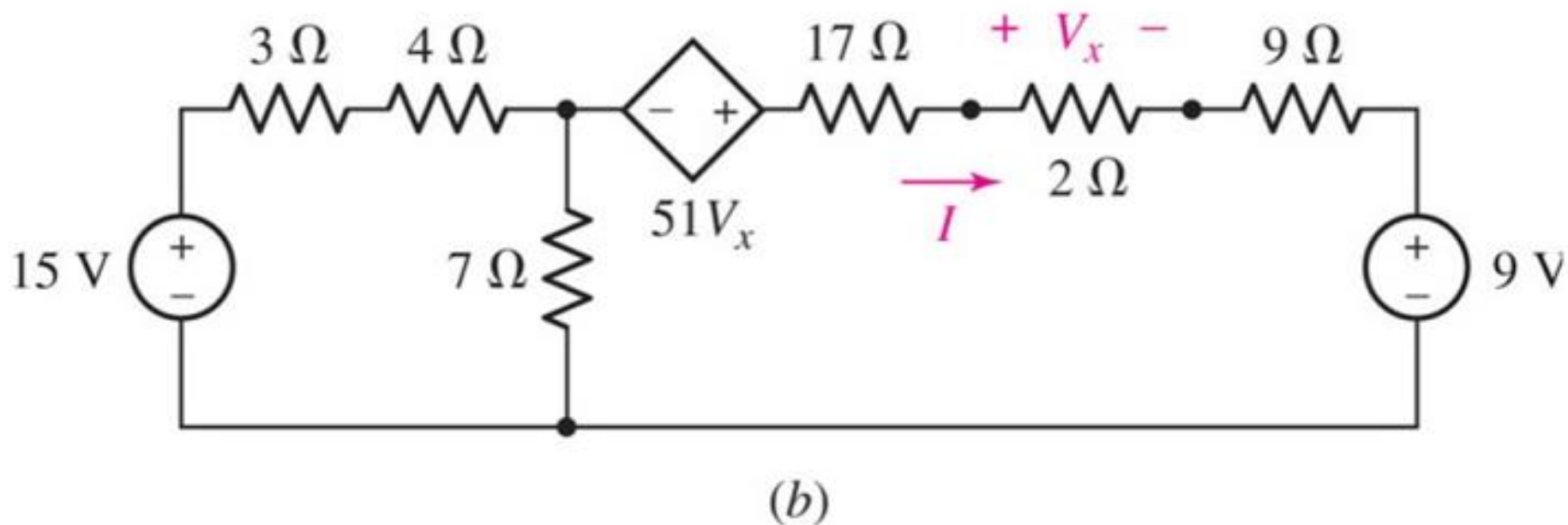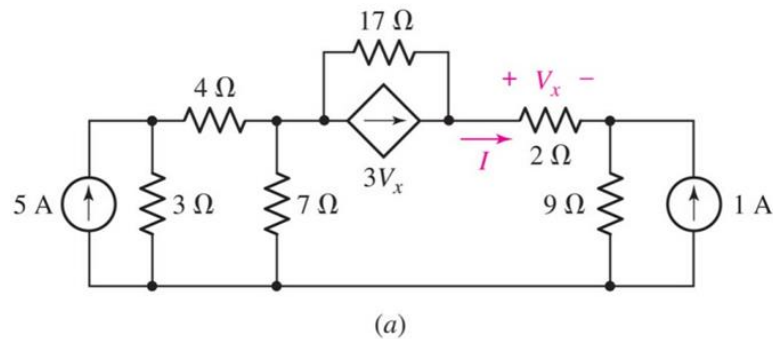


Example:

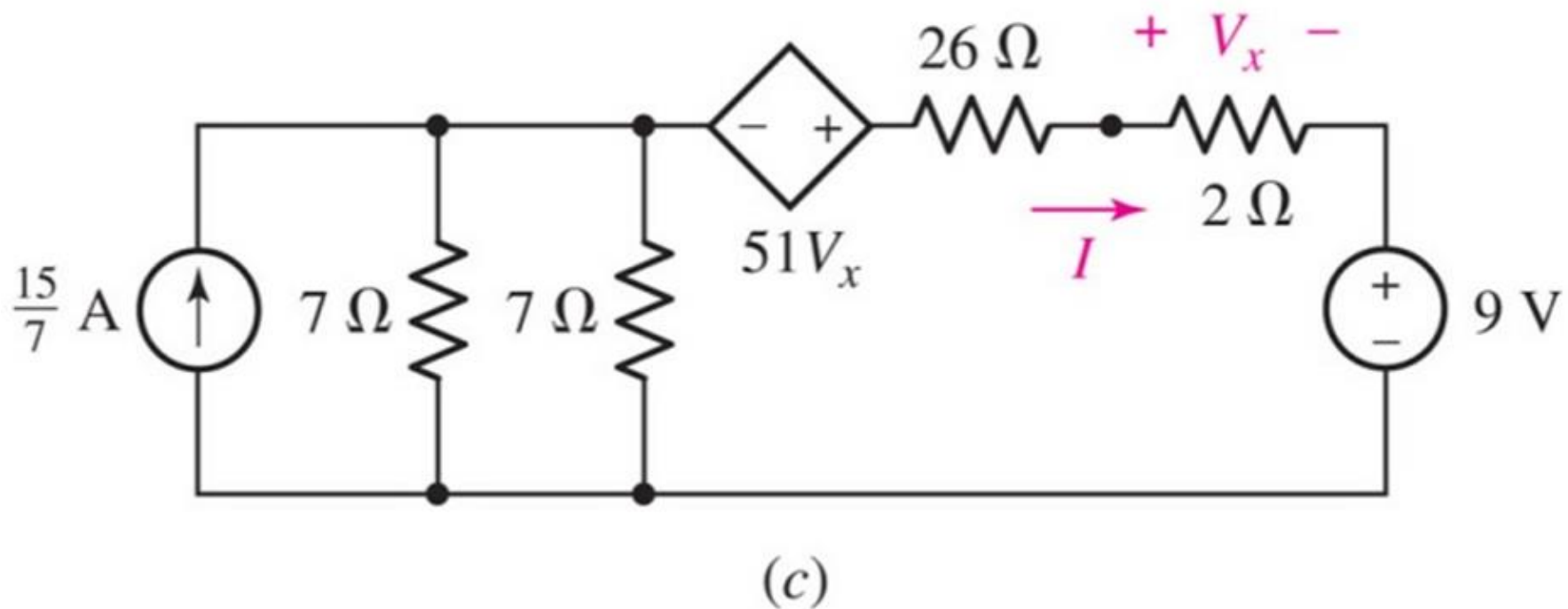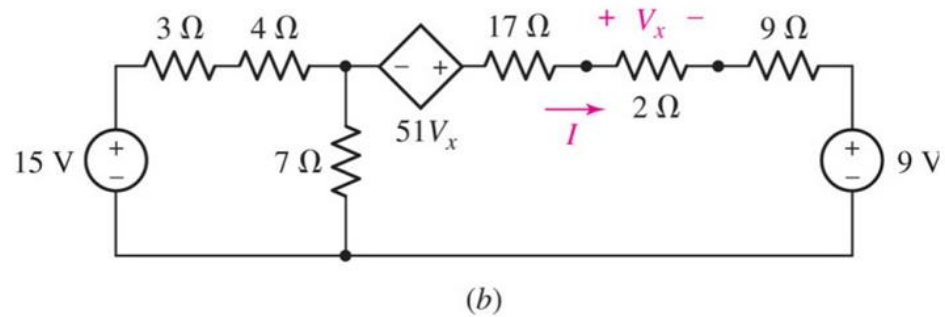


Example:

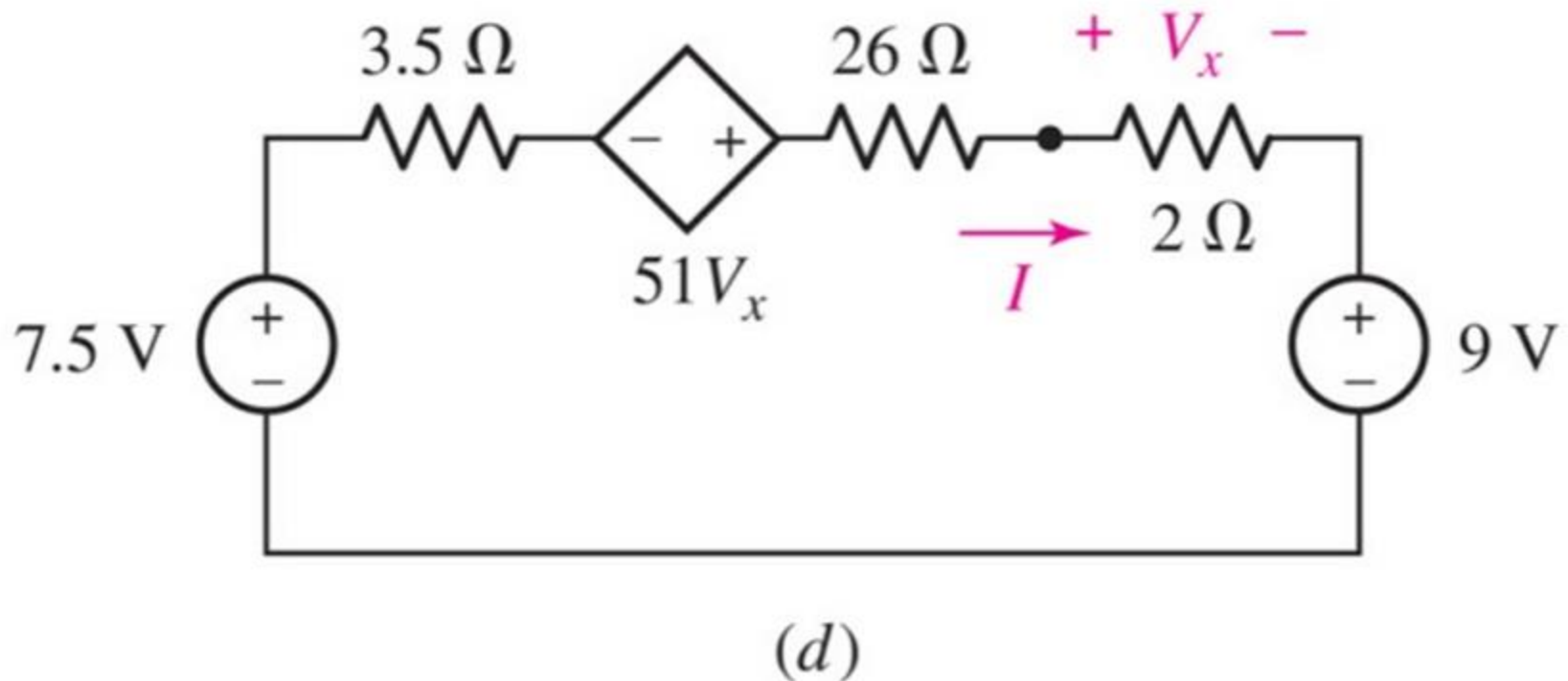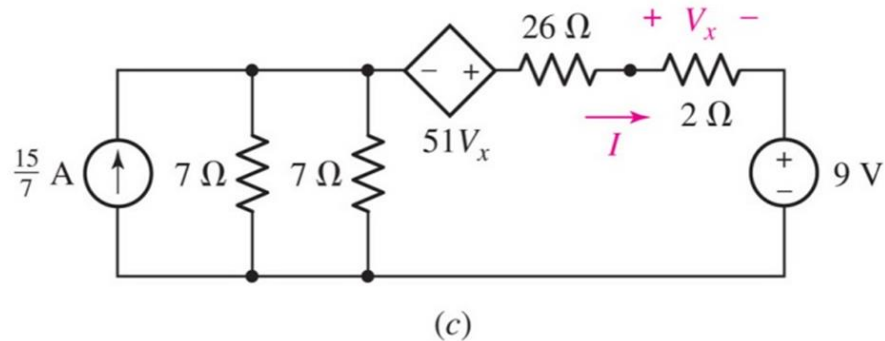

The equivalents:

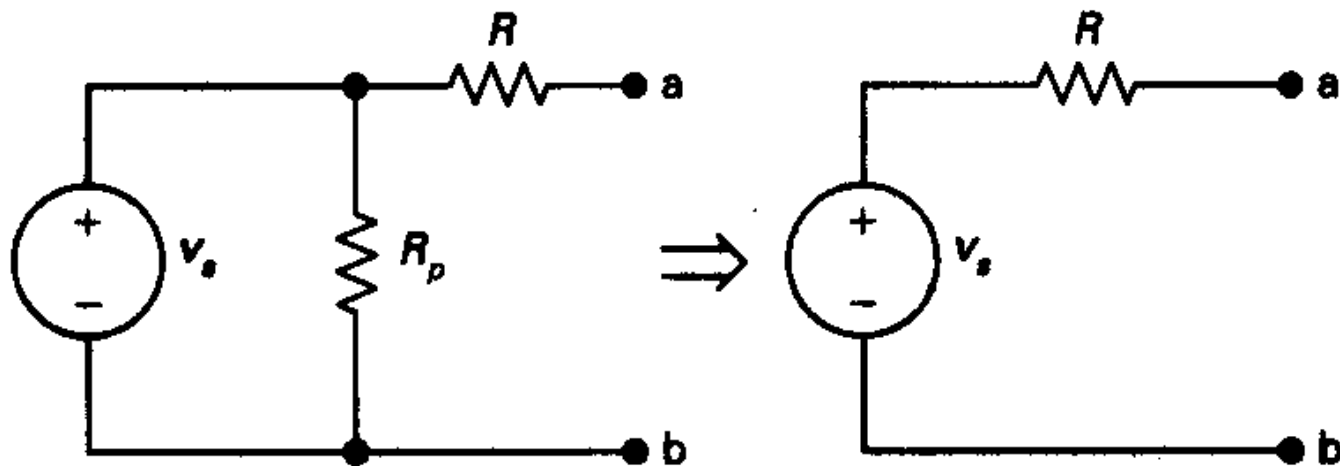


(a)

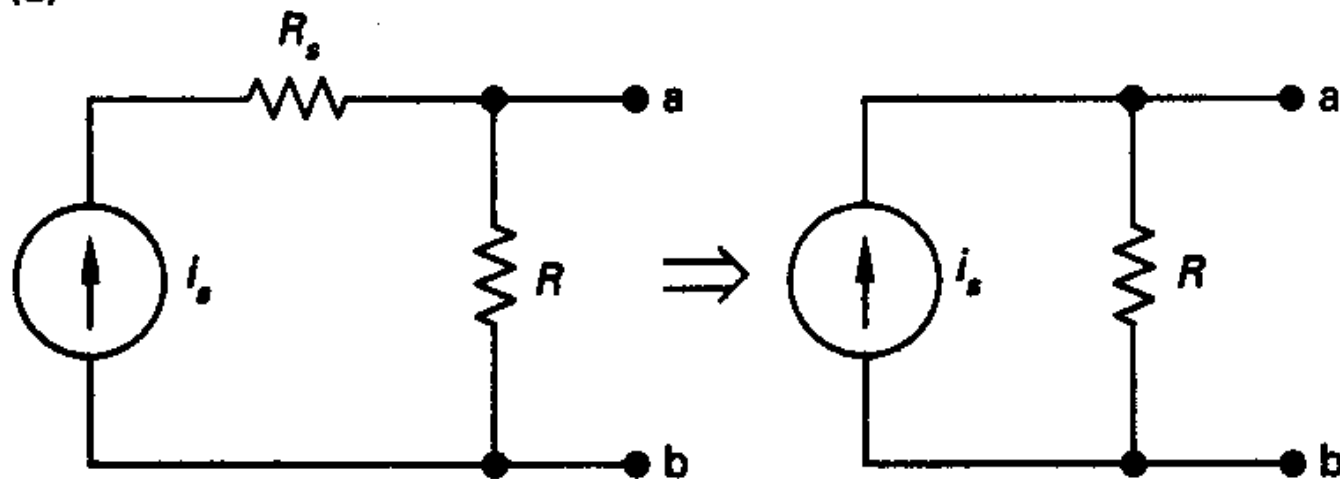

(b)


Practice: 5.4

Compute the voltage V

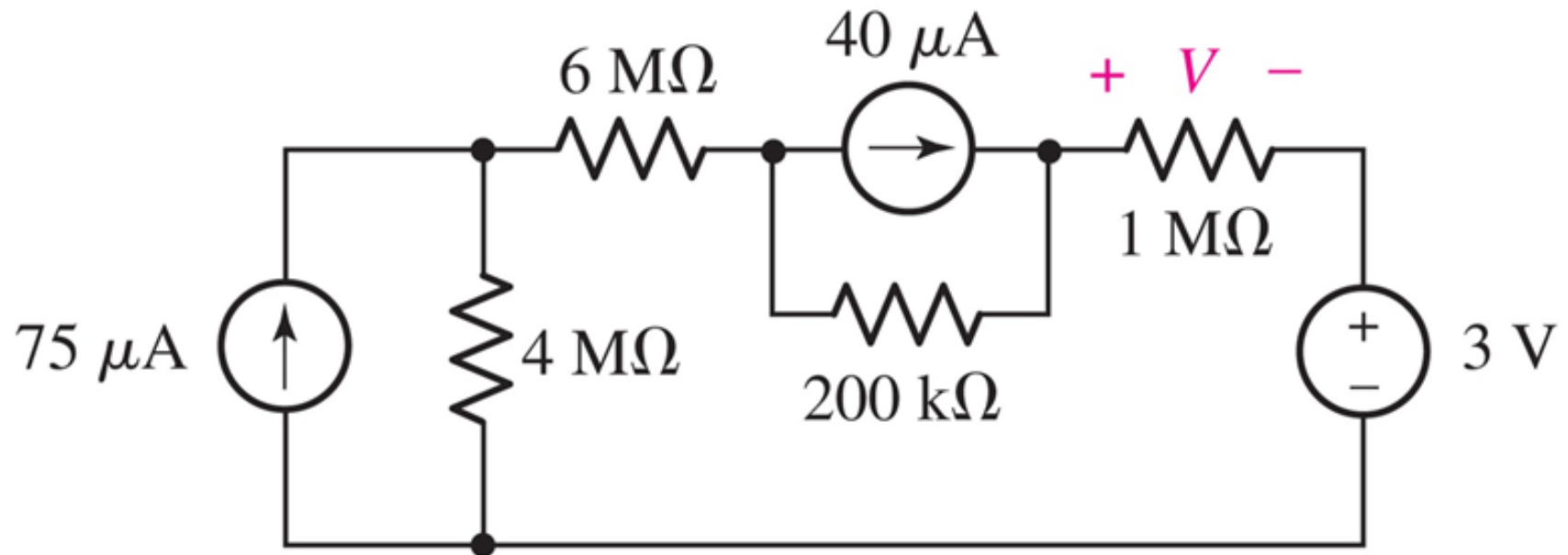



Example:

Find the voltage v_o

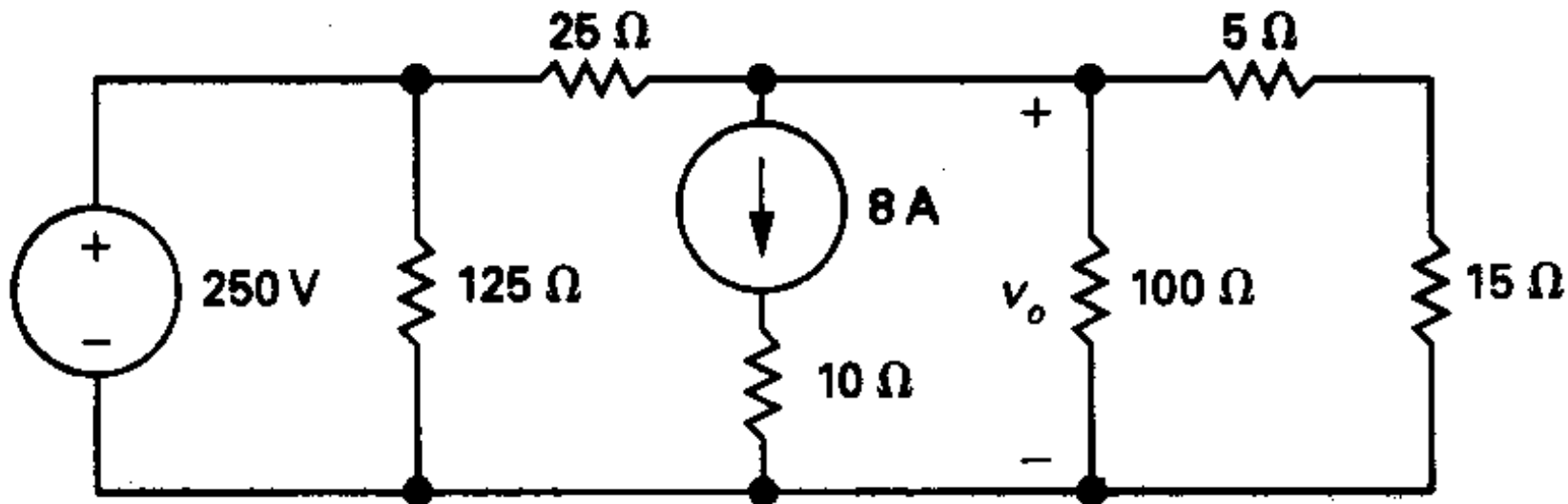



Example:

Find the voltage v_o

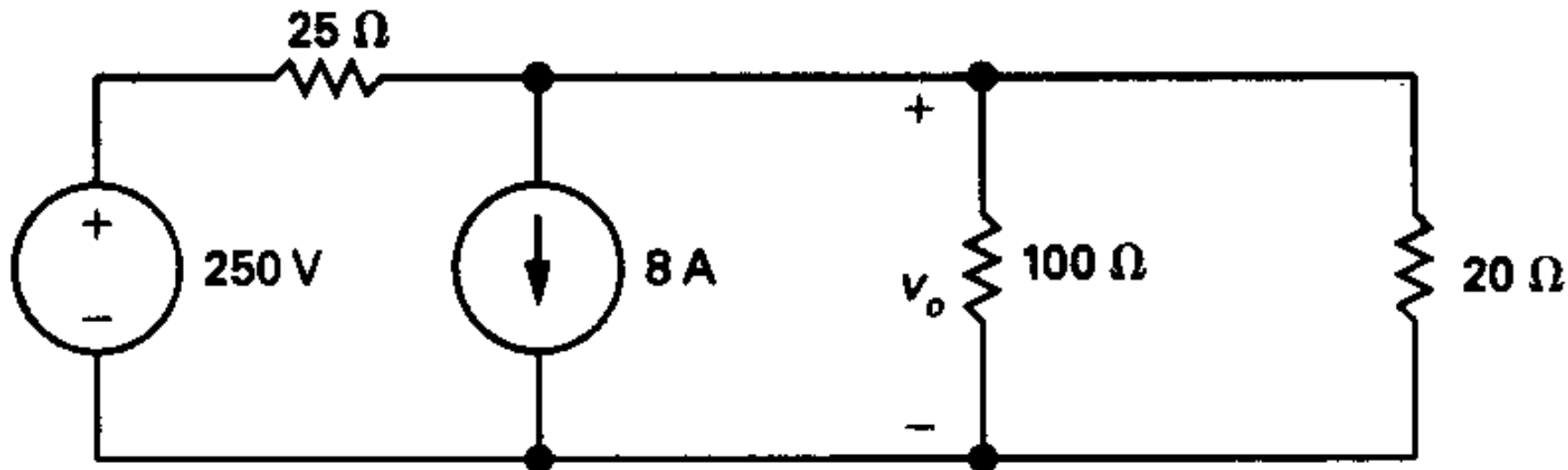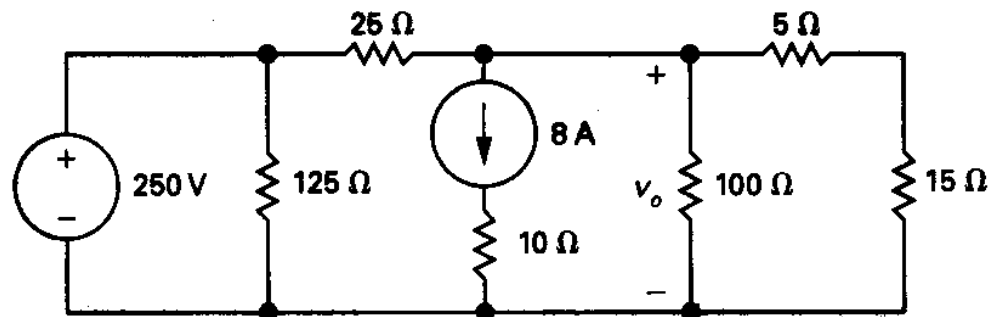


Example:

Find the voltage v_o

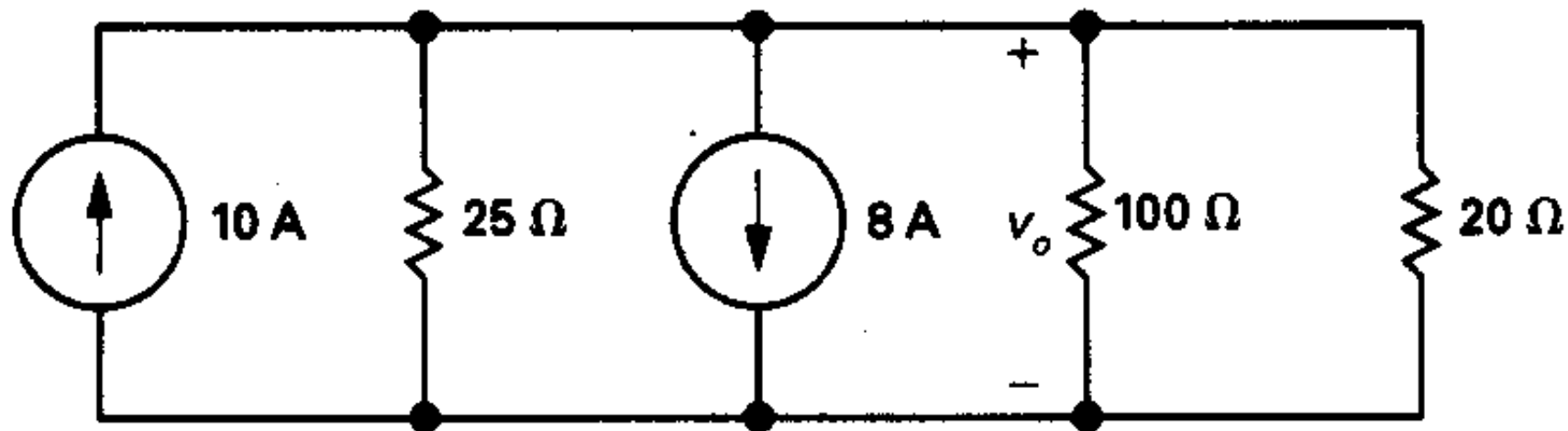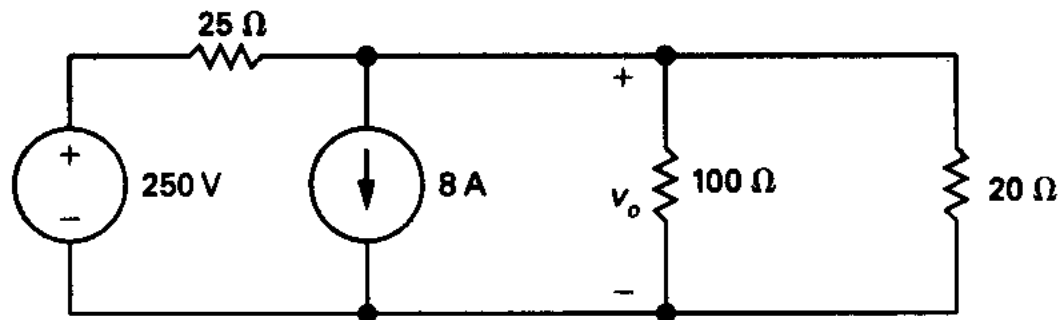

Thevenin and Norton Equi. :

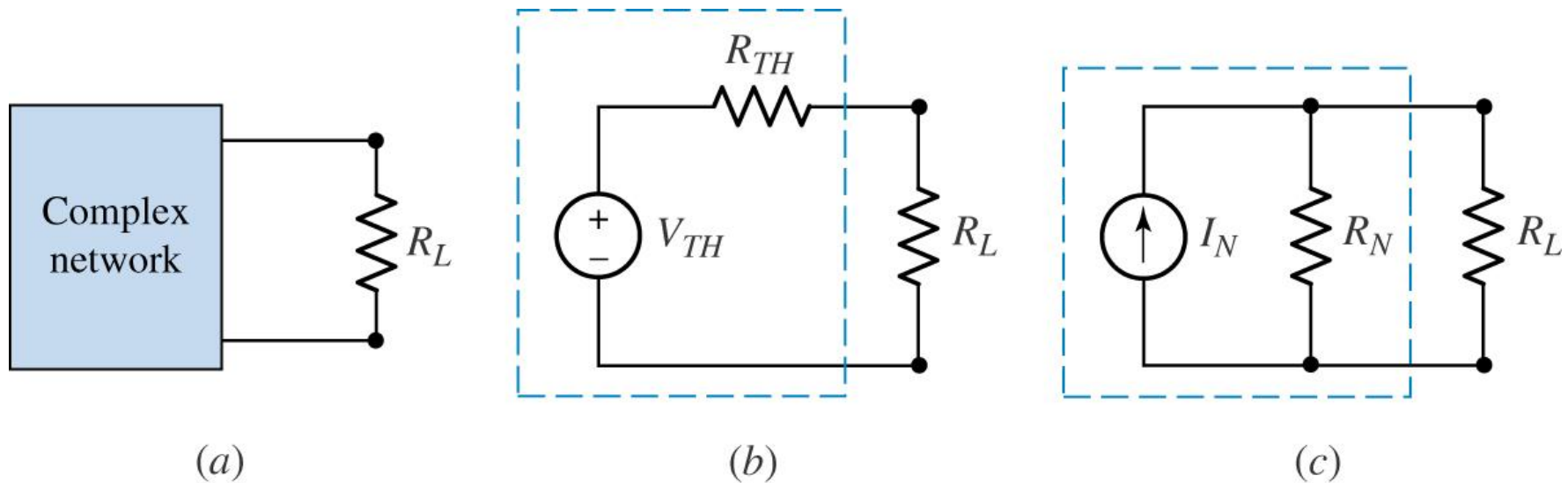






- (a) A complex network including a load resistor R_L .
- (b) A Thévenin equivalent network connected to R_L .
- (c) A Norton equivalent network connected to R_L .

Thevenin's theorem:

Given any linear circuit, rearrange it in the form of two networks A and B connected by two wires. Define a voltage v_{oc} as the **open-circuit voltage** which appears across the terminals of A when B is disconnected. Then all currents and voltages in B will remain unchanged if all *independent* voltage and current sources in A are “killed” or “zeroed out,” and an independent voltage source v_{oc} is connected, with proper polarity, in series with the dead (inactive) A network.




Example 5.6:

Determine the Thevenin equivalent.

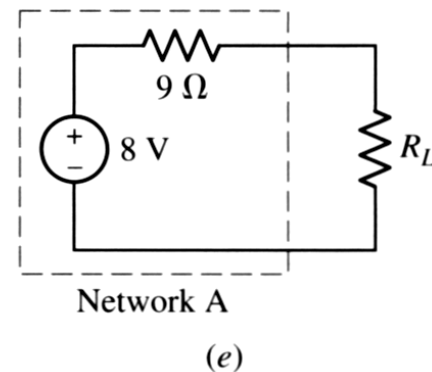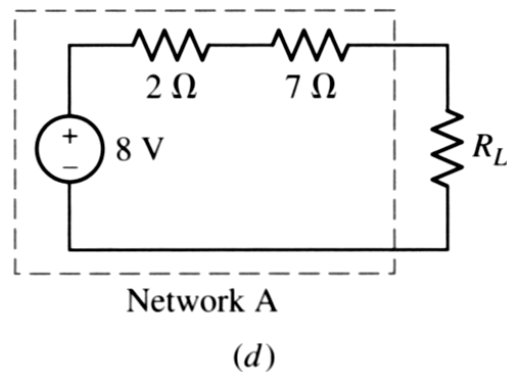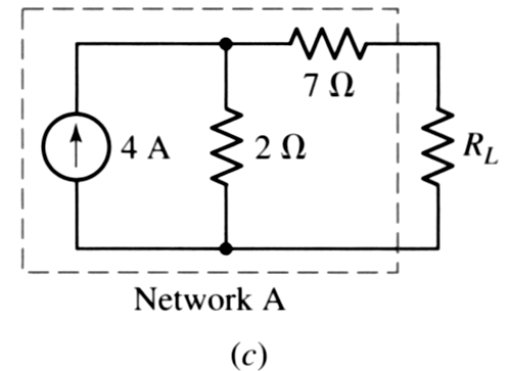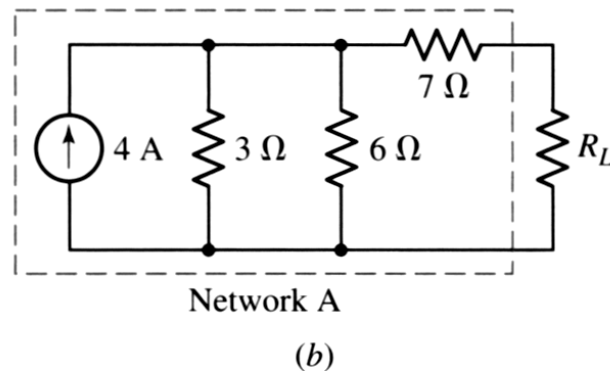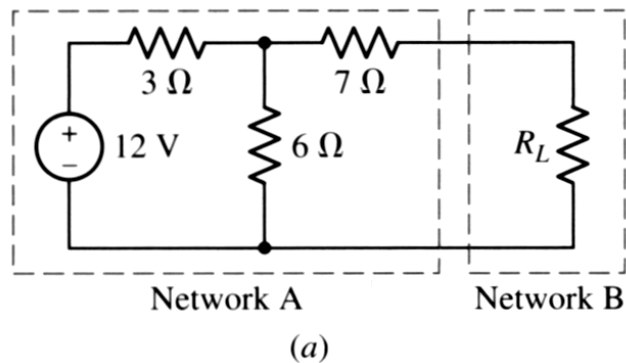

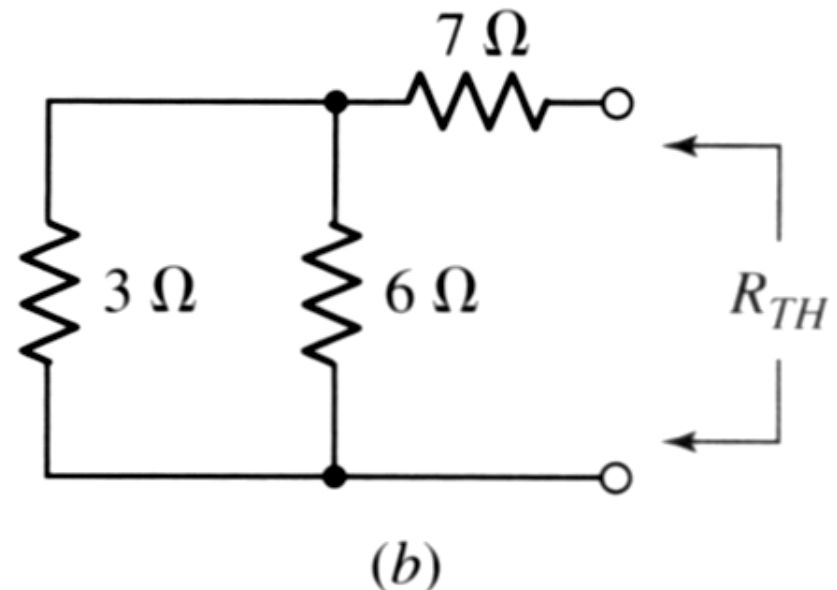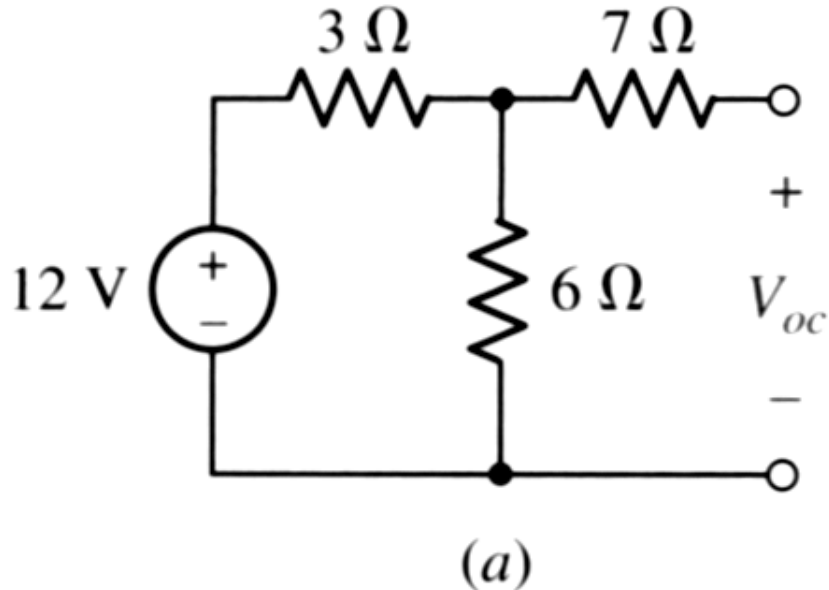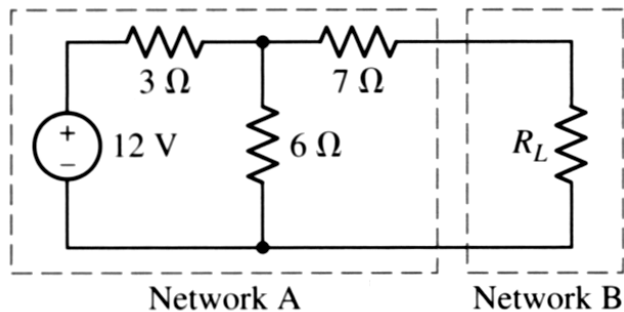
Example:

Determine the Thevenin equivalent. (use Theory)




Practice: 5.5

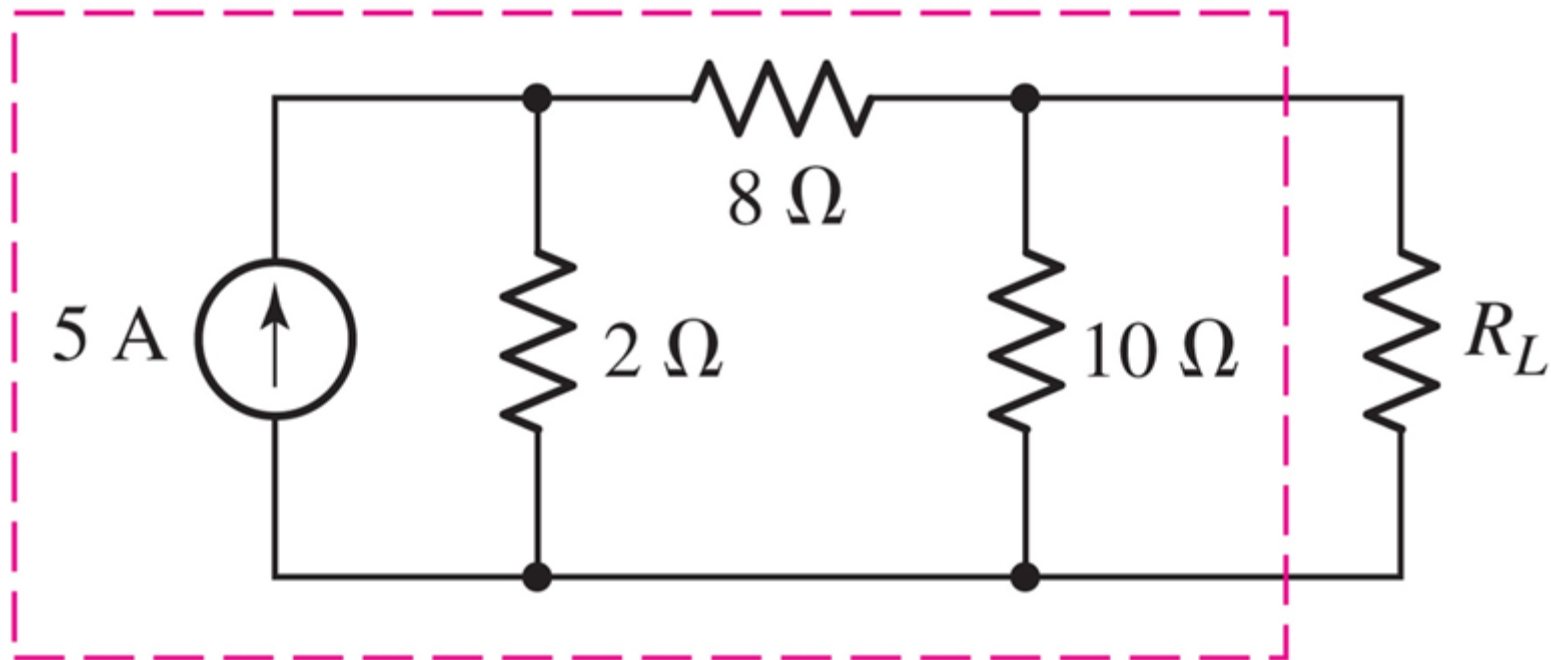Using repeated source transformations, determine the Norton equivalent of the highlighted network




Practice: 5.6

Use Thevenin's theorem to find the current through the 2- Ω resistor

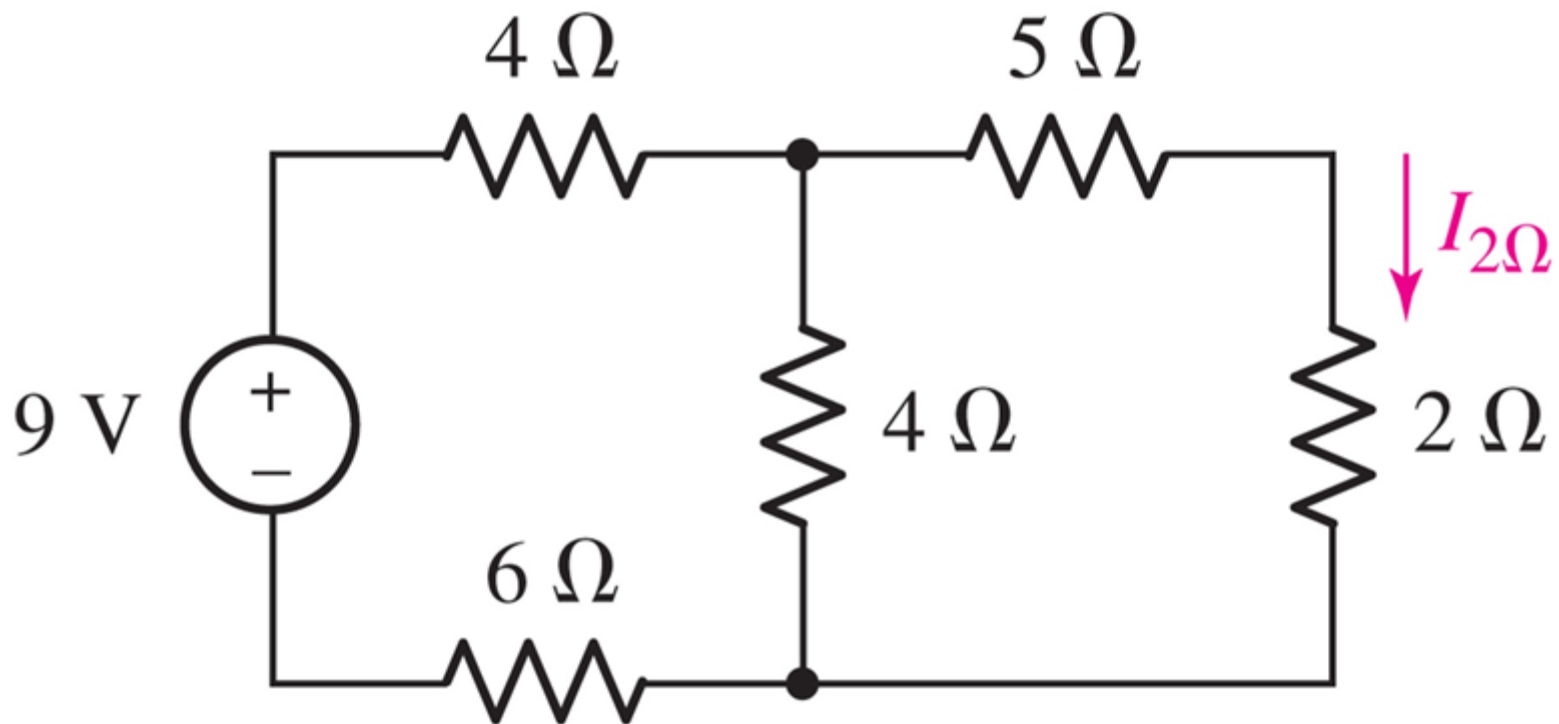



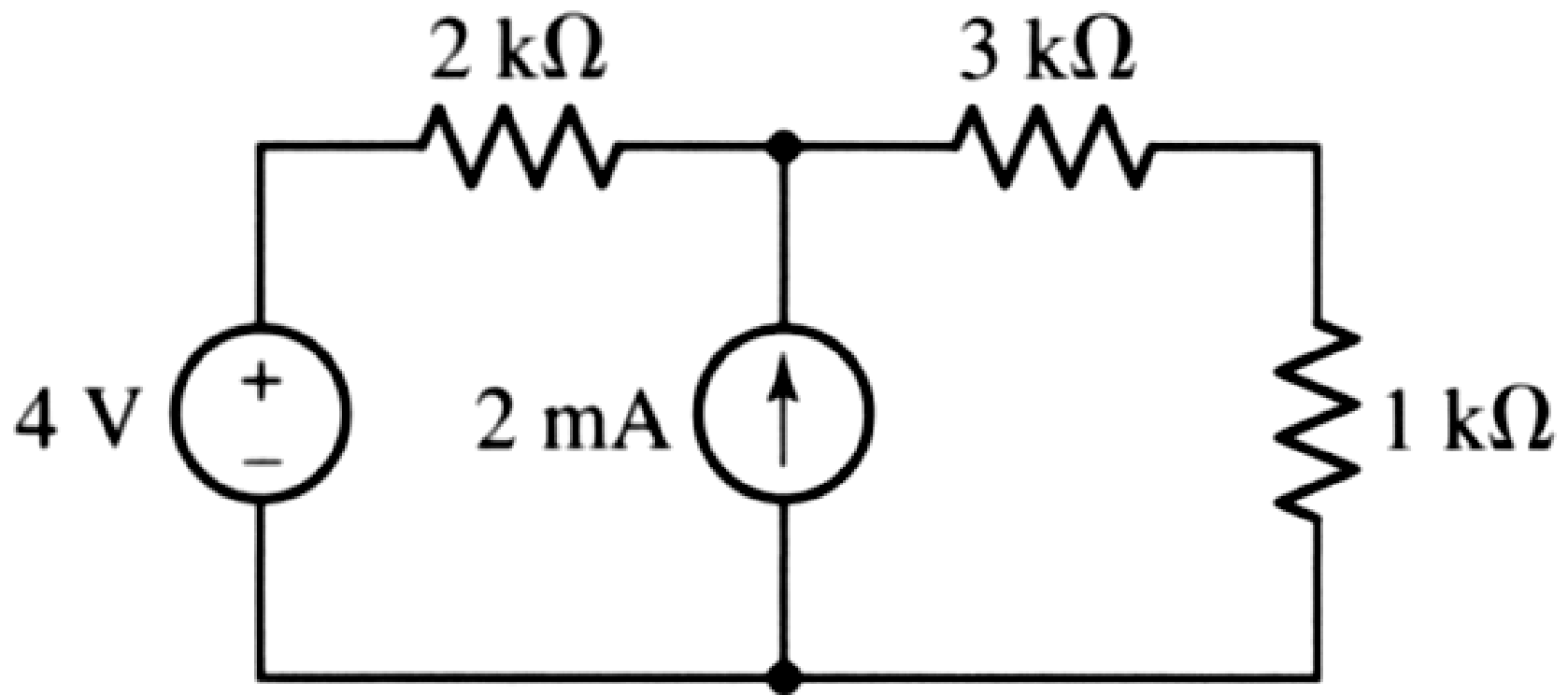
Example 5.8:

Determine the **Thevenin equivalent** for the network faced by 1-kohm .



Example:

Determine the Thevenin equivalent.

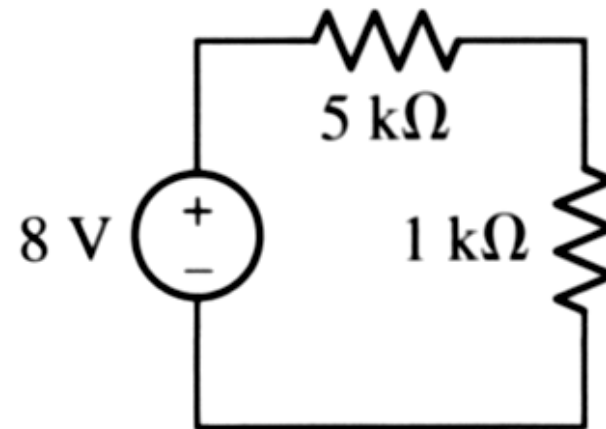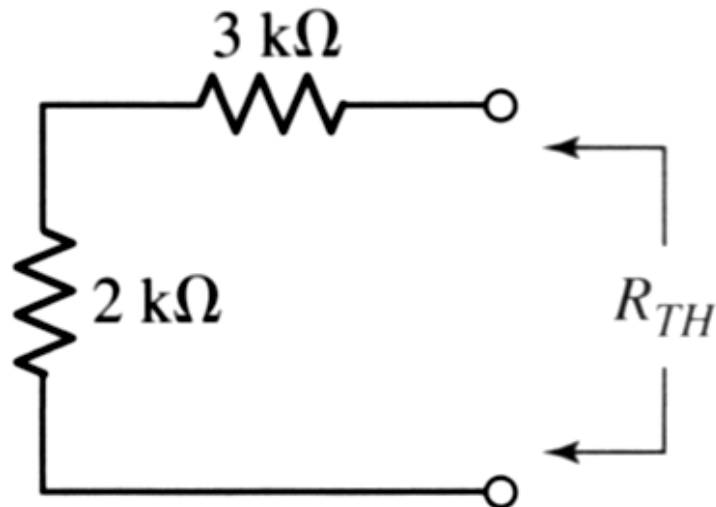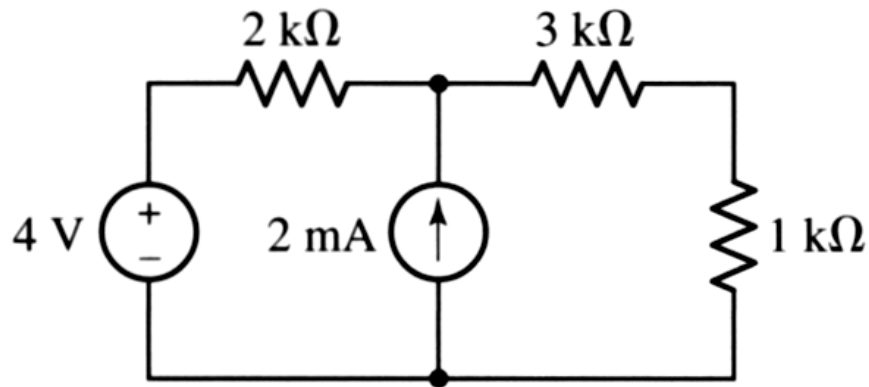


Norton's theorem:

Given any linear circuit, rearrange it in the form of two networks A and B connected by two wires. If either network contains a dependent source, its control variable must be in that same network.

Define a current i_{sc} as the **short circuit current** that appears when B is disconnected and the terminals of A are short-circuited. Then all currents and voltages in B will remain unchanged if all *independent* voltage and current sources in A are “killed” or “zeroed out,” and an independent current source i_{sc} is connected, with proper polarity, in parallel with the dead (inactive) A network


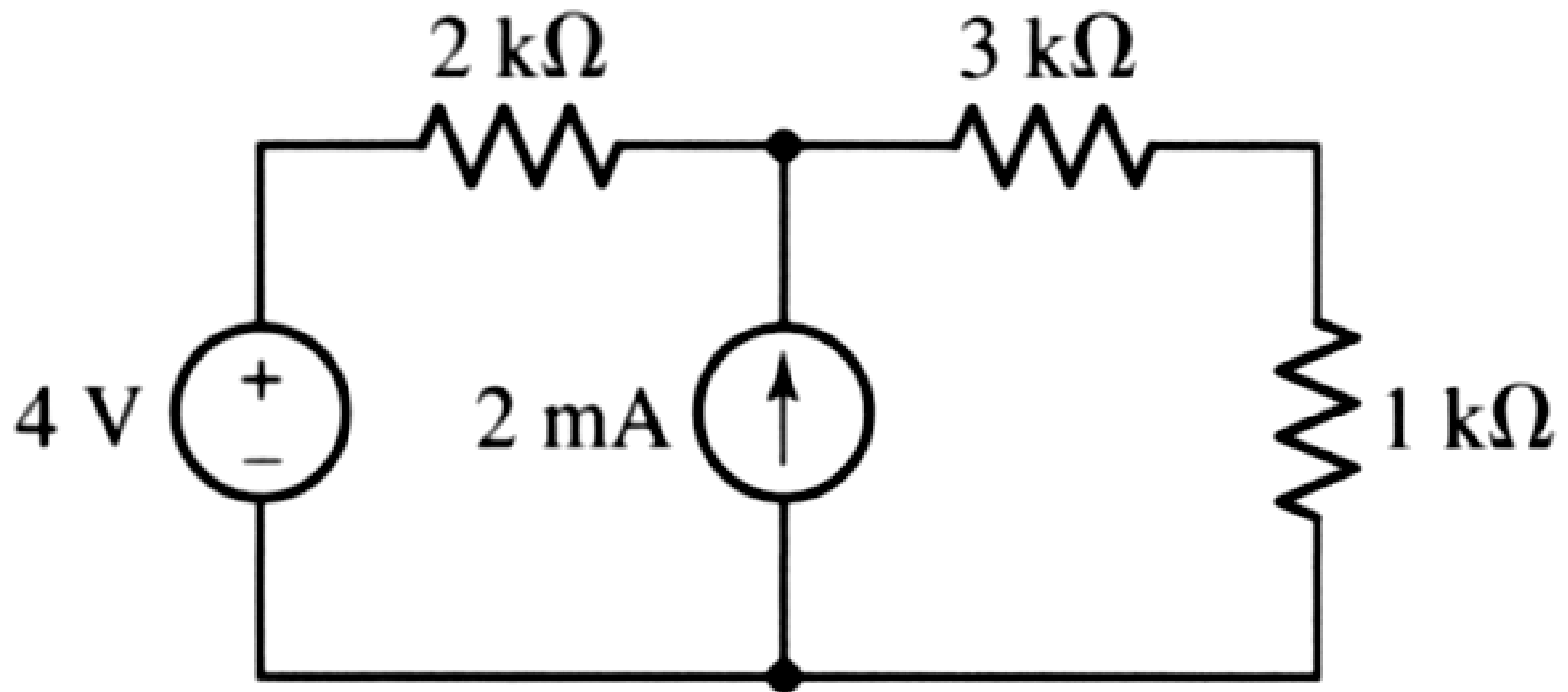
Example:

Determine the **Norton equivalent** for the network faced by 1-kohm .




Example:

Determine the Norton equivalent.

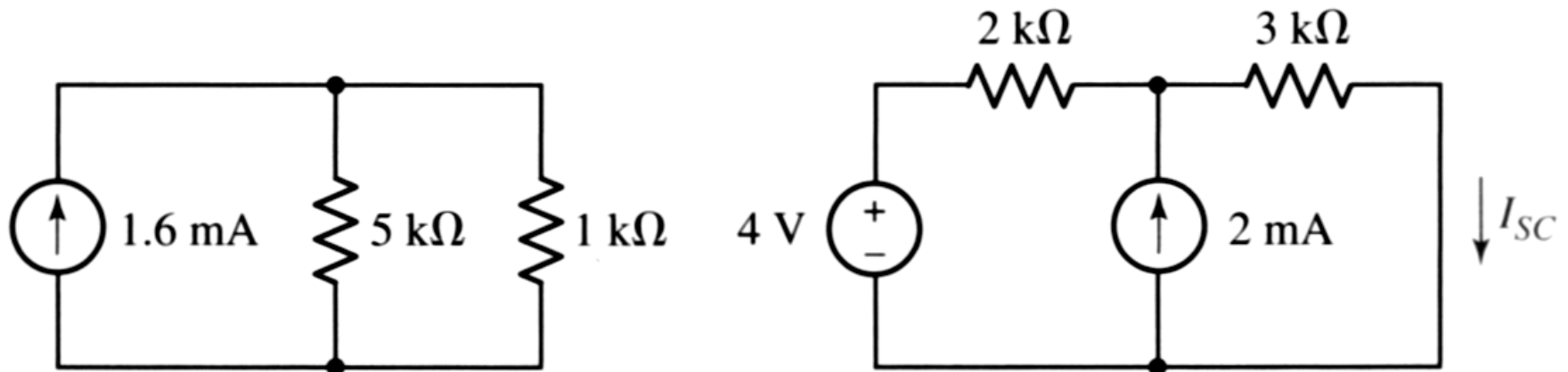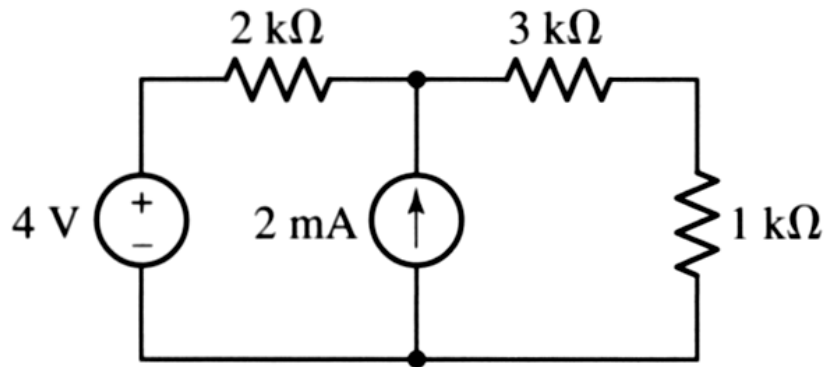


Practice: 5.7

Determine the Thevenin and Norton equivalents

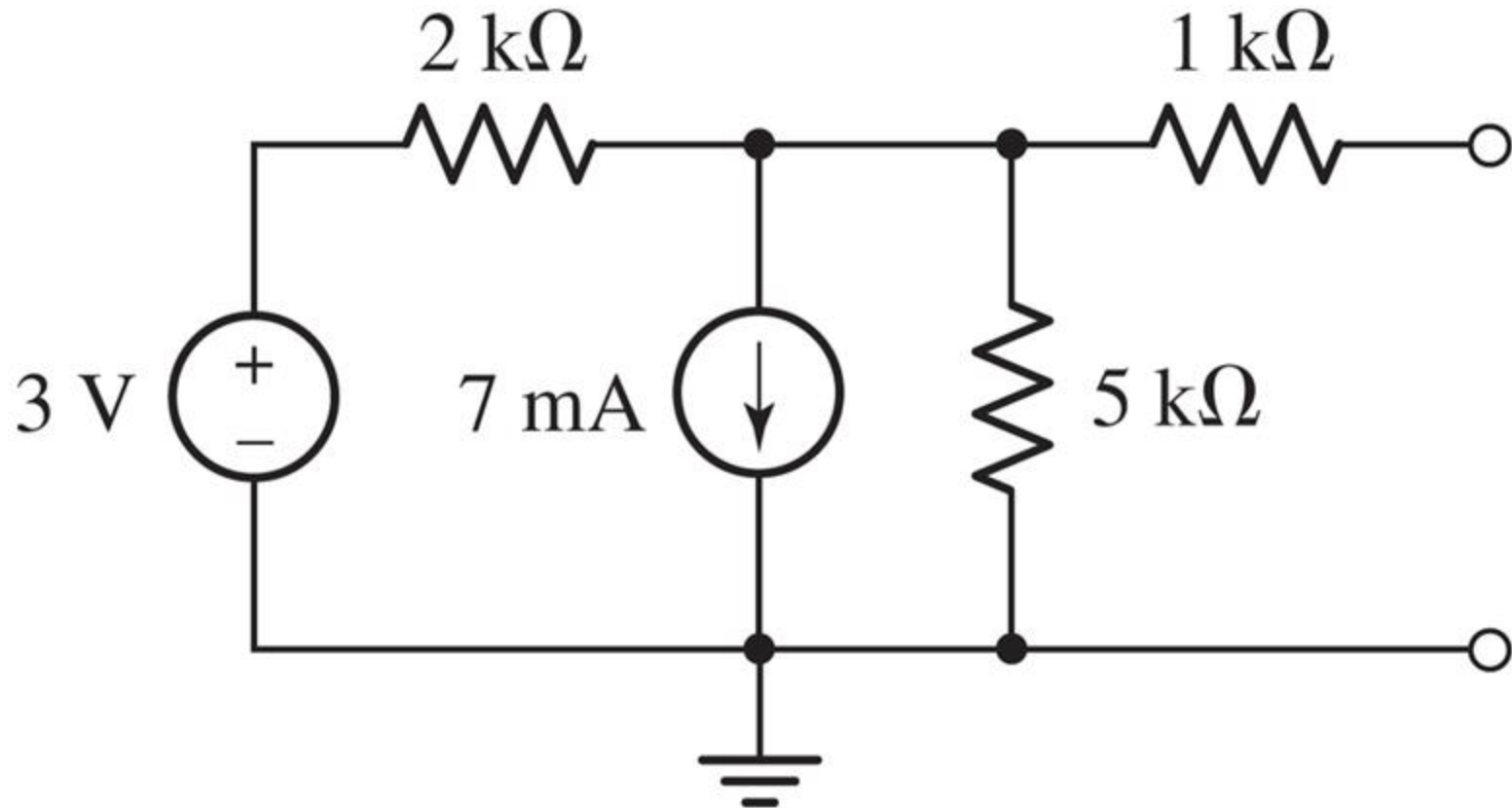

Example 5.9:


Determine the Thevenin equivalent.

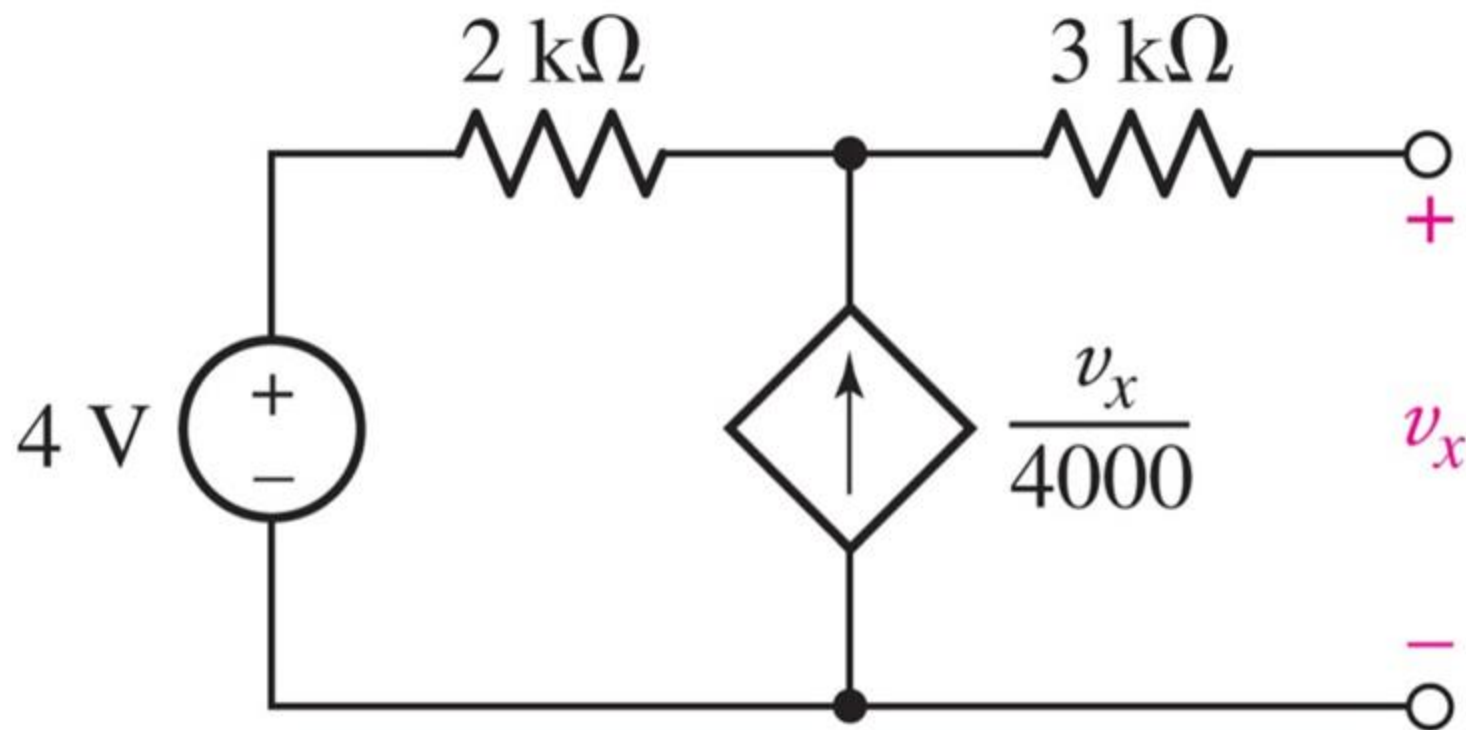

(a)

Example:

Determine the Thevenin equivalent.

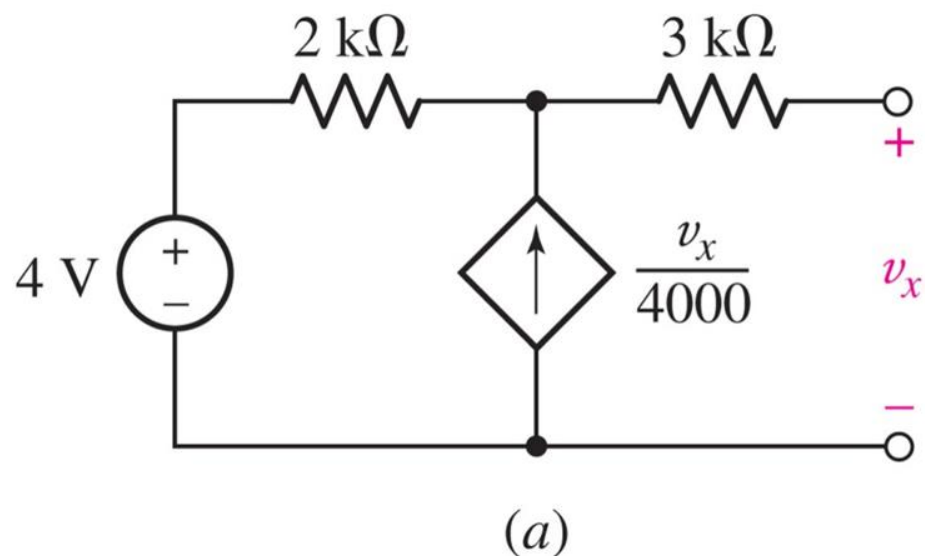

Find V_{oc} : $V_{oc} = V_x$


$$-4 + 2k \left(\frac{-V_x}{4000} \right) + 3k(0) + V_x = 0$$

$$\therefore V_x = 8 \text{ V.}$$


Find I_{sc} : $I_{sc} = \frac{4}{(2k + 3k)} = 0.8 \text{ mA.}$

$$\therefore R_{TH} = \frac{V_{oc}}{I_{SC}} = \frac{8}{0.8 \times 10^{-3}} = 10k\Omega$$


Example:

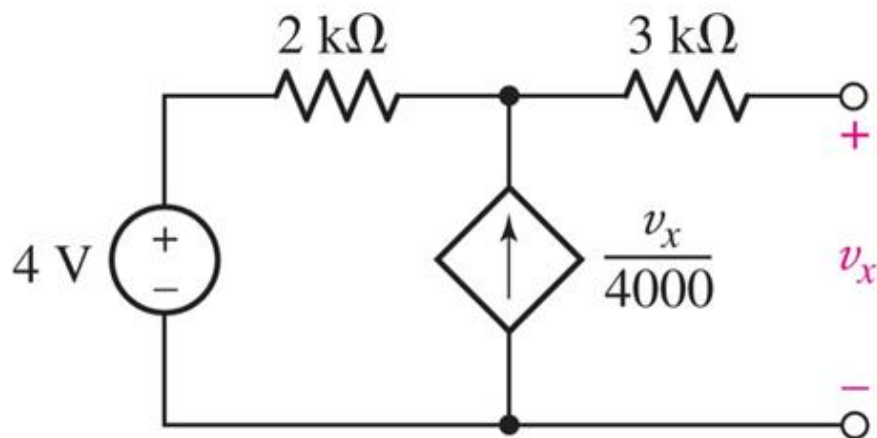

(a)

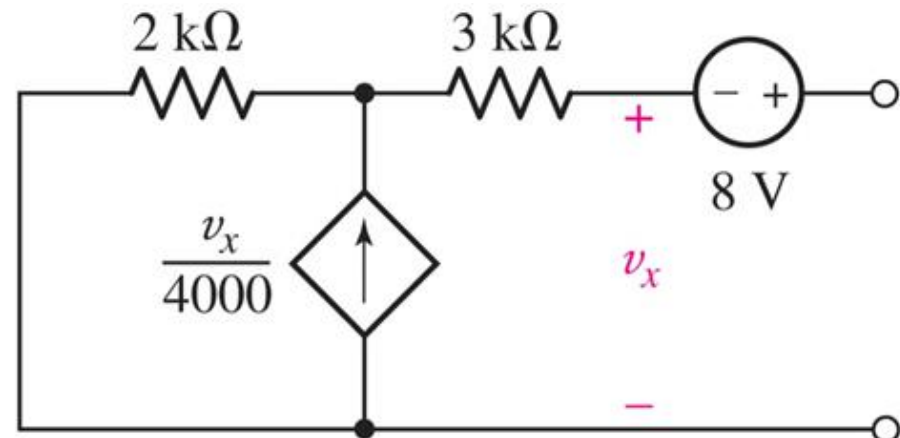


(b)

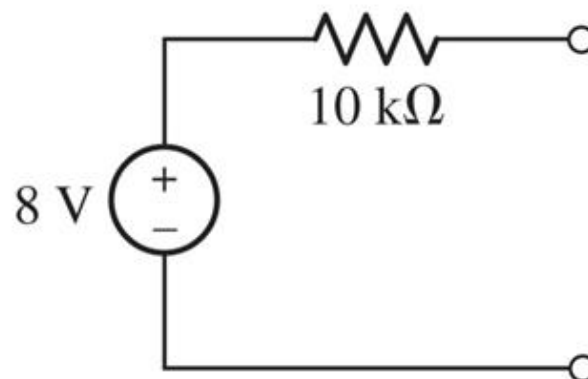

(c)


Practice: 5.8

Determine the Thevenin equivalent

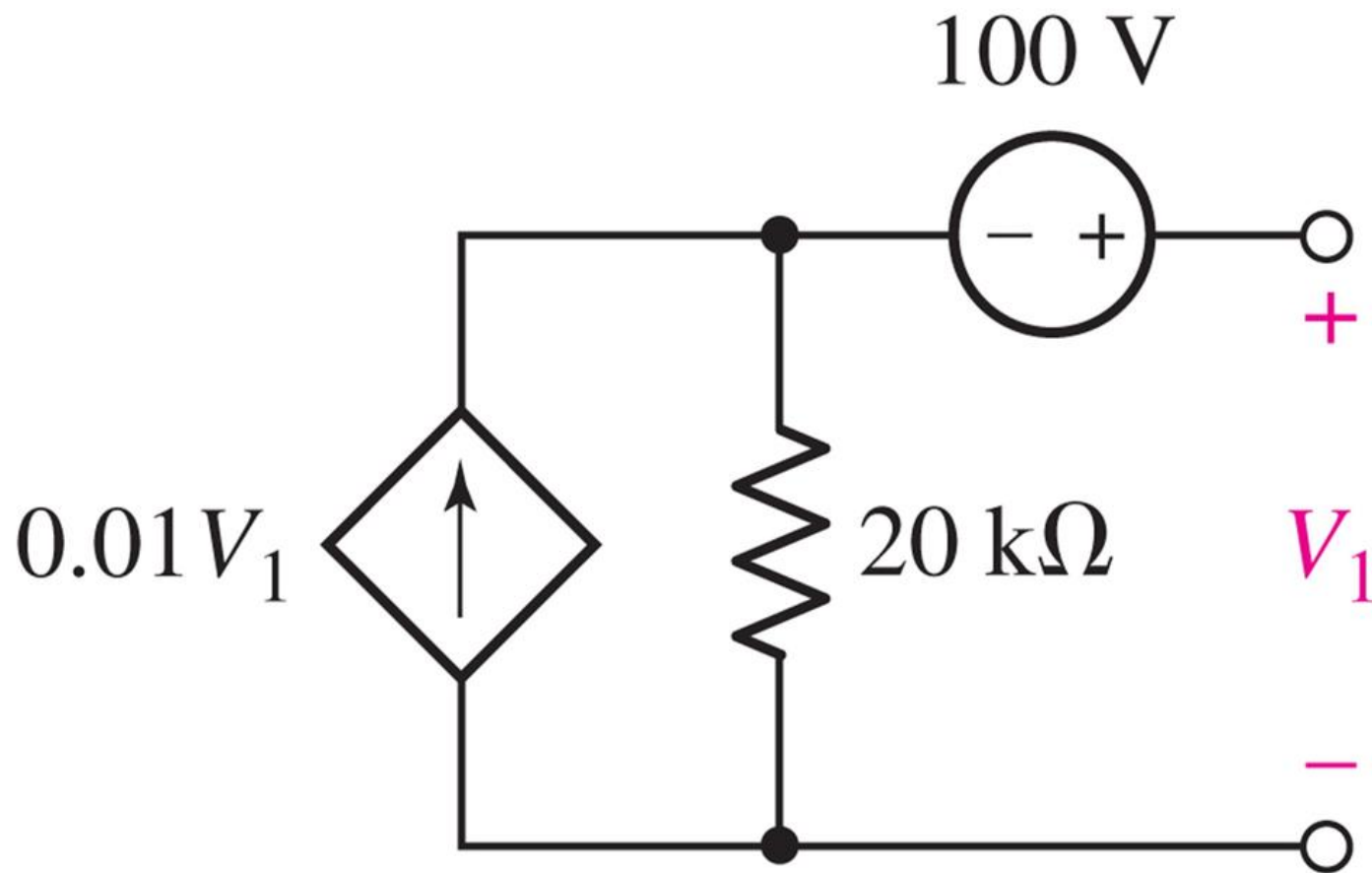

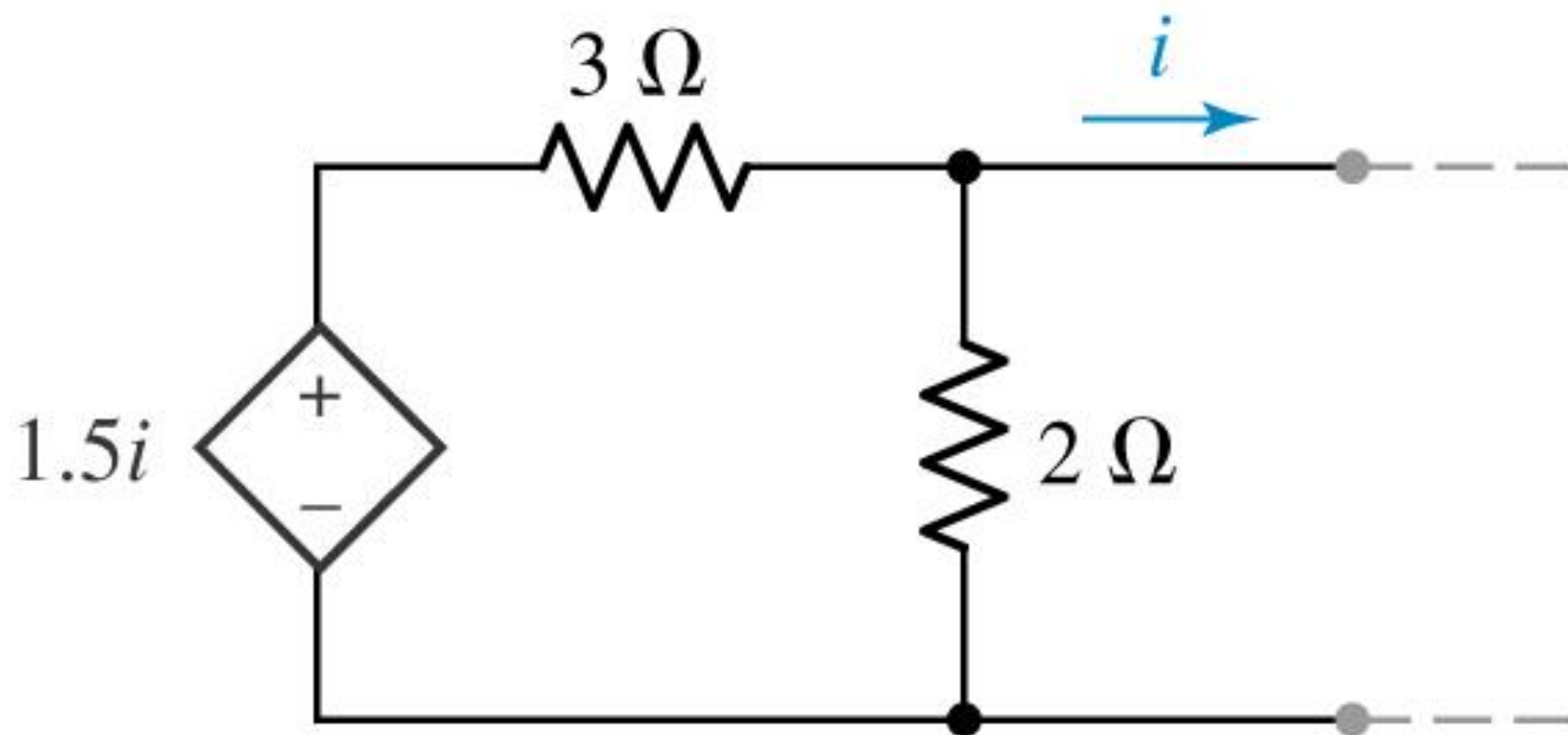
Example 5.10:

Find the Thévenin equivalent of the circuit shown.



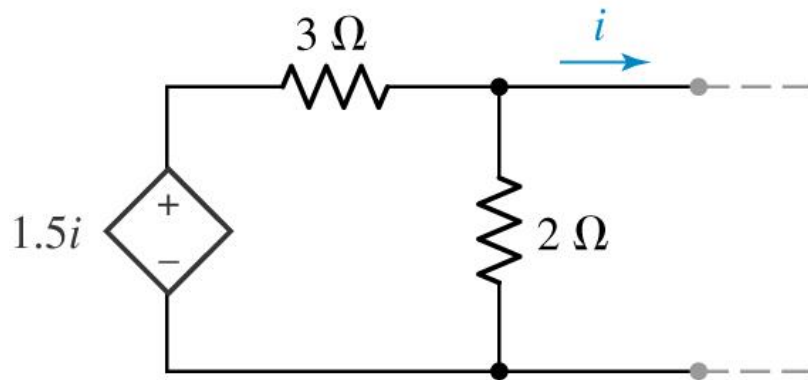Example:

Find the Thévenin equivalent of the circuit shown.




$$\text{Find } V_{oc} : \because i = 0; \therefore V_{oc} = 0$$

Apply a 1-A. source,

$$\frac{v_{test} - 1.5(-1)}{3} + \frac{v_{test}}{2} - 1 = 0$$


$$\therefore v_{test} = 0.6 \text{ V.}$$

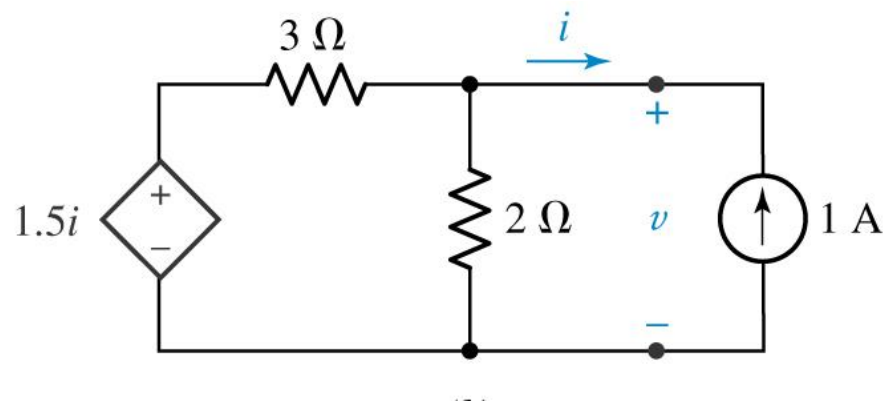

$$\text{Thus } R_{TH} = \frac{v_{test}}{1A} = 0.6\Omega$$


Example:

the Thévenin equivalent

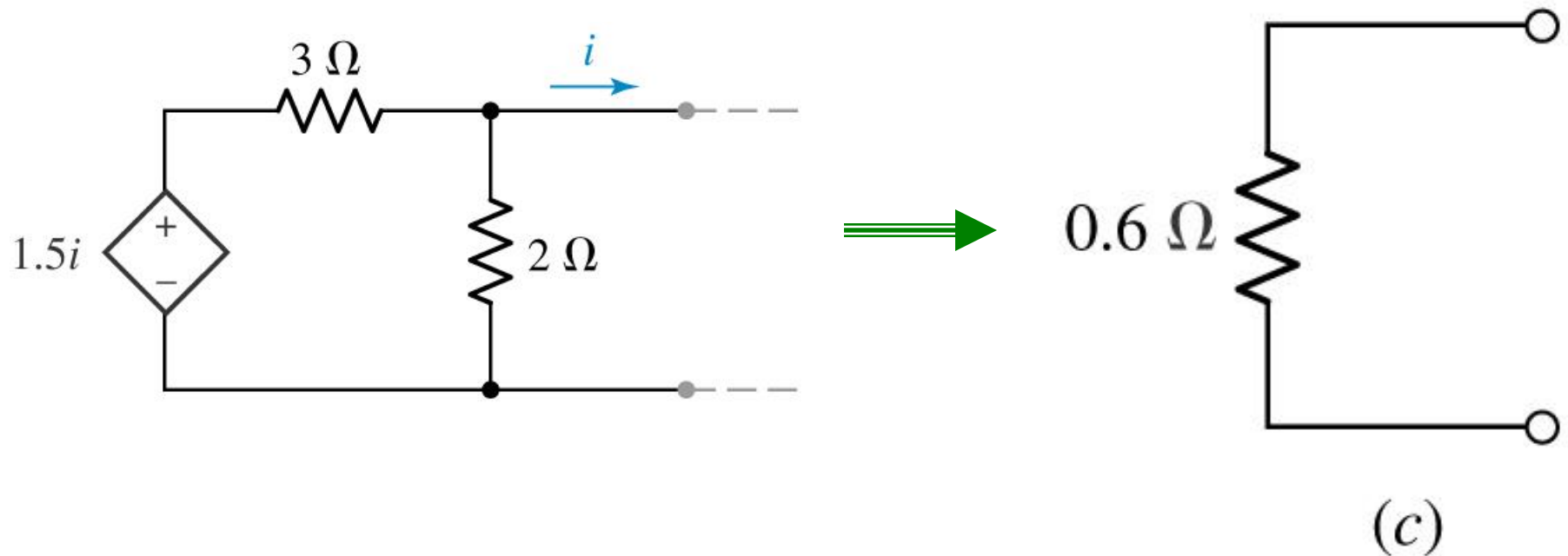

Practice: 5.9

Determine the Thevenin equivalent

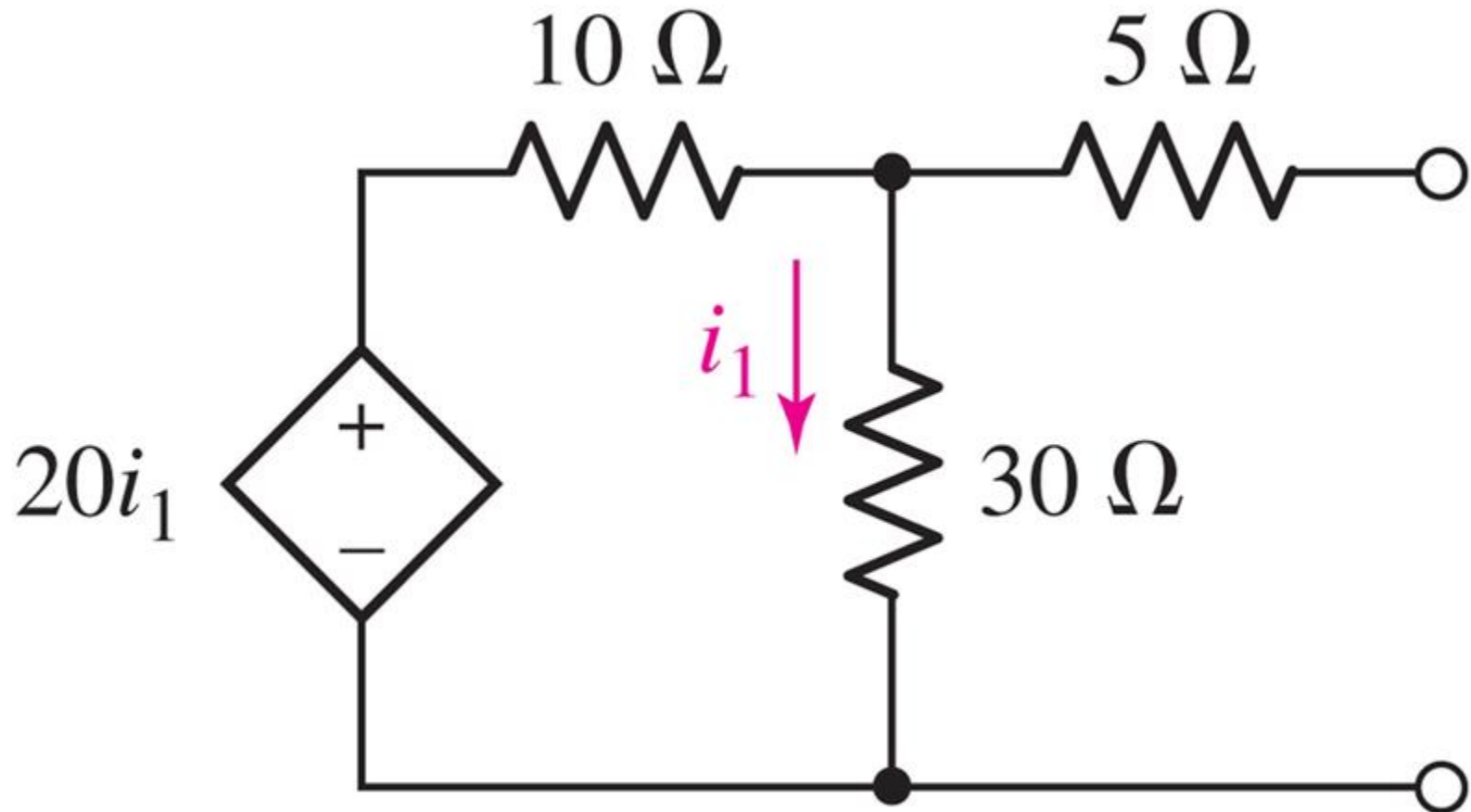

Maximum Power Transfer:

The power delivered to the load R_L is


$$p_L = i_L^2 R_L = \frac{v_s^2 R_L}{(R_s + R_L)^2}$$

To find the value of R_L that absorbed a maximum power from the given practical source, we differentiate with respect to R_L :

$$\frac{dp_L}{dR_L} = \frac{(R_s + R_L)^2 v_s^2 - v_s^2 R_L 2(R_s + R_L)}{(R_s + R_L)^4} = 0$$


Or

$$R_s = R_L$$

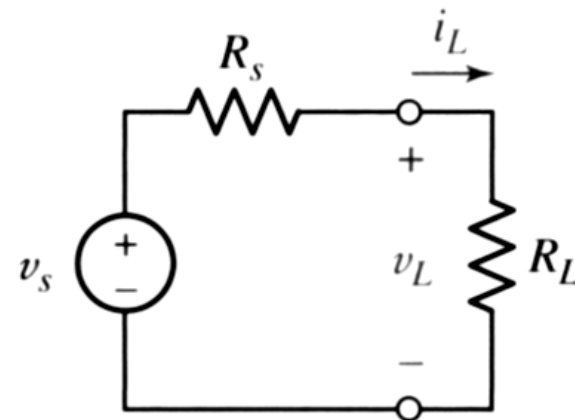

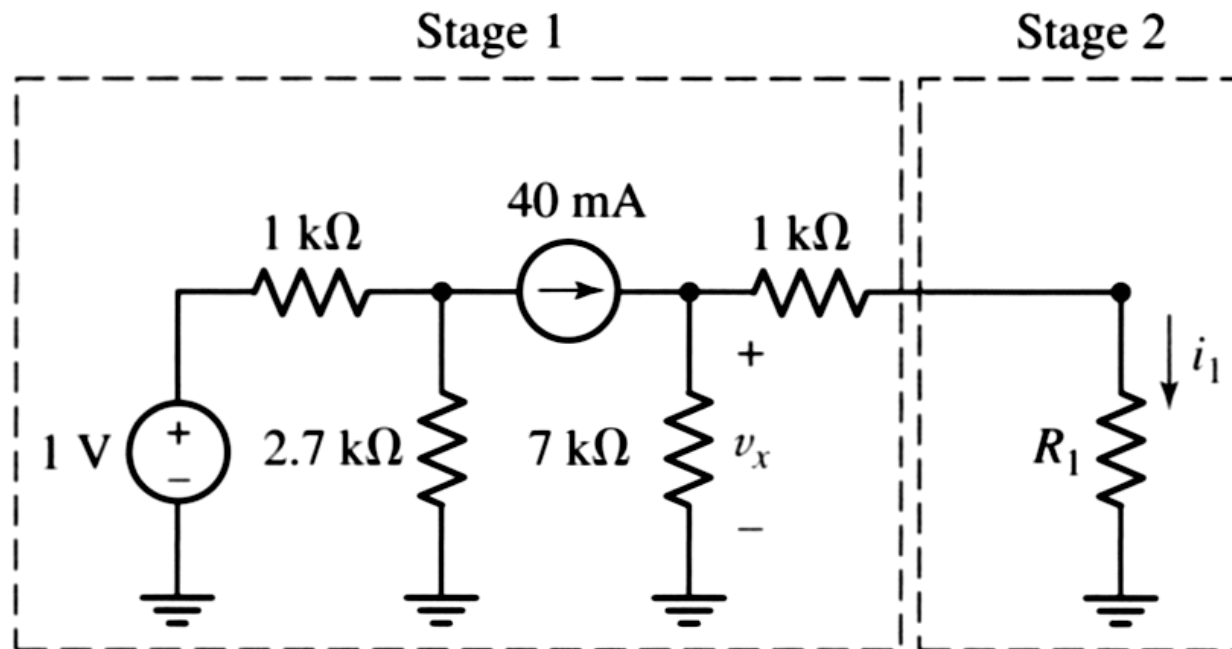Example:

Ex55p141: Select R_1 so that maximum power is transferred from stage 1 to stage 2



Example:

Ex55p141: Select R_1 so that maximum power is transferred from stage 1 to stage 2

55. Thévenize the left-hand network, assigning the nodal voltage V_x at the free end of right-most 1-k Ω resistor.

A single nodal equation: $40 \times 10^{-3} = \frac{V_x|_{oc}}{7 \times 10^3}$


So $V_{TH} = V_x|_{oc} = 280 \text{ V}$

$R_{TH} = 1 \text{ k} + 7 \text{ k} = 8 \text{ k}\Omega$

Select $R_1 = R_{TH} = 8 \text{ k}\Omega$.

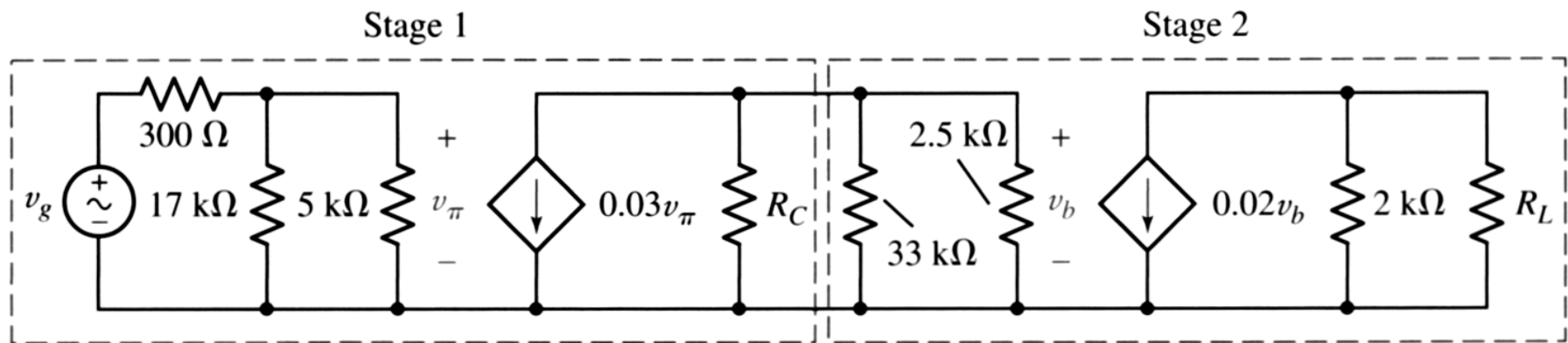Example 5.11:




the circuit shown is a model of a two-stage bipolar junction transistor amplifier. Determine the value of R_C required for the first stage to deliver maximum power to the second stage.



Example:

Stage 1



Stage 2

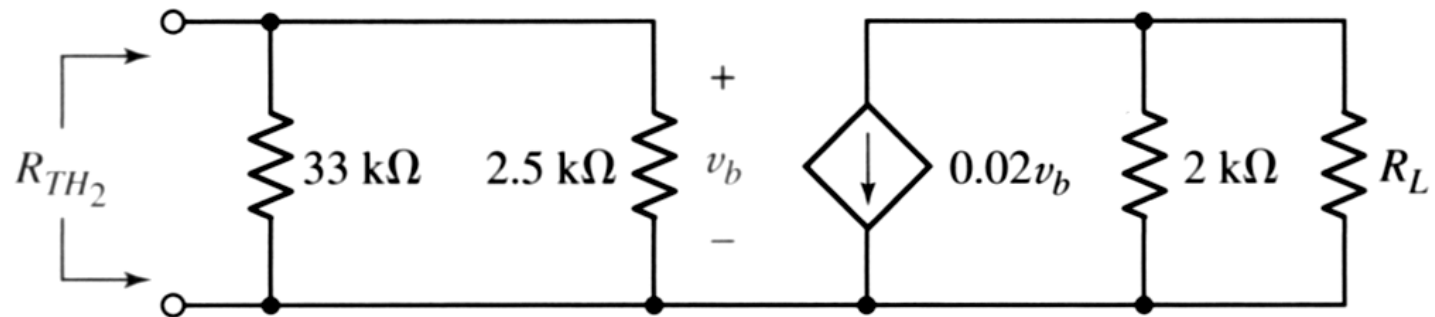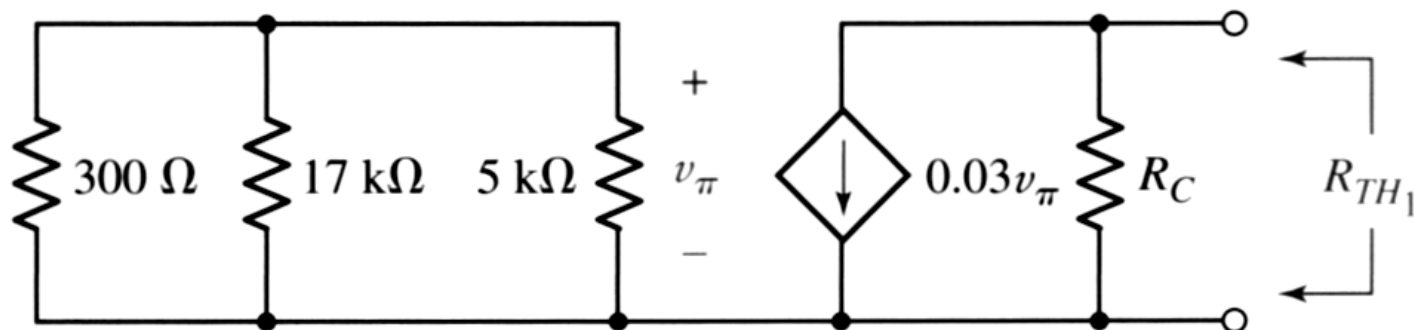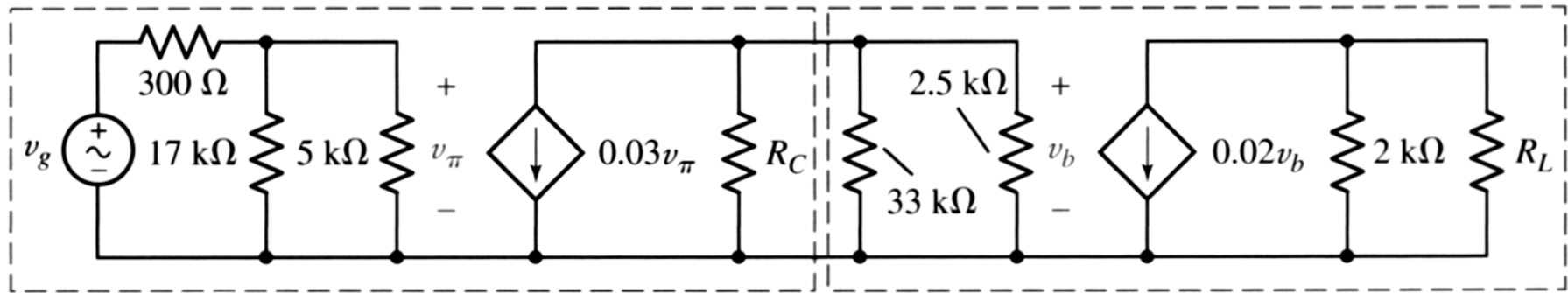

Example:


Stage 1

Stage 2

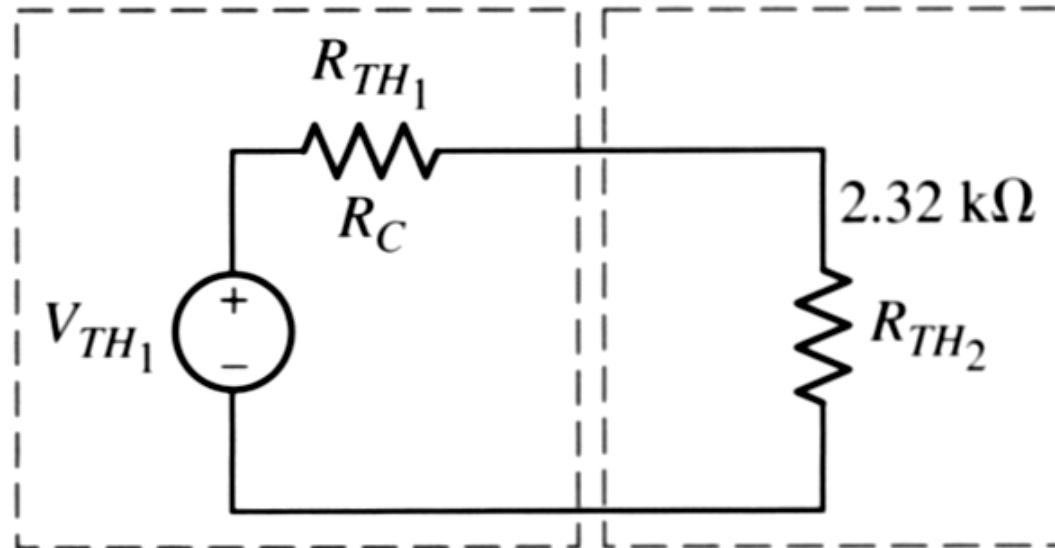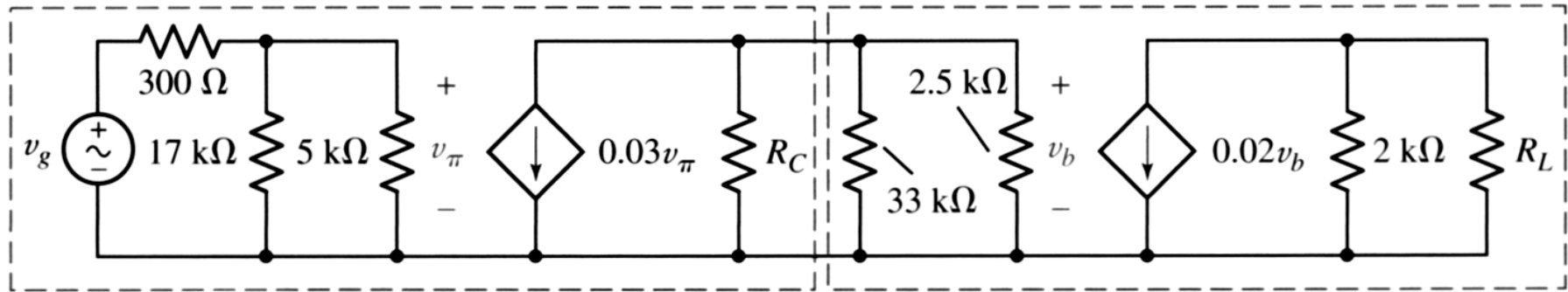



Practice: 5.10

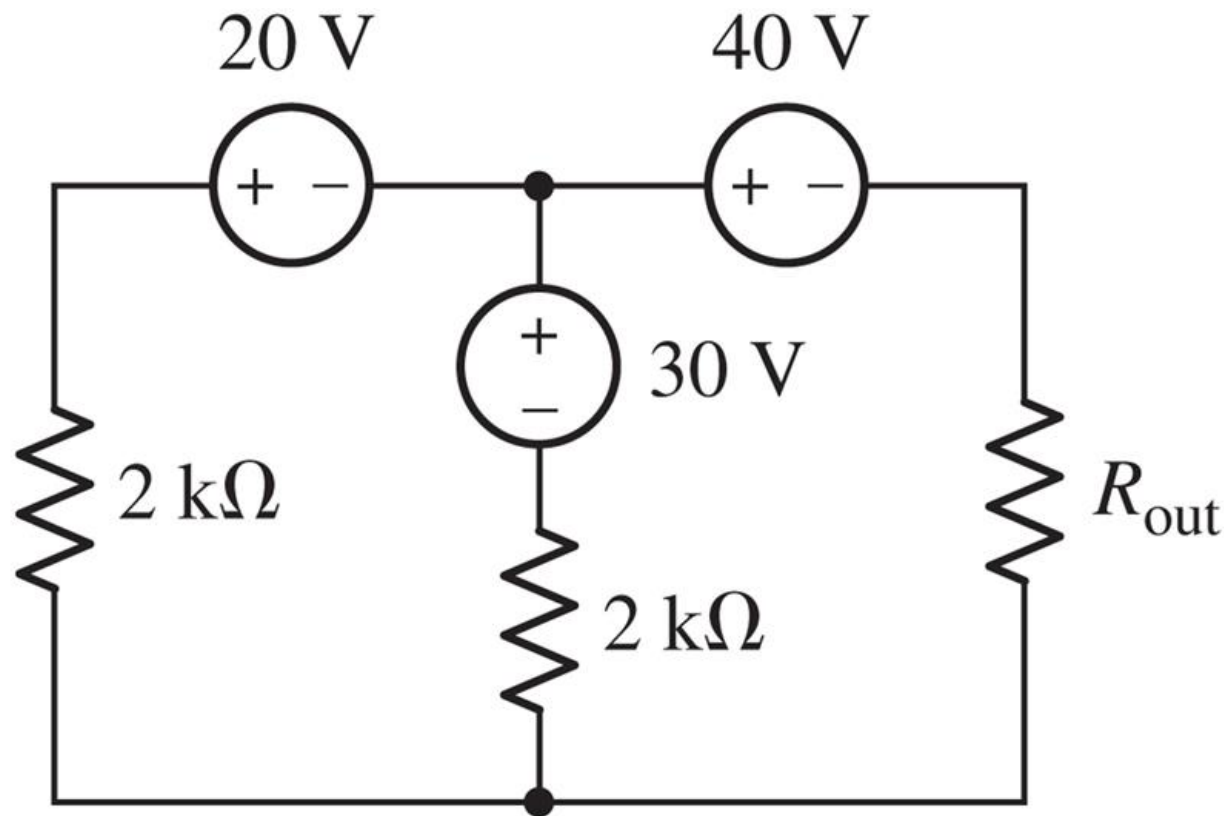- (a) If $R_{out} = 3\text{ k}\Omega$, find the power delivered to it
- (b) What is the maximum power that can be delivered to any R_{out}
- (c) What two different values of R_{out} will have exactly 20 mW delivered to them?





Delta-Wye Conversion:

A **delta** network: (Δ)

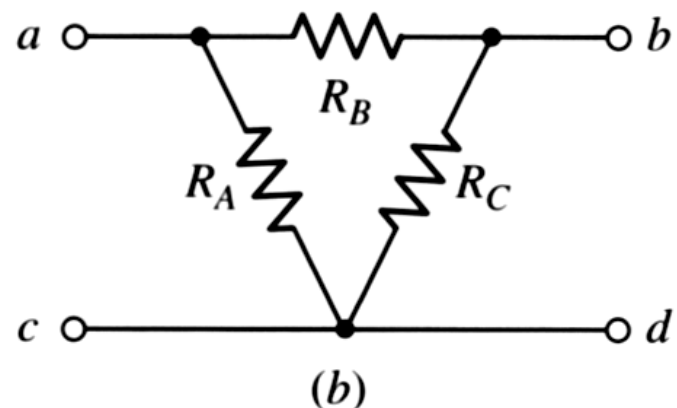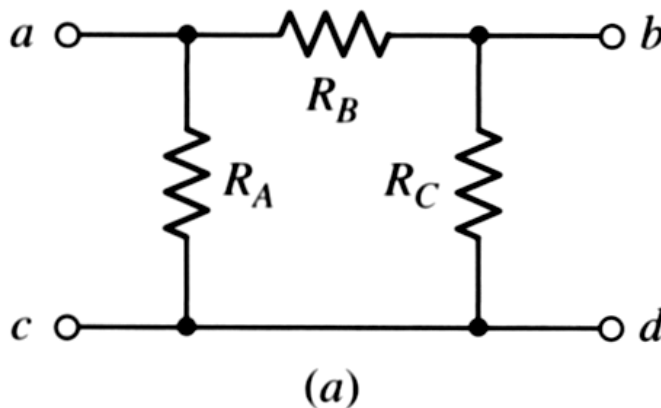

A **Wye** network: (Y)

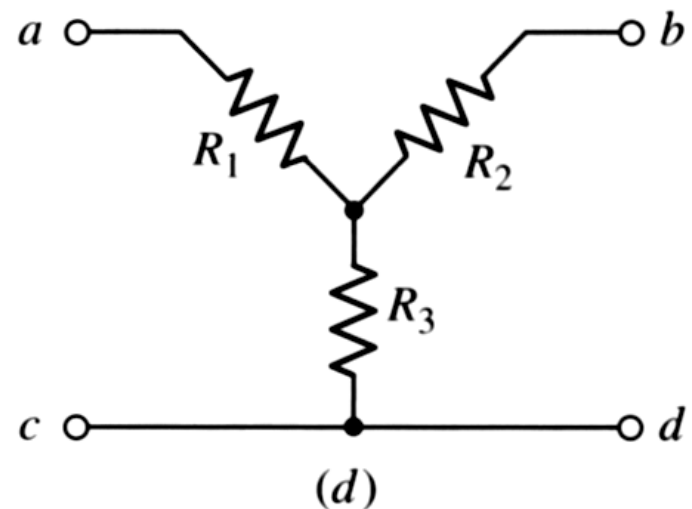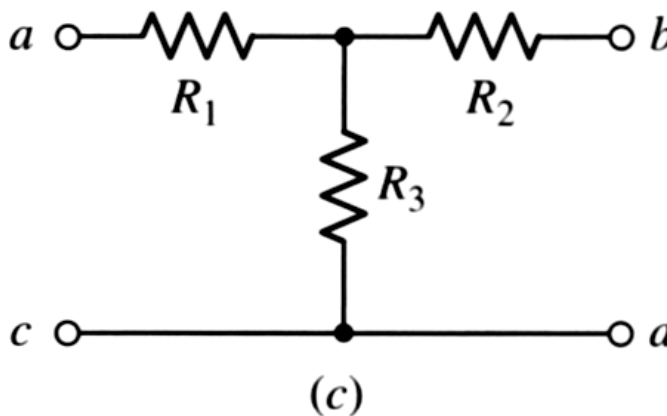

Delta-Wye Conversion:

$$R_{ab} = R_1 + R_2$$

$$= R_B // (R_A + R_C) \dots (1)$$

$$R_{bc} = R_2 + R_3$$

$$= R_C // (R_A + R_B) \dots (2)$$

$$R_{ac} = R_1 + R_3$$

$$= R_A // (R_B + R_C) \dots (2)$$

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$


$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$


$$R_3 = \frac{R_C R_A}{R_A + R_B + R_C}$$

Example 5.12:

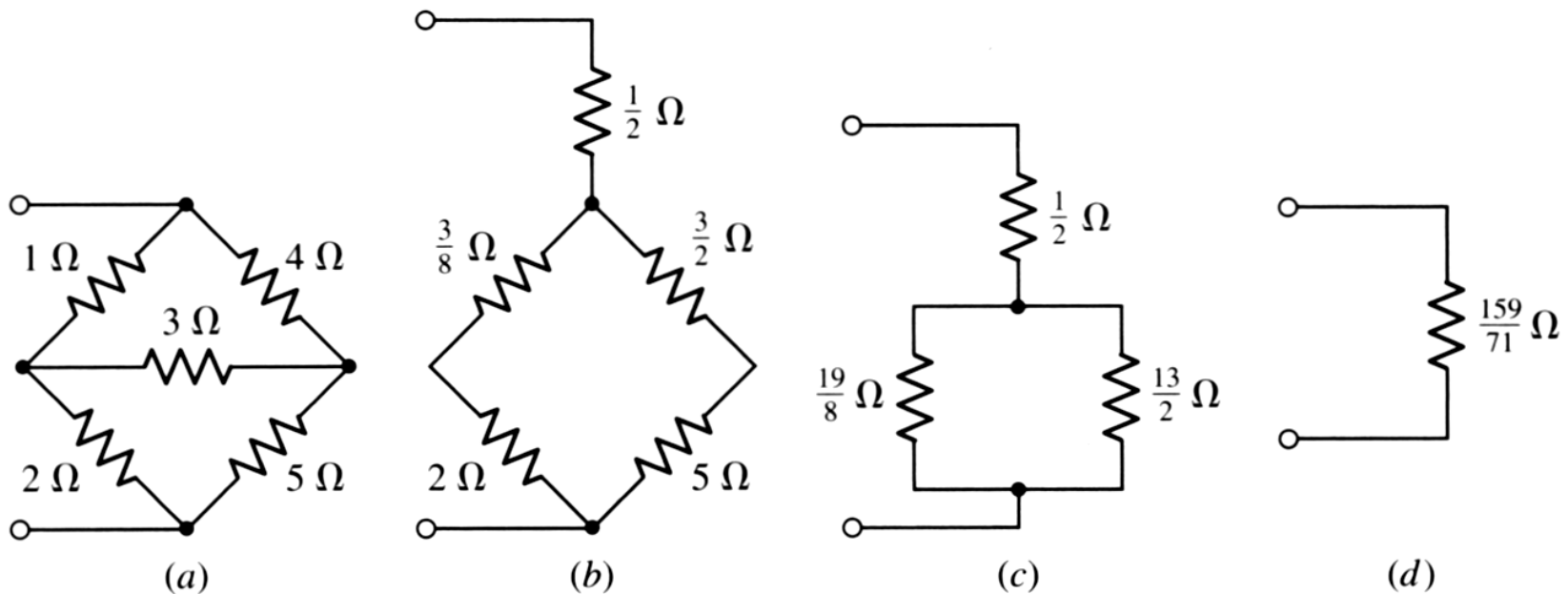


Practice: 5.11

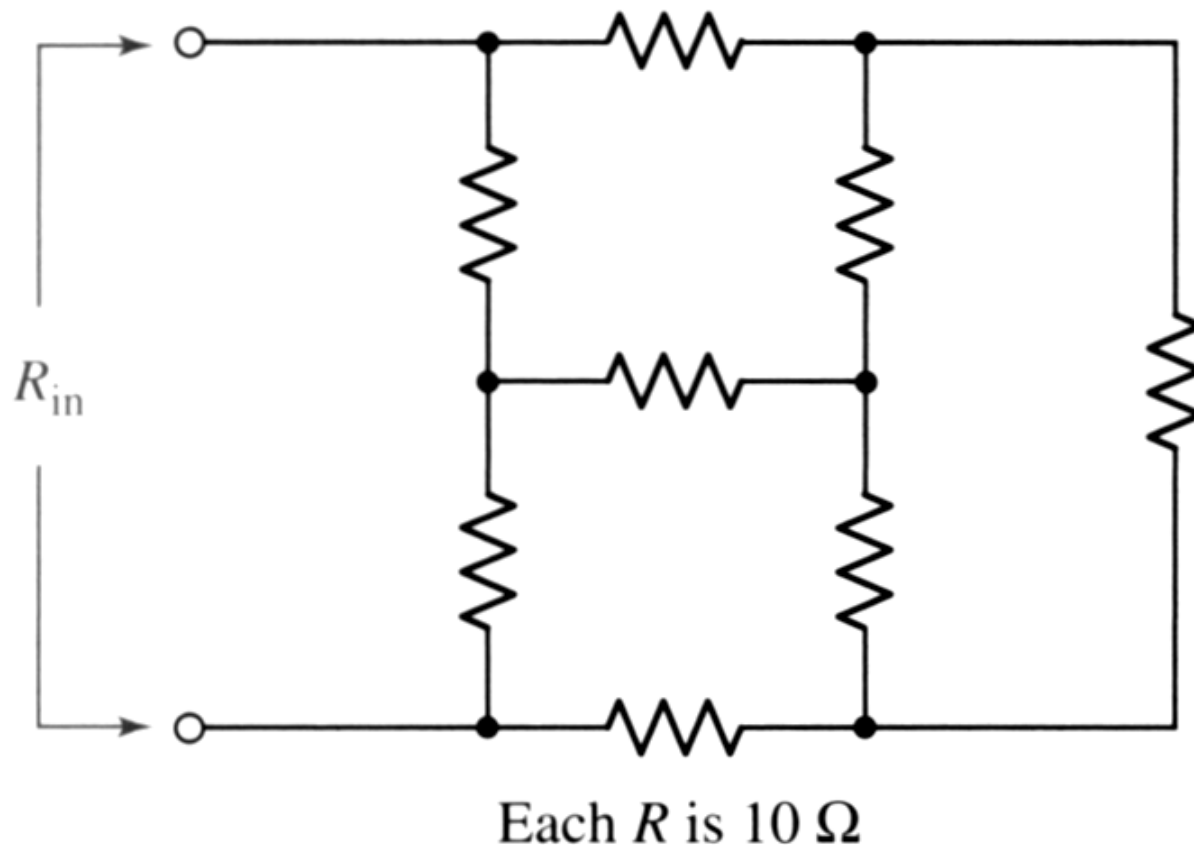Use the technique of Y- Δ conversion to find the thévenin equivalent resistance of the circuit



Example:

Ch5-66, page 143, Sixth Edition

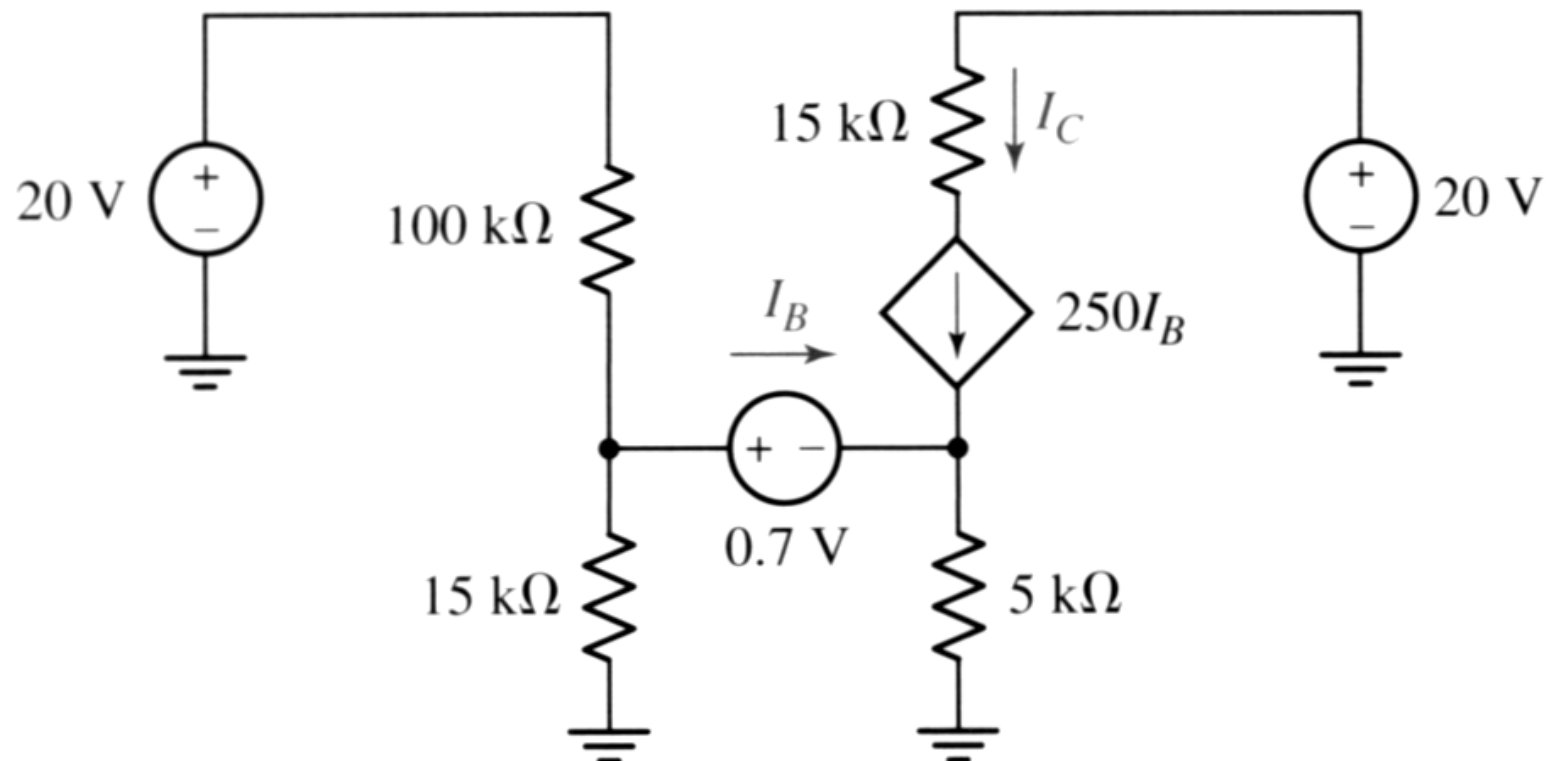

Homework:

W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.

Copyright ©2002 McGraw-Hill. All rights reserved.