

# Component Measurements



EIE 240 Electrical and Electronic Measurement  
Class 9, February 9, 2012


werapon.chi@kmutt.ac.th

1

## Component RLC

- Impedance =  $\frac{\text{Potential Difference Phasor}}{\text{Current Phasor}}$
- Impedance = Resistance + j Reactance ,  $j = \sqrt{-1}$

$$\begin{aligned} Z &= R + j X \\ &= |Z|\cos\phi + j |Z|\sin\phi \\ &= |Z|e^{j\phi} \\ &= |Z| \angle \phi \end{aligned}$$

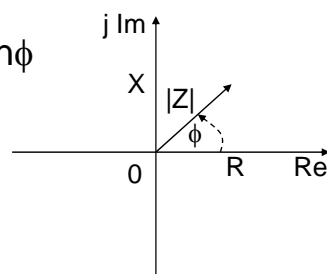


$$\begin{aligned} \text{where } |Z| &= \sqrt{R^2 + X^2} \\ \phi &= \tan^{-1}(X/R) \end{aligned}$$

2

## AC Response

- Resistor

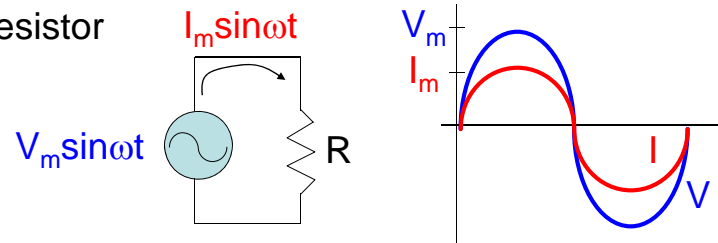


Resistance

$$V = R I$$

$$= R I_m \sin \omega t$$

$$= V_m \sin \omega t$$

(V and I in phase)

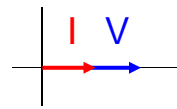


Phasor Diagram

3
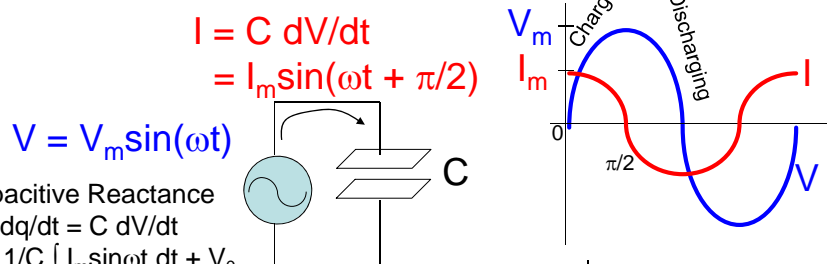
## AC Response (Cont'd)

- Capacitor is a passive component storing the energy in an electric field charged by the voltage across the dielectric.



Capacitive Reactance

$$I = dq/dt = C dV/dt$$

$$V = 1/C \int I_m \sin \omega t dt + V_0$$


$$= -1/\omega C I_m \cos \omega t$$

$$= 1/\omega C I_m \sin(\omega t - \pi/2)$$

$$= X_C I_m \sin(\omega t - \pi/2)$$

$$= V_m \sin(\omega t - \pi/2)$$

(V lags I by 90°)

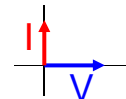

Phasor Diagram

$$X_C = 1/\omega C = 1/2\pi f C = \tau/2\pi C, \text{ Higher } f, \text{ Lower } X_C \text{ (Lowpass Filter)}$$

4



## AC Response (Cont'd)

- Inductor is a passive component storing the energy in a magnetic field induced by the electric current passing through it.

$$V = L \, di/dt$$

$$= V_m \sin(\omega t + \pi/2)$$

$$I_m \sin(\omega t)$$

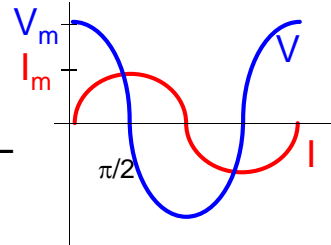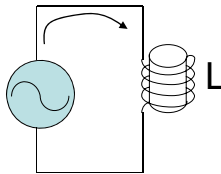

Inductive Reactance

$$V = d(N\phi)/dt$$

$$= L \, d(I_m \sin \omega t)/dt$$


$$= \omega L \, I_m \cos \omega t$$

$$= \omega L \, I_m \sin(\omega t + \pi/2)$$

$$= X_L I_m \sin(\omega t + \pi/2)$$

$$= V_m \sin(\omega t + \pi/2)$$

(V leads I by  $90^\circ$ )

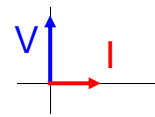

Phasor Diagram


$$X_L = \omega L = 2\pi fL = 2\pi L/\tau \quad , \quad \text{Higher } f, \text{ Higher } X_L \text{ (Highpass Filter)}$$

5

## Frequency Response

- The resonance of a series RLC circuit occurs when the inductive and capacitive reactances are equal in magnitude but cancel each other because they are  $180^\circ$  apart in phase, ( $Z = \sqrt{R^2 + (X_L - X_C)^2} = R$ ) and  $1 / 2\pi f_0 C = 2\pi f_0 L$

$$f_0 = 1 / 2\pi \sqrt{LC}$$

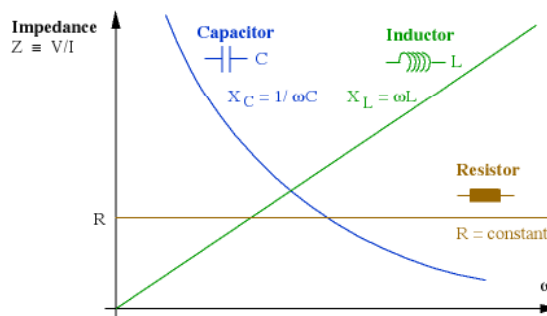


6
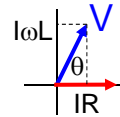
## Q-Factor and D-Factor


- Q-factor is to express the quality of component in ability to store and release energy or quality of L  
 $\rightarrow L+R$ ,

$$\begin{aligned} Q &= \text{Energy Stored} / \text{Power Loss} \\ &= \text{Reactance} / \text{Resistance} \\ &= \omega L / R \\ &= \tan \theta \end{aligned}$$



- D-factor is for a dissipation of C  $\rightarrow C + R$ ,
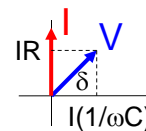
$$\begin{aligned} D &= 1/Q \\ &= \text{Power Loss} / \text{Energy Stored} \\ &= R / (1/\omega C) \\ &= \omega RC \\ &= \tan \delta \end{aligned}$$



7


## Capacitor Model

- An ideal capacitor stores but does not dissipate energy.




- Because the dielectric separating the capacitor plates are not a perfect insulator, it causes a small leakage current flowing through the capacitors  $\rightarrow$  parallel model.

$$D = V^2/R / V^2/X_C = 1/\omega RC$$

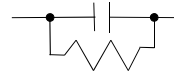

- Plate loss due to the resistances of the plates and leads can become quite significant in higher frequency case  $\rightarrow$  series model.

$$D = I^2 R / I^2 X_C = \omega RC$$

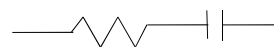


8

## Inductor Model

- An ideal inductor stores but does not dissipate energy.
- Time-varying current in a ferromagnetic inductor, which causes a time-varying magnetic field in its core, causes energy losses in the core material that are dissipated as heat → parallel model.

$$Q = V^2/X_L / V^2/R = R/\omega L$$

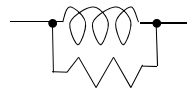


- Resistance of the wire → series model.

$$Q = I^2 X_L / I^2 R = \omega L/R$$



9

## AC Bridge

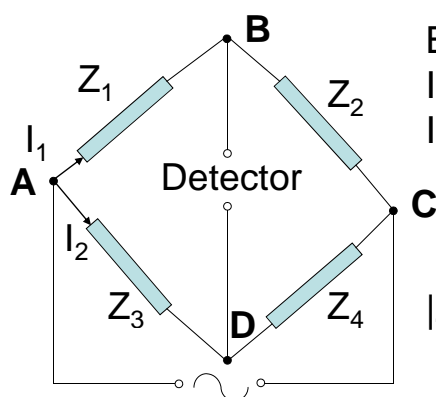

Wheatstone Bridge

Balanced Bridge,

$$I_1 |Z_1| / \phi_1 = I_2 |Z_3| / \phi_3$$

$$I_1 |Z_2| / \phi_2 = I_2 |Z_4| / \phi_4$$

$$|Z_1|/|Z_2| / \phi_1 - \phi_2 = |Z_3|/|Z_4| / \phi_3 - \phi_4$$


$$\frac{R_1 + jX_1}{R_2 + jX_2} = \frac{R_3 + jX_3}{R_4 + jX_4}$$

10
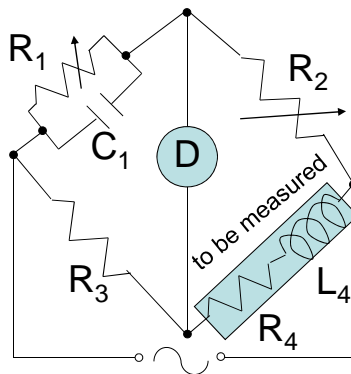
## Inductance Measurement

There is no pure components, e.g. an inductor can be considered to be a pure inductance ( $L_4$ ) in series with a pure resistance ( $R_4$ ).

Maxwell-Wien Bridge (for medium  $Q = 1-10$ )



Impedances,

$$1/Z_1 = 1/R_1 + 1/(1/j\omega C_1)$$

$$Z_1 = R_1 / (1 + j\omega R_1 C_1)$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + j\omega L_4$$

11

## Maxwell-Wien Bridge (Cont'd)

Balanced bridge,

$$Z_1 / Z_2 = Z_3 / Z_4$$

$$Z_4 = Z_2 Z_3 / Z_1$$

$$\begin{aligned} R_4 + j\omega L_4 &= R_2 R_3 (1 + j\omega R_1 C_1) / R_1 \\ &= R_2 R_3 / R_1 + j\omega R_2 R_3 C_1 \end{aligned}$$

Real part:  $R_4 = R_2 R_3 / R_1$

Imagination part:  $L_4 = R_2 R_3 C_1$

The balancing is independent of frequency.


Adjust  $R_1$  and  $R_2$  to get the bridge balanced (Null)

$$Q = \omega L_4 / R_4 = \omega (R_2 R_3 C_1) / (R_2 R_3 / R_1) = \omega R_1 C_1$$

12

# Hay Bridge

For high  $Q \geq 10$

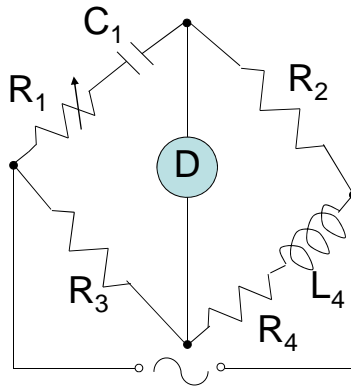

Impedances,

$$Z_1 = R_1 + 1/j\omega C_1 \\ = R_1 - j/\omega C_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + j\omega L_4$$

13

## Hay Bridge (Cont'd)

Balanced bridge,

$$Z_4 = Z_2 Z_3 / Z_1$$

$$R_4 + j\omega L_4 = R_2 R_3 / (R_1 - j/\omega C_1)$$

$$(R_1 R_4 + L_4 / C_1) + j (\omega R_1 L_4 - R_4 / \omega C_1) = R_2 R_3$$

Imagination part:  $\omega R_1 L_4 = R_4 / \omega C_1$

$$L_4 = R_4 / \omega^2 R_1 C_1$$

Real part:  $R_1 R_4 + L_4 / C_1 = R_2 R_3$

$$R_1 R_4 + R_4 / \omega^2 R_1 C_1^2 = R_2 R_3$$

$$R_4 (R_1 + 1/\omega^2 R_1 C_1^2) = R_2 R_3$$

$$R_4 (\omega^2 R_1^2 C_1^2 + 1) / (\omega^2 R_1 C_1^2) = R_2 R_3$$

$$R_4 = (\omega^2 R_1 R_2 R_3 C_1^2) / (\omega^2 R_1^2 C_1^2 + 1)$$

$$L_4 = (R_2 R_3 C_1) / (\omega^2 R_1^2 C_1^2 + 1)$$

14

## Hay Bridge (Cont'd)

$$Q = \omega L_4 / R_4$$


$$= 1 / \omega R_1 C_1$$

Therefore,  $L_4 = (R_2 R_3 C_1) / ( (1/Q^2) + 1 )$

$$\approx R_2 R_3 C_1 \quad \text{if } Q \geq 10$$

15

## Owen Bridge

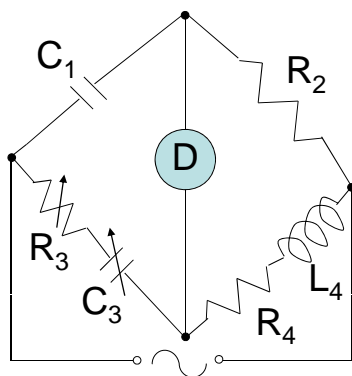

Impedances,

$$Z_1 = 1/j\omega C_1$$

$$Z_2 = R_2$$

$$Z_3 = R_3 - j/\omega C_3$$

$$Z_4 = R_4 + j\omega L_4$$

16



## Owen Bridge (Cont'd)

Balanced bridge,

$$Z_4 = Z_2 Z_3 / Z_1$$

$$\begin{aligned} R_4 + j\omega L_4 &= R_2 (R_3 - j/\omega C_3) j\omega C_1 \\ &= R_2 C_1 / C_3 + j\omega R_2 R_3 C_1 \end{aligned}$$

Real part:  $R_4 = R_2 C_1 / C_3$

Imagination part:  $L_4 = R_2 R_3 C_1$

The balancing is independent of frequency.

$$Q = \omega L_4 / R_4 = \omega R_2 R_3 C_1 C_3 / R_2 C_1 = \omega R_3 C_3$$

17

## References

- Electronics Demonstrations webpage:  
<http://www.falstad.com/circuit/e-index.html>

18