

# Bridge Method




EIE 240 Electrical and Electronic Measurement (2/2011)  
Class 8, February 2, 2012

Werapon Chiracharit  
werapon.chi@kmutt.ac.th

1
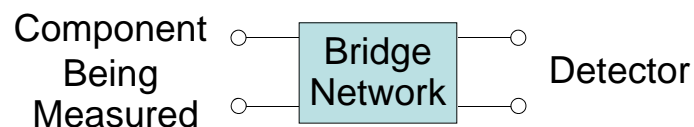
# Bridge Method


- Diode bridge is an arrangement of four or more diodes for AD/DC full-wave rectifier.
- Component bridge methods are used for measurement of resistance, capacitance, inductance, etc.
- The network will be balanced when the detector reading becomes zero.



2
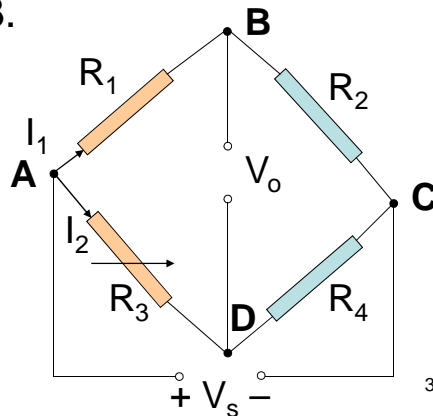
# Wheatstone Bridge

- Wheatstone bridge was invented by Samuel Hunter Christie in 1833 and improved and popularized by Sir Charles Wheatstone in 1843.
- DC supply,  $V_s$
- Output voltage,  $V_o$



## Wheatstone Bridge (Cont'd)

- When  $V_o = 0$  V, the potential at B must equal to the potential at D

$$I_1 R_1 = I_2 R_3$$

$$I_1 R_2 = I_2 R_4$$


$$\text{Hence } I_1 R_1 = I_2 R_3 = (I_1 R_2 / R_4) R_3$$

$$R_1 / R_2 = R_3 / R_4$$

- The balance condition is independent of  $V_s$
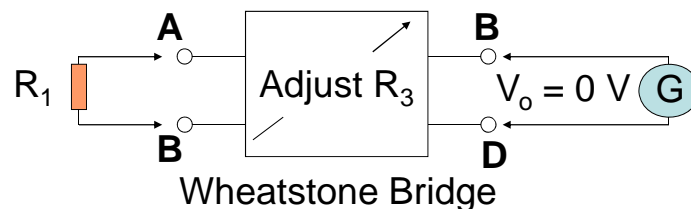
## Wheatstone Bridge (Cont'd)

- $R_1$  is the input resistance to be measured by comparing to accurately known resistors (standard).
- $R_2$  and  $R_4$  are known-fixed resistances.
- $R_3$  can be adjusted to give the zero potential difference condition.



5

## Wheatstone Bridge (Cont'd)

- Change in  $R_1$ , change  $R_3$
- The precision is about  $1\ \Omega$  to  $1\ \text{M}\Omega$ .
- The accuracy is mainly up to the known resistors and the sensitivity of the null detector ( $\pm 0.1$  to  $0.2\%$ ).
- Error comes from changes in resistances of the bridge arms by changes in temperatures or thermoelectric EMF in contacts.

6

## Sensitivity of the Bridge

- If no galvanometer at the output,

$$V_{AB} = V_s R_1 / (R_1 + R_2)$$

$$V_{AD} = V_s R_3 / (R_3 + R_4)$$

Thus,  $V_o = V_{AB} - V_{AD}$

$$V_o = V_s ( R_1 / (R_1 + R_2) - R_3 / (R_3 + R_4) )$$

- The relationship between  $V_o$  and  $R_1$  is non-linear
- $V_o = 0$  V when  $R_1/R_2 = R_3/R_4$

7

## Sensitivity of the Bridge (Cont'd)

- Changing  $R_1$  to  $R_1 + \Delta R_1$  gives a change of  $V_o$  to  $V_o + \Delta V_o$

$$V_o + \Delta V_o = V_s ((R_1 + \Delta R_1) / ((R_1 + \Delta R_1) + R_2) - R_3 / (R_3 + R_4))$$

$$\begin{aligned} \text{Then } (V_o + \Delta V_o) - V_o &= V_s \left( \frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) \\ &\quad - V_s \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) \\ \Delta V_o &= V_s \left( \frac{R_1 + \Delta R_1}{R_1 + \Delta R_1 + R_2} - \frac{R_1}{R_1 + R_2} \right) \end{aligned} \quad 8$$

## Sensitivity of the Bridge (Cont'd)

- If small changes  $\Delta R_1 \ll R_1$  then the sensitivity of Wheatstone bridge can be computed from,

$$\Delta V_o \approx \Delta R_1 V_s / (R_1 + R_2)$$
$$\Delta V_o / \Delta R_1 \approx V_s / (R_1 + R_2)$$

- Higher  $R_1$  to be measured, lower sensitivity
- Amplifier can be used to amplify  $V_o$

9

## Unbalanced Bridge

- If there is a galvanometer,  $R_g$ , between the two output terminals, the current  $I_g$  can be determined by Thévenin equivalent circuit.


$$V_{th} = V_o = V_s ( R_1 / (R_1 + R_2) - R_3 / (R_3 + R_4) )$$

- Short voltage source, then Thévenin resistance is  $R_1 // R_2 + R_3 // R_4$

$$R_{th} = R_1 R_2 / (R_1 + R_2) + R_3 R_4 / (R_3 + R_4)$$

10

## Unbalanced Bridge (Cont'd)

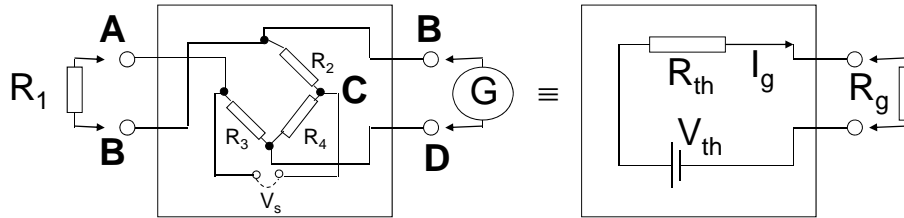

For unbalanced bridge,

$$I_g = V_{th} / (R_{th} + R_g)$$

and


$$\begin{aligned} V_g &= I_g R_g \\ &= V_{th} R_g / (R_{th} + R_g) \end{aligned}$$

If balanced or  $V_g = 0$  V  $\Rightarrow$  like no movement

11
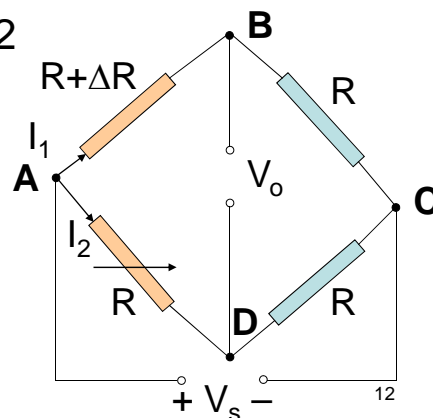
## Slightly Unbalanced Bridge

- If  $R_2 = R_3 = R_4 = R$  and  $R_1 = R + \Delta R$
- $V_{AB} = V_s (R + \Delta R) / (R + \Delta R + R)$   
 $= V_s (R + \Delta R) / (2R + \Delta R)$
- $V_{AD} = V_s R / (R + R) = V_s / 2$
- $V_o = V_{AB} - V_{AD}$   
 $= V_s \left( \frac{(R + \Delta R)}{(2R + \Delta R)} - \frac{1}{2} \right)$   
 $= V_s \Delta R / (4R + 2\Delta R)$
- If  $\Delta R < 5\%$  of  $R$   
 $V_o \approx V_s \Delta R / 4R$



## Slightly Unbalanced Bridge (Cont'd)

- For Thévenin's equivalent circuit,

$$\begin{aligned} V_{th} &= V_o \\ &= V_s \Delta R / 4R \end{aligned}$$


$$\begin{aligned} R_{th} &= (R + \Delta R) // R + R // R \\ &= R(R + \Delta R) / (2R + \Delta R) + R/2 \\ &\approx R/2 + R/2 = R \end{aligned}$$

$$\begin{aligned} I_g &= V_{th} / (R_{th} + R_g) \\ V_g &= I_g R_g \end{aligned}$$

13

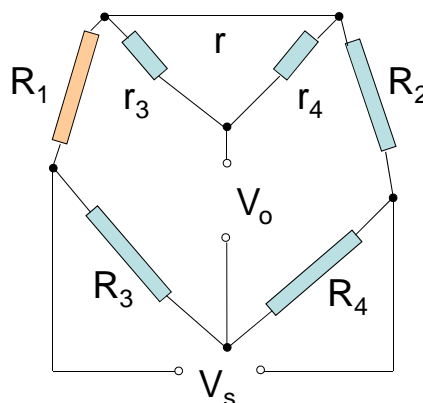
## Kelvin Double Bridge

- A modification of Wheatstone bridge for low resistance measurement ( $R_1 < 1\Omega$ )
- Because non-perfect wire resistances affect the measurement.



14

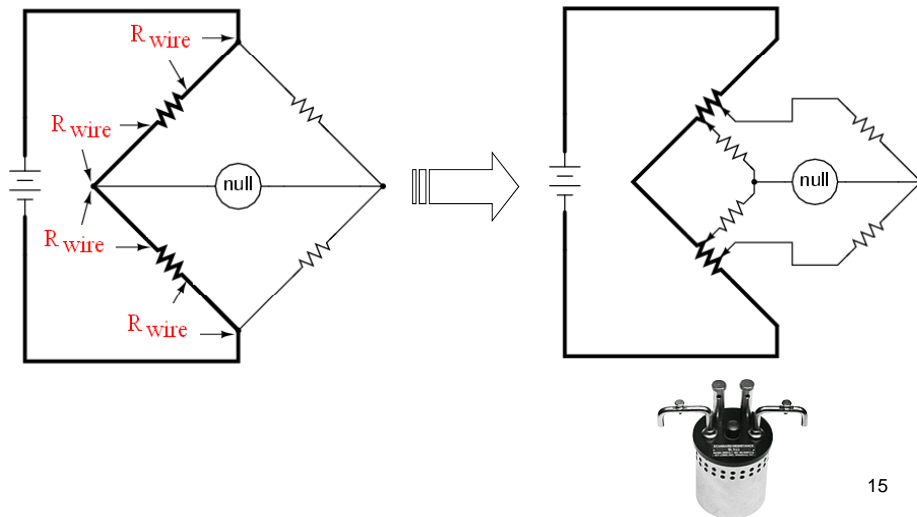- Using four-terminal resistors (two for voltage supply and 2 for current supply)




15

- The yoke  $r$  is connected to  $R_1$  and  $R_2$
- The relationship between  $r_3$ ,  $r_4$ ,  $R_3$  and  $R_4$

$$R_3/R_4 = r_3/r_4$$

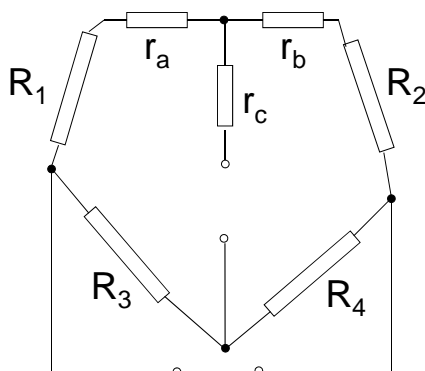- Using the delta-star transformation, the equivalent circuit



$$r_a = r_3 r / (r_3 + r_4 + r)$$

$$r_b = r_4 r / (r_3 + r_4 + r)$$

16




## Note

- $\Delta$ -Y Transformation

$$R_a = R_1 R_2 / (R_1 + R_2 + R_3)$$

$$R_b = R_2 R_3 / (R_1 + R_2 + R_3)$$

$$R_c = R_1 R_3 / (R_1 + R_2 + R_3)$$

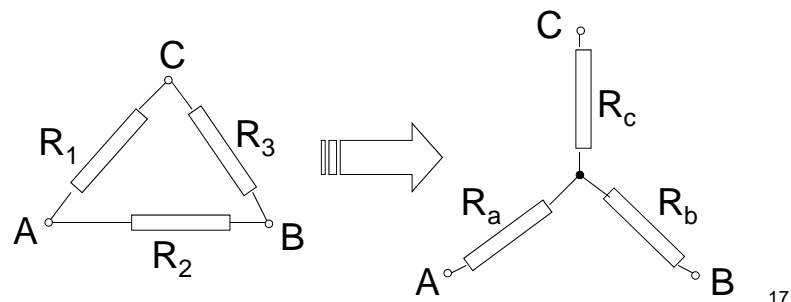

17

- The balance condition is the same as Wheatstone bridge (Null  $V_o = 0$  V)

$$(R_1 + r_a) / (R_2 + r_b) = R_3 / R_4$$

$$\begin{aligned} R_1 &= R_3(R_2 + r_b) / R_4 - r_a \\ &= R_3 R_2 / R_4 + R_3 r_b / R_4 - r_a \\ &= R_3 R_2 / R_4 + R_3 r_4 r / (r_3 + r_4 + r) R_4 \\ &\quad - r_3 r / (r_3 + r_4 + r) \\ &= R_3 R_2 / R_4 \\ &\quad + r_4 r (R_3 / R_4 - r_3 / r_4) / (r_3 + r_4 + r) \end{aligned}$$


$$R_1 = R_3 R_2 / R_4$$

$$\text{Therefore } R_1 / R_2 = R_3 / R_4 = r_3 / r_4$$

18
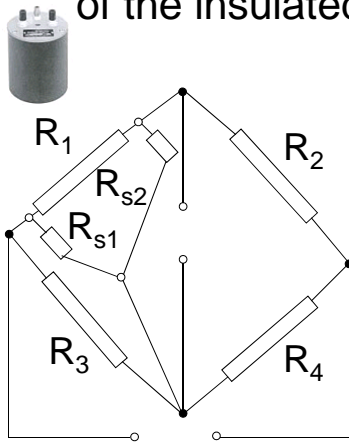
## High Resistance Bridge

- For very high resistance, e.g. 1,000 M $\Omega$ , there is leakage currents over the surface of the insulated post.



- Using three-terminal resistors (parallel with 2 leakage resistances)
- $R_{s1} \gg R_3$  and  $R_{s1} // R_3$  to avoid the leakage effect
- $R_{s2}$  may affect the detector sensitivity

19


## Bridge Compensation

- The resistance of long leads will be affected by changes in temperatures
- To avoid this, 3 leads are required to connect to the coils
- They are all the same length and resistance

20
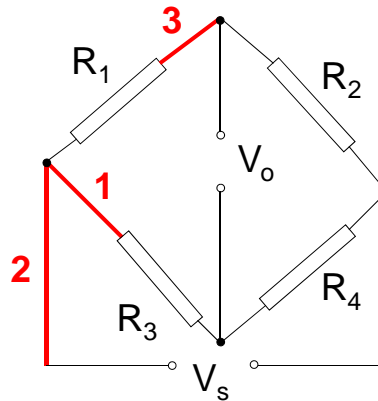
## Bridge Compensation (Cont'd)

- Any changes in lead resistance will affect all 3 leads equally and occur in 2 arms of bridge and will cancel out.



21

## Bridge Controlled Circuits

- The bridge can be used as an error detector in a control circuit, using the potential difference at the output of the bridge that is sensitive to any physical parameters.
- Passive circuit elements such as strain gauges, temperature sensitive resistors (thermistors) or photo resistors are used as one arm of Wheatstone bridge.
- A change in the elements (pressure, heat or light) causes the bridge to be unbalanced.

22

## References

- Hotek Technologies, Inc webpage :  
<http://www.hotektech.com/>
- Yokogawa webpage:  
<http://tmi.yokogawa.com/us/>
- MAGNET LAB – Wheatstone Bridge webpage:  
<http://www.magnet.fsu.edu/education/tutorials/java/wheatstonebridge/index.html>