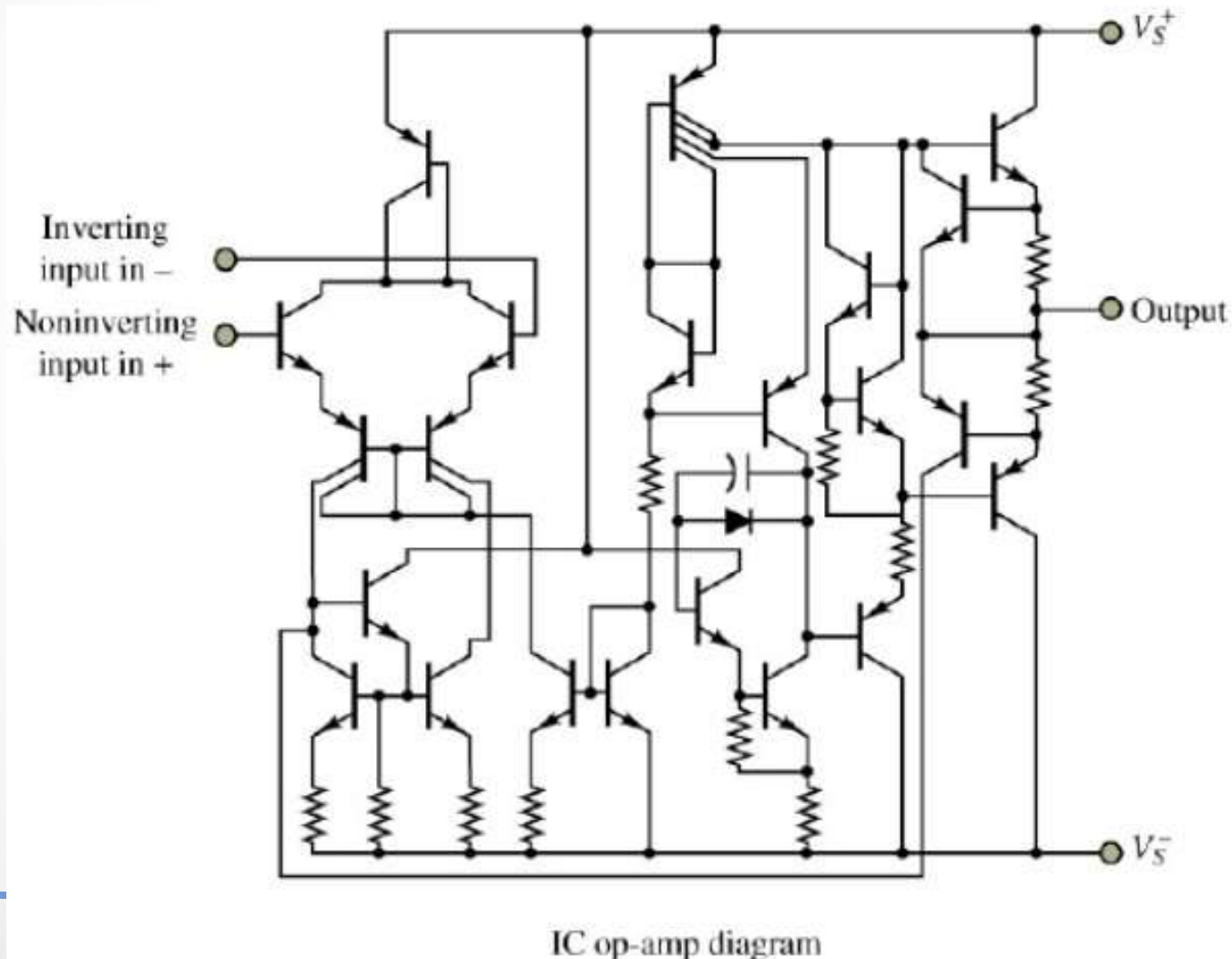


ENE/EIE 211 : Electronic Devices  
and Circuit Design II  
Lecture 5: Differential Amps


## The BJT Differential Pair

The differential pair or differential amplifier configuration is the most widely used building block in analog integrated ckt design. For instance, the input stage of every op amp is a differential amplifier. Also, the BJT differential amp is the basis of a very-high-speed logic circuit family called emitter-coupled logic (ECL).



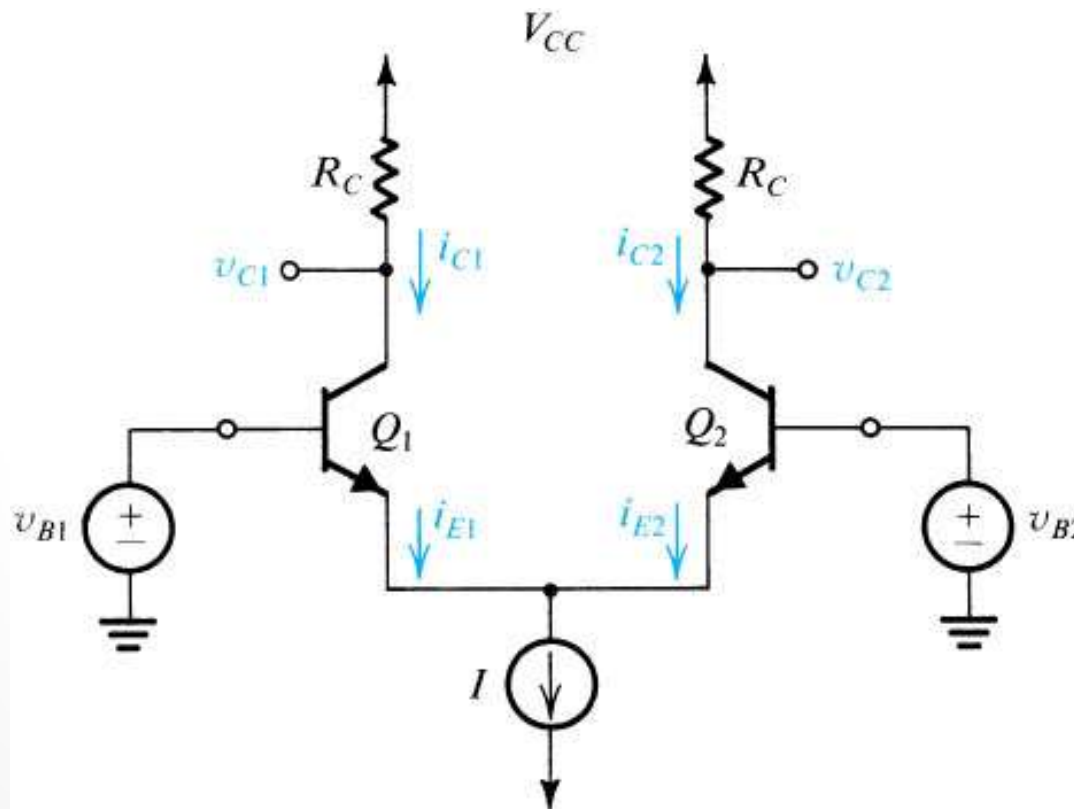
## The Configuration and the Basic Operation

It consists of two matched transistors  $Q_1$  and  $Q_2$ , whose emitter are joined together and biased by a constant-current source  $I$ . The latter is usually implemented by a transistor ckt of the type we studied previously. Sometimes the collectors of both transistors may be connected to an active loads (such as transistors) instead of a resistive load. It is essential that the collectors of both transistors never enter saturation.



## A common-mode operation

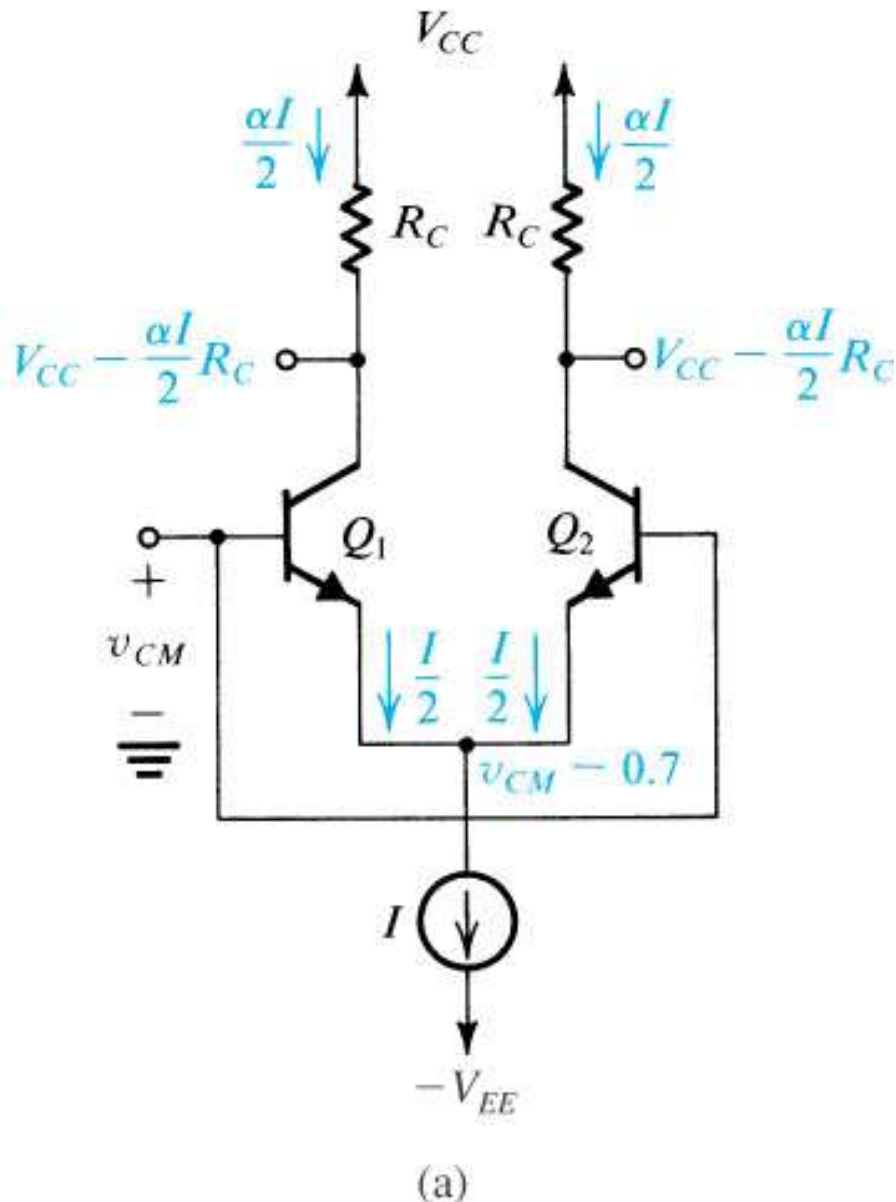


$$I_{C1} - I_{C2} = 0$$

$$V_{C1} - V_{C2} = 0$$


As long as Q1 and Q2 remain in the active region the current  $I$  will still divide equally between Q1 and Q2 and the voltages at the collectors will not change.

Thus, the differential pair does not respond (i.e. it rejects) common-mode input signals.

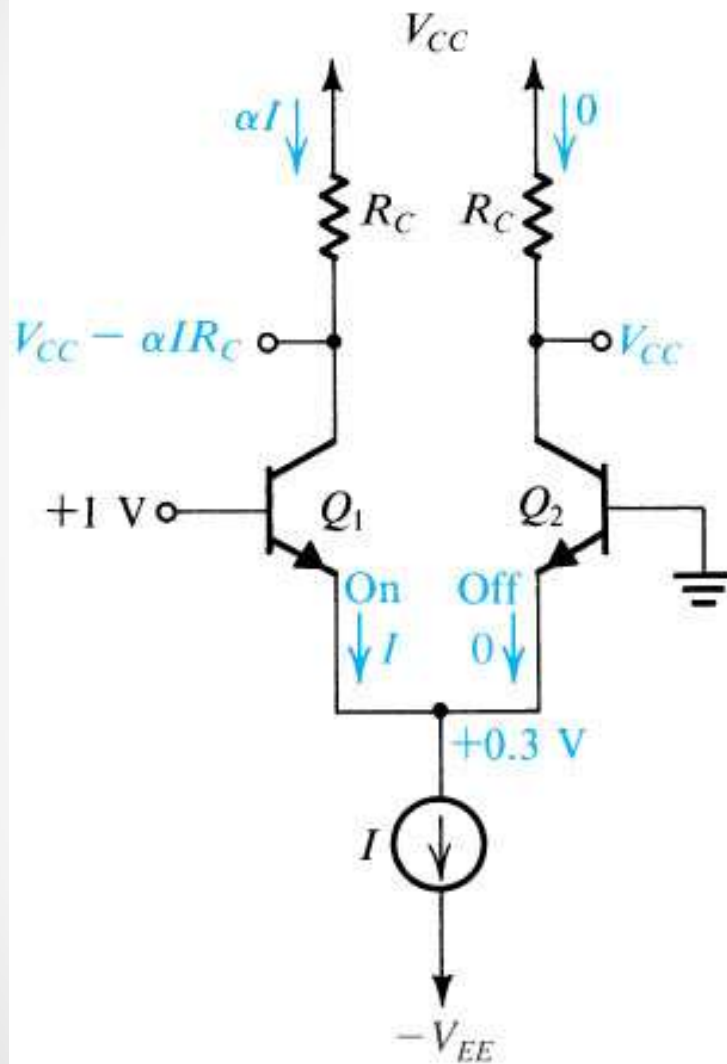**A differential-mode operation:** shows the current-steering ability




(b)

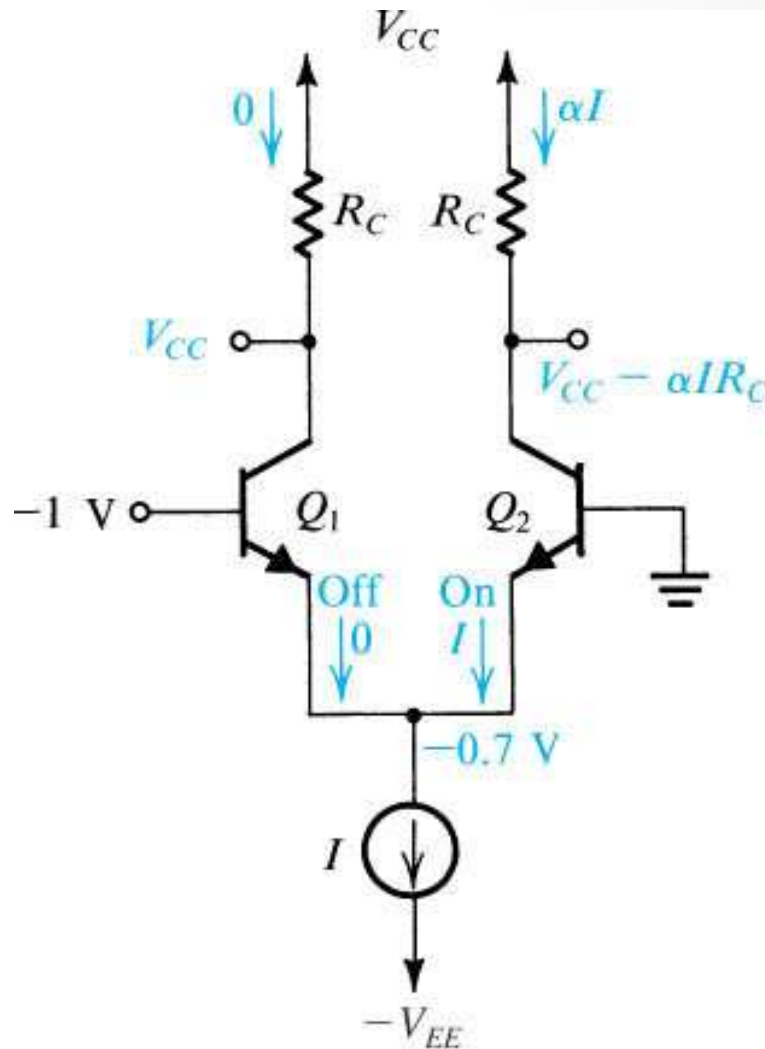

(c)

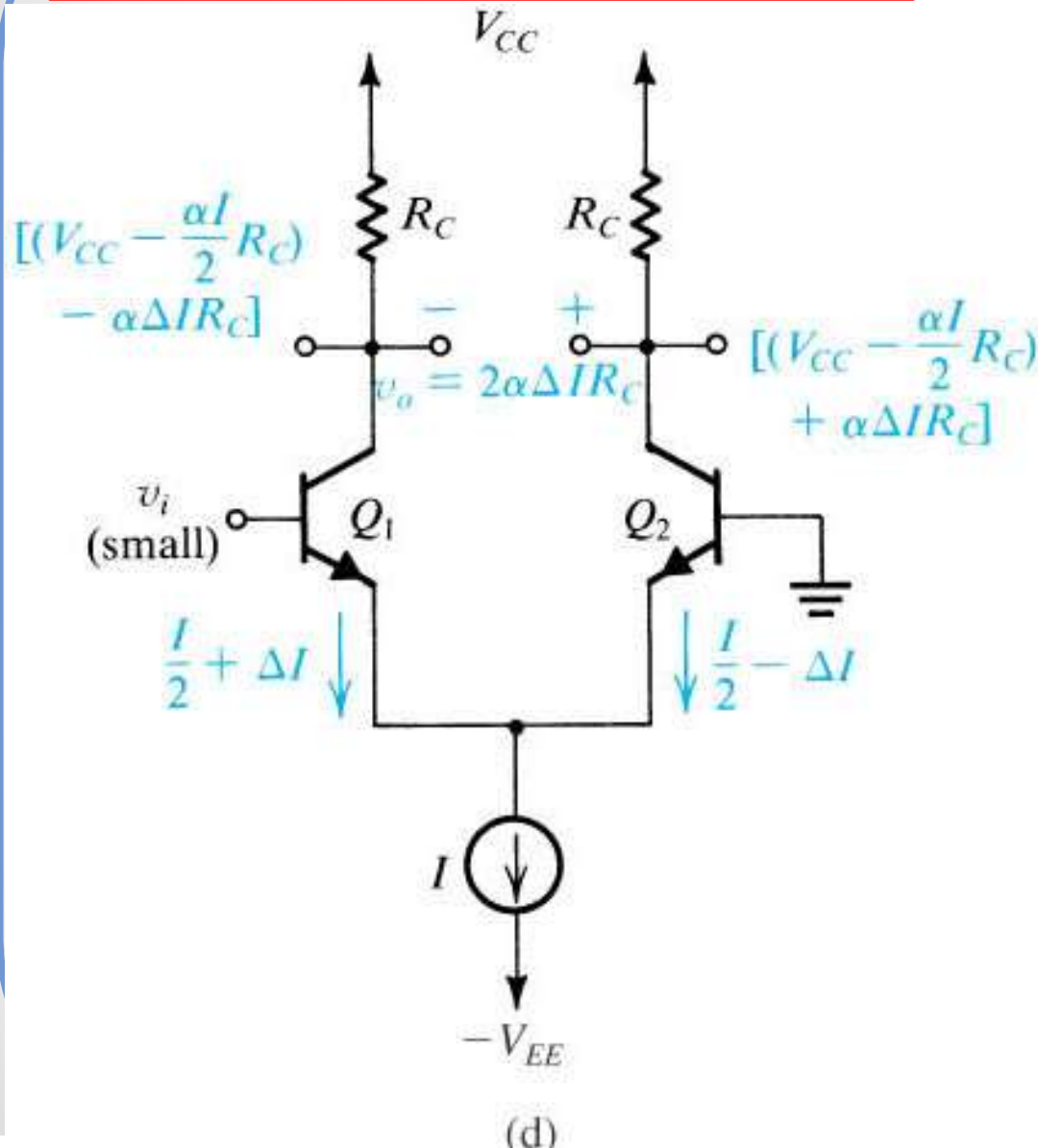
## A differential-mode operation: a general case




The differential pair responds to large differential mode signals. In fact, with relatively small difference voltages we are able to steer the entire bias current from one side of the pair to the other.




**Example:** Find  $v_E$ ,  $v_{C1}$  and  $v_{C2}$  in the ckt below. Assume that  $|v_{BE}|$  of a conducting transistor is approximately 0.7 V and that  $\alpha = 1$ .

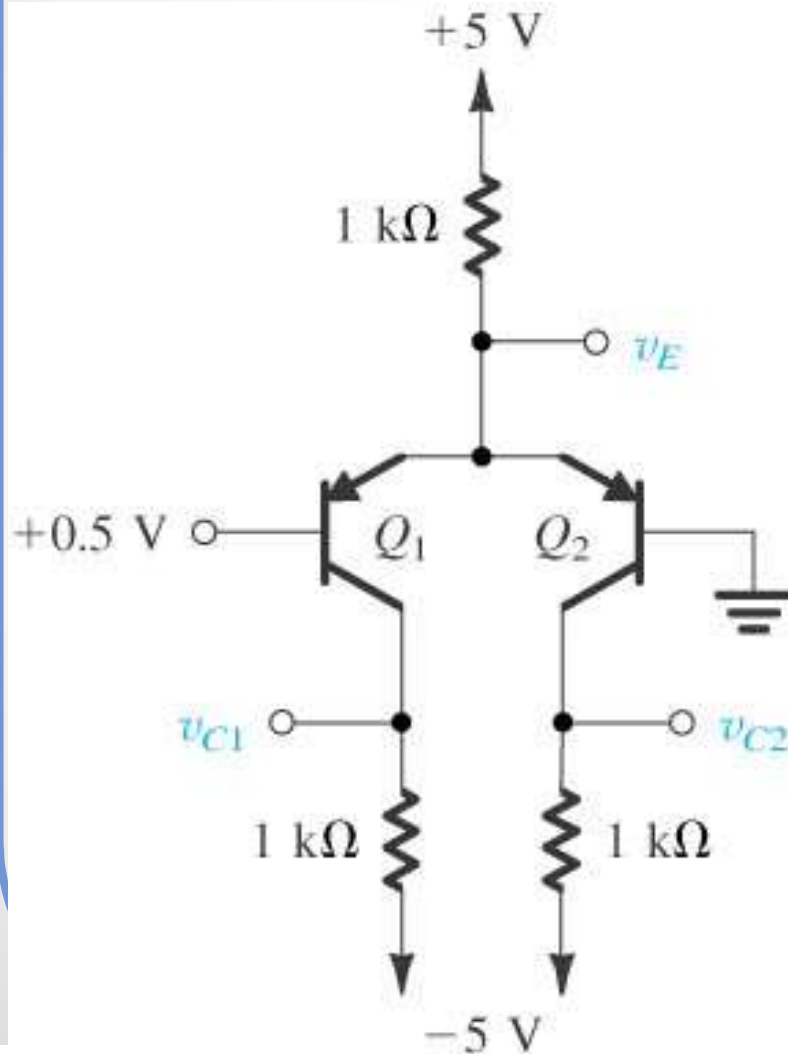



Large signal operation

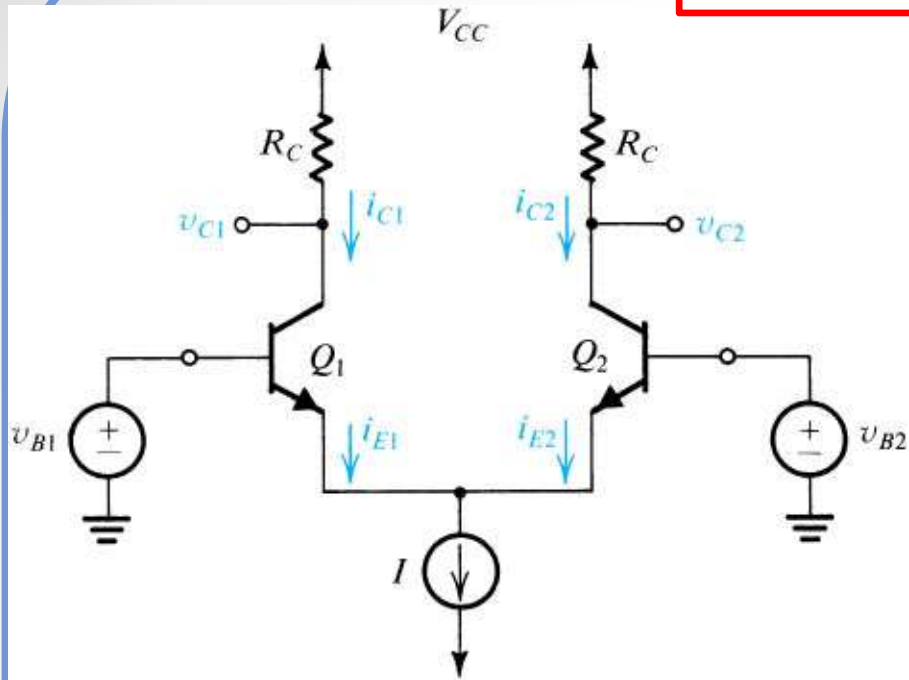



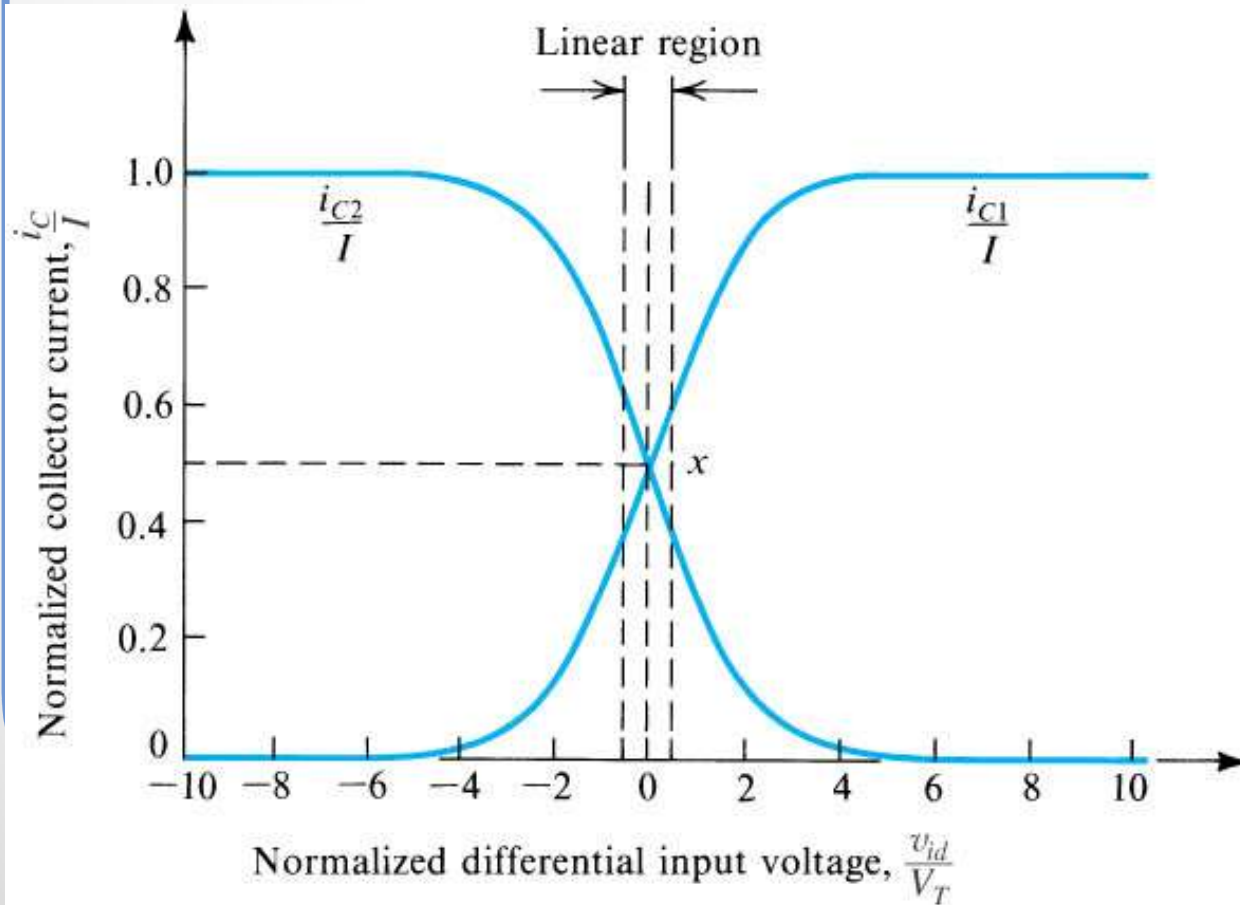


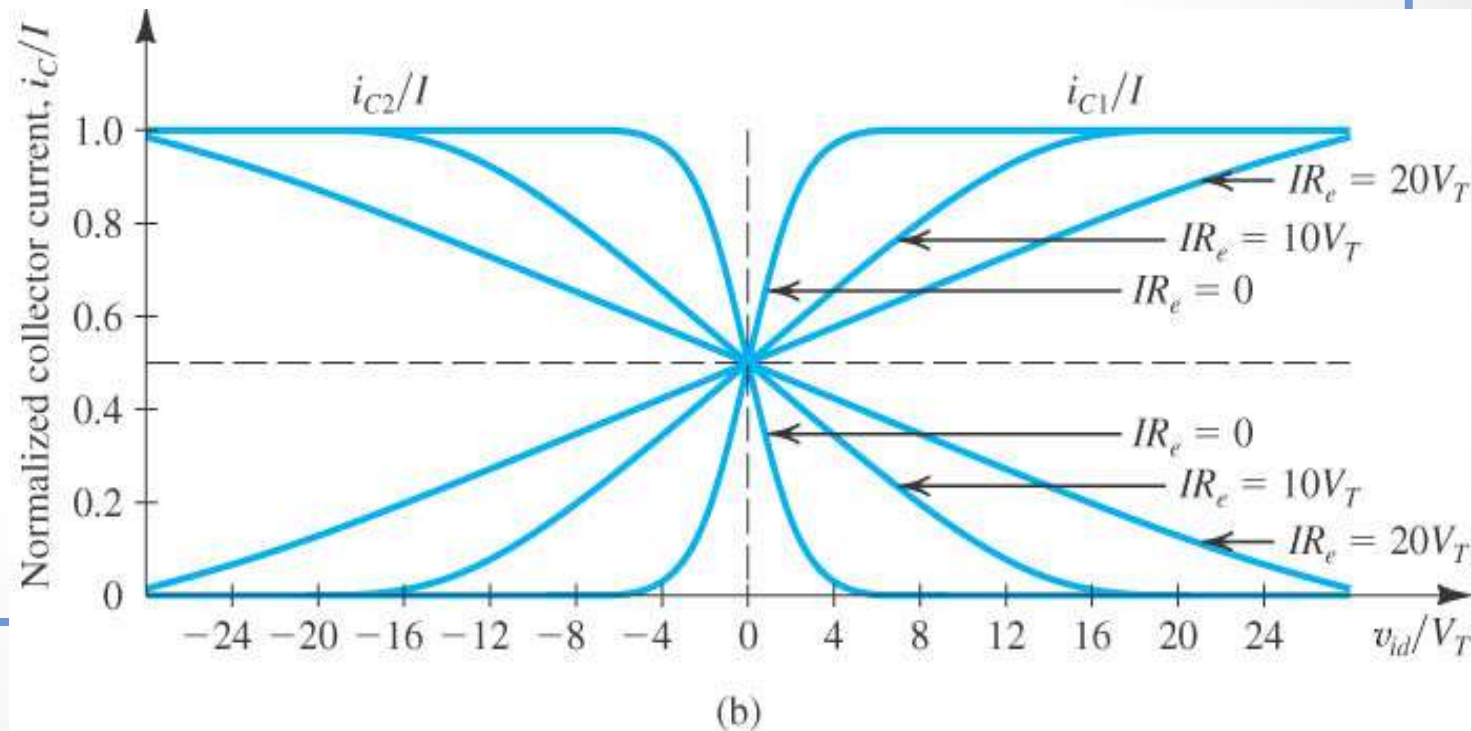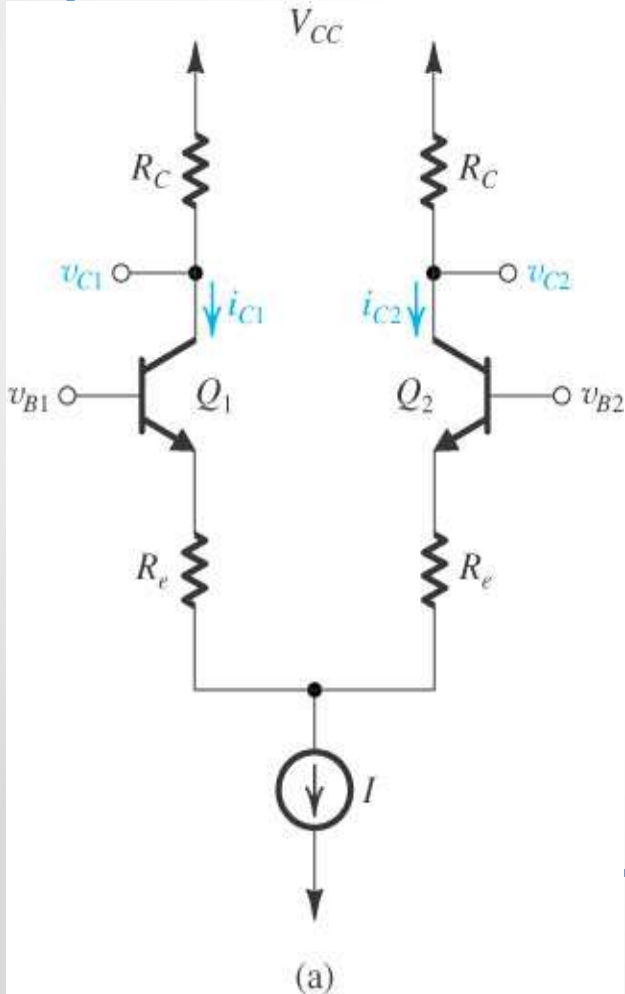Adding resistors  $R_e$  can extend the linear range of operation. But the expansion of the linear range is obtained at the expense of reduced  $g_m$  (which is the slope of the transfer curve at  $v_{id} = 0$ ) and hence reduced gain.





## Small-signal operation

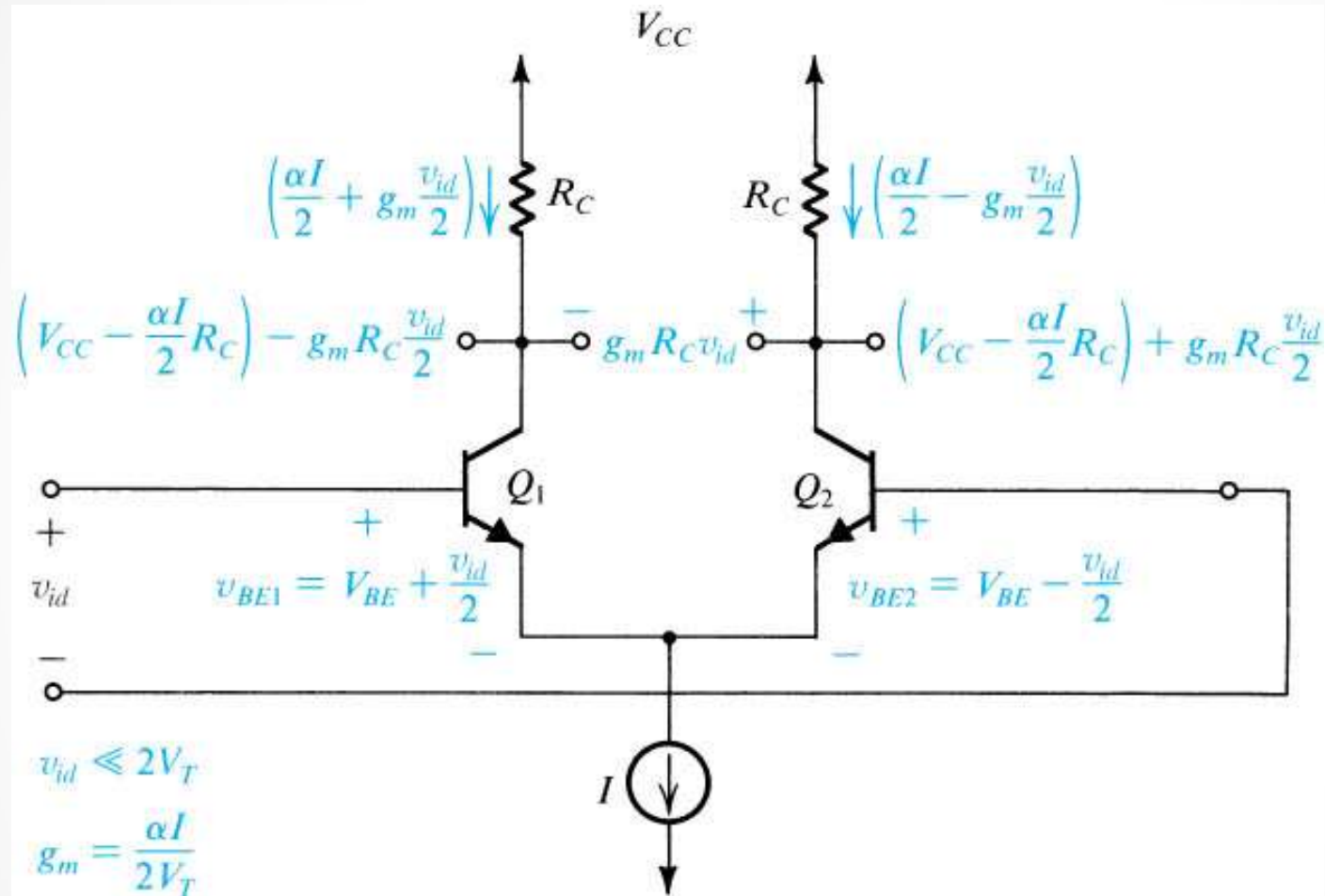


$$i_{C1} = I_{C1} + i_{c1} = \frac{\alpha I}{1 + e^{-v_{id}/V_T}} \approx \frac{\alpha I}{2} + \frac{\alpha I}{2V_T} \frac{v_{id}}{2}$$

$$i_{C2} = I_{C2} + i_{c2} = \frac{\alpha I}{1 + e^{+v_{id}/V_T}} \approx \frac{\alpha I}{2} - \frac{\alpha I}{2V_T} \frac{v_{id}}{2}$$

$$g_m = \frac{I_C}{V_T} = \frac{\alpha I / 2}{V_T}$$

## Input Resistance

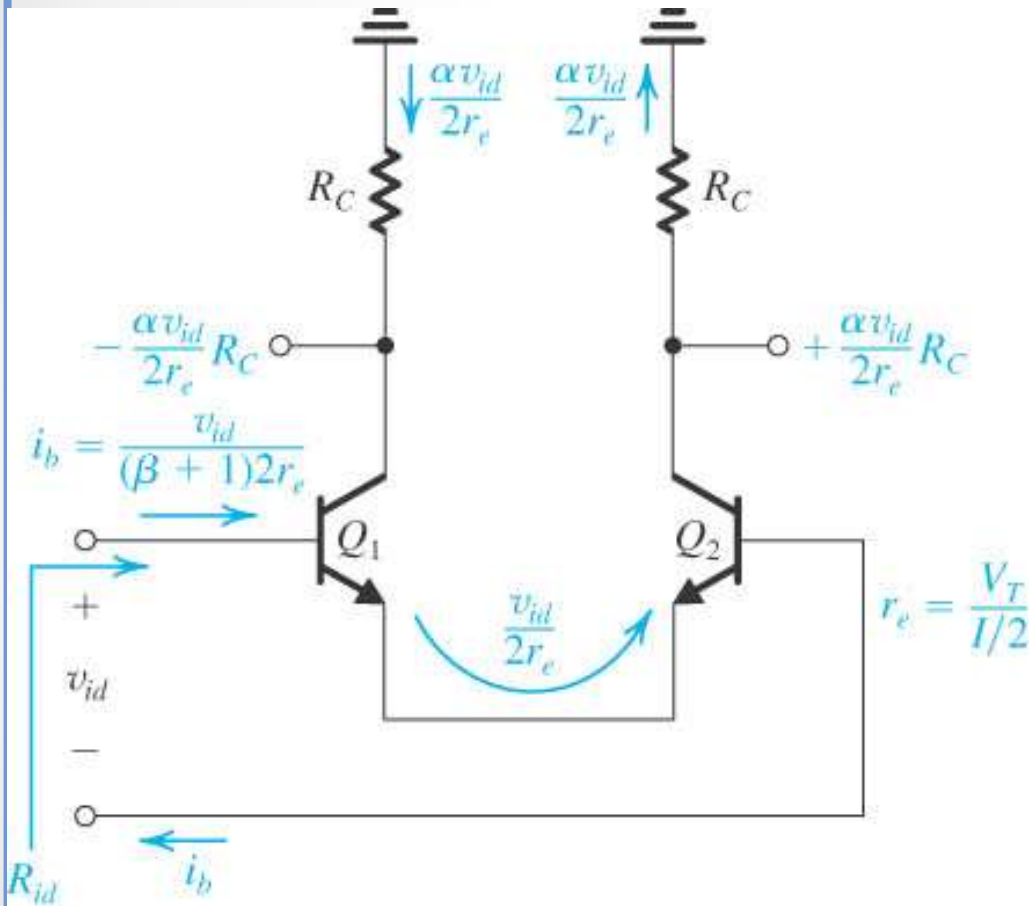


$$i_e = \frac{v_{id}}{2r_e}$$

$$i_b = \frac{i_e}{\beta + 1} = \frac{v_{id} / 2r_e}{\beta + 1}$$

$$R_{id} = \frac{v_{id}}{i_b} = (\beta + 1)2r_e = 2r_{\pi}$$

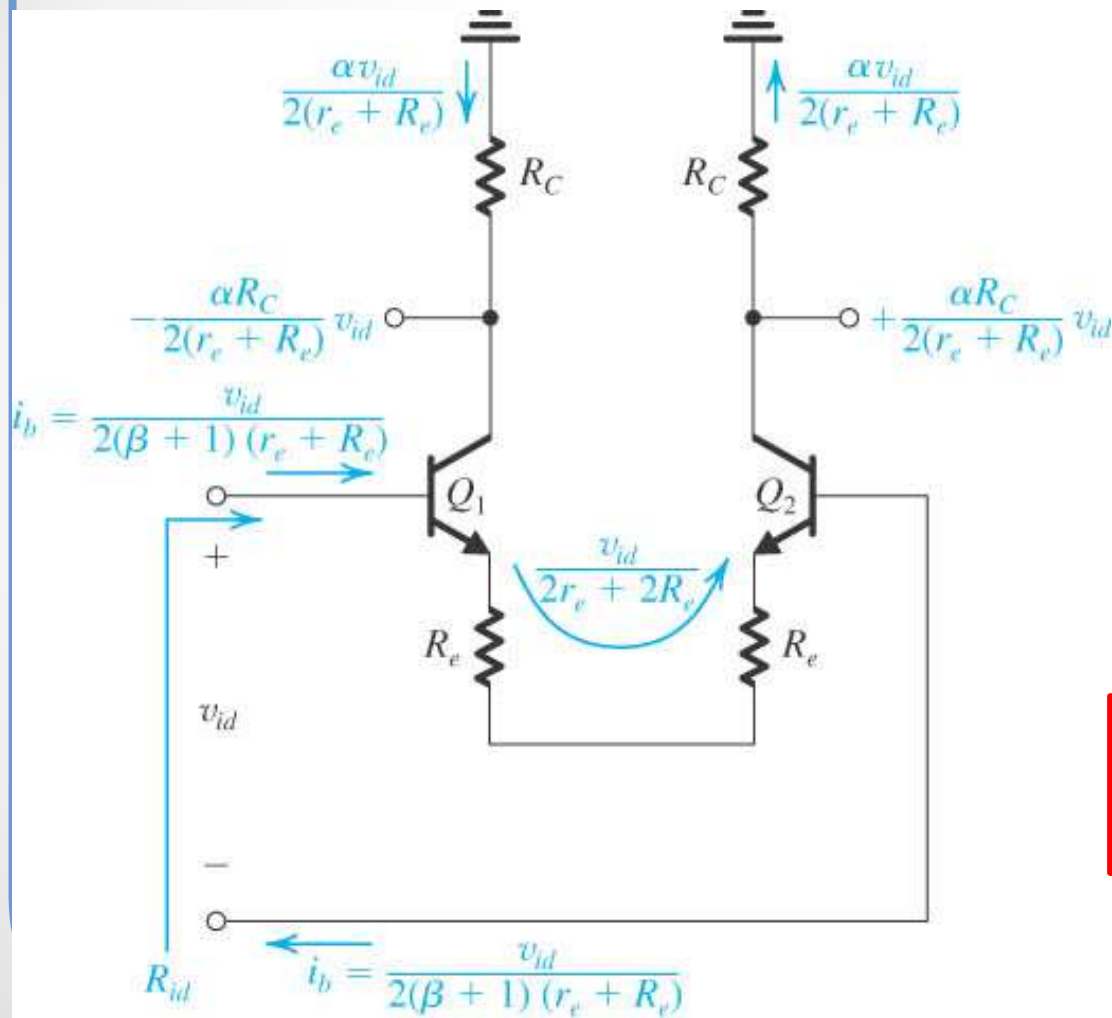
# Input resistance with resistors $R_e$ 's in the emitters



$$R_{id} = \frac{v_{id}}{i_b} = (\beta + 1)(2r_e + 2R_e)$$



## Differential Voltage Gain

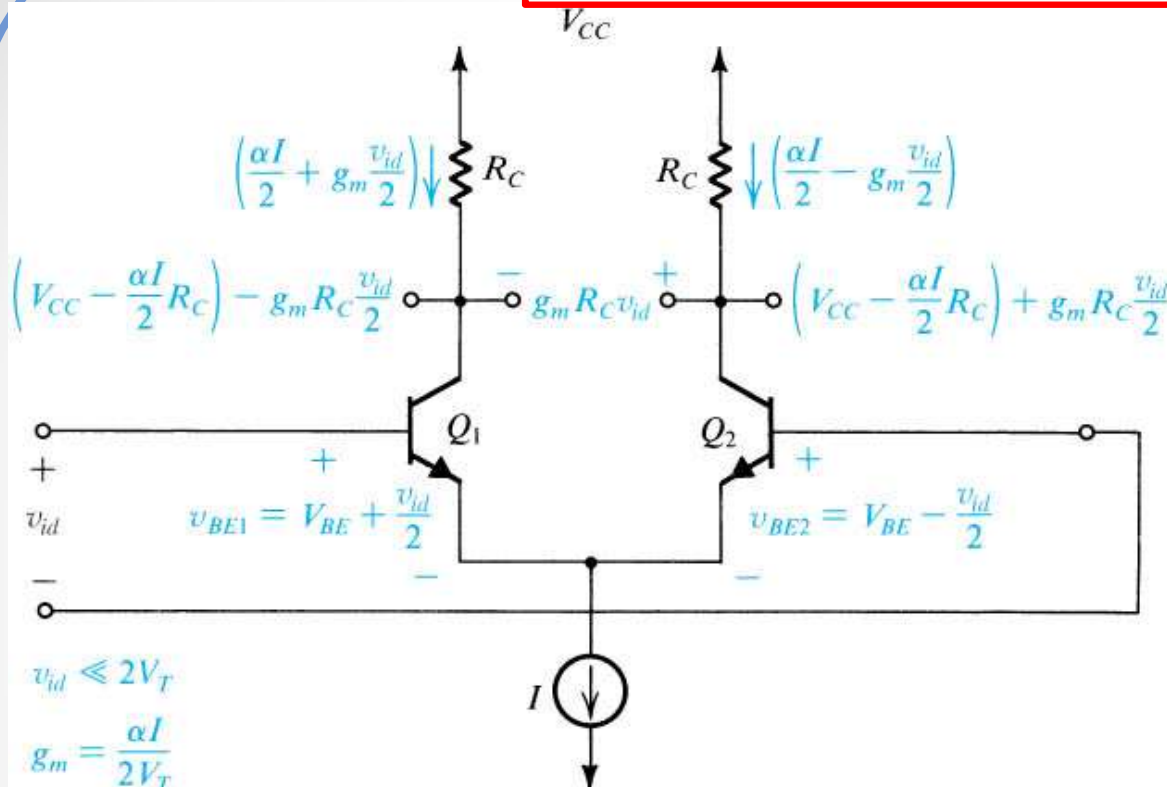

If the output is taken differentially,  $A_d = \frac{v_{c1} - v_{c2}}{v_d} = -g_m R_C$


If the output is taken single-endedly,  $A_d = \frac{v_{c1}}{v_d} = -\frac{1}{2} g_m R_C$

For the diff amp with resistances in the emitters, and the output is taken differentially,


$$A_d = -\frac{\alpha(2R_C)}{2r_e + 2R_e} = -\frac{R_C}{r_e + R_e}$$


## Equivalence of differential amp to a common-emitter amp

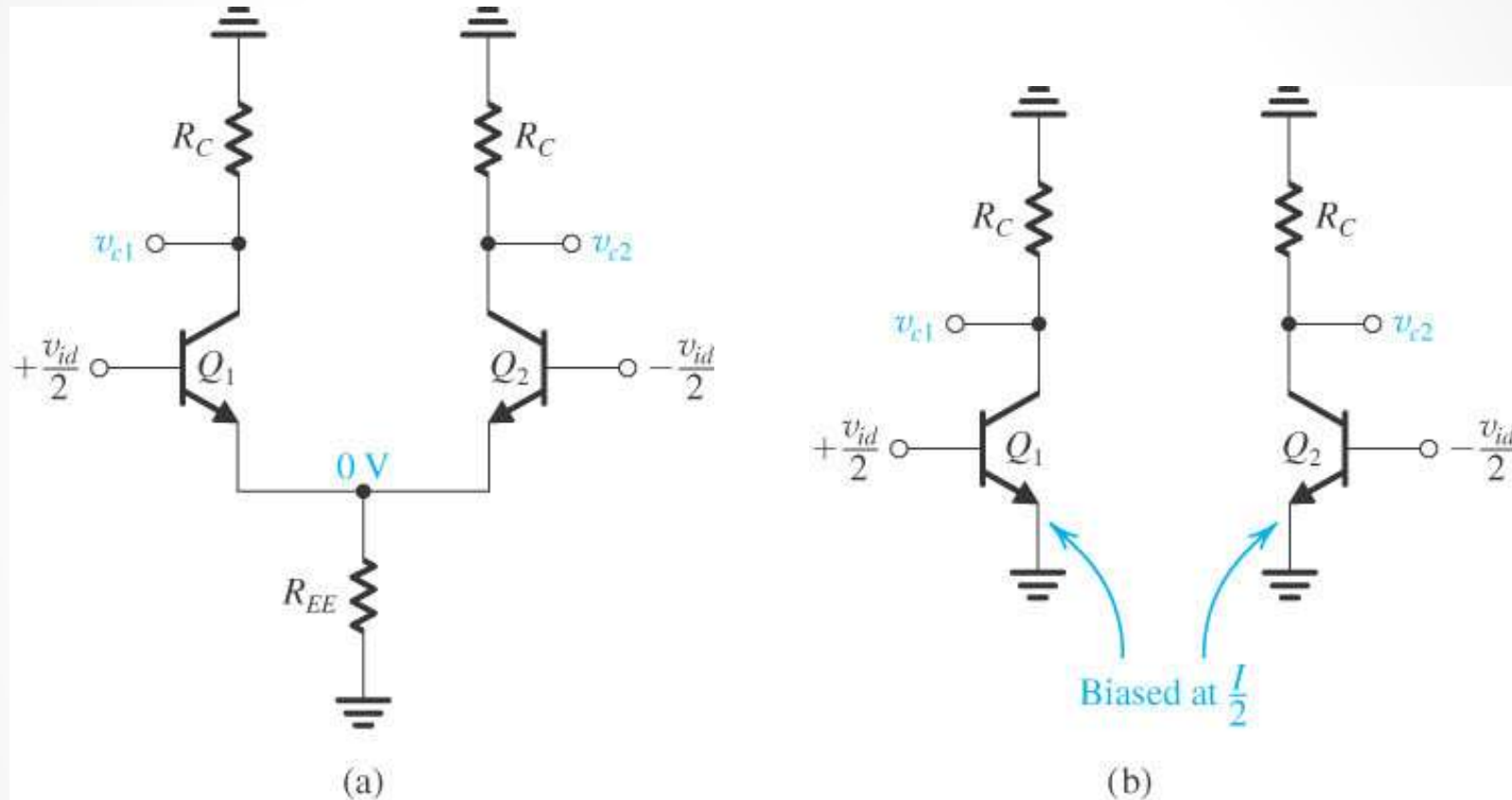1. The differential signal  $v_{id}$  is applied in a complementary (or balanced) manner.



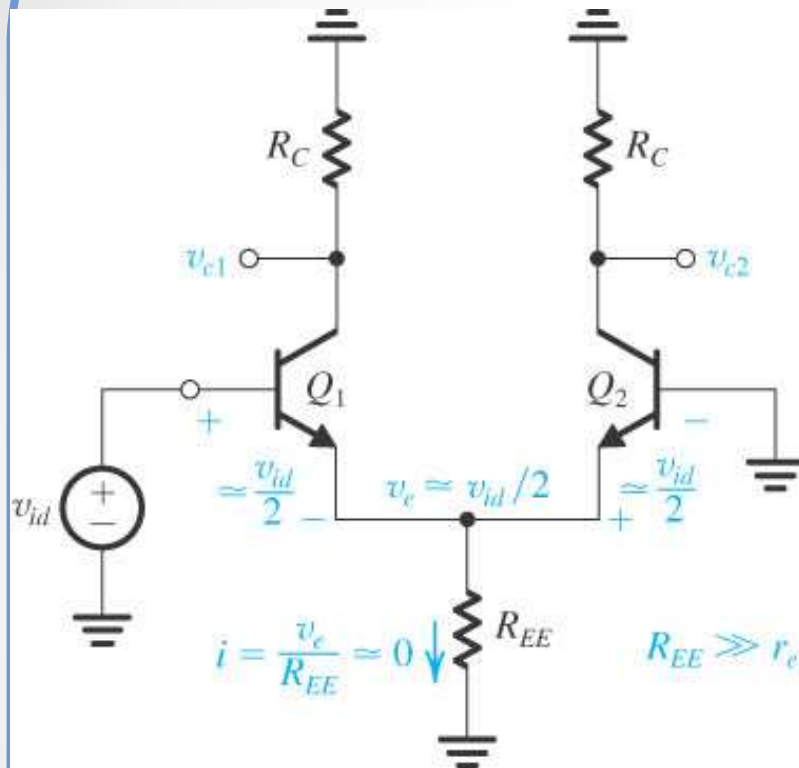2. The differential signal  $v_{id}$  is applied in a single-ended manner.



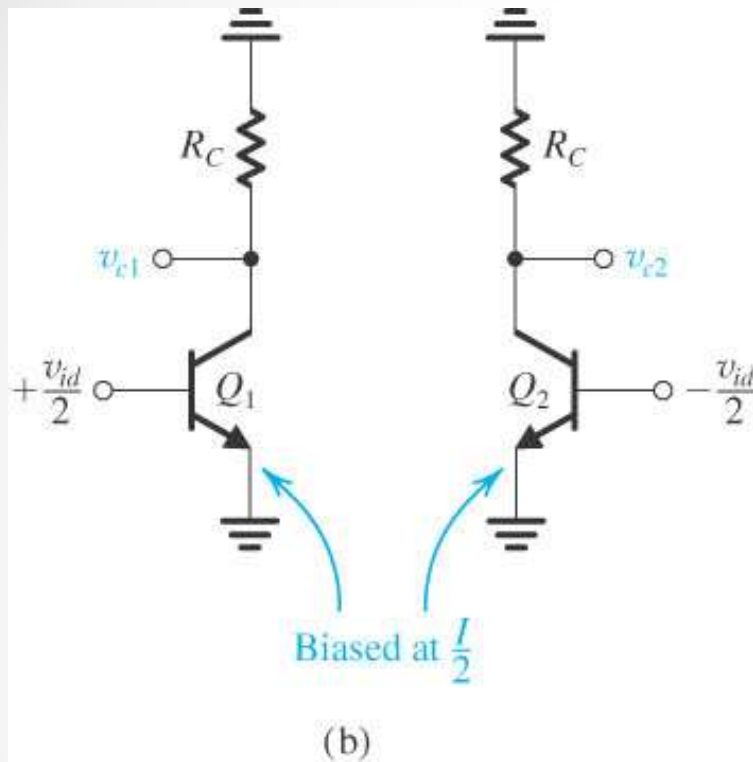


Since  $v_{C2} = -v_{C1}$ , the two common-emitter transistors yield similar results about the performance of the diff amp. Thus, only one is needed to analyze the differential small-signal operation of the amp, and it is known as **the differential half-circuit**.

Its low-freq equivalent model is shown below. Keep in mind, the bias current is at  $I/2$  for each of the halves.



When output is taken differentially, the gain is given by

$$A_d = -g_m(R_C \parallel r_o)$$

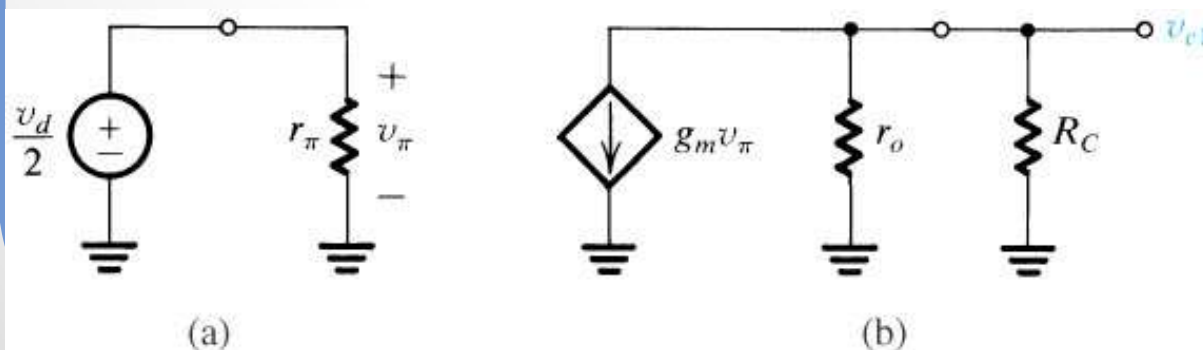

- The voltage gain of the diff amp ( when the output is taken differentially) is equal to the voltage gain of the half-circuit. - The input differential resistance is twice of the half-circuit, that is  $2r_e$ .

## Common-mode gain and CMRR

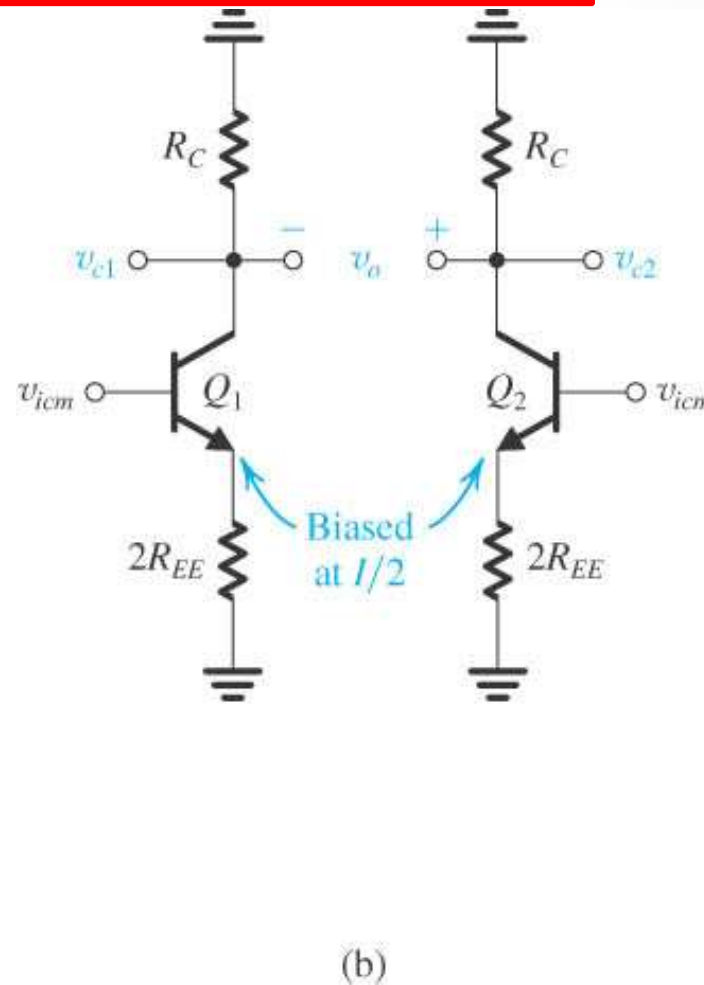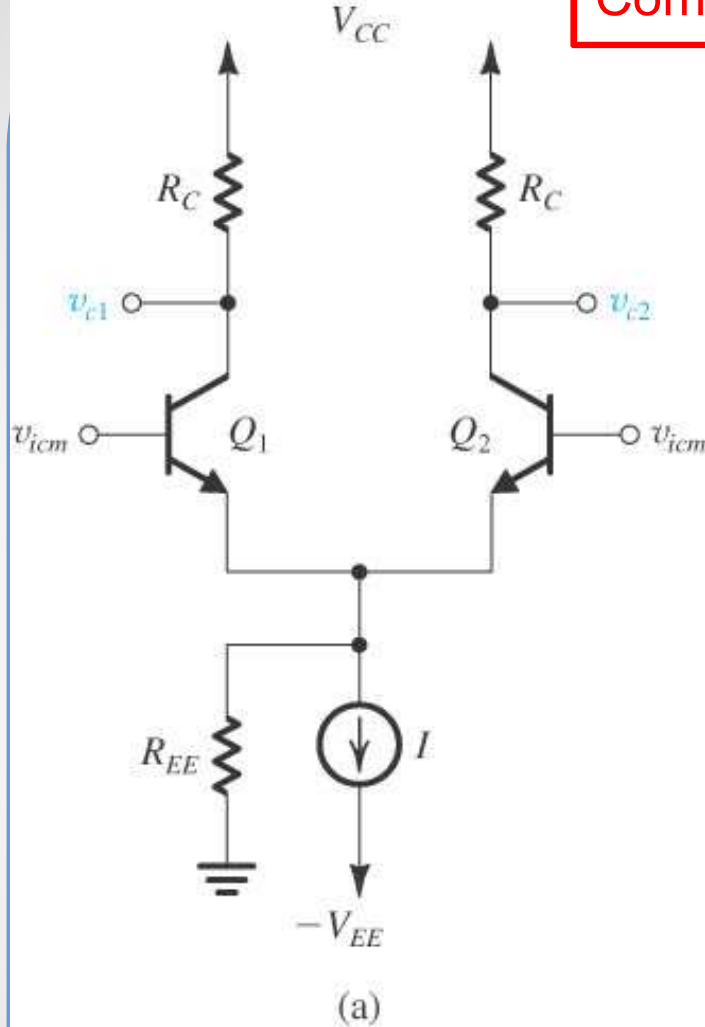

$$v_{c1} = -v_{icm} \frac{\alpha R_C}{2R_{EE} + r_e} \approx -v_{icm} \frac{\alpha R_C}{2R_{EE}}; \quad v_{c2} = -v_{icm} \frac{\alpha R_C}{2R_{EE} + r_e} \approx -v_{icm} \frac{\alpha R_C}{2R_{EE}}$$

$$A_{cm} = v_{c1} - v_{c2} = 0 \quad \text{for differential-ended output}$$

$$A_{cm} = v_{c2} = -\frac{\alpha R_C}{2R_{EE}} \quad \text{for single-ended output}$$

$$CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right|$$

$$CMRR = \infty \quad \text{for differential-ended output}$$


$$CMRR = 20 \log |g_m R_{EE}| \quad \text{for single-ended output because } A_d = -\frac{1}{2} g_m R_C$$

$$v_o = A_d (v_1 - v_2) + A_{cm} \left( \frac{v_1 + v_2}{2} \right)$$

If the diff amp is not symmetric due to the mismatched between  $R_C$ 's, then

$$A_{cm} = \frac{\alpha \Delta R_C}{2R_{EE} + r_e}$$

## Input common-mode resistance

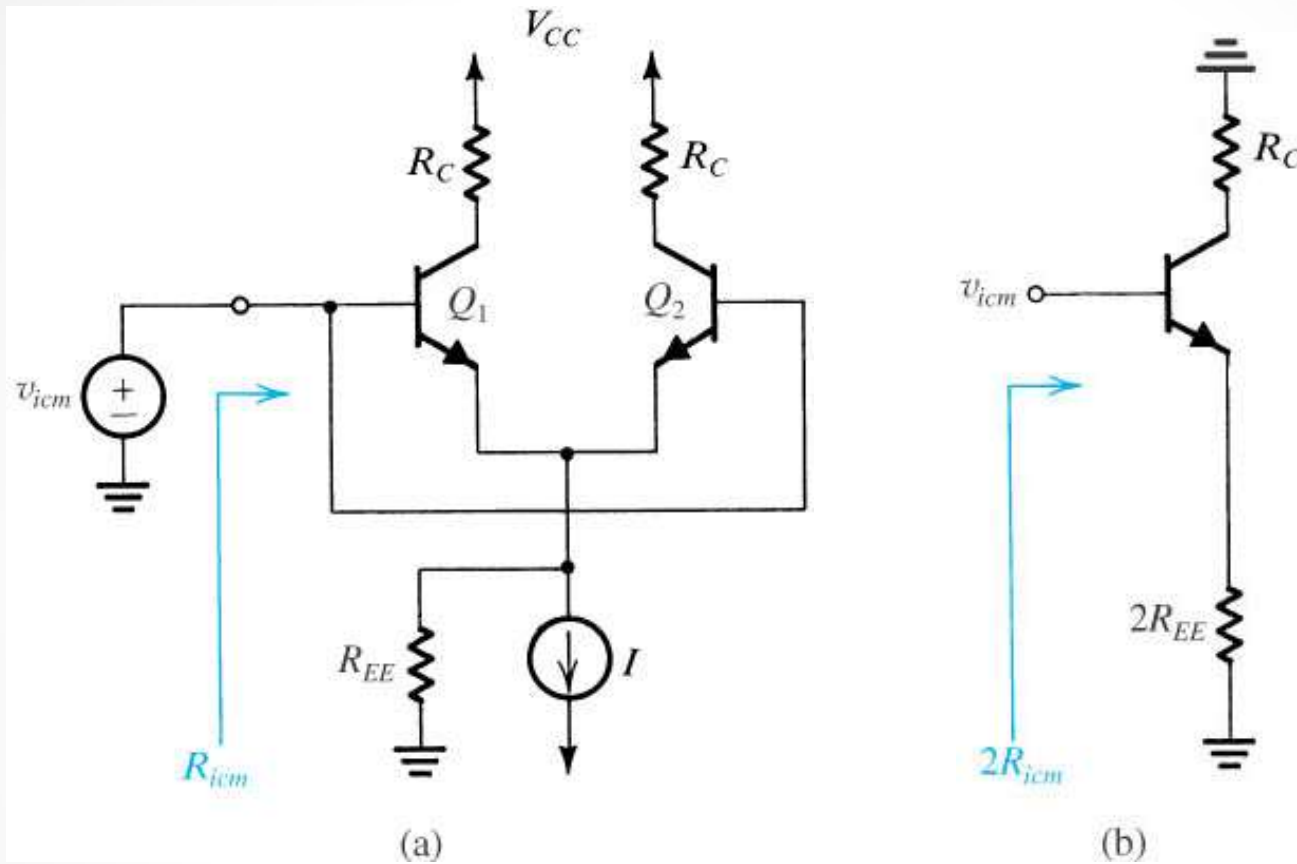


$$2R_{icm} \approx (\beta + 1)((2R_{EE} + 2r_e) \parallel r_o)$$

$$R_{icm} \approx (\beta + 1)((R_{EE} + r_e) \parallel \frac{r_o}{2})$$



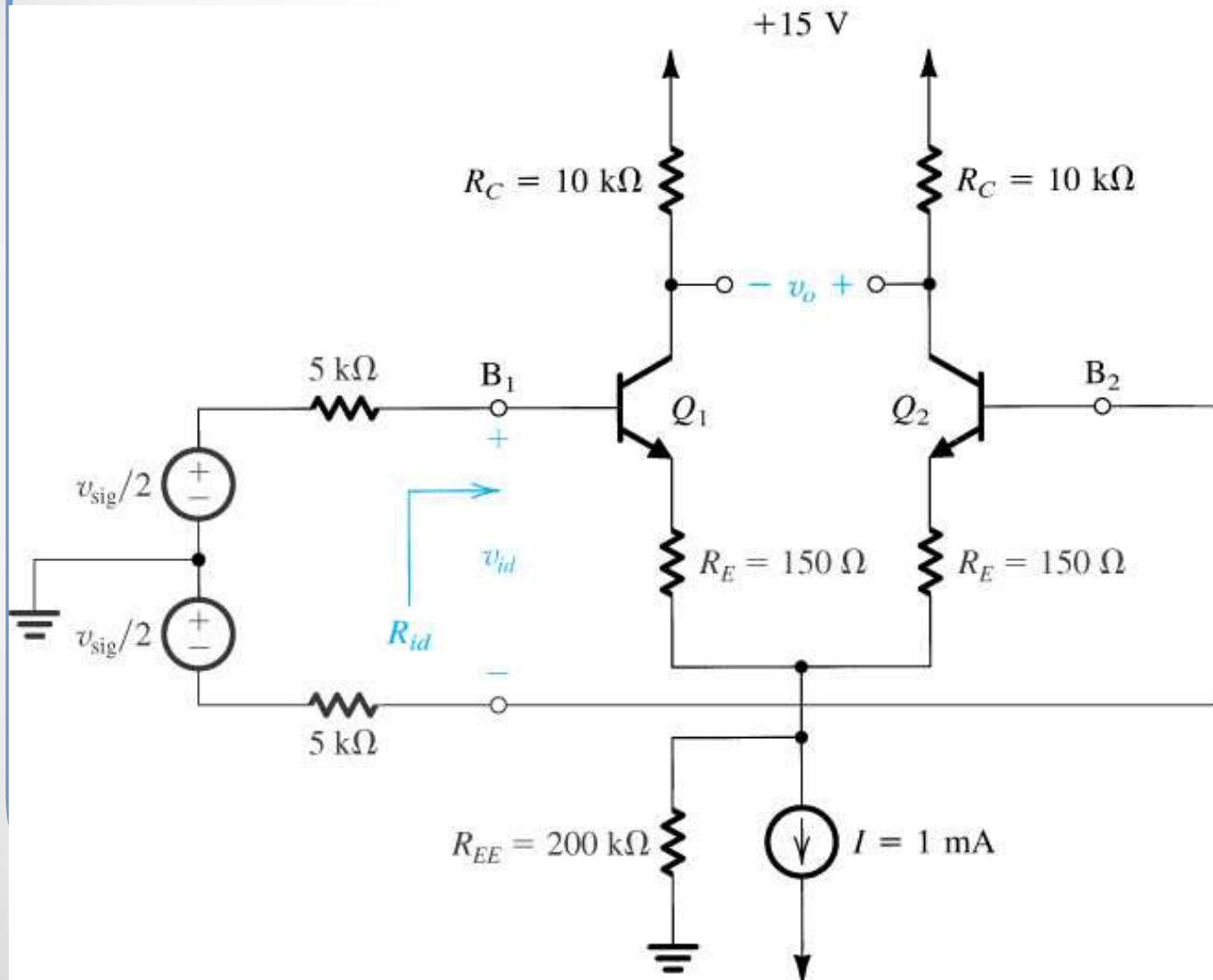
Example: from the ckt below, determine the following parameters:



- a) The input differential resistance  $R_{id}$
- b) The overall differential voltage gain  $v_o/v_{sig}$  (neglect the effect of  $r_o$ )
- c) The worst-case common-mode gain if the two collector resistances are accurate to within  $\pm 1\%$
- d) The CMRR in dB
- e) The input common-mode resistance (assuming that the Early voltage  $V_A = 100\text{ V}$ )


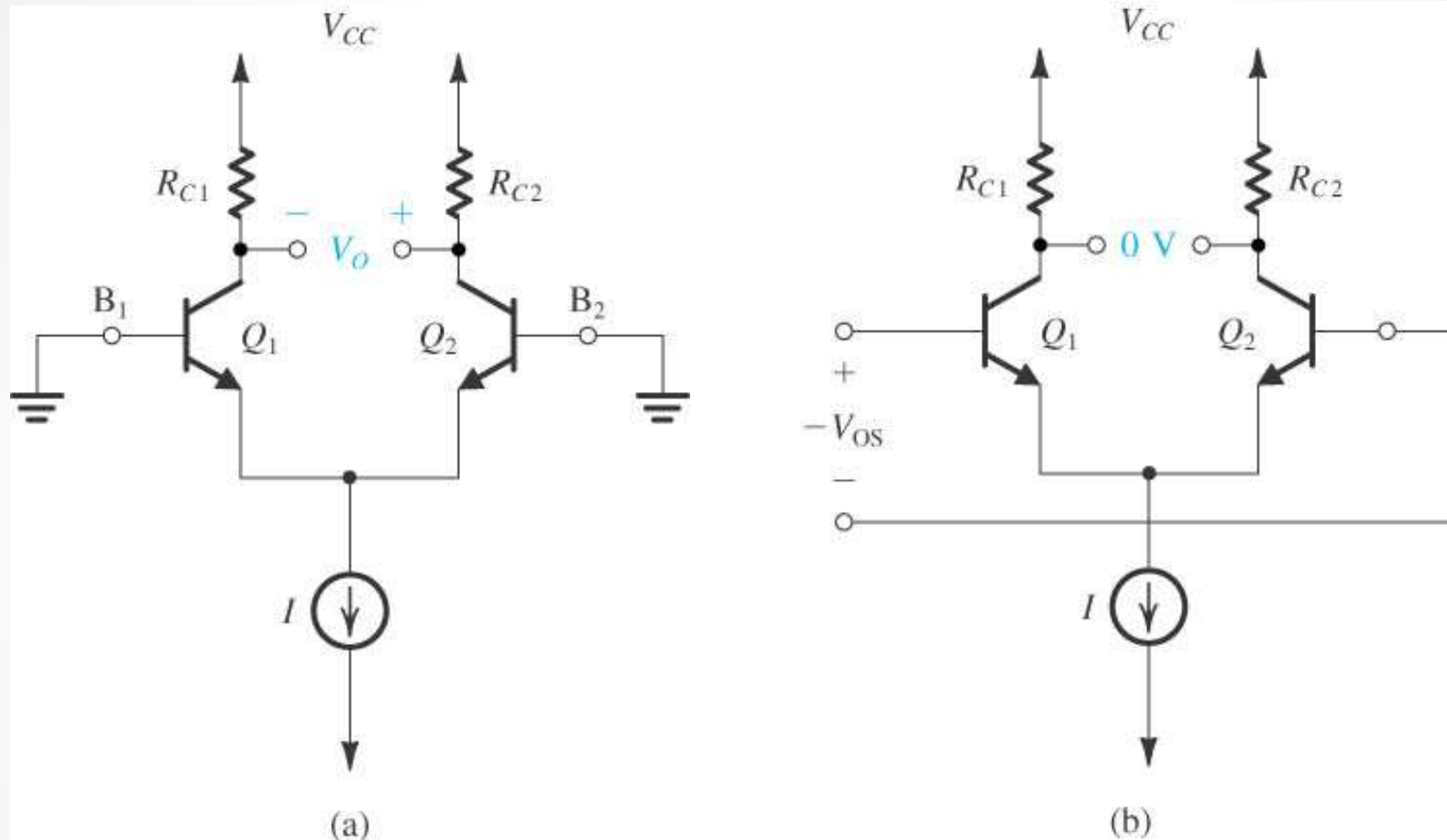
# Input offset voltage of the bipolar differential pair



**(a)** The BJT differential pair with both inputs grounded. Device mismatches result in a finite dc output  $V_O$ . **(b)** Application of the input offset voltage  $V_{OS}$ ;  $V_O/A_d$  to the input terminals with opposite polarity reduces  $V_O$  to zero.

The input offset voltage due to the mismatches between  $R_{C1}$  and  $R_{C2}$  is given by

$$|V_{OS}| = V_T \left( \frac{\Delta R_C}{R_C} \right)$$

The input offset voltage due to the mismatches between the emitter-base junction area is given by

$$|V_{OS}| = V_T \left( \frac{\Delta I_S}{I_S} \right)$$

Since the two contributions are not correlated, an estimate of the total input offset voltage can be found as


$$|V_{OS}| = V_T \sqrt{\left( \frac{\Delta R_C}{R_C} \right)^2 + \left( \frac{\Delta I_S}{I_S} \right)^2}$$

If there is a mismatch in  $\beta$ , there will be an offset current of


$$I_{OS} = I_B \left( \frac{\Delta \beta}{\beta} \right)$$


where  $I_B$  is the input bias current.

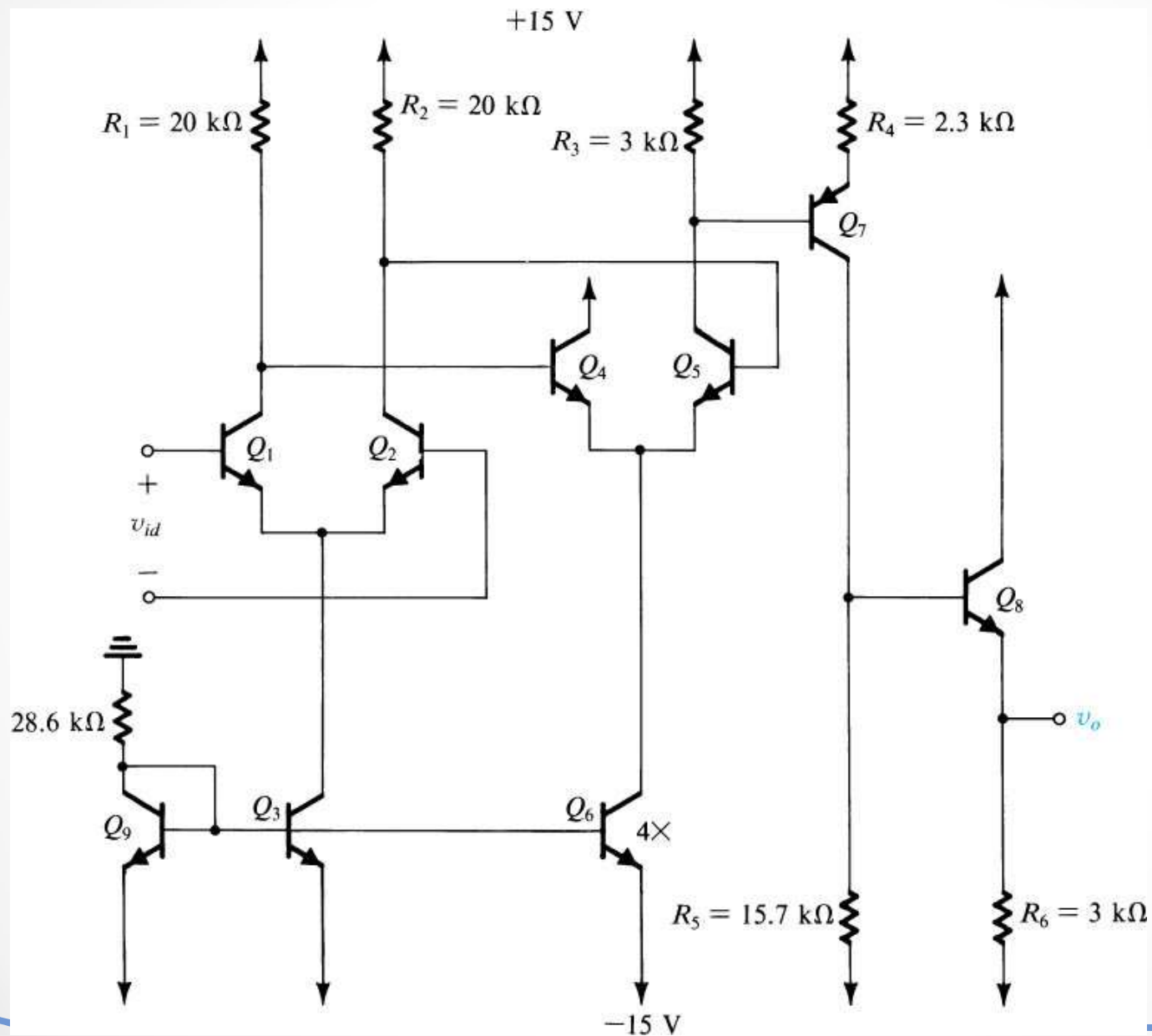



**Example:** a multistage bipolar op amp




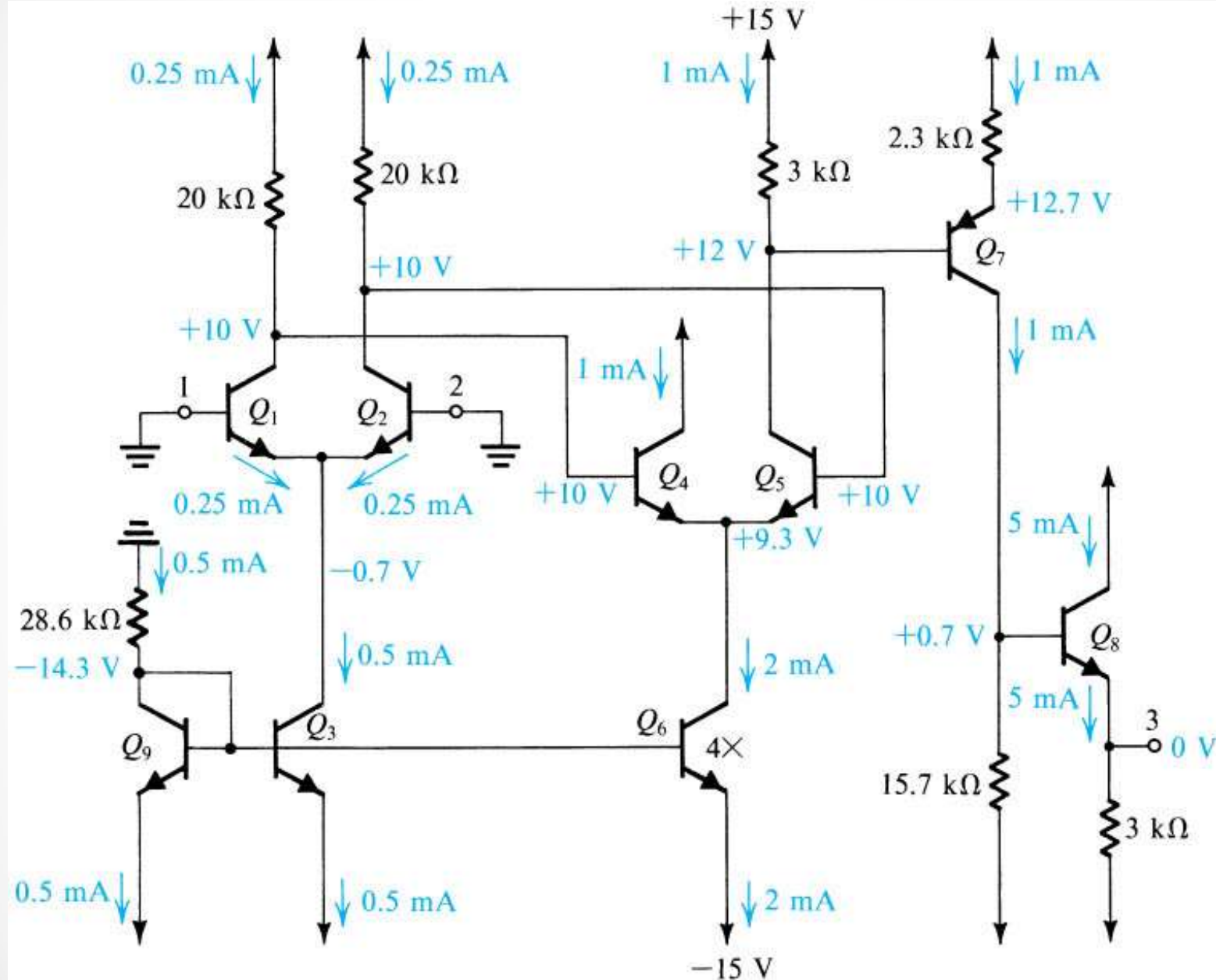


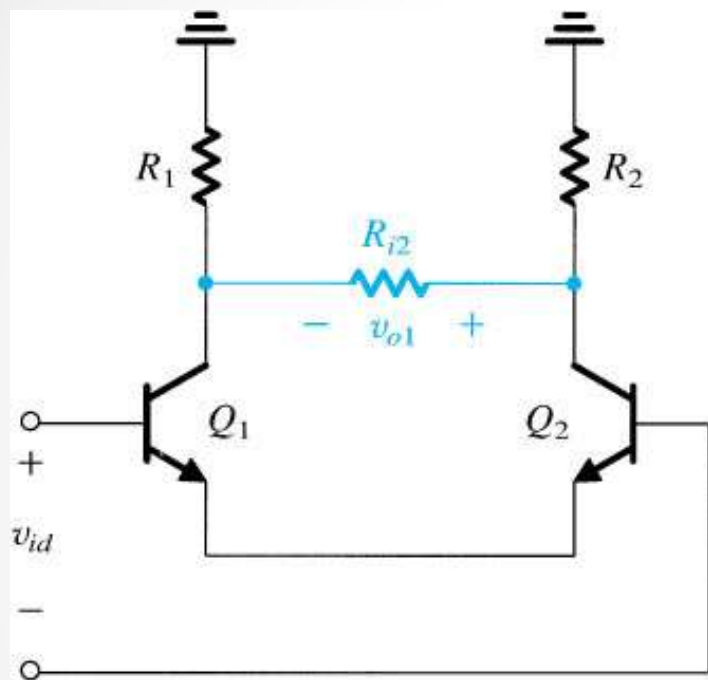


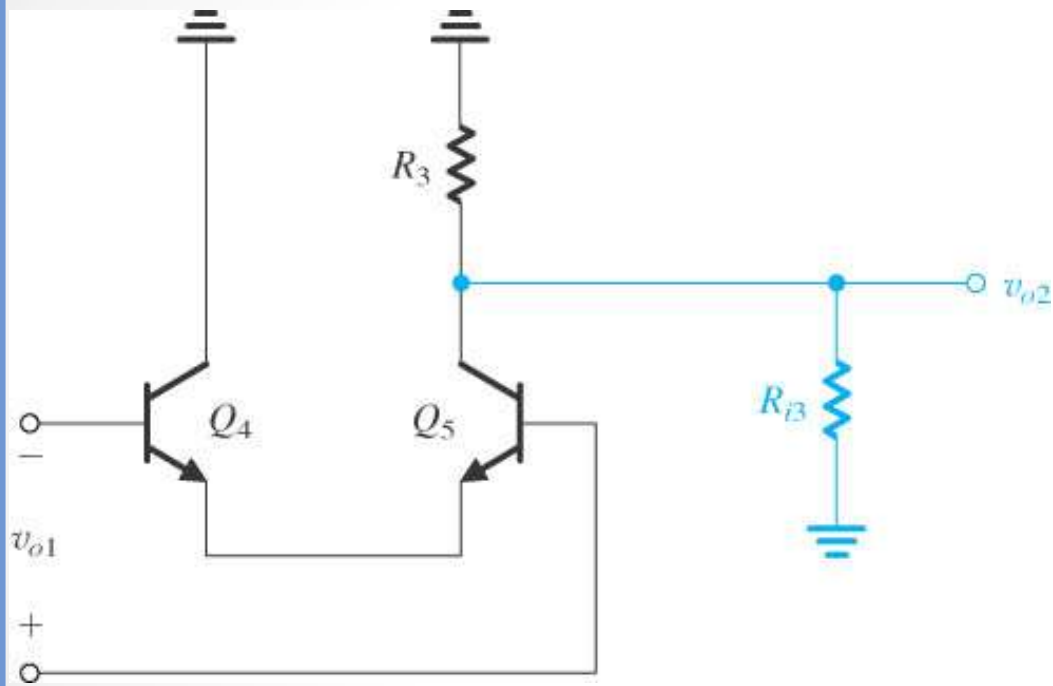

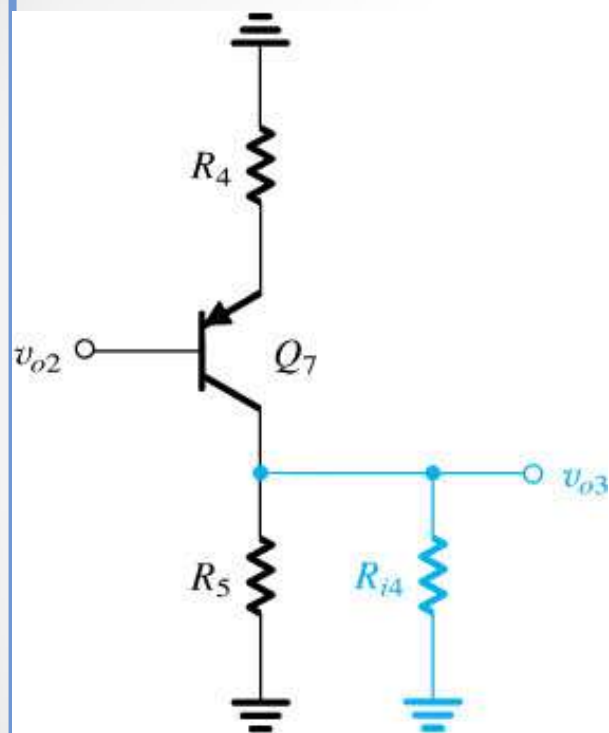


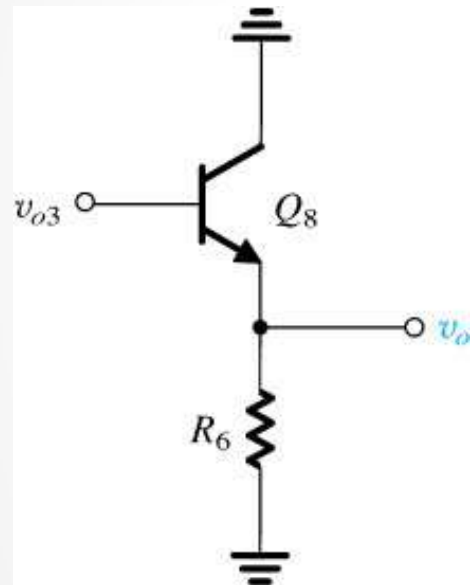

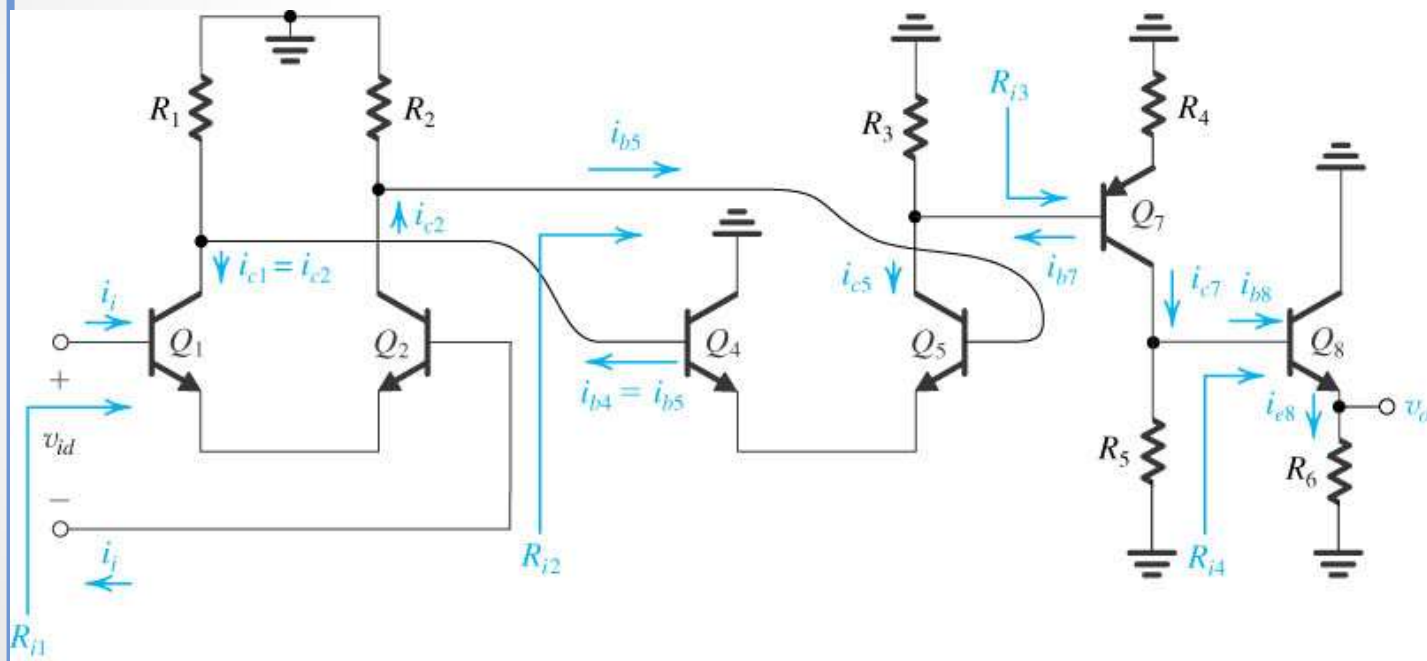

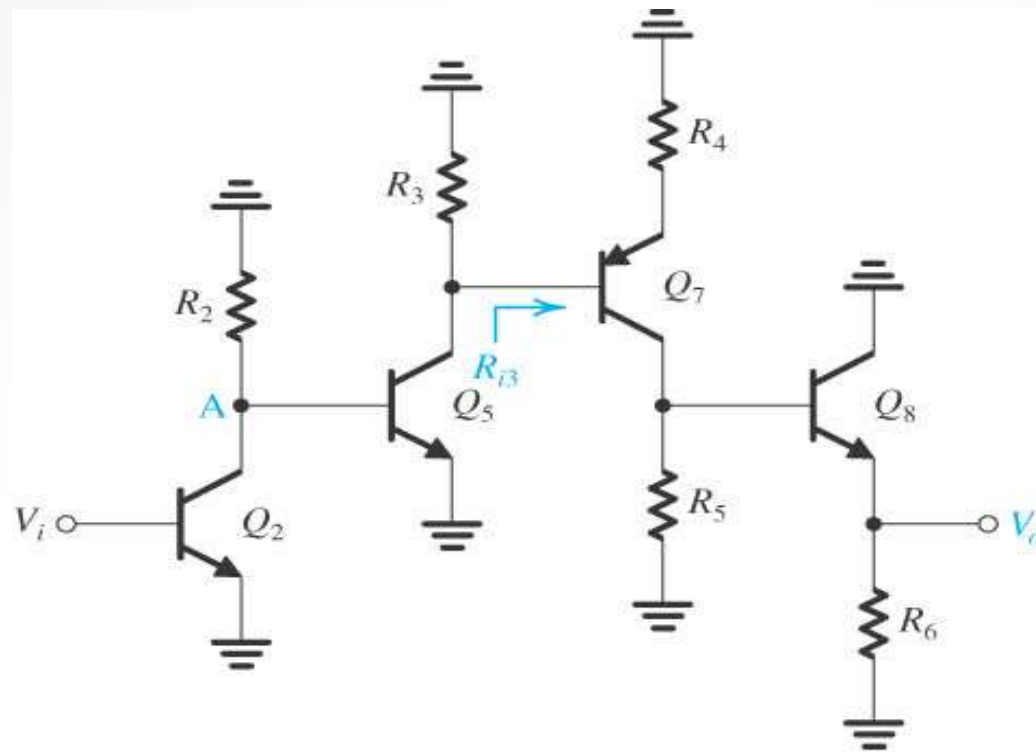

(a)

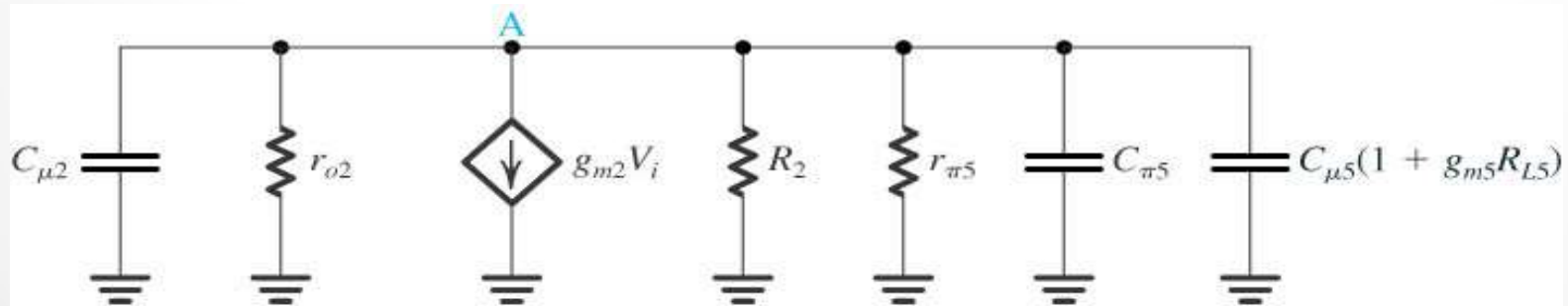


(b)





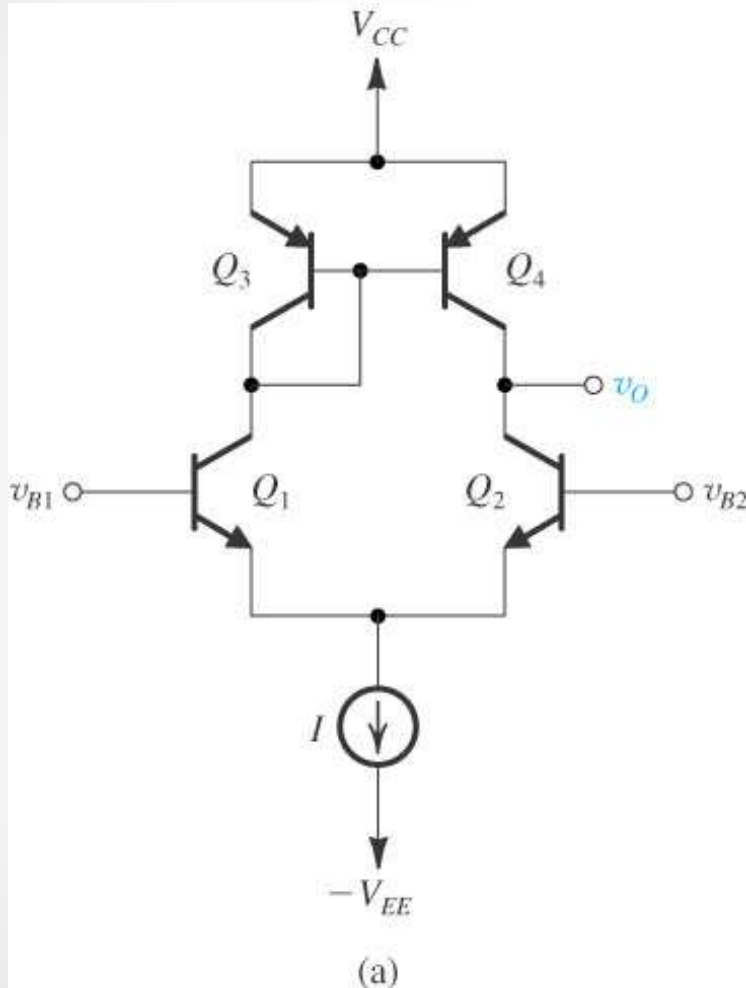
## The bipolar differential pair with active load



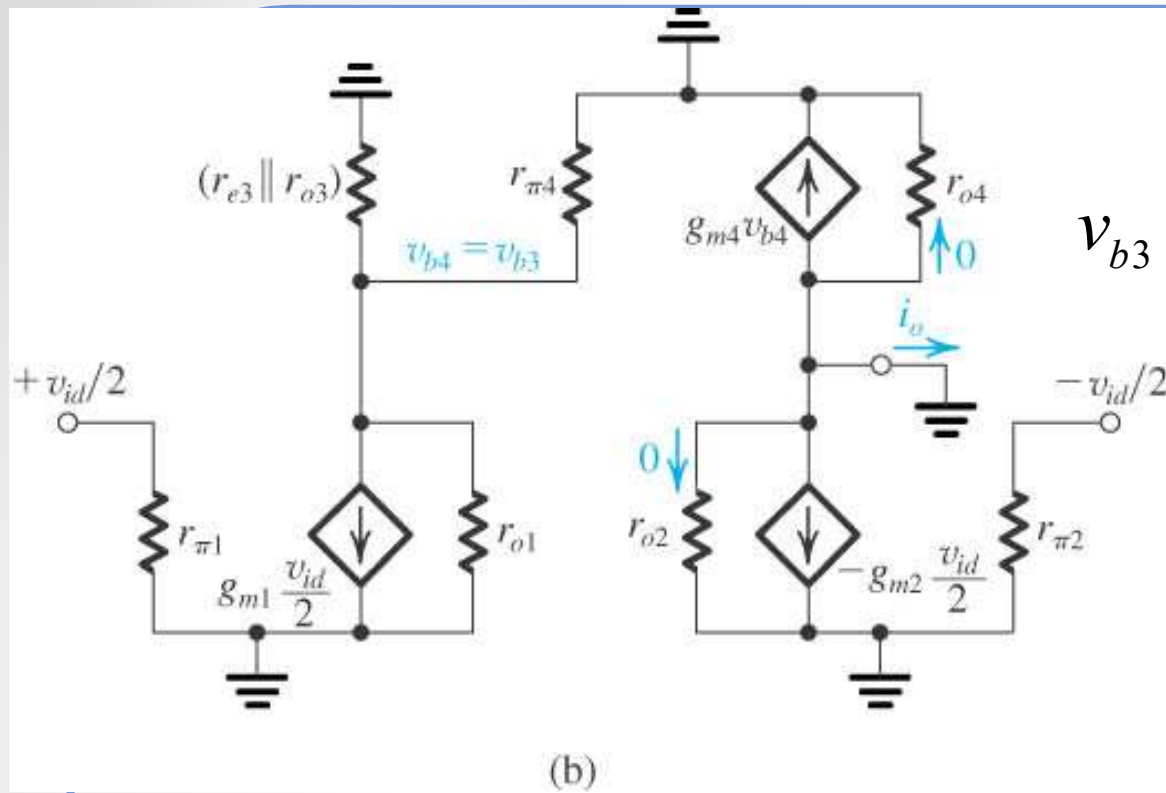- Q3 and Q4 act as active loads.
- An improved performance over the passive load version.
- An effective way to convert from a differential-ended output to a single-ended output



$$r_{e3} = \alpha_3 / g_{m3} = \alpha / g_m \approx 1 / g_m$$

$$v_{b3} = -g_{m1} \left( \frac{v_{id}}{2} \right) (r_{e3} \parallel r_{o3} \parallel r_{o1} \parallel r_{\pi4})$$

$$= -g_{m1} r_{e3} \left( \frac{v_{id}}{2} \right)$$


$$g_{m4} v_{b4} = -g_{m4} g_{m1} r_{e3} \left( \frac{v_{id}}{2} \right)$$

$$i_o = g_{m2} \left( \frac{v_{id}}{2} \right) - g_{m4} v_{b4}$$

$$i_o = g_{m2} \left( \frac{v_{id}}{2} \right) + g_{m4} g_{m1} r_{e3} \left( \frac{v_{id}}{2} \right)$$

$$g_{m1} = g_{m2} = g_{m4} = g_m = \frac{I/2}{V_T}$$

$$G_m = g_m$$

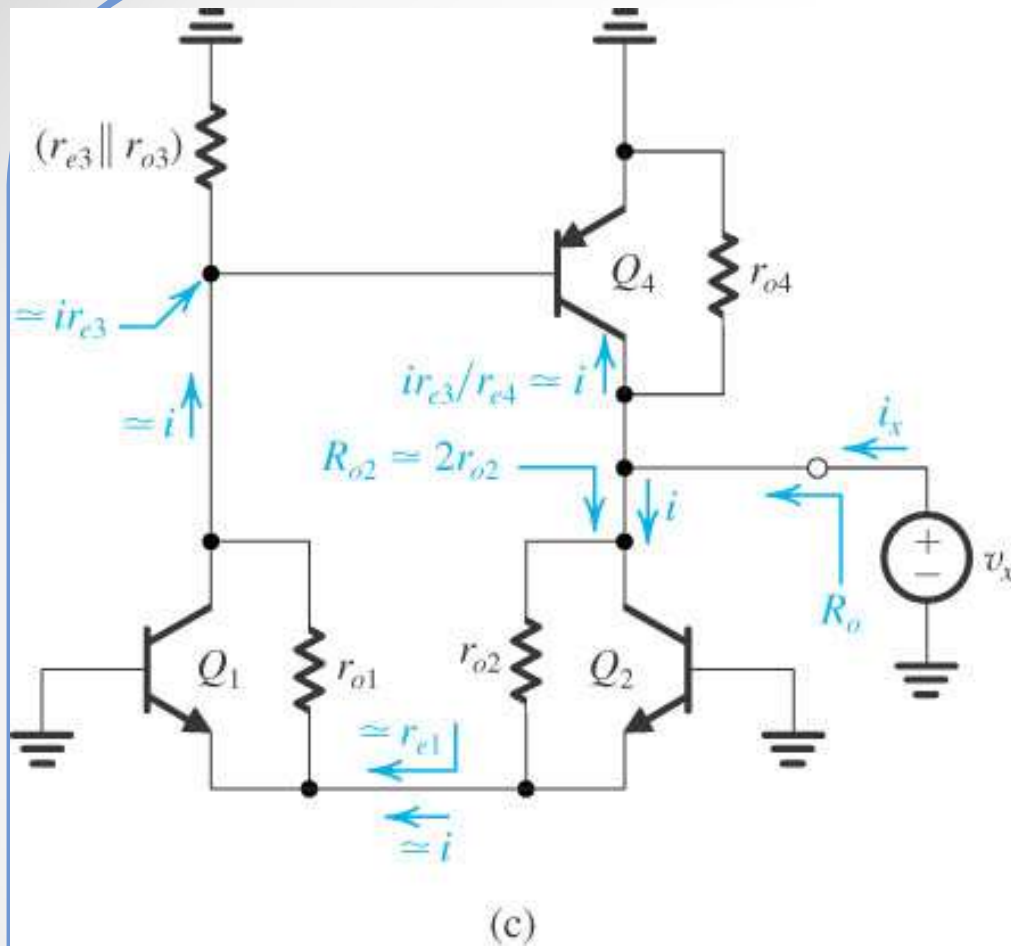

$$R_{o2} = r_{o2}[1 + g_{m2}(r_{e1} \parallel r_{\pi2})]$$

$$= r_{o2}[1 + g_{m2}r_{e1}]$$

$$= 2r_{o2}$$

$$i = \frac{v_x}{R_{o2}} = \frac{v_x}{2r_{o2}}$$

$$i_x = 2i + \frac{v_x}{r_{o4}} = \frac{v_x}{r_{o2}} + \frac{v_x}{r_{o4}}$$

$$R_o = \frac{v_x}{i_x} = r_{o2} \parallel r_{o4}$$

$$R_{id} = 2r_{\pi}$$

$$A_d = \frac{v_o}{v_{id}} = g_m(r_{o2} \parallel r_{o4}) = -\frac{1}{2}g_m r_o$$

## Reference

Microelectronic Circuits by Adel S. Sedra & Kenneth C. Smith. Saunders College Publishing



# OSMOSIS

Diffusion of molecules from a place of higher concentration to a place of lower concentration until the concentration on both sides is equal

ICANHASCHEEZBURGER.COM BY 🍕 💰 🍕





FINE ART PHOTOGRAPHY  
ABE BLAIR GALLERY