

Capacitance Measurement II




EIE 240 Electrical and Electronic Measurement
Class 9, April 3, 2015

1

Transformer Ratio Bridges

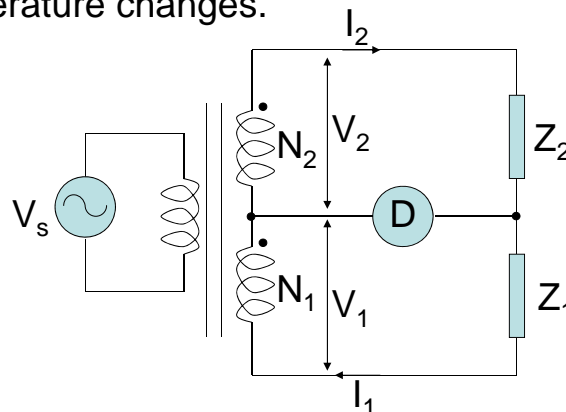Not only varying the impedances, but bridge can be also balanced by varying the turns ratio of a transformer. There is a small number of standard resistors and capacitors and no effect of temperature changes.



2

Single Ratio Transformer Bridge

Tap a transformer \Rightarrow voltage divider of V_s

$$V_1 = kN_1 = I_1 Z_1 \Rightarrow I_1 = kN_1 / Z_1$$

$$V_2 = kN_2 = I_2 Z_2 \Rightarrow I_2 = kN_2 / Z_2$$

To balance the bridge or no current through the detector, $\textcircled{D} = \text{Null}$

$$I_1 = I_2 \Rightarrow Z_1 / Z_2 = N_1 / N_2$$

Impedance Ratio Turn Ratio

3

Single Ratio Transformer Bridge (Cont'd)

- Resistance Measurement

$Z_1 = \text{Unknown resistor } R_x$

$Z_2 = \text{Standard resistor } R_s$

$$R_x = R_s \frac{N_1}{N_2}$$

4

Single Ratio Transformer Bridge (Cont'd)

- Capacitance Measurement

$$\begin{aligned}Z_1 &= \text{Unknown } C_x \parallel R_x \text{ (leakage resistance)} \\&= 1/(1/R_x + j\omega C_x) \\&= R_x / (1+j\omega R_x C_x)\end{aligned}$$

$$\begin{aligned}Z_2 &= \text{Standard } C_s \parallel R_s \\&= R_s / (1+j\omega R_s C_s)\end{aligned}$$

5

Single Ratio Transformer Bridge (Cont'd)

- Capacitance Measurement (Cont'd)

$$\text{Balanced, } Z_1 / Z_2 = N_1 / N_2$$

$$1/Z_1 = (N_2/N_1) 1/Z_2$$

$$(1+j\omega R_x C_x)/R_x = (N_2/N_1) (1+j\omega R_s C_s)/R_s$$

$$1/R_x + j\omega C_x = (N_2 / N_1 R_s) + j\omega C_s N_2/N_1$$

$$\text{Real part: } R_x = R_s N_1/N_2$$

$$\text{Imagination part: } C_x = C_s N_2/N_1$$

6

Single Ratio Transformer Bridge (Cont'd)

- Inductance Measurement

$$\begin{aligned} Z_1 &= \text{Unknown } L_x \parallel R_x \\ &= 1/(1/R_x + 1/j\omega L_x) \\ &= 1/(1/R_x - j/\omega L_x) \end{aligned}$$

$$\begin{aligned} Z_2 &= \text{Standard } C_s \parallel R_s \\ &= 1/(1/R_s + j\omega C_s) \\ &= 1/(1/R_s - j\omega C_s) \quad , \text{ Reversed Current} \end{aligned}$$

7

Single Ratio Transformer Bridge (Cont'd)

- Inductance Measurement (Cont'd)

$$\begin{aligned} \text{Balanced, } 1/Z_1 &= (N_2/N_1) 1/Z_2 \\ 1/R_x - j/\omega L_x &= (N_2/N_1) (1/R_s - j\omega C_s) \end{aligned}$$


$$\text{Real part: } R_x = R_s N_1/N_2$$

$$\begin{aligned} \text{Imagination part: } 1/\omega L_x &= (N_2/N_1)\omega C_s \\ L_x &= N_1 / N_2 \omega^2 C_s \end{aligned}$$

8

Double Ratio Transformer Bridge

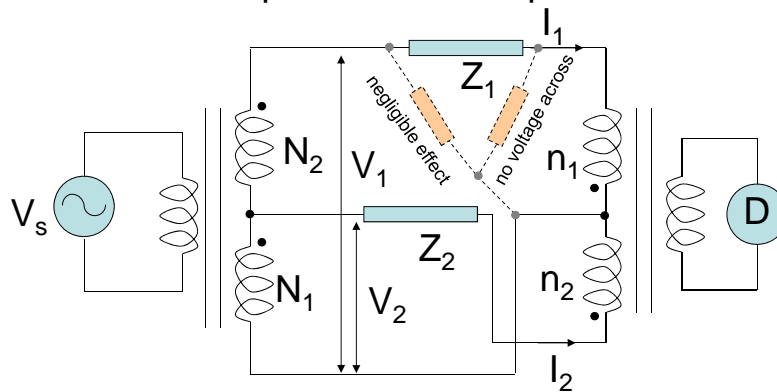To measure the impedance of components *in Situ*.



$$I_1 = V_1 / Z_1 = k(N_1 + N_2) / Z_1$$

$$I_2 = V_2 / Z_2 = kN_2 / Z_2$$

9

Double Ratio Transformer Bridge (Cont'd)

Balanced, null current or zero magnetic flux,

$$n_1 I_1 = n_2 I_2$$

$$n_1 (N_1 + N_2) / Z_1 = n_2 N_2 / Z_2$$

$$Z_1 = Z_2 \frac{n_1 (N_1 + N_2)}{n_2 N_2}$$


10

Q-Meter

RLC Series Resonance

$$Z = R + j\omega L + 1/j\omega C$$

$$= R + j(\omega L - 1/\omega C)$$

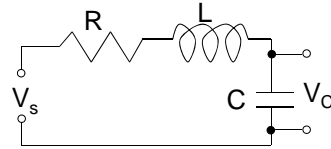


Resonant frequency

(When the voltage across C is a maximum.)

$$\omega_0 L = 1/\omega_0 C$$

$$\omega_0^2 = 1/LC$$

$$\omega_0 = 1/\sqrt{LC}$$

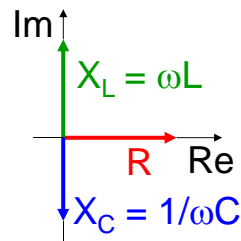

11

Q-Meter (Cont'd)

$$I_0 = V_s/R$$

$$V_C = I_0 X_C$$

$$= (V_s/R)(1/\omega_0 C)$$

$$= (1/\omega_0 RC) V_s$$

$$= Q V_s$$

$$\propto Q$$

where $Q = \text{Reactance/Resistance}$

$$= \omega_0 L / R$$


$$= \omega_0 (1/\omega_0^2 C) / R$$

$$= 1 / \omega_0 RC$$

(Unloaded)

12

Q-Meter (Cont'd)

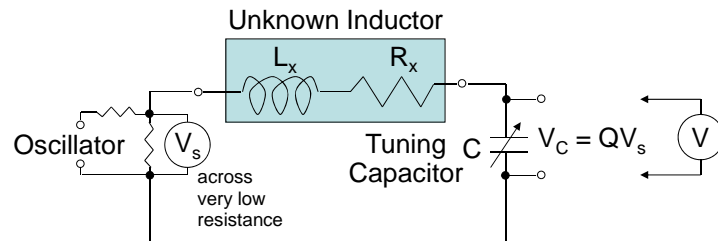


Tuning to resonance, $\omega_0 = 1/\sqrt{LC}$

$$L_x = 1 / \omega_0^2 C$$

$$R_x = 1 / Q\omega_0 C$$

13

Q-Meter: Low Impedance Measurement

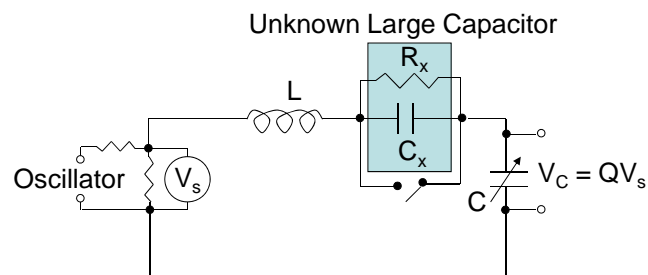

Short circuit \Rightarrow tuning $C = C_1$, $L_1 = L$, R_1

$$Q_1 = 1/\omega_0 R_1 C_1$$

$$R_1 = 1/\omega_0 C_1 Q_1$$

14

Q-Meter: Low Impedance Measurement (Cont'd)

Remove short circuit \Rightarrow then tuning $C = C_2$

$$C_2 \text{ \& } C_x = C_1, L_2 = L, R_2 = R_1 \text{ \& } R_x$$

$$\begin{aligned} \text{Series capacitors, } C_1 &= 1 / (1/C_x + 1/C_2) \\ &= C_2 C_x / (C_x + C_2) \end{aligned}$$

$$C_1 C_x + C_1 C_2 = C_2 C_x$$

$$C_x = C_1 C_2 / (C_2 - C_1)$$

$$Q_2 = 1/\omega_0 R_2 C_2$$

$$R_2 = 1/\omega_0 C_2 Q_2$$

15

Q-Meter: Low Impedance Measurement (Cont'd)

$$R_1 = R_2 - R_x$$

$$R_x = R_2 - R_1, \text{ Leakage resistance}$$

$$= 1/\omega_0 C_2 Q_2 - 1/\omega_0 C_1 Q_1$$

$$= (C_1 Q_1 - C_2 Q_2) / (\omega_0 C_1 C_2 Q_1 Q_2)$$

$$Q_x = 1/\omega_0 R_x C_x$$

$$= (\omega_0 C_1 C_2 Q_1 Q_2)(C_2 - C_1) /$$

$$\omega_0 (C_1 Q_1 - C_2 Q_2) C_1 C_2$$

$$= Q_1 Q_2 (C_2 - C_1) / (C_1 Q_1 - C_2 Q_2)$$

16

Q-Meter: Low Impedance Measurement (Cont'd)

If the unknown component is an inductor,

$$L_x = 1/\omega_0^2 C_x$$

$$= (C_2 - C_1) / \omega_0^2 C_1 C_2$$


If the unknown component is a pure resistor (no reactance),

$$R_x = (C_1 Q_1 - C_2 Q_2) / (\omega_0 C_1 C_2 Q_1 Q_2)$$

$$= (Q_1 - Q_2) / \omega_0 C_1 Q_1 Q_2, \quad C_1 = C_2$$

17

Q-Meter: High Impedance Measurement

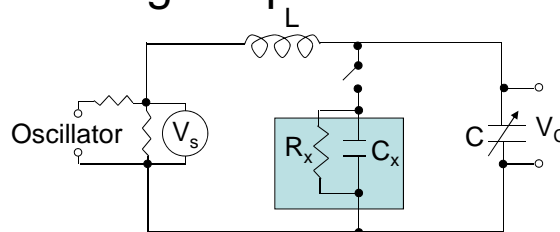

For high resistance, inductance > 100mH, or capacitance < 400 pF

Open circuit and tune $C = C_1$, $L_1 = L$, R_1

Then short circuit and tune $C = C_2$

$$C_2 // C_x = C_1, \quad L_2 = L, \quad R_2 = R_x // R_1$$

$$C_x + C_2 = C_1 \quad \Rightarrow \quad C_x = C_1 - C_2$$

$$R_2 = R_x // R_1 = R_x R_1 / (R_x + R_1) \Rightarrow R_x = R_1 R_2 / (R_1 - R_2)$$

18

Q-Meter: High Impedance Measurement (Cont'd)

Parallel RLC $\Rightarrow Q = \omega_0 RC$ (loaded)

$$R_1 = Q_1 / \omega_0 C_1 \text{ and } R_2 = Q_2 / \omega_0 C_2$$

Therefore

$$\begin{aligned} R_x &= Q_1 Q_2 \omega_0 C_1 C_2 / \omega_0^2 C_1 C_2 (Q_1 C_2 - Q_2 C_1) \\ &= Q_1 Q_2 / \omega_0 (Q_1 C_2 - Q_2 C_1) \end{aligned}$$

$$\begin{aligned} Q_x &= \omega_0 R_x C_x \\ &= \omega_0 Q_1 Q_2 (C_1 - C_2) / \omega_0 (Q_1 C_2 - Q_2 C_1) \\ &= Q_1 Q_2 (C_1 - C_2) / (Q_1 C_2 - Q_2 C_1) \end{aligned}$$

19

Q-Meter: High Impedance Measurement (Cont'd)

For unknown inductance,

$$\begin{aligned} L_x &= 1 / \omega_0^2 C_x \\ &= 1 / \omega_0^2 (C_1 - C_2) \end{aligned}$$

For pure resistance,

$$\begin{aligned} R_x &= Q_1 Q_2 / \omega_0 (Q_1 C_2 - Q_2 C_1) \\ &= Q_1 Q_2 / \omega_0 C_1 (Q_1 - Q_2) \quad , C_1 = C_2 \end{aligned}$$

20