



Seat No.: _____

**King Mongkut's University of Technology Thonburi
Final Exam of Second Semester, Academic Year 2015**

CPE 223 Digital System Design

CPE(Inter.) Students

Tuesday 10 May 2016

13.00-16.00

Instructions

1. This examination contains 7 problems, 9 pages (including this cover page),
The total score is 40 points.
2. The answers must be written in the space provided.
3. Students are allowed to use **calculator**.
4. **Books, notes, and dictionary** are **NOT** allowed.

**Students must raise their hand to inform to the proctor upon their
completion of the examination, to ask for permission to leave the
examination room.**

**Students must not take the examination and the answers out of the
examination room.**

**Students will be punished if they violate any examination rules. The highest
punishment is dismissal.**

This examination is prepared by

Asst. Prof. Sanan Srakaew

Tel. 0-2470-9083

This examination paper is approved by Computer Engineering Department.

Problem	1	2	3	4	5	6	7	Total Points
Points Earned								
Points	5	5	5	5	5	5	10	40

Student Name: _____ I.D.: _____

1. In Figure 1, a 4-to-1 multiplexer circuit.

(5 points)

 


Figure 1: A 4-to-1 multiplexer circuit.

(a) Write a Verilog module using gate-level design(structural Verilog)

(b) Rewrite a Verilog module in (a) using behavioral model.

2. Given a half adder Verilog module

```
module half_adder((x, y, s, c);  
input x,y;  
output s,c;  
    assign s = x ^ y;  
    assign c = x & y;  
endmodule
```

(5 points)

(a) Write a full adder Verilog module, namely **full_adder**, using half_adder.

(b) Write a 4-bit full adder Verilog module, namely **adder_4bit**, using **full_adder**.

3. Given a dataflow Verilog module below:

```
module fun(E,A,D);  
input E;  
input [1:0] A;  
output [3:0] D;  
    assign D[0] = ~(~E & ~A[1] & ~A[0]);  
    assign D[1] = ~(~E & ~A[1] & A[0]);  
    assign D[2] = ~(~E & A[1] & ~A[0]);  
    assign D[3] = ~(~E & A[1] & A[0]);  
endmodule
```

Draw a NAND-gate-only circuit to represent the Verilog module above. (5 points)

4. Write a Verilog code using **if... else** statement to implement an 8-bit 2-to-1 multiplexer as shown in Figure 2 below:

 


Figure 2: An 8-bit 2-to-1 multiplexer.

(5 points)

5. Given a 4-bit BCD counter circuit using JK flip-flops shown in Figure 3 below:

 


Figure 3: A 4-bit BCD counter using JK flip-flops.

```

module JKFF (input J, K, Clk, Reset, output reg Q);
  always @ (posedge Clk, negedge Reset)
    if (!Reset) Q <= 1'b0;
    else
      case ({J,K})
        2'b00: Q <= Q;
        2'b01: Q <= 1'b0;
        2'b10: Q <= 1'b1;
        2'b11: Q <= ~Q;
      endcase
    endmodule

```

(5 points)

- (a) Using JKFF module above, write a Verilog module to implement the 4-bit BCD counter of the circuit above.

(b) Rewrite the 4-bit BCD counter Verilog module using behavioral model.

6. From a simple CPU structure given in Figure 4 below:

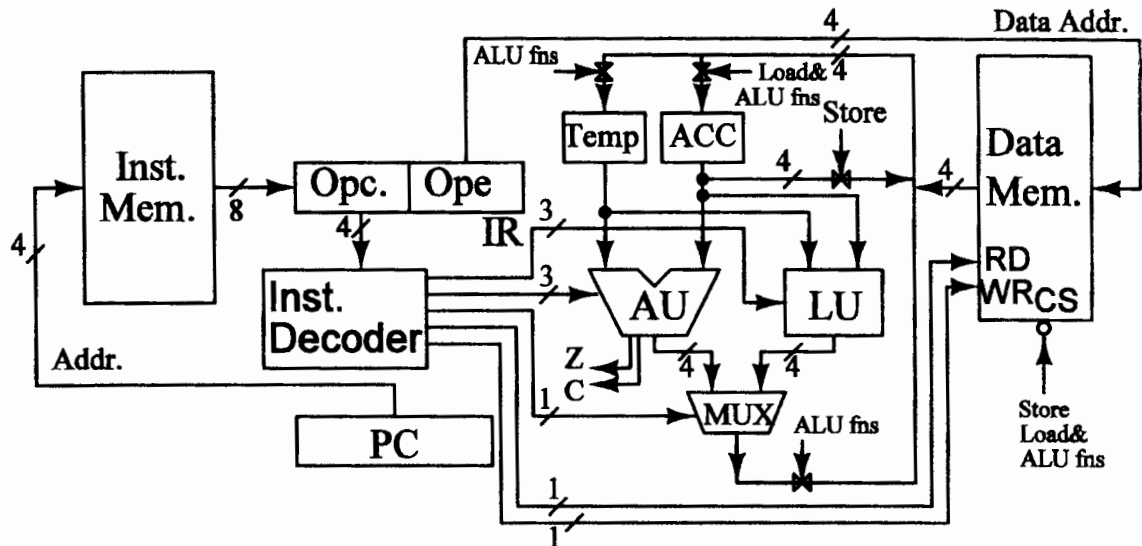


Figure 4. A simple CPU structure.

Write a Verilog code to implement a Data Memory module.

(5 points)

7. What is your Final project name? Draw a block diagram of the top module of your Final project. Pick one module in the top module and write a Verilog code for that module. (10 points)