



Seat Number

**King Mongkut's University of Technology Thonburi**  
**Final Examination**

**Semester 1 -- Academic Year 2013**

**Subject:** EIE 210 Electronic Devices and Circuit Design I

**For:** Electrical Communication and Electronic Engineering, 2<sup>nd</sup> Yr (Inter. Program)

**Exam Date:** Wednesday November 27, 2013

**Time:** 13.00-16.00 pm.

**Instructions:-**

1. This exam consists of 5 problems with a total of 6 pages, including the cover.
2. This exam is closed books.
3. You are **not** allowed to use any written A4 note for this exam.
4. Answer each problem on the exam itself.
5. A calculator compiling with the university rule is allowed.
6. A dictionary is **not** allowed.
7. **Do not** bring any exam papers and answer sheets outside the exam room.
8. Open Minds ... No Cheating! GOOD LUCK!!!

**Remarks:-**

- Raise your hand when you finish the exam to ask for a permission to leave the exam room.
- Students who fail to follow the exam instruction might eventually result in a failure of the class or may receive the highest punishment with university rules.
- Carefully read the entire exam before you start to solve problems. Before jumping into the mathematics, think about what the question is asking. Investing a few minutes of thought may allow you to avoid twenty minutes of needless calculation!

Exam No.	1	2	3	4	5	6	7	8	TOTAL
Full Score									
Graded Score									

Name \_\_\_\_\_ Student ID \_\_\_\_\_


This examination is designed by  
Dr. Kamon Jirasereeamornkul; Tel: 9067.

**This examination has been approved by the committees of the ENE department.**


*A. Wudhichai*

(Assoc. Prof. Wudhichai Assawinchaichote, Ph.D.)  
Head of Electronic and Telecommunication Engineering Department

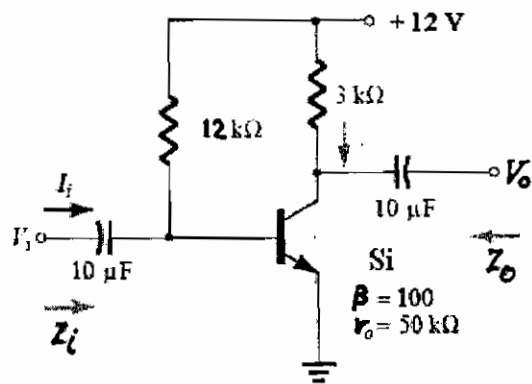
1. From the Fixed bias circuit, determine  $I_{BQ}$ ,  $I_{CQ}$  and  $V_{CEQ}$ . (10 marks)



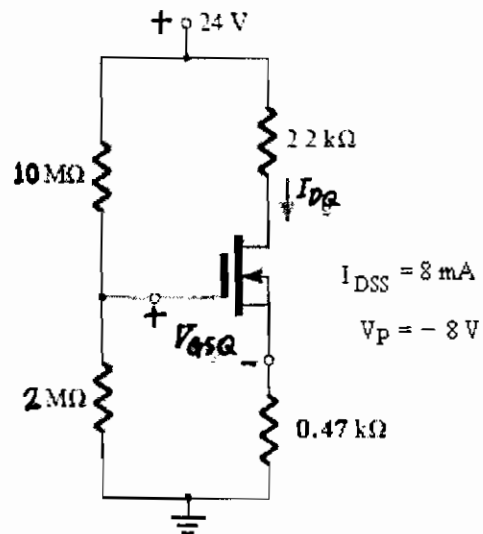
2. Consider the following circuit, determine  $V_{GSQ}$  and  $I_{DQ}$ . (10 marks)



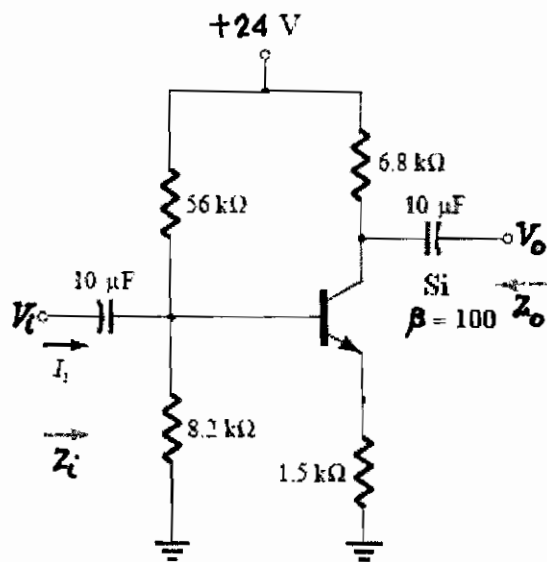3. From the following amplifier circuit, determine  $I_{CQ}$  and  $V_{CEQ}$ . Also, find  $Z_i$ ,  $Z_o$  and  $A_v$  by using  $r_e$  model. (20 marks)



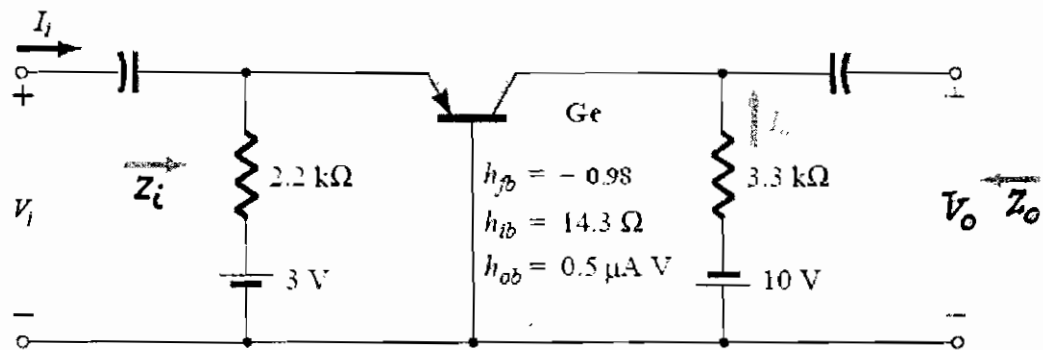4. Please determine  $Z_i$ ,  $Z_o$  and  $A_v$  of Common-Base Amplifier. (5 marks)



5. Please analyze the following circuit and conclude its function. Assume that the input voltage has only 2 levels, 0 V or 15 V. (5 marks)

