



Seat Number

King Mongkut's University of Technology Thonburi
Midterm Examination
Semester 1 -- Academic Year 2016

Subject: EIE 210 Electronic Devices and Circuit Design I

For: Electrical Communication and Electronic Engineering, 2nd Yr (Inter. Program)

Exam Date: Wednesday September 21, 2016

Time: 13.00-16.00 pm.

Instructions:-

1. This exam consists of 5 problems with a total of 8 pages, including the cover.
2. This exam is closed books.
3. You are **not** allowed to use any written A4 note for this exam.
4. Answer each problem on the exam itself.
5. A calculator compiling with the university rule is allowed.
6. A dictionary is **not** allowed.
7. **Do not** bring any exam papers and answer sheets outside the exam room.
8. Open Minds ... No Cheating! GOOD LUCK!!!

Remarks:-

- **Raise your hand when you finish the exam to ask for a permission to leave the exam room.**
- **Students who fail to follow the exam instruction might eventually result in a failure of the class or may receive the highest punishment with university rules.**
- **Carefully read the entire exam before you start to solve problems. Before jumping into the mathematics, think about what the question is asking. Investing a few minutes of thought may allow you to avoid twenty minutes of needless calculation!**

Exam No.	1	2	3	4	5	6	7	8	TOTAL
Full Score	<u>10</u>	<u>10</u>	<u>20</u>	<u>30</u>	<u>10</u>				<u>80</u>
Graded Score									

Name _____ Student ID _____

This examination is designed by
Asst. Prof. Kamon Jirasereeamornkul. Ph.D, & Prof. Niel S. Kurt. Ph.D.; Tel: 9067.

This examination has been approved by the committees of the ENE department.

(Assoc. Prof. Rardchawadee Silapunt, Ph.D.)
Head of Electronic and Telecommunication Engineering Department

Name.....Student ID.....Seat #.....

2

1. A pn-junction silicon diode ($T = 350 \text{ K}$) is doped with the following concentrations: $N_A = 2.5 \times 10^{16} \text{ cm}^{-3}$, $N_D = 4.5 \times 10^{13} \text{ cm}^{-3}$. Calculate the intrinsic carrier density n_i of silicon and the junction built-in voltage V_0 (10 marks).

2. Analyze and draw the output of the clipper in Figure 1. Assume that the diode is an ideal one (10 marks).

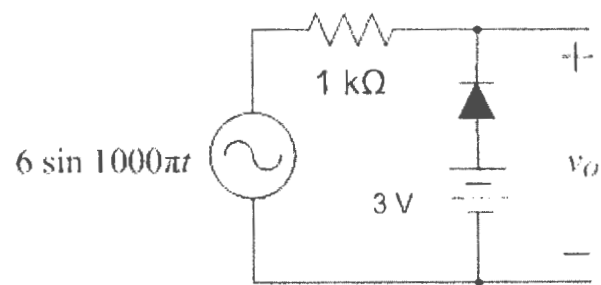


Fig. 1

3. Consider the circuit in Figure 2. Sketch the waveform of output voltage v_O and current i_O compare with secondary voltage v_s . Also, determine the peak values of i_O and the reverse voltage at D_1 . (20 marks)


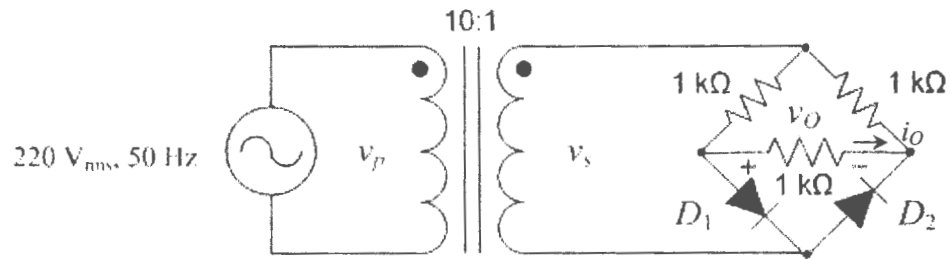


Fig. 2

4. A zener diode whose nominal voltage is 7.2 V at 20 mA is used in the design of a shunt regulator fed from a 24-V supply. The knee current I_{ZK} is specified to be 5 mA. The load current varies over a range of 0 mA to 200 mA.
- 4.1) Draw a sketch of the circuit (input voltage, zener diode, shunt resistor R_S , and load R_L) (10 marks).
 - 4.2) Find a suitable value for the shunt resistor R_S (10 marks).
 - 4.3) Calculate the maximum power dissipation of the zener diode and of the shunt resistor R_S (10 marks)?

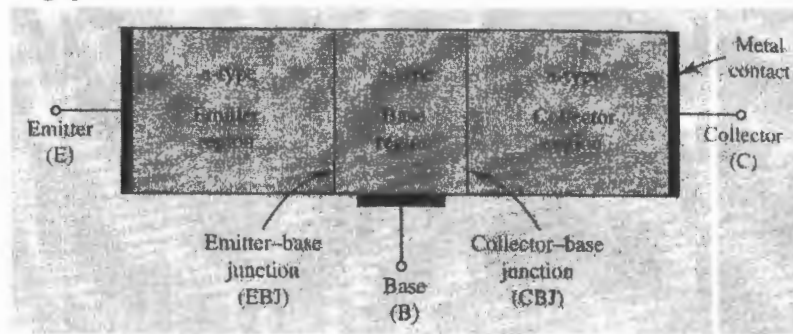5. Bipolar junction transistor in npn-format and in active mode: Check the answers for the following questions (10 marks):



The emitter-base junction is in forward bias	<input type="checkbox"/> yes	<input type="checkbox"/> no	
The collector-base junction is in forward bias	<input type="checkbox"/> yes	<input type="checkbox"/> no	
The collector current depends on the collector-base voltage	<input type="checkbox"/> yes	<input type="checkbox"/> no	
The collector current depends on the emitter-base voltage	<input type="checkbox"/> yes	<input type="checkbox"/> no	
The common-emitter current gain β is in the range of	<input type="checkbox"/> 0.1 - 10	<input type="checkbox"/> 50 - 200	<input type="checkbox"/> $10^5 - 10^7$

Summary of given formulars

Table 1.3 Summary of Important Semiconductor Equations		
Quantity	Relationship	Values of Constants and Parameters (for Intrinsic Si at $T = 300\text{ K}$)
Carrier concentration in intrinsic silicon (cm^{-3})	$n_i = BT^{3/2} e^{-E_g/2kT}$	$B = 7.3 \times 10^{15} \text{ cm}^{-3} \text{ K}^{-3/2}$ $E_g = 1.12 \text{ eV}$ $k = 8.62 \times 10^{-5} \text{ eV/K}$ $n_i = 1.5 \times 10^{10} / \text{cm}^3$
Diffusion current density (A/cm^2)	$J_p = -qD_p \frac{dp}{dx}$ $J_n = qD_n \frac{dn}{dx}$	$q = 1.60 \times 10^{-19} \text{ coulomb}$ $D_p = 12 \text{ cm}^2/\text{s}$ $D_n = 34 \text{ cm}^2/\text{s}$
Drift current density (A/cm^2)	$J_{\text{drift}} = q(p\mu_p + n\mu_n)E$	$\mu_p = 480 \text{ cm}^2/\text{V} \cdot \text{s}$ $\mu_n = 1350 \text{ cm}^2/\text{V} \cdot \text{s}$
Resistivity ($\Omega \cdot \text{cm}$)	$\rho = 1/[q(p\mu_p + n\mu_n)]$	μ_p and μ_n decrease with the increase in doping concentration
Relationship between mobility and diffusivity	$\frac{D_n}{\mu_n} = \frac{D_p}{\mu_p} = V_T$	$V_T = kT/q \approx 25.9 \text{ mV}$
Carrier concentration in n-type silicon (cm^{-3})	$n_{n0} \approx N_D$ $p_{n0} = n_i^2/N_D$	
Carrier concentration in p-type silicon (cm^{-3})	$p_{p0} \approx N_A$ $n_{p0} = n_i^2/N_A$	
Junction built-in voltage (V)	$V_0 = V_T \ln\left(\frac{N_A N_D}{n_i^2}\right)$	
Width of depletion region (cm)	$\frac{x_n}{x_p} = \frac{N_A}{N_D}$ $W = x_n + x_p$ $= \sqrt{\frac{2\epsilon_s}{q} \left(\frac{1}{N_A} + \frac{1}{N_D}\right) (V_0 + V_R)}$	$\epsilon_s = 11.7\epsilon_0$ $\epsilon_0 = 8.854 \times 10^{-14} \text{ F/cm}$

Table 1.3 continued		
Quantity	Relationship	Values of Constants and Parameters (for Intrinsic Si at $T = 300$ K)
Charge stored in depletion layer (coulomb)	$Q_d = q \frac{N_A N_D}{N_A + N_D} A W$	
Forward current (A)	$I = I_p + I_n$ $I_p = A q n_i^2 \frac{D_p}{L_p N_D} (e^{V/V_T} - 1)$ $I_n = A q n_i^2 \frac{D_n}{L_n N_A} (e^{V/V_T} - 1)$	
Saturation current (A)	$I_s = A q n_i^2 \left(\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right)$	
I - V relationship	$I = I_s (e^{V/V_T} - 1)$	
Minority-carrier lifetime (s)	$\tau_p = L_p^2/D_p \quad \tau_n = L_n^2/D_n$	$L_p, L_n = 1 \mu\text{m to } 100 \mu\text{m}$ $\tau_p, \tau_n = 1 \text{ ns to } 10^4 \text{ ns}$
Minority-carrier charge storage (coulomb)	$Q_p = \tau_p I_p \quad Q_n = \tau_n I_n$ $Q = Q_p + Q_n = \tau_T I$	
Depletion capacitance (F)	$C_{p0} = A \sqrt{\left(\frac{\epsilon_s q}{2} \right) \left(\frac{N_A N_D}{N_A + N_D} \right) \frac{1}{V_0}}$ $C_j = C_{p0} / \left(1 + \frac{V_R}{V_0} \right)^m$	$m = \frac{1}{3} \text{ to } \frac{1}{2}$
Diffusion capacitance (F)	$C_d = \left(\frac{\tau_T}{V_T} \right) I$	