

---

ENE 104

# Electric Circuit Theory

---



## Lecture 08: The RLC Circuit (cont.)

---

**Week #9 : Dejwoot KHAWPARISUTH**

office: CB40906 Tel: 02-470-9065

Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)


<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

# Objectives : Ch9

---

- the characteristic damping factor and resonant frequency for both **series** and **parallel** RLC circuits
- **overdamped**, **critically** damped, and **underdamped** response
- the complete response
- op amps

# Summary:

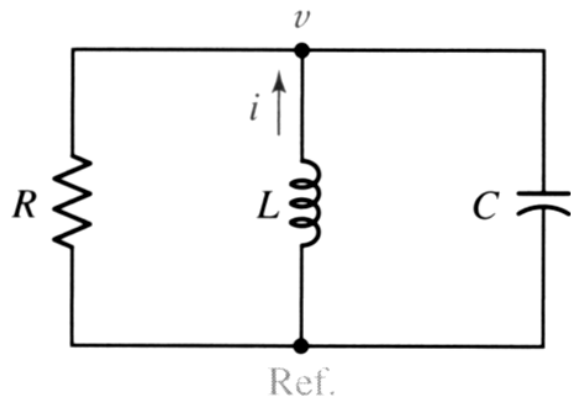


$$\alpha = \frac{1}{2RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Damping	Natural Response Equations	Coefficient Equations Overdamped
Overdamped ( $\alpha > \omega_0$ )	$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$x(0) = A_1 + A_2$ $\left. \frac{dx}{dt} \right _{t=0^+} = A_1 s_1 + A_2 s_2$
Critically damped ( $\alpha = \omega_0$ )	$x(t) = e^{-\alpha t} (B_1 t + B_2)$	$x(0) = B_2$ $\left. \frac{dx}{dt} \right _{t=0^+} = B_1 - \alpha B_2$
Underdamped ( $\alpha < \omega_0$ )	$x(t) = e^{-\alpha t} (C_1 \cos \omega_d t + C_2 \sin \omega_d t)$ Note: $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$x(0) = C_1$ $\left. \frac{dx}{dt} \right _{t=0^+} = -\alpha C_1 + \omega_d C_2$

# Example:

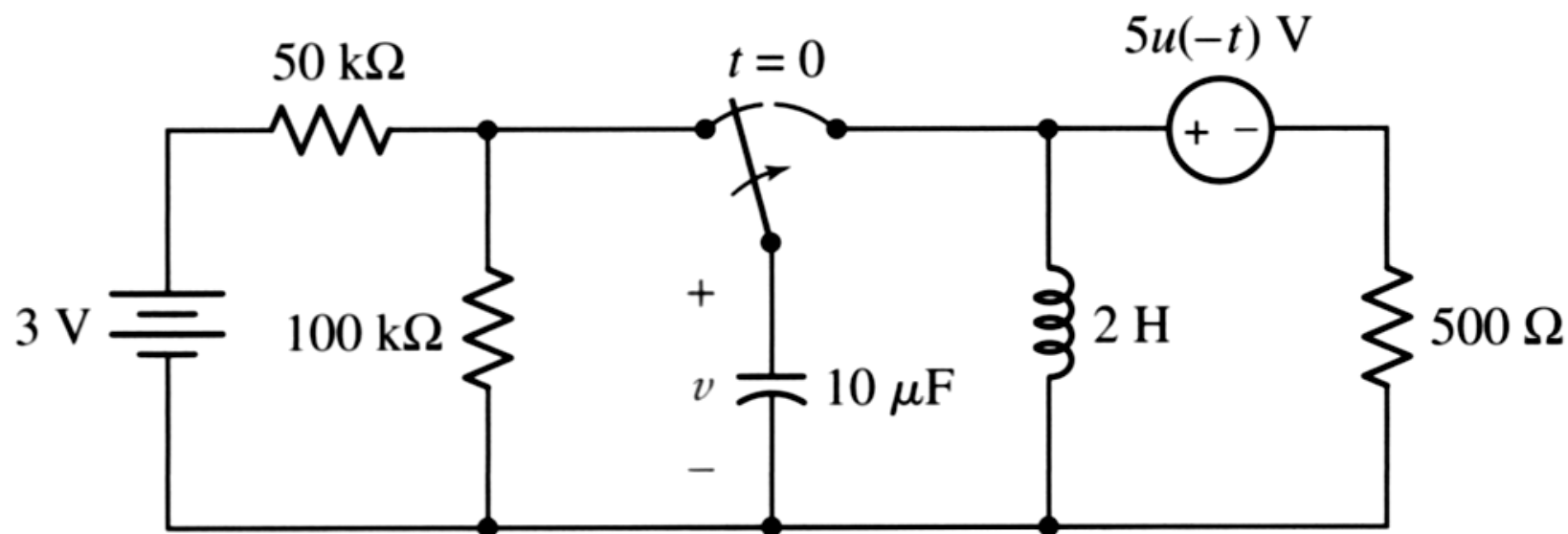


- Find
- $\frac{dv}{dt}$  at  $t = 0^+$
  - $v(t)$  at  $t = 1$  ms.
  - $t_0$ , the first value of  $t$  greater than zero at which  $v = 0$

# Example:

From

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

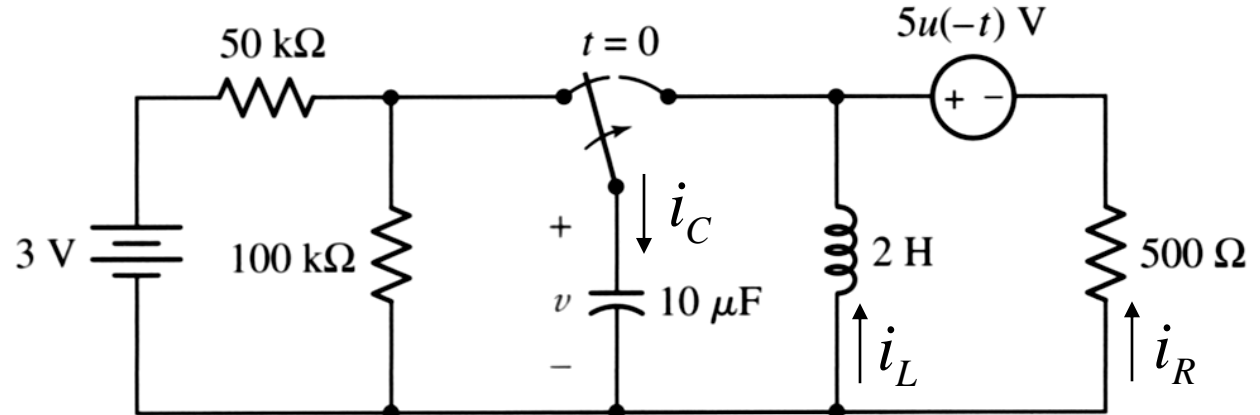

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{i_C(t=0^+)}{C} = \frac{i_L(0^+) + i_R(0^+)}{C} = \frac{i_L(0^-) + i_R(0^+)}{C} \text{ V/s.}$$

$$i_L(0^-) = \frac{-5 \text{ V}}{500 \Omega} = -0.01 \text{ A.}$$

$$i_R(0^+) = \frac{-v_C(0^+)}{500 \Omega} = \frac{-v_C(0^-)}{500 \Omega} = \frac{-2 \text{ V}}{500 \Omega} = -0.004 \text{ A.}$$

$$\longrightarrow \left. \frac{dv}{dt} \right|_{t=0^+} = -1400 \text{ V/s.}$$


# Example: $v(t=1\text{ms.})$

$$\alpha = \frac{1}{2RC}$$

$$= \frac{1}{2 \cdot 500\Omega \cdot 10\mu F} = 100 \text{ s}^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$
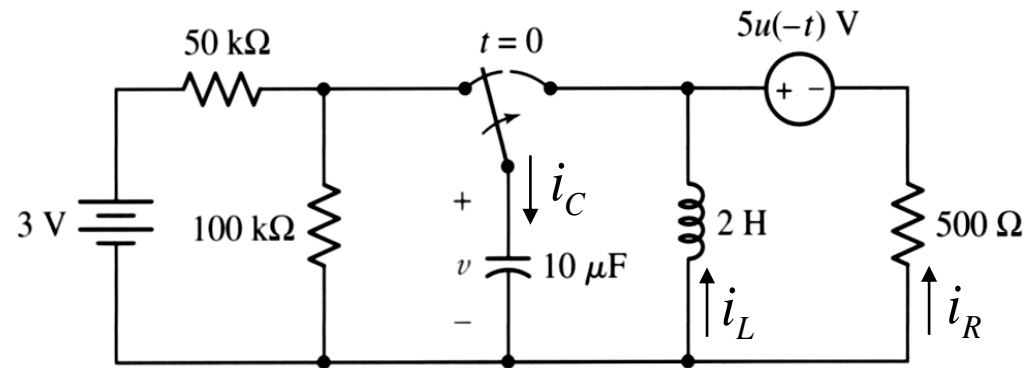
$$= \frac{1}{\sqrt{2H \cdot 10\mu F}} = 223.6 \text{ rad/s}$$




$$\alpha < \omega_0$$



$$v(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

# Example: $v(t=1\text{ms.})$

$$\alpha < \omega_0$$

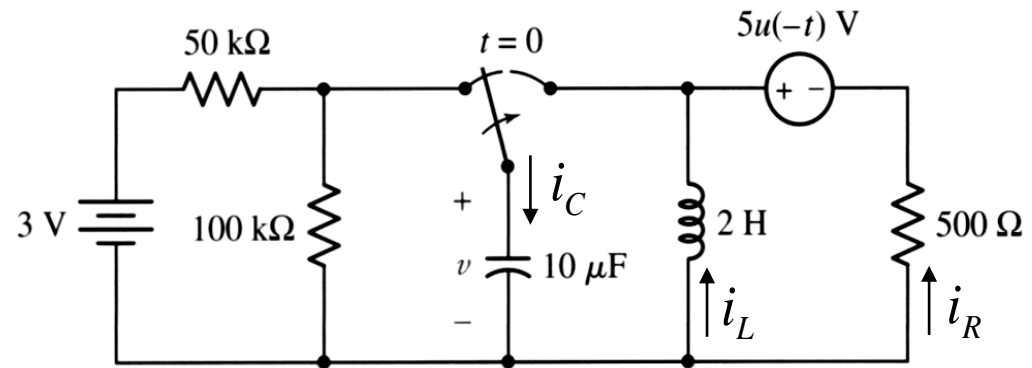

An underdamped C/T

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 200 \text{ rad/s}$$

$$\longrightarrow v(t) = e^{-100t} (B_1 \cos 200t + B_2 \sin 200t)$$

$$\text{At } t = 0, \Rightarrow x(0) = B_1 \dots (*) \quad ; B_1 = v(0^+) = 2$$

And evaluating the derivative at  $t = 0$ ,

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2 \dots (**)$$

# Example: $v(t=1\text{ms.})$

---

$$v(t) = e^{-100t} (B_1 \cos 200t + B_2 \sin 200t) \quad ; B_1 = 2$$

From  $i_C(t) = C \frac{dv_C(t)}{dt}$


$$\left. \frac{dv}{dt} \right|_{t=0^+} = -1400 = -100B_1 + 200B_2 \quad \Rightarrow B_2 = -6$$

$$\Rightarrow v(t) = e^{-100t} (2 \cos 200t - 6 \sin 200t)$$

$$\therefore v(t = 1\text{ms.}) = 0.695 \quad V.$$




# The Source-Free Series RLC C/T: Page 9

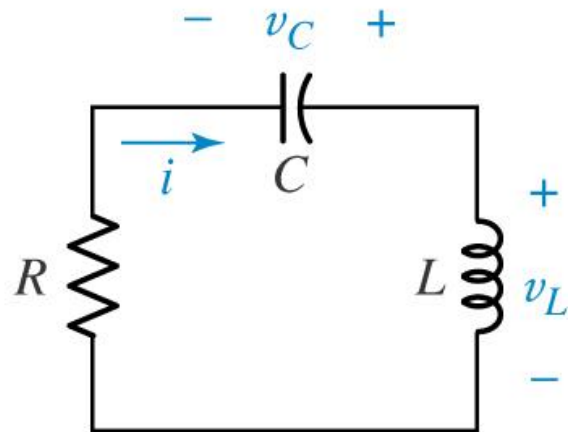

(a)

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int_{t_0}^t i dt' - v_C(t_0) = 0$$
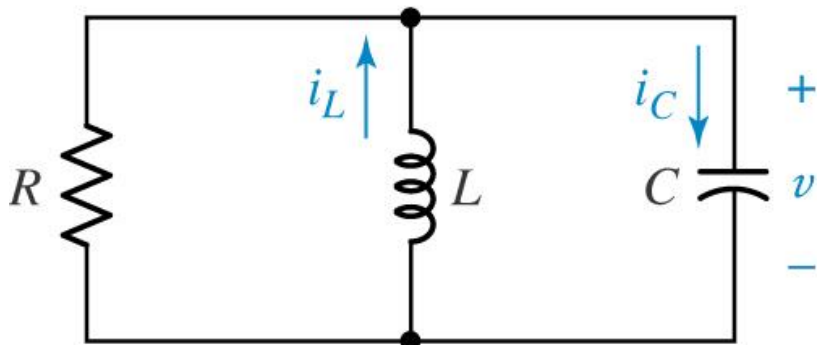
$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$



(b)

$$C \frac{dv}{dt} + \frac{1}{R} v + \frac{1}{L} \int_{t_0}^t v dt' - i_L(t_0) = 0$$


$$C \frac{d^2 v}{dt^2} + \frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

# The Series RLC Response:

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

The overdamped response:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

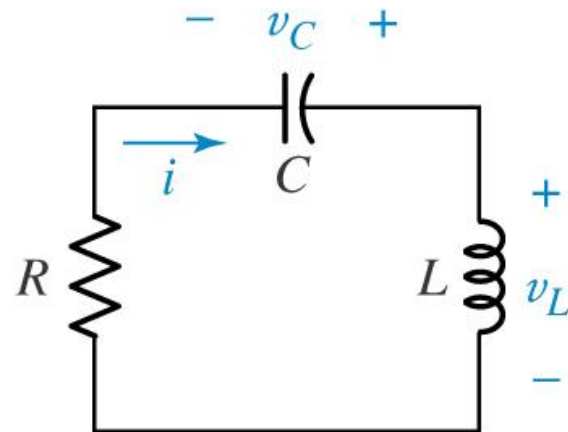

where

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

thus

$$\alpha = \frac{R}{2L} \quad \text{and} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

# The Series RLC Response:

$$L \frac{d^2 i}{dt^2} + R \frac{di}{dt} + \frac{1}{C} i = 0$$

The overdamped response:

$$i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


The critically damped response:

$$i(t) = e^{-\alpha t} (A_1 t + A_2)$$

The underdamped response:

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

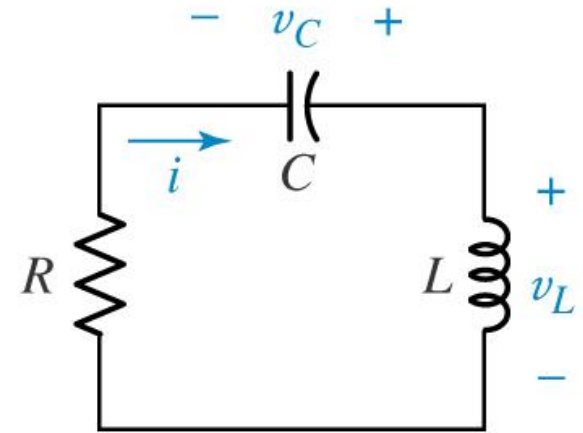
where  $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$



$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{R}{2L}, \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

# Summary:

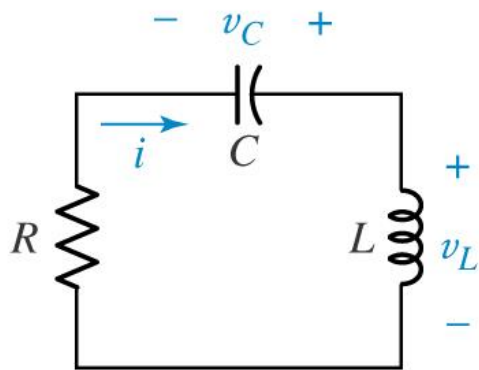


$$\alpha = \frac{R}{2L} \qquad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

Damping	Natural Response Equations	Coefficient Equations Overdamped
Overdamped ( $\alpha > \omega_0$ )	$x(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$	$x(0) = A_1 + A_2$ $\left. \frac{dx}{dt} \right _{t=0^+} = A_1 s_1 + A_2 s_2$
Critically damped ( $\alpha = \omega_0$ )	$x(t) = e^{-\alpha t} (B_1 t + B_2)$	$x(0) = B_2$ $\left. \frac{dx}{dt} \right _{t=0^+} = B_1 - \alpha B_2$
Underdamped ( $\alpha < \omega_0$ )	$x(t) = e^{-\alpha t} (C_1 \cos \omega_d t + C_2 \sin \omega_d t)$ Note: $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$x(0) = C_1$ $\left. \frac{dx}{dt} \right _{t=0^+} = -\alpha C_1 + \omega_d C_2$


# Practice: 9.5

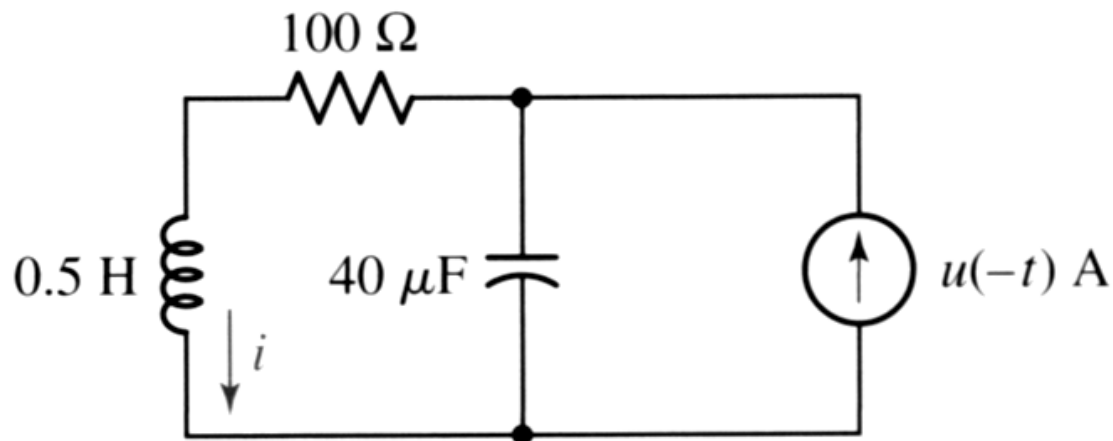

**Find**

- $\alpha$
- $\omega_0$
- $i(0^+)$
- $\left. \frac{di}{dt} \right|_{t=0^+}$  at  $t = 0^+$
- $i(12\text{ms})$

# Practice :

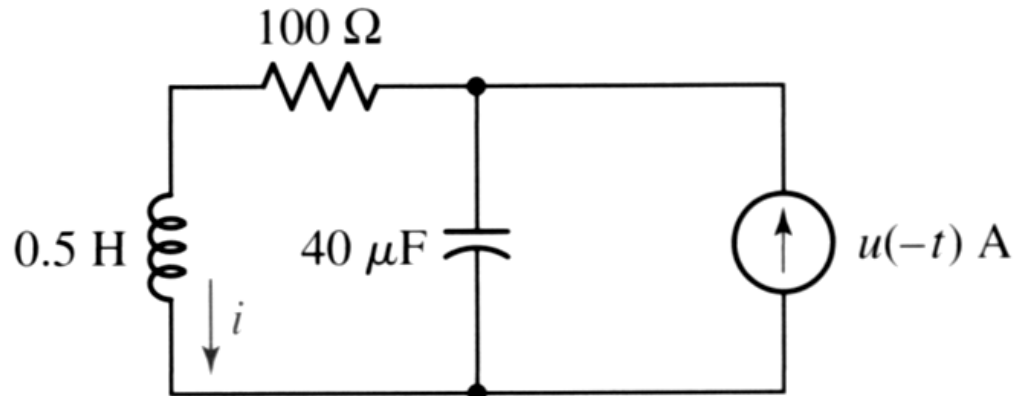


$$\begin{aligned}\alpha &= \frac{R}{2L} \\ &= \frac{100\Omega}{2 \cdot 0.5H} = 100 \text{ s}^{-1}\end{aligned}$$

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{0.5H \cdot 40\mu F}} = 223.6 \text{ rad/s}\end{aligned}$$

$$i(0^+) = i_L(0^-) = 1 \text{ A.}$$

# Practice :

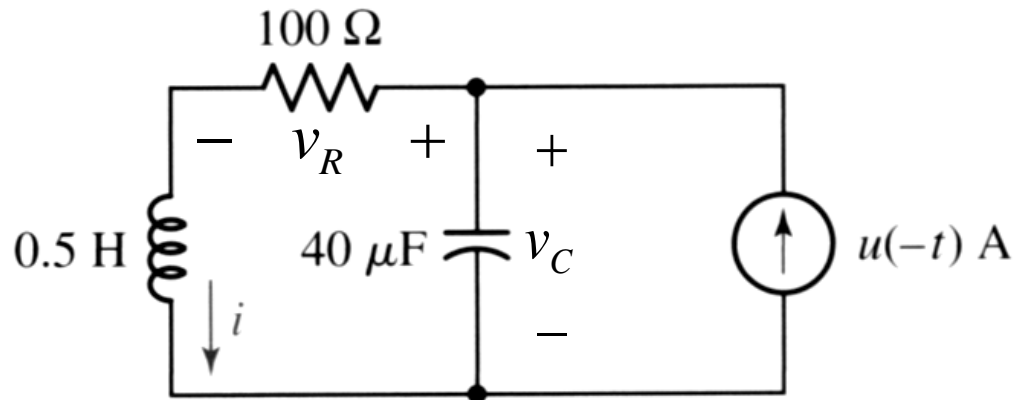

$$\alpha = 100 \text{ s}^{-1}$$


$$\omega_0 = 223.6 \text{ rad/s}$$

$$i(0^+) = 1 \text{ A.}$$

from  $v_L(t) = L \frac{di_L}{dt}$

$$\left. \frac{di}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{v_C(0^+) - v_R(0^+)}{L} = \frac{100 - 100}{L} = 0$$

# Practice : $i(t=12\text{ms.})$

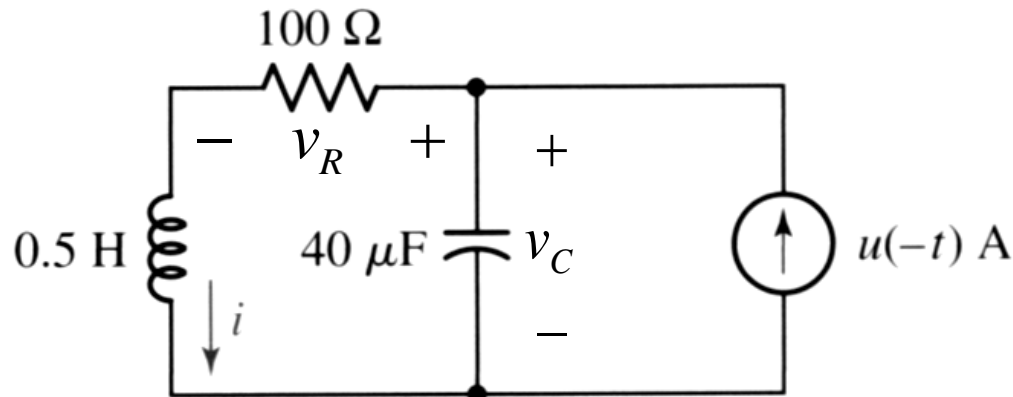

$$\alpha = 100 \text{ s}^{-1}$$

$$\omega_0 = 223.6 \text{ rad / s}$$

$$i(0^+) = 1 \text{ A.}$$

$$\alpha < \omega_0$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = 0$$

An underdamped C/T


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 200 \text{ rad / s}$$

$$i(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\longrightarrow i(t) = e^{-100t} (B_1 \cos 200t + B_2 \sin 200t)$$



# Practice : $i(t=12\text{ms.})$

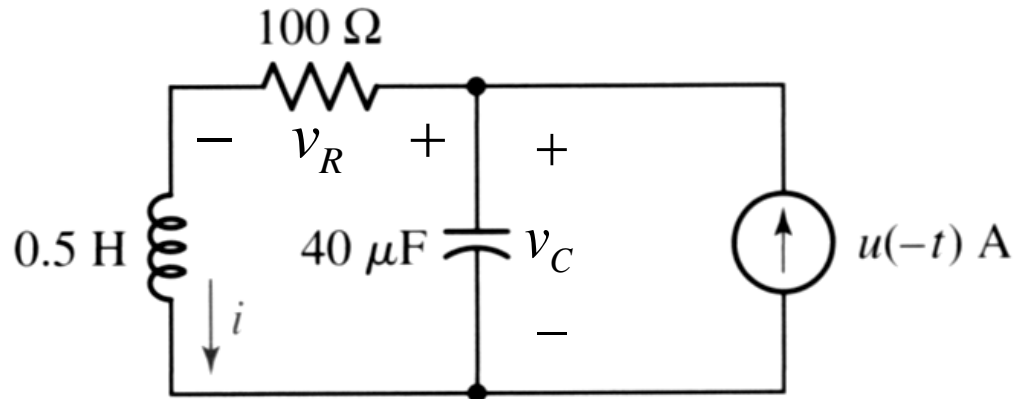

$$\alpha = 100 \text{ s}^{-1}$$

$$\omega_d = 200 \text{ rad/s}$$

$$i(0^+) = 1 \text{ A.}$$

$$\left. \frac{di}{dt} \right|_{t=0^+} = 0$$

$\alpha < \omega_0$  An underdamped C/T

$$x(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$


$$\Rightarrow x(0) = B_1 \dots (*)$$

$$\Rightarrow \left. \frac{dx}{dt} \right|_{t=0} = -\alpha B_1 + \omega_d B_2 \dots (**)$$

$$\therefore B_1 = i(0) = 1$$

$$\therefore B_2 = 0.5$$

# Practice : $i(t=12\text{ms.})$

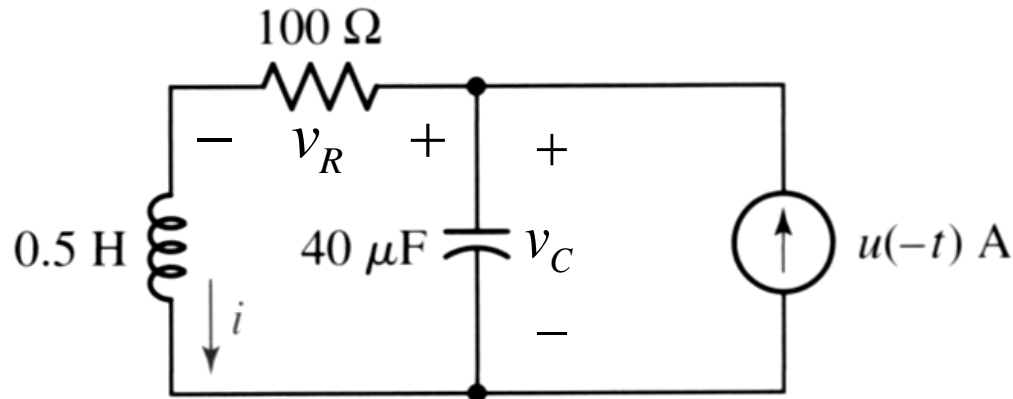

$$\alpha = 100 \quad s^{-1}$$

$$\omega_d = 200 \quad rad / s$$

$$B_1 = 1, B_2 = 0.5$$

$$\alpha < \omega_0$$

An underdamped C/T

$$x(t) = e^{-\alpha t} (B_1 \cos \omega_d t + B_2 \sin \omega_d t)$$

$$\longrightarrow i(t) = e^{-100t} (\cos 200t + 0.5 \sin 200t)$$

$$\therefore i(12\text{ms.}) = -0.1204 \quad A.$$

# The Complete Response:

---

The complete response

= a force response + a natural response

a force response:

$$v_f(t) = V_f$$

a natural response:

$$v_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$


The complete response:  $v(t) = V_f + A_1 e^{s_1 t} + A_2 e^{s_2 t}$

# Summary:


---

Damping	Step Response Equations	Coefficient Equations Overdamped
Overdamped ( $\alpha > \omega_0$ )	$x(t) = X_f + A_1' e^{s_1 t} + A_2' e^{s_2 t}$	$x(0) = X_f + A_1' + A_2'$ $\left. \frac{dx}{dt} \right _{t=0^+} = A_1' s_1 + A_2' s_2$
Critically damped ( $\alpha = \omega_0$ )	$x(t) = X_f + e^{-\alpha t} (B_1' t + B_2')$	$x(0) = X_f + B_2'$ $\left. \frac{dx}{dt} \right _{t=0^+} = B_1' - \alpha B_2'$
Underdamped ( $\alpha < \omega_0$ )	$x(t) = X_f + e^{-\alpha t} (C_1' \cos \omega_d t + C_2' \sin \omega_d t)$ Note: $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$	$x(0) = X_f + C_1'$ $\left. \frac{dx}{dt} \right _{t=0^+} = -\alpha C_1' + \omega_d C_2'$


# Example:

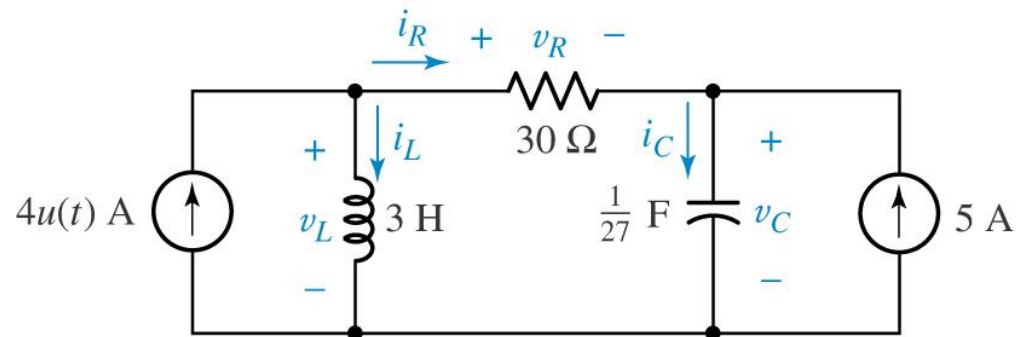

(a)

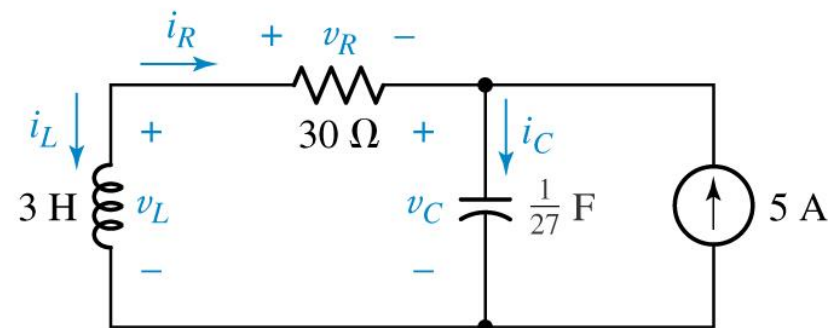

(b)


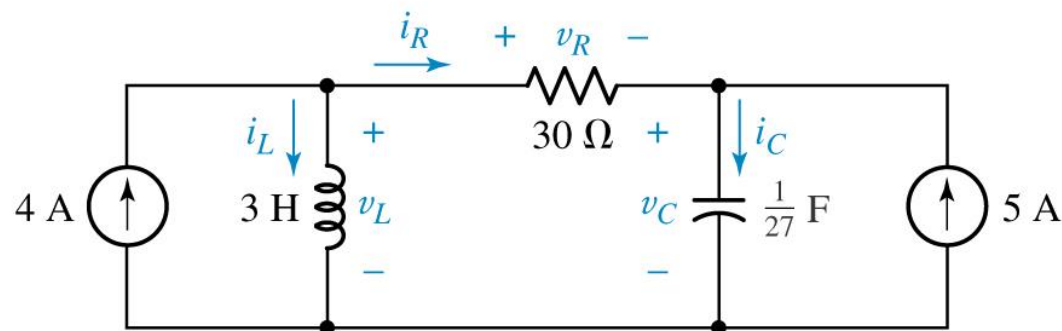


(c)

An RLC circuit that is used to illustrate several procedures by which the initial conditions may be obtained. The desired response is nominally taken to be  $v_C(t)$ .

# Example:

$t < 0$

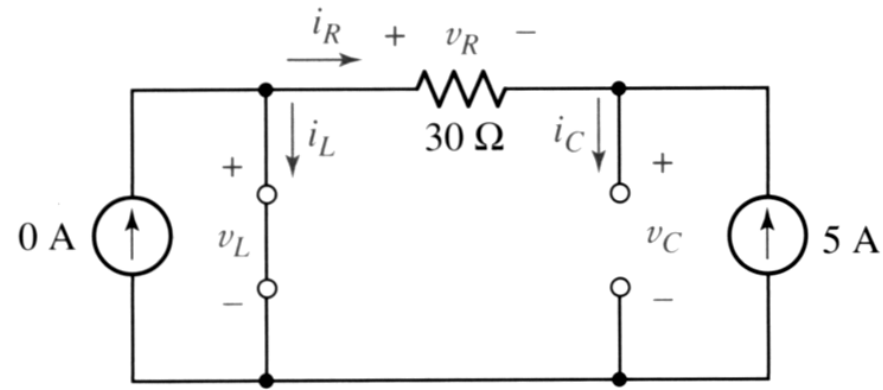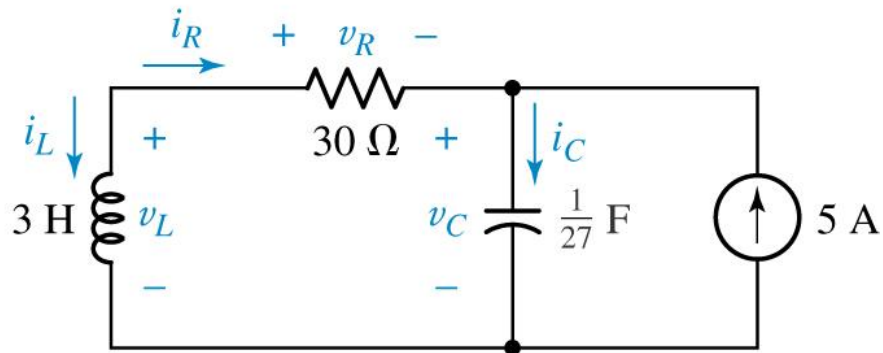



$$i_L(0^-) = 5A. \quad v_C(0^-) = (5A.) \cdot (30\Omega) = 150V.$$

$$i_R(0^-) = -5A. \quad v_R(0^-) = -150V.$$

$$i_C(0^-) = 0 \quad v_L(0^-) = 0$$

# Example:

$t \geq 0$

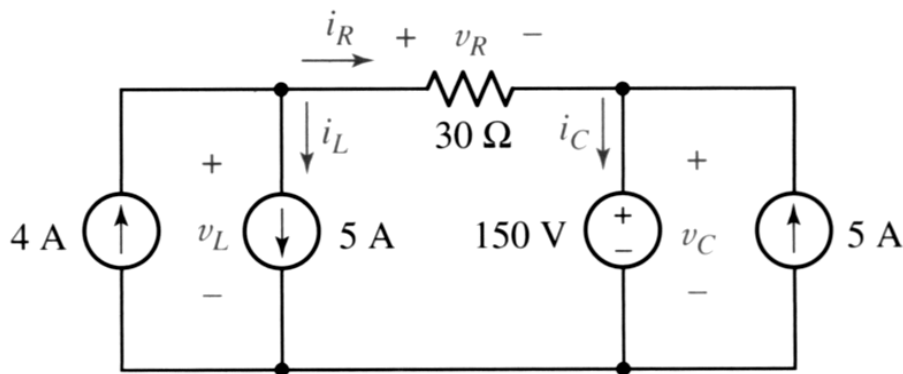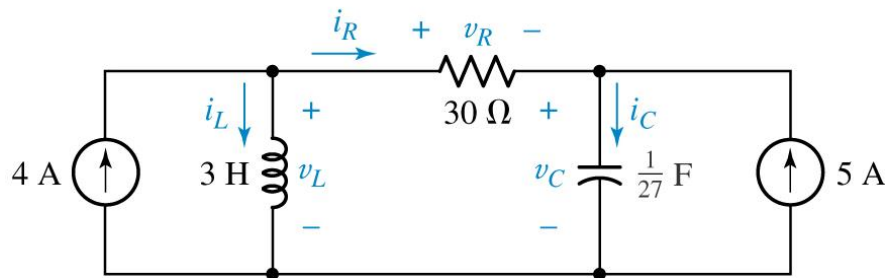

$$i_L(0^+) = i_L(0^-) = 5A.$$

$$i_R(0^+) = 4 - i_L(0^+) = -1A.$$

$$i_C(0^+) = 5 + i_R(0^+) = 4A.$$

$$v_C(0^+) = v_C(0^-) = 150V.$$

$$v_R(0^+) = i_R(0^+) \cdot 30\Omega = -30V.$$

$$v_L(0^+) = v_C(0^+) + v_R(0^+) = 120V.$$

# Example:

---

from  $v_L(t) = L \frac{di_L}{dt}$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{120}{3} = 40 \text{ A/s.}$$

from  $4 - i_L - i_R = 0 \Rightarrow 0 - \frac{di_L}{dt} - \frac{di_R}{dt} = 0$

therefore  $\left. \frac{di_R}{dt} \right|_{t=0^+} = -\frac{di_L}{dt} = -40 \text{ A/s.}$

from  $5 - i_C + i_R = 0 \Rightarrow 0 - \frac{di_C}{dt} + \frac{di_R}{dt} = 0$

therefore  $\left. \frac{di_C}{dt} \right|_{t=0^+} = \frac{di_R}{dt} = -40 \text{ A/s.}$



# Example:

---

from  $i_C(t) = C \frac{dv_C}{dt}$

$$\left. \frac{dv_C}{dt} \right|_{t=0^+} = \frac{i_C(0^+)}{C} = \frac{4}{\frac{1}{27}} = 108 \quad V/s.$$

from ...


$$\left. \frac{dv_R}{dt} \right|_{t=0^+} = -1200 \quad A/s.$$

from ...

$$\left. \frac{dv_L}{dt} \right|_{t=0^+} = -1092 \quad A/s.$$

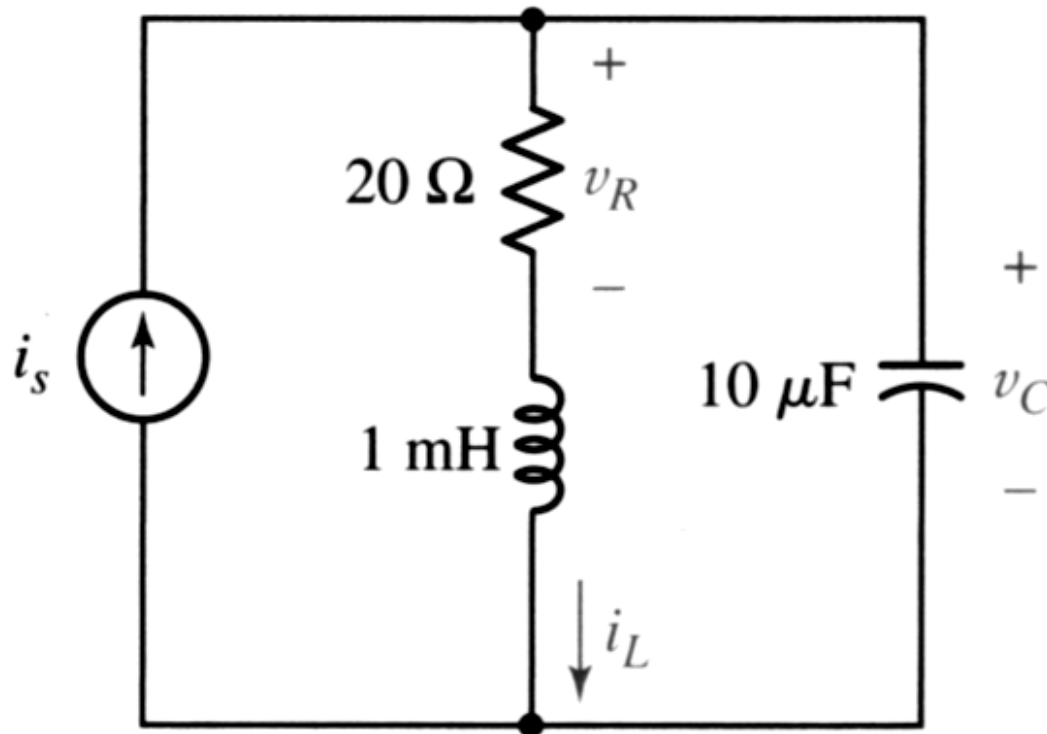
# Practice: 9.6

Let  $i_s = 10u(-t) - 20u(t)$  A. in Figure. Find (a)  $i_L(0^-)$ ; (b)  $v_C(0^+)$ ; (c)  $v_R(0^+)$ ; (d)  $i_{L,(\infty)}$ ; (e)  $i_L(0.1ms)$ .


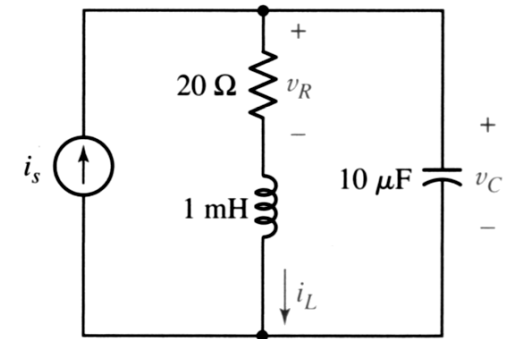
# Practice: 9.6

Let  $i_s = 10u(-t) - 20u(t)$  A. in Figure. Find (a)  $i_L(0^-)$ ; (b)  $v_C(0^+)$ ; (c)  $v_R(0^+)$ ; (d)  $i_{L,(\infty)}$ ; (e)  $i_L(0.1ms)$ .



(a)  $i_L(0^+) = i_L(0^-) = \underline{10 \text{ A}}$  ( $i_s = 10 \text{ A}, t < 0$ )

(b)  $v_C(0^+) = v_C(0^-) = 20(10) = \underline{200 \text{ V}}$

(c) Since the inductor current cannot change in zero time,  $v_R(0^+) = 20(10) = \underline{200 \text{ V}}$

(d)  $i_L(\infty) = \underline{-20 \text{ A}}$  due to  $i_s \rightarrow -20 \text{ A}$

(e)  $\alpha = \frac{R}{2L} = 10\,000 \text{ s}^{-1}$  and  $\omega_o = \frac{1}{\sqrt{LC}} = 10\,000 \text{ rad/s}$

$\therefore$  circuit is critically damped. So,

# Practice: 9.6

Let  $i_s = 10u(-t) - 20u(t)$  A. in Figure. Find (a)  $i_L(0^-)$ ; (b)  $v_C(0^+)$ ; (c)  $v_R(0^+)$ ; (d)  $i_{L,(\infty)}$ ; (e)  $i_L(0.1ms)$ .

$$i_L(t) = e^{-10^4 t} (A_1 t + A_2) - 20$$

Applying initial conditions,

$$i_L(0^+) = 10 = A_2 - 20 \quad [1]$$

and so  $A_2 = 30$


$$\frac{di_L}{dt} = -10^4 e^{-10^4 t} (A_1 t + A_2) + A_1 e^{-10^4 t}$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = -10^4 A_2 + A_1 = \frac{1}{L} [v_C(0^+) - v_R(0^+)]$$


$$\text{or } A_1 - 30 \times 10^4 = 10^3 (200 - 200)$$

$$\text{so } A_1 = 30 \times 10^4$$
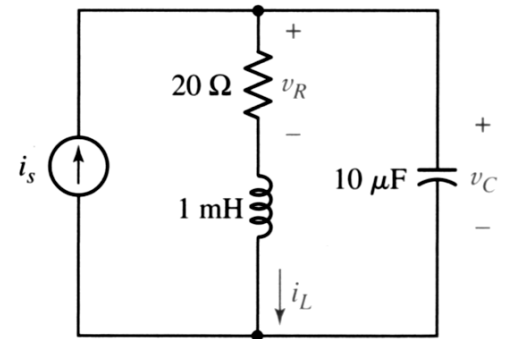
$$\begin{aligned} \text{Thus, } i_L(t) &= e^{-10^4 t} (30 \times 10^4 t + 30) - 20 \\ &= \underline{2.073 \text{ A}} \end{aligned}$$



# Practice: 9.7

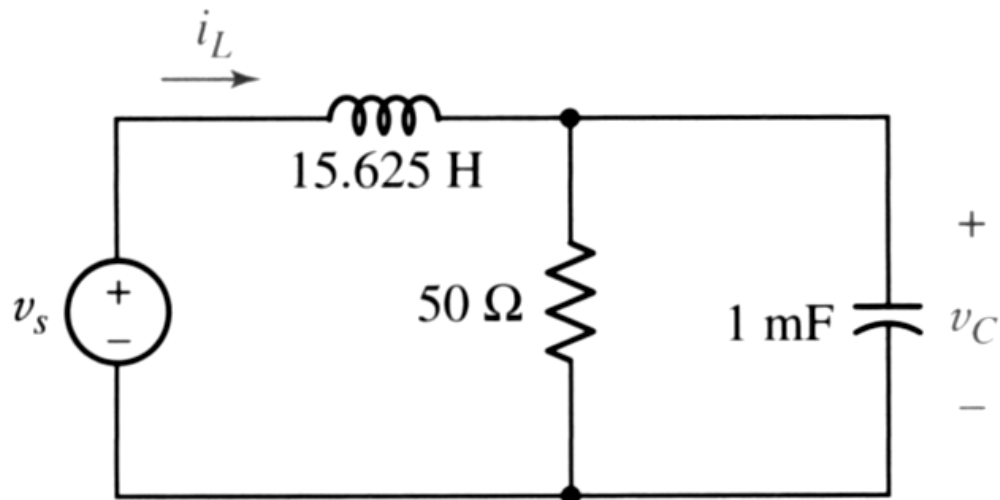

Let  $v_s = 10 + 20u(t)$  V.


Find: -  $i_L(0)$

-  $v_C(0)$

-  $i_{L,f}$

-  $i_L(0.1s.)$


# Practice :

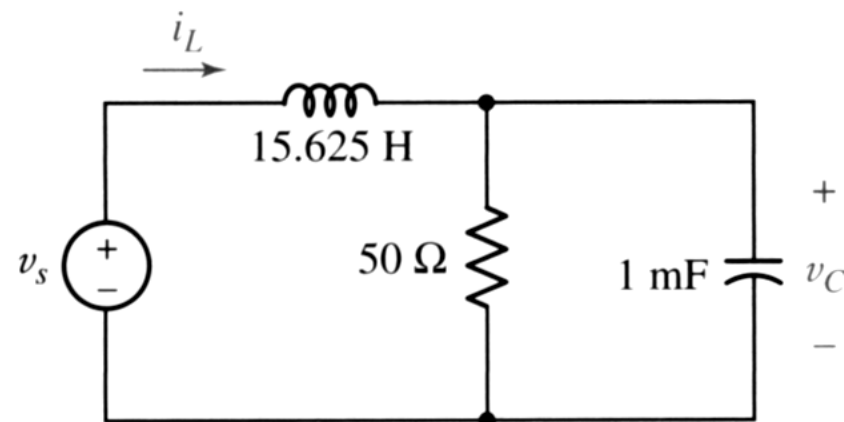

- Find:
- $i_L(0) = \frac{10V}{50\Omega} = 0.2 \text{ A.}$
  - $v_C(0) = i_L(0) \cdot 50\Omega = 10 \text{ V.}$
  - $i_{L,f} = \frac{10 + 20}{50\Omega} = 0.6 \text{ A.}$
  - $i_L(0.1s.) = \dots$

# Practice :

---

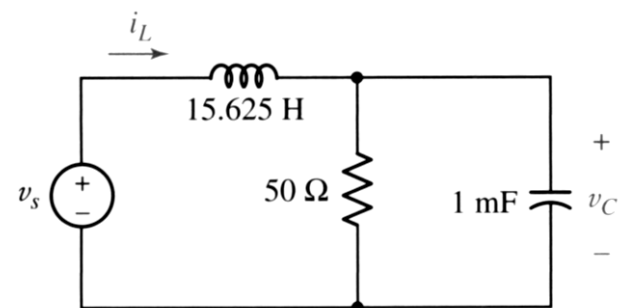

$$(d) \quad \alpha = \frac{1}{2RC} = 10 \text{ s}^{-1} \quad \text{and} \quad \omega_o = \frac{1}{\sqrt{LC}} = 8 \text{ rad/s}$$

Thus, the circuit is overdamped and


$$i_L(t) = Ae^{s_1 t} + Be^{s_2 t} + 0.6$$

where  $s_1 = -4 \text{ s}^{-1}$  and  $s_2 = -16 \text{ s}^{-1}$

$$i_L(0) = 0.2 = A + B + 0.6 \quad [1]$$

# Practice :

---

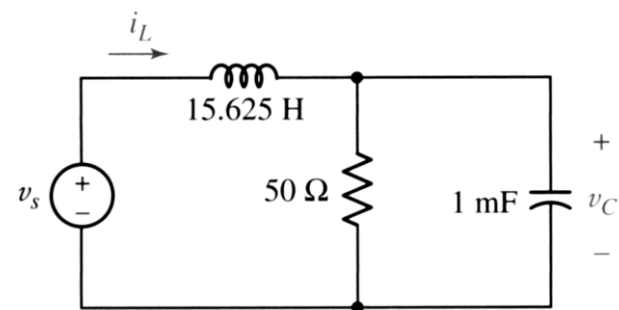

$$\frac{di_L}{dt} = -4Ae^{-4t} - 16Be^{-16t}$$

$$\text{so } \left. \frac{di_L}{dt} \right|_{t=0^+} = -4A - 16B = \frac{1}{L}[-v_C(0) + 30] \quad \text{or} \quad -4A - 16B = \frac{20}{15.625} \quad [2]$$

Solving Eqns. [1] and [2] simultaneously,  $A = -0.4267$  and  $B = 0.02667$



so that  $i_L(t) = -426.7e^{-4t} + 26.67e^{-16t} + 600 \text{ mA}$

Thus,  $i_L(0.1) = \underline{319.4 \text{ mA}}$



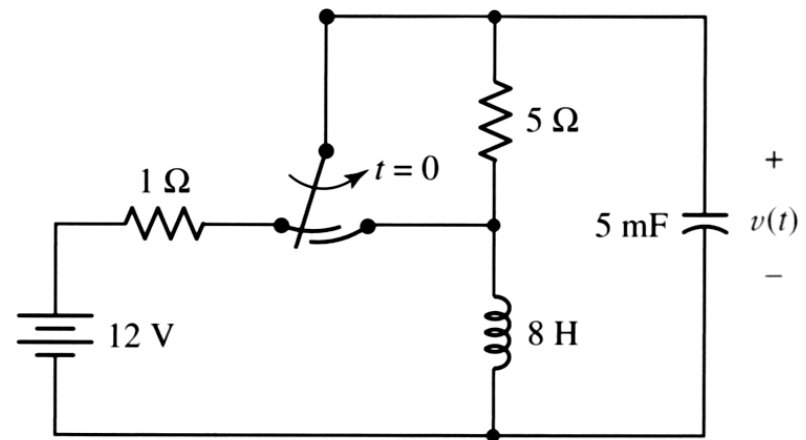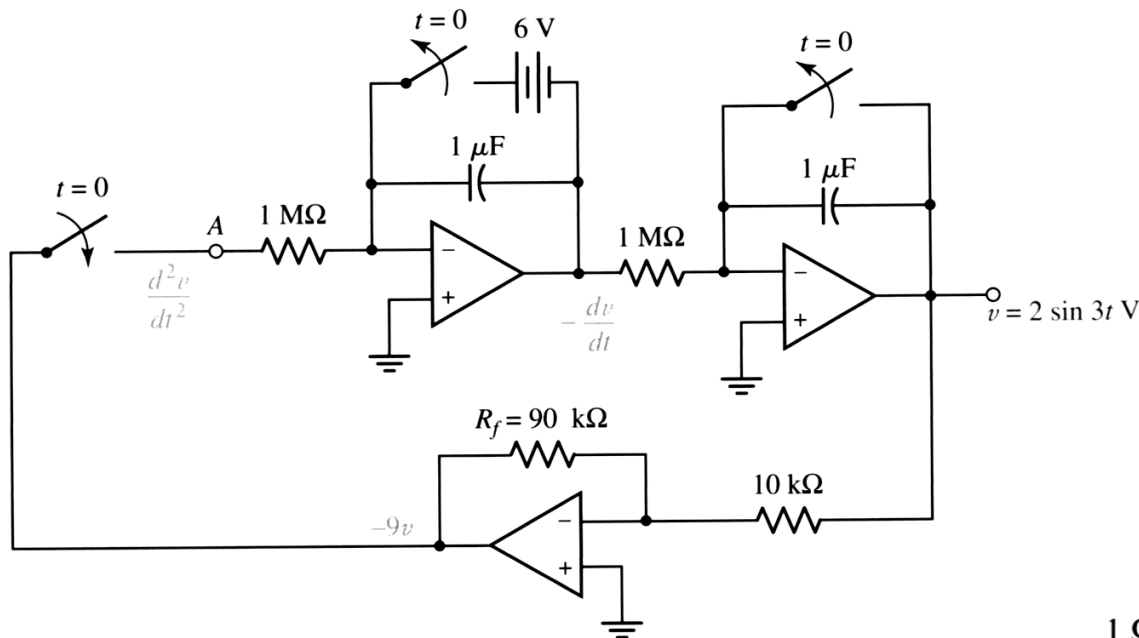
# Practice: 9.8

Give new values for  $R_f$  and the two initial voltages in the circuit on the left if the output represents the voltage  $v(t)$  in the circuit on the right.



# Practice: 9.8

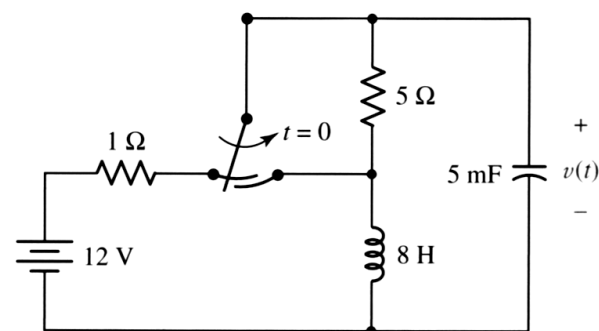

$$i_L(0^-) = \frac{12}{1+5} = 2 \text{ A} \quad = i_L(0^+)$$


$$v(0^-) = 12 \frac{5}{1+5} = 10 \text{ V} \quad = v(0^+)$$

- define  $i$  flowing out of “+” reference of  $v(t)$ .


$$v = L \frac{di}{dt} \quad \text{and} \quad i = -C \frac{dv}{dt} \quad \text{Thus, } v = -LC \frac{d^2v}{dt^2} \quad \text{or} \quad \frac{d^2v}{dt^2} = -25v$$

$$\left. \frac{dv}{dt} \right|_{t=0^+} = \frac{-i_L(0^+)}{C} = \frac{-2}{0.005} = -400 \text{ V/s}$$


# Practice: 9.8

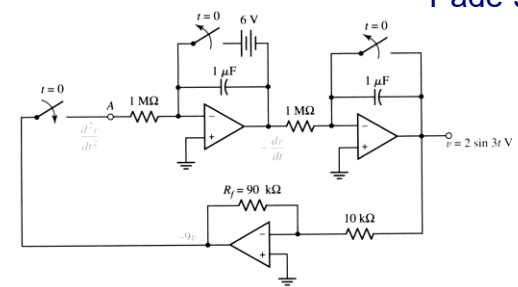

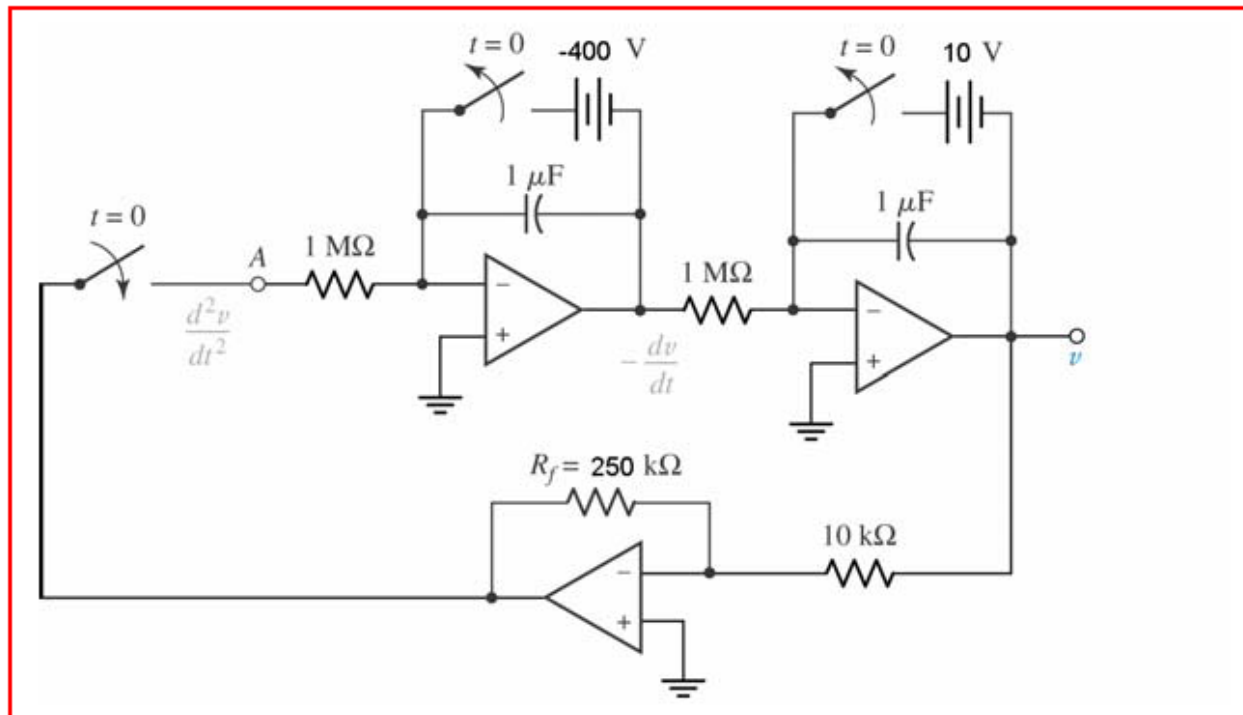so an initial voltage of +400 V is required where  $-6\text{ V}$  was needed previously. At the  $v(t)$  node, an initial voltage of +10 V is required where  $0\text{ V}$  was previously needed. Previously a gain of  $-9$  was obtained using  $R_1 = 10\text{ k}\Omega$  and  $R_f = 90\text{ k}\Omega$ . Now we require a gain of  $-25$ , so replace  $R_f$  with 250 kΩ.



# Example: Ex 42 Page 300

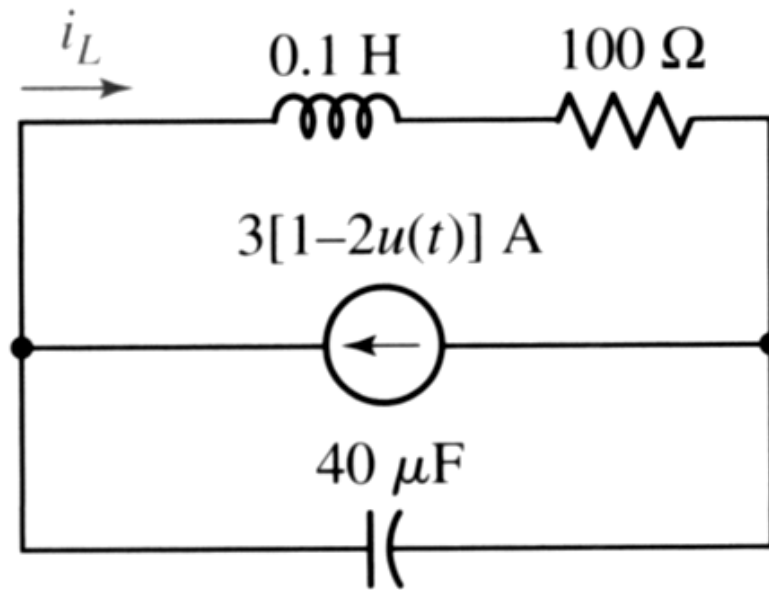


- Find -  $i_L(t)$
- At what instant of time after  $t = 0$  is  $i_L(t) = 0$ ?

Series RLC:

$$\begin{aligned}\alpha &= \frac{R}{2L} \\ &= \frac{100\Omega}{2 \cdot 0.1H} = 500 \quad s^{-1}\end{aligned}$$
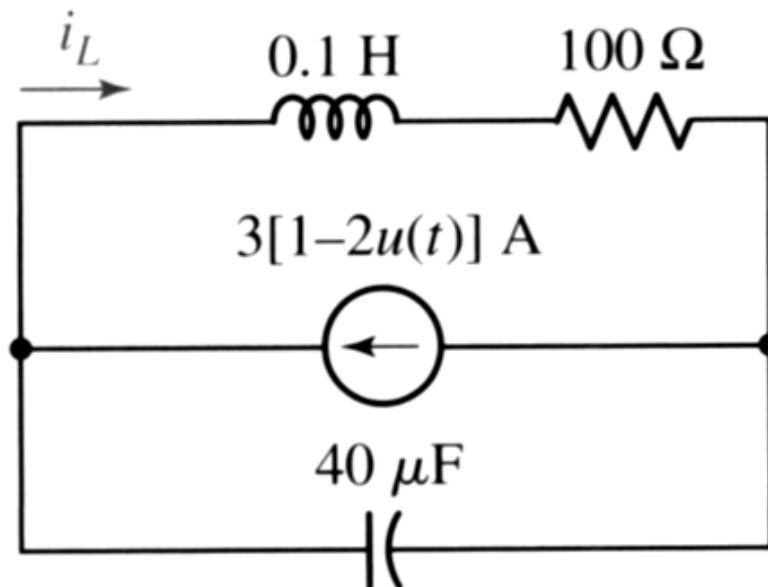
$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{LC}} \\ &= \frac{1}{\sqrt{0.1H \cdot 40\mu F}} = 500 \quad rad/s\end{aligned}$$




# Example: Ex 42 Page 300

Series RLC:

Critically damped

$$(\alpha = \omega_0)$$

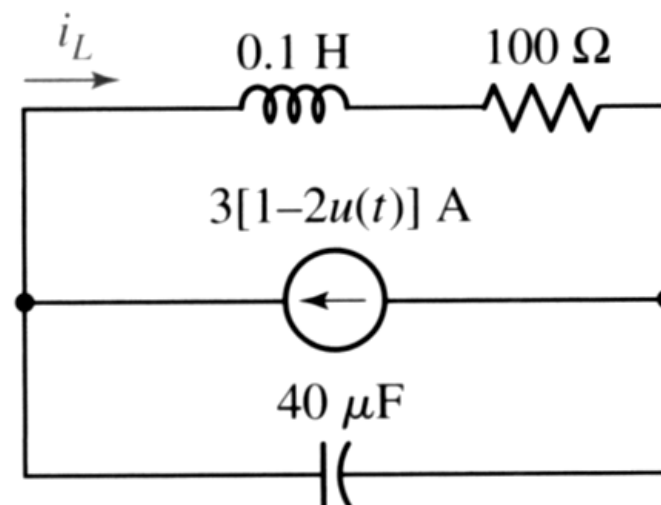

$$x(t) = X_f + e^{-\alpha t} (B_1' t + B_2')$$


$$x(0) = X_f + B_2'$$

$$\left. \frac{dx}{dt} \right|_{t=0^+} = B_1' - \alpha B_2'$$

Series RLC:

Critically damped

$$(\alpha = \omega_0)$$

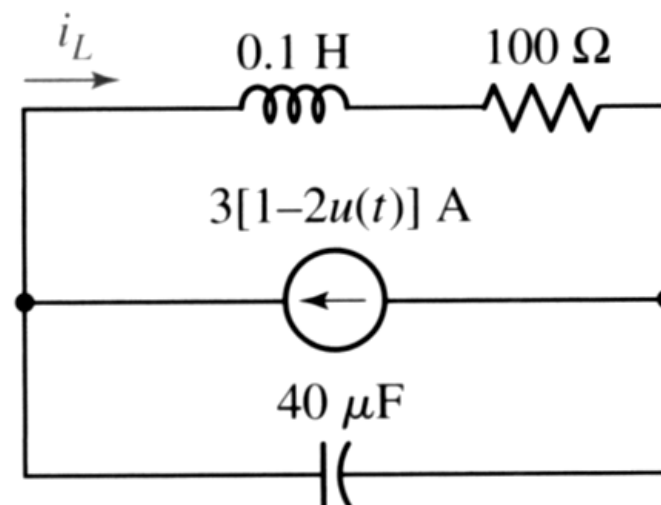

$$i_L(t) = I_f + e^{-\alpha t} (B_1' t + B_2')$$

$$i_L(0) = I_f + B_2'$$


$$\left. \frac{di_L}{dt} \right|_{t=0^+} = B_1' - \alpha B_2'$$

# Example: Ex 42 Page 300

Series RLC:

Critically damped

$$(\alpha = \omega_0)$$

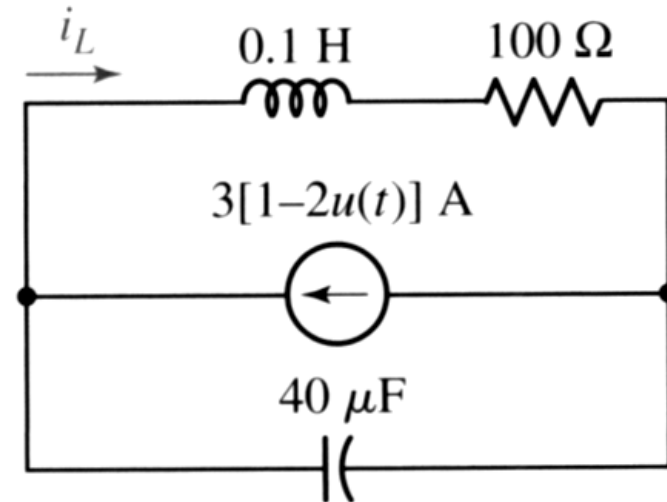

$$i_L(t) = I_f + e^{-\alpha t} (B_1' t + B_2')$$

$$i_L(0) = I_f + B_2'$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = B_1' - \alpha B_2'$$

$$i_L(0) = 3$$

$$I_f = 3(1 - 2) = -3$$

$$v_C(0) = 300$$




# Example: Ex 42 Page 300

Series RLC:

Critically damped

$$(\alpha = \omega_0)$$

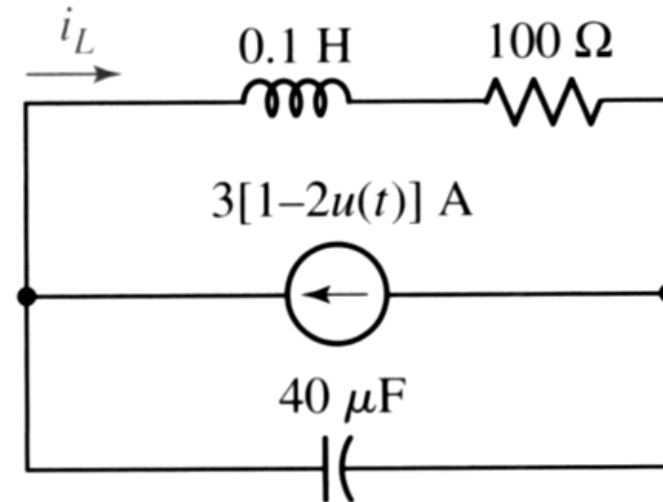

$$i_L(t) = I_f + e^{-\alpha t} (B_1' t + B_2')$$

$$i_L(0) = I_f + B_2'$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = B_1' - \alpha B_2'$$


$$\begin{aligned} \left. \frac{di}{dt} \right|_{t=0^+} &= \frac{v_L(0^+)}{L} \\ &= \frac{v_C(0^+) - v_R(0^+)}{L} \\ &= \frac{300 - 300}{L} = 0 \end{aligned}$$

# Example: Ex 42 Page 300

Series RLC:

Critically damped

$$(\alpha = \omega_0)$$

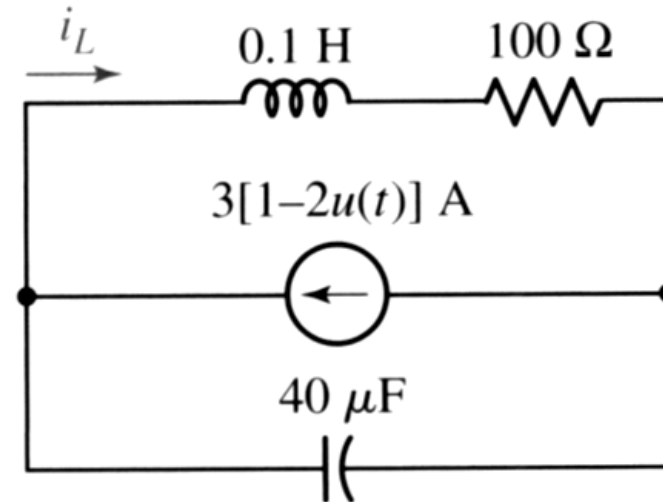

$$i_L(t) = I_f + e^{-\alpha t} (B_1' t + B_2')$$

$$i_L(0) = I_f + B_2'$$

$$B_2' = 6$$


$$B_1' = 3000$$

$$\left. \frac{di_L}{dt} \right|_{t=0^+} = B_1' - \alpha B_2'$$

Series RLC:

Critically damped


$$(\alpha = \omega_0)$$

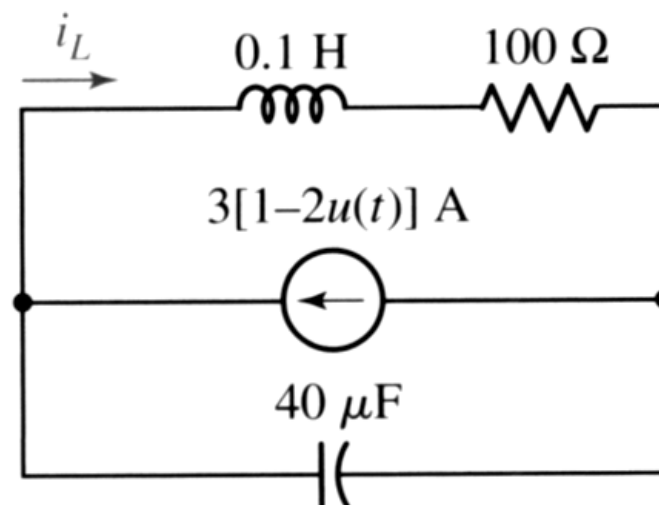

$$i_L(t) = -3 + e^{-500t} (3000t + 6), t > 0$$

$$\therefore i_L(t) = 3u(-t) + \{-3 + e^{-500t} (3000t + 6)\}u(t)$$

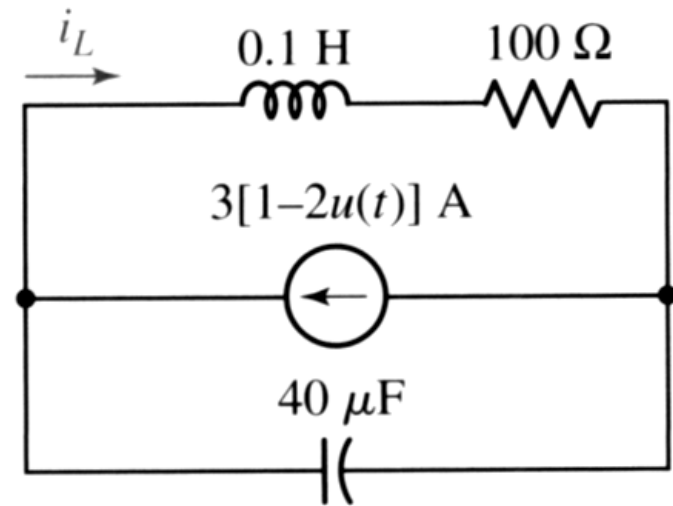Find - At what instant  
of time after  $t = 0$   
is  $i_L(t) = 0$ ?




From 
$$i_L(t) = -3 + e^{-500t}(3000t + 6), t > 0$$

$$i_L(t) = -3 + e^{-500t}(3000t + 6) = 0$$

$$\Rightarrow t_0 = 3.357 \text{ ms.}$$

# Example: Ex 43 Page 300

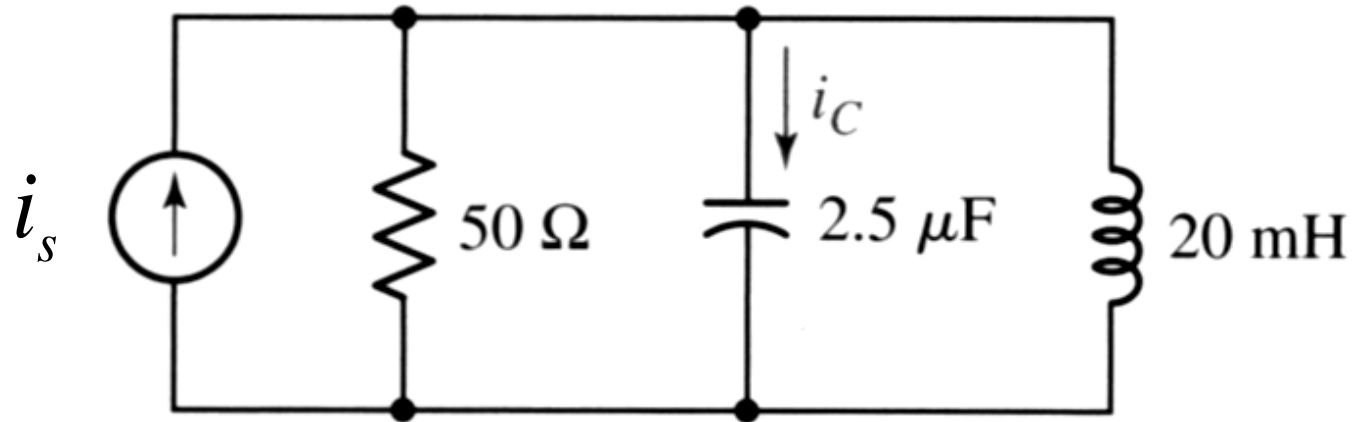


With  $i_s = 2[1 + u(t)]$  A. Find  $i_c(t)$

Parallel RLC:


$$\begin{aligned}\alpha &= \frac{1}{2RC} \\ &= \frac{10^6}{2 \cdot 50\Omega \cdot 2.5} = 4000 \text{ s}^{-1}\end{aligned}$$
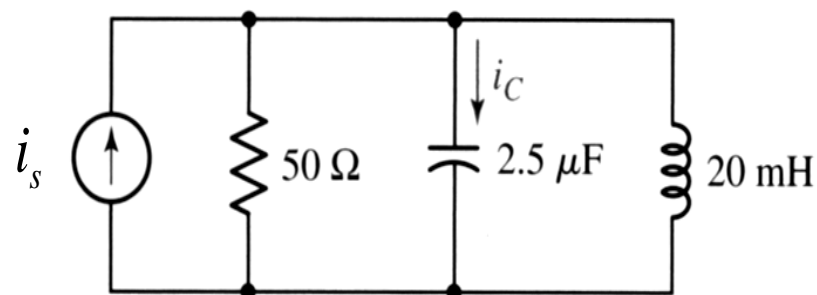
$$\begin{aligned}\omega_0^2 &= \frac{1}{LC} \\ &= \frac{1}{20\text{mH} \cdot 2.5\mu\text{F}} = 20 \times 10^6\end{aligned}$$



Parallel RLC:  
Underdamped

$$(\alpha < \omega_0)$$

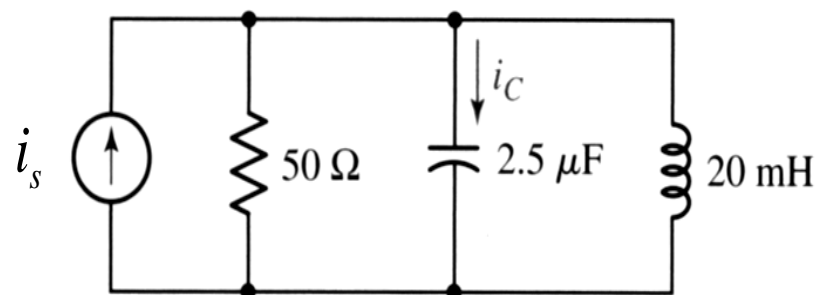


$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = 2000$$

$$i_L(0) = 2$$

$$I_{C,f} = 0$$

$$v_C(0) = 0$$

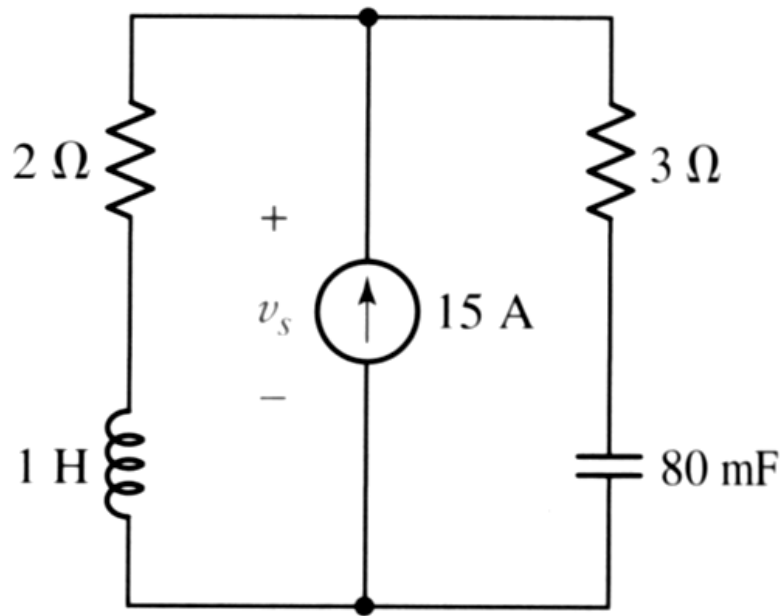

ในวงจร ตามรูป แหล่งจ่ายกระแส เปลี่ยนค่าจาก  $15 \text{ A}$ . เป็น  $22 \text{ A}$ .  
ทันทีทันใด ที่เวลา  $t = 0$  จงหา

$$v_s(0^-), v_s(0^+), v_s(\infty), \text{ and } v_s(3.4 \text{ s.})$$




$$v_s(0^-) = 15\text{ A} \cdot 2\Omega = 30$$


$$\begin{aligned} v_s(0^+) &= i_C(0^+) \cdot 3\Omega + v_C(0^+) \\ &= (22 - i_L(0^+)) \cdot 3\Omega + v_s(0^+) \\ &= 51 \end{aligned}$$

$$v_s(\infty) = 22\text{ A} \cdot 2\Omega = 44$$

$$v_s(3.4\text{ s.}) = \dots$$

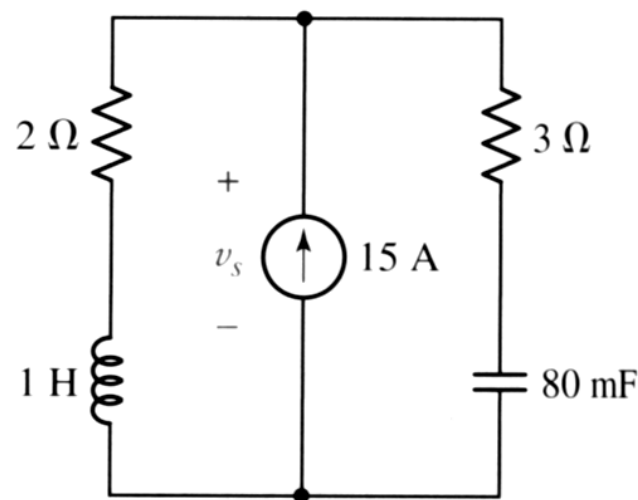

# Example: Final 2/47

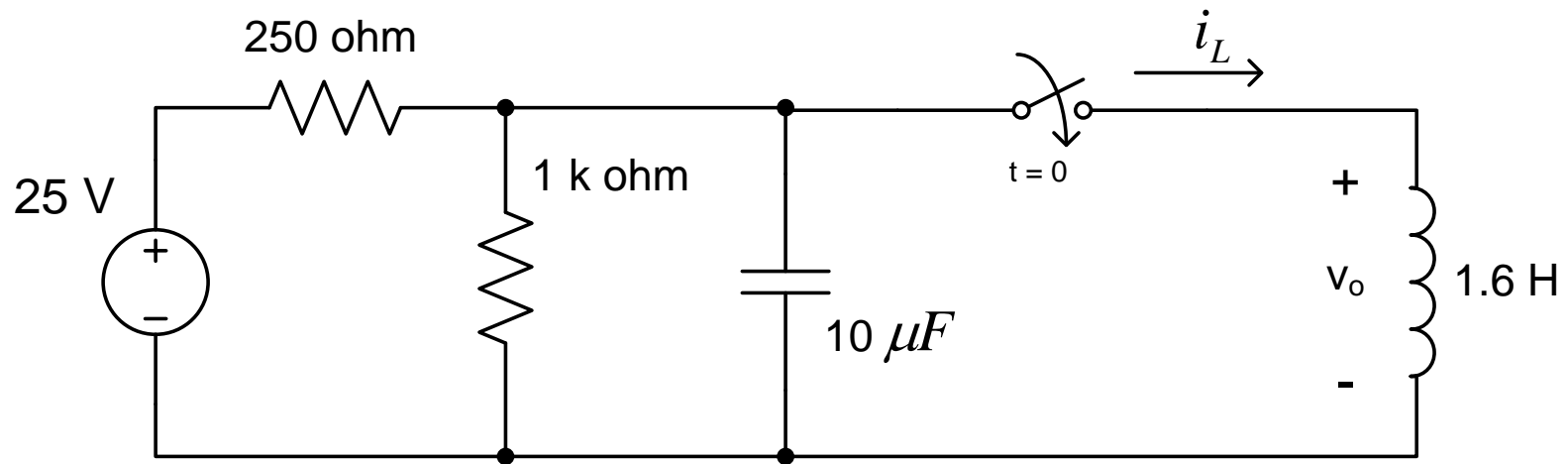

Find

$$i_L(t = 0^+) \quad \frac{dv_o(0^+)}{dt}$$

$$v_o(t = 0^+) \quad i_L(t)$$

$$\frac{di_L(0^+)}{dt} \quad v_o(t)$$


# Example: Final 2/47

$$i_L(t = 0^+) = i_L(0^-) = 0$$

$$v_o(t = 0^+) = v_C(0^-) = \frac{1000}{1000 + 250} \cdot 25 = 20$$

$$\frac{di_L(0^+)}{dt} = \frac{v_L(0^+)}{L} = \frac{20}{1.6} = 12.5$$
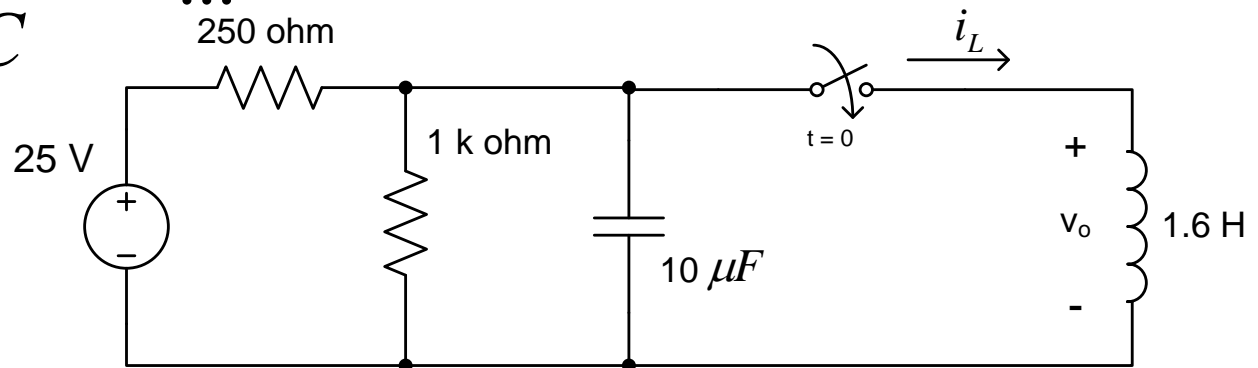
$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{C} = \dots$$




# Example: Final 2/47

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{C} = \dots$$

From 
$$\frac{v_C(0^+) - 25}{250} + \frac{v_C(0^+)}{1000} + i_C(0^+) = 0$$

$$\Rightarrow i_C(0^+) = 0$$

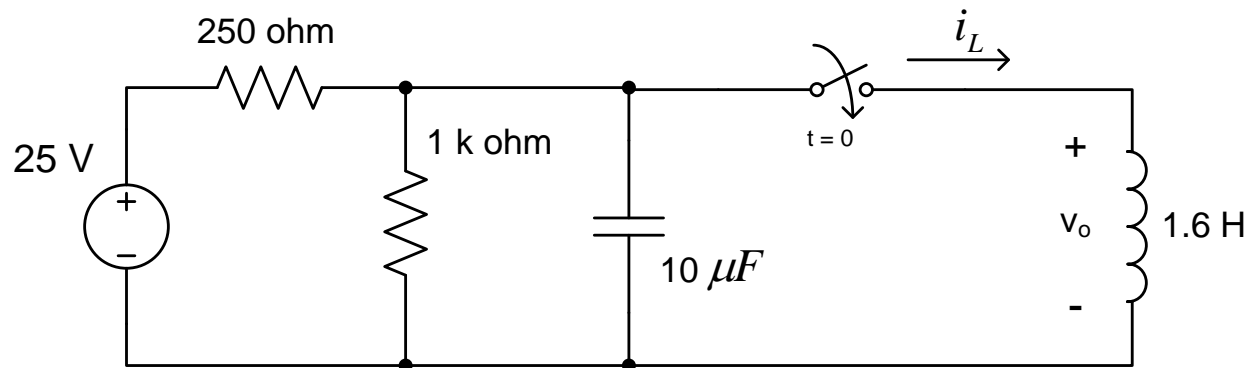

# Ex:

---

สำหรับวงจร RLC แบบขนานที่มี voltage response

$$v(t) = D_1 t e^{-4000t} + D_2 e^{-4000t}, t \geq 0$$

ค่า initial current ในตัว inductor มีค่า 5 mA, และ  
ค่า initial voltage ในตัวเก็บประจุมีค่า 25 V. โดยที่ค่า  
inductance ของตัว inductor มีขนาด 5 H. ให้หา

- a) ค่าของ R, C,  $D_1$ ,  $D_2$
- b)  $i_C(t)$  สำหรับ  $t > 0^+$

$$[a] \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = (4000)^2$$

$$\therefore C = \frac{1}{(16 \times 10^6)(5)} = 12.5 \text{ nF}$$

$$\frac{1}{2RC} = 4000$$

$$\therefore R = \frac{10^9}{(8000)(12.5)} = 10 \text{ k}\Omega$$

$$v(0) = D_2 = 25 \text{ V}$$

$$i_R(0) = \frac{25}{10} = 2.5 \text{ mA}$$

$$i_C(0) = -2.5 - 5 = -7.5 \text{ mA}$$


$$\frac{dv}{dt}(0) = D_1 - 4000D_2 = \frac{-7.5 \times 10^{-3}}{12.5 \times 10^{-9}} = -6 \times 10^5$$

$$\therefore D_1 = -6 \times 10^5 + 4000(25) = -5 \times 10^5$$

$$[b] \quad v = -5 \times 10^5 t e^{-4000t} + 25 e^{-4000t}$$

$$\frac{dv}{dt} = [20 \times 10^8 t - 6 \times 10^5] e^{-4000t}$$
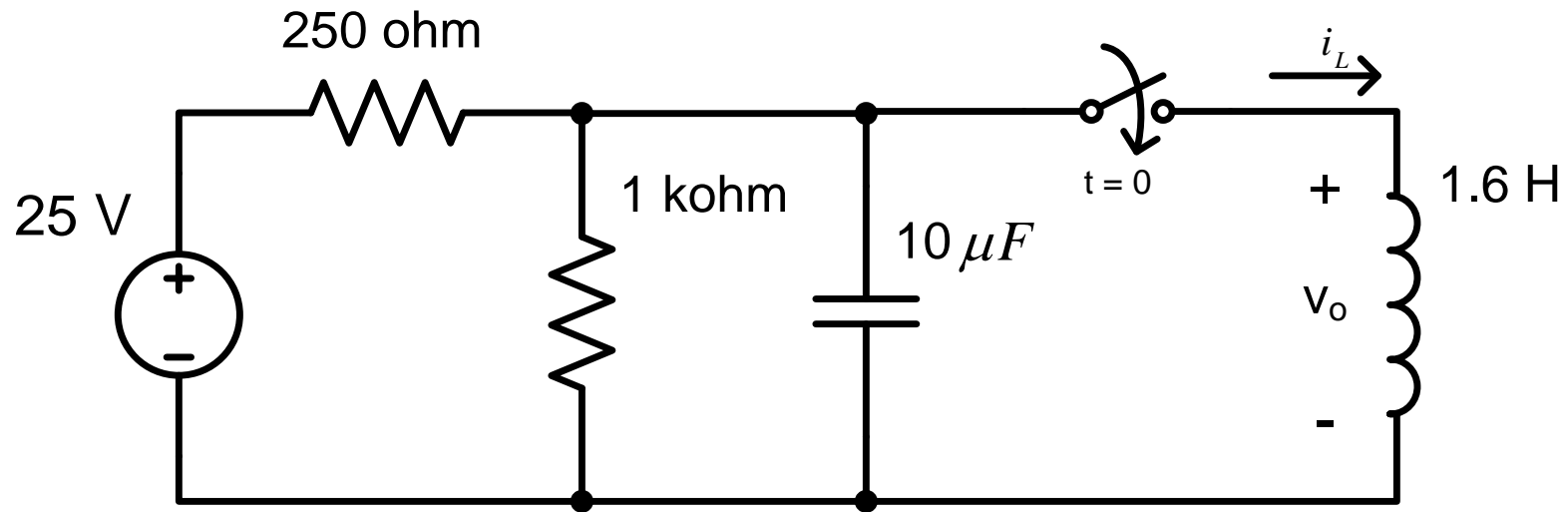
$$\begin{aligned} i_C &= C \frac{dv}{dt} = 12.5 \times 10^{-9} [20 \times 10^8 t - 6 \times 10^5] e^{-4000t} \\ &= (25,000t - 7.5) e^{-4000t} \text{ mA}, \quad t > 0 \end{aligned}$$



ให้หา

a)  $v_o(t)$  ,  $t \geq 0^+$

b)  $i_L(t)$  ,  $t \geq 0$




## Ex:


$$v_o(0^-) = v_o(0^+) = \frac{1000}{1250}(25) = 20 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

$t > 0$

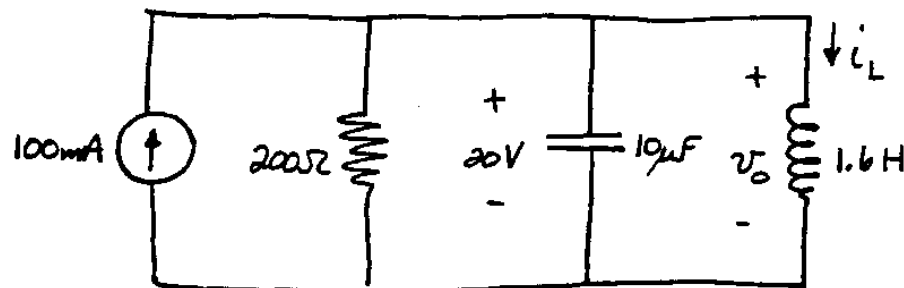
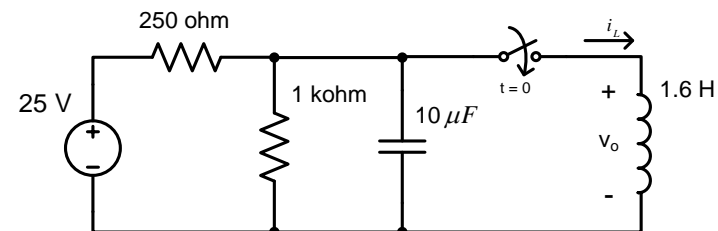
$$-100 + \frac{20}{0.2} + i_C(0^+) + 0 = 0; \quad \therefore i_C(0^+) = 0$$



$$\frac{1}{2RC} = \frac{10^6}{(400)(10)} = 250 \text{ nepers}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{10(1.6)} = 62,500$$

$$\therefore \alpha^2 = \omega_o^2 \text{ critically damped}$$

$$v_o = V_f + D'_1 t e^{-250t} + D'_2 e^{-250t}$$

$$V_f = 0$$


$$\frac{dv_o(0)}{dt} = -250D'_2 + D'_1 = 0$$

$$v_o(0^+) = 20 = D'_2$$

$$D'_1 = 250D'_2 = 5000 \text{ V/s}$$

$$\therefore v_o = 5000t e^{-250t} + 20e^{-250t} \text{ V}, \quad t \geq 0^+$$

## Ex:

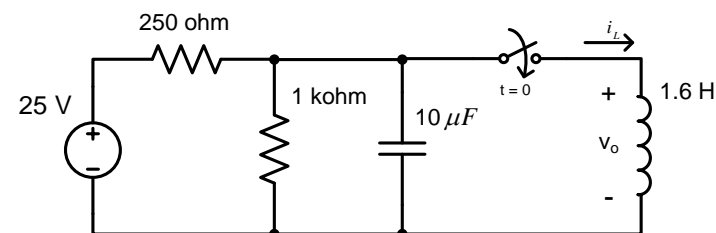

$$[b] \quad i_L = I_f + D'_3 t e^{-250t} + D'_4 e^{-250t}$$

$$i_L(0^+) = 0; \quad I_f = 100 \text{ mA}; \quad \frac{di_L(0^+)}{dt} = \frac{20}{1.6} = 12.5 \text{ A/s}$$

$$\therefore 0 = 100 + D'_4; \quad D'_4 = -100 \text{ mA};$$

$$-250D'_4 + D'_3 = 12.5; \quad D'_3 = -12.5 \text{ A/s}$$

$$\therefore i_L = 100 - 12,500t e^{-250t} - 100e^{-250t} \text{ mA} \quad t \geq 0$$



**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**