

---

ENE 104

# Electric Circuit Theory

---



## Lecture 09: Sinusoidal Steady-State Analysis

---

**Week #11 : Dejwoot KHAWPARISUTH**  
office: CB40906 Tel: 02-470-9065  
Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>

- sinusoidal functions
- impedance and admittance
- use phasors to determine the forced response of a circuit subjected to sinusoidal excitation
- Apply techniques using phasors

# Introduction:


## Characteristics of Sinusoids

$$v(t) = V_m \sin \omega t$$


$$f = \frac{1}{T}$$

$$\omega T = 2\pi$$

$$\omega = 2\pi f$$

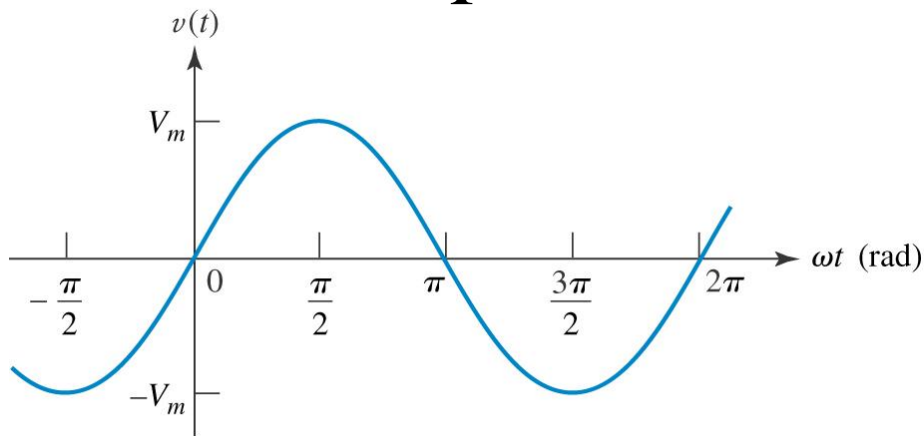

(a)

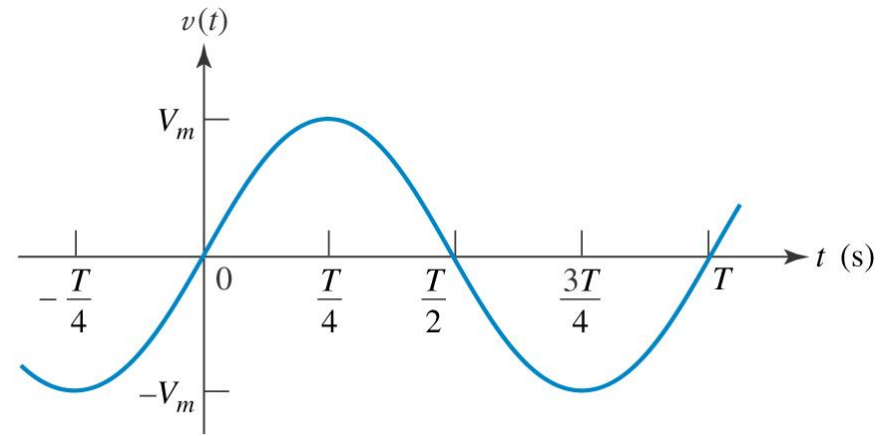


(b)

The sinusoidal function  $v(t) = V_m \sin \omega t$  is plotted

(a) versus  $\omega t$

and (b) versus  $t$ .


# Lagging and leading:

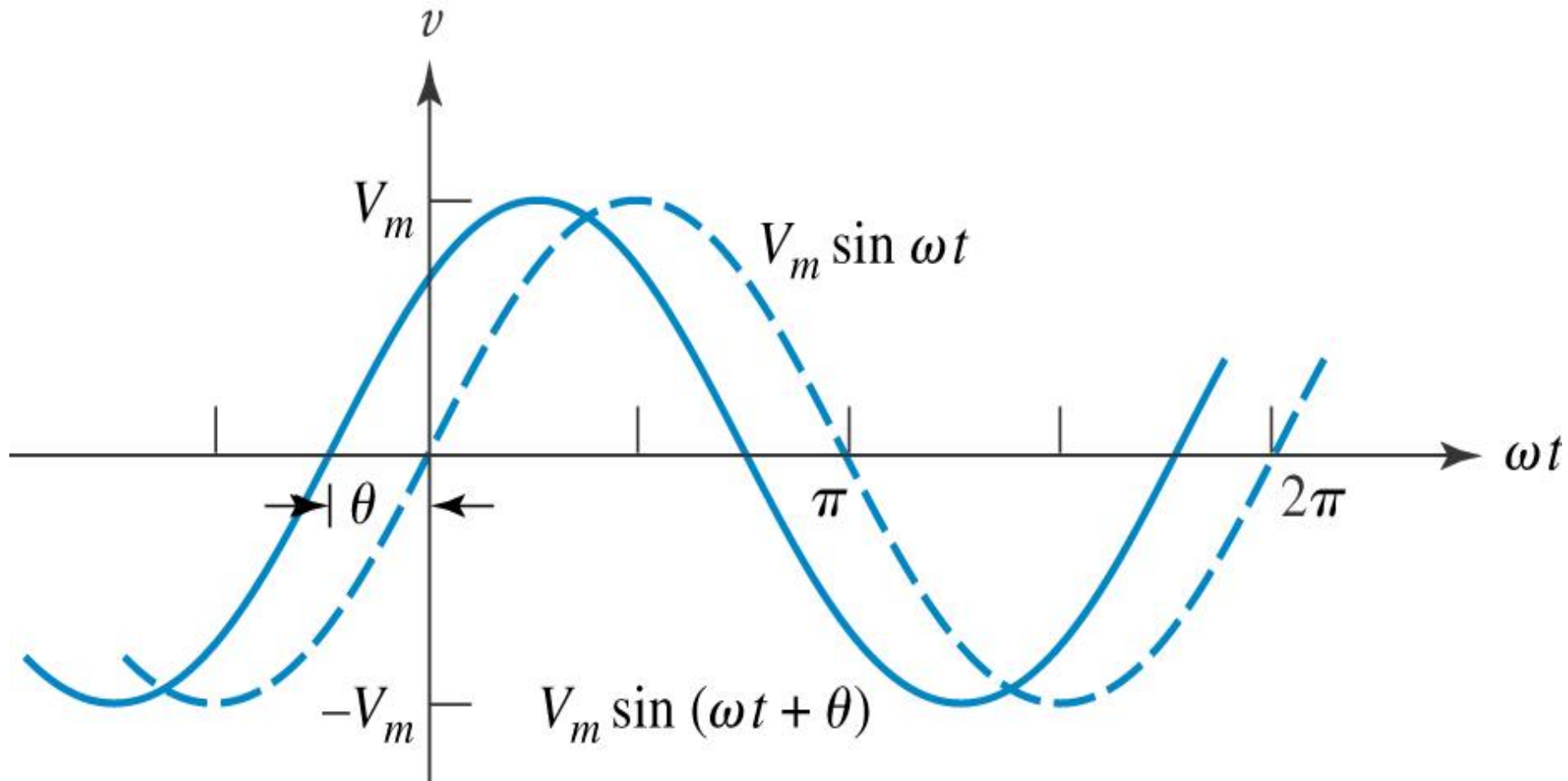

**The sine wave  $V_m \sin(\omega t + \theta)$  leads  $V_m \sin \omega t$  by  $\theta$  rad.**

# Lagging and leading:

## Converting Sines to Cosines

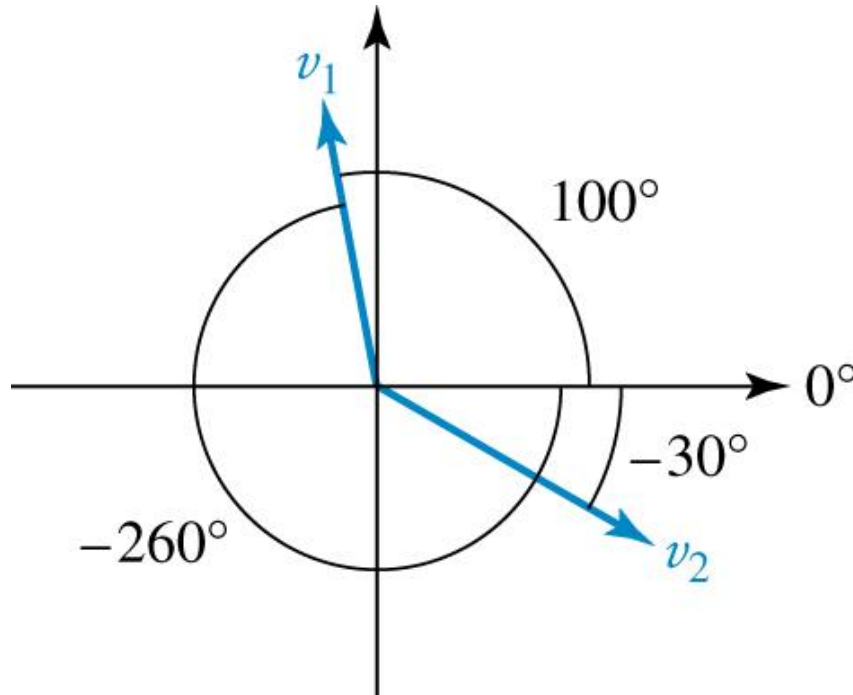

$$\begin{aligned}
 v_1 &= V_{m1} \cos(5t + 10^\circ) \\
 &= V_{m1} \sin(5t + 90^\circ + 10^\circ) \\
 &= V_{m1} \sin(5t + 100^\circ)
 \end{aligned}$$

$$v_2 = V_{m2} \sin(5t - 30^\circ)$$

In electrical engineering, the phase angle is commonly given in degrees, rather than radian.

# Lagging and leading:

---

Two sinusoidal waves whose phase are to be compared must:

1. Both be written as sine waves, or both as cosine waves.
2. Both be written with positive amplitudes.
3. Each have the same frequency.

Normally, the difference in phase between two sinusoids is expressed by that angle which is less than or equal to 180 degree in magnitude

# Practice: 10.1

---

Find the angle by which  $i_1$  lags  $v_1$  if  $v_1 = 120\cos(120\pi t - 40^\circ)$  V and  $i_1$  equals (a)  $2.5\cos(120\pi t + 20^\circ)$  A; (b)  $1.4\sin(120\pi t - 70^\circ)$  A; (c)  $A\cos 100t + B\sin 100t = C\cos(100t + \phi)$ .

$$v_1 = 120\cos(120\pi t - 40^\circ)$$

(a)  $2.5\cos(120\pi t + 20^\circ)$  lags  $v_1$  by  $-40 - 20 = \underline{-60^\circ}$

(b)  $1.4\sin(120\pi t - 70^\circ) = 1.4\cos(120\pi t - 160^\circ)$  lags  $v_1$  by  $-40 - (-160) = \underline{120^\circ}$

(c)  $-0.8\cos(120\pi t - 110^\circ) = 0.8\cos(120\pi t + 70^\circ)$  lags  $v_1$  by  $-40 - 70 = \underline{-110^\circ}$

Find A, B, C, and  $\phi$  if  $40 \cos(100t - 40^\circ) - 20 \sin(100t + 170^\circ) = A \cos 100t + B \sin 100t = C \cos(100t + \phi)$ .



# Practice: 10.2

---

$$\begin{aligned}
 &40 \cos(100t - 40^\circ) - 20 \sin(100t + 170^\circ) \\
 &= A \cos 100t + B \sin 100t \\
 &= C \cos(100t + \theta)
 \end{aligned}$$

$$\begin{aligned}
 40 \cos(100t - 40^\circ) &= 40 [\cos 100t \cdot \cos(-40^\circ) - \sin 100t \cdot \sin(-40^\circ)] \\
 &= 30.64 \cos 100t + 25.71 \sin 100t \\
 -20 \sin(100t + 170^\circ) &= -20 [\cos 170^\circ \cdot \sin 100t + \sin 170^\circ \cdot \cos 100t] \\
 &= 19.70 \sin 100t - 3.473 \cos 100t
 \end{aligned}$$

$$\begin{aligned}
 \text{Thus, } A &= 30.64 - 3.473 = \underline{27.17} \\
 B &= 25.71 + 19.70 = \underline{45.41}
 \end{aligned}$$


$$\begin{aligned}
 C &= \sqrt{A^2 + B^2} = \underline{52.92} \\
 \theta &= \tan^{-1}\left(\frac{-B}{A}\right) = \underline{-59.11^\circ}
 \end{aligned}$$

# Forces Response:

---

Forces Response to sinusoidal Functions:

## The Steady-State Response

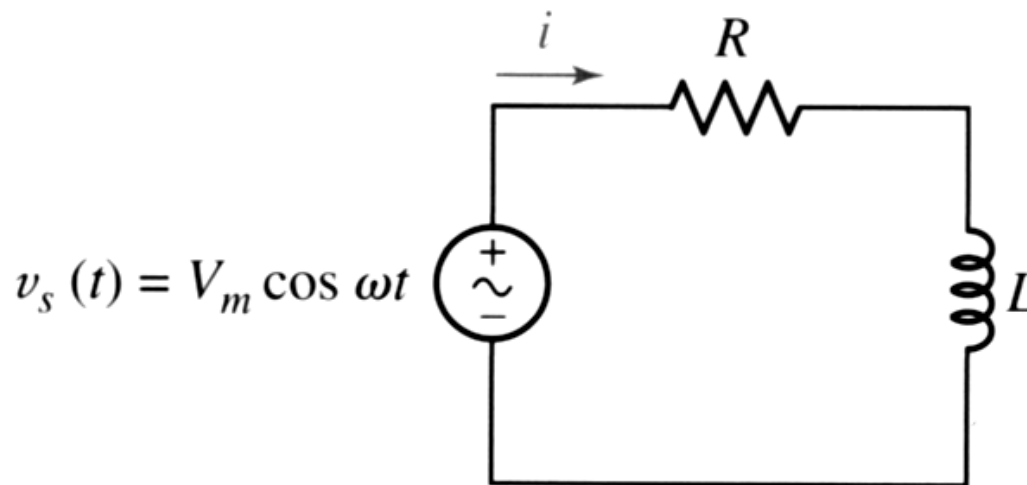

$$L \frac{di}{dt} + Ri = V_m \cos \omega t$$

# Forces Response:

---

The force response will have the general form

$$i(t) = I_1 \cos \omega t + I_2 \sin \omega t$$

Substitute,  $L \frac{di}{dt} + Ri = V_m \cos \omega t$

$$L(-I_1 \omega \sin \omega t + I_2 \omega \cos \omega t) + R(I_1 \cos \omega t + I_2 \sin \omega t) = V_m \cos \omega t$$

Obtain,

$$(-LI_1 \omega + RI_2) \sin \omega t + (LI_2 \omega + RI_1 - V_m) \cos \omega t = 0$$

# Forces Response:

---

Thus,

$$-LI_1\omega + RI_2 = 0$$


And

$$LI_2\omega + RI_1 - V_m = 0$$

Leads to,

$$I_1 = \frac{RV_m}{R^2 + \omega^2 L^2}, \quad I_2 = \frac{\omega LV_m}{R^2 + \omega^2 L^2}$$

# Forces Response:

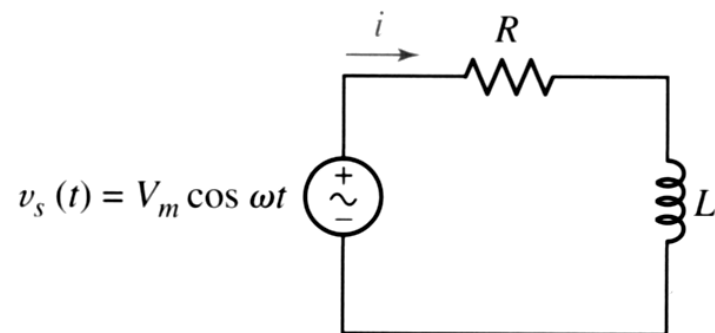

Thus the force response is obtained


$$i(t) = \frac{RV_m}{R^2 + \omega^2 L^2} \cos \omega t + \frac{\omega L V_m}{R^2 + \omega^2 L^2} \sin \omega t$$

The alternate form:

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos \left( \omega t - \tan^{-1} \frac{\omega L}{R} \right)$$



# Example:

Find the current  $i_L$

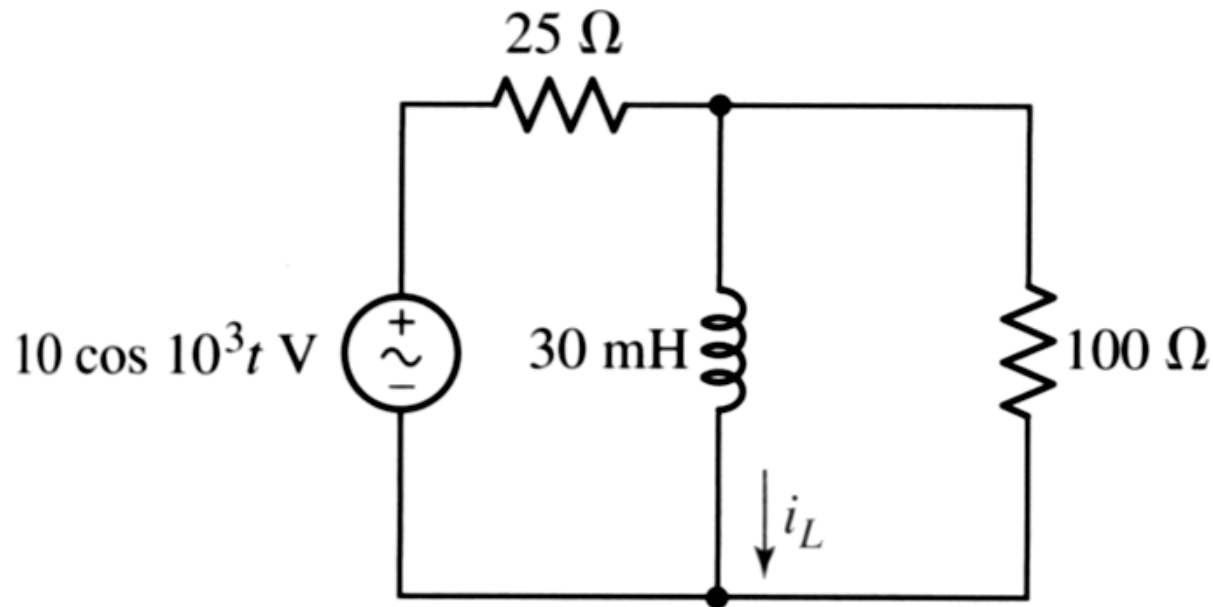

# Example:


Find the current  $i_L$

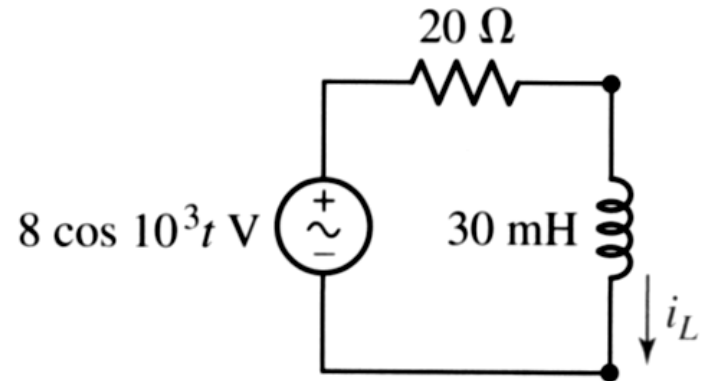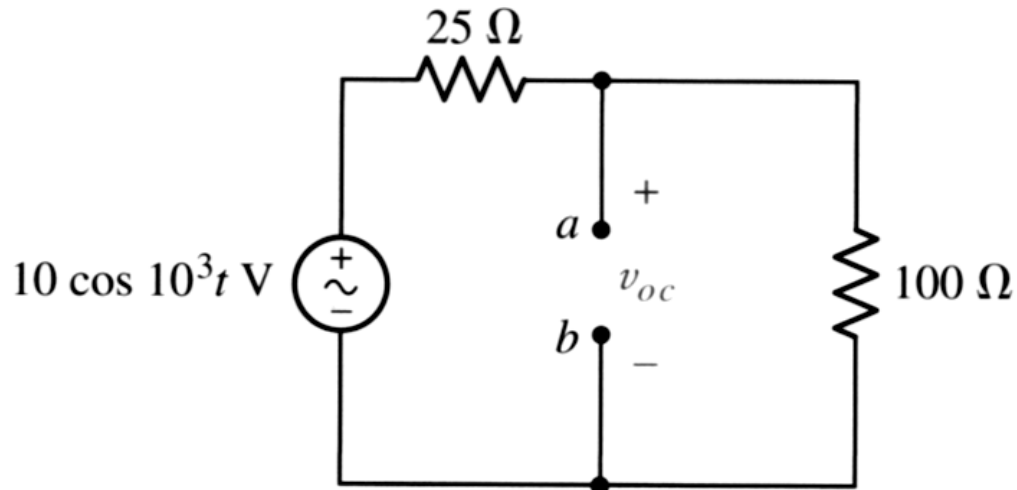

$$\begin{aligned}
 i(t) &= \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right) \\
 &= \frac{8}{\sqrt{20^2 + (10^3 \times 30 \times 10^{-3})^2}} \cos\left(10^3 t - \tan^{-1} \frac{(10^3 \times 30 \times 10^{-3})}{20}\right) \\
 &= 222 \cos(10^3 t - 56.3^\circ) \text{ mA.}
 \end{aligned}$$

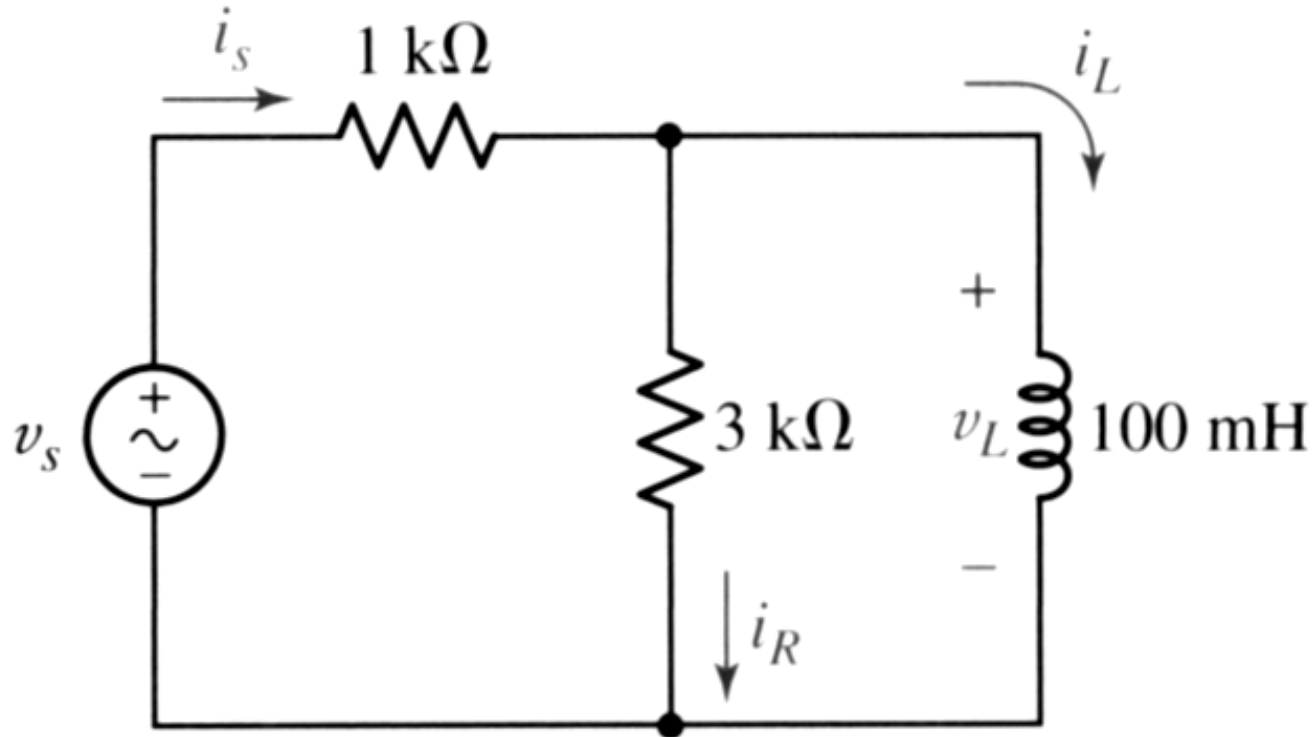
## Practice: 10.3

Let  $v_s = 40\cos 8000t$  V in the circuit. Use Thevenin's theorem where it will do the most good, and find the value at  $t = 0$  for (a)  $i_L$ ; (b)  $v_L$ ; (c)  $i_R$ ; (d)  $i_s$





# Practice: 10.3

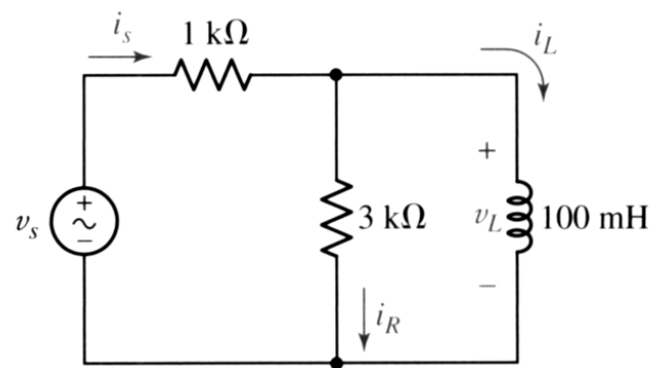


- Removing the inductor temporarily,

$$v_{oc} = 40 \cos 8000t \left( \frac{3}{1+3} \right) = 30 \cos 8000t \text{ V}$$

$$\text{and } R_{TH} = 1\text{ k}\Omega // 3\text{ k}\Omega = 750\text{ }\Omega$$

$$\begin{aligned} \text{Thus, } i_L(t) &= \frac{30}{\sqrt{750^2 + 800^2}} \cos \left( 8000t - \tan^{-1} \frac{800}{750} \right) \\ &= 27.36 \cos (8000t - 46.85^\circ) \text{ mA} \end{aligned}$$

# Practice: 10.3

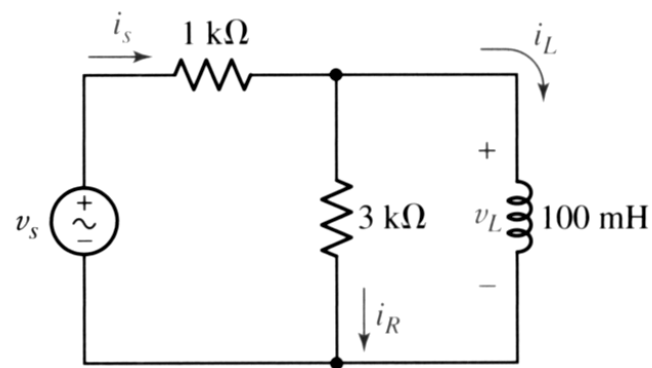


(a)  $i_L(0) = 27.36 \cos(-46.85^\circ) = \underline{18.71\text{ mA}}$

(b)  $v_L(t) = L \frac{di_L}{dt} = (-100 \times 10^{-3})(0.02736)(8000) \sin(8000t - 46.85^\circ)$  so  $v_L(0) = \underline{15.97\text{ V}}$

(c)  $i_R(0) = \frac{v_L(0)}{3000} = \underline{5.323\text{ mA}}$

(d)  $i_s(0) = i_L(0) + i_R(0) = \underline{24.03\text{ mA}}$

# The Complex Forcing Fn:

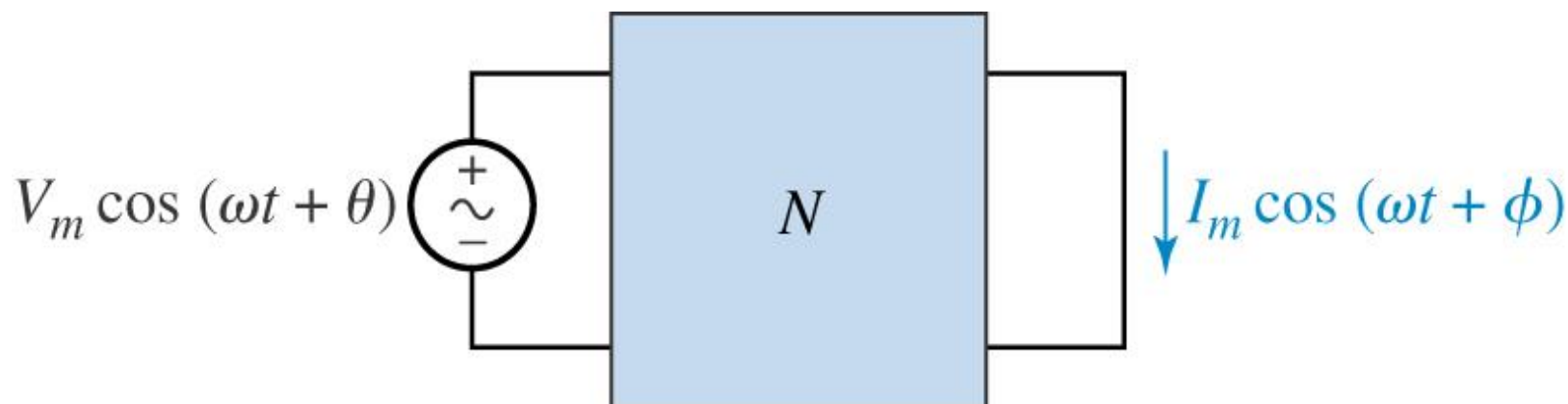

Shifting the phase of the forcing function by 90 degree

$$V_m \cos(\omega t + \theta - 90^\circ) = V_m \sin(\omega t + \theta)$$

A corresponding response

$$I_m \cos(\omega t + \phi - 90^\circ) = I_m \sin(\omega t + \phi)$$


# The Complex Forcing Fn:

Imaginary Sources Lead to ... Imaginary Response  
Apply

$$jV_m \sin(\omega t + \theta)$$

The response is

$$jI_m \sin(\omega t + \phi)$$

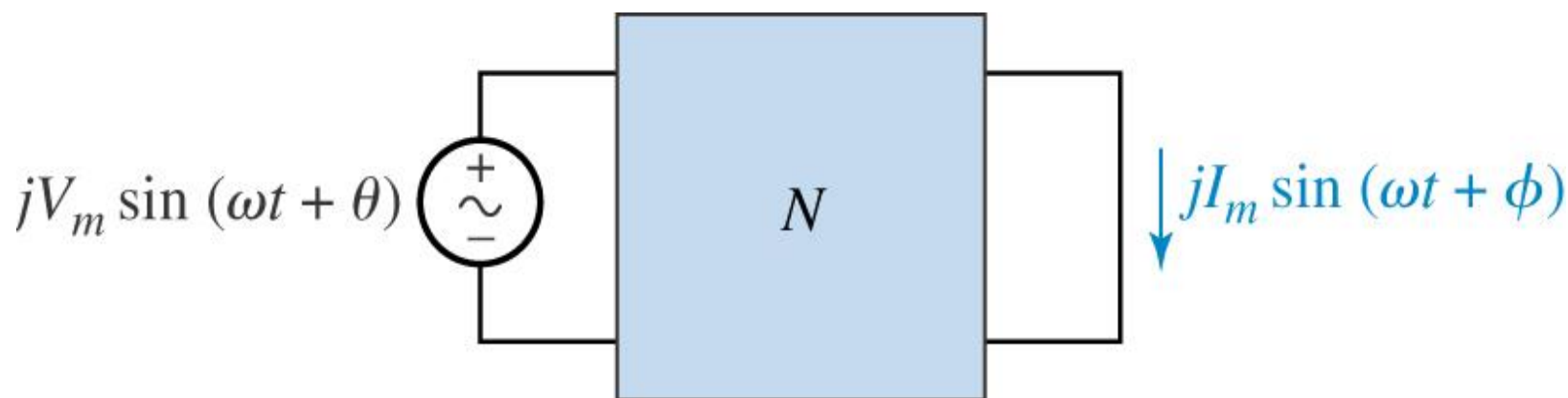

# The Complex Forcing Fn:


## Applying a Complex Forcing Function

Apply

$$V_m \cos(\omega t + \theta) + jV_m \sin(\omega t + \theta) \xrightarrow{\text{Euler's identity}} V_m e^{j(\omega t + \theta)}$$

Produce a response
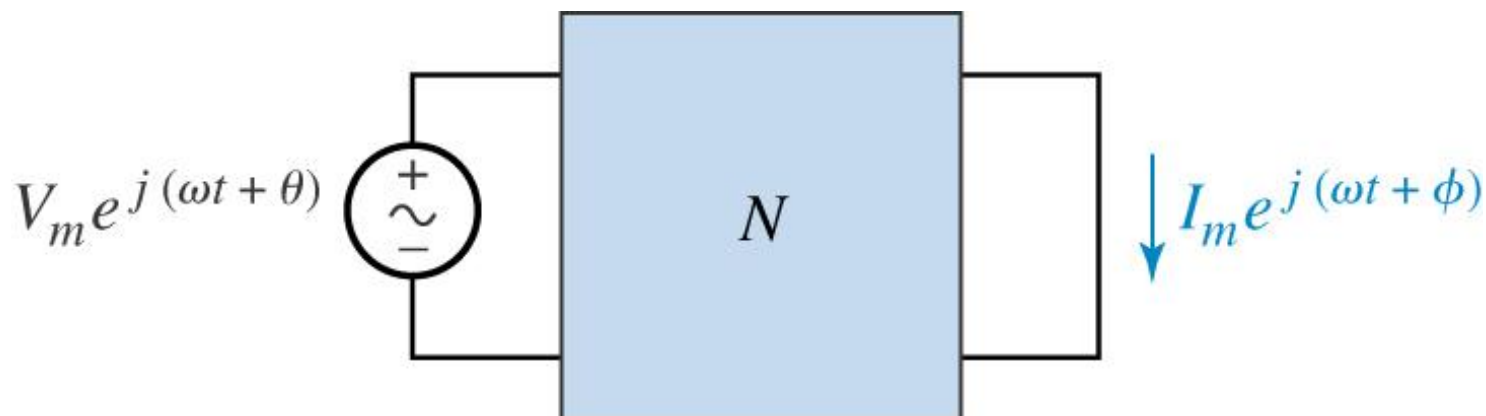
$$I_m \cos(\omega t + \phi) + jI_m \sin(\omega t + \phi) \xrightarrow{\text{Euler's identity}} I_m e^{j(\omega t + \phi)}$$



# The Complex Forcing Fn:

## An Algebraic Alternative to Differential Equations


Note:  $\cos \omega t = \operatorname{Re}\{e^{j\omega t}\}$

The necessary complex source is

$$V_m e^{j\omega t}$$

The complex response is

$$I_m e^{j(\omega t + \phi)}$$

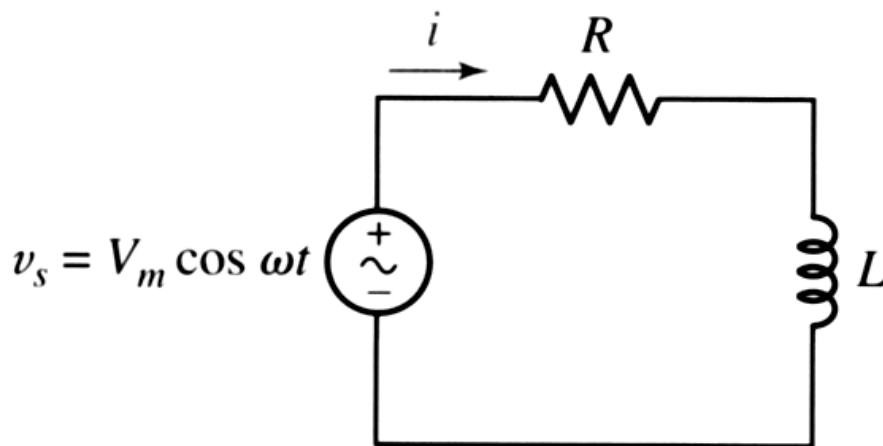

# The Complex Forcing Fn:

---

The differential equation from the circuit

$$Ri + L \frac{di}{dt} = v_s$$

Insert complex expressions for  $v_s$  and  $i$

$$RI_m e^{j(\omega t + \phi)} + L \frac{d}{dt} (I_m e^{j(\omega t + \phi)}) = V_m e^{j\omega t}$$

$$RI_m e^{j(\omega t + \phi)} + j\omega L (I_m e^{j(\omega t + \phi)}) = V_m e^{j\omega t}$$

$$RI_m e^{j\phi} + j\omega L I_m e^{j\phi} = V_m$$

# The Complex Forcing Fn:

---

Factor the left side:

$$I_m e^{j\phi} (R + j\omega L) = V_m$$

Rearrange:

$$I_m e^{j\phi} = \frac{V_m}{R + j\omega L}$$

Expressing the right side in polar form


$$I_m e^{j\phi} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} e^{j(\tan^{-1} \omega L / R)}$$


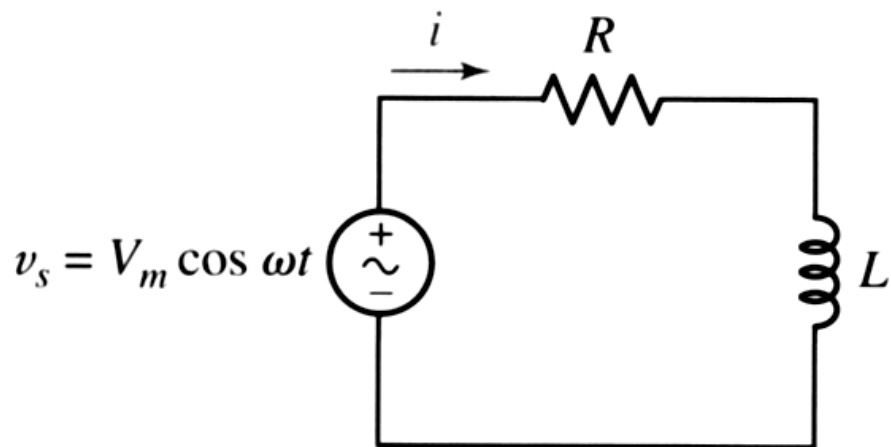
# The Complex Forcing Fn:

Thus

$$I_m = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}}$$



And

$$\phi = -\tan^{-1} \frac{\omega L}{R}$$

$$I_m \angle \phi,$$

$$V_m / \sqrt{R^2 + \omega^2 L^2} \angle -\tan^{-1} \omega L / R$$

We find that

$$i(t) = I_m \cos(\omega t + \phi) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos\left(\omega t - \tan^{-1} \frac{\omega L}{R}\right)$$

## Practice: 10.4

---

Evaluate and express the result in rectangular form:

(a)  $[(2\angle 30^\circ)(5\angle -110^\circ)](1 + 2j)$ ; (b)  $(5\angle -200^\circ) + 4\angle 20^\circ$ .

Evaluate and express the result in polar form: (c)  $(2 - j7)/(3 - j)$ ; (d)  $8 - j4 + [(5\angle 80^\circ)/(2\angle 20^\circ)]$ .

# Practice: 10.4

---

$$\begin{aligned}
 \text{(a)} \quad & (2\angle 30^\circ)(5\angle -110^\circ)(1+j2) = (2\angle 30^\circ)(5\angle -110^\circ)(2.236\angle 63.43^\circ) \\
 & = 2 \times 5 \times 2.236 \angle (30^\circ - 110^\circ + 63.43^\circ) \\
 & = 22.36 \angle -16.57^\circ = \underline{21.43 - j6.377}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad & 5\angle -200^\circ + 4\angle 20^\circ \\
 & = -4.698 + j1.710 + 3.759 + j1.368 \\
 & = \underline{-0.939 + j3.078}
 \end{aligned}$$

$$\text{(c)} \quad \frac{2-j7}{3-j} = \frac{7.280\angle -74.05^\circ}{3.162\angle -18.43^\circ} = \underline{2.302\angle -55.62^\circ}$$

$$\begin{aligned}
 \text{(d)} \quad & 8-j4 + \frac{5\angle 80^\circ}{2\angle 20^\circ} = 8-j4 + 2.5\angle 60^\circ \\
 & = 8-j4 + 1.25 + j2.165 \\
 & = 9.25 - j1.835 = \underline{9.43\angle -11.22^\circ}
 \end{aligned}$$

## Practice: 10.5

---

If the use of the passive sign convention is specified, find the (a) complex voltage that results when the complex current  $4e^{j800t}$  A is applied to the series combination of a 1-mF capacitor and a 2- $\Omega$  resistor; (b) complex current that results when the complex voltage  $100e^{j2000t}$  V is applied to the parallel combination of a 1-mH inductor and a 50- $\Omega$  resistor.

# Practice: 10.5

---

$$\begin{aligned} \text{(a)} \quad v_{\text{combination}} &= \frac{1}{10^{-3}} \int_{-\infty}^t 4 e^{j800t'} dt' + 2 \times 4 e^{j800t} \\ &= \frac{4}{j800 \times 10^{-3}} e^{j800t} + 8 e^{j800t} \\ &= -j5 e^{j800t} + 8 e^{j800t} = (8 - j5) e^{j800t} \\ &= 9.434 e^{-j32.0^\circ} e^{j800t} \\ &= \underline{9.434 e^{j(800t - 32^\circ)}} \text{ V} \end{aligned}$$

# Practice: 10.5

---

$$\begin{aligned} \text{(b)} \quad i_{\text{source}} &= \frac{1}{10 \times 10^{-3}} \int_{-\infty}^t 100 e^{j2000t'} dt' + \frac{100}{50} e^{j2000t} \\ &= \frac{10000}{j2000} e^{j2000t} + 2 e^{j2000t} \\ &= (2 - j5) e^{j2000t} = 5.385 e^{-j68.2^\circ} e^{j2000t} \\ &= \underline{5.385 e^{j(2000t - 68.2^\circ)}} \text{ A} \end{aligned}$$

# The Phasor:

A phasor transformation:

$$i(t) = I_m \cos(\omega t + \phi)$$



$$i(t) = \text{Re}\{I_m e^{j(\omega t + \phi)}\}$$



$$\mathbf{I} = I_m e^{j\phi}$$



$$\mathbf{I} = I_m \angle \phi$$

$$v(t) = V_m \cos(\omega t) \longrightarrow V_m \angle 0^\circ$$

$$i(t) = I_m \cos(\omega t + \phi) \longrightarrow I_m \angle \phi$$

## Practice: 10.6

---

Transform each of the following functions of time into phasor form: (a)  $-5\sin(580t - 110^\circ)$ ; (b)  $3\cos 600t - 5\sin(600t + 110^\circ)$ ; (c)  $8\cos(4t - 30^\circ) + 4\sin(4t - 100^\circ)$ .

Hint: First convert each into a single cosine function with a positive magnitude



# Practice: 10.6

---

$$\begin{aligned}
 \text{(a)} \quad -5 \sin(580t - 110^\circ) &= 5 \cos(580t - 110^\circ + 180^\circ - 90^\circ) \\
 &= 5 \cos(580t - 20^\circ) \Rightarrow \underline{5 \angle -20^\circ}
 \end{aligned}$$

$$\begin{aligned}
 \text{(b)} \quad &3 \cos 600t - 5 \sin(600t + 110^\circ) \\
 &= 3 \cos 600t - 5 \cos(600t + 110^\circ - 90^\circ) \\
 &= 3 \cos 600t - 5 \cos 600t \cos 20^\circ + 5 \sin 600t \sin 20^\circ \\
 &= 3 \cos 600t - 4.698 \cos 600t + 1.71 \sin 600t \\
 &= -1.698 \cos 600t + 1.71 \sin 600t \\
 &= -2.41 \cos(600t + 45.2^\circ) \\
 &= 2.41 \cos(600t - 134.8^\circ) \Rightarrow \underline{2.41 \angle -134.8^\circ}
 \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad & 8\cos(4t - 30^\circ) + 4\sin(4t - 100^\circ) \\ &= 8\cos(4t - 30^\circ) + 4\cos(4t - 190^\circ) \\ &= 8\cos 4t \cos(-30^\circ) - 8\sin 4t \sin(-30^\circ) + 4\cos 4t \cos(-190^\circ) - 4\sin 4t \sin(-190^\circ) \\ &= (6.928 - 3.939)\cos 4t + (4 - 0.6946)\sin 4t \\ &= 2.989\cos 4t + 3.305\sin 4t \\ &= 4.456\cos(4t - 47.87^\circ) \Rightarrow \underline{4.456\angle -47.87^\circ} \end{aligned}$$

## Practice: 10.7

---

Let  $\omega = 2000$  rad/s and  $t = 1$  ms. Find the instantaneous value of each of the currents given here in phasor form: (a)  $j10$  A; (b)  $20 + j10$  A; (c)  $20 + j(10\angle 20^\circ)$  A.

# Practice: 10.7

---

$$\omega = 2000 \text{ rad/s} \quad \text{and} \quad t = 1 \text{ ms}$$

$$(a) \quad j10 \text{ A} = 10 \angle +90^\circ \text{ A} \quad \text{so} \quad i(t) = 10 \cos(2000t + 90^\circ) \text{ A} \quad \text{and} \quad i(10^{-3}) = \underline{-9.093 \text{ A}}$$

$$(b) \quad 20 + j10 \text{ A} = 22.36 \angle 26.57^\circ \text{ A} \quad \text{so} \quad i(t) = 22.36 \cos(2000t + 26.57^\circ) \text{ A} \\ \text{and} \quad i(10^{-3}) = \underline{-17.42 \text{ A}}$$

$$(c) \quad 20 + j(10 \angle 20^\circ) \text{ A} = 20 + (1 \angle 90^\circ)(10 \angle 20^\circ) \text{ A} \\ = 20 + 10 \angle 110^\circ \text{ A} \\ = 19.06 \angle 29.54^\circ \text{ A} \\ \text{so} \quad i(t) = 19.06 \cos(2000t + 29.54^\circ) \text{ A} \quad \text{and} \quad i(10^{-3}) = \underline{-15.45 \text{ A}}$$

# Phasor Relationship:

## The Resistors


$$v(t) = Ri(t)$$

## Apply the complex voltage

$$v(t) = V_m e^{j(\omega t + \theta)} = V_m \cos(\omega t + \theta) + jV_m \sin(\omega t + \theta)$$
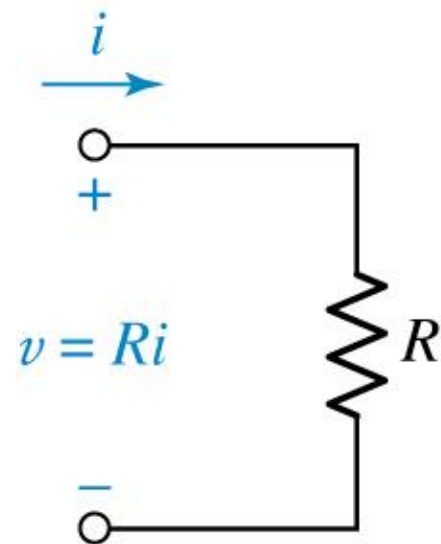
## Assume the complex current response


$$i(t) = I_m e^{j(\omega t + \phi)} = I_m \cos(\omega t + \phi) + jI_m \sin(\omega t + \phi)$$


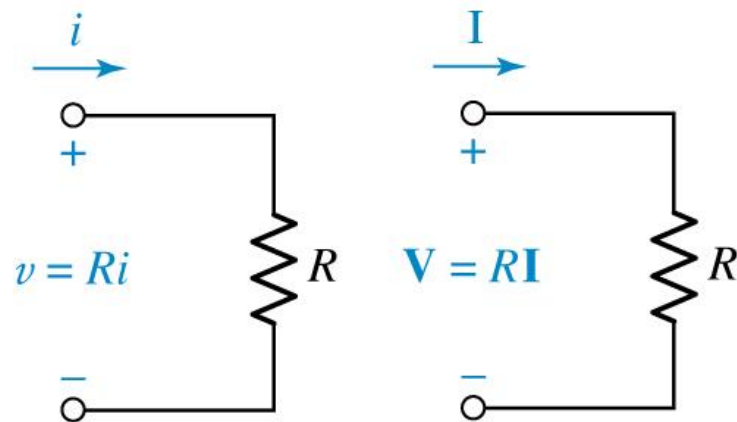
# Phasor Relationship:

So that

$$V_m e^{j(\omega t + \theta)} = R I_m e^{j(\omega t + \phi)}$$



Dividing throughout by  $e^{j\omega t}$

$$V_m e^{j\theta} = R I_m e^{j\phi}$$

In polar form:  $V_m \angle \theta = R I_m \angle \phi$

Thus,

$$\mathbf{V} = R \mathbf{I}$$



# Phasor Relationship:

The Inductor:  $v(t) = L \frac{di}{dt}$

$$\begin{aligned} V_m e^{j(\omega t + \theta)} &= L \frac{d}{dt} I_m e^{j(\omega t + \phi)} \\ &= j\omega L I_m e^{j(\omega t + \phi)} \end{aligned}$$



Dividing throughout by  $e^{j\omega t}$
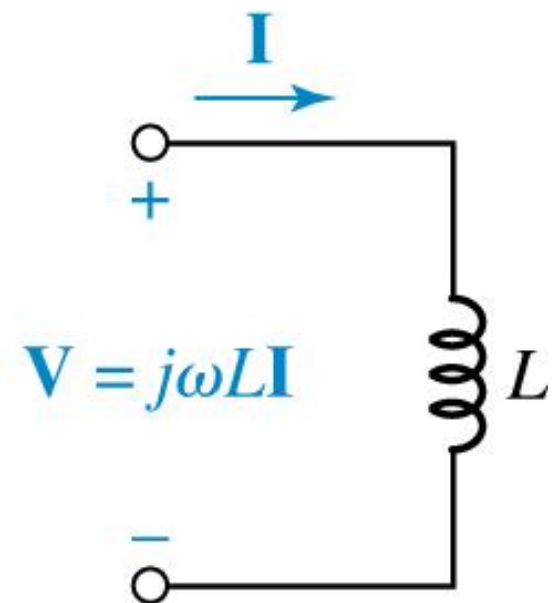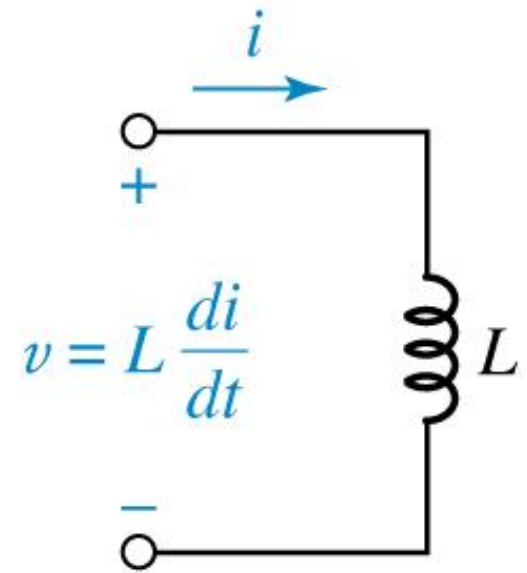
$$V_m e^{j\theta} = j\omega L I_m e^{j\phi}$$









# Phasor Relationship:

The Capacitor:  $i(t) = C \frac{dv}{dt}$

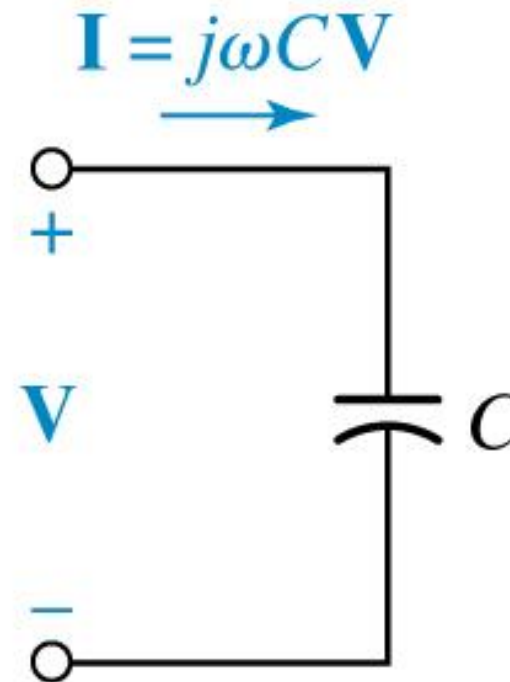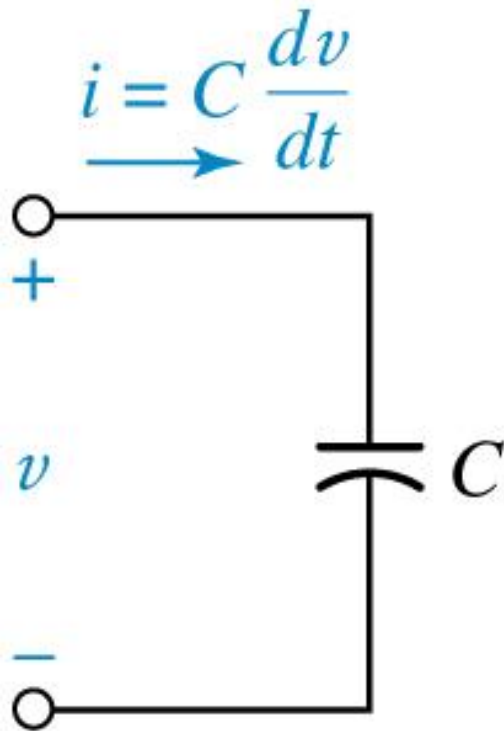

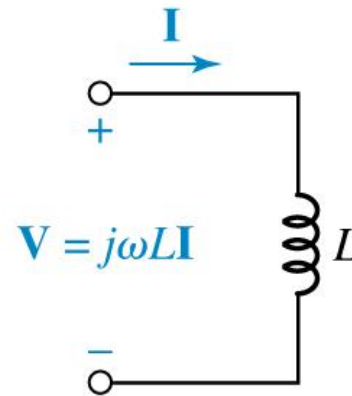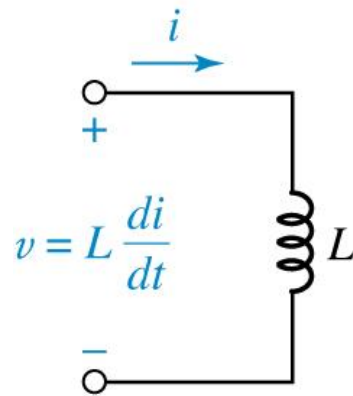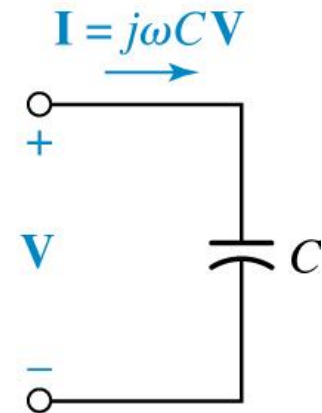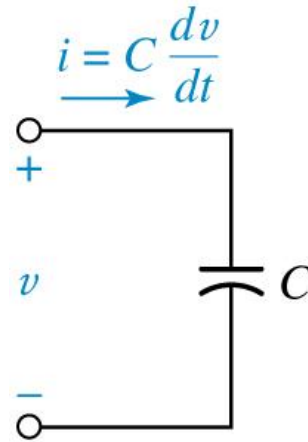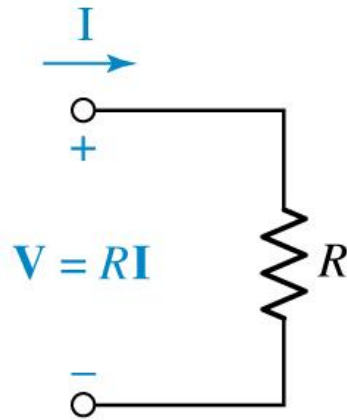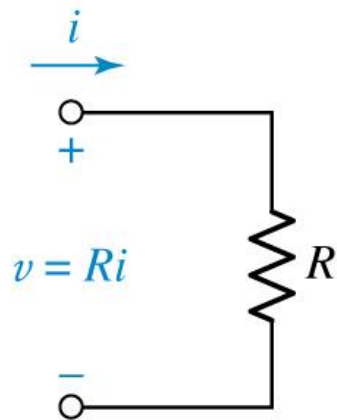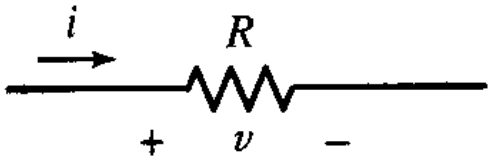

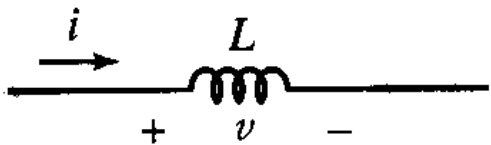
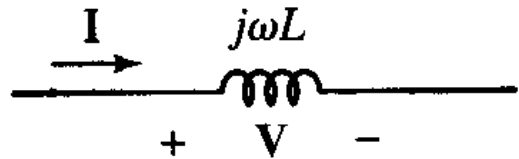
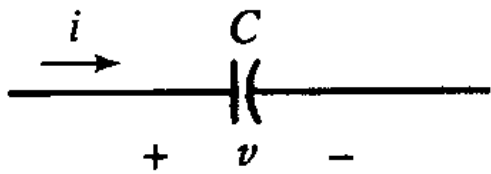
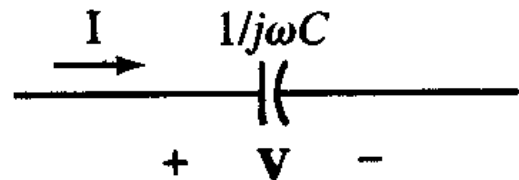


# Phasor Relationship:



# Phasor Relationship:

**Table 10.1** | Comparison of time-domain and frequency-domain voltage-current expressions

Time domain	Frequency domain		
	$v = Ri$	$\mathbf{V} = R\mathbf{I}$	
	$v = L \frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$	
	$v = \frac{1}{C} \int i dt$	$\mathbf{V} = \frac{1}{j\omega C}\mathbf{I}$	

# Phasor:

---

## Kirchhoff's Laws Using Phasors


In the time domain

$$v_1(t) + v_2(t) + \dots + v_N(t) = 0$$

We can obtain

$$V_1 + V_2 + \dots + V_N = 0$$

# Phasor:

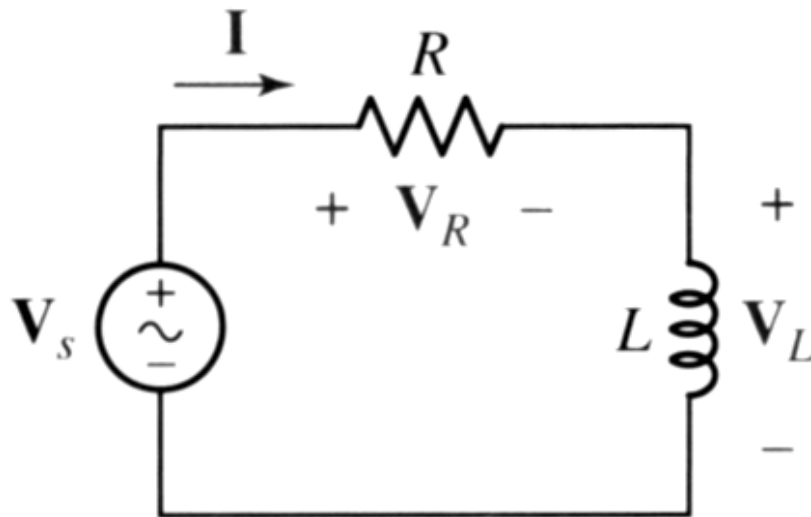

$$\mathbf{V}_R + \mathbf{V}_L = \mathbf{V}_s$$

$$R\mathbf{I} + j\omega L\mathbf{I} = \mathbf{V}_s$$


$$\mathbf{I} = \frac{\mathbf{V}_s}{R + j\omega L}$$

$$\mathbf{I} = \frac{V_m \angle 0^\circ}{R + j\omega L}$$


$$\mathbf{I} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \angle (-\tan^{-1}(\omega L/R))$$
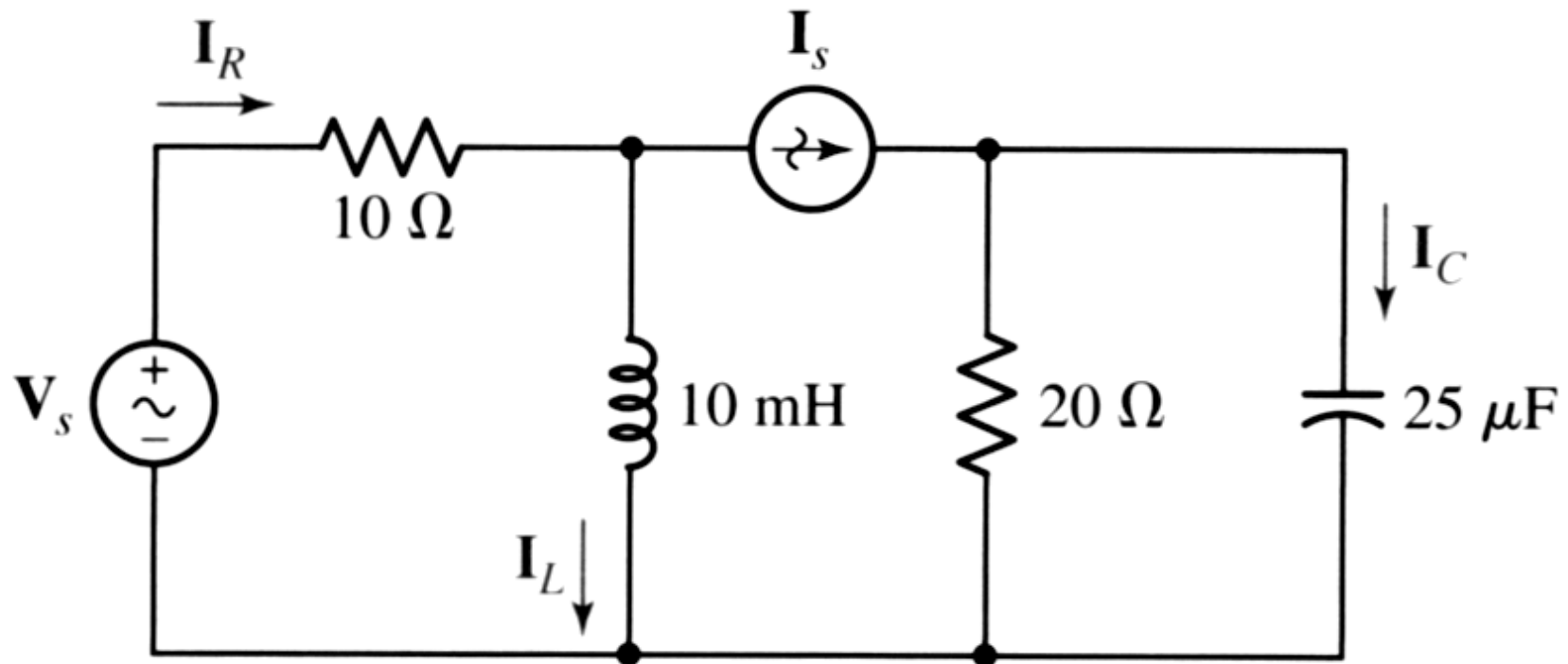
# Practice: 10.8

In the circuit, let  $\omega = 1200$  rad/s,  $\mathbf{I}_C = 1.2\angle 28^\circ$  A, and  $\mathbf{I}_L = 3\angle 53^\circ$  A. Find (a)  $\mathbf{I}_s$ ; (b)  $\mathbf{V}_s$ ; (c)  $i_R(t)$ .



# Practice: 10.8

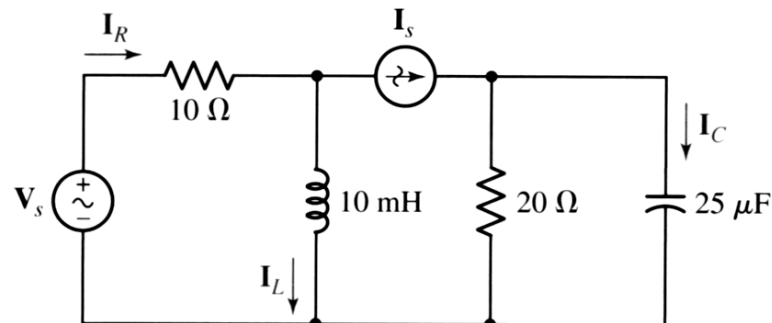

The inductor is represented by a  $j(10 \times 10^{-3})(1200) = j12 \Omega$  impedance and the capacitor by a  $\frac{-j}{(1200)(25 \times 10^{-6})} = -j33.33 \Omega$  impedance.

(a) The voltage across the  $20\text{-}\Omega$  resistor is then

$$(1.2 \angle 28^\circ)(-j33.33) = 40 \angle -62^\circ \text{ V and the current through it is } \frac{40 \angle -62^\circ}{20} = 2 \angle -62^\circ \text{ A}$$

$$\begin{aligned} \text{Thus, } \mathbf{I}_s &= 2 \angle -62^\circ + 1.2 \angle 28^\circ && \text{(by KCL)} \\ &= \underline{2.332 \angle -31.04^\circ \text{ A}} \end{aligned}$$

$$\begin{aligned} \text{(b) } \mathbf{V}_s &= 10\mathbf{I}_R + (j12)\mathbf{I}_L \\ &= 10(\mathbf{I}_L + \mathbf{I}_s) + (12 \angle 90^\circ)\mathbf{I}_L \\ &= 10(3 \angle 53^\circ + 2.332 \angle -31.04^\circ) + (12 \angle 90^\circ)(3 \angle 53^\circ) \\ &= \underline{34.86 \angle 74.55^\circ \text{ V}} \end{aligned}$$

$$\begin{aligned} \text{(c) } \mathbf{I}_R &= \mathbf{I}_L + \mathbf{I}_s = 3 \angle 53^\circ + 2.332 \angle -31.04^\circ = 3.986 \angle 17.42^\circ \\ \therefore i_R(t) &= \underline{3.986 \cos(1200t + 17.42^\circ) \text{ A}} \end{aligned}$$

# Impedance: $\mathbf{Z}$

From

$$\mathbf{V} = R\mathbf{I} \quad \mathbf{V} = j\omega L\mathbf{I} \quad \mathbf{V} = \frac{\mathbf{I}}{j\omega C}$$

phasor voltage/phasor current ratio as impedance

$$\frac{\mathbf{V}}{\mathbf{I}} = R \quad \frac{\mathbf{V}}{\mathbf{I}} = j\omega L \quad \frac{\mathbf{V}}{\mathbf{I}} = \frac{1}{j\omega C}$$

$$\mathbf{Z}_R = R$$

$$\mathbf{Z}_L = j\omega L$$


$$\mathbf{Z}_C = \frac{1}{j\omega C}$$

A resistance

A reactance

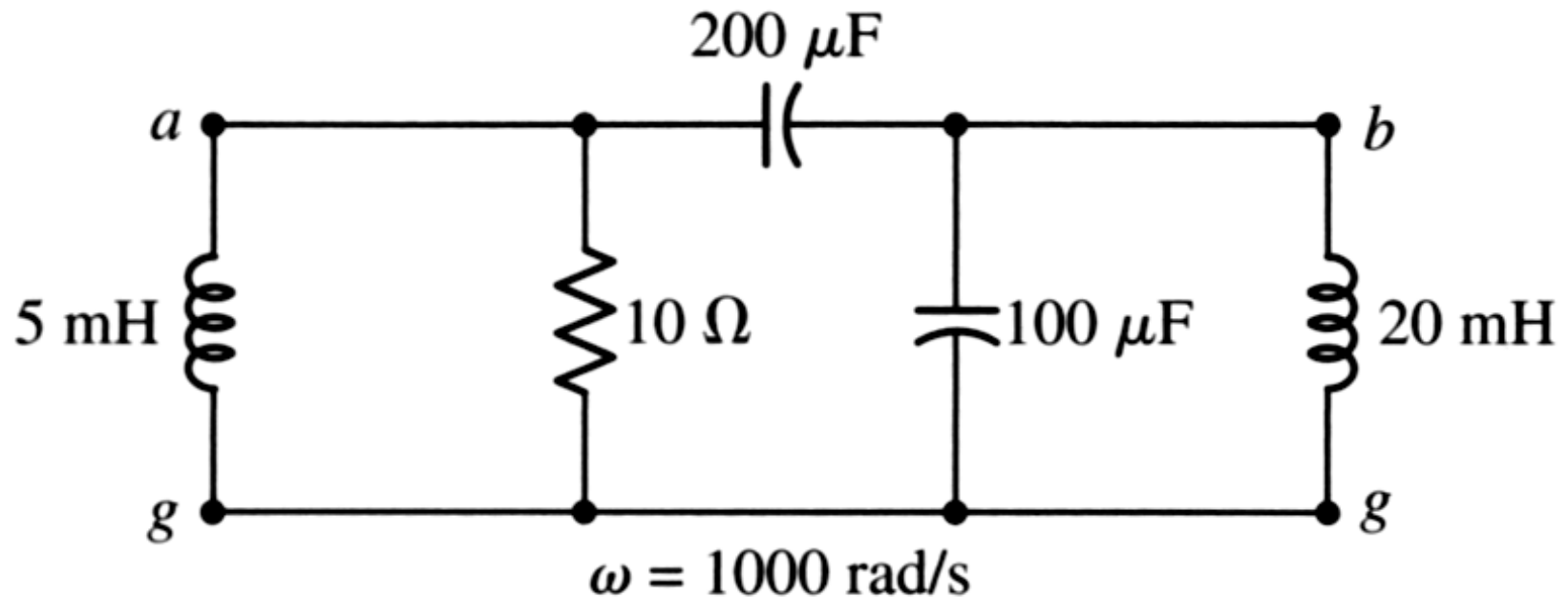
## Practice: 10.9

With reference to the network shown, find the input impedance  $\mathbf{Z}_{in}$  that would be measured between terminals: (a) a and g; (b) b and g; (c) a and b





# Practice: 10.9

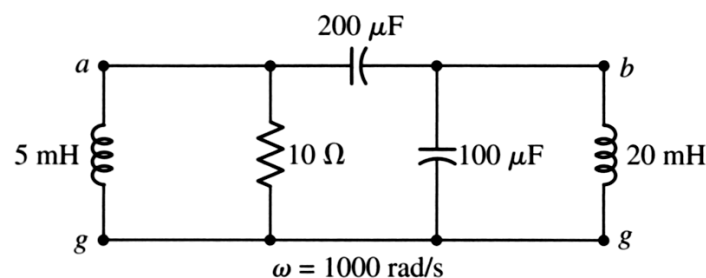

$$5 \text{ mH} \rightarrow j5 \Omega; 20 \text{ mH} \rightarrow j20 \Omega$$


$$200 \mu\text{F} \rightarrow -j5 \Omega; 100 \mu\text{F} \rightarrow -j10 \Omega$$

$$\begin{aligned} \text{(a)} \quad \mathbf{Z}_{in}(a, g) &= (j5 // 10) // [-j5 + (-j10 // j20)] \\ &= (2 + j4) // [-j25] \\ &= \underline{2.809 + j4.494 \Omega} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad \mathbf{Z}_{in}(b, g) &= (j20 // -j10) // [-j5 + (10 // j5)] \\ &= -j20 // (2 - j) = \underline{1.798 - j1.124 \Omega} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad \mathbf{Z}_{in}(a, b) &= -j5 // [(j5 // 10) + (-j10 // j20)] \\ &= -j5 // (2 + j4 + (-j20)) \\ &= -j5 // (2 - j16) = \underline{0.1124 - j3.820 \Omega} \end{aligned}$$

# Example: find $i(t)$

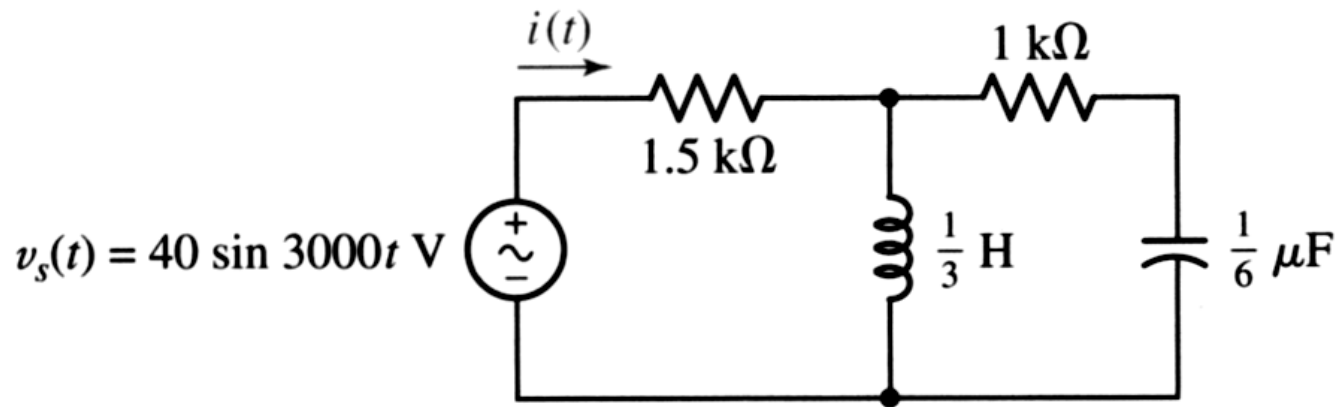


$$40 \sin(3000t) = 40 \cos(3000t - 90^\circ) \rightarrow 40 \angle -90^\circ$$

$$\begin{aligned} j\omega L &= j \cdot 3000 \cdot \frac{1}{3} \\ &= j1k \quad \Omega \end{aligned}$$

$$\begin{aligned} \frac{1}{j\omega C} &= \frac{-j}{3000 \cdot \frac{1}{6} \mu} \\ &= -j2k \quad \Omega \end{aligned}$$

# Example:

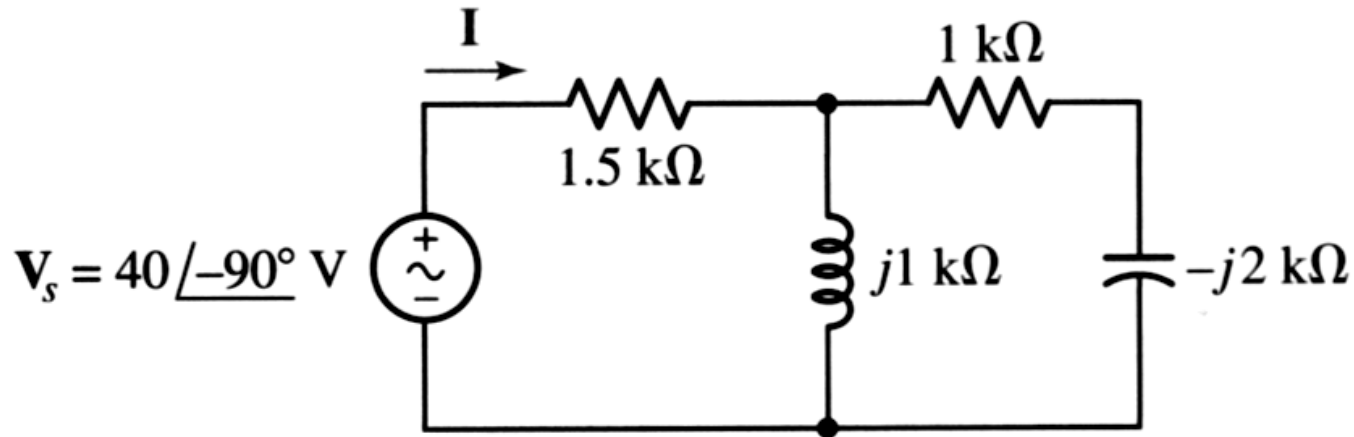


$$\begin{aligned}
 Z_{total} &= 1.5 + \frac{(j) \cdot (1 - 2j)}{j + 1 - 2j} \\
 &= 2 + j1.5 = 2.5 \angle 36.87^\circ \text{ k}\Omega
 \end{aligned}$$

$$I = \frac{V_s}{Z_{total}} = \frac{40 \angle -90^\circ}{2.5 \angle 36.87^\circ} \text{ mA} = 16 \angle -126.9^\circ \text{ mA}$$


$$\rightarrow 16 \cos(3000t - 126.9^\circ) \text{ mA}$$
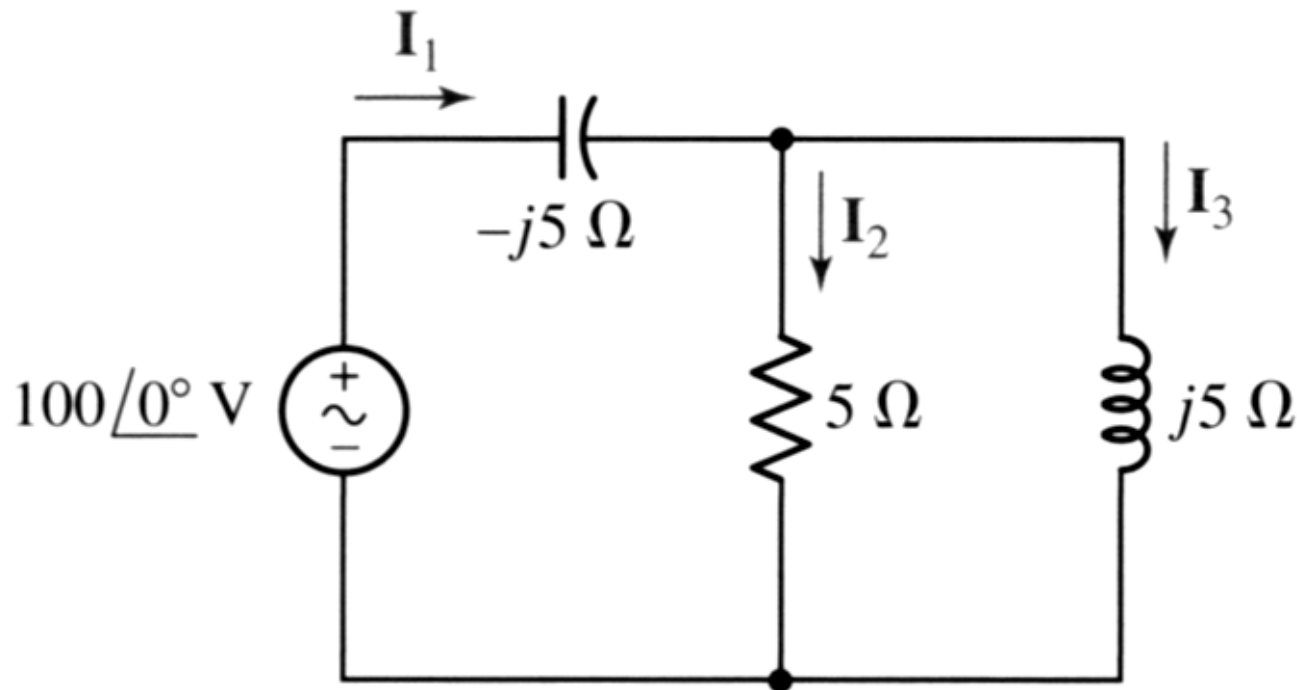
# Practice: 10.10

In the frequency-domain circuit, find (a)  $\mathbf{I}_1$ ; (b)  $\mathbf{I}_2$ ; (c)  $\mathbf{I}_3$



# Practice: 10.10

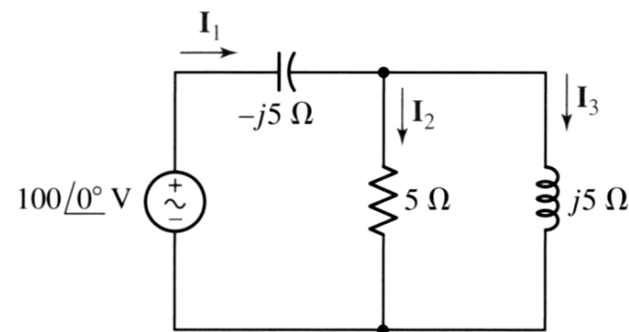

$$\begin{aligned} \text{(a)} \quad \mathbf{I}_1 &= \frac{100}{-j5 + 5 // j5} = \frac{100}{2.5 - j2.5} = \frac{100}{3.536 \angle -45^\circ} \\ &= \underline{28.28 \angle 45^\circ \text{ A}} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad \mathbf{I}_2 &= \mathbf{I}_1 \frac{j5}{5 + j5} = 28.28 \angle 45^\circ \left( \frac{5 \angle 90^\circ}{7.071 \angle 45^\circ} \right) \\ &= \underline{20 \angle 90^\circ \text{ A}} \end{aligned}$$

$$\begin{aligned} \text{(c)} \quad \mathbf{I}_3 &= \mathbf{I}_1 - \mathbf{I}_2 = 28.28 \angle 45^\circ - 20 \angle 90^\circ \\ &= 20 \angle -0.009^\circ \text{ A} \approx \underline{20 \angle 0^\circ \text{ A}} \end{aligned}$$

## Admittance

$$\mathbf{Y} = \frac{\mathbf{I}}{\mathbf{V}}$$

$$\mathbf{Y} = \frac{1}{\mathbf{Z}}$$

$$\mathbf{Y} = G + jB = \frac{1}{\mathbf{Z}} = \frac{1}{R + jX}$$

G = the conductance

B = the susceptance

R = the resistance

X = the reactance

... immittance

Determine the admittance (in rectangular form) of (a) an impedance  $\mathbf{Z} = 1000 + j400 \, \Omega$ ; (b) a network consisting of the parallel combination of an  $800\text{-}\Omega$  resistor, a  $1\text{-mH}$  inductor, and a  $2\text{-nF}$  capacitor, if  $\omega = 1 \text{ Mrad/s}$ ; (c) a network consisting of the series combination of an  $800\text{-}\Omega$  resistor, a  $1\text{-mH}$  inductor, and a  $2\text{-nF}$  capacitor, if  $\omega = 1 \text{ Mrad/s}$

# Practice: 10.11

---

$$(a) \quad \mathbf{Z} = 1000 + j400 \, \Omega = 1077 \angle 21.80^\circ \, \Omega$$

$$\begin{aligned} \therefore \mathbf{Y} &= \frac{1}{\mathbf{Z}} = 928.5 \angle -21.8^\circ \, \mu\text{S} \\ &= \underline{862.1 - j344.8 \, \mu\text{S}} \end{aligned}$$

$$(b) \quad \text{at } \omega = 10^6 \text{ rad/s, } 1 \text{ mH} \rightarrow j10^6 \, \Omega, 2 \text{ nF} \rightarrow -j500 \, \Omega$$

$$\mathbf{Y} = \frac{1}{800} + \frac{1}{j10^6} - \frac{1}{j500} = \underline{1.25 + j2 \text{ mS}}$$


$$(c) \quad \mathbf{Z} = 800 + j10^6 - j500 = 999.5 \times 10^3 \angle 89.95^\circ \, \Omega$$

$$\begin{aligned} \mathbf{Y} &= \frac{1}{\mathbf{Z}} = 1.0005 \angle -89.95^\circ \, \mu\text{S} \\ &= \underline{800.8 - j10^6 \text{ pS}} \end{aligned}$$



# Nodal and Mesh Analysis:

Example: find  $v_1(t)$  and  $v_2(t)$

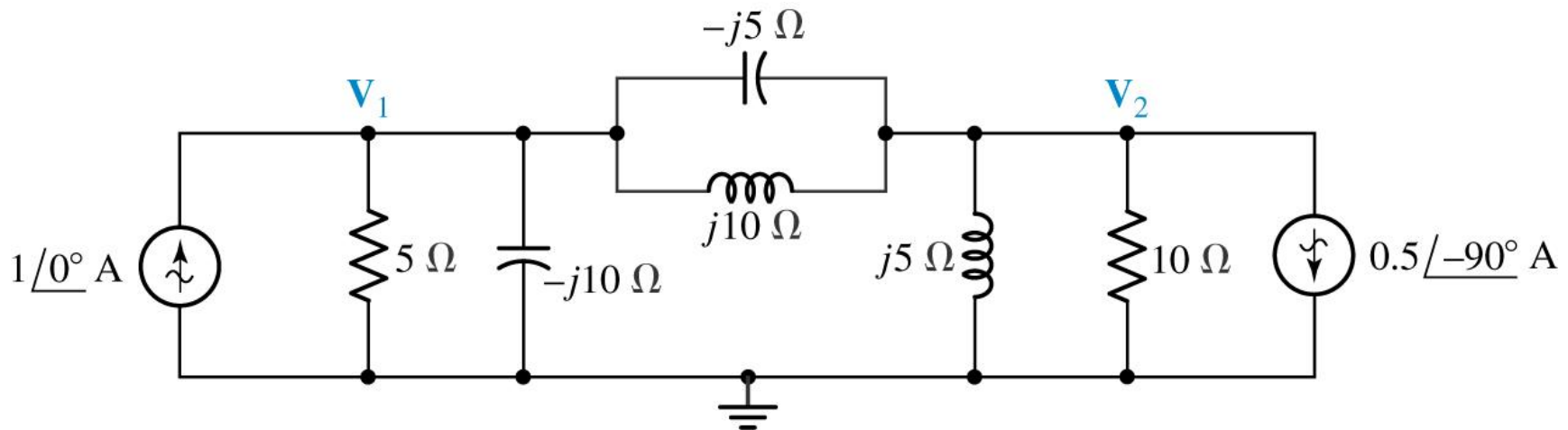


$$\frac{V_1}{5} + \frac{V_1}{-j10} + \frac{V_1 - V_2}{-j5} + \frac{V_1 - V_2}{j10} = 1 \angle 0^\circ = 1 + j0$$


$$\frac{V_2 - V_1}{-j5} + \frac{V_2 - V_1}{j10} + \frac{V_2}{j5} + \frac{V_2}{10} = -(0.5 \angle 0^\circ) = j0.5$$
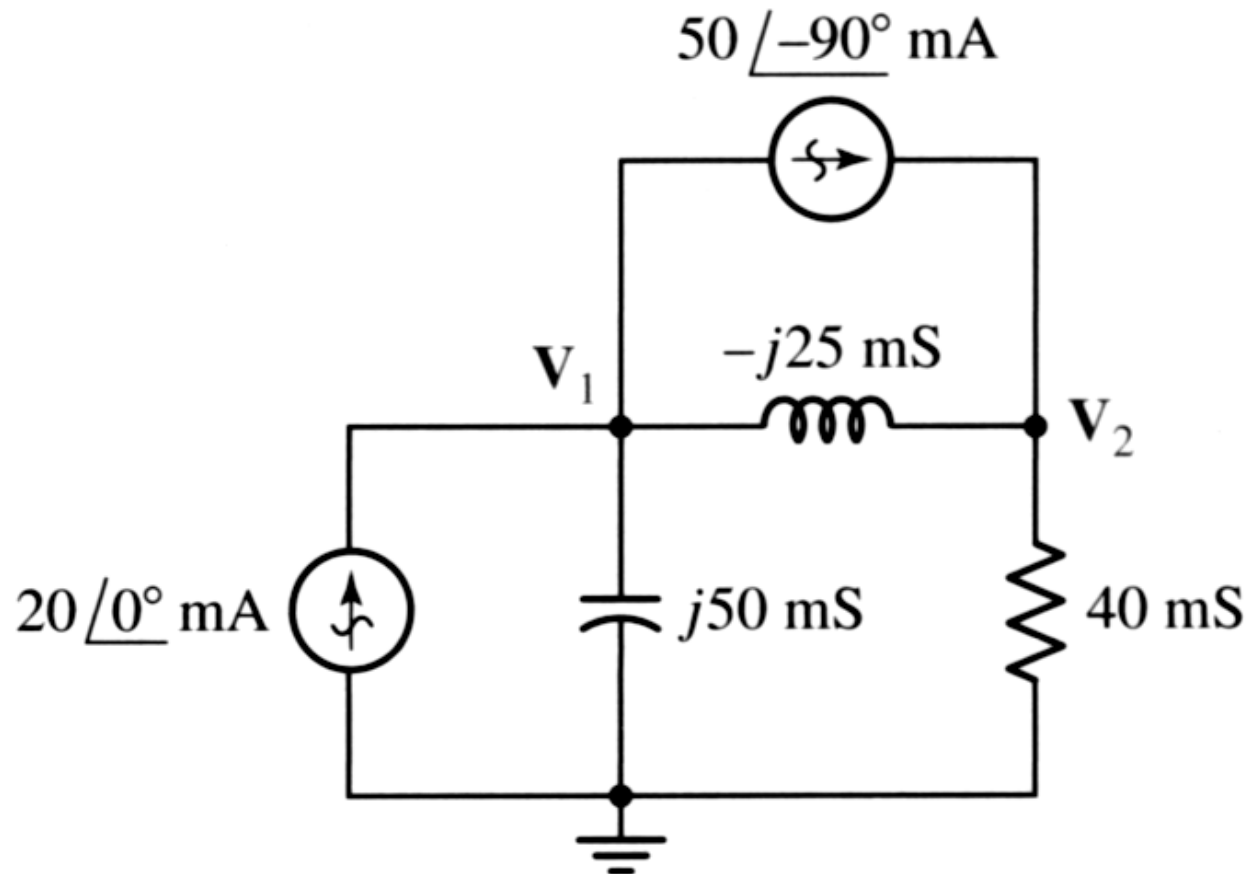
# Practice: 10.12

Use nodal analysis on the circuit to find  $V_1$  and  $V_2$ .



# Practice: 10.12

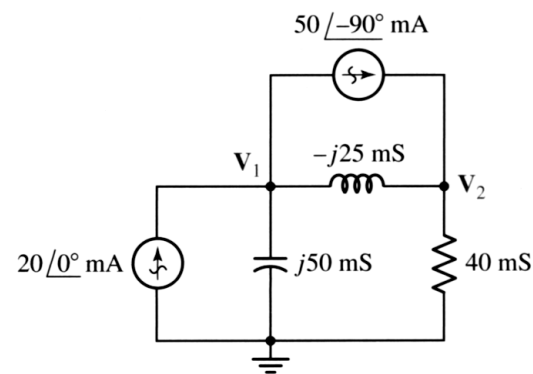

$$-50\angle -90^\circ + 20 = j50\mathbf{V}_1 - j25(\mathbf{V}_1 - \mathbf{V}_2) \quad [1]$$

$$50\angle -90^\circ = 40\mathbf{V}_2 - j25(\mathbf{V}_2 - \mathbf{V}_1) \quad [2]$$

- rewrite, grouping terms:

$$20 + j50 = j25\mathbf{V}_1 + j25\mathbf{V}_2 \quad [1]$$

$$-j50 = j25\mathbf{V}_1 + (40 - j25)\mathbf{V}_2 \quad [2]$$

- Solving,


$$\mathbf{V}_1 = 0.9756 + j0.4195 = \underline{1.062\angle 23.27^\circ \text{ V}}$$

and

$$\mathbf{V}_2 = 1.024 - j1.2195 = \underline{1.593\angle -49.97^\circ \text{ V}}$$

# Nodal and Mesh Analysis:

Example: find  $I_1$  and  $I_2$



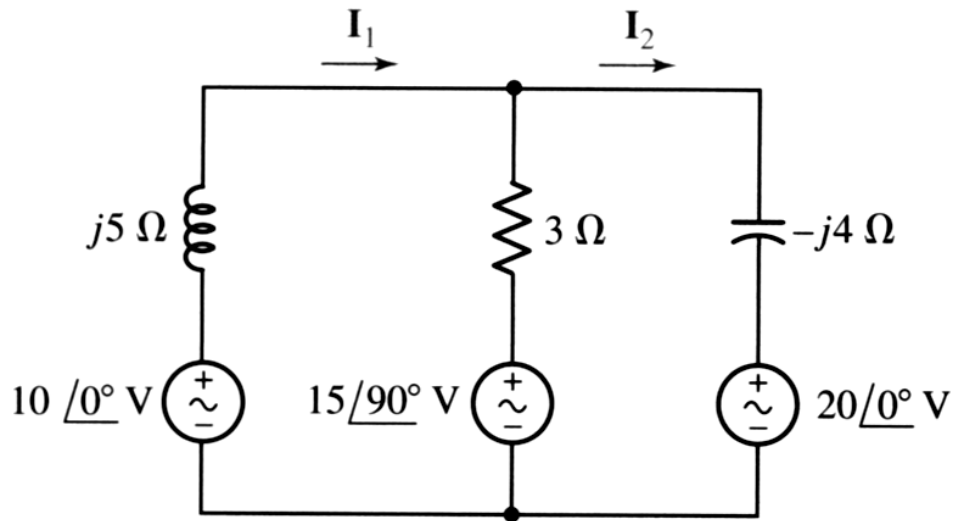


$$-10 \angle 0^\circ + j5(I_1) + 3(I_1 - I_2) + 15 \angle 90^\circ = 0$$

$$-15 \angle 90^\circ + 3(I_2 - I_1) - j4(I_2) + 20 \angle 0^\circ = 0$$


# Superposition:

Example: find  $V_1$

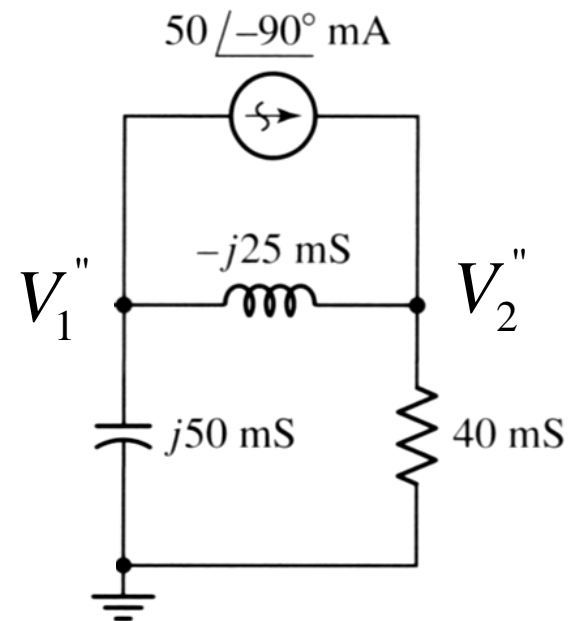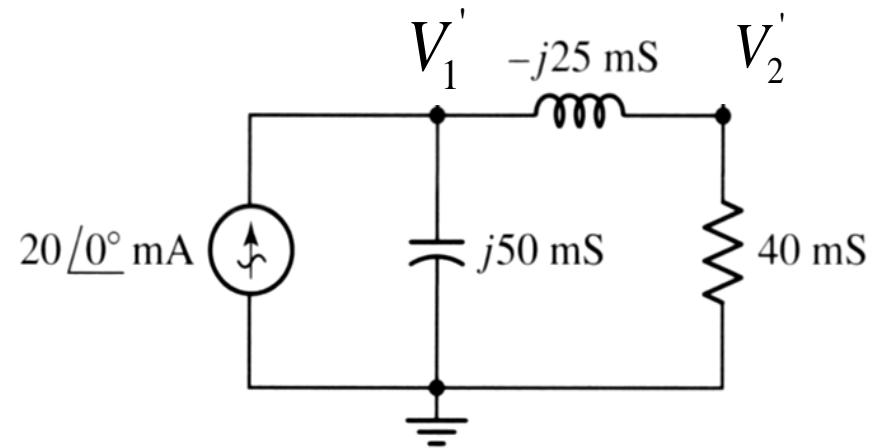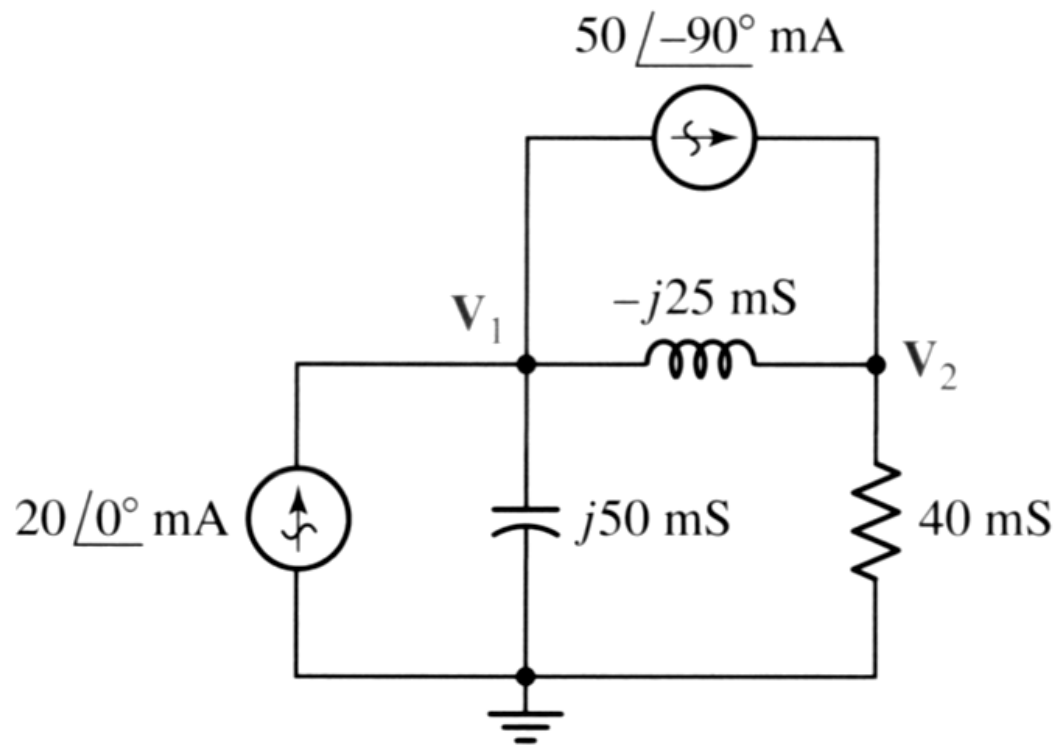

# Superposition:

Example: find  $V_1$

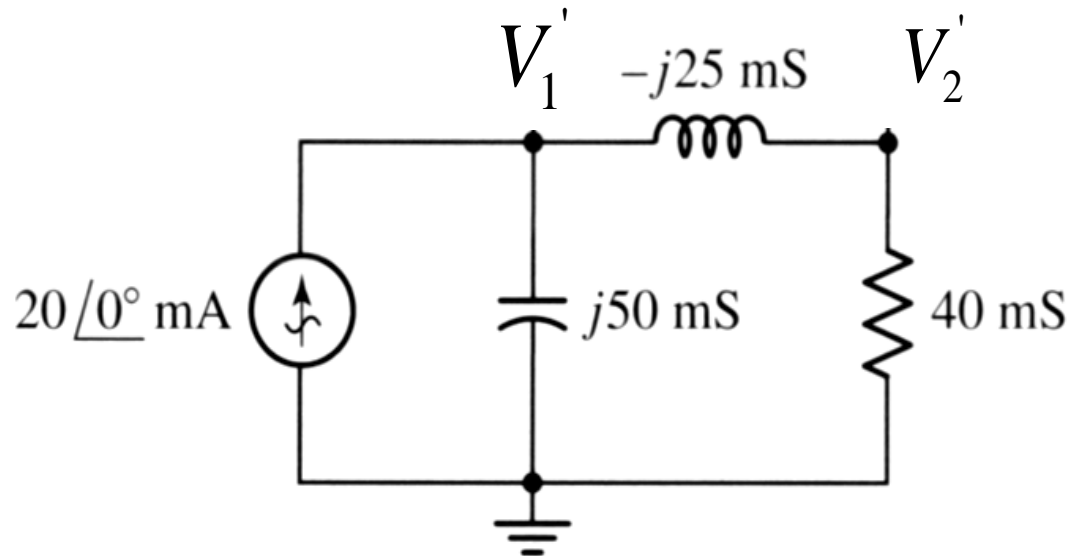


$$\begin{aligned}
 V_1' &= \frac{I}{Y} = \frac{20}{j50 + \frac{(40) \cdot (-j25)}{40 - j25}} \\
 &= 0.1951 - j0.5561
 \end{aligned}$$

# Superposition:

Example: find  $V_1$


$$V_1'' = \frac{-I}{j50m}$$

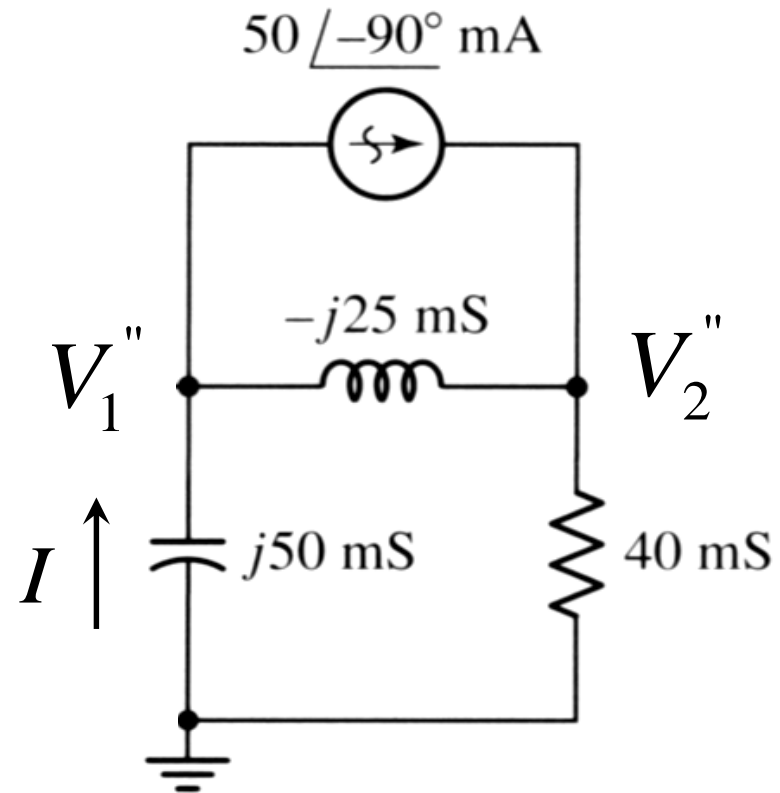

$$I = \frac{\left( \frac{1}{-j25m} \right)}{\left( \frac{1}{40m} + \frac{1}{j50m} \right) + \left( \frac{1}{-j25m} \right)} \cdot (50 \angle -90^\circ \text{ m})$$

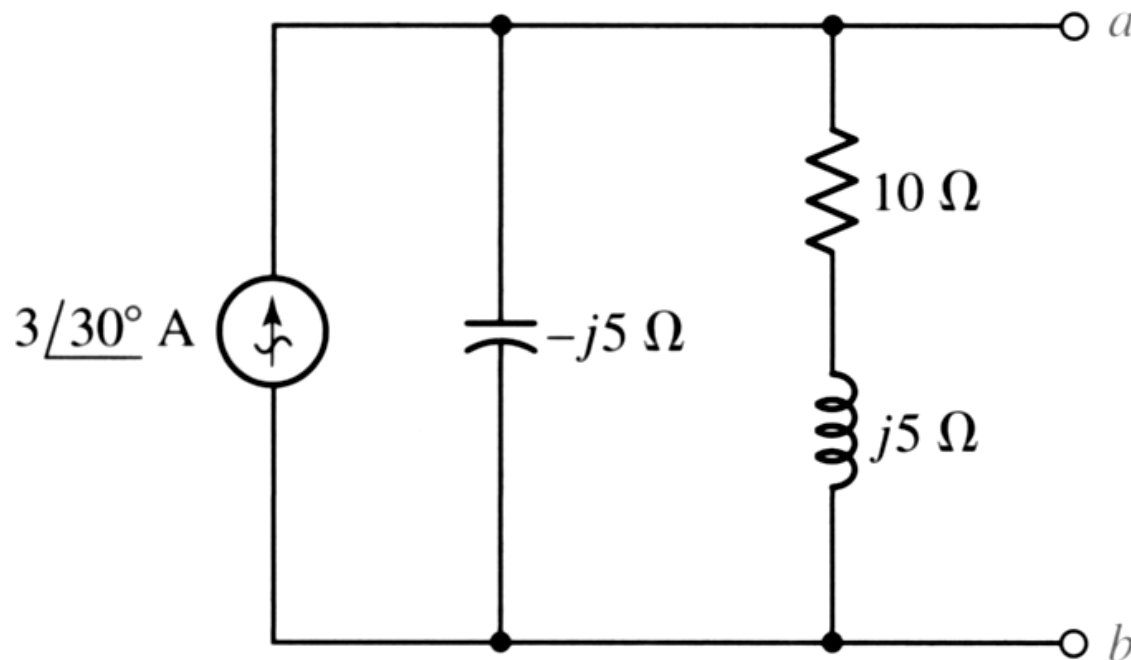
# Practice: 10.15

For the circuit, find the (a) open-circuit voltage  $V_{ab}$ ; (b) downward current in a short circuit between a and b; (c) Thevenin-equivalent impedance  $Z_{ab}$  in parallel with the current source.





# Practice: 10.15

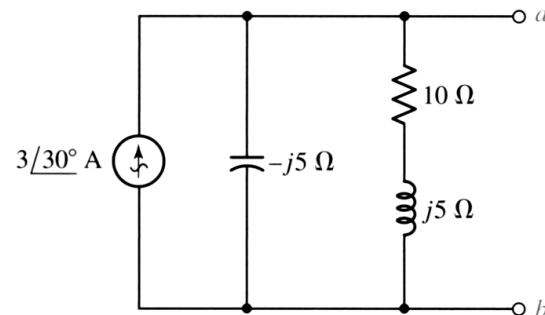

$$(a) \quad \mathbf{V}_{ab} = (3\angle 30^\circ) [-j5 // (10 + j5)] = \underline{16.77\angle -33.43^\circ \text{ V}}$$


$$(b) \quad \mathbf{Z}_{ab} = -j5 // (10 + j5) = 5.59\angle -63.43^\circ \Omega$$

$$\mathbf{I}_{SC} = \frac{\mathbf{V}_{ab}}{\mathbf{Z}_{ab}} = 3\angle 30^\circ \text{ A} = \underline{2.598 + j1.5 \text{ A}}$$


$$(c) \quad \mathbf{Z}_{ab} = 5.59\angle -63.43^\circ \Omega = \underline{2.5 - j5 \Omega}$$
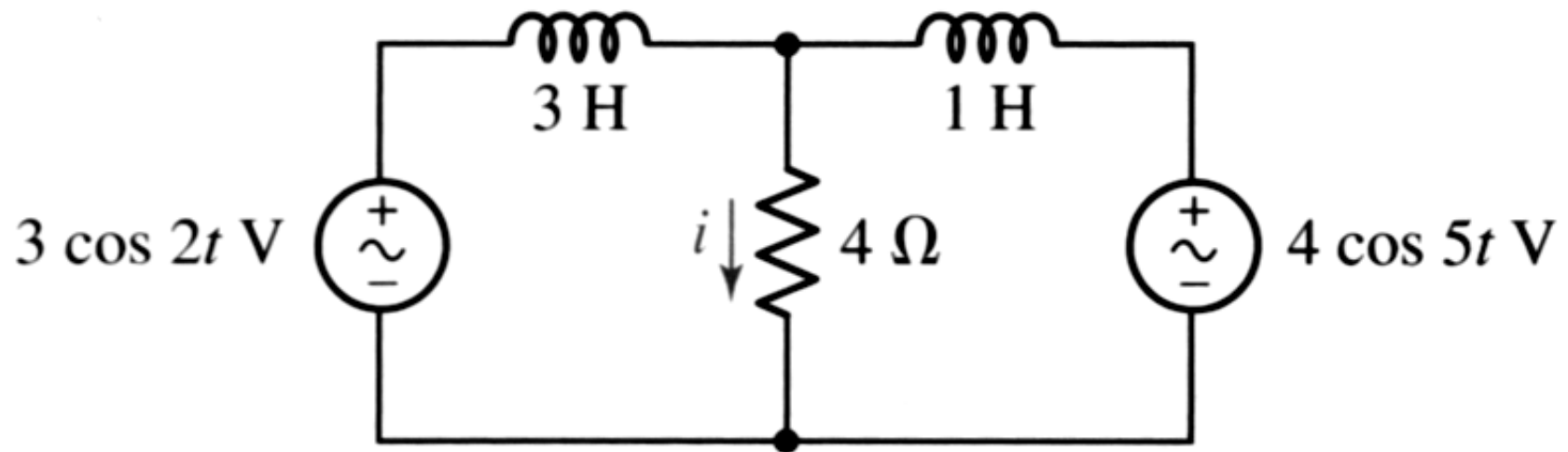
# Practice: 10.16


Determine the current  $i$  through the  $4\text{-}\Omega$  resistor



# Practice: 10.16

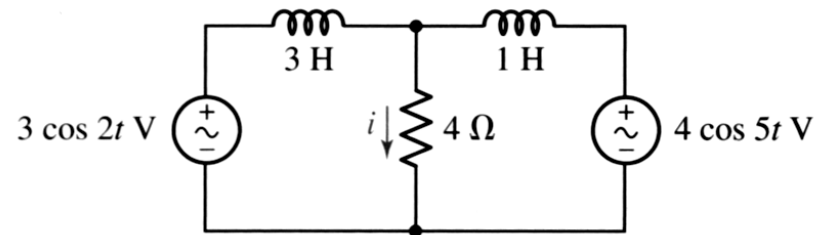


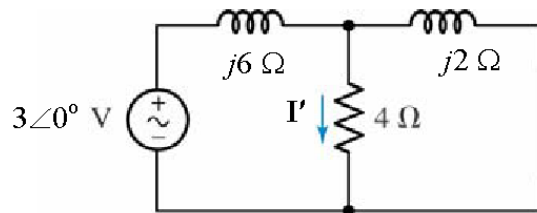- Since the two sources do not operate at the same frequency, we must use superposition in the time domain.



$$\begin{aligned} V'_{4\Omega} &= 3 \frac{(4 // j2)}{j6 + (4 // j2)} \\ &= 3 \frac{0.8 + j1.6}{0.8 + j7.6} \\ &= 0.7022 \angle -20.56^\circ \text{ V} \end{aligned}$$
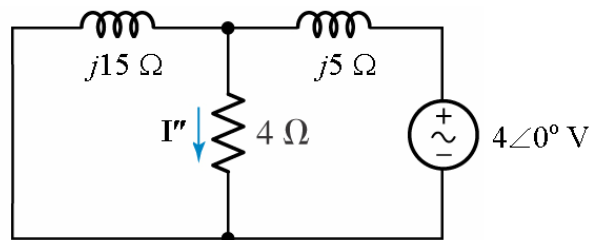
$$\begin{aligned} I' &= \frac{1}{4} V'_{4\Omega} = 175.6 \angle -20.56^\circ \text{ mA} \\ \text{so } i'(t) &= 175.6 \cos(2t - 20.56^\circ) \text{ mA} \end{aligned}$$




$$\begin{aligned} V''_{4\Omega} &= 4 \frac{(4 // j15)}{j5 + (4 // j15)} = 4 \frac{(3.734 + j0.9959)}{3.734 + j5.996} \text{ V} \\ &= 2.188 \angle -43.15^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} I'' &= \frac{1}{4} V''_{4\Omega} = 547.1 \angle -43.15^\circ \text{ A} \\ \text{so } i''(t) &= 547.1 \cos(5t - 43.15^\circ) \text{ mA} \end{aligned}$$

and since  $i(t) = i'(t) + i''(t)$ ,  $i(t) = \underline{175.6 \cos(2t - 20.56^\circ) + 547.1 \cos(5t - 43.15^\circ) \text{ mA}}$


# Phasor Diagram:

---

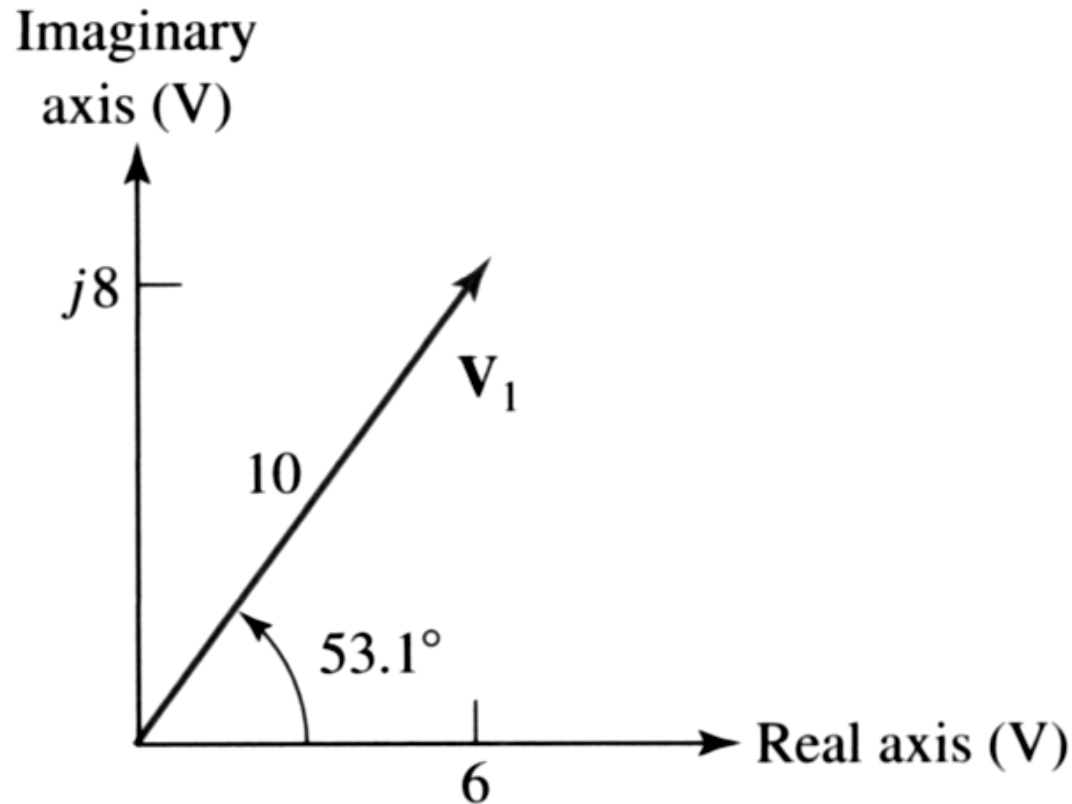


$$V_1 = 6 + j8 = 10 \angle 53.1^\circ$$

# Phasor Diagram:

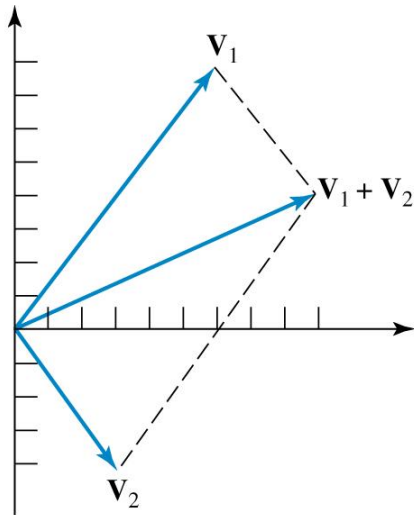

(a)

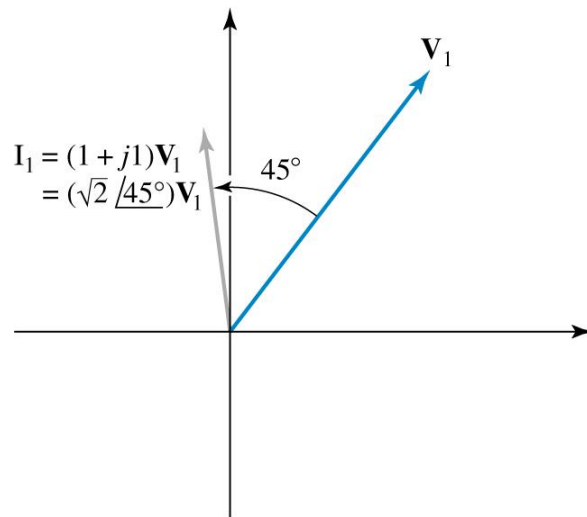
- (a) A phasor diagram showing the sum of  $\mathbf{V}_1 = 6 + j8$  V and  $\mathbf{V}_2 = 3 - j4$  V,  $\mathbf{V}_1 + \mathbf{V}_2 = 9 + j4$  V =  $9.85 \angle 24.0^\circ$  V.




(b)

- (b) The phasor diagram shows  $\mathbf{V}_1$  and  $\mathbf{I}_1$ , where  $\mathbf{I}_1 = \mathbf{Y}\mathbf{V}_1$  and  $\mathbf{Y} = 1 + j$  S =  $1.4 \angle 45^\circ$  S. The current and voltage amplitude scales are different.

# Phasor Diagram:


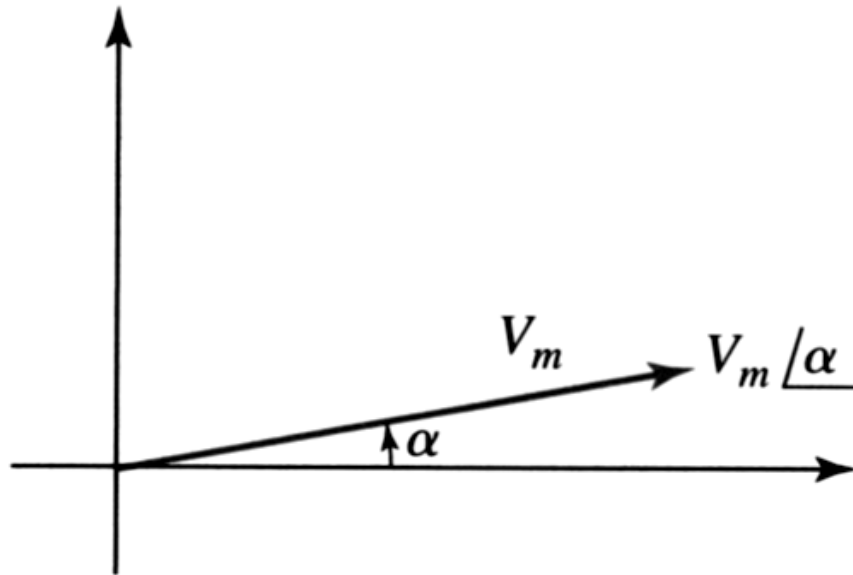


(a)


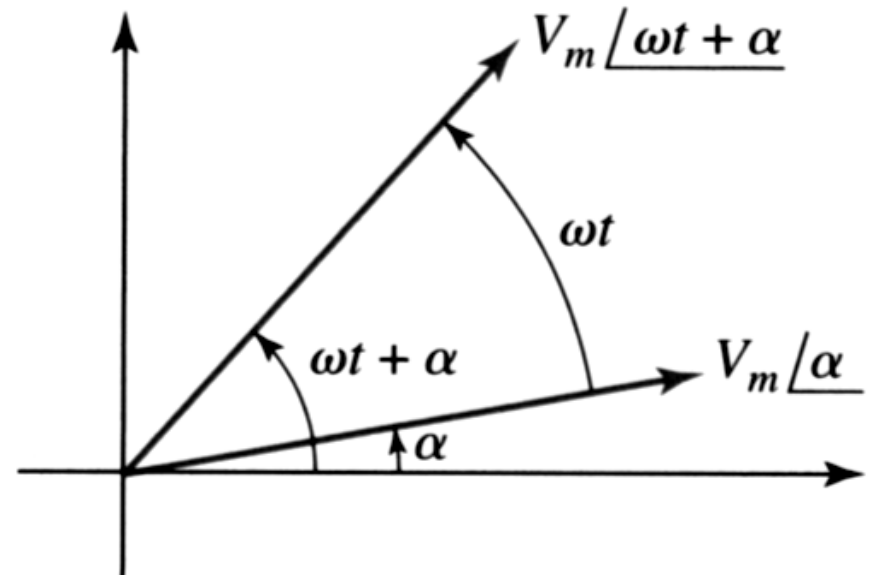


(b)

# Phasor Diagram:

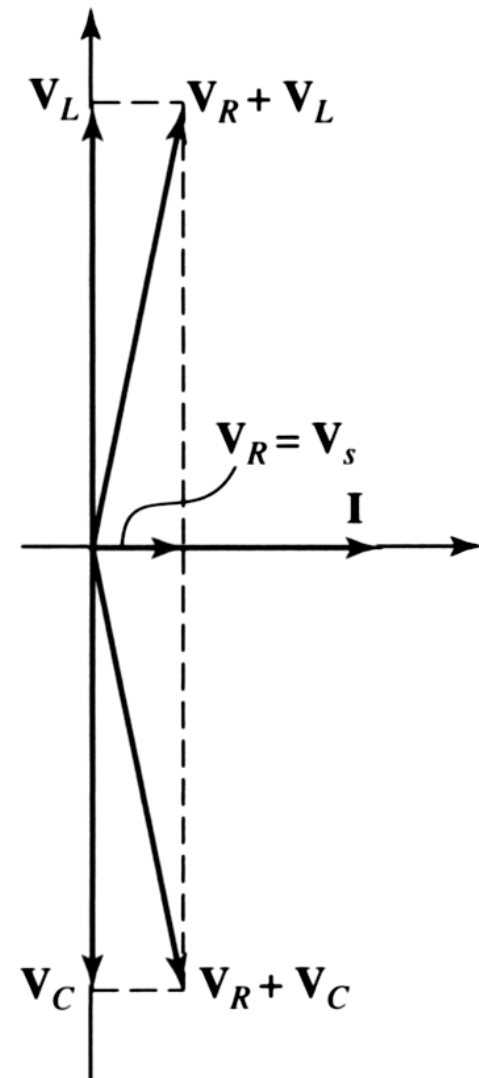
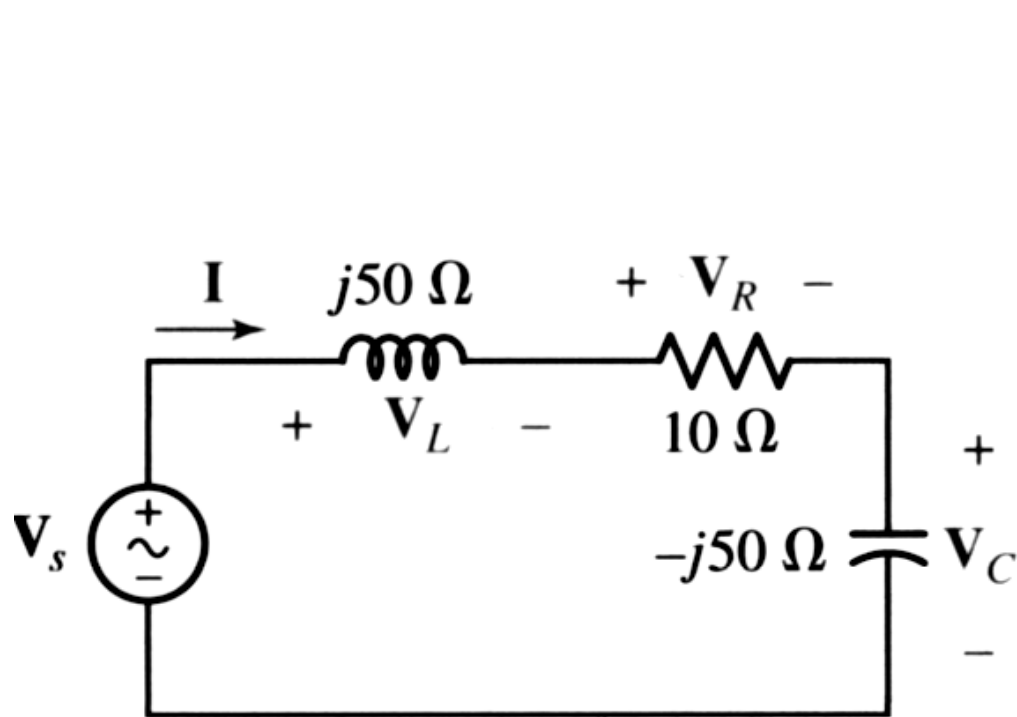


# Phasor Diagram:

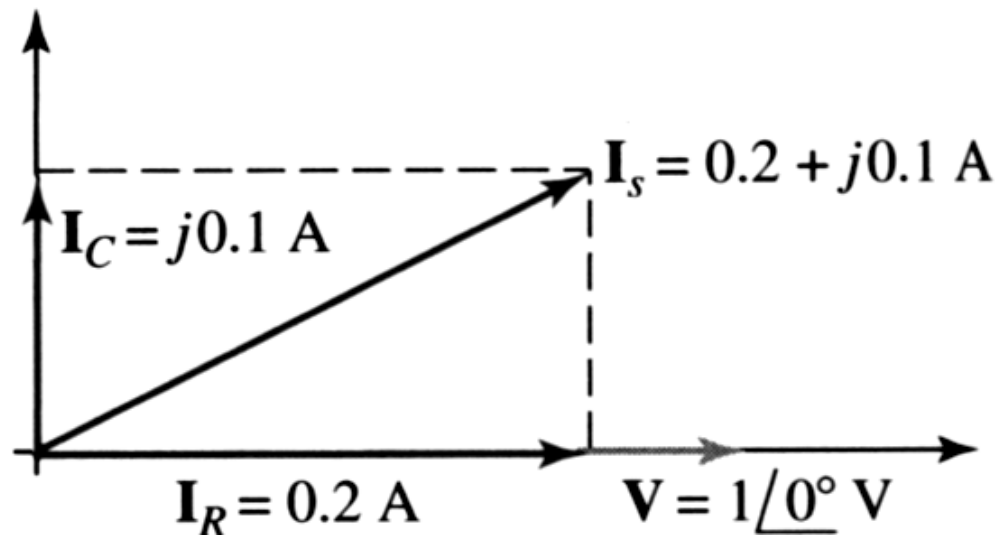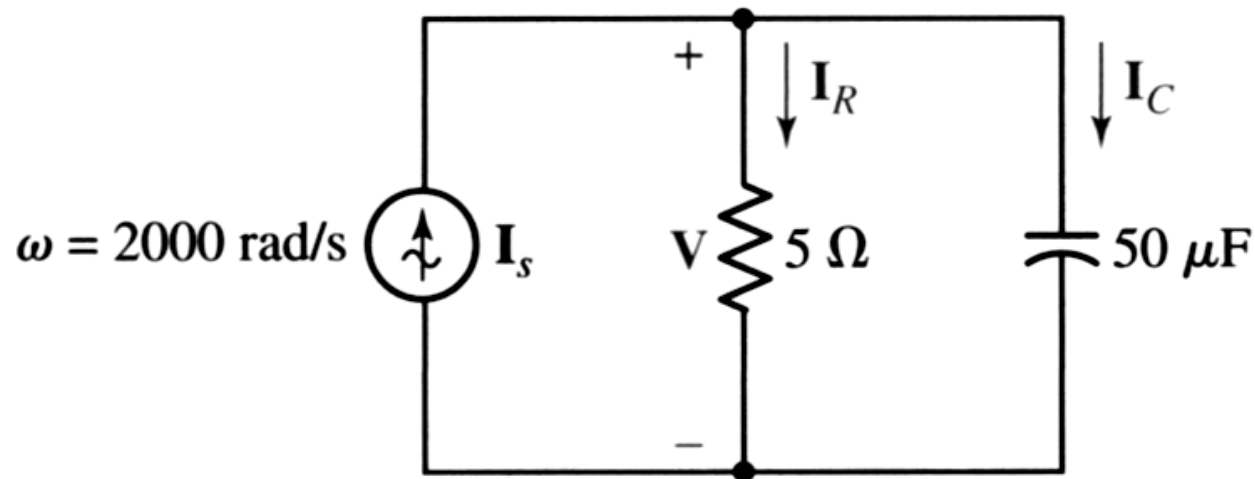







# Example:

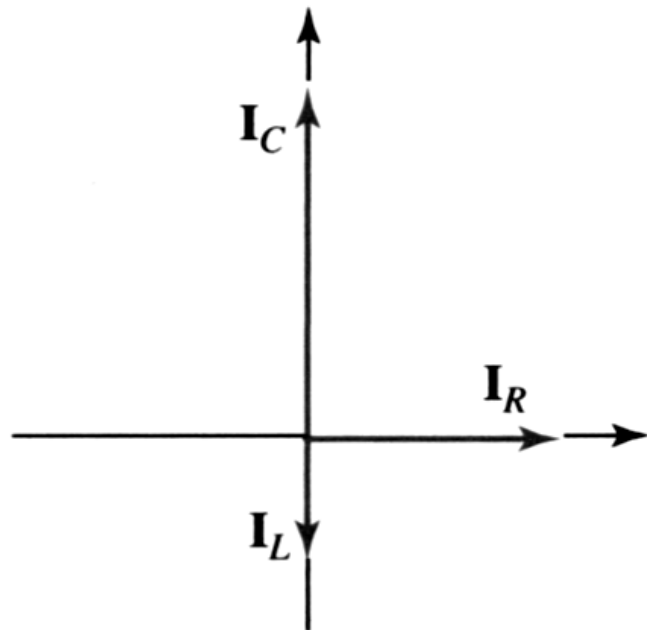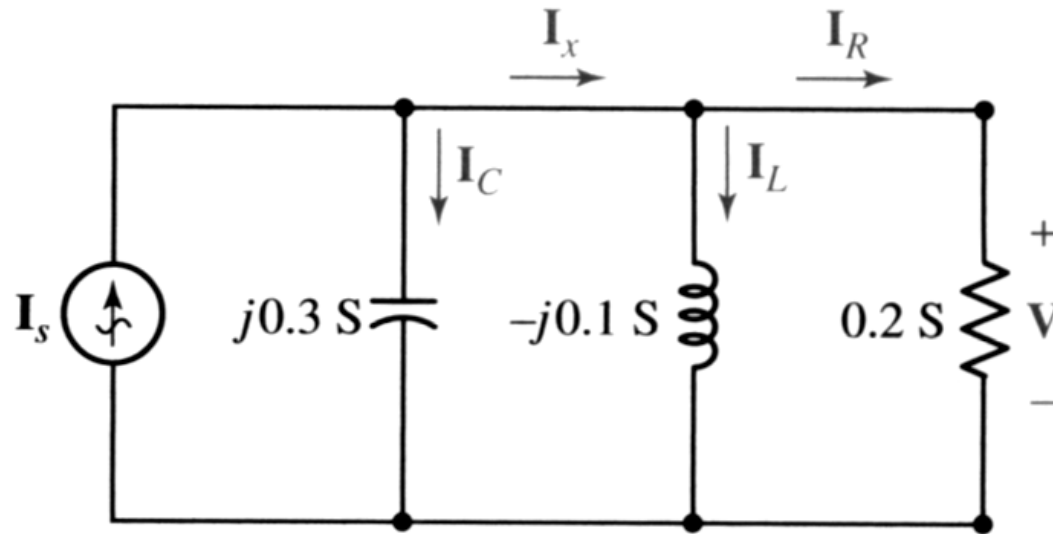


Select  $\mathbf{V} = 1 \angle 0^\circ$

$$\begin{aligned} & ; \quad \mathbf{I}_R = (0.2) \cdot 1 \angle 0^\circ \\ & \mathbf{I}_L = (-j0.1) \cdot 1 \angle 0^\circ = 0.1 \angle -90^\circ \\ & \mathbf{I}_C = (j0.3) \cdot 1 \angle 0^\circ = 0.3 \angle 90^\circ \end{aligned}$$


# Example:

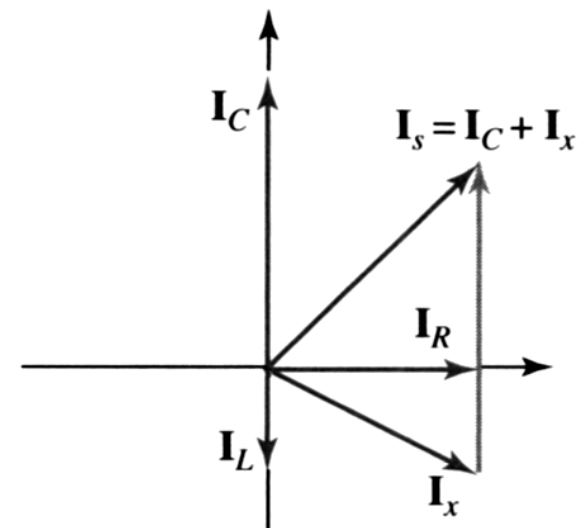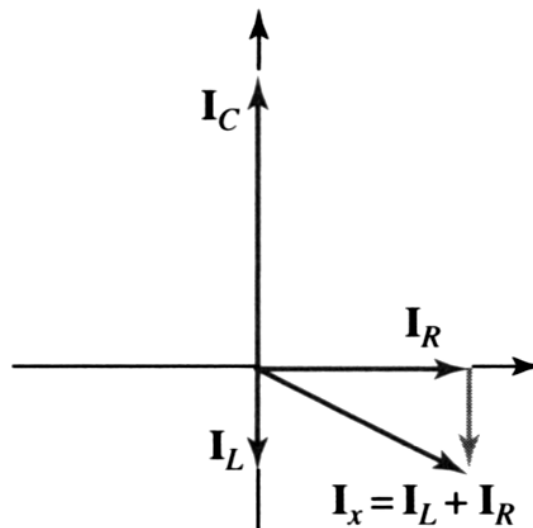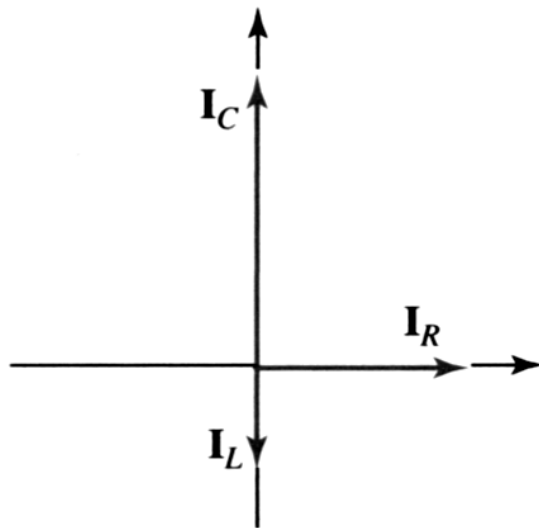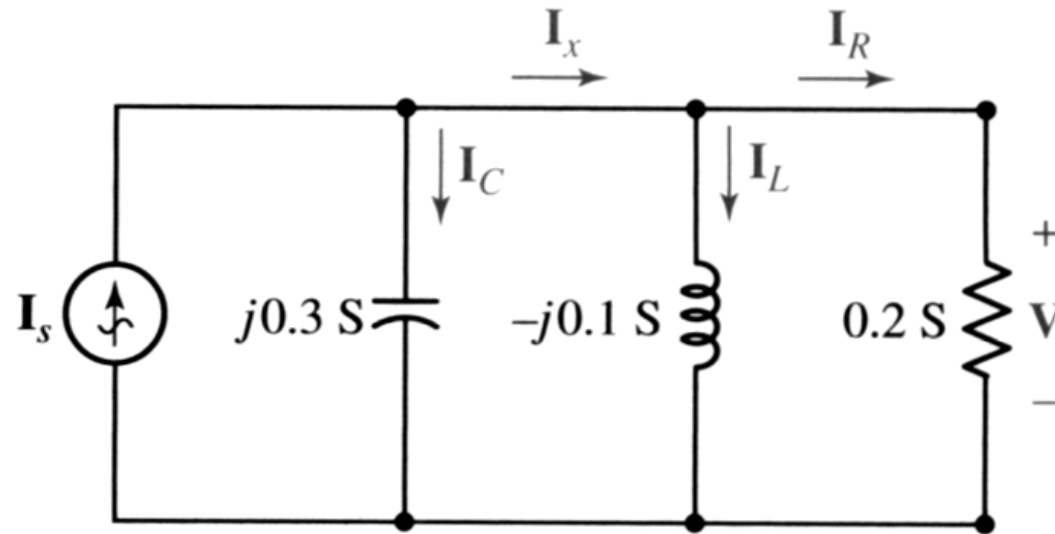

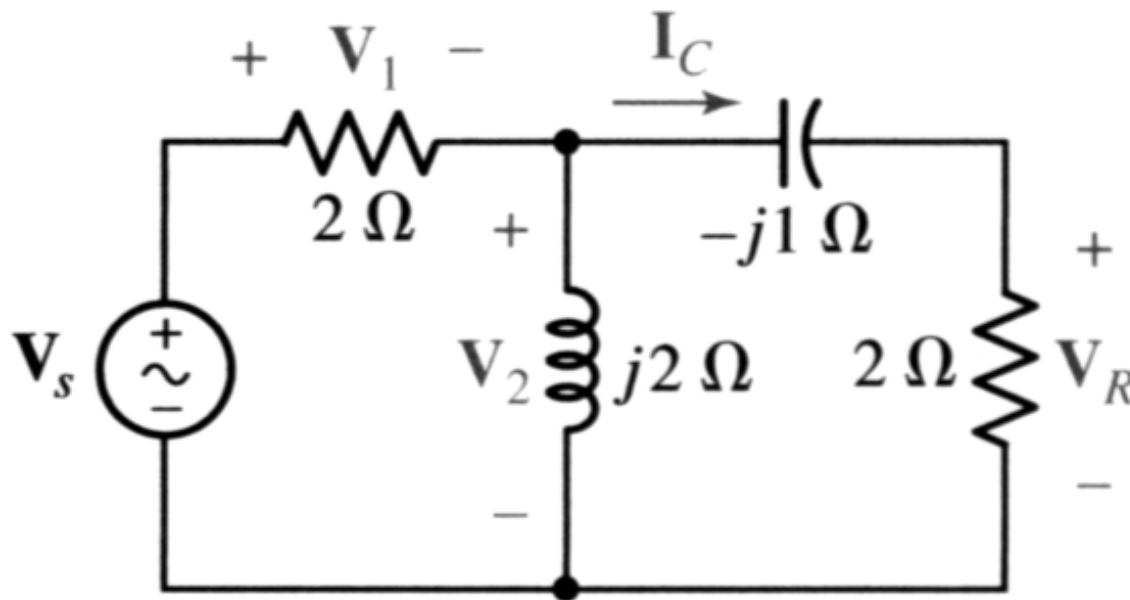Select some convenient reference value for  $\mathbf{I}_C$  in the circuit, draw a phasor diagram showing  $\mathbf{V}_R$ ,  $\mathbf{V}_2$ ,  $\mathbf{V}_1$ , and  $\mathbf{V}_s$ , and measure the ratio of the lengths of (a)  $\mathbf{V}_s$  to  $\mathbf{V}_1$ ; (b)  $\mathbf{V}_1$  to  $\mathbf{V}_2$ ; (c)  $\mathbf{V}_s$  to  $\mathbf{V}_R$



# Practice: 10.17

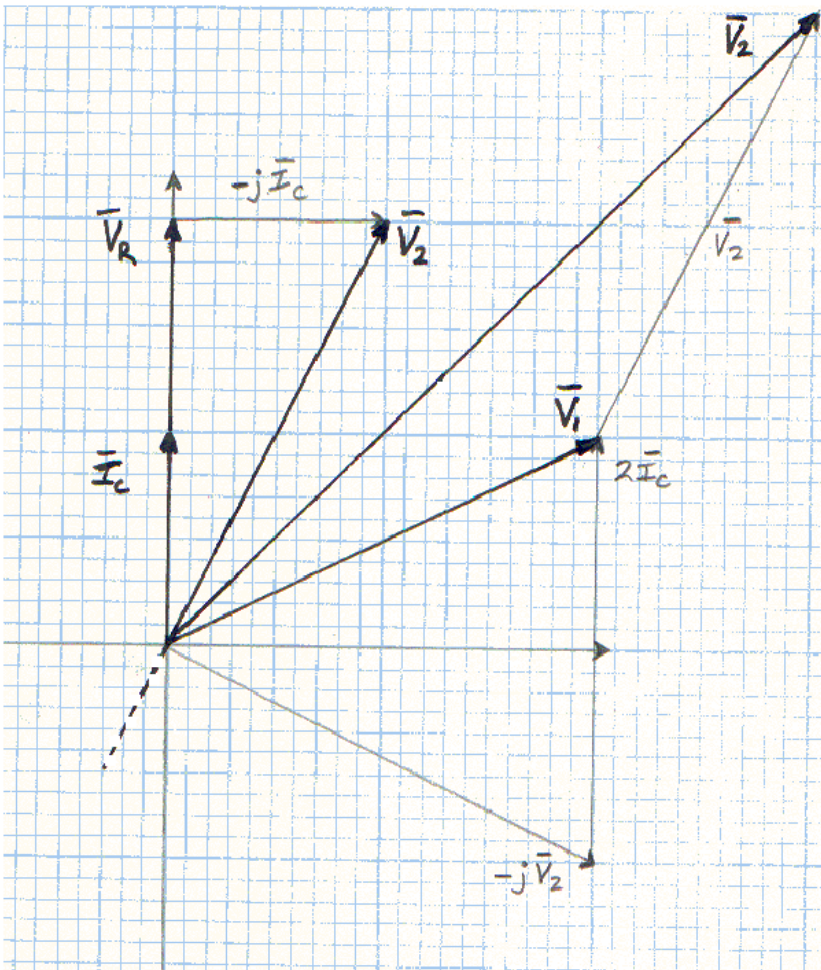

$$\bar{V}_R = 2\bar{I}_C$$

$$\bar{V}_2 = -j\bar{I}_C + \bar{V}_R = \bar{I}_C \angle -90^\circ + \bar{V}_R$$

$$\bar{V}_1 = 2 \left( \frac{\bar{V}_2}{j2} + \bar{I}_C \right) = \bar{V}_2 \angle -90^\circ + 2\bar{I}_C$$

$$\bar{V}_s = \bar{V}_1 + \bar{V}_2$$

Using a ruler on the actual size graph (10 small squares = 25.5 mm):  
 $V_s = 10.8$  mm,  $V_1 = 5.7$  mm,  
 $V_2 = 5.7$  mm,  $V_R = 5.1$  mm.


(a)  $V_s / V_1 = \underline{1.90}$

(b)  $V_1 / V_2 = \underline{1.00}$

(c)  $V_s / V_R = \underline{2.12}$
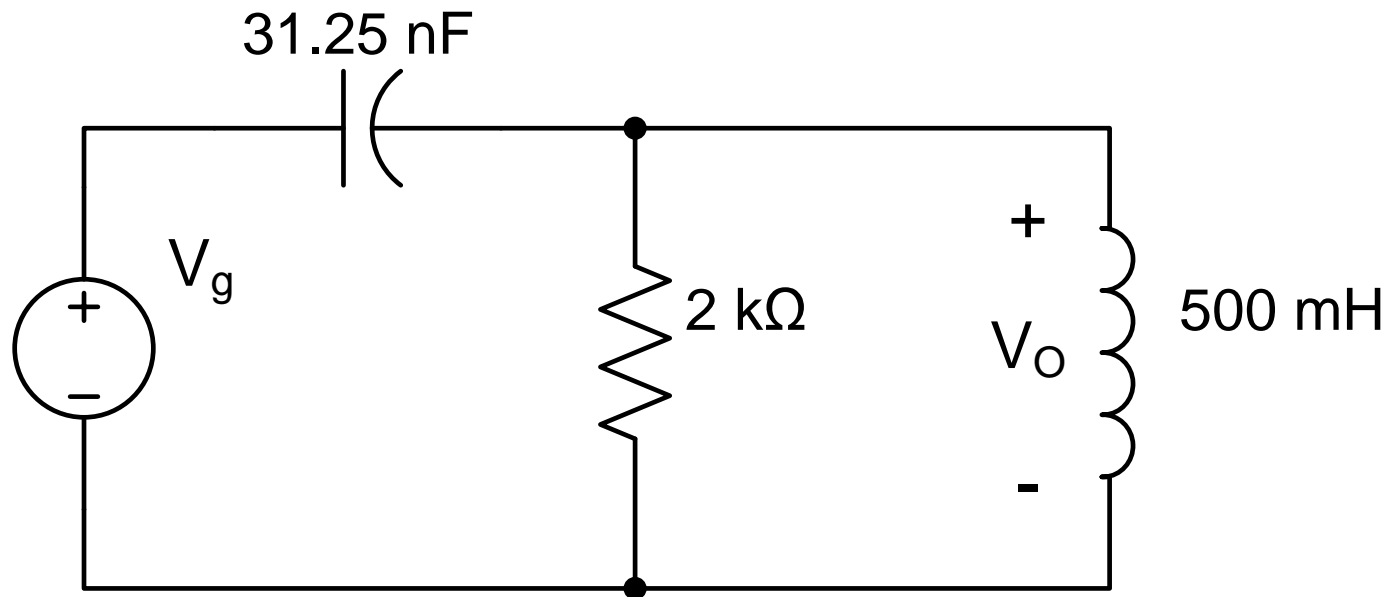
# Ex:


The circuit is operating in the sinusoidal steady state. Find the steady-state expression for  $v_o(t)$  if  $v_g(t) = 64 \cos 8000t$  V.



$$\frac{1}{j\omega C} = \frac{10^9}{(31.25)(8000)} = -j4000 \Omega$$

$$j\omega L = j8000(500)10^{-3} = j4000 \Omega$$

$$V_g = 64\angle 0^\circ \text{ V}$$

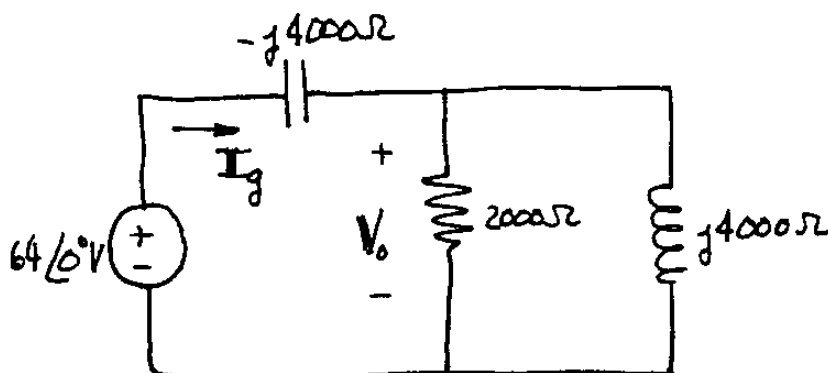

$$Z_e = \frac{(2000)(j4000)}{2000 + j4000} = 1600 + j800 \Omega$$

$$Z_T = 1600 + j800 - j4000 = 1600 - j3200 \Omega$$

$$I_g = \frac{64\angle 0^\circ}{1600 - j3200} = 8 + j16 \text{ mA}$$

$$V_o = Z_e I_g = (1600 + j800)(0.008 + j0.016) = j32 = 32\angle 90^\circ$$

$$v_o = 32 \cos(8000t + 90^\circ) \text{ V}$$



**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**