

---

ENE 104

# Electric Circuit Theory

---



## Lecture 03: Basic Nodal and Mesh Analysis

---

**Week #3 : Dejwoot KHAWPARISUTH**

office: CB40906 Tel: 02-470-9065

Email: [dejwoot.kha@mail.kmutt.ac.th](mailto:dejwoot.kha@mail.kmutt.ac.th)

<http://webstaff.kmutt.ac.th/~dejwoot.kha/>


# Objectives :

---

- Implementation of the **nodal analysis**
- Implementation of the **mesh analysis**
- **Supernodes** and **Supermeshes**
- Basic computer-aided circuit analysis

# Example: 4.2

find the nodes voltages:

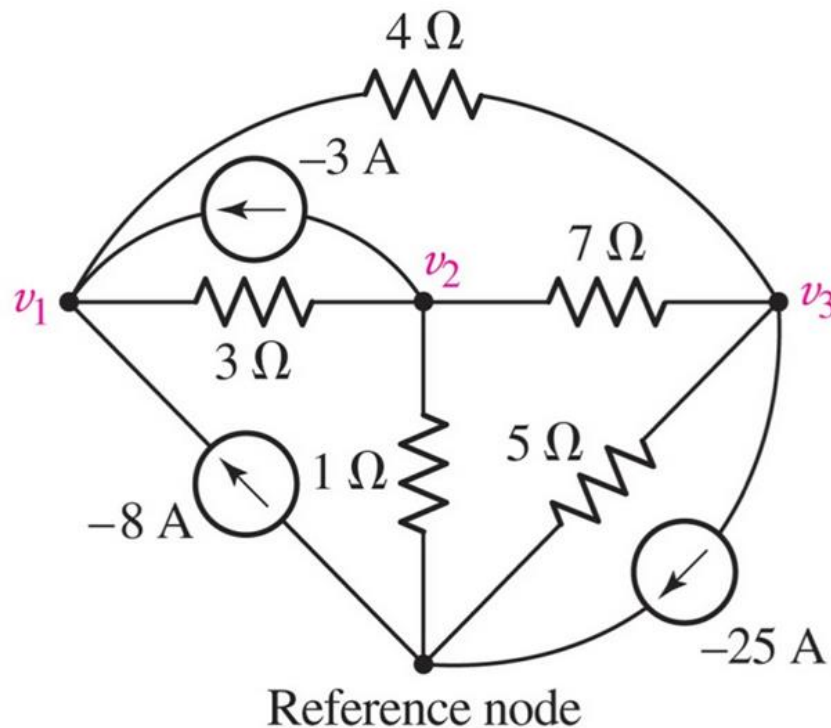

A KCL equation for node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

Node 2:


$$\frac{v_2 - v_3}{7} + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) = 0$$

Node 3:


$$\frac{v_3 - v_2}{7} + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$

# Practice: 4.2

---

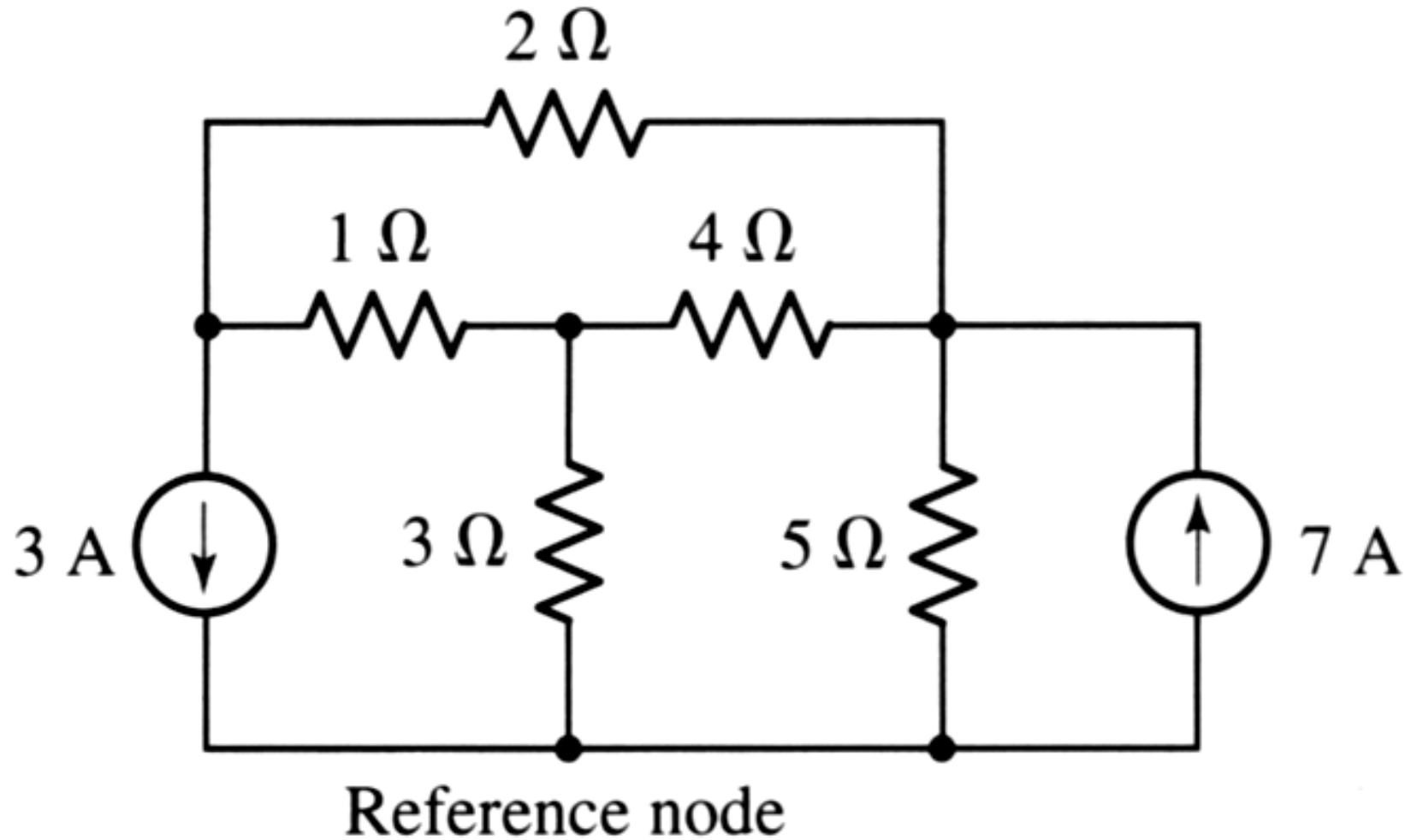

# Practice: 4.2

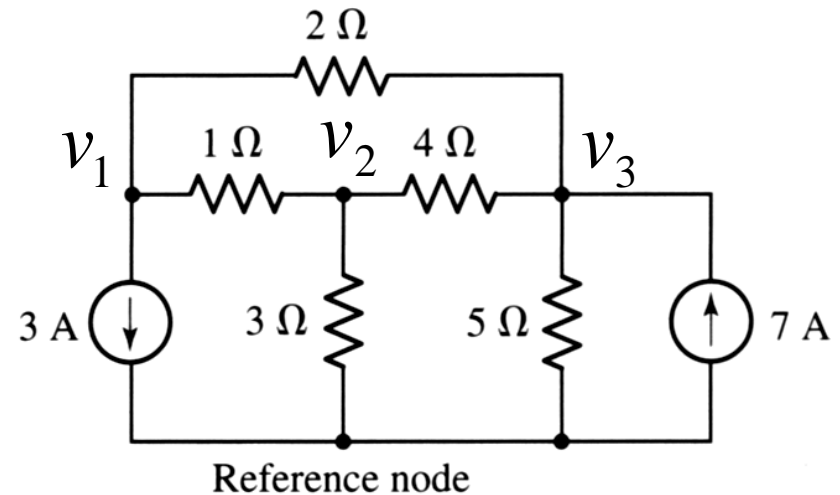


Node 1: 
$$3 + \frac{v_1 - v_3}{2\Omega} + \frac{v_1 - v_2}{1\Omega} = 0$$

Node 2: 
$$\frac{v_2 - v_1}{1\Omega} + \frac{v_2}{3\Omega} + \frac{v_2 - v_3}{4\Omega} = 0$$

Node 3: 
$$-7 + \frac{v_3 - v_1}{2\Omega} + \frac{v_3 - v_2}{4\Omega} + \frac{v_3}{5\Omega} = 0$$


# The Supernode:

find the nodes voltages:

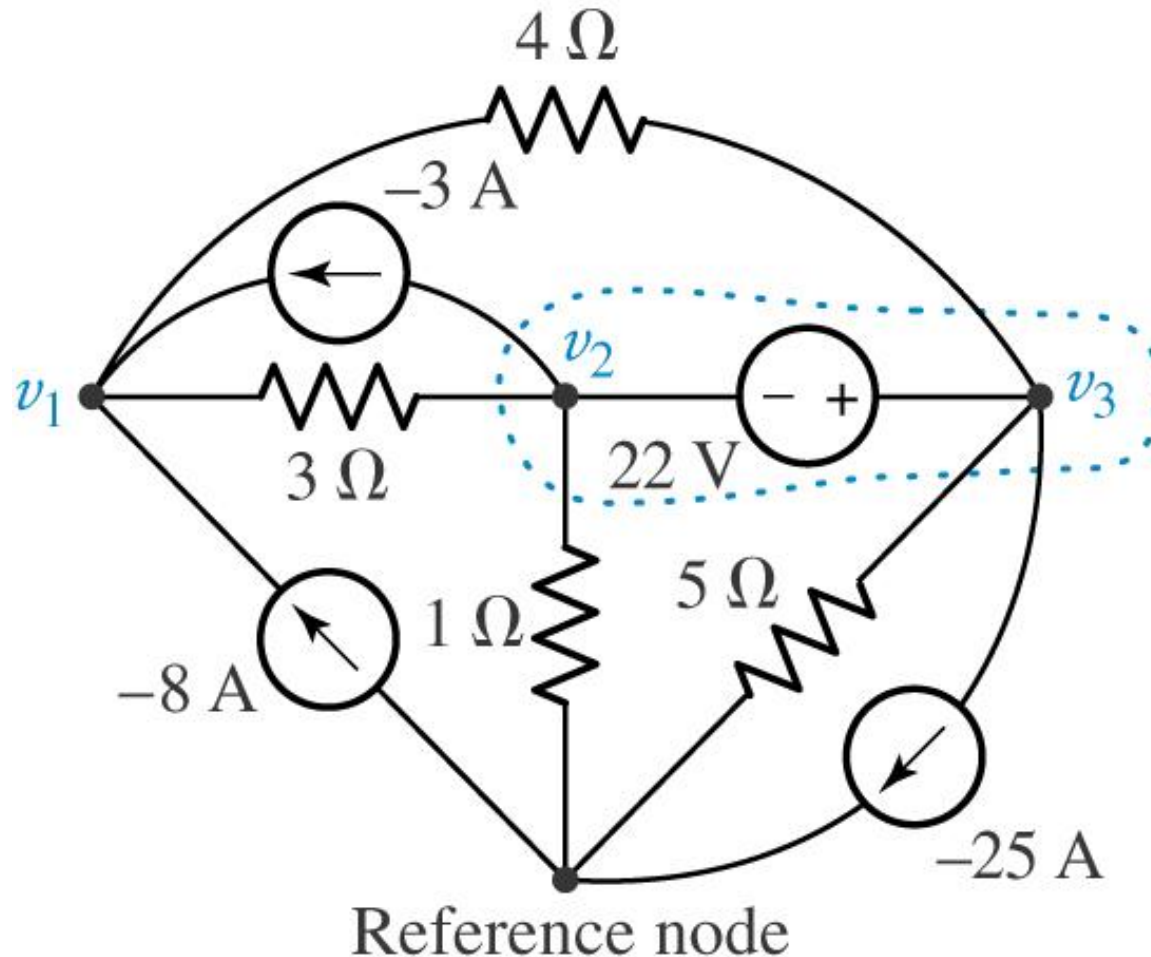

# The Supernode:

find the nodes voltages:

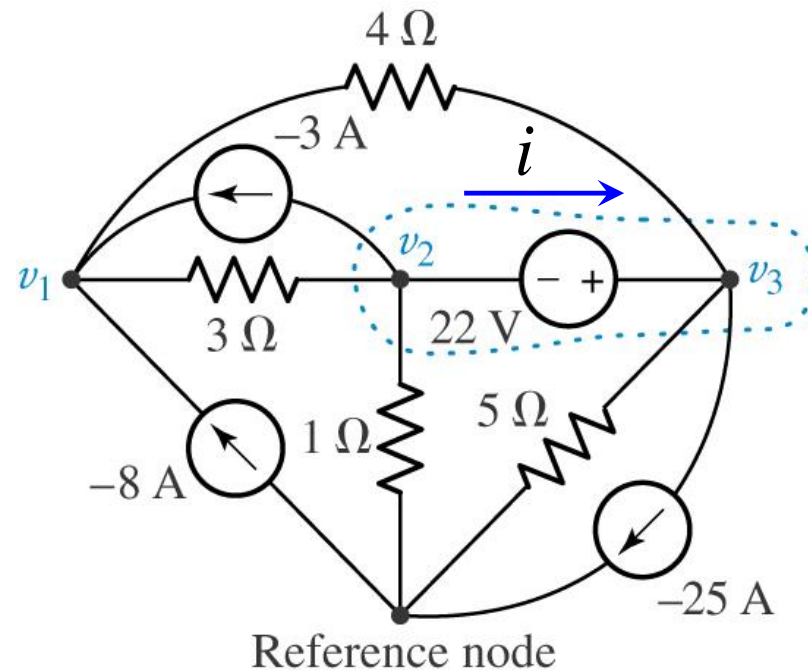

A KCL equation for  
Node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

Node 2:


$$i + \frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) = 0$$

Node 3:

$$-i + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$

# The Supernode:

find the nodes voltages:

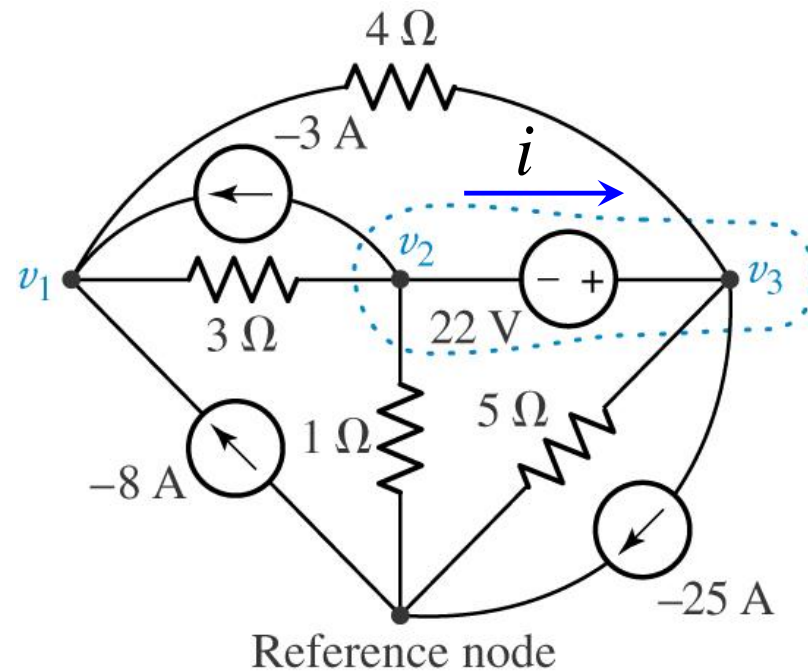

A KCL equation for Node 1:

$$\frac{v_1 - v_3}{4} - (-3) + \frac{v_1 - v_2}{3} - (-8) = 0$$

The Supernode (Node 2+3):

$$\frac{v_2}{1} + \frac{v_2 - v_1}{3} + (-3) + \frac{v_3}{5} + (-25) + \frac{v_3 - v_1}{4} = 0$$


And one additional equation:

$$v_3 - v_2 = 22$$



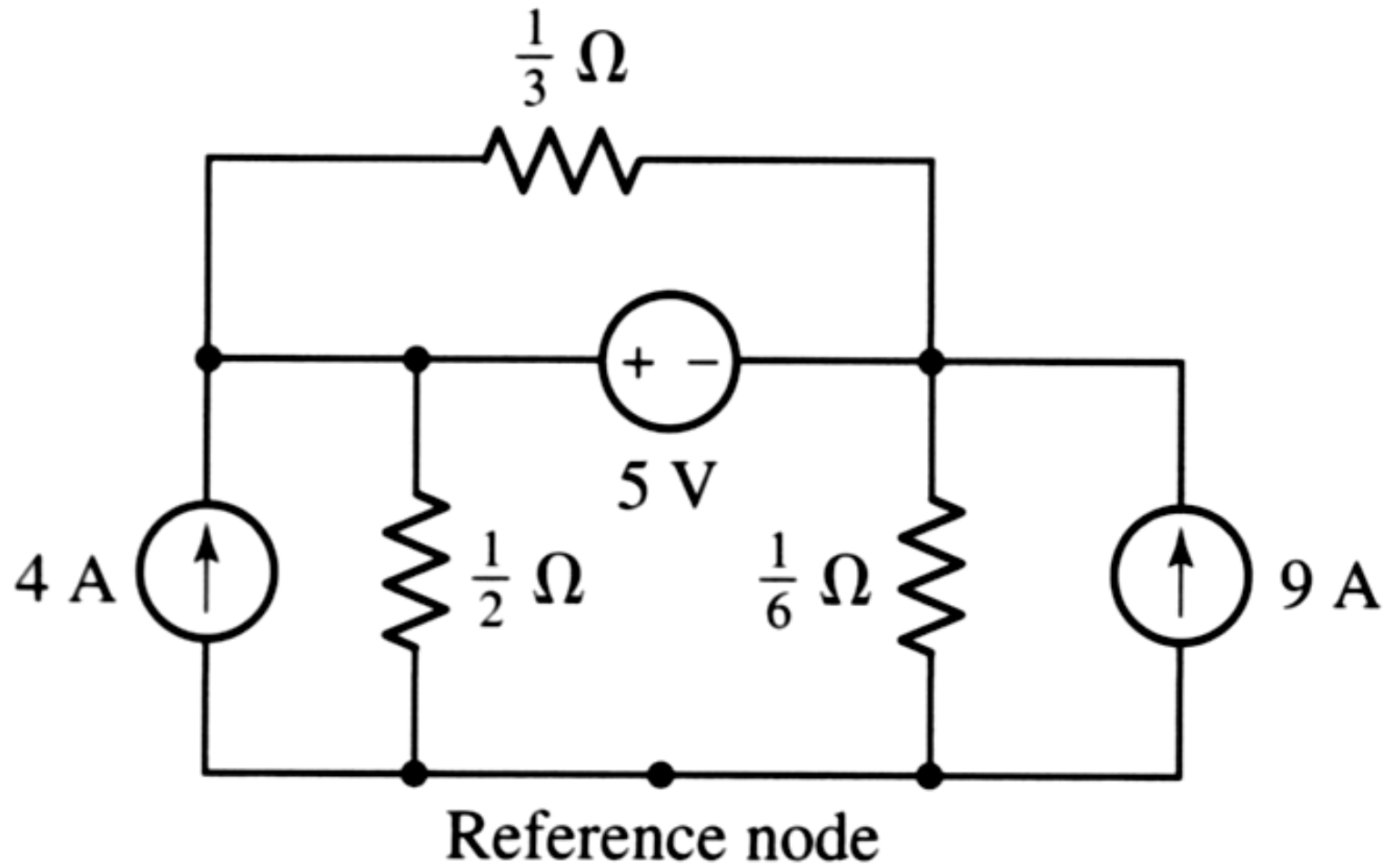
# Practice: 4.3

Compute the voltage across each current source



# Practice: 4.3

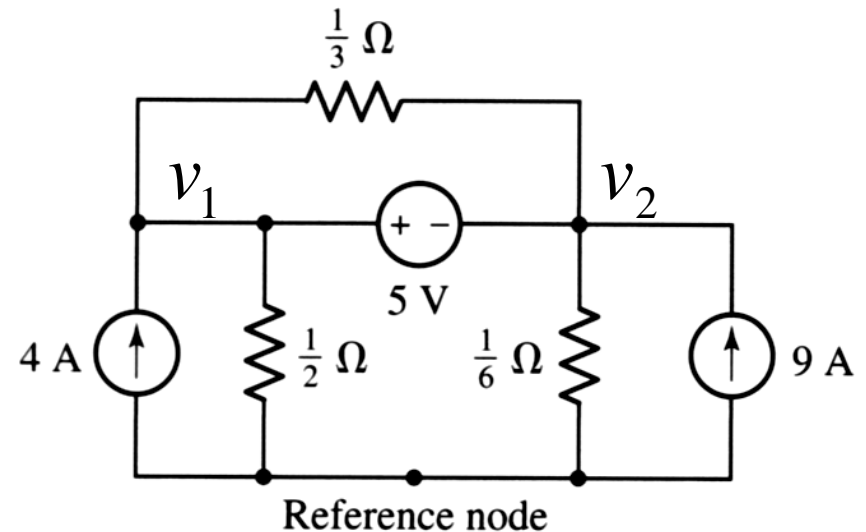

Node 1:

$$-4 + \frac{v_1 - v_2}{\frac{1}{3}\Omega} + i + \frac{v_1}{\frac{1}{2}\Omega} = 0$$

Node 2:


$$\frac{v_2 - v_1}{\frac{1}{3}\Omega} - i + \frac{v_2}{\frac{1}{6}\Omega} - 9 = 0$$

Supernode 1-2:

$$-4 + \frac{v_1 - v_2}{\frac{1}{3}\Omega} + \frac{v_1}{\frac{1}{2}\Omega} + \frac{v_2 - v_1}{\frac{1}{3}\Omega} + \frac{v_2}{\frac{1}{6}\Omega} - 9 = 0$$
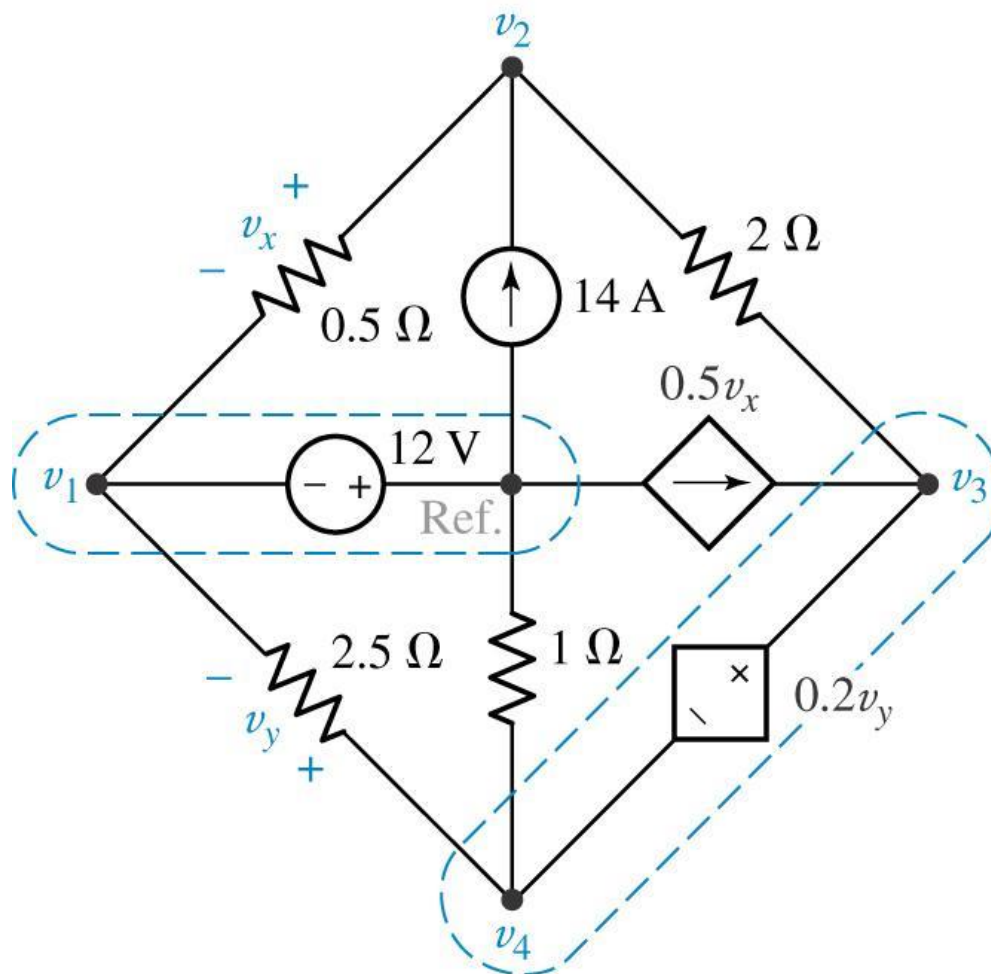
# Example: 4.4

Determine the node-to-reference voltages in the circuit below.



# Example:

**Determine the node-to-reference voltages in the circuit below.**

Node 1:

$$v_1 = -12 \text{ V.}$$

Node 2:

$$\frac{v_2 - v_1}{0.5} + \frac{v_2 - v_3}{2} - 14 = 0$$

The 3-4 supernode:


$$\frac{v_3 - v_2}{2} - 0.5v_x + \frac{v_4}{1} + \frac{v_4 - v_1}{2.5} = 0$$

$$\frac{v_3 - v_2}{2} - 0.5(v_2 - v_1) + \frac{v_4}{1} + \frac{v_4 - v_1}{2.5} = 0$$

Need an additional equation:


$$v_3 - v_4 = 0.2v_y$$

$$v_3 - v_4 = 0.2(v_4 - v_1)$$

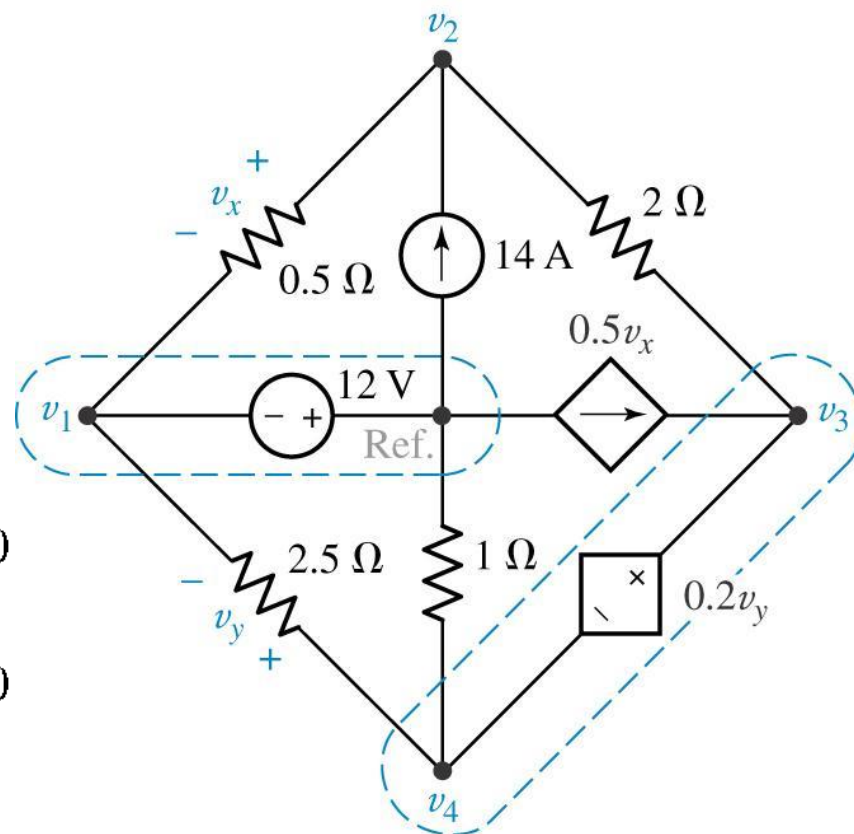

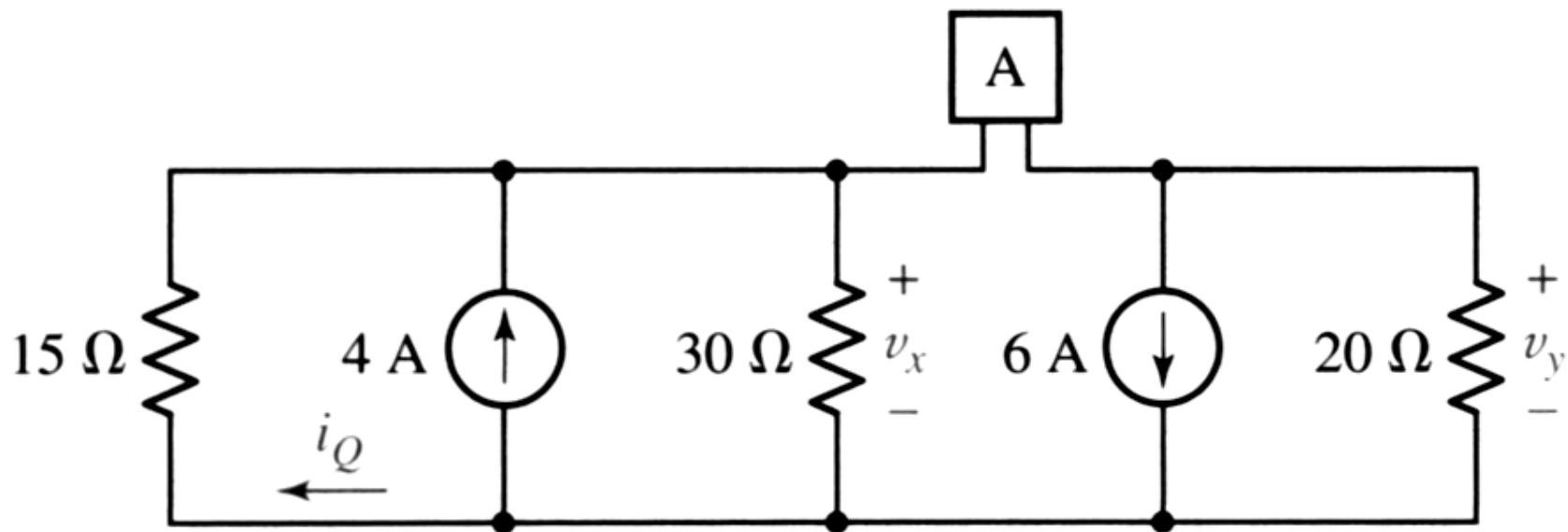
# Practice: 4.4

Use nodal analysis to find  $v_x$ , if element A is (a) a  $25\ \Omega$ ; (b) a 5-A current source, arrow pointing right; (c) a 10-V voltage source, positive terminal on the right; (d) a short circuit



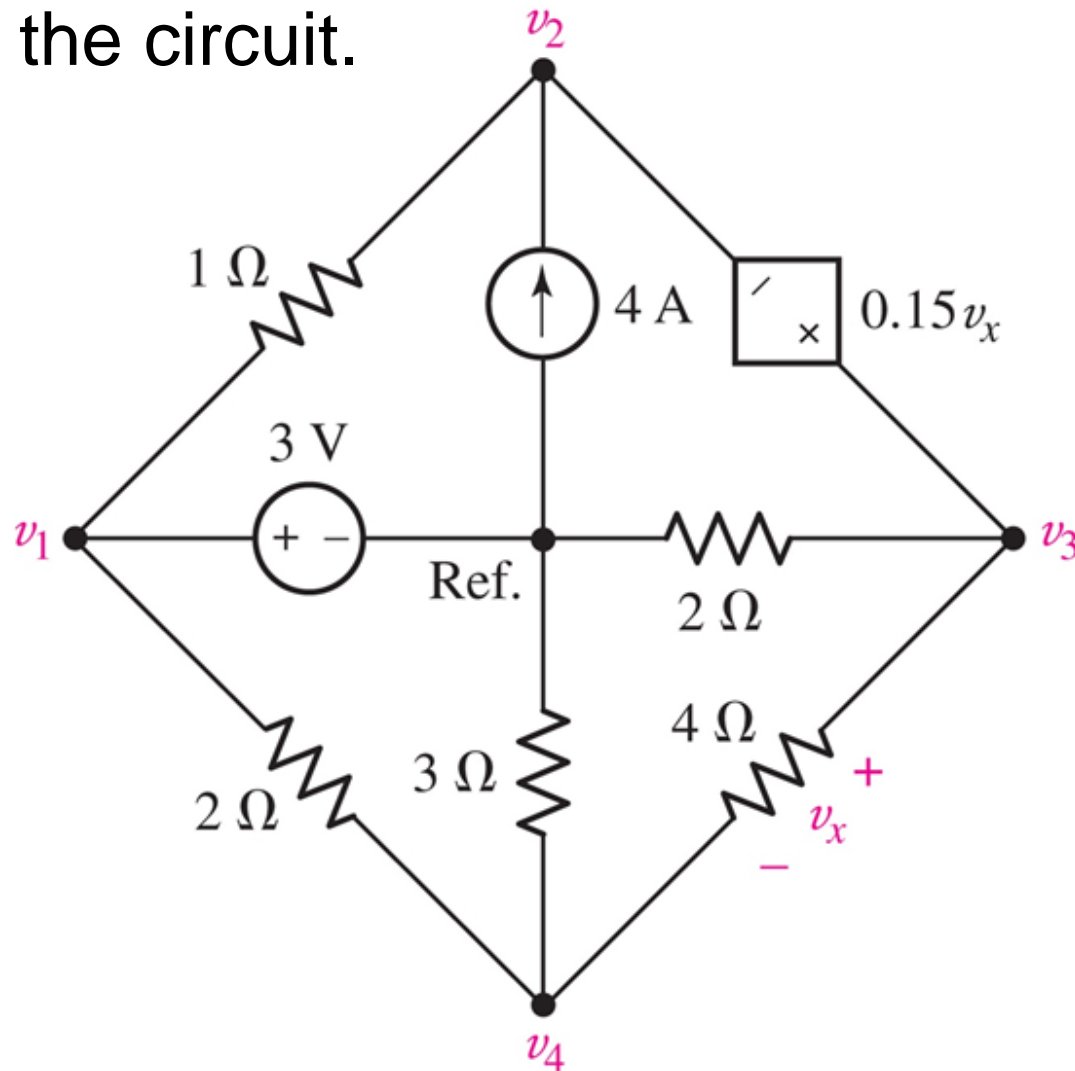
# Practice:

Use nodal analysis to determine the nodal voltage in the circuit.


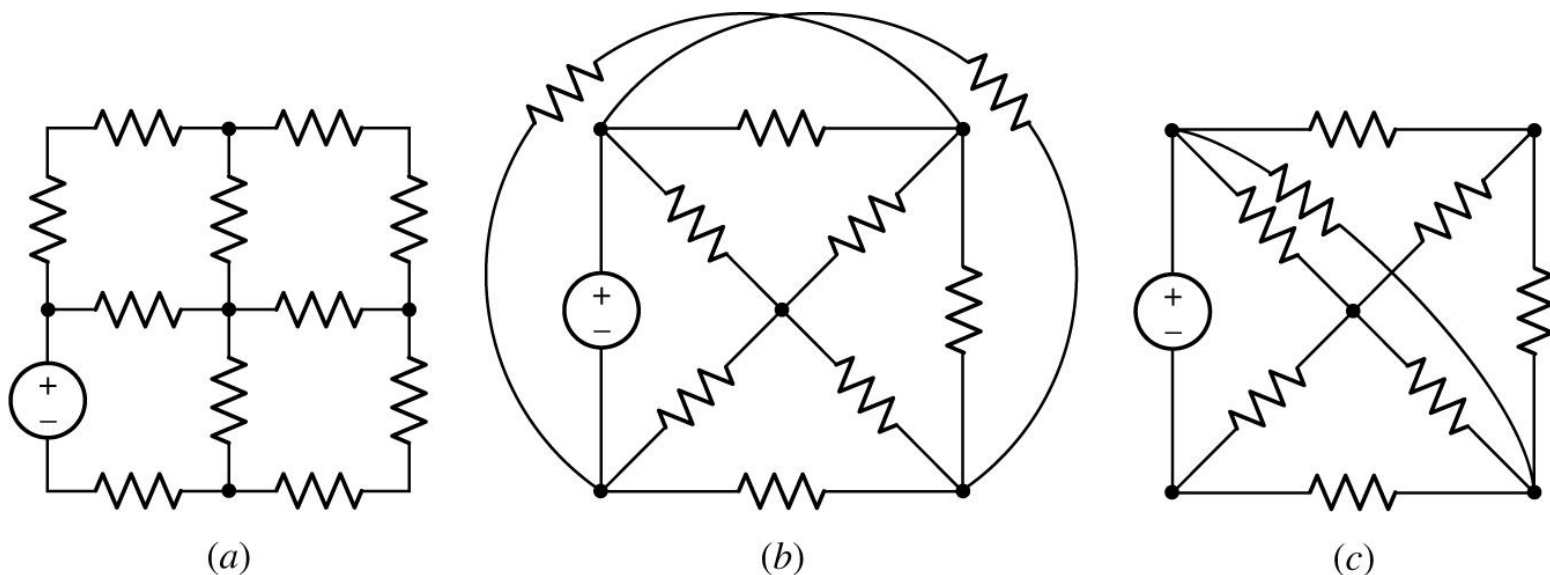
# Mesh Analysis:


Mesh analysis is applicable only to those networks which are planar.



**Examples of planar and nonplanar networks**

**Mesh is a loop that doesn't contain any other loops.**

# Path, Closed path, and Loop:

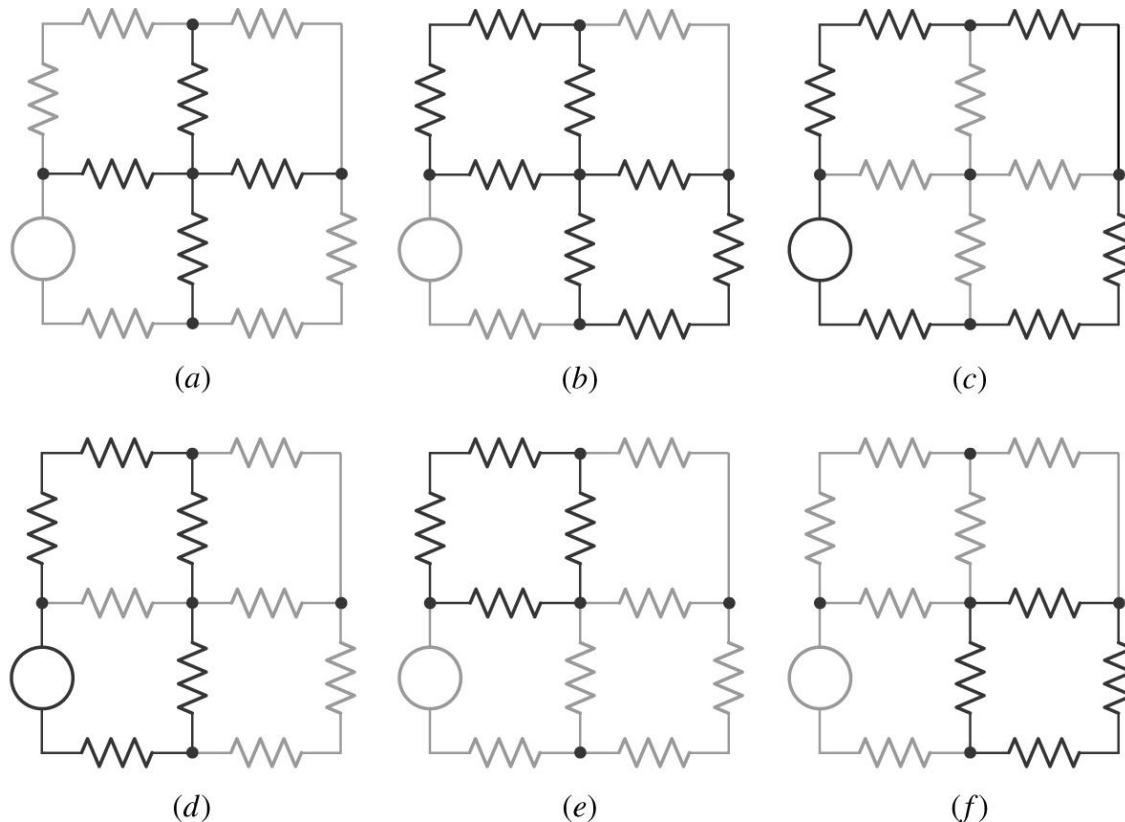


**(a)** The set of branches identified by the heavy lines is neither a path nor a loop. **(b)** The set of branches here is not a path, since it can be traversed only by passing through the central node twice. **(c)** This path is a loop but not a mesh, since it encloses other loops. **(d)** This path is also a loop but not a mesh. **(e, f)** Each of these paths is both a loop and a mesh.


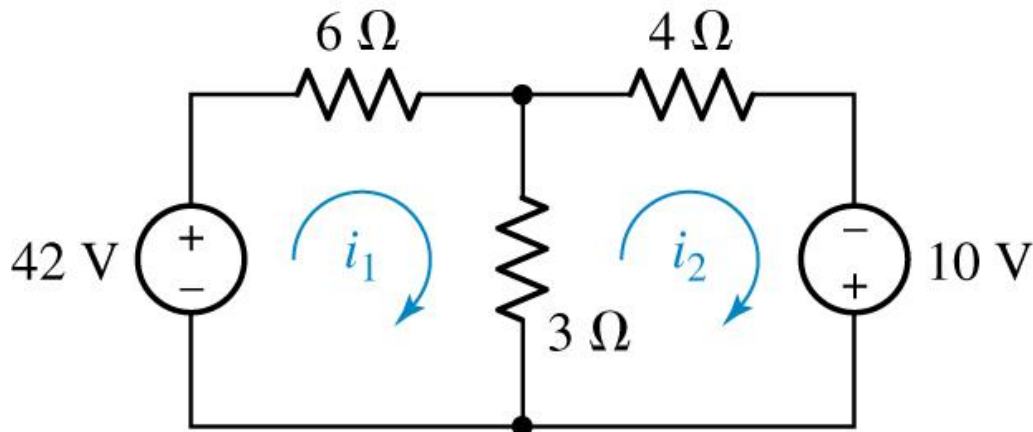
# Example: 4.6

Determine the two mesh currents,  $i_1$  and  $i_2$ , in the circuit below.



For the left-hand mesh,

$$-42 + 6 i_1 + 3 (i_1 - i_2) = 0$$

For the right-hand mesh,


$$3 (i_2 - i_1) + 4 i_2 - 10 = 0$$

Solving, we find that  $i_1 = 6$  A and  $i_2 = 4$  A.

(The current flowing downward through the 3-Ω resistor is therefore  $i_1 - i_2 = 2$  A.)


# Practice: 4.5

Determine  $i_1$  and  $i_2$

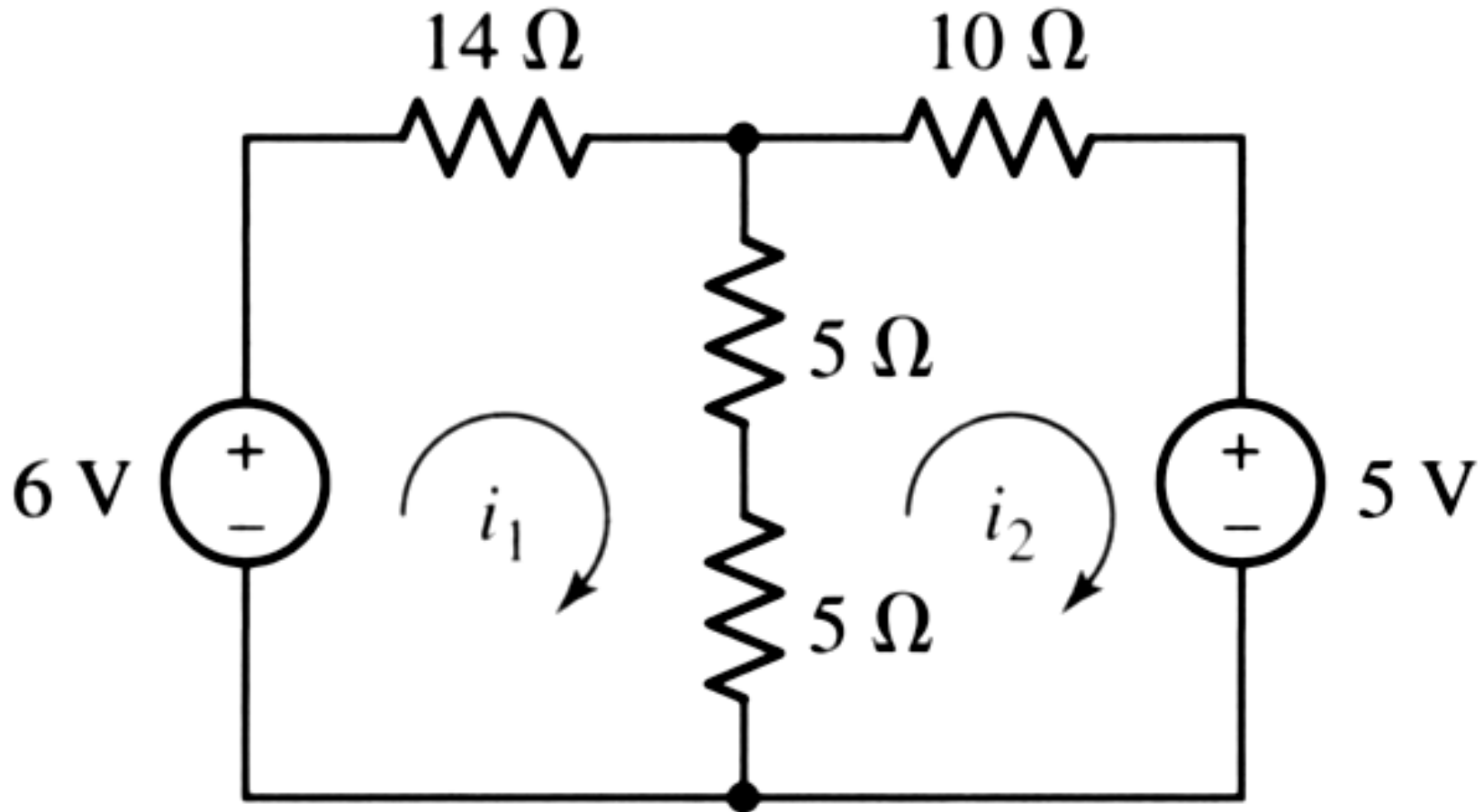

# Practice: 4.5

---

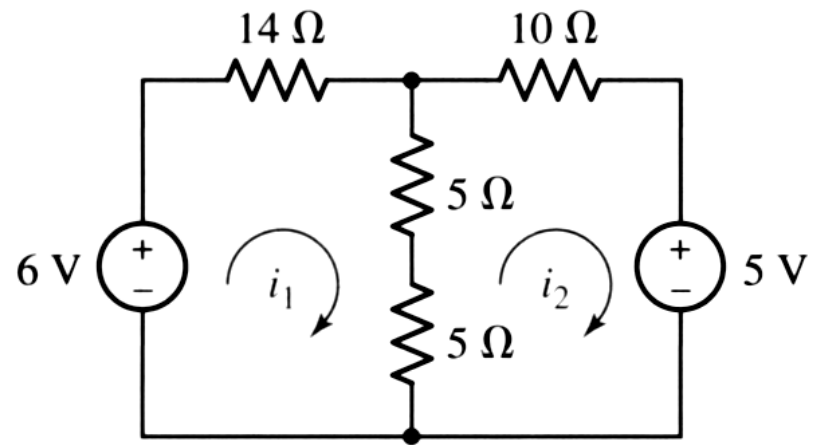


Mesh 1: 
$$-6 + 14i_1 + 10(i_1 - i_2) = 0$$

Mesh 2: 
$$10(i_2 - i_1) + 10i_2 + 5 = 0$$


# Example: 4.7

**determine the three mesh currents**

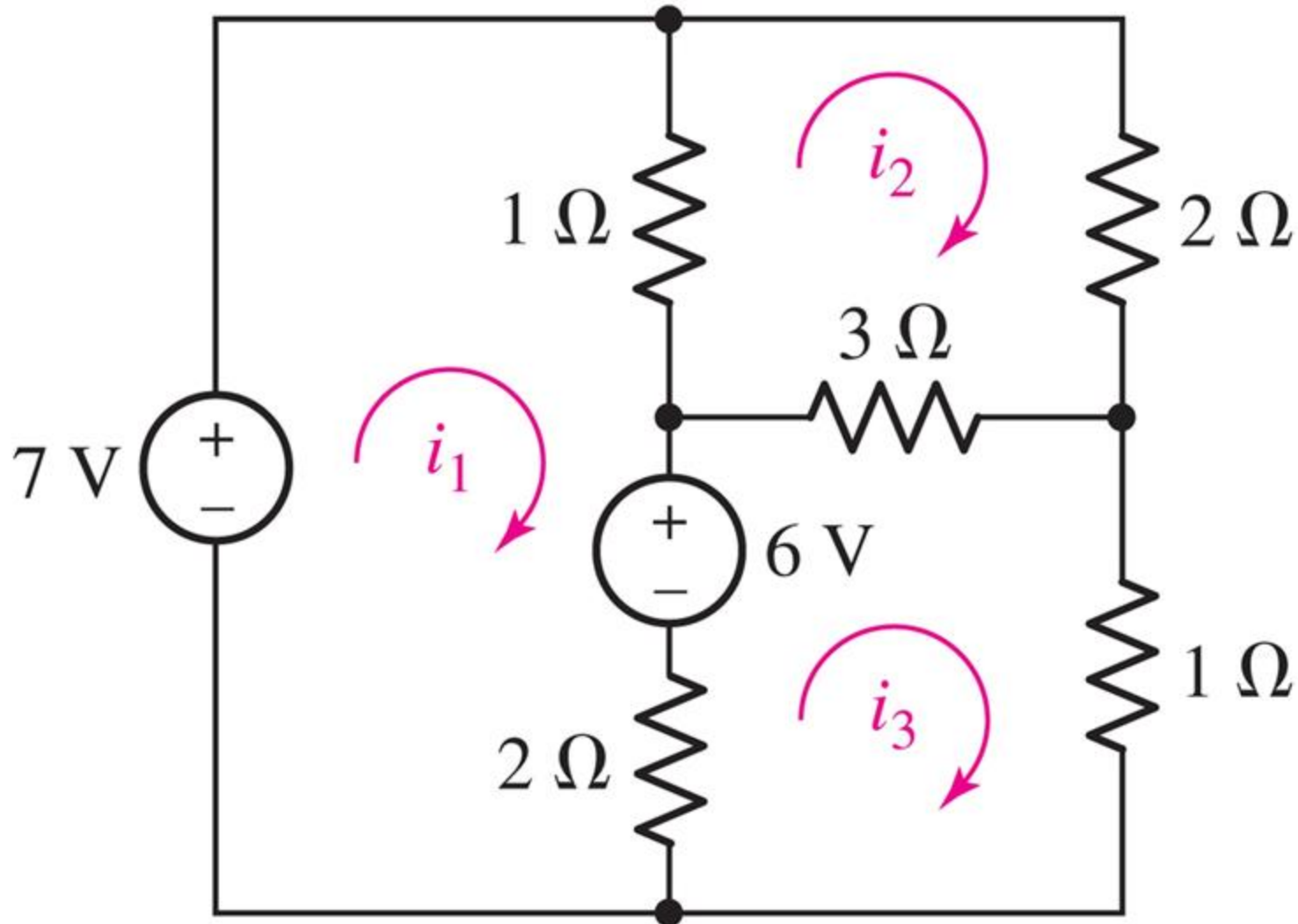

# Example:

**determine the three mesh currents**

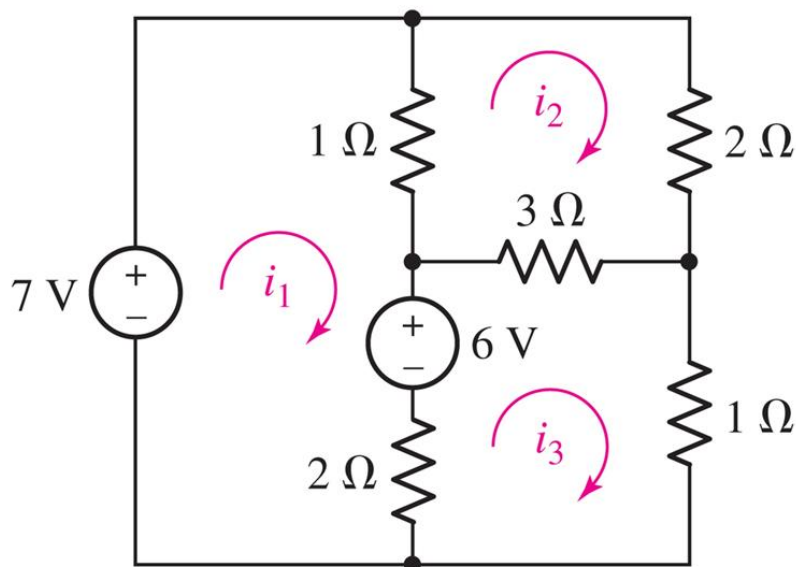

Mesh  $i_1$ :

$$-7 + 1(i_1 - i_2) + 6 + 2(i_1 - i_3) = 0$$

Mesh  $i_2$ :


$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

Mesh  $i_3$ :


$$2(i_3 - i_1) - 6 + 3(i_3 - i_2) + 1i_3 = 0$$

# Practice: 4.6

Determine  $i_1$  and  $i_2$

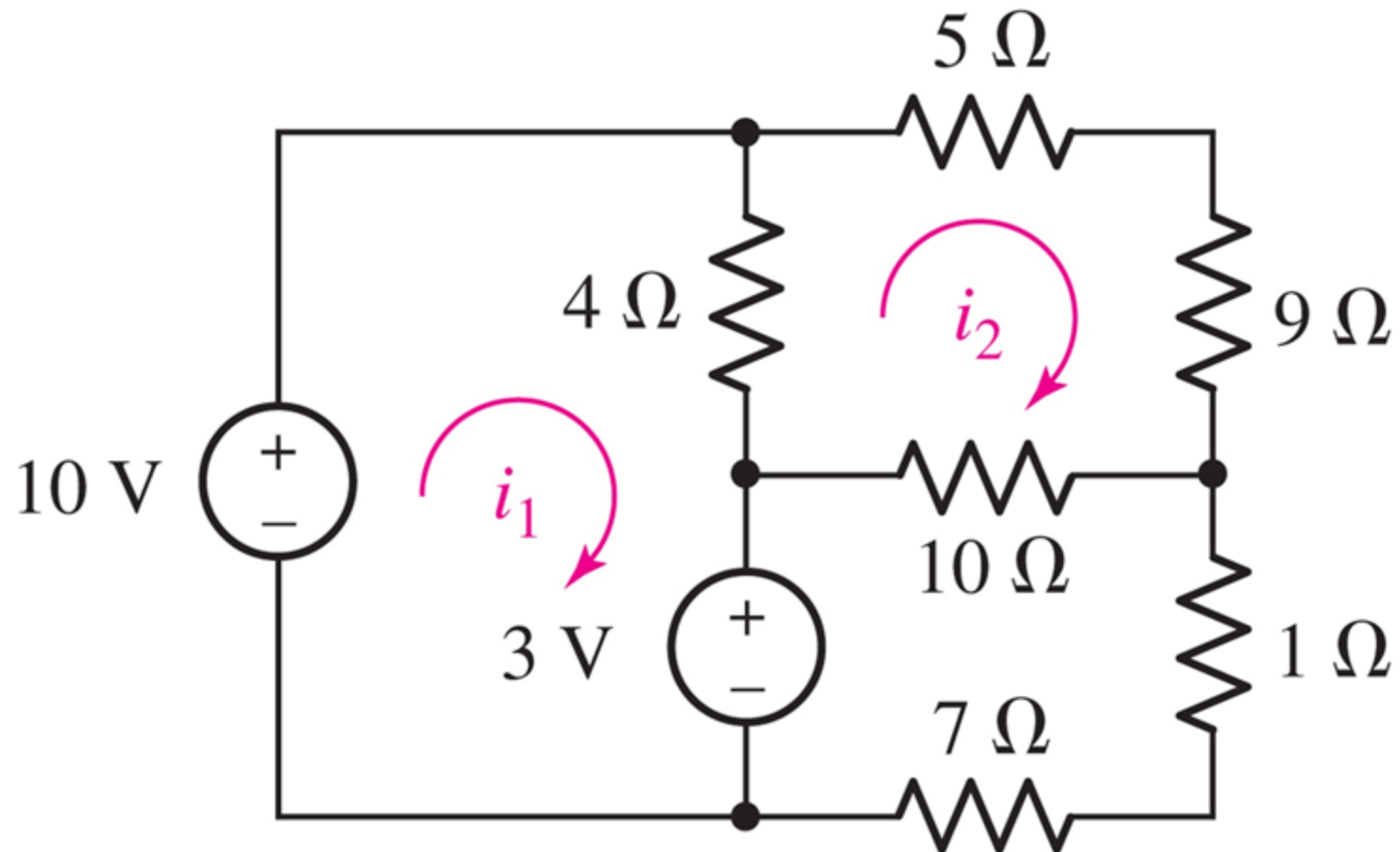

# Practice: 4.6

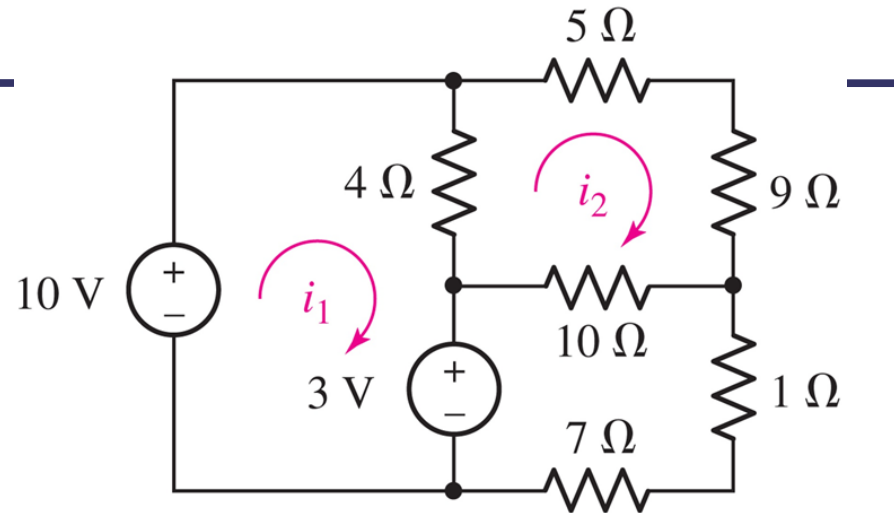


Mesh 1: 
$$-10 + 4(i_1 - i_2) + 3 = 0$$

Mesh 2: 
$$4(i_2 - i_1) + 5i_2 + 9i_2 + 10(i_2 - i_3) = 0$$

Mesh 3: 
$$-3 + 10(i_3 - i_2) + 8i_3 = 0$$
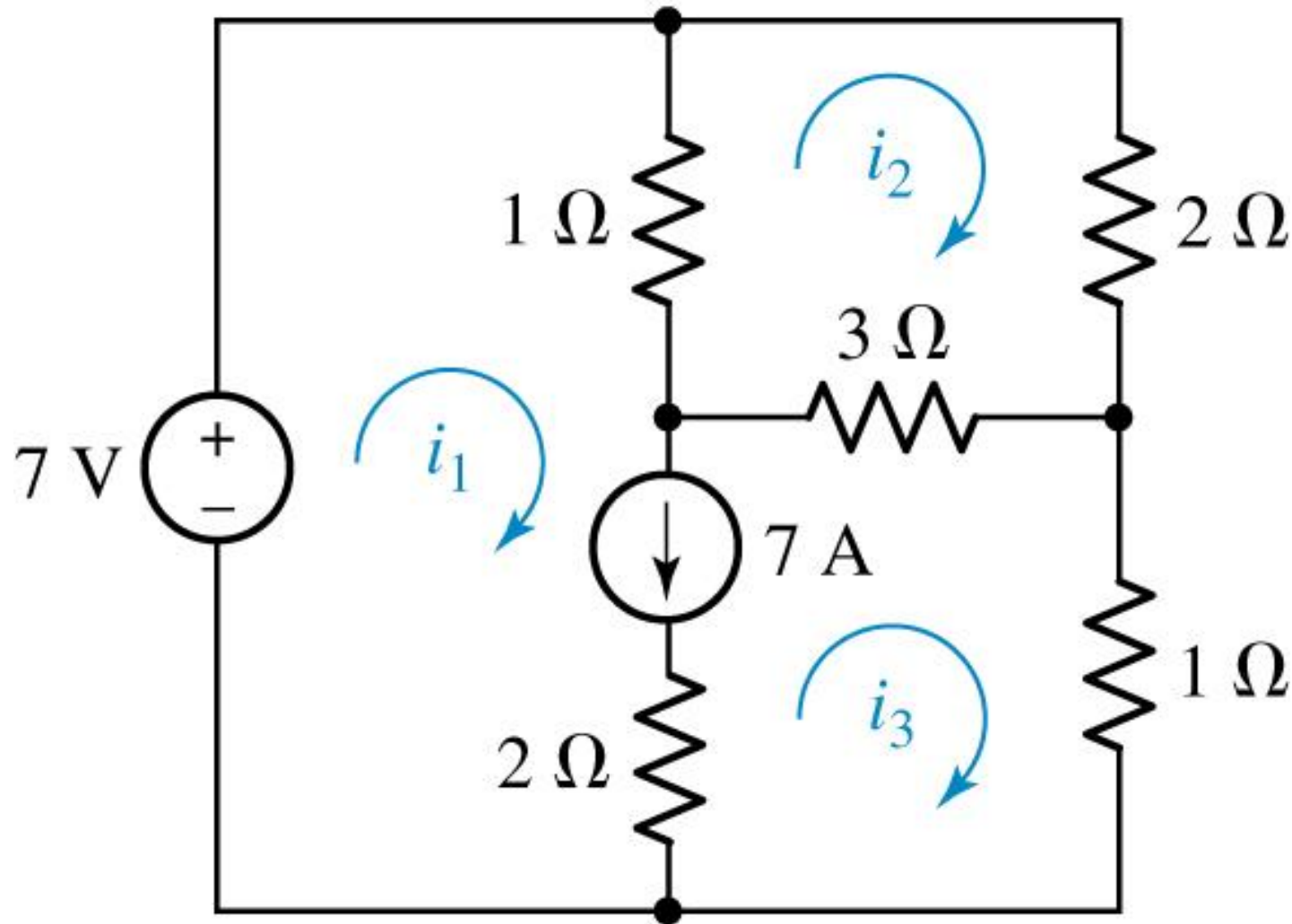
# The Supermesh:

Find the three mesh currents in the circuit below.





# The Supermesh:

Find the three mesh currents in the circuit below.

Apply KVL:

Mesh  $i_1$ :


$$-7 + 1(i_1 - i_2) + v + 2(i_1 - i_3) = 0$$

Mesh  $i_2$ :


$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

Mesh  $i_3$ :
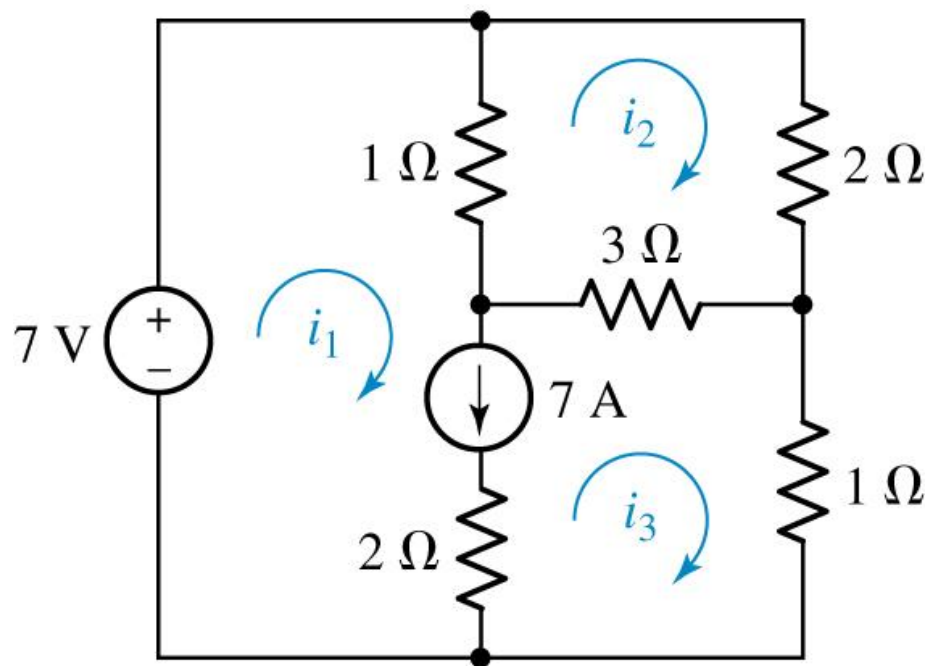
$$2(i_3 - i_1) - v + 3(i_3 - i_2) + 1i_3 = 0$$



# The Supermesh:

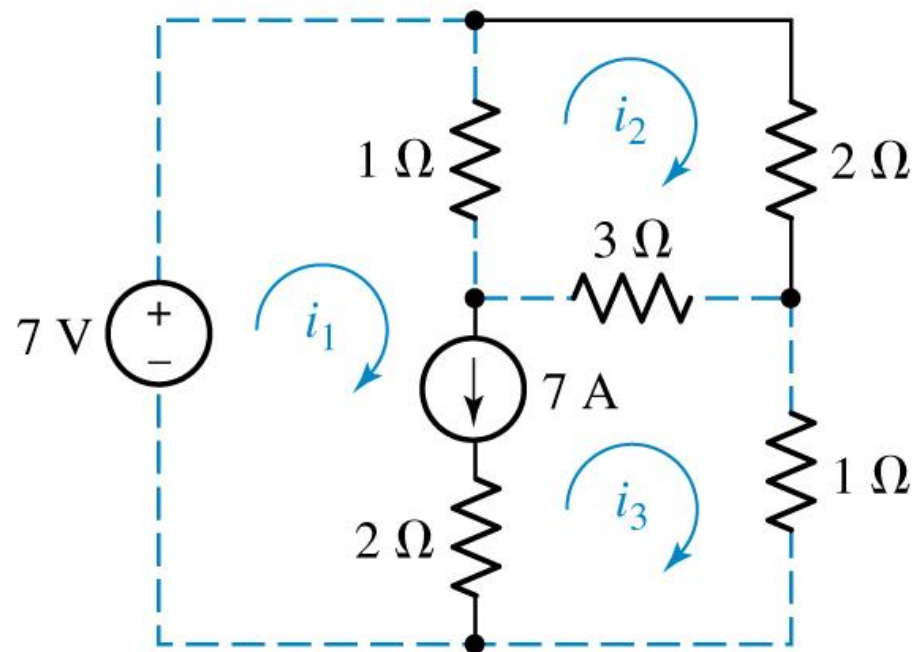

A supermesh ( $i_1, i_3$ ):


$$-7 + 1(i_1 - i_2) + 3(i_3 - i_2) + 1i_3 = 0$$

Mesh:  $i_2$


$$1(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$
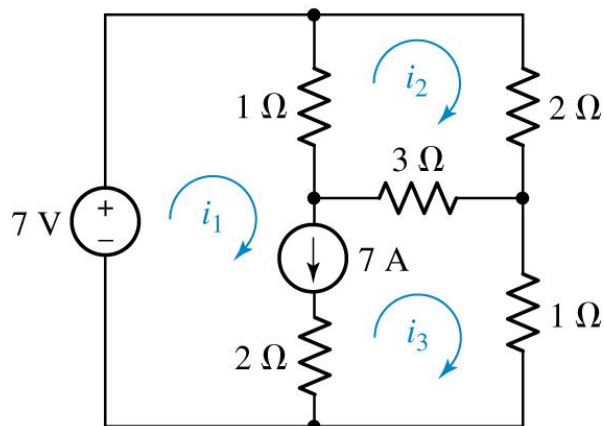
# The Supermesh:

Find the three mesh currents in the circuit below.



(a)

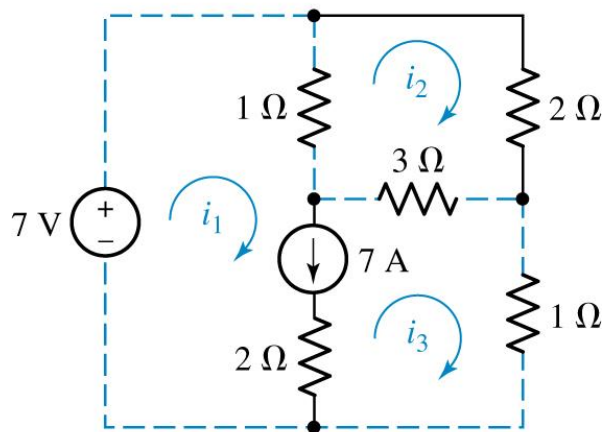

(b)

Creating a “supermesh” from meshes 1 and 3:

$$-7 + 1 (i_1 - i_2) + 3 (i_3 - i_2) + 1 i_3 = 0 \quad [1]$$

Around mesh 2:

$$1 (i_2 - i_1) + 2 i_2 + 3 (i_2 - i_3) = 0 \quad [2]$$

Finally, we relate the currents in meshes 1 and 3:

$$i_1 - i_3 = 7 \quad [3]$$

Rearranging,

$$i_1 - 4 i_2 + 4 i_3 = 7 \quad [1]$$

$$-i_1 + 6 i_2 - 3 i_3 = 0 \quad [2]$$


$$i_1 - i_3 = 7 \quad [3]$$

Solving,

$$i_1 = 9 \text{ A}, \quad i_2 = 2.5 \text{ A}, \quad \text{and} \quad i_3 = 2 \text{ A}.$$
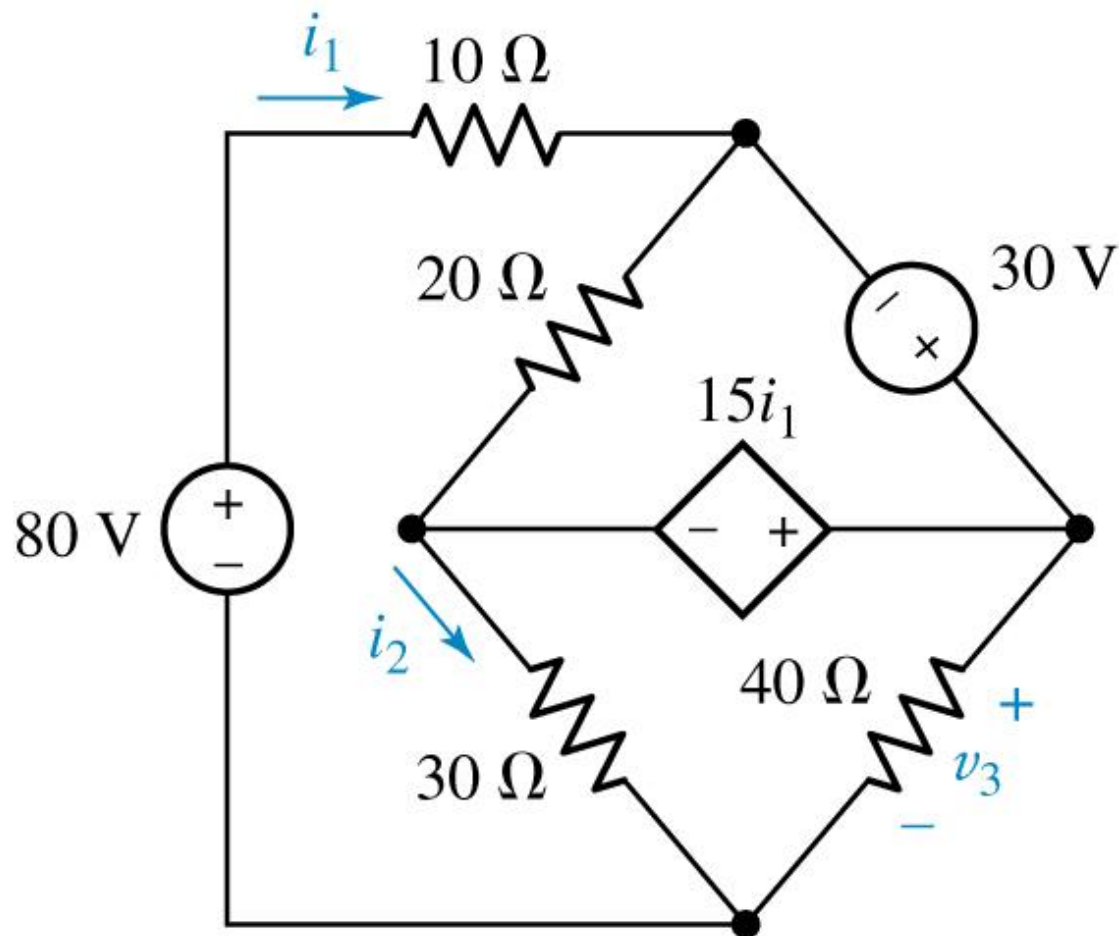
# Practice: 4.8


Find the voltage  $v_3$  in the circuit below.



# Practice: 4.8

Find the voltage  $v_3$  in the circuit below.

Mesh  $i_A$ :

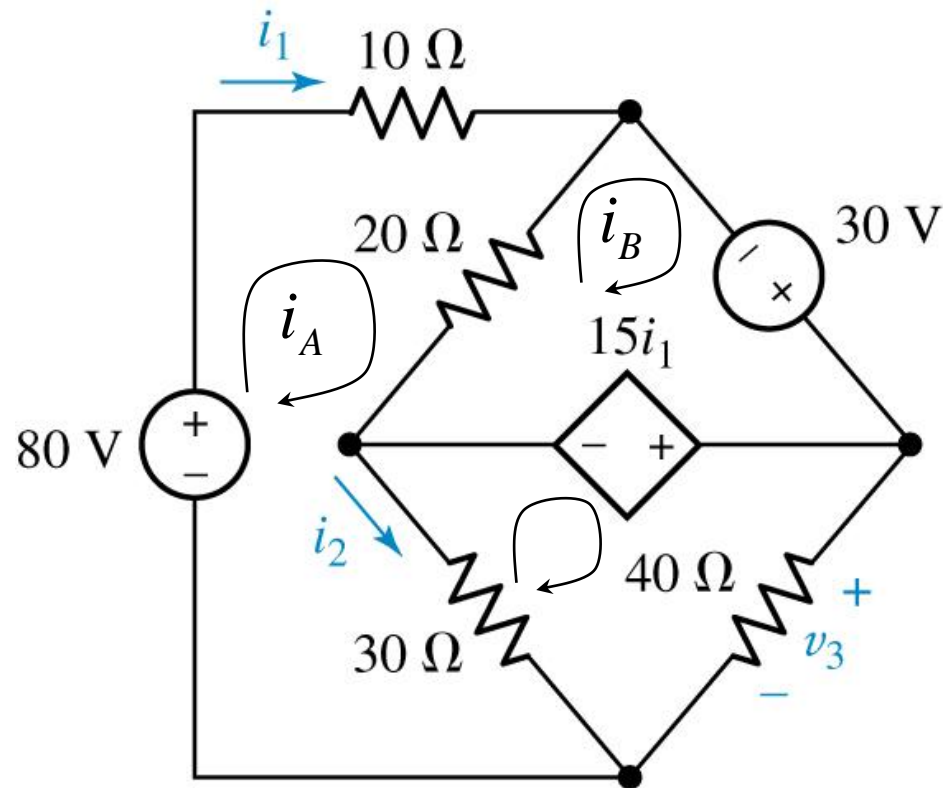

# Practice: 4.8

Find the voltage  $v_3$  in the circuit below.

Mesh  $i_A$ :

$$-80 + 10i_A + 20(i_A - i_B) + 30(i_A - i_C) = 0$$

Mesh  $i_B$ :


$$20(i_B - i_A) - 30 + 15i_1 = 0$$

$$20(i_B - i_A) - 30 + 15i_A = 0$$


Mesh  $i_C$ :

$$30(i_C - i_A) - 15i_1 + 40i_C = 0$$

$$30(i_C - i_A) - 15i_A + 40i_C = 0$$

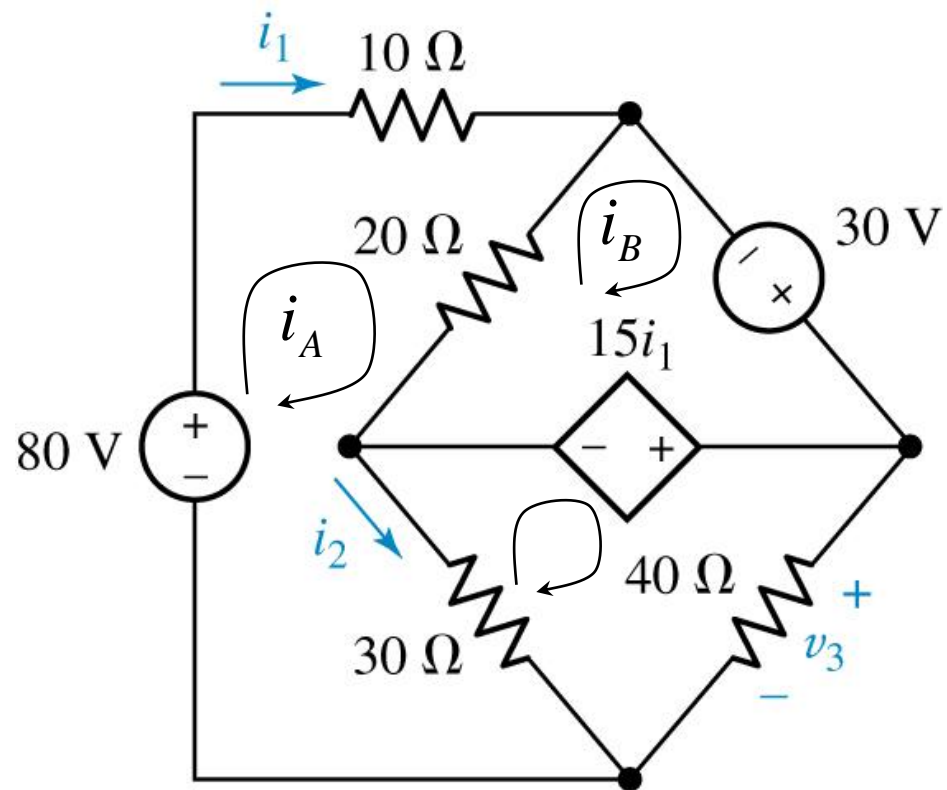

# A comparison:

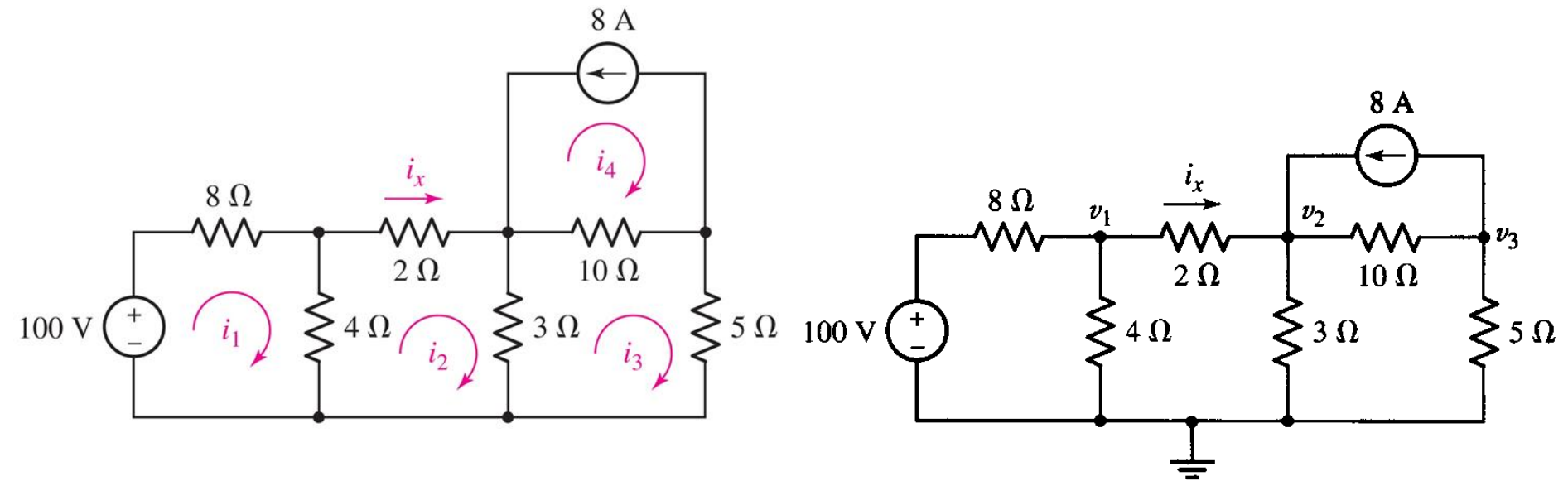

# A comparison:

Node  $v_1$  :

$$\frac{v_1 - 100}{8} + \frac{v_1}{4} + \frac{v_1 - v_2}{2} = 0$$

Node  $v_2$  :


$$\frac{v_2 - v_1}{2} + \frac{v_2}{3} + \frac{v_2 - v_3}{10} - 8 = 0$$

Node  $v_3$  :

$$8 + \frac{v_3 - v_2}{10} + \frac{v_3}{5} = 0$$


Solving;  $v_1 = 25.89$  V.,  $v_2 = 20.31$
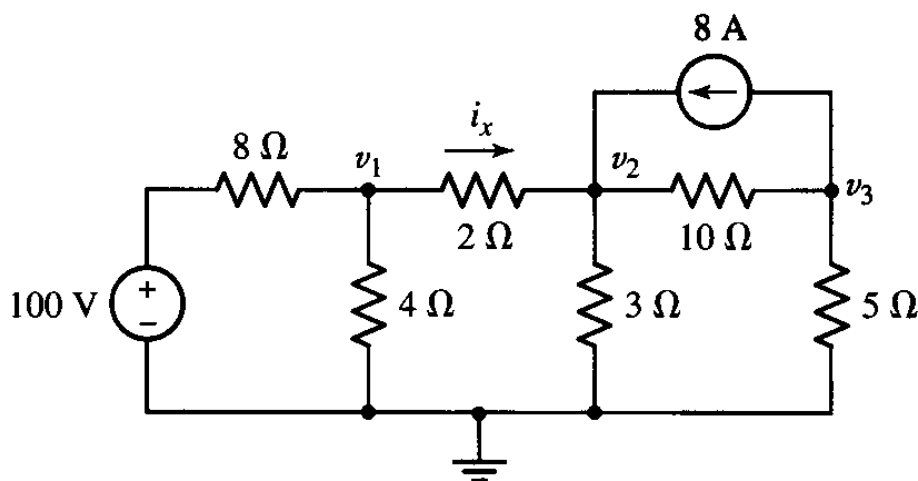
$$\therefore i_x = \frac{v_1 - v_2}{2} = 2.79 \text{ A.}$$





# A comparison:

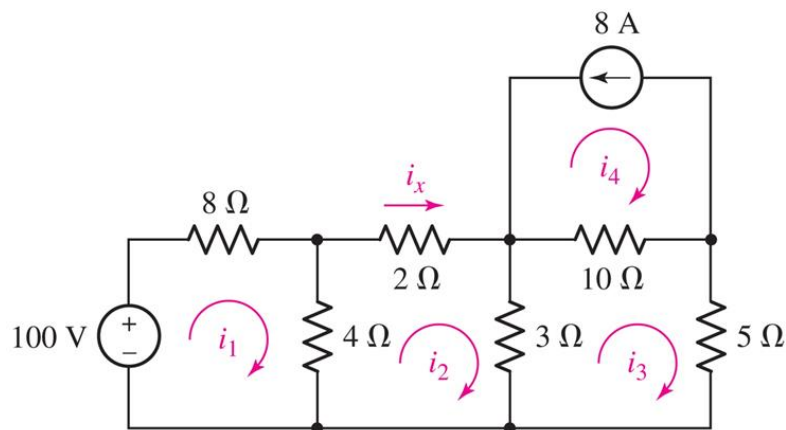

Mesh  $i_1$  :

$$-100 + 8i_1 + 4(i_1 - i_2) = 0$$

Mesh  $i_2$  :


$$4(i_2 - i_1) + 2i_2 + 3(i_2 - i_3) = 0$$

Mesh  $i_3$  :


$$3(i_3 - i_2) + 10(i_3 + 8) + 5i_3 = 0$$



# A comparison:

---


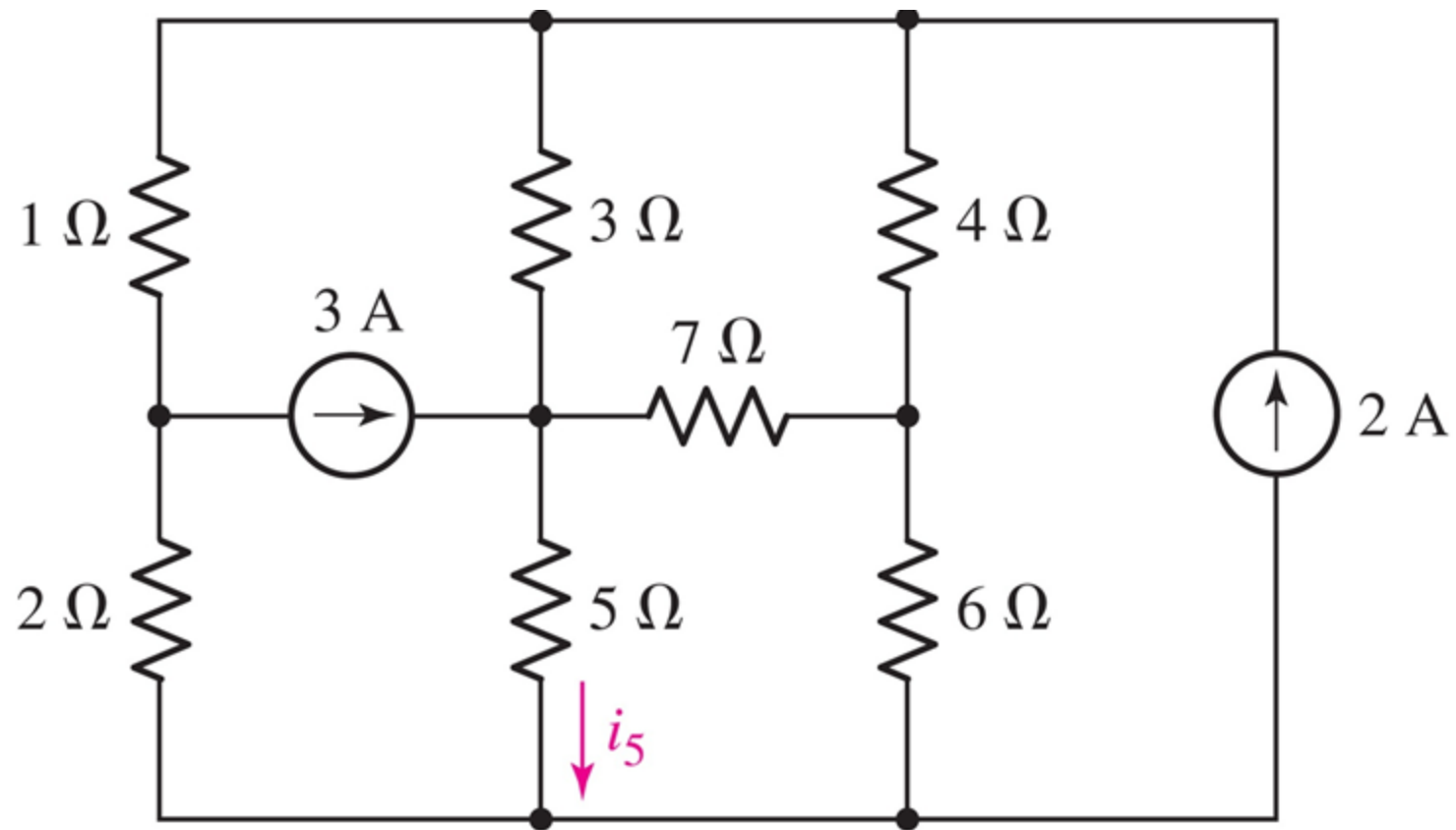


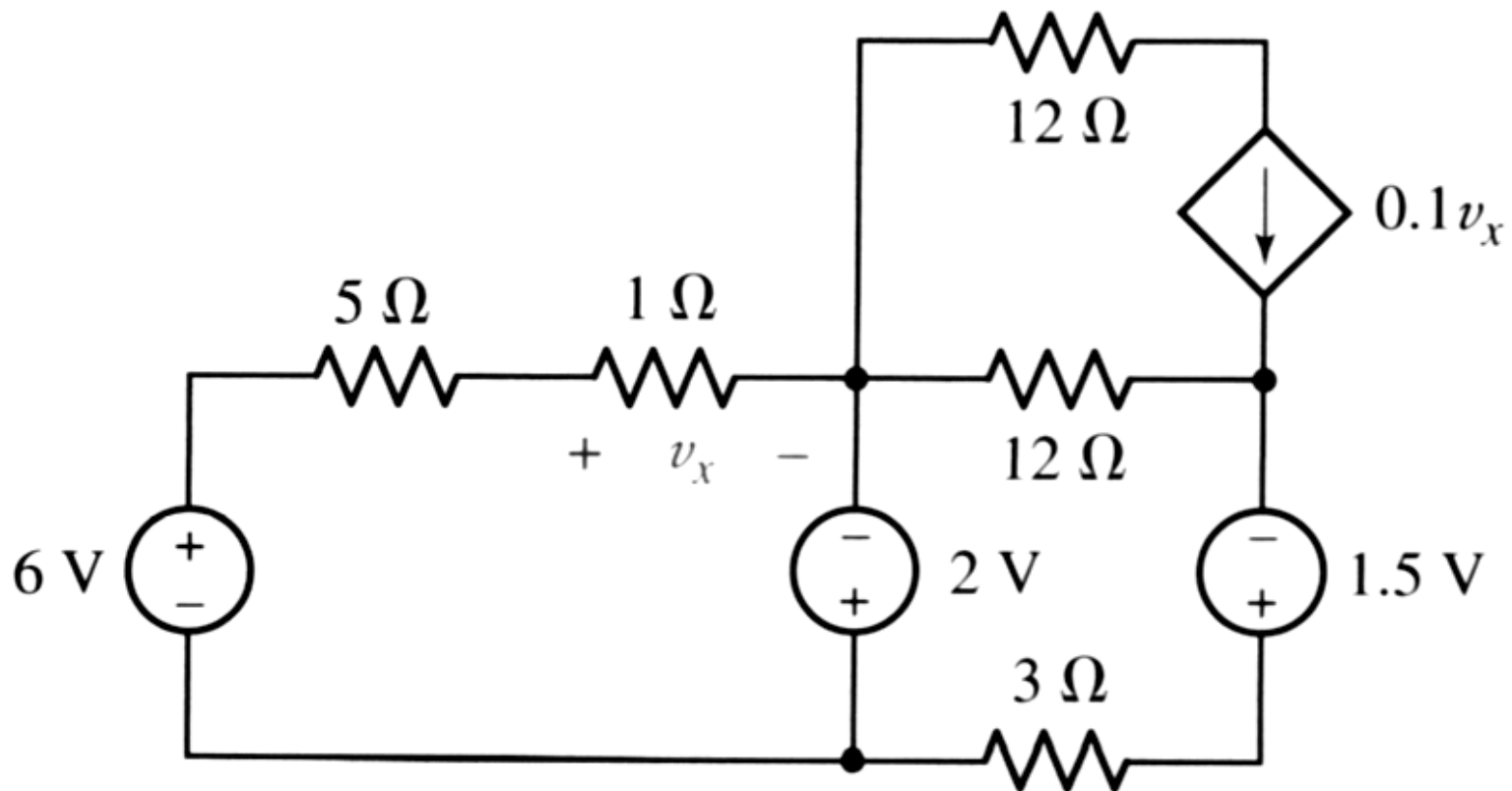Ch4-26 p.94 Determine each mesh current in the circuit



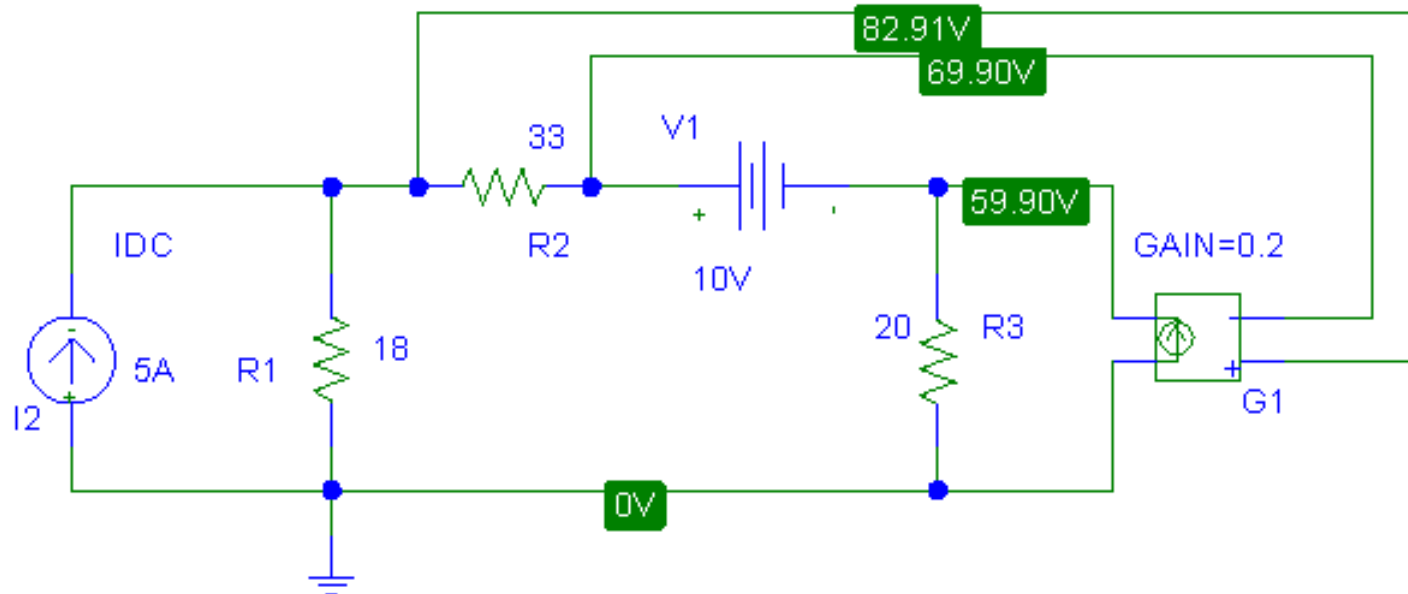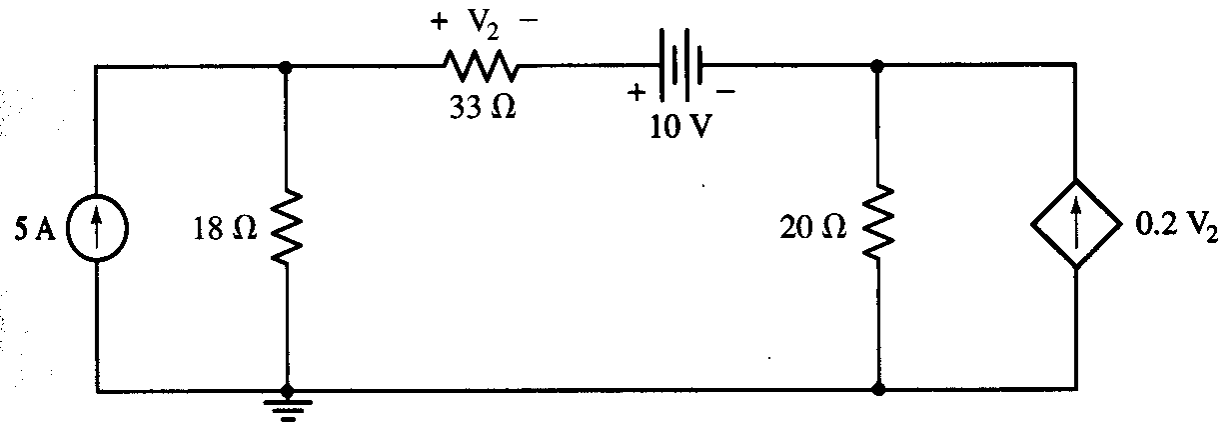


# Computer-Aided:

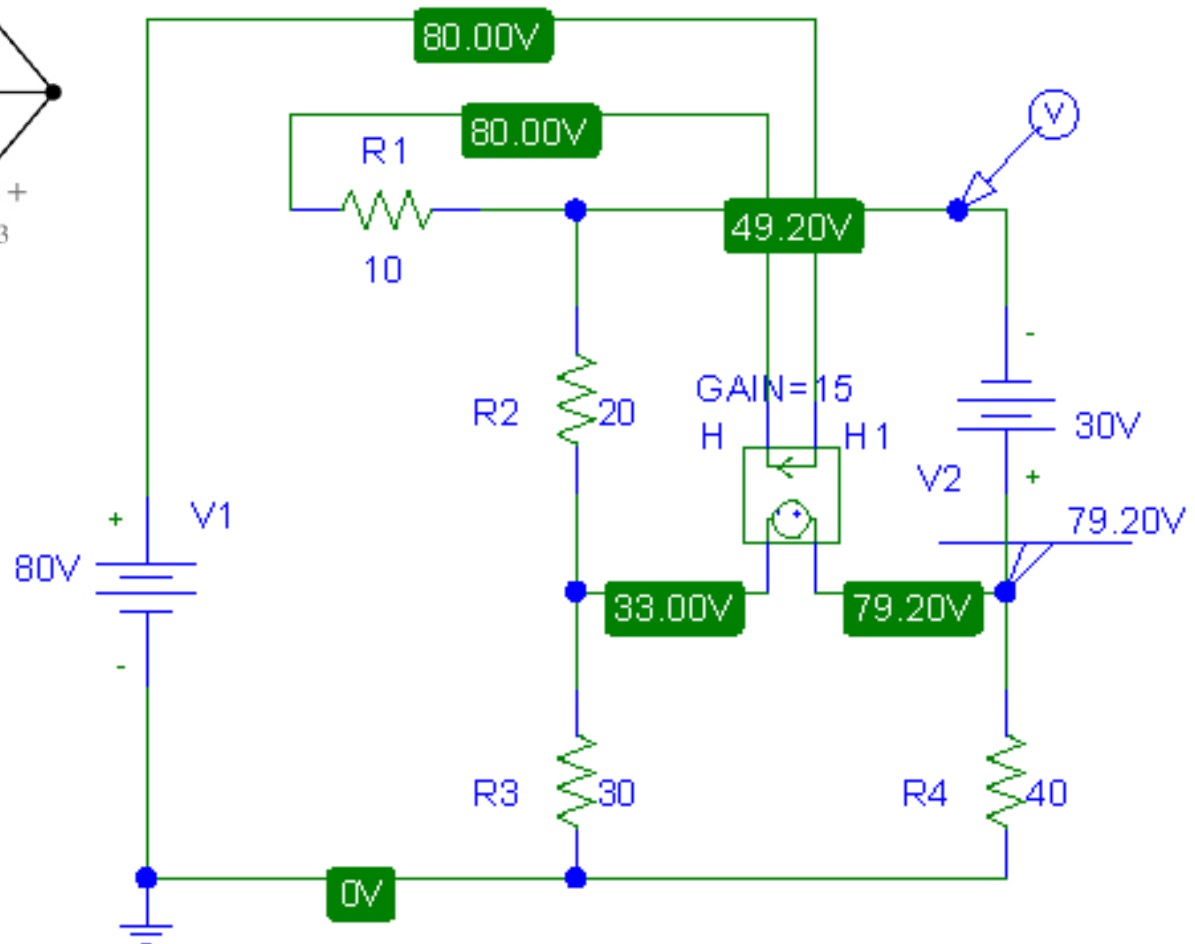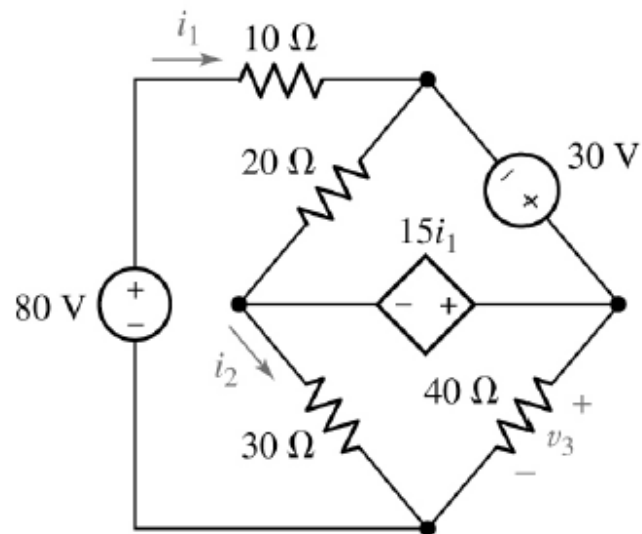
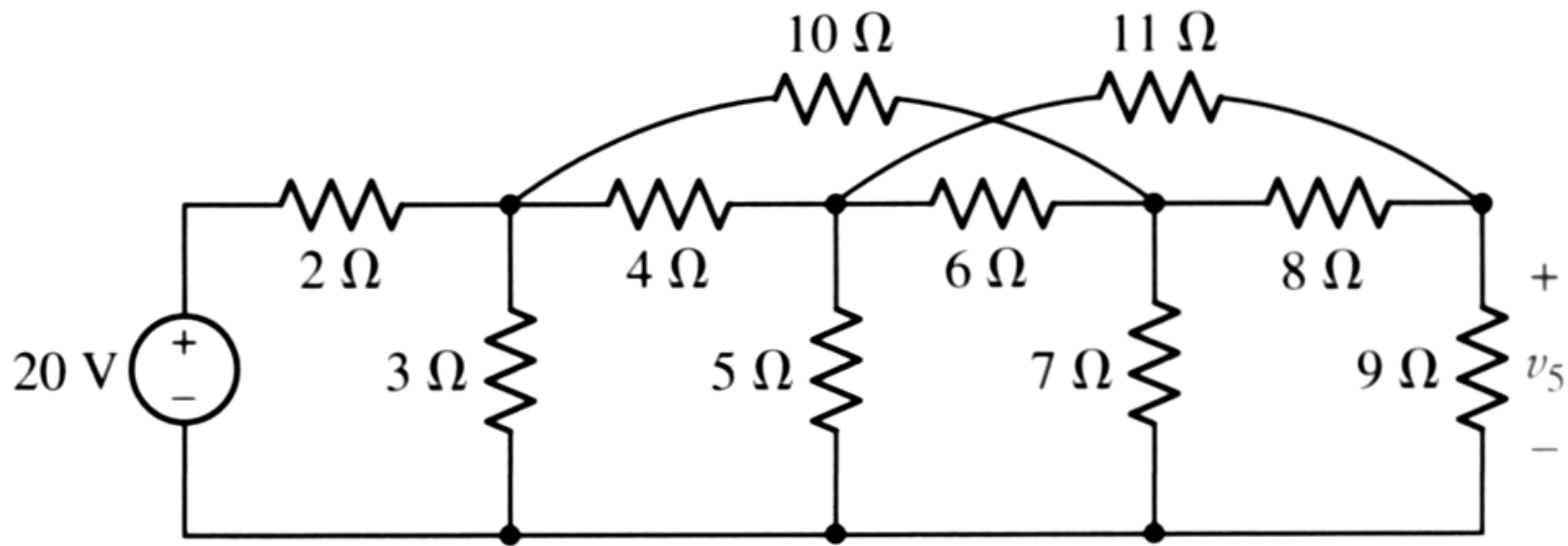
# Example:

**Ch4.58 p.100** Write an appropriate input deck for SPICE to find  $v_5$  in the circuit. Submit a printout of the output file, with the solution highlight



# Homework:

---

**W.H. Hayt, Jr., J.E. Kemmerly, S.M. Durbin, Engineering Circuit Analysis, Sixth Edition.**

**Copyright ©2002 McGraw-Hill. All rights reserved.**