

# Sources of Error



EIE 240 Electrical and Electronic Measurement

Class 3, December 22, 2011

werapon.chi@kmutt.ac.th

## Errors in Electrical Measurements

- Systematic error  $\Rightarrow$  every times you measure e.g. loading or insertion of the measurement instrument
- Meter error  $\Rightarrow$  scaling (inaccurate marking), pointer bending, friction
- Random error  $\Rightarrow$  temperature effect, noises (unwanted signals)
- Reading error  $\Rightarrow$  parallax

## Background


- Electric charge,  $e^- = 1.6 \times 10^{-19}$  Coulombs
- Current,  $I = dq/dt$  C/sec = Amps
- Voltage, the difference in electrical potential between two points (Joules/Coulomb)
- Power,  $P = IV$  Watts
- Energy,  $E = Pt$  Units (kW·hr)
- Ohm's Law,  $V = IR$

3

## Background (Cont'd)


- Kirchhoff's Current Law (KCL)

$$I_1 - I_2 - I_3 = 0$$

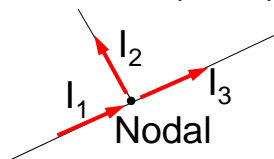

- Kirchhoff's Voltage Law (KVL)


$$-V_1 + I_1 R_1 + V_2 + I_2 R_2 = 0$$

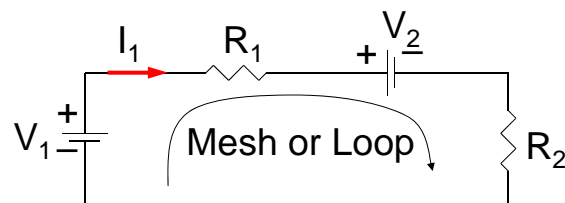


4

## Background (Cont'd)

- Thévenin's Theorem

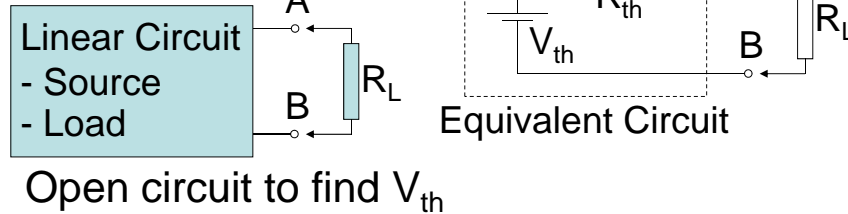

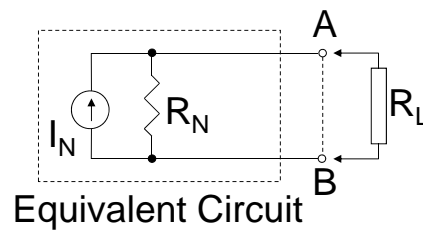- Norton's Theorem  
Short circuit to find  $I_N$




5


## Background (Cont'd)

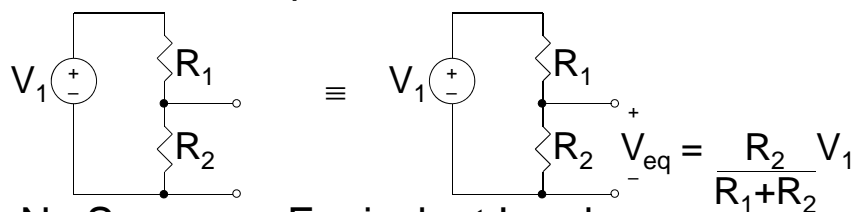Example

No Load  $\Rightarrow$  Equivalent Source




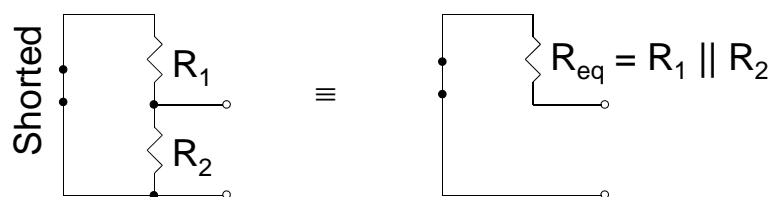
No Source  $\Rightarrow$  Equivalent Load



6
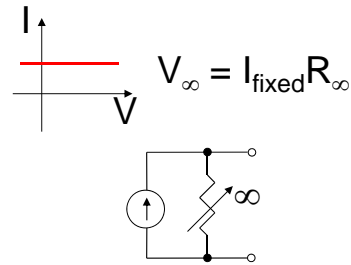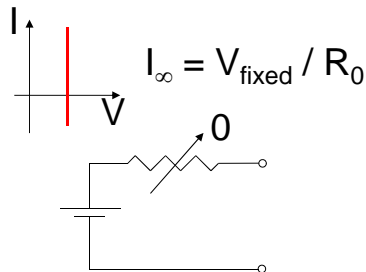
## Background (Cont'd)

- Ideal Voltage Source Vs. Ideal Current Source



- Superposition Theorem (for linear resistive network containing several sources)


Voltage source  $\text{---} \oplus \text{---} \Rightarrow$  Short Circuit  $\text{---} 0 \text{ V} \text{---}$

Current source  $\text{---} \rightarrow \text{---} \Rightarrow$  Open Circuit  $\text{---} 0 \text{ A} \text{---}$

Vector summation of the individual voltage or current caused by each separate source 7

## Background (Cont'd)


### Example

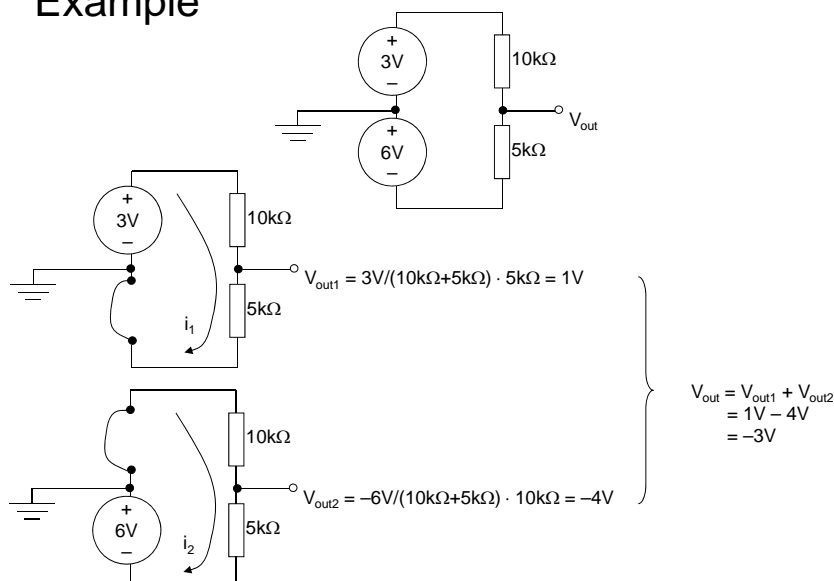

8

## Background (Cont'd)

- The Maximum Power Transfer Theorem

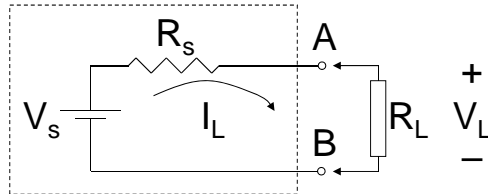

If  $V_s$  and  $R_s$  are fixed, when  $I_L \uparrow$  then  $V_L \downarrow$

Maximum power is at  $R_L = R_s$

Therefore  $V_L = V_s / 2$  and  $I_L = V_s / 2R_L$


$$P_L = (I_L)^2 R_L = (V_s / 2R_L)^2 R_L = V_s^2 / 4R_L$$

9


## Ammeter Loading

For current measurement, open circuit to put an ammeter.

DC Circuit

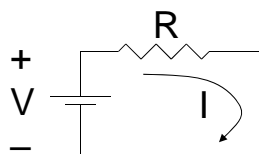

$$I = V/R$$

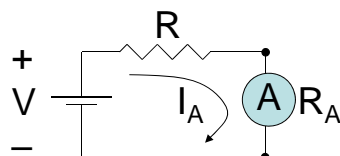

$$I_A = V/(R+R_A)$$

10

## Ammeter Loading (Cont'd)

$$\begin{aligned}\text{Loading error, } I_A - I &= V/(R+R_A) - V/R \\ &= \frac{VR - V(R+R_A)}{R(R+R_A)} \\ &= \frac{-VR_A}{R(R+R_A)}\end{aligned}$$


$$\begin{aligned}\% \text{ Loading Error} &= (I_A - I)/I \times 100\% \\ &= \frac{-R_A}{R+R_A} \times 100\%\end{aligned}$$

It means if  $R_A \uparrow$  then error  $\uparrow$

11
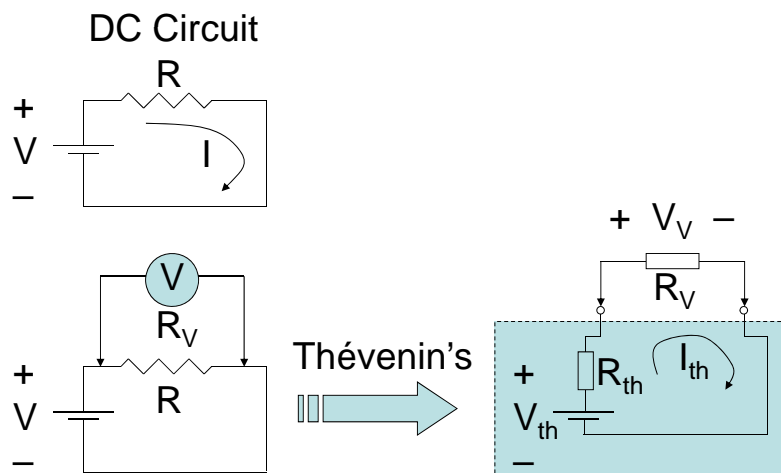
## Voltmeter Loading

For voltage measurement, voltmeter is placed in parallel with the circuit element.



12

## Voltmeter Loading (Cont'd)

$$I_{th} = V_{th} / (R_{th} + R_V)$$

$$V_V = I_{th} R_V = V_{th} R_V / (R_{th} + R_V)$$

$$\text{Error} = V_V - V_{th}, \quad V_{th} = V \quad (\text{no load})$$

$$= \left( \frac{R_V}{R_{th} + R_V} - 1 \right) V_{th}$$

$$\% \text{ Error} = (V_V - V_{th}) / V_{th} \times 100\%$$


$$= \frac{-R_{th}}{R_{th} + R_V} \times 100\%$$

It means if  $R_V \uparrow$  then error  $\downarrow$

13

## Ohmmeter Loading

Using a circuit within the instrument


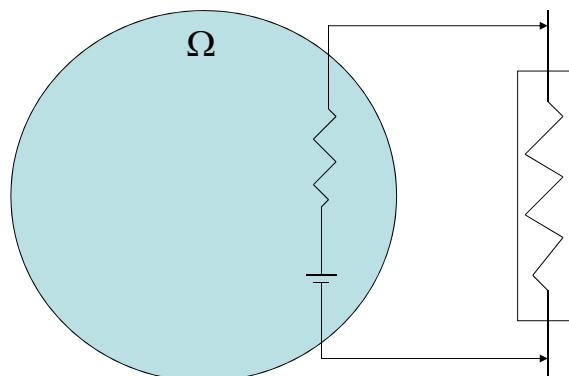


14

# Loading for a Potentiometer

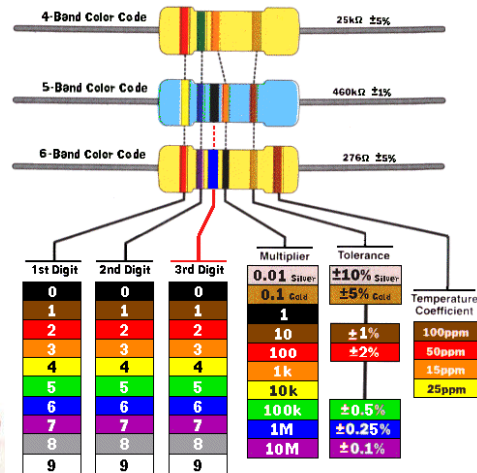
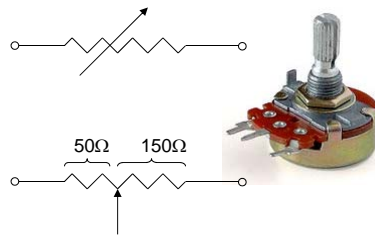
## Resistor

- Fixed
- Adjustable rheostat and potentiometer




15

## Loading of a Potentiometer (Cont'd)

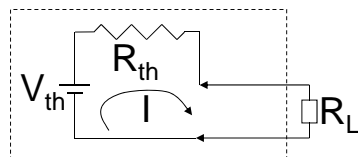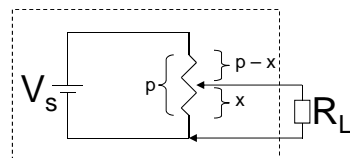

Thévenin's

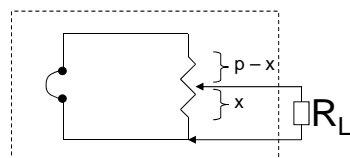

Superposition

Voltage Divider

$$V_{th} = (x/p) V_s$$

$$\frac{1}{R_{th}} = \frac{1}{(x/p)R_p} + \frac{1}{((p-x)/p)R_p}$$

$$R_{th} = (x/p)R_p(1 - x/p)$$

16



## Loading of a Potentiometer (Cont'd)

$$\begin{aligned}
 V_{th} &= I (R_{th} + R_L) \\
 (x/p)V_s &= I [ (x/p)(1 - x/p)R_p + R_L ] \\
 I &= \frac{(x/p)V_s}{(x/p)(1 - x/p)R_p + R_L} \\
 V_L = IR_L &= \frac{(x/p)V_s R_L}{(x/p)(1 - x/p)R_p + R_L} \\
 &= \frac{(x/p)V_s}{(R_p/R_L)(x/p)(1 - x/p) + 1}
 \end{aligned}$$

It means the relationship between  $V_L$  and  $x$  is nonlinear!

17

## Loading of a Potentiometer (Cont'd)

Error,

$$\begin{aligned}
 V_{th} - V_L &= (x/p)V_s \left( 1 - \frac{1}{(R_p/R_L)(x/p)(1 - x/p) + 1} \right) \\
 &= (x/p)V_s \left( \frac{(R_p/R_L)(x/p)(1 - x/p)}{(R_p/R_L)(x/p)(1 - x/p) + 1} \right)
 \end{aligned}$$

If  $R_L \gg R_p$  then  $R_p/R_L \approx 0$

Error  $\approx (x/p)V_s(R_p/R_L)(x/p)(1 - x/p)$

$\approx V_s(R_p/R_L)[(x/p)^2 - (x/p)^3]$  ,  $R_L \uparrow$  error  $\downarrow$

% Error  $\approx (R_p/R_L) [(x/p) - (x/p)^2] \times 100\%$

18

## Loading of a Potentiometer (Cont'd)

$$\text{Let } d(\text{Error})/dx = V_s(R_p/R_L)[2x/p^2 - 3x^2/p^3] = 0$$

$$\text{We get } 2x/p^2 = 3x^2/p^3$$

$$x/p = 2/3 \quad \text{for the maximum}$$

Therefore,

$$\text{the max error} = V_s(R_p/R_L)[(2/3)^2 - (2/3)^3]$$

$$\approx 0.148 V_s(R_p/R_L)$$

$$\text{and the max \% error} \approx 22.2 (R_p/R_L) \%$$

19